

## PGA309 Microcontroller Application

Tim Green

High-Performance Linear Products

### ABSTRACT

The PGA309 programmable gain amplifier can be used with an external microcontroller. In this type of application, the PGA309 becomes a programmable sensor signal conditioner block that also measures temperature. One key feature of the PGA309 in this application is the test pin, described in detail. This document then discusses two general applications of the PGA309 with an external microcontroller.


## 1 Test Pin

The PGA309 has a user-accessible test pin (*Test*, pin 9) that stops the internal state machine cycle and enables the output drive ( $V_{OUT}$ ) when it is brought high (logic '1'). This mode can be used for simple troubleshooting or initial configuration diagnostics during the system design phase. During normal (stand-alone) operation, the Test pin must be pulled or shorted to GND (logic '0'). If the Test pin is pulled high at any time, the following conditions occur:

- The PGA309 internal state machine is interrupted and reset to its initial state. Any EEPROM transactions are interrupted and the two-wire bus is released.
- The PGA309 output ( $V_{OUT}$ ) is enabled.
- All internal registers remain at their current values. If the Test pin is high when the supply becomes valid, the registers stay in the initial (POR) state, and output is enabled immediately.
- An external controller can modify any of the writeable PGA309 registers using either a one-wire or two-wire digital interface.
- The Test pin has a 25 $\mu$ A typical pull-down current source.
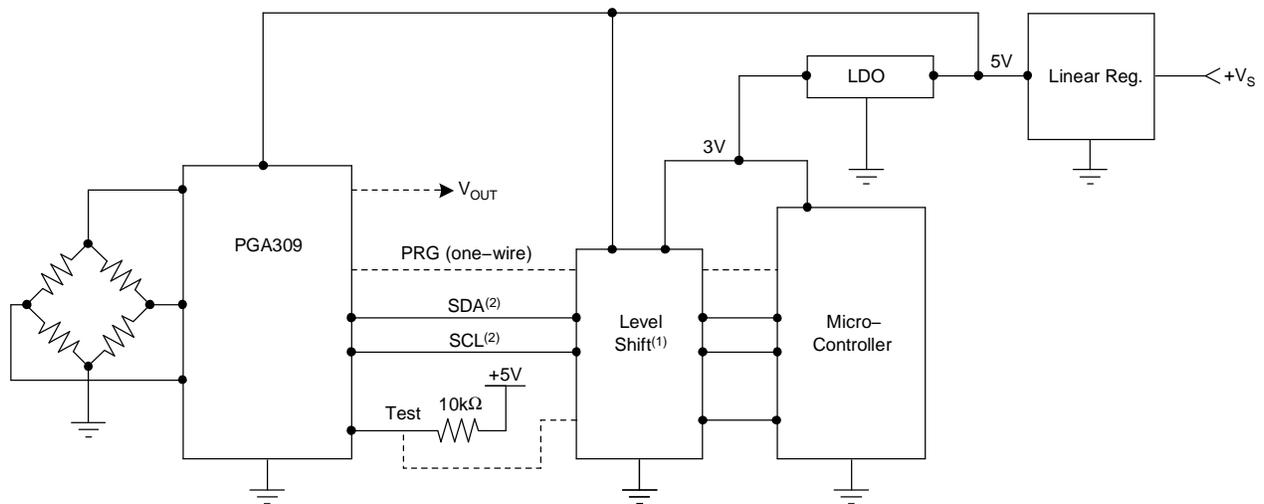
## 2 Microcontroller and PGA309 Applications


This section reviews two general applications of the PGA309 with an external microcontroller. Application 1 ([Figure 1](#)) illustrates a PGA309 that is powered from +5V and a microcontroller powered from +3V. (The +5V power supply is used in this application in order to get the best signal-to-noise ratio from the analog signal conditioning chain.) Application 2 shows both the PGA309 and the microcontroller powered from +5V; see [Figure 2](#).



Notes: (1) May be one resistor and internal port pin ESD diode.  
 (2) SDA, SCL need open drain outputs.

Also, be sure to analyze speed limitations.

**Figure 1. Application 1: PGA309 at +5V, Microcontroller at +3V**

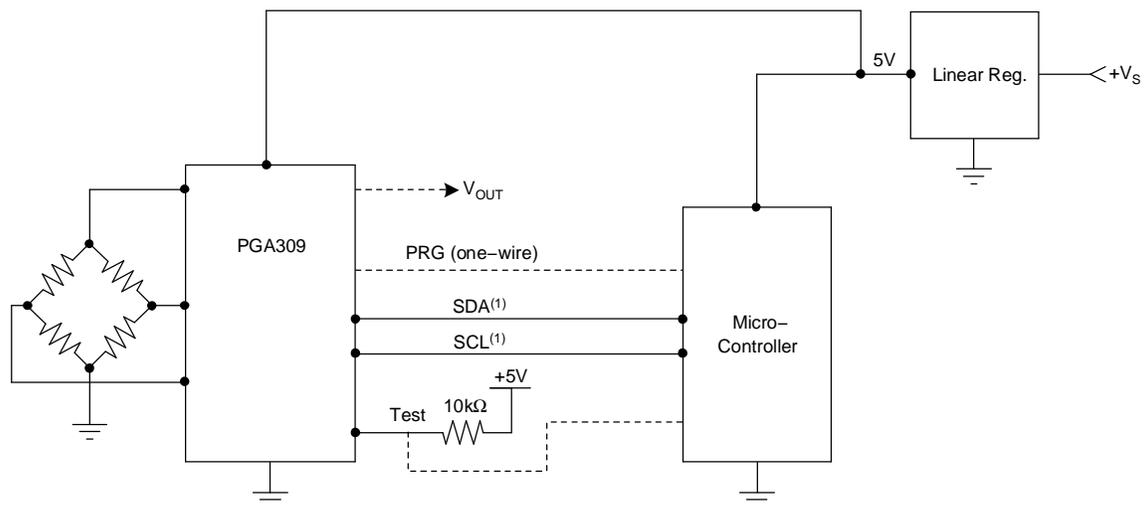

Note: (1) SDA, SCL need open drain outputs.

**Figure 2. Application 2: PGA309 and Microcontroller at +5V**

### 3 Common Design Guidelines for Application 1 and Application 2

The following design guidelines are relevant to both applications.

- If the PGA309  $V_{OUT}$  is to be used in the system, it may be optimal for the microcontroller to control the Test pin in order to keep  $V_{OUT}$  at high impedance until the microcontroller has configured the PGA309 for the desired settings.
- If the user desires to have the internal Temperature Analog-to-Digital Converter (Temp ADC) on the PGA309 read the analog  $V_{OUT}$  of the PGA309, this configuration can be accomplished by using an algorithm similar to that depicted in [Figure 3](#). The Temp ADC conversion time is denoted by ***tconv\_uc***. This time is user-selectable, depending upon the desired Temp ADC resolution. In addition, if the internal temperature sense mode is to be used on the PGA309, then one can calibrate out the Temp ADC offset before reading the PGA309  $V_{OUT}$  by connecting the TEMPIN pin to ground and then configuring the Temp ADC to read the TEMPIN pin. This result can be stored and subtracted from all PGA309  $V_{OUT}$  readings. The offset of the Temp ADC is its dominant error.
- In both example applications, the PGA309 operates as a programmable sensor signal conditioner. Its internal state machine for compensation is not active. Therefore, all computations for setting the Gain and Zero Digital-to-Analog Converters (DACs) while the temperature changes must be performed by the microcontroller.
- Either the one-wire interface or the two-wire interface may be used by the microcontroller to communicate with the PGA309. The two-wire interface is compatible with microcontrollers that have a dedicated I<sup>2</sup>C™ port.
- If using either the two-wire or one-wire interface, the port pins must be open drain to allow either the PGA309 or the microcontroller to pull down.
- Application 1 may have some level-shifting considerations, depending on the microcontroller port pin capabilities. The SCL and SDA lines of the PGA309 have 85µA (typical) pull-up current sources to the PGA309  $V_{SD}$  supply pin.
- The internal pull-up current sources on the PGA309 SCL and SDA (85µA, typical) will need to be evaluated in the specific application. External pull-up resistors may need to be added, depending on capacitive loading and bus speed.

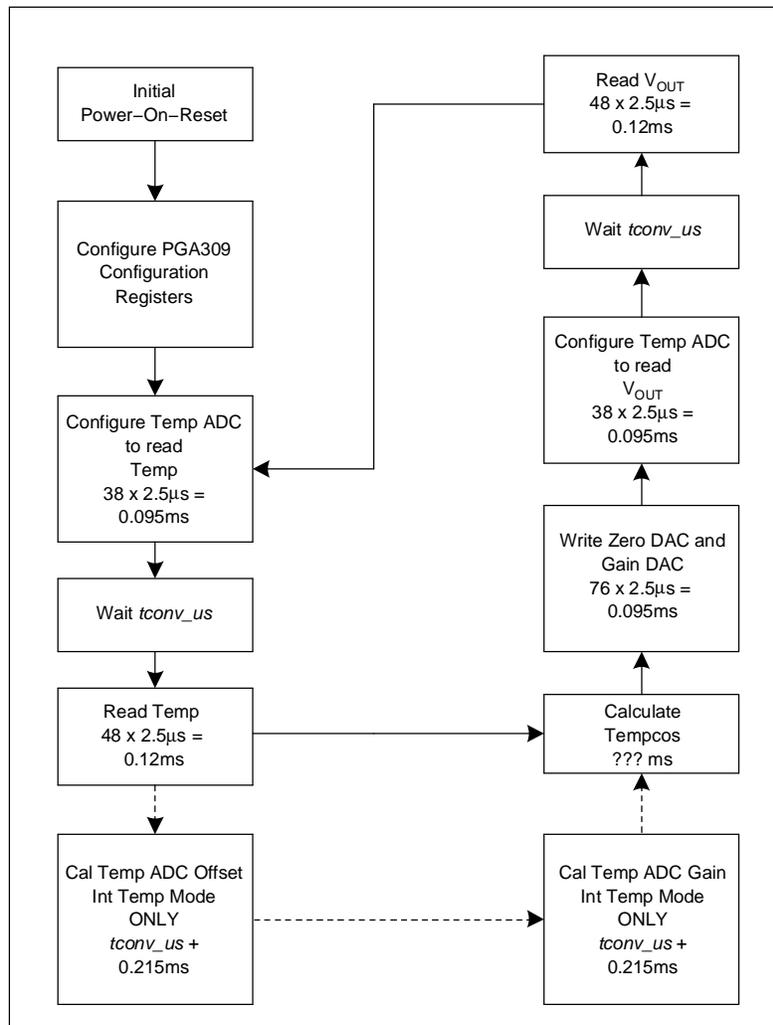


Figure 3. Typical Flowchart for External Microcontroller and PGA309 Application

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

<b>Products</b>		<b>Applications</b>	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
		Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
		Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments  
Post Office Box 655303 Dallas, Texas 75265