

Automotive Current Monitoring Using High Speed Amplifiers



With vehicle electrification increasing and as fully electric vehicles become more mainstream, the number of electric motors and digital power control systems in automobiles are expanding. Many of these systems require high-speed current monitoring circuits to ensure proper operation and to protect against potentially damaging overcurrent conditions. One of the most effective ways to accomplish this function is to employ a low side current shunt monitoring circuit like the one shown in Figure 1.

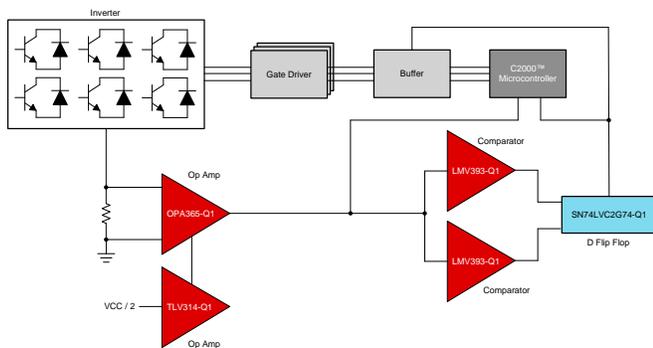


Figure 1. Automotive Current Monitoring Diagram

This circuit provides overcurrent and short-circuit protection with the use of two op amps, two comparators and a D-type flip-flop. The OPA365-Q1 operational amplifier (op amp) used in the circuit performs a differential voltage measurement across a shunt resistor. The voltage across the resistor corresponds to the current that flows through the inverter. It is important that the op amp used in this part of the circuit has low noise and low offset to minimize degradation of the low voltage signal measured across the shunt resistor. It is also critical that the amplifier has fast settling time and a high slew rate in order to achieve a fast response time to detect overcurrent or short-circuit conditions. High bandwidth also enables a single high-gain stage to be implemented in a single amplifier to drive the input of the comparator and analog to digital converter (ADC) in the circuit.

The zero-crossover, rail-to-rail, OPA365-Q1 CMOS op amp is ideal for this application. It has 50MHz of bandwidth, noise of only 4.5nV per root hertz and a low offset of only 100 micro volts. The device also features a fast settling time of only 0.3 micro seconds and a slew rate of 25 volts per micro second. The

amplifier also has an operating temperature range of -40 to 125 degrees Celsius and is AEC Q100 grade 1 qualified for automotive applications. The key specifications for the OPA365-Q1 op amp are summarized in Table 1.

Table 1. OPA365-Q1 Key Specifications

OPA365-Q1 Key Specifications	
Bandwidth	50 MHz
Noise	4.5 nV/√Hz @ 100 kHz
Offset	100 μV
Settling Time	0.3 μs to 0.01%
Slew Rate	25 V/μs
Ambient Temperature	-40°C to 125°C
Package Size (Body)	2.9 mm x 1.6 mm SOT-23(5)

The TLV314-Q1 is used in the circuit as a voltage follower and functions as a source for the reference voltage. This amplifier provides high stability at unity gain and has the ability to drive capacitive loads up to 300 pF. In this circuit, the TLV314-Q1 provides a reference voltage of V_{CC} divided by 2 to the OPA365-Q1. With this configuration, the output voltage range of the OPA365-Q1 varies from $1/2$ of V_{CC} to V_{CC} for one direction of shunt current and from $1/2$ of V_{CC} to GND for the other direction of shunt current. This circuit is shown below in Figure 2.

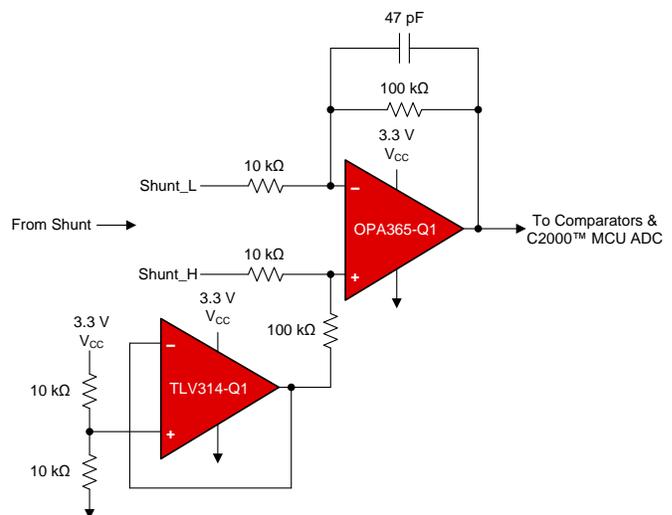


Figure 2. Reference Voltage Circuit

The output of the OPA365-Q1 is connected to the comparator circuit and the analog to digital converter input on the C2000™ microcontroller. The C2000 TMS320F28052 microcontroller is part of TI's Piccolo™ family of MCUs. It has a 12-bit, 3.75 mega sample per second ADC that is driven by the OPA365-Q1 amplifier and can be used to monitor or log the shunt current. The C2000 microcontroller has been specifically designed for use in automotive motor control and digital power applications.

Since a short circuit or overcurrent condition can potentially be harmful, a comparator-based shut-off circuit with an extremely fast response time is also implemented. This comparator-based circuit can disable the gate drivers in the system much faster than the MCU. In the circuit, the OPA365-Q1 differential op amp output is connected to the inputs of the dual channel LMV393-Q1 comparator. This device integrates two comparators into a single package and provides a cost-effective, space-saving design for this portion of the circuit. The comparators have trigger levels that correspond to an overcurrent condition. One comparator is set up in an inverted configuration to make it possible to detect current peaks in the shunt resistor in the opposite direction. When an overcurrent or short-circuit current occurs on one of the phases of the inverter, the responsible comparator detects it and changes its output state accordingly. The dual comparator circuit is shown in Figure 3.

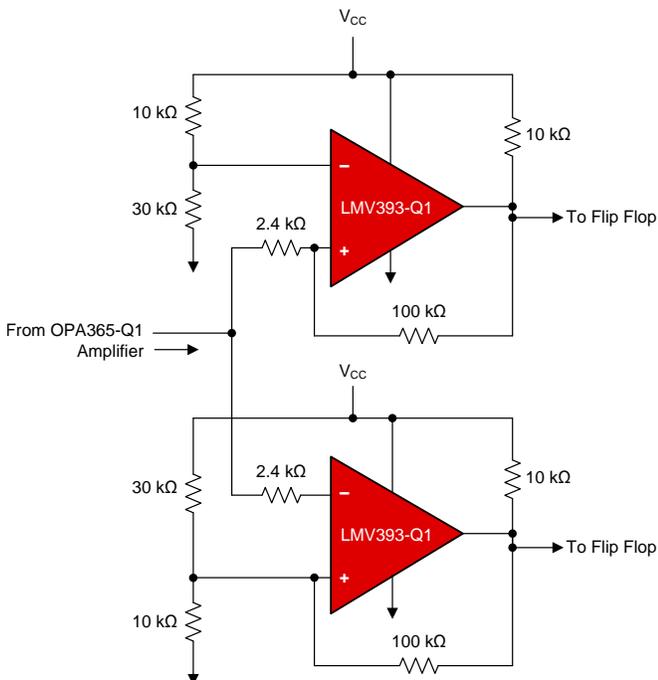


Figure 3. Dual Comparator Circuit

When the comparator changes state, it triggers the SN74LVC2G74-Q1 D flip-flop in the circuit to disable the buffer between the MCU and gate drivers. When the buffer is disabled, the gate driver input signals are pulled down through the low-side resistors connected to each control line and the gate drivers force the Insulated-Gate Bipolar Transistors or IGBTs in the system to turn off. This comparator based circuit has a very fast response time that can potentially help prevent damage from occurring to the system in the event of a short circuit fault.

This current monitoring circuit is featured in a TI Design, or reference design, for a high-voltage, high-power motor drive circuit for automotive heating, ventilation and air conditioning (HVAC) compressors. The reference design features a three-phase inverter drive which is based on a discrete IGBT for driving brushless DC (BLDC) motors for automotive A/C compressors using sensorless torque control. More information about the TI Design, including full design schematics, can be downloaded from the following web link: <http://www.ti.com/tool/tida-01418>. The circuit board for the reference design is shown in Figure 4.



Figure 4. TI Design TIDA-01418 Circuit Board

With the number of electric motors and digital power systems increasing in automobiles the need for high-speed current monitoring systems is becoming more important. The zero-crossover, rail-to-rail, OPA365-Q1 op amp is in integral part in these systems. It has fast settling time and a high slew rate in order to achieve a fast response time to detect overcurrent or short-circuits in these systems to prevent potentially damaging conditions from occurring.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated