

How to Meet 24-V Hot Plug-in Test for Charge Front-End bq243xx

Mao Ye

PMP - Battery Charge Management

ABSTRACT

The maximum input voltage rating of the bq243xx family of ICs is 30 V. However, some customers like to perform a 24-V hot plug-in transient test to prove its high-voltage capability and reliability from a system level. It is important for system designers to properly design the charging system with correct system-level protections. Usually, a TVS (transient voltage suppression) Zener diode is used for clamping such high-pulse transient voltage so that the maximum input voltage from the charge front-end (CFE) protectors bq243xx is less than absolute maximum voltage for safe operation.

Test Setup:

Figure 1 shows the 24-V hot plug-in transient test schematic. A 1- μ F input and a 1- μ F output capacitors are used for CFE. First, a soft start-up with a 24-V voltage is applied to show that a slow, ramp-up input voltage does not generate any overvoltage spike. Secondly, a 24-V hot plug-in was tested to show that without the TVS Zener diode, the voltage spike can exceed the bq243xx absolute maximum voltage of 30 V. After that, a proper TVS Zener diode was added to show that it clamps the voltage to make the bq243xx devices work in a safe range.

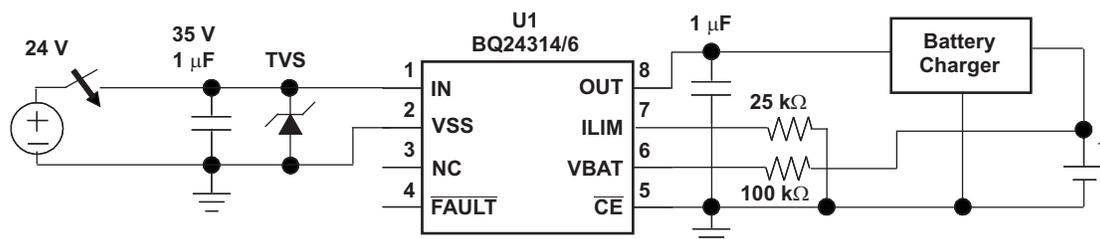


Figure 1. 24-V Hot Plug-in Transient Test Schematic

In the following test waveforms, CH3 and CH4 are represented as follows:

CH3: IN pin

CH4: input current, measured before the input capacitor, 5 A/div.

Test One: No TVS Zener Diode, 24-V Soft Start-up

Figure 2 shows the input voltage and current waveforms. Due to the soft start-up, neither voltage spike nor input inrush current occurs at input pin of the bqCFE .

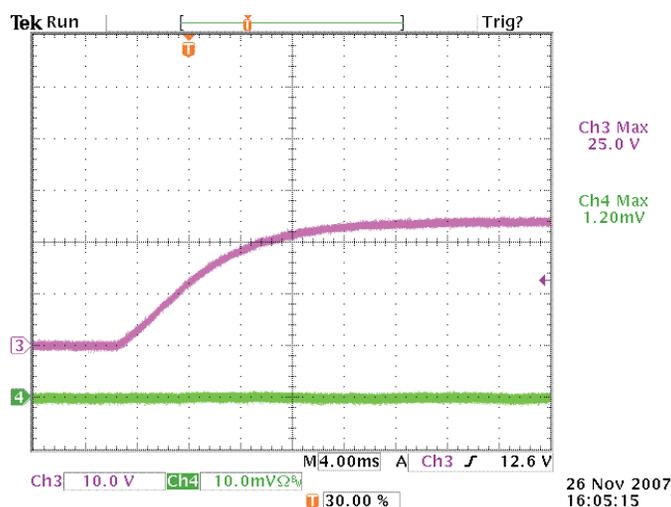


Figure 2. Soft Start-up of 24-V Input Voltage, CH3 10 V/div, CH4 5 A/div

Test Two: No TVS Zener Diode, 24-V Hot Plug-in

Due to the hot plug-in, the input pin of the bq243xx can have very high voltage due to the resonance between the cable inductance and the input decoupling capacitor of the bq243xx. Ideally, the voltage spike can be up to two times the input voltage. But the equivalent resistance of the cable and the input capacitor damp the oscillation. The practical voltage spike is approximately 1.2 to 1.8 times the input voltage as shown in Figure 3. Without any additional component, this high voltage may damage the bq243xx.

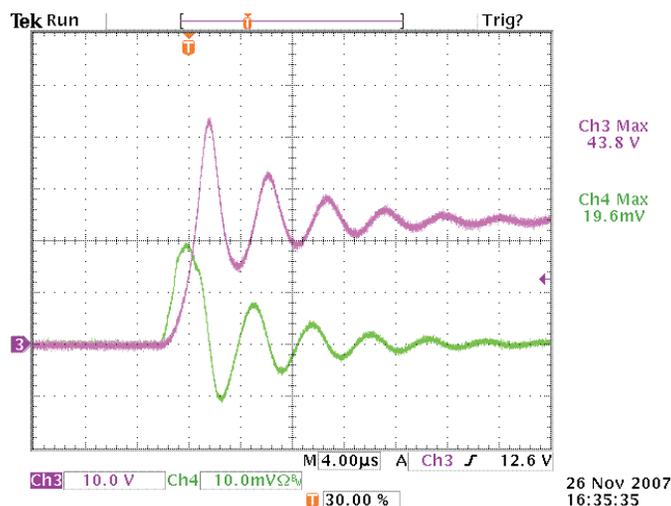


Figure 3. 24-V Hot Plug-in Without TVS Zener Diode, CH3 10 V/div, CH4 5 A/div

Test Three: Add TVS Zener Diode MMBZ27VCLT, 24-V Hot Plug-in

A SOT-23 package TVS Zener Diode MMBZ27VCLT (<http://www.onsemi.com>) was added at input side to clamp the voltage spike. The hot plug-in waveform is shown in Figure 4. The peak voltage spike is limited to 31 V. The clamping voltage is determined by the inrush current flowing through the Zener diode. The higher the inrush current, the higher the clamping voltage is. Select a Zener diode which has a lower clamping voltage with the same amount of inrush current.

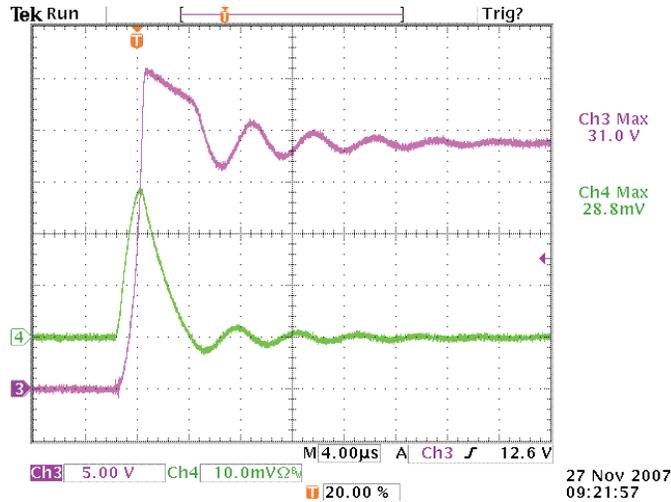


Figure 4. 24V Hot Plug-in With TVS Zener Diode MMBZ27VCLT, CH3 5V/div, CH4 5A/div

Test Four: Add TVS Zener Diode DFLT24A, 24-V Hot Plug-in

A PowerDI-123 package TVS Zener Diode DFLT24A (<http://www.diodes.com>) was added at the input side to clamp the voltage spike. The test result is shown in Figure 5. The peak voltage spike is limited to 29 V. This Zener diode has better performance compared with the previous one. It has lower clamping voltage under the same amount of current flowing through the Zener diode.

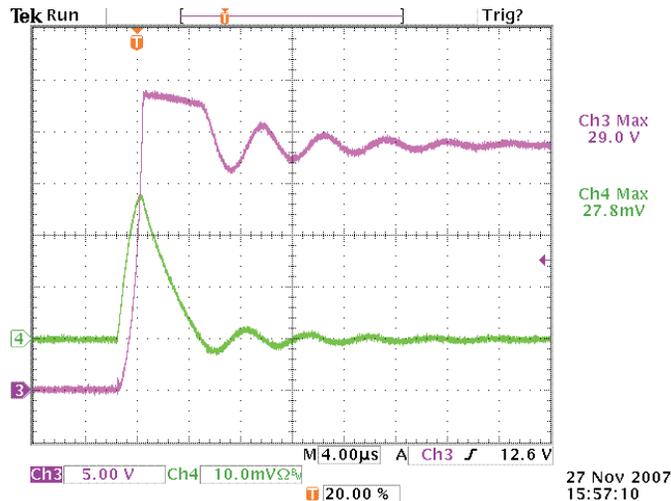


Figure 5. 24-V Hot Plug-in With TVS Zener Diode DFLT24A, CH3 5 V/div, CH4 5 A/div

Conclusion

For a 24-V hot plug-in test, use a TVS Zener diode to clamp the input voltage spike. In summary, bq243xx devices can pass the 24-V hot plug-in transient test with the setup shown Figure 1 using the recommended TVS Zener diodes.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright 2008, Texas Instruments Incorporated