

Factors That Determine Light Load PSM Switching Frequency for TPS6102x Boost Converters

Will Hadden

Power Management Products / Portable Power DC-DC Applications

ABSTRACT

This application report explains the factors that determine the low output power switching frequencies when using the TPS6102x step up converters.

Contents

1	Introduction	1
2	References	7

List of Figures

1	PSM Output Ripple (Top Waveform) 50 mV/div vs PWM Output Ripple (Bottom Waveform) 50 mV/div	2
2	Output Capacitance Effect on Switching Frequency	3
3	Output Capacitance Effect on Switching Frequency	3
4	Output Capacitance Effect on Switching Frequency	4
5	Output Capacitance Effect on Switching Frequency	4
6	Output Capacitance Effect on Switching Frequency	5
7	Inductor Effect on Switching Frequency	5
8	Inductor Effect on Switching Frequency	6
9	Inductor Effect on Switching Frequency	6
10	Inductor Effect on Switching Frequency	7
11	Inductor Effect on Switching Frequency	7

1 Introduction

To increase light load efficiency, the TPS6102x family of switching converters operate in power save mode (PSM). In PSM, the converter only switches when the output voltage is below the programmed threshold which results in a reduced switching frequency at light loads. The output voltage is user programmable for the TPS61020, TPS61028 and TPS61029 using an external resistor divider and is factory programmed for the TPS61024-TPS61027. When the voltage at FB falls to 98.4% of the reference voltage (500 mV typical), the IC begins switching. The IC switches at a constant switching frequency (600 kHz typical) with a duty cycle determined by the ratio of the input voltage and the voltage at FB. As the IC switches, the output voltage steadily rises. The IC reduces the on-time of the power switching MOSFET as the FB voltage rises. Reducing the on-time results in the inductor current falling to zero, which triggers the IC to stop switching. It normally takes several pulses for the inductor current to drop to zero, depending on the input/output voltage. For this document, the PSM frequency is defined as the timing of these groups of pulses. At light or no load, this is the larger *frequency* component of the output ripple. As the load increases, the PSM frequency increases until the IC's off time is reduced to zero. At this point, the IC transitions back into fixed frequency PWM mode at the 600-kHz internal oscillator frequency. [Figure 1](#) illustrates the difference between light load and heavy load output ripple to clarify this point. Both of these waveforms are taken with an output of 5 V and an input of 3.6 V.

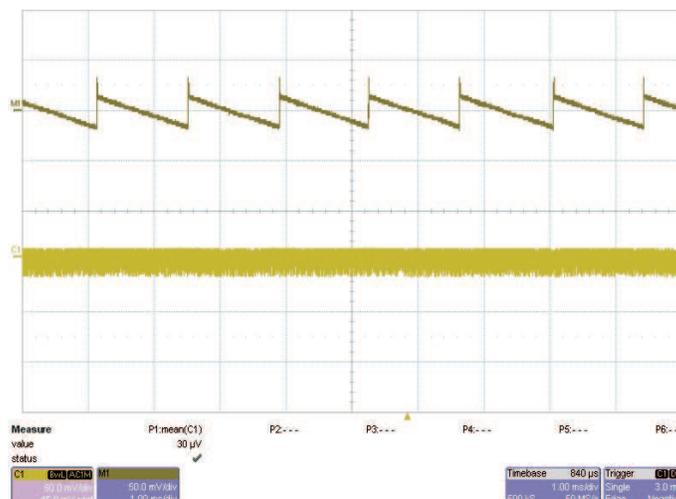


Figure 1. PSM Output Ripple (Top Waveform) 50 mV/div vs PWM Output Ripple (Bottom Waveform) 50 mV/div

As the load increases in PSM mode, the number of pulses in the rising edge increases and the fall time decreases. This results in higher switching frequencies for heavier loads. The switching frequency at light loads is dependant on factors such as output load, the input and output voltage, and external component values.

1.1 Input/Output Voltage

The input and output voltage determine the IC's duty cycle during the switching cycles. The duty cycle changes the peak-to-peak current in the inductor. This in turn affects the rate at which the output capacitor is charged during each switching cycle. The output voltage also affects the amount of voltage drop required to trip the error amplifier. Since the voltage at FB is resistor divided down from the output, the higher the output, the more the output voltage must fall before FB falls below 98.4% of the reference. Conversely, the more the output must rise to come back into regulation. This means that a higher output voltage has a lower switching frequency. [Figure 2](#) through [Figure 11](#) show PSM switching frequency vs load current for several input and output voltage combinations.

1.2 Output Capacitance

The output capacitance determines the fall time of the output voltage as well as part of the rise time. As the load bleeds the charge out of the output capacitors, the output falls. Once the output falls below 98.4% of the feedback threshold of the error amplifier the IC switches to bring the output back into regulation. The rate at which the output falls for a given load is totally dependant on the output capacitance. With more output capacitance, the longer it takes for the output to fall. This longer output fall time results in a lower frequency. At very light or no load conditions, this fall time dominates the total period. During the switching cycles, the output capacitor determines the rate at which the output rises during each cycle. As energy is transferred from the inductor to the output capacitor, the output voltage rises. With a larger output capacitor, it takes longer for the output to rise. Increasing the size of the output capacitor decreases the switching frequency substantially because it affects both rise and fall time of the output. [Figure 2](#) through [Figure 6](#) show the affect of output capacitance on switching frequency. The graphs illustrate the PSM frequency. The endpoint of the graphs is the point at which the IC operates in PWM mode.

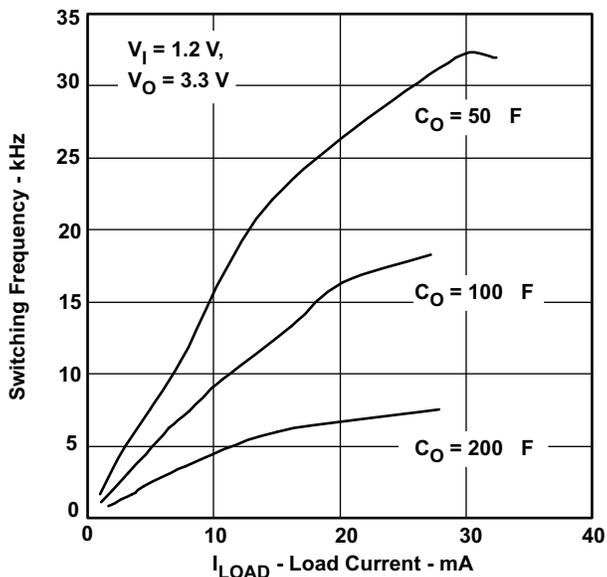


Figure 2. Output Capacitance Effect on Switching Frequency

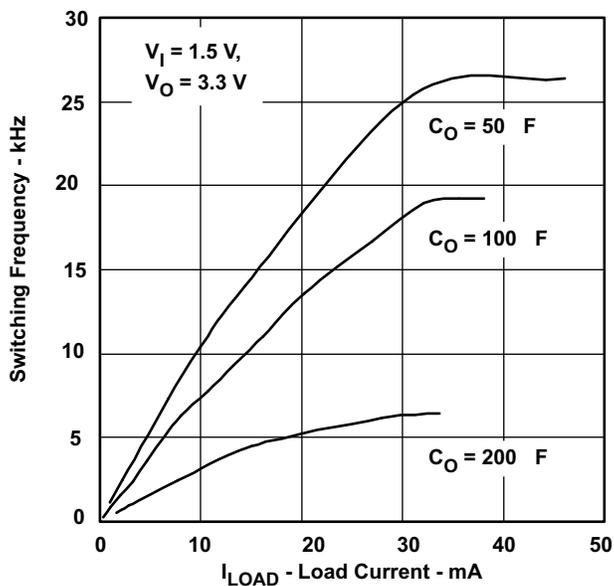


Figure 3. Output Capacitance Effect on Switching Frequency

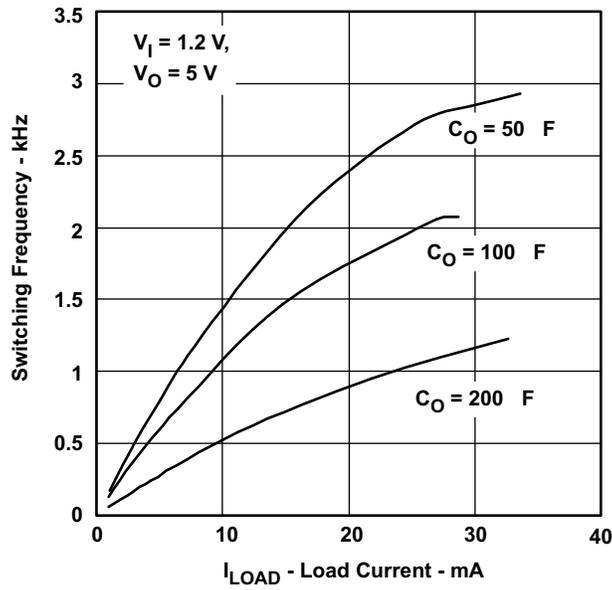


Figure 4. Output Capacitance Effect on Switching Frequency

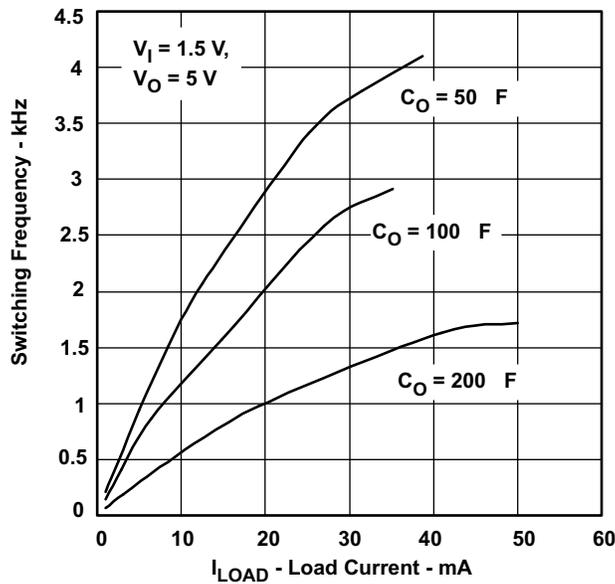


Figure 5. Output Capacitance Effect on Switching Frequency

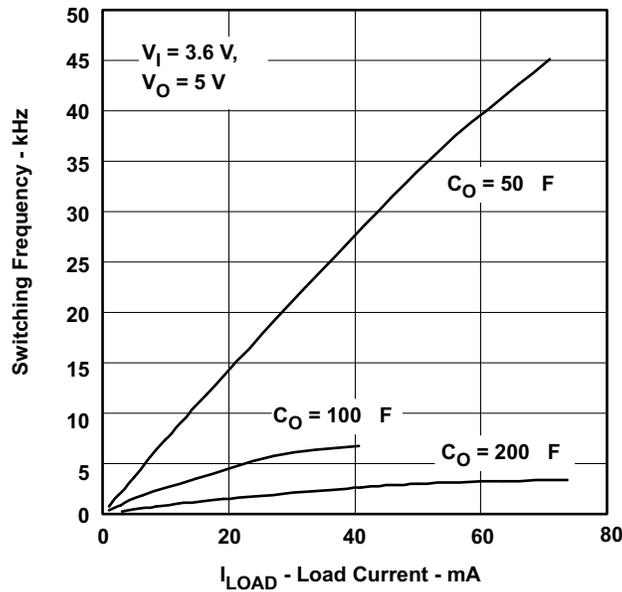


Figure 6. Output Capacitance Effect on Switching Frequency

1.3 Inductor Value

The inductor value determines how much energy is transferred to the output capacitor during each switching cycle. A larger inductor produces lower current ripple. This translates to a lower switching frequency because the output is not charged up as much during each switching cycle. See Figure 7 through Figure 11 for examples of the inductor's effect on switching frequency.

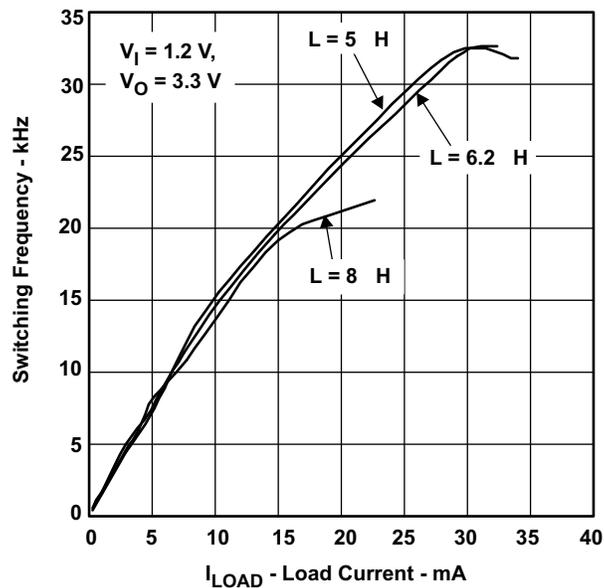


Figure 7. Inductor Effect on Switching Frequency

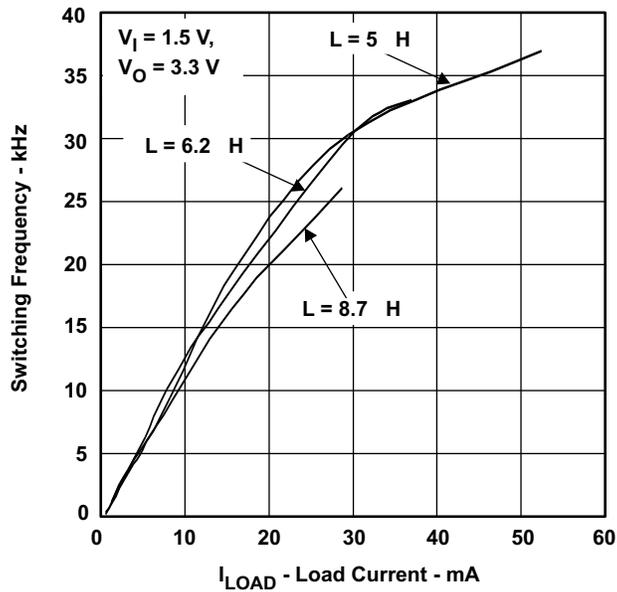


Figure 8. Inductor Effect on Switching Frequency

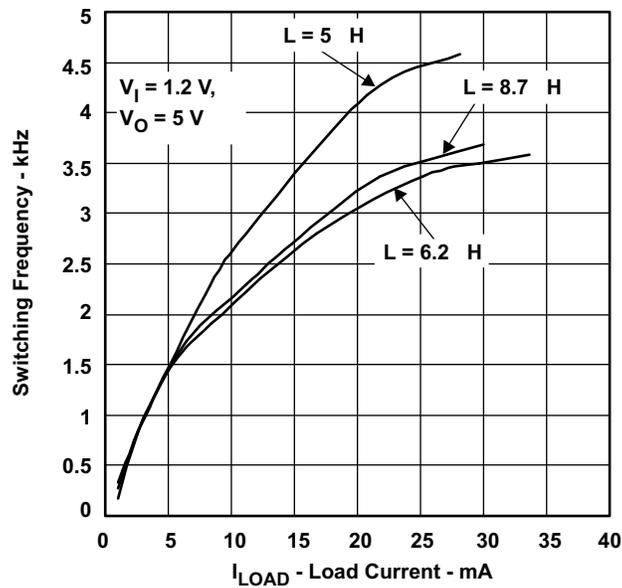


Figure 9. Inductor Effect on Switching Frequency

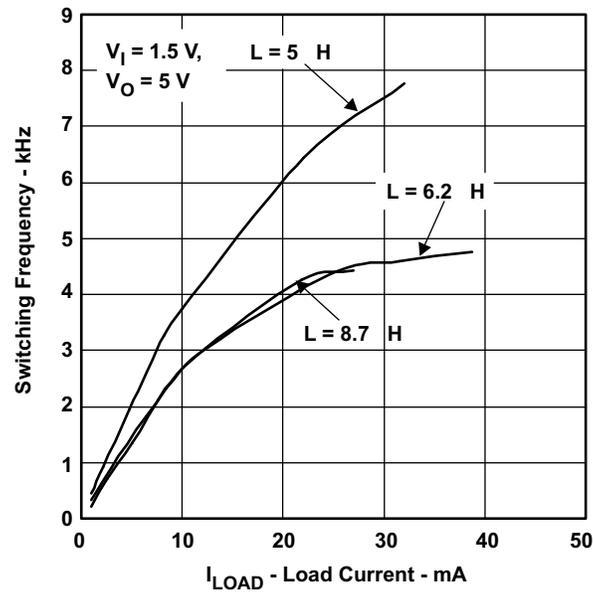


Figure 10. Inductor Effect on Switching Frequency

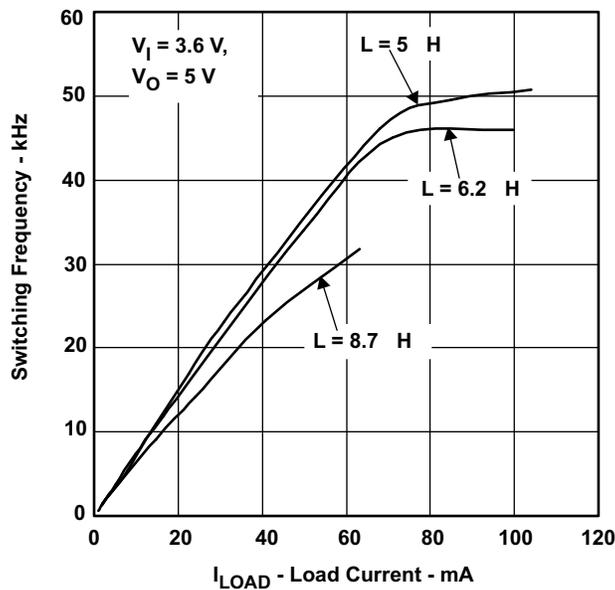


Figure 11. Inductor Effect on Switching Frequency

PSM frequency is dependant factors such as input/output voltage, external components and load current. The graphs in this appnote provide the user with a good starting point. The end circuit should be prototyped in order to verify that the circuit operates at the required PSM frequency for the end application.

2 References

1. TPS61020 Data sheet ([SLVS451D](#))
2. TPS61020EVM User's Guide ([SLVU100](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2006, Texas Instruments Incorporated