

## Optimizing the TLV62090 Output Filter

Daniel Katz

Battery Power Applications

### ABSTRACT

The TLV62090 family of devices uses a variation of the inherently stable hysteretic control topology called DCS-Control™, which allows for a wider range of inductor and output capacitor values than traditional voltage mode buck converters. The inductor and output capacitor values can be chosen to accomplish specific design goals, such as transient response or loop stability based on an application's needs. This application note discusses how to choose the output filter for the TLV62090 Vin buck converter in order to meet the specific requirements of a design.

### Choosing and LC Combination

The designer must consider many factors when choosing an inductor and output capacitor combination for any switching regulator. For example, lower inductances can be physically smaller due to fewer windings which can save board space; however, the peak switch current and output voltage ripple will increase. Larger voltage ripple can be offset by using a higher capacitance at the cost of larger size and slower transient response.

Stability is also a key factor that is affected by the inductor and capacitor values. The LC filter forms a double pole in the control loop which has a strong impact on the frequency response and stability of the system. [Table 1](#) shows the stability of different LC combinations that have been tested in the laboratory with an input voltage of 4.2 V and a load current of 1.5 A at an output voltage of 1.8 V. Although the stable combinations in the table satisfies the requirements for control loop stability, certain combinations may not work in every system due to other measures of performance – such as output voltage ripple, load transient response or maximum output current.

**Table 1. Stability versus Effective LC Corner Frequency**

Inductance Value	Capacitance			
	10 $\mu$ F	22 $\mu$ F	47 $\mu$ F	100 $\mu$ F
<b>1.0 <math>\mu</math>H</b> Coilcraft XFL4020-102	222.2 kHz 53.55 deg	125.2 kHz 51.04 deg	82.09 kHz 49.06 deg	46.83 kHz 38.45 deg
<b>2.2 <math>\mu</math>H</b> Coilcraft XFL4020-222	116.5 kHz 57.18 deg	72.71 kHz 47.81 deg	49.07 kHz 37.61 deg	28.58 kHz 31.22 deg
	Recommended LC combination			
	Acceptable LC combination depending on application			
	Not recommended			

[Table 1](#) shows control loop stability versus effective corner and indicates the corresponding nominal inductance and capacitance. The colors of the boxes indicate the stability of the system – white is recommended, yellow is acceptable, depending on application, and red is not recommended.

### Optimizing Load Transient Response

The load transient response describes the controller's ability to recover from sudden changes in output current, such as those caused by a processor changing states. The amount of voltage deviation and the time that the controller takes to recover are the main measures of a controller's load transient performance.

The response time of the controller is directly related to the bandwidth of the control loop. A higher bandwidth allows the controller to respond faster. Since the control loop compensation is fixed inside the IC, the bandwidth is primarily impacted by the corner frequency of the LC filter which forms a double pole in the control loop. The corner frequency of the filter is given as:

$$f_{LC} = \frac{1}{2\pi\sqrt{LC}} \quad (1)$$

Higher LC corner frequencies allow for higher control loop bandwidths. To increase the LC corner frequency, decrease the product of the inductance and capacitance.

Secondly, the amount of voltage deviation that occurs during a change in load must be restricted to keep the power supply voltage within the requirements of the system. This can especially pose a problem for processors that may operate incorrectly at low voltages. There are two main things that determine the amount of voltage deviation: the output capacitance and control loop bandwidth.

From the equation  $I = C \times dV/dt$ , the output voltage deviation in response to a load step is defined as:


$$\#SLVA5187082 \quad V_{DEV} = V_{OUT}(t_2) - V_{OUT}(t_1) = \frac{1}{C} \int_{t_1}^{t_2} [i_L(t) - i_{Load}(t)] dt \quad (2)$$

Where  $t_1$  is the time the load step begins and  $t_2$  is the time that the average inductor current equals the new load current (see [Figure 1](#)). The time between  $t_1$  and  $t_2$  is an initial time period during which the output capacitor must supply the extra load current and therefore the capacitor voltage must decrease. From [Equation 2](#), the most obvious way to reduce this initial deviation is to use a larger capacitance. It is worth noting that a larger capacitance will have a negative impact on the controller's response time.

[Figure 2](#) shows the effect of a larger output capacitor on voltage deviation and settling time, or the time it takes for the output voltage to settle within a tolerable percentage of the nominal voltage. [Figure 3](#) shows the transient load response with a 2.2- $\mu$ H inductor and 10- $\mu$ F capacitor.

[Figure 3](#) shows the transient load response with the same inductor and a 100- $\mu$ F capacitor. The 10- $\mu$ F capacitor has a voltage deviation of about 80 mV, while the 100- $\mu$ F capacitor has a deviation of about 65 mV. The downside of using the larger capacitor is that the settling time of the output voltage is about one and a half times as long as the smaller capacitance. [Figure 4](#) and [Figure 5](#) show the control loop bandwidth for each circuit as measured by the method presented in [SLVA465](#). As expected, [Figure 3](#) has a lower bandwidth which translates to a longer response time.

At time  $t_2$ , when the average inductor current is equal to the new load current, the controller begins to supply the extra current rather than the output capacitor. At this time, the voltage has deviated by its maximum amount from the desired value and the controller will begin to recharge the output capacitor. Therefore, another way to reduce the amount of voltage deviation is to decrease the amount of time that the controller takes to respond and thus reduce the time between  $t_1$  and  $t_2$ . This is accomplished by decreasing the inductance, which will increase the bandwidth of the controller.

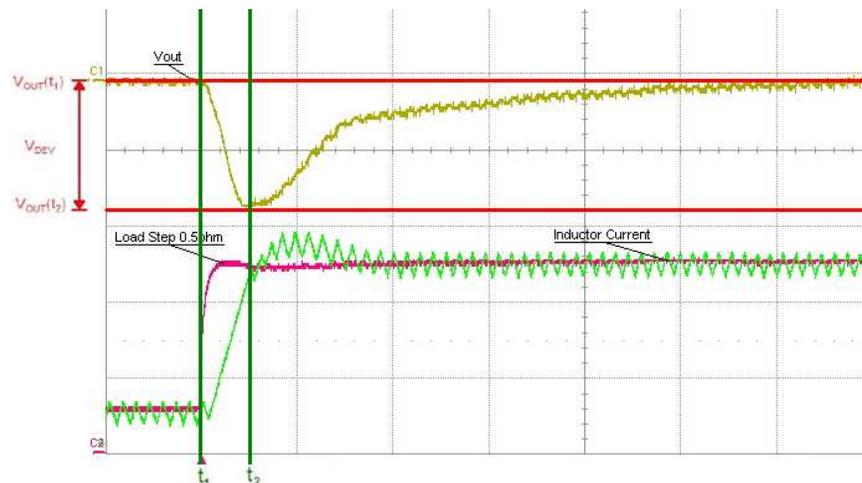

**Figure 1. Load Transient Response of the TLV62090**

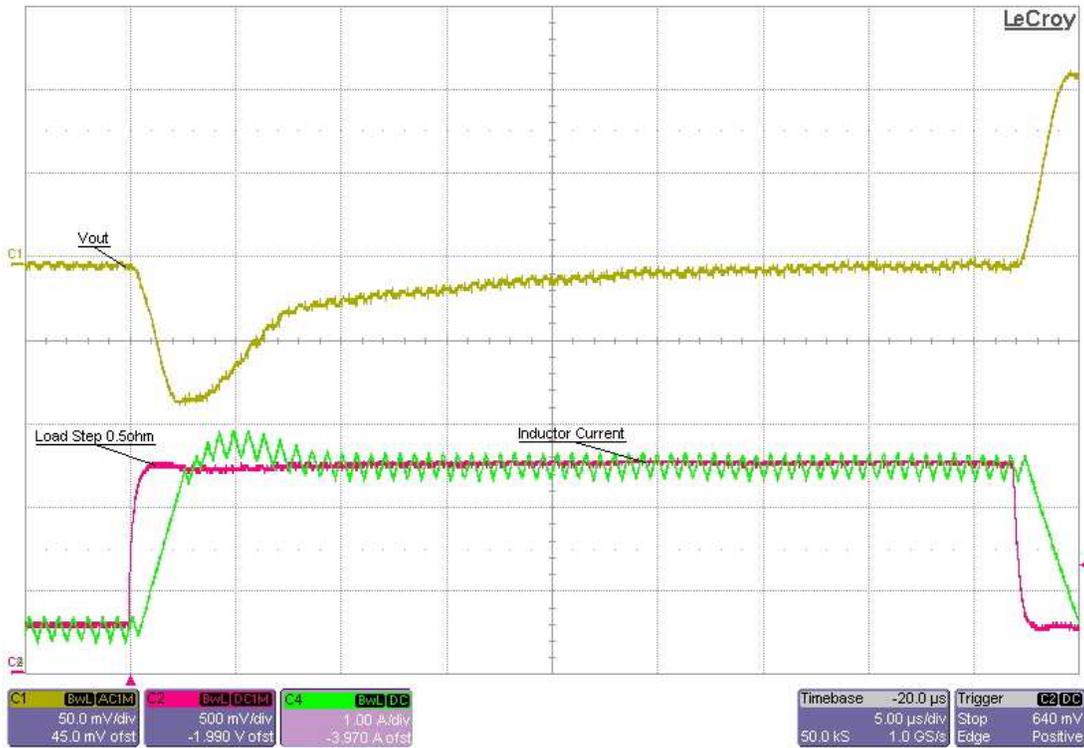


Figure 2. Load Transient with 2.2-µH Inductor and 10-µF Capacitor

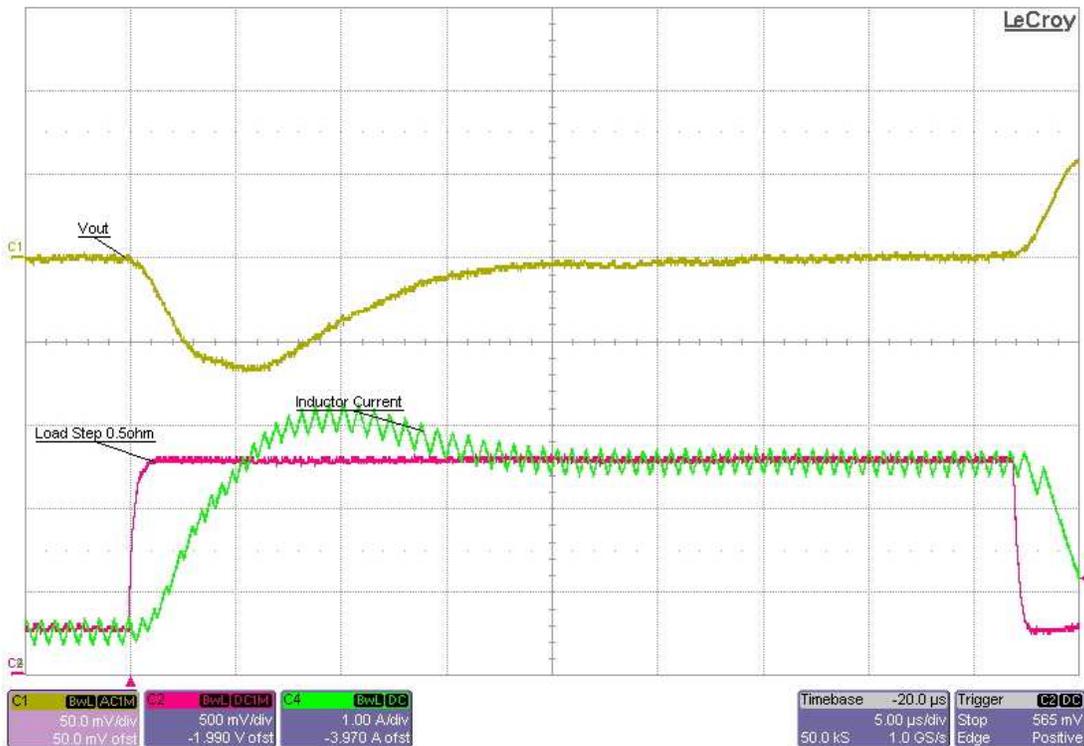


Figure 3. Load Transient with 2.2-µH Inductor and 100-µF Capacitor

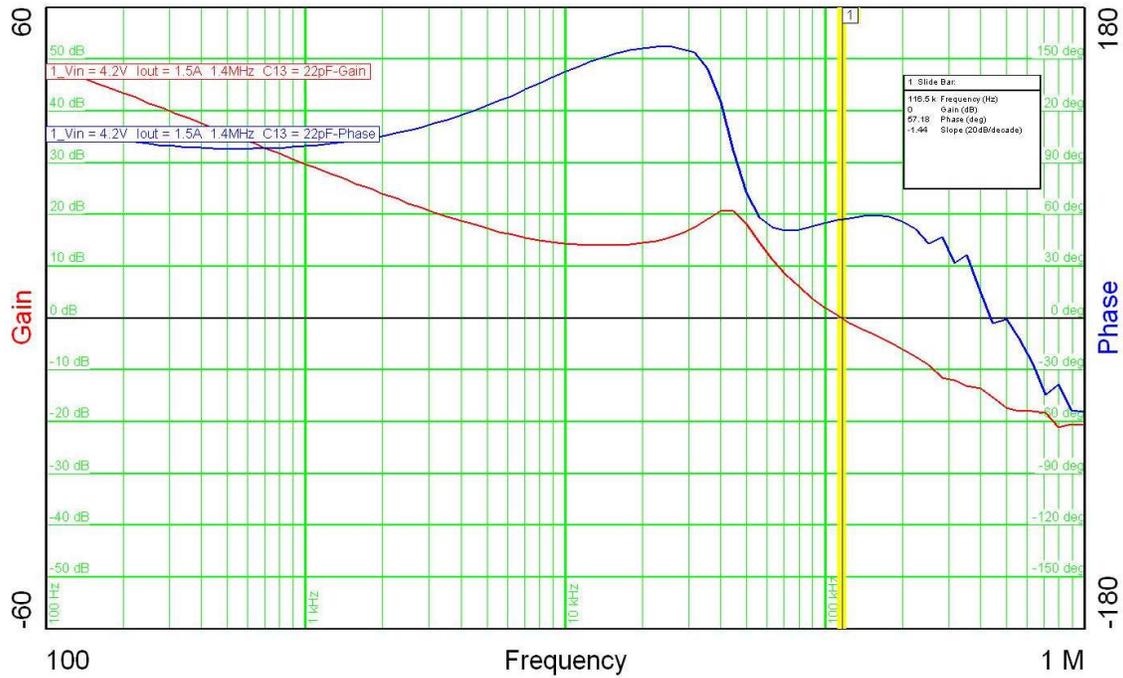


Figure 4. Control Loop Gain with 2.2- $\mu$ H Inductor and 10- $\mu$ F Capacitor

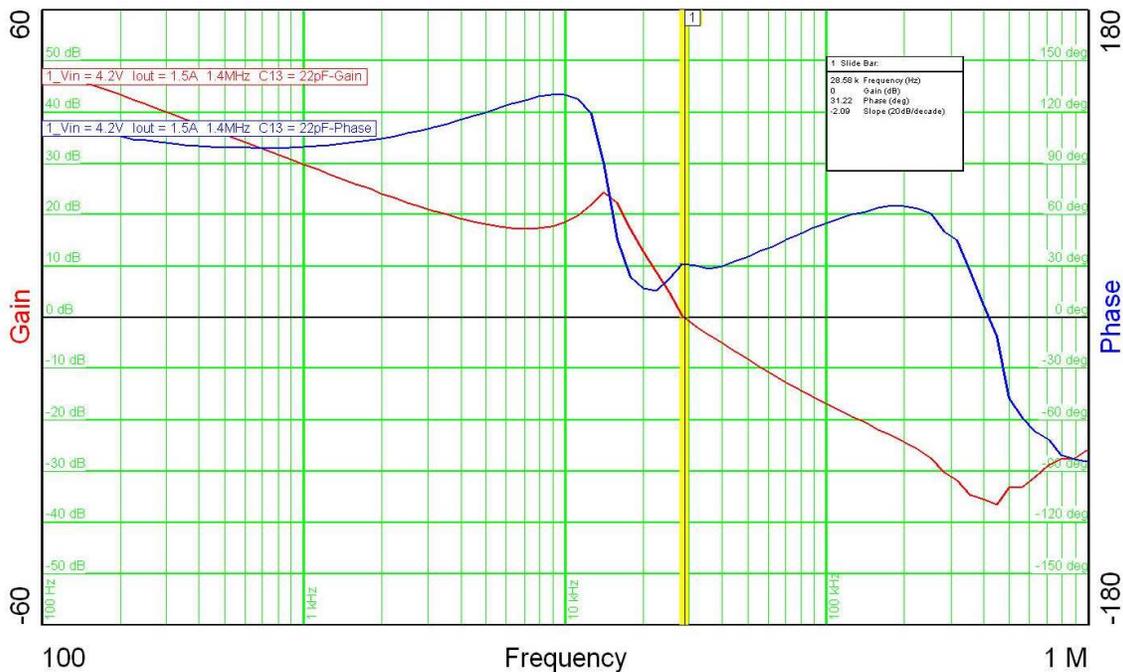


Figure 5. Control Loop Gain with 2.2- $\mu$ H Inductor and 100- $\mu$ F Capacitor

## Conclusion

This application note has presented methods to ensure stability and improve the load transient response with the TLV62090 device. The methods presented in this application note, as well as in the references, allow for a wide variety of external components to be used to achieve the desired power supply performance. The benefits and tradeoffs associated with designing the output filter, as discussed here, aid with the design of a TLV62090 power supply.

## References

1. Measuring the Control Loop Gain of a DCS-Control Device™ ([SLVA465](#))
2. TLV62090 Datasheet ([SLVSBB9B](#))

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46C and to discontinue any product or service per JESD48B. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components which meet ISO/TS16949 requirements, mainly for automotive use. Components which have not been so designated are neither designed nor intended for automotive use; and TI will not be responsible for any failure of such components to meet such requirements.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

**TI E2E Community** [e2e.ti.com](http://e2e.ti.com)