

TPS65250/1/2/3

Line Consumer Analog Product Group

TPS65250/1/2/3 LAYOUT GUIDE

The TPS65250, TPS65251, TPS65252, and TPS65253 family of power management ICs provides easy to use, flexible, 2xDCDC and 3xDCDC configurations. In order for the converters to perform optimally, certain layout rules should be followed. Passive components should be placed as close as possible to their respective pins in order to reduce trace parasitics. Input and output filters have the highest placement priority, while the placement of LDO decoupling caps is least important. A four layer board is recommended for optimal thermal management, and the power pad should be connected to the ground plane. Adherence to these guidelines will help the proper operation of your TPS65250/1/2/3 device.

Table of Contents

1 TPS65250/1/2/3 Layout Guide..... 4

1.1 Why a Good Layout is Important 4

1.2 Component Placement Rules 5

1.3 PCB Stack-Up (4 Layers) 5

1.4 Thermal Management 5

1.5 Two Layer Board Usage..... 5

1.6 Buck Current Flow During D Stage (Creation of AC Pulsed Current)..... 5

1.7 Buck Current During (1-D) Stage (Creation of AC Pulsed Current)..... 6

1.8 Input Capacitor Placement 7

1.9 Bad PCB Layout..... 8

1.10 Output Filter Considerations 9

1.11 Output Considerations 2 11

1.12 Control Components Placement 12

1.13 Feedback Traces..... 12

Appendix A. TPS65250/1/2/3 Layout Examples 14

Figures

Figure 1.	PMIC Layout.....	4
Figure 2.	Current Flow through D Stage.....	6
Figure 3.	Buck Current (1-D) Stage.....	6
Figure 4.	Input Capacitor Placement.....	7
Figure 5.	Capacitor Placement.....	8
Figure 6.	Bad PCB Layout 1.....	8
Figure 7.	Bad PCB Layout 2.....	9
Figure 8.	Ouput Filter Considerations 1.....	10
Figure 9.	Feedback Traces.....	13
Figure A-1.	TPS6251 Top Layer.....	14
Figure A-2.	TPS65251 Ground (2nd) Layer.....	14
Figure A-3.	TPS65251 3rd Layer.....	15
Figure A-4.	TPS65251 Bottom Layer.....	15
Figure A-5.	TPS65251 Placement Example 1.....	16
Figure A-6.	TPS65251 Placement Example 2.....	16
Figure A-7.	TPS65251 Placement Example 3.....	17
Figure A-8.	TPS65251 Placement Example 4.....	17
Figure A-9.	TPS65251 Power Pad Example.....	18
Figure A-10.	TPS65252 Top Layer.....	18
Figure A-11.	TPS65252 Ground (2nd) Layer.....	19
Figure A-12.	TPS65252 3rd Layer.....	19
Figure A-13.	TPS65252 Bottom Layer.....	20

1 TPS65250/1/2/3 Layout Guide

For the best performance of the chip, it is recommended that TPS6525x be used on a 4-layer board. For operation on a 2-layer board current and voltage de-rating is required, and it is application related. For further discussion, please contact the LCA Product Line.

1.1 Why a Good Layout is Important

There are different levels of activity on each PMIC pin. Pins HF AC activity are critical and the layout around them are also critical.

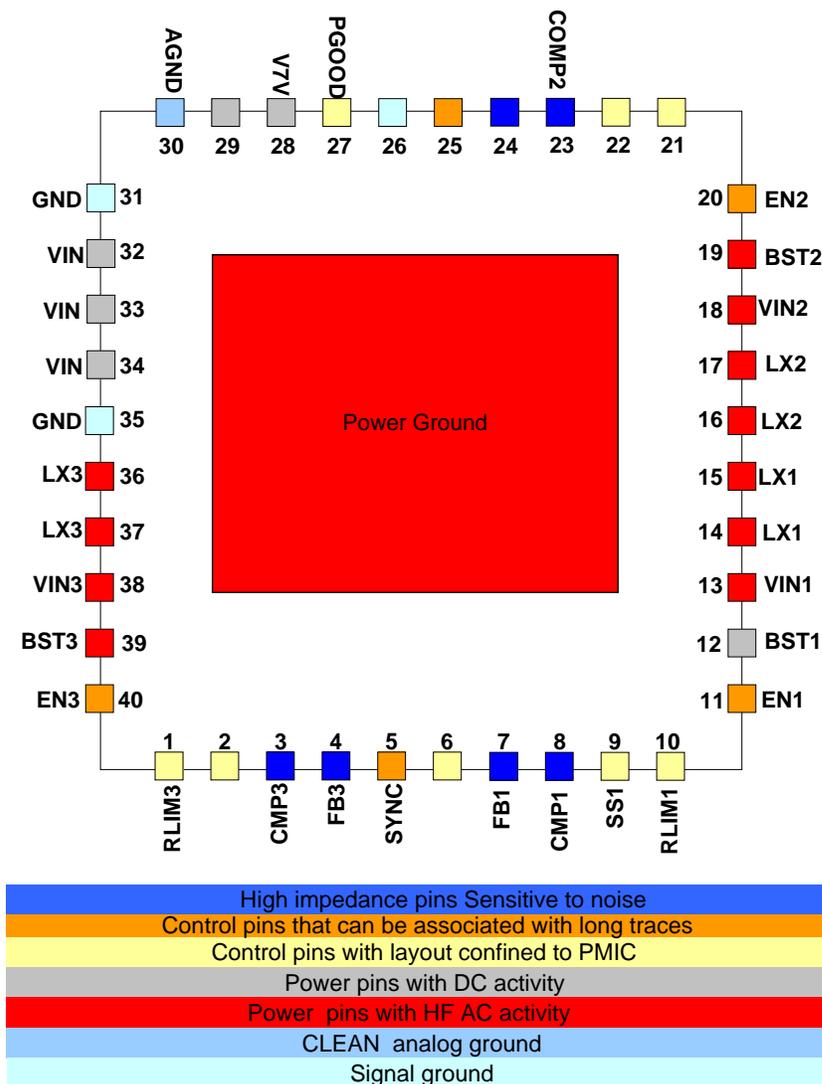


Figure 1. PMIC Layout

1.2 Component Placement Priority

In general, all external components need to be placed as close as possible to the power IC. The priorities of placement are as follows:

1. Input V_{in} capacitors
2. Output filter LC of switching regulators
3. COMPx pin components
4. Current limit control IRLMx,
5. OSC, SYNC pin
6. ENx pin capacitors
7. V3V and V7V output caps

1.3 PCB Stack-Up (4 Layers)

The top layer of the chip should contain DC-DC power traces and most signal lines. Any remaining area on the top layer should be filled with ground and be connected to bottom and internal grounds by strong via connection. Layer 2 is ground only and Layer 3 contains V_{IN} connections and remaining signal lines. It is critical to have a strong ground connection from all layers to each other, especially under the thermal pad. Layer 4 should be used for any additional non critical signals and ground. Use 2-oz copper for all layers if possible. See the appendix for TPS65251EVM (3 bucks) and TPS65252 (2 bucks) layout. The top side layer of the EVM is laid out in a manner typical of a multi-function DC/DC application layout.

1.4 Thermal Management

The power pad connection is used for both the thermal path and the electrical GND path in TPS6525x. Connection of power pad to ground plane helps thermal dissipation and lowers thermal resistance of the package. Moreover, the source of the low side FETs in DC-DC converters (Power ground –PGND) are connected to the power path and the thermal dissipation passes through the vias under the power pad. The EVM used 35 vias (each via: inside hole size = 0.03mm and outside hole size = 0.05mm).

1.5 Two Layer Board Usage

The TPS6525x supports both 2oz and 1oz copper trace 4 layers PCB board applications. Please contact TI before supporting the 2 layers board PCB layout.

1.6 Buck Current Flow During D Stage (Creation of AC Pulsed Current)

It is important to make sure that the GND path between input caps, output cap and the power pad GND is very short. The connection from Lx pins to inductors should be as close as possible. The current AC path includes input capacitor, HS fet, output inductor, and output capacitor. The PMIC current path includes V_{in} Pin, Lx pins and power PAD.

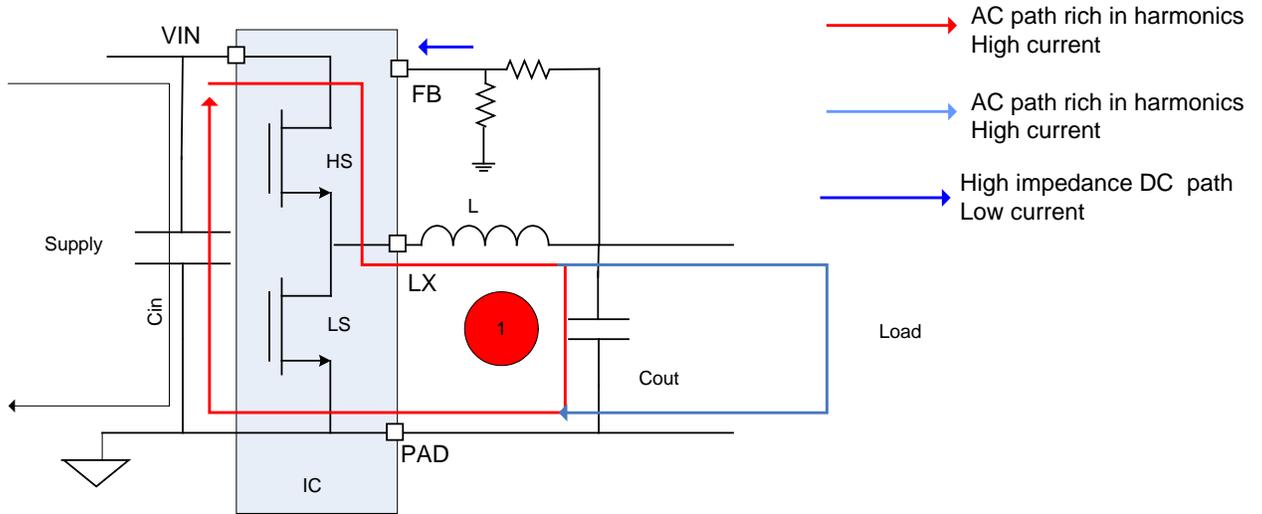


Figure 2. Current Flow through D Stage

1.7 Buck Current During (1-D) Stage (Creation of AC Pulsed Current)

The current AC path includes LS fet, output inductor and the output capacitor. The PMIC current path includes the Lx Pins and the power pad.

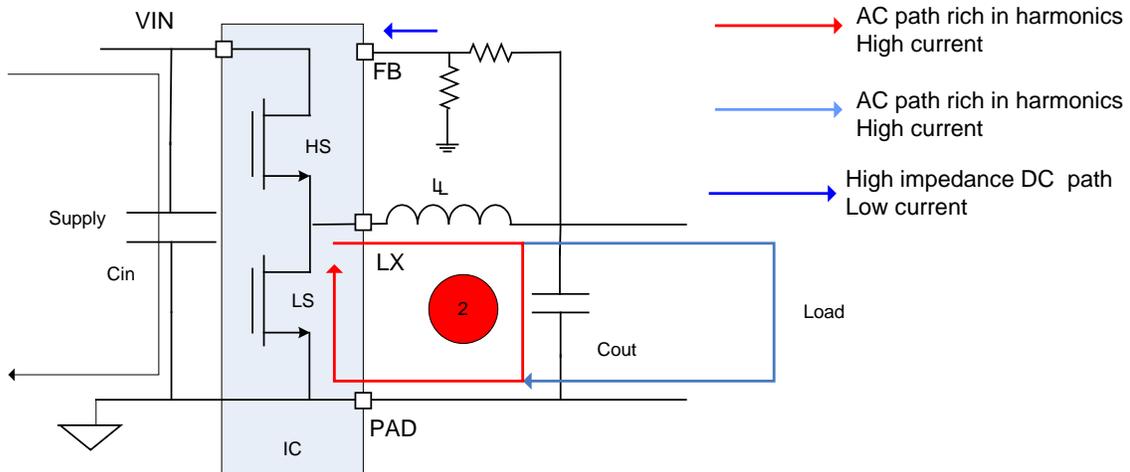


Figure 3. Buck Current During (1-D) Stage

1.8 Input Capacitor Placement

The placement and connection of input capacitor is critical. The goal is to reduce parasitic inductance between input capacitor and V_{in} input pins. Also, the input capacitor ground should be directly connected to power ground through multiple areas to reduce ground connection inductance. High parasitic inductances increase spike voltage on internal FETs during switching rise and fall time due to $L di/dt$ rule. Ultimately reducing these parasitic inductances is essential to prevent EOS events. Parasitic inductance can be reduced by making the path from input capacitor to IC V_{in} pin as short and wide as possible. The goal is to make the connection around 0.05 inches (1 to 1.5 mm). See figure 5 simple block diagram of L_{par} .

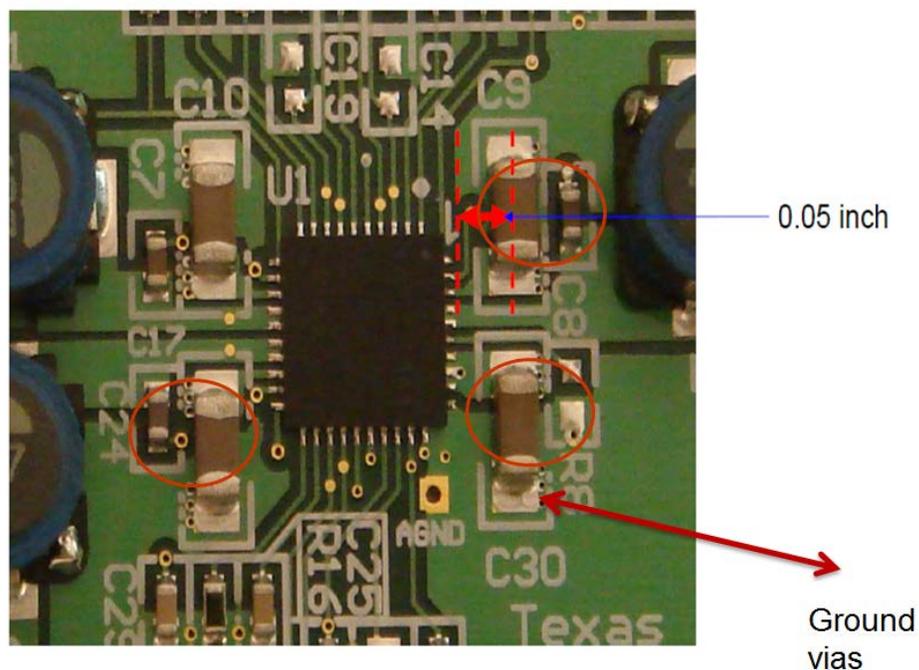


Figure 4. Input Capacitor Placement

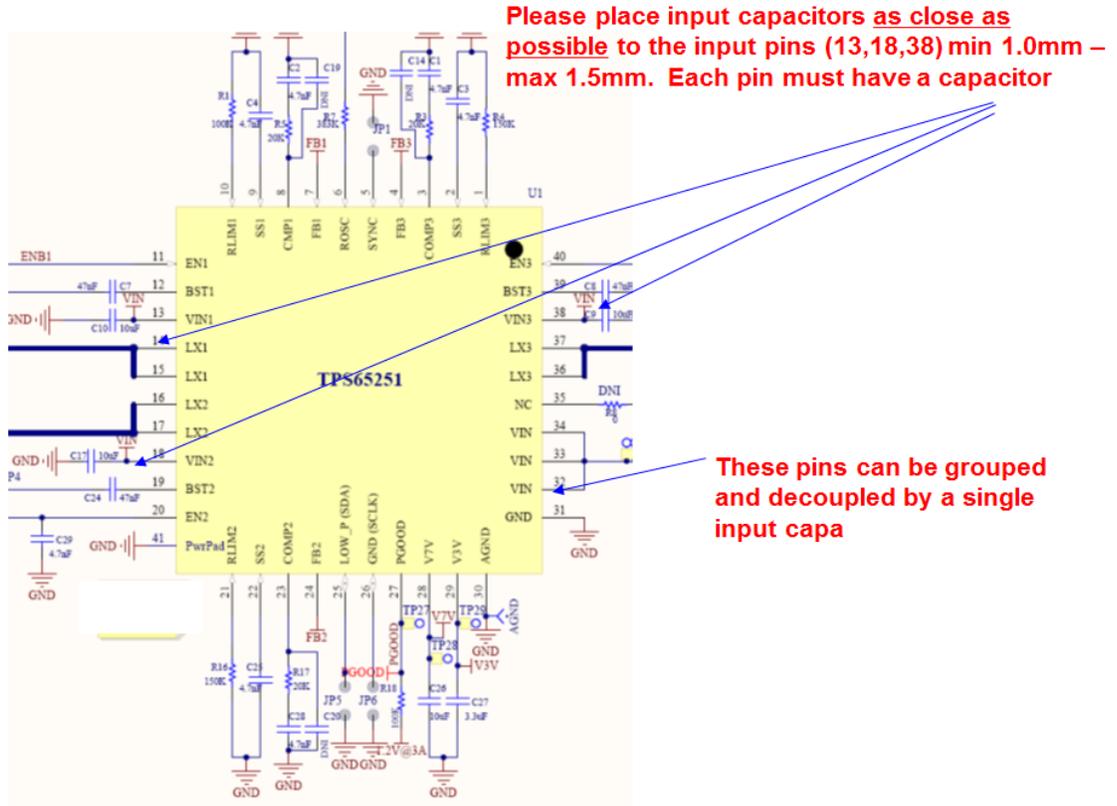


Figure 5. Capacitor Placement

1.9 Bad PCB Layout


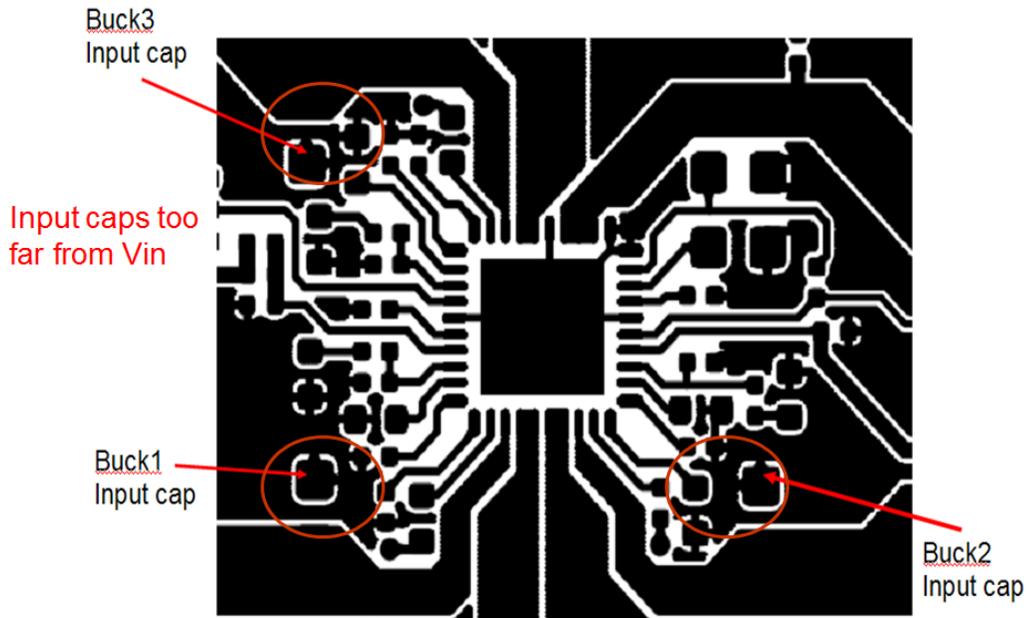


Figure 6. Bad PCB Layout 1

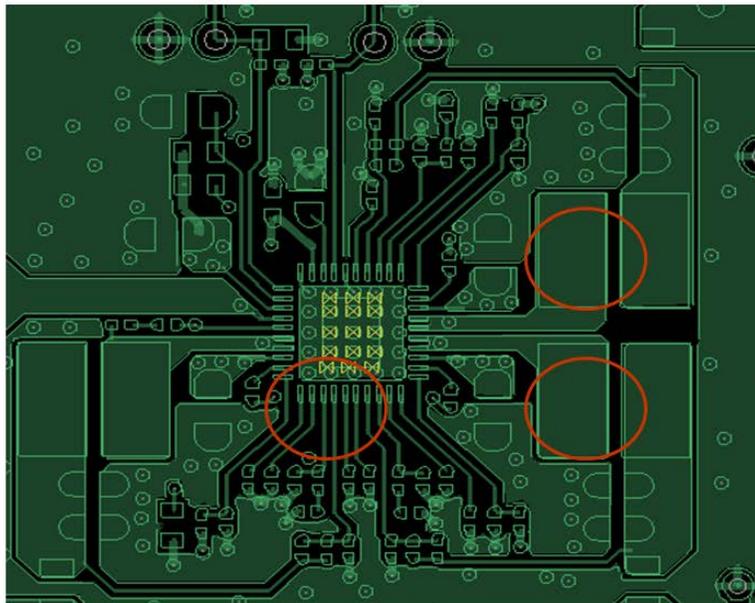

Input caps too far
from Vin
Input cap connection
to pin is too narrow

Figure 7. Bad PCB Layout 2

1.10 Output Filter Considerations 1

For the output considerations, the inductor traces should be on top of the board. Try to make inductor connection to LX width around 2.5mm. Also, make the inductor trace to LX as short as possible. The distance should be minimized from output capacitor ground to input capacitor ground and power pad. The vias should be added to the GND connection of output capacitor. If possible connect beginning of feedback divider to output capacitor. FBx trace connects to a high impedance pin. Make the trace as short as possible and avoid noisy areas (associated with AC Paths). Make sure the ground of the feedback divider connects to a clean section of the ground plane (not on the path of AC currents).


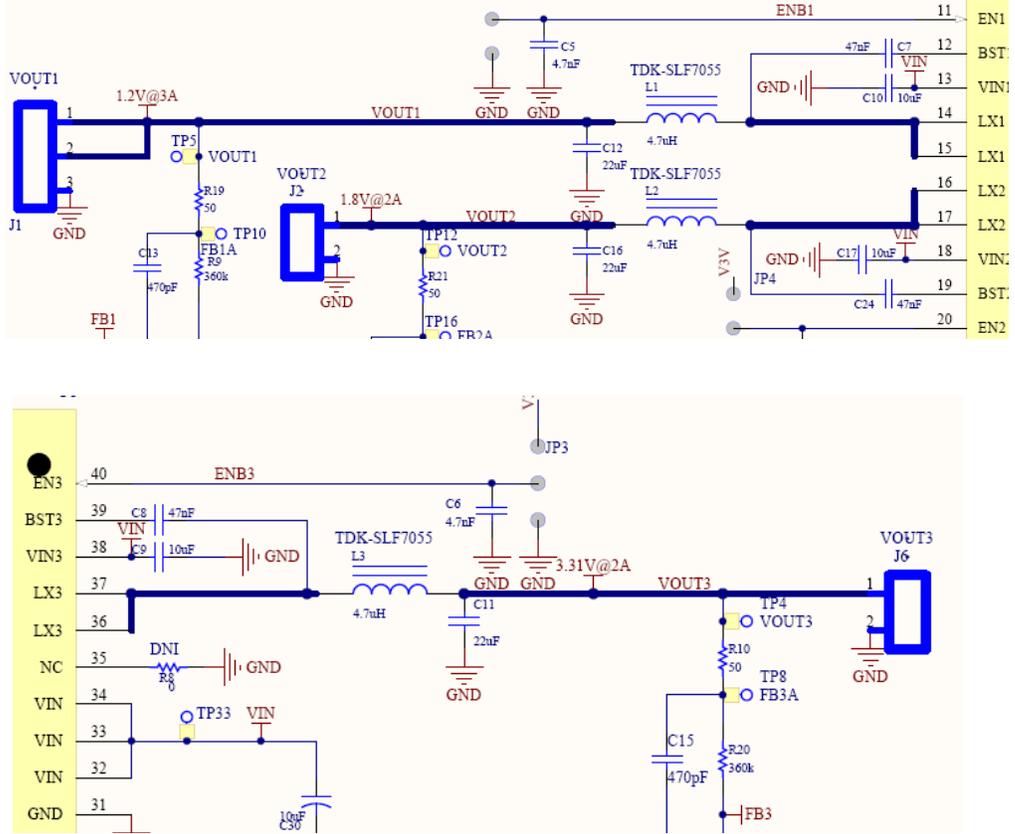


Figure 8. Output Filter Considerations 1

1.11 Output Filter Considerations 2

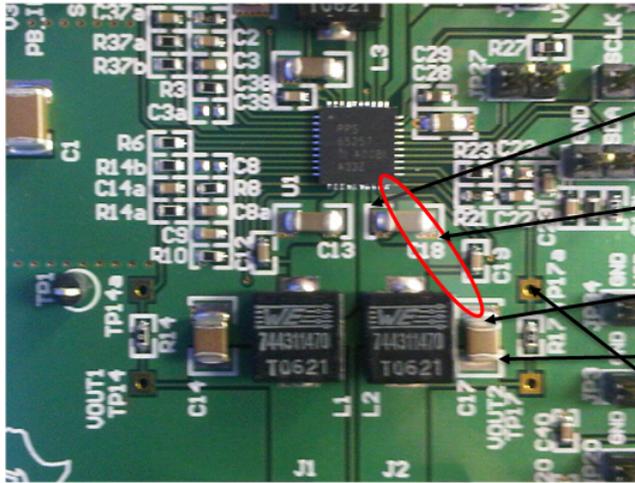


- Try to make inductor connection to LX width around 2.5mm
- Make the inductor trace to LX as short as possible
- Minimize the distance from output capacitor ground to input capacitor ground and power pad
- Add vias to GND connection of output capacitor
- If possible connect beginning of feedback divider to output capacitor
- FBx trace connects to a high impedance pin. Make the trace as short as possible and avoid noisy areas (associated with AC Paths).
- Make sure the ground of the feedback divider connects to a clean section of the ground plane (not on the path of AC currents)

Noisy and Sensitive Signals, Compensation and BST Caps.

Noisy and sensitive signals should be routed far away from each other. In switching regulators, LX switching nodes and BST (bootstrap) are among the noisiest source. Most sensitive analog signals are compensation and FB routes. Care should be taken to make sure that LX and BST signals are not coupling into FB and compensation pattern routes.

1.12 Control Components Placement

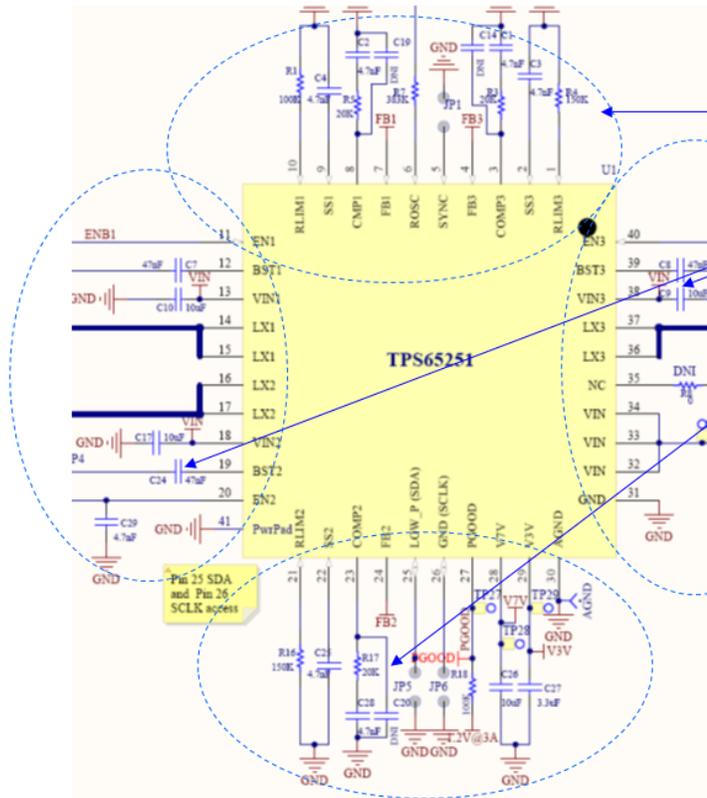

Please place the passive elements associated with the pin as possible. Applies to

- ROSC, RLIMx, SSx, ENx pins
- COMPx pins. These pins are high impedance pins, make traces as short as possible and components closer to the pin.
- Make sure connection to GND of passive components is good (add a via to GND planex next to each ground connection)
- If SYNC and Enx pins are driven by host processor, traces to the pins need to be routed away from noisy AC paths. Contemplate the possibility of guarding the traces.
- Place Bootstrap capacitors close to pin and treat connection to BSTx pin as a noisy trace.

1.13 Feedback Traces

With the feedback traces, make sure point of regulation is close to the output capacitor, and the point of regulation trace to feedback resistor is a separated trace (kelvin) connected to the feedback divider. Also, make sure the trace is short, not routed close to noise paths, and the Mid-point of the divider is a high impedance point. The trace to pin should be short. Keep connections to the top layer, avoid changing layers, and make sure divider ground is connected to a clean ground section.


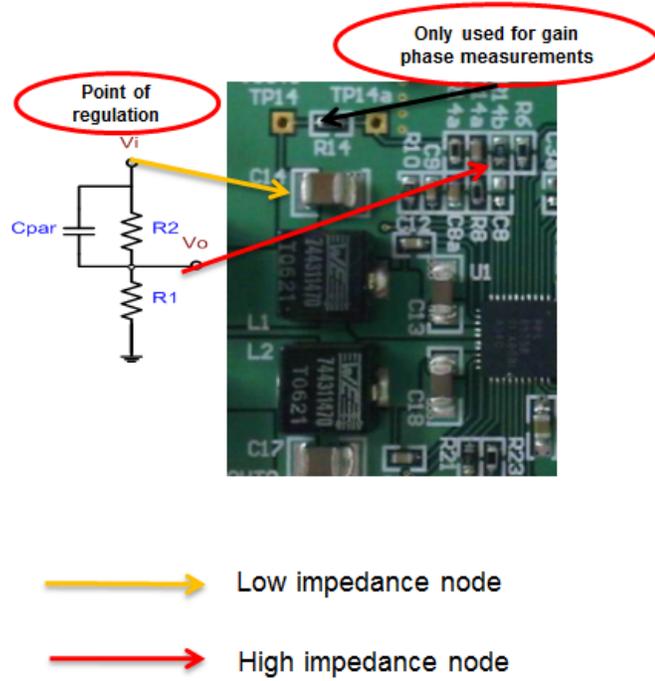


Figure 9: Feedback Traces

Appendix A. TPS6525x Layout Examples

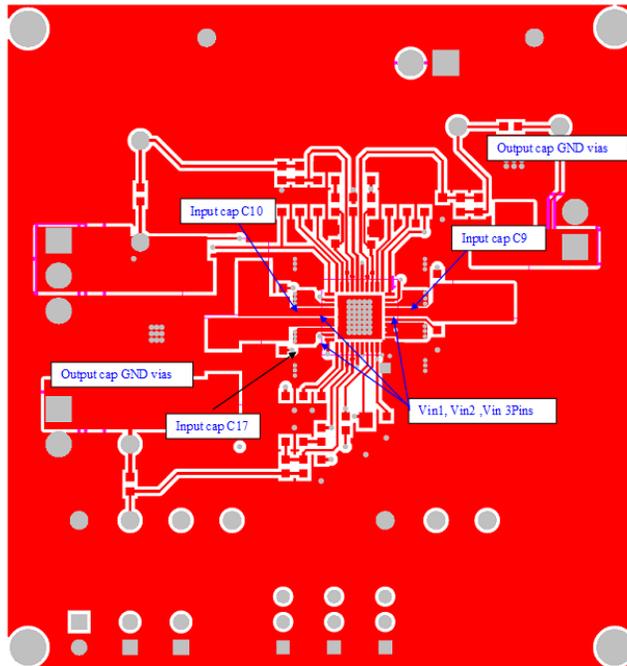

See input cap location and output cap GND vias for high current pass support.

Figure A-1. TPS65251 Top Layer

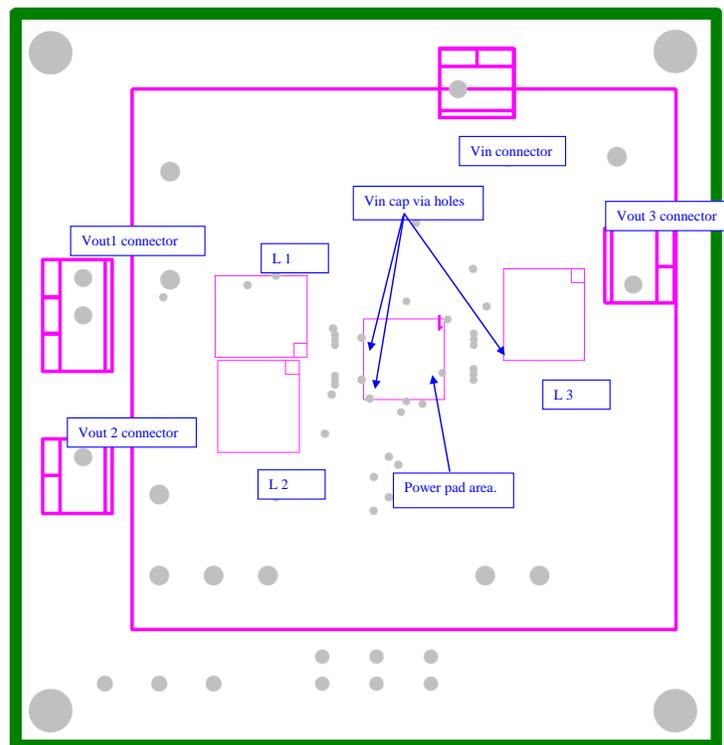


Figure A-2. TPS65251 Ground (2nd) Layer


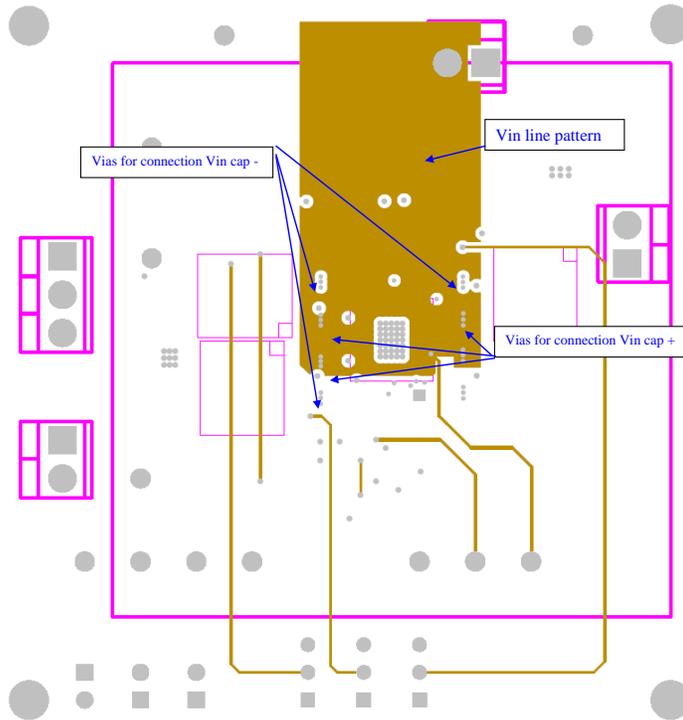


Figure A-3. TPS65251 3rd Layer

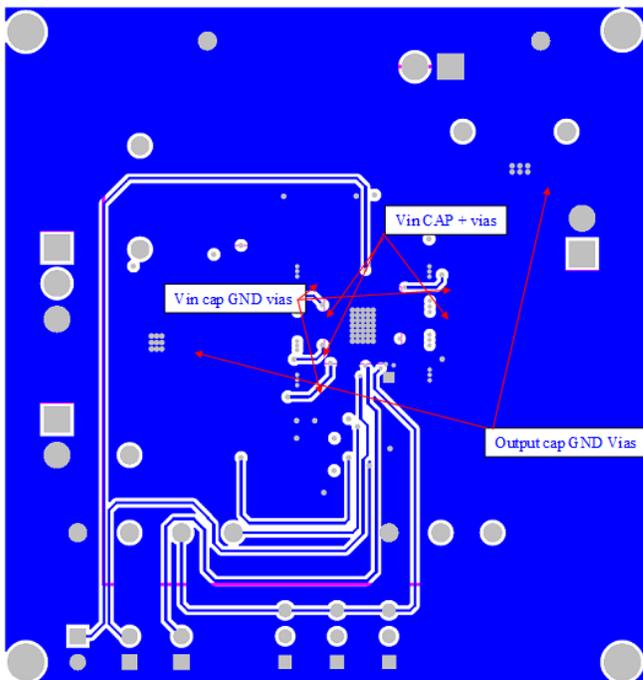

Bottom layer can be used to improve thermal dissipation by filling it with GND. Do not cut the GND plane area with traces near the TPS65251.

Figure A-4. TPS65251 Bottom Layer

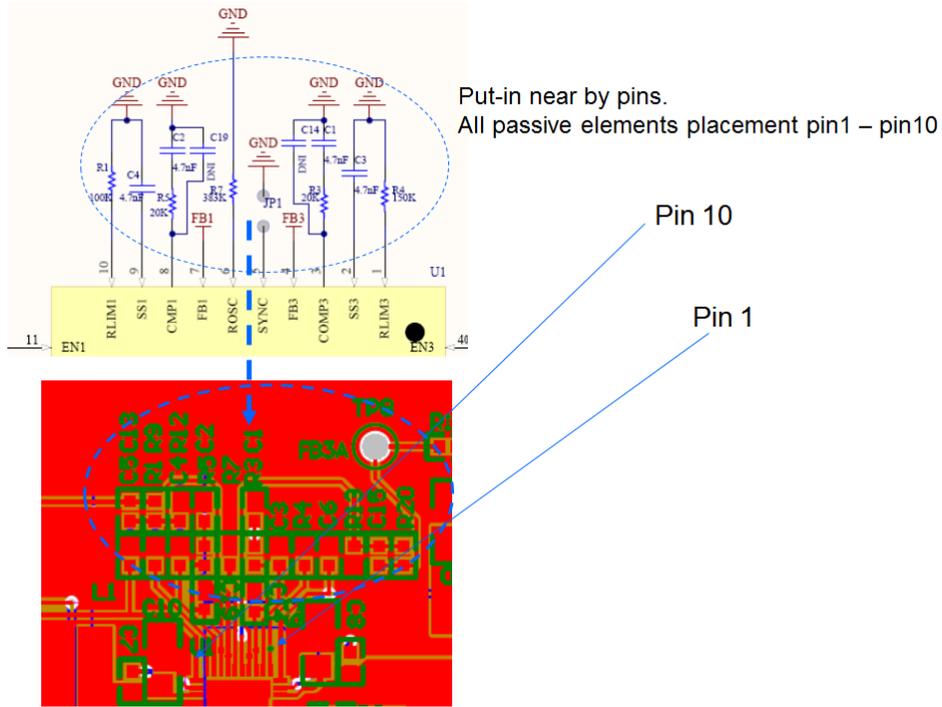


Figure A-5. TPS6251 Placement Example 1

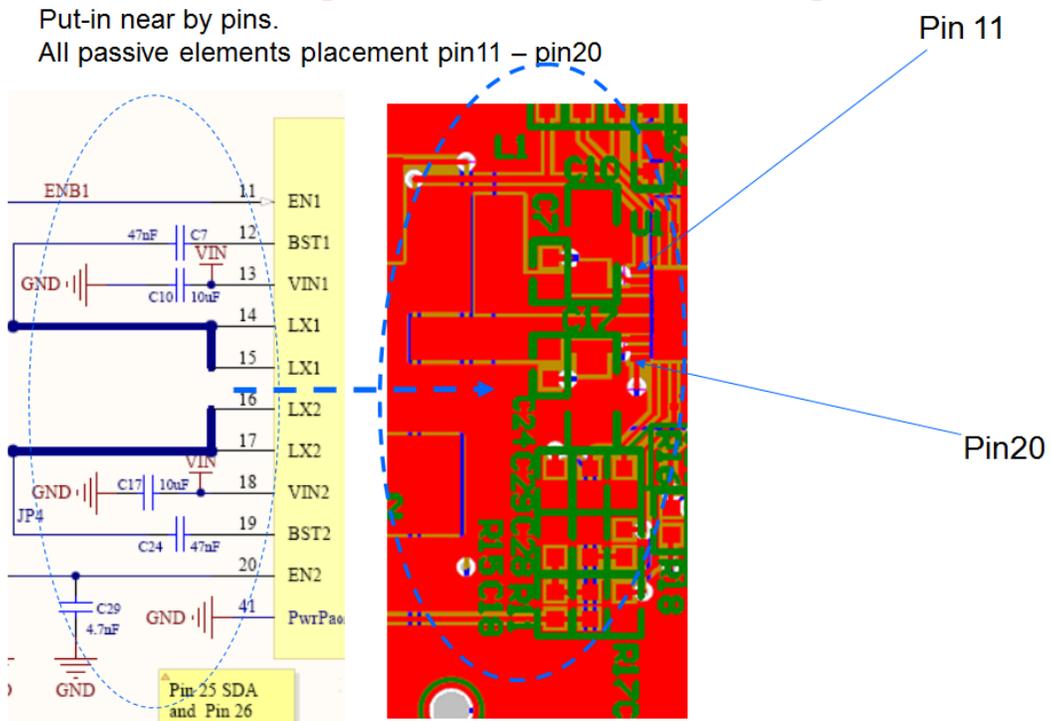


Figure A-6. TPS65251 Placement Example 2

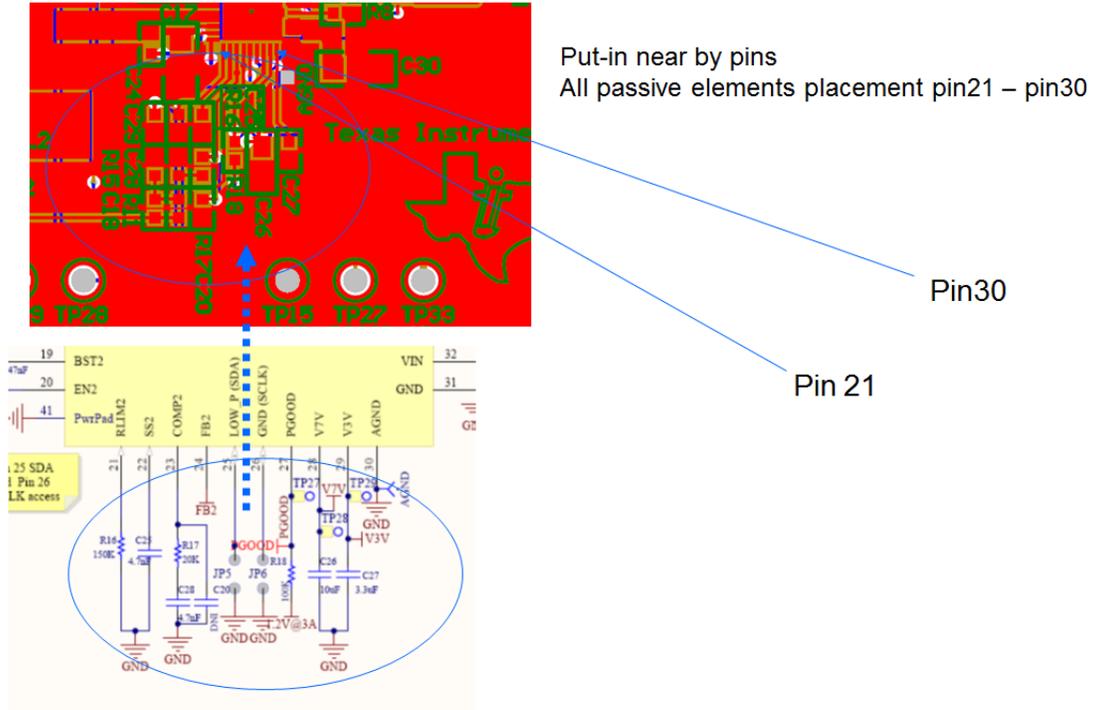


Figure A-7. TPS65251 Placement Example 3

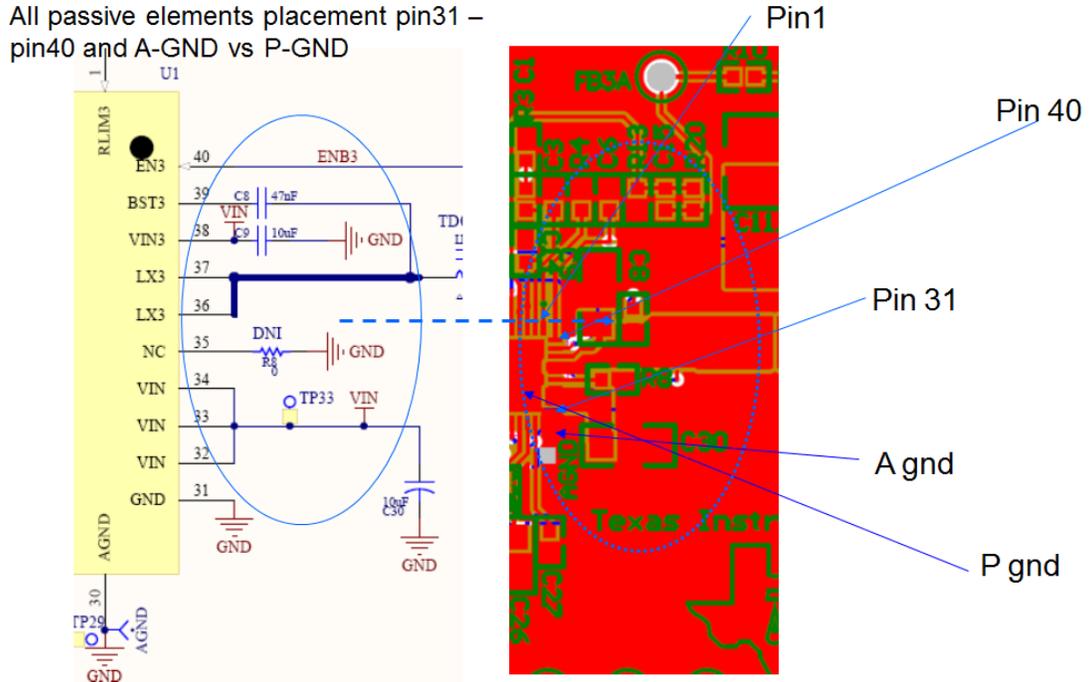


Figure A-8. TPS65251 Placement Example 4

40pin QFN package
Power PAD via holes.

Inside hole D = around less than 0.03mm

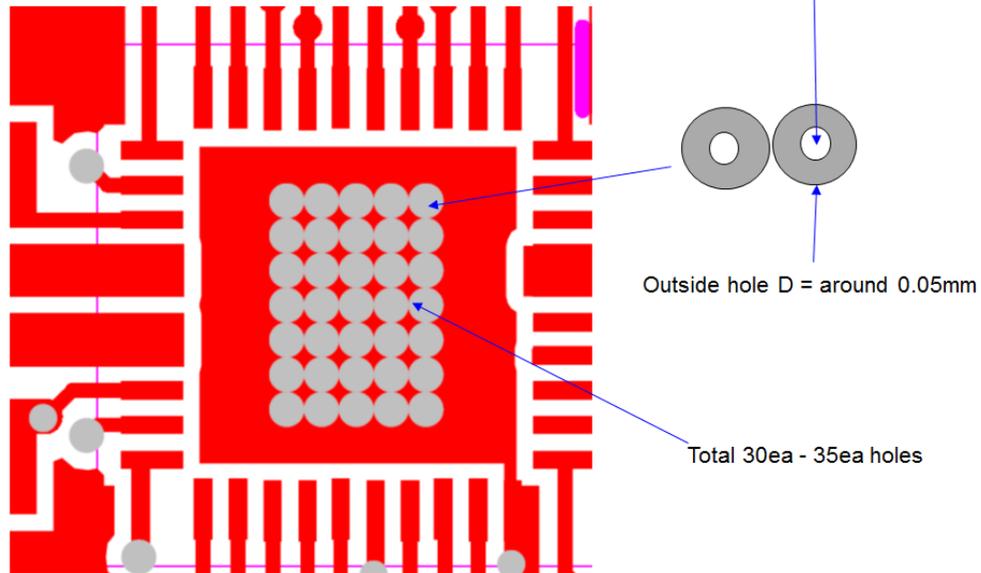


Figure A-9. TPS65251 Power Pad Example

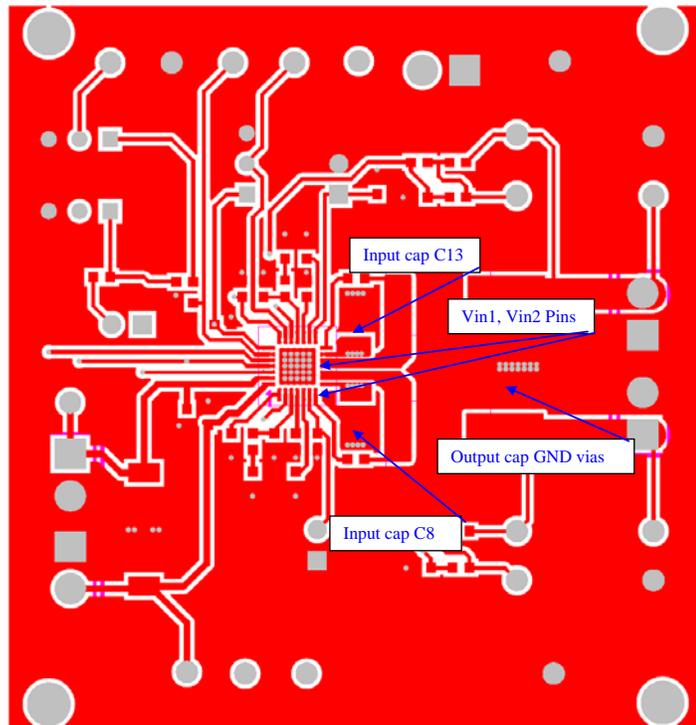


Figure A-10. TPS65252 Top Layer

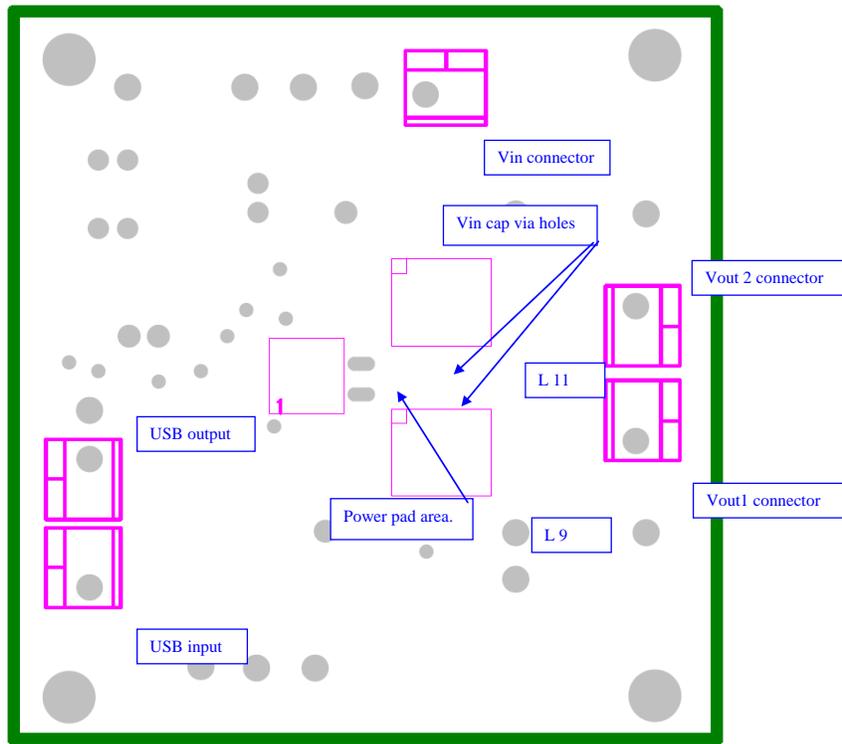


Figure A-11. TPS65252 Ground (2nd) Layer

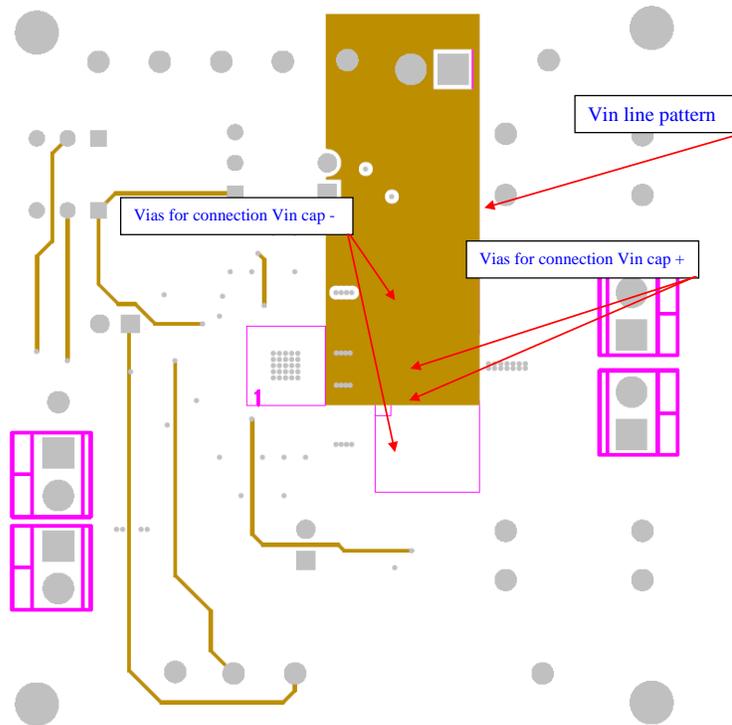


Figure A-12. TPS65252 3rd Layer

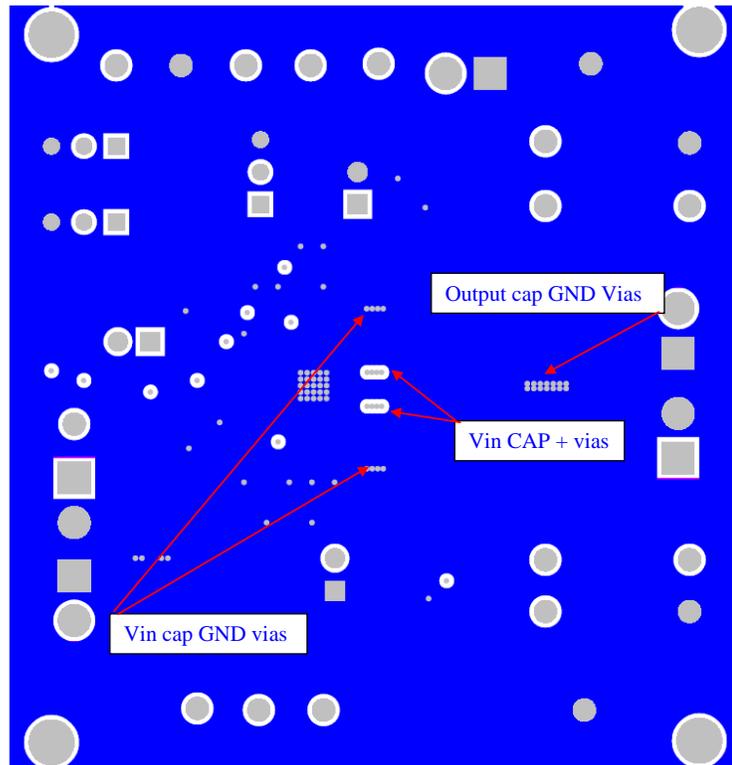


Figure A-13. TPS65252 Bottom Layer

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com