

High-Precision Negative-Voltage APD Power Supply Design with TPS61391



Helen Chen

ABSTRACT

Avalanche Photodiodes (APDs) were widely used in the LIDAR and fiber optic communication systems. However, some APDs require a high reverse voltage bias of -20 V to -150 V or even lower. Current negative power supply options are bulky while with low precision. This application note delivers a low cost, high-precision and small-sized power supply design for the negative-voltage-biased APD application with TPS61391.

Table of Contents

1 Introduction	2
2 Design Process	3
2.1 Schematic Design.....	3
2.2 Parameter Calculation.....	4
3 Test Result	5
4 Summary	8
5 References	8

List of Figures

Figure 2-1. 3.3 V Input -90 V Output Conversion with TPS61391.....	3
Figure 3-1. Input Voltage Start-up Waveform (Vin=3.3 V, Vout=-90 V).....	5
Figure 3-2. Enable Start-up Waveform (Vin=3.3 V, Vout=-90 V).....	5
Figure 3-3. Output Voltage Ripple at 1mA load Current (Vin=3.3 V, Vout=-90 V).....	6
Figure 3-4. Output Voltage Ripple at 2mA load Current (Vin=3.3 V, Vout=-90 V).....	6
Figure 3-5. Load Dynamic Performance at 2mA Load Step (Vin=3.3 V, Vout=-90 V).....	7

List of Tables

Table 3-1. Line Load Regulation.....	7
--------------------------------------	---

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

The TPS61391 is a fully integrated boost converter with an 85-V FET to convert a low input voltage to a higher voltage for biasing the APD. The TPS61391 supports an input voltage ranging from 2.5 V to 5.5 V, the maximum output voltage can reach 85 V. In some applications, for example, mechanically scanning LIDAR, robot LIDAR, or laser distance meters, negative voltage biased APD were also used, the voltage range is from -20 V to -150 V or even lower. Those negative supply voltage need to be of high precision, low ripple, and small solution size.

This application note delivers a low cost, high-precision and small-sized power supply design for the negative-voltage-biased APD application with TPS61391. The output voltage is tightly regulated at a certain value regardless of the line voltage or load current change. This design can cooperate with trans-impedance amplifier, similar to LMH32401 for light detection and ranging (LIDAR) applications, or laser distance measurement systems.

2 Design Process

2.1 Schematic Design

Figure 2-1 shows the schematic of this application note. To achieve -90 V output, two negative charge-pump cells were used. The maximum output voltage of TPS61391 can reach 85 V, so if the required negative voltage is within 0 to -80 V, only one charge pump cell needed; if the required negative voltage is within -80 to -160 V, two charge pump cells should be adopted.

To convert the negative output voltage to a positive feedback voltage, a level shift circuit is implemented. It uses a current mirror circuit built with two inexpensive PNP transistors, and one NPN transistor to regulate the output voltage. For best performance and tighter regulation accuracy, a matched pair can be used, so that the two V_{BE} can be canceled out.

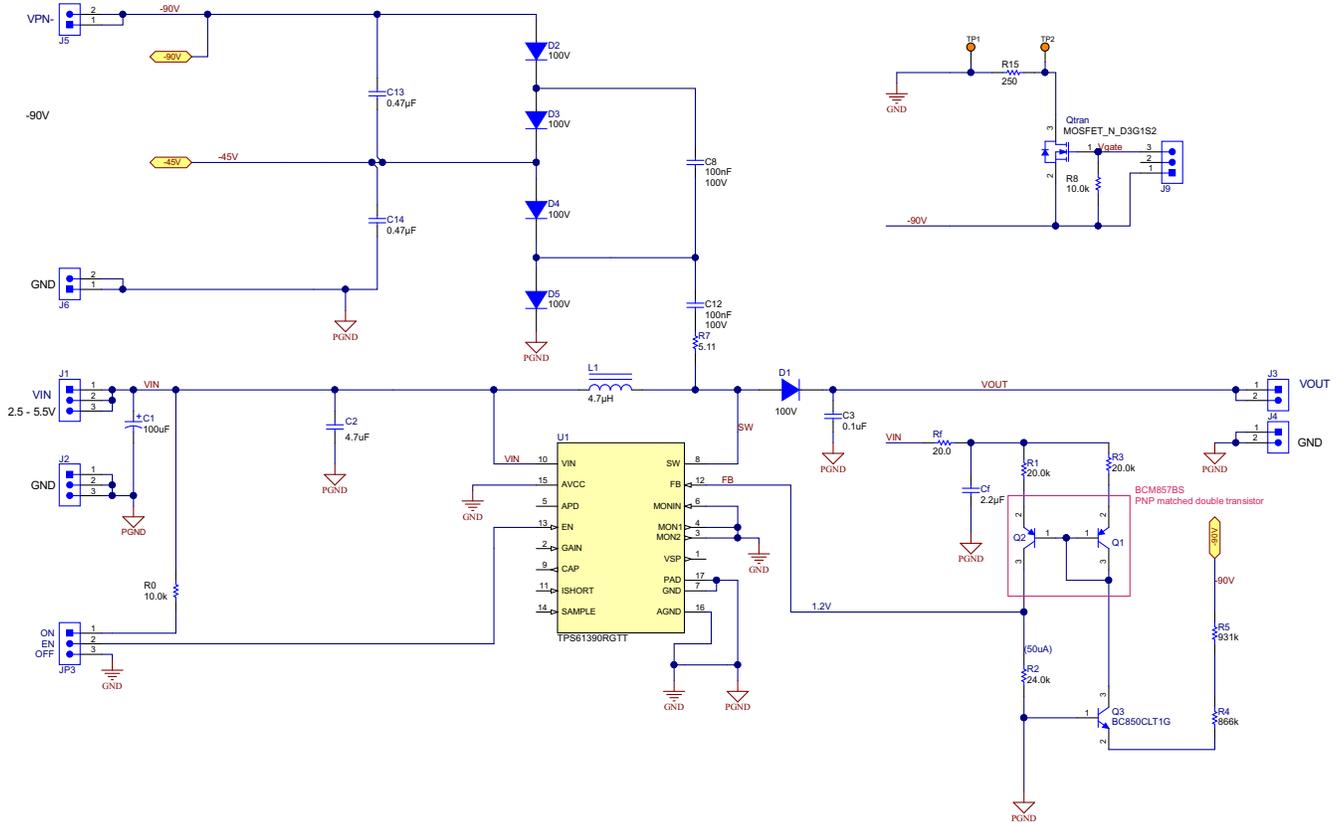


Figure 2-1. 3.3 V Input -90 V Output Conversion with TPS61391

2.2 Parameter Calculation

During normal working, the current I_{FB} flowing through R2 and Q2 equals to $V_{ref}/R2$. The current flowing through Q1 is effected by the V_{BE} mismatch of Q1 and Q2, but the V_{BE} mismatch can be reduced to a minimum level by using matched double transistors in the design. For the PNP matched double transistors, the V_{BE} mismatch is lower than 2mV, neglect this mismatch, I_{Q1} can be derived from the below equation:

$$I_{Q1} = \frac{V_{REF}}{R2} \quad (1)$$

The output voltage equals to:

$$V_{OUT} = -\frac{V_{REF}}{R2} \times (R_4 + R_5) - V_{BE} \quad (2)$$

The precision of the output voltage is mainly determined by the tolerance of the output voltage dividing network R2, R4 and R5, the tolerance of the reference voltage V_{ref} and V_{BE} . Set $I_{FB} = 50\mu A$, then $R2 = 24k$ ohm based on 1.2 V reference voltage. The value of R1 and R3 is limited by the minimum input voltage, therefore a 20k ohm resistor is chosen in this application note. The total value of R4 and R5 can be calculated by below equation:

$$R_4 + R_5 = -\frac{V_O + V_{BE}}{V_{REF}} \times R_2 = -\frac{-90 V + 0.5 V}{1.2 V} \times 24 k = 1790 \Omega \quad (3)$$

In this application note, the total value of R4 and R5 is set at 1797k ohm, which is quite close to the calculated value.

The output voltage drift caused by the V_{BE} mismatch of the PNP matched double transistors Q1 and Q2 can be calculated by the below equations:

$$V_{OUT} = -\left(\frac{V_{REF}}{R_2} \mp \frac{\Delta V_{BE}}{R_3}\right) \times (R_4 + R_5) - V_{BE} \quad (4)$$

The output voltage variation caused by the V_{BE} mismatch is:

$$\Delta V_{OUT_BE} = \pm \frac{\Delta V_{BE}}{R_3} \times (R_4 + R_5) = \pm \frac{2 mV}{20 k} \times 1797 k = \pm 179.7 mV \quad (5)$$

In this application note, BCM857BS is chosen for its <2m V small V_{BE} mismatch.

3 Test Result

Figure 3-1 shows the 3.3 V input voltage startup waveform of SLVAEZ7. The output voltage decreases monotonically from 0 V to -90 V.

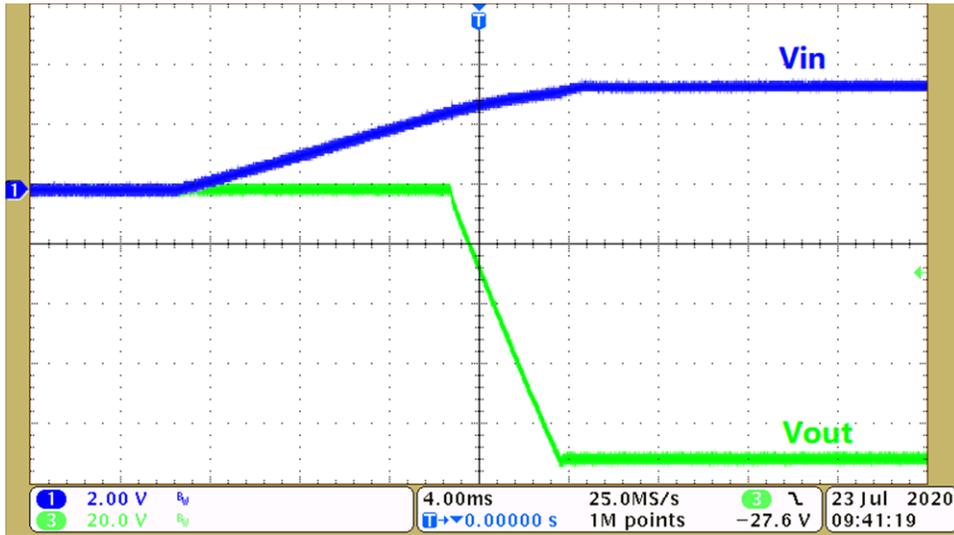


Figure 3-1. Input Voltage Start-up Waveform (Vin=3.3 V, Vout=-90 V)

Figure 3-2 shows the enable startup waveform of SLVAEZ7. The output voltage decreases monotonically from 0 V to -90 V.

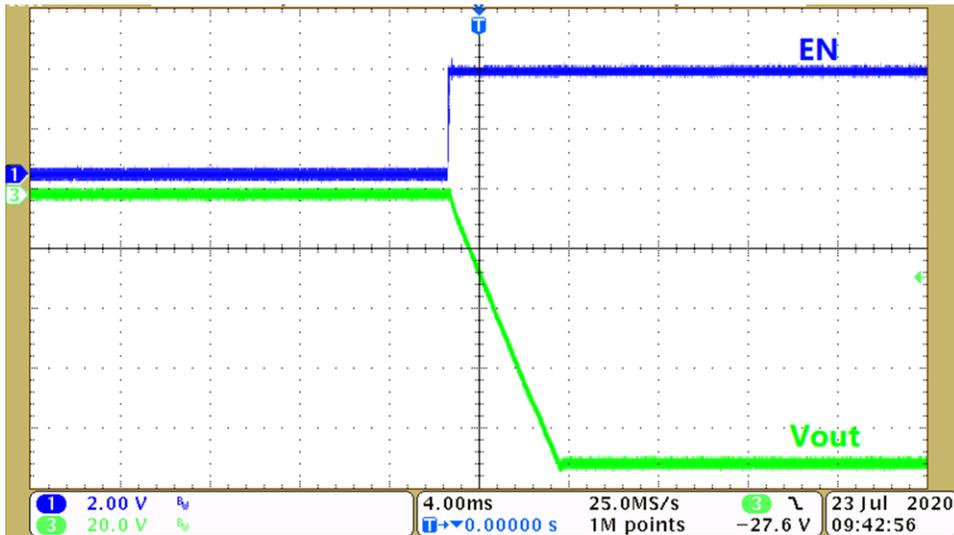


Figure 3-2. Enable Start-up Waveform (Vin=3.3 V, Vout=-90 V)

Figure 3-3 and Figure 3-4 show the output voltage ripple at 1mA and 2mA load current respectively. The output voltage ripple is around 20mV at 2mA load current based on schematic show in Figure 2-1.

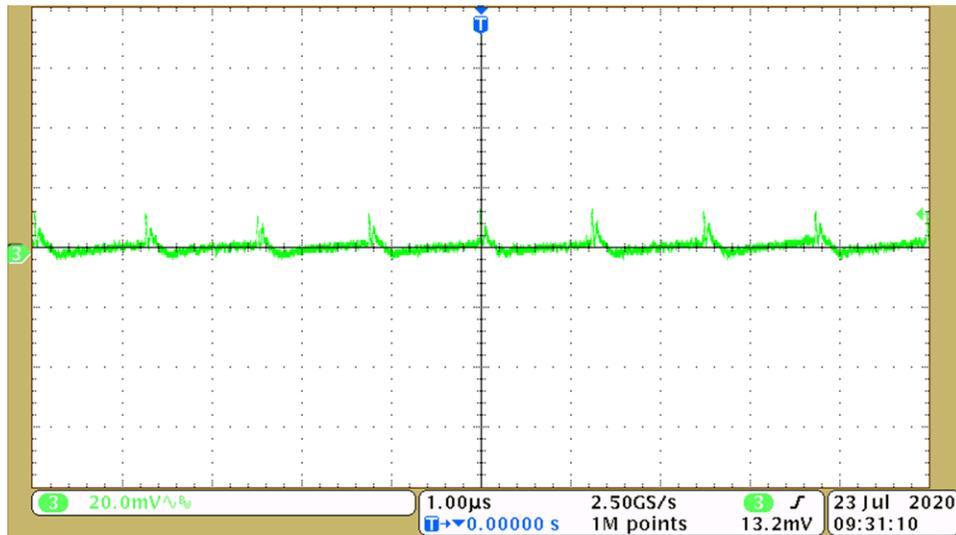


Figure 3-3. Output Voltage Ripple at 1mA load Current ($V_{in}=3.3\text{ V}$, $V_{out}=-90\text{ V}$)

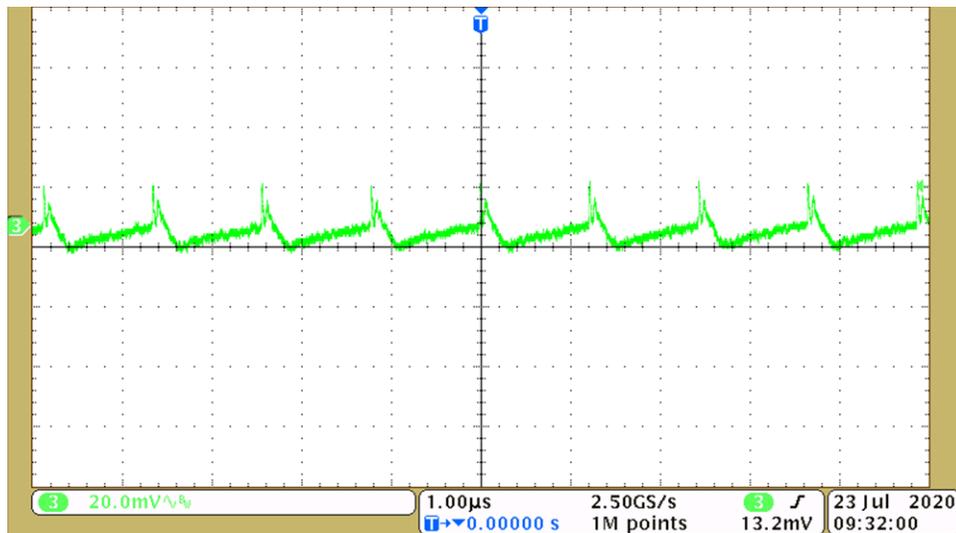


Figure 3-4. Output Voltage Ripple at 2mA load Current ($V_{in}=3.3\text{ V}$, $V_{out}=-90\text{ V}$)

Figure 3-5 shows the load dynamic performance. When V_{gate} high, there's a current flowing through R15. We control the V_{gate} high-low level to generate a dynamic load current. The voltage drop on the -90 V output is less than 500mV with a 2mA load step.

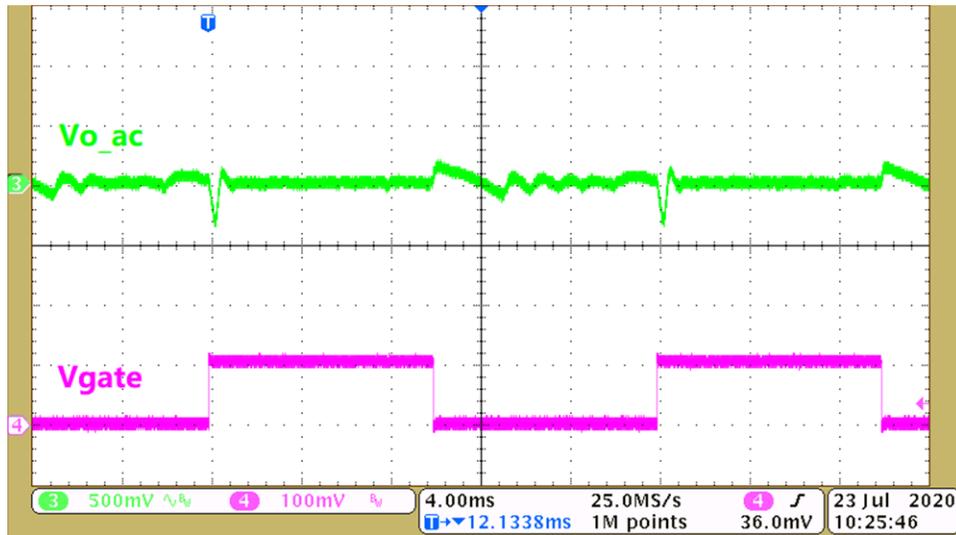


Figure 3-5. Load Dynamic Performance at 2mA Load Step ($V_{in}=3.3\text{ V}$, $V_{out}=-90\text{ V}$)

Table 3-1 shows the line and load regulation performance. The output voltage doesn't change with the load, but slightly changes with the input voltage.

Table 3-1. Line Load Regulation

Vin(V)	Vout(V)		
	Io=0mA	Io=1mA	Io=2mA
3.3	-90.1	-90.1	-90.1
4	-90.0	-90.0	-90.0
5	-89.9	-89.9	-89.9

4 Summary

This application note delivers a low cost, high-precision and small-sized power supply design for the negative-voltage-biased APD application with TPS61391. The output voltage is tightly regulated at -90 V regardless of the line load change. It is of small ripple and good dynamic performance. This circuit can cooperate with the transimpedance amplifier LMH32401 to form a detection circuit for light detection and ranging (LIDAR) applications, laser distance measurement applications or various robot LIDAR applications.

5 References

1. Texas Instruments, [85-VOUT Boost Converter with Current Mirror data sheet](#)
2. Texas Instruments, [TPS61391 85-VOUT Boost Converter with Current Mirror Integrated](#)
3. Texas Instruments, [LMH32401 450-MHz, Programmable Gain, Differential Output Transimpedance Amplifier data sheet](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated