

1

An Adaptable, Low Loss, Selective Filter And Gain Topology With Low Sensitivity To External Components

Norberto Sanchez-Dichi

ABSTRACT

Contents

1	Introduction	1
2	The Åckerberg-Mossberg Topology	2
3	Setup	2
4	Stability	3
5	Interface with the TDC1000	3
6	Measured Results	3
	References	

List of Figures

1	Åckerberg-Mossberg Topology with the Input Connected to TDC1000's LNA_OUT Pin.	2
2	AC Coupling to Ensure Optimum Performance of the Zero-cross Detect Comparator in the TDC1000	3
3	Measured Magnitude Response Using Component Values In	4

List of Tables

1	Summarzied Component Values for the Åckerberg-Mossberg Topology.	3
---	--	---

1 Introduction

Single supply electronics often require low current consumption in the few hundred picoamperes during shutdown mode. For example, battery operated ultrasonic gas flow meters also require amplifying a received signal of 200kHz by at least 20dB (in an acoustic path of length 40mm). In addition to gain, the filter must select only the frequency of the signal in interest to obtain the maximum possible accuracy and precision in time-of-flight measurements in presence of a noisy environment. TI's LMV881 23MHz low power CMOS EMI hardened operational amplifier with logic shutdown, 12 V/µs slew rate at 3.6V supply, input noise voltage of 5nV/VHz at 200kHz, and rail-to-rail output voltage swing compliments the TDC1000-GASEVM for gas flow applications. The gain requirement at a transducer's resonant frequency becomes stringent when the acoustic path increases in a flow meter system architecture and amplifier GBW is fixed. The maximum possible selectivity factor of the filter suffers and so a trade-off with gain is unavoidable. Although a cascaded filter may provide the benefit of a high-order filter, factors such as pole-zero pairing, cascading sequence, and gain distribution require consideration or else the cascaded circuit will operate with intolerable specification errors. The Åckerberg-Mossberg topology is an alternative solution that provides the benefit of independently tuning the frequency of interest, the selectivity factor, an arbitrary notch, and the gain in the passband and stopband while being relatively insensitive to passive and active component tolerances compared to other 2nd order filters. This provides the designer with the greatest flexibility to fine tune a filter for a specific ultrasonic transducer resonant frequency and acoustic distance.

All trademarks are the property of their respective owners.



The Ackerberg-Mossberg Topology

www.ti.com

2 The Ackerberg-Mossberg Topology

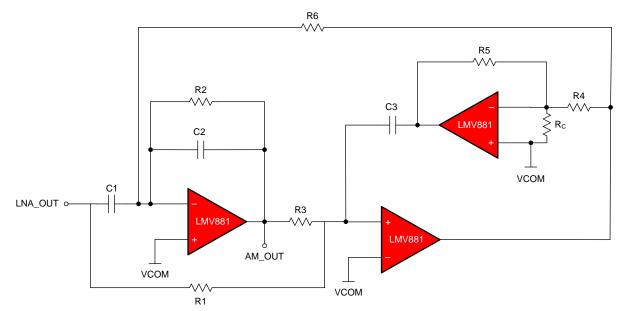


Figure 1. Ackerberg-Mossberg Topology with the Input Connected to TDC1000's LNA_OUT Pin.

The Åckerberg-Mossberg topology in Figure 1 consists of the inverting Miller Integrator and the noninverting integrator with active compensation. These two integrators compensate each other by reducing the dependence of the selectivity factor Q to the finite GBW of the LMV881. This configuration extends the usability of the LMV881 when the resonant frequencies of typical ultrasonic transducers in the market may be different or the temperature of the system varies. The Ackerberg-Mossberg topology aims to keep the selectivity factor Q constant across different transducer resonant frequencies and temperatures for best filter performance.

3 Setup

Minimum selectivity factor Q dependence on a limited bandwidth requires that:

$$C_2 = C_3 = C$$
 and $R_3 = R_6 = R$.

The gas sensor resonant frequency is:

$$f_0 = \frac{1}{2\pi \text{RC}} \tag{2}$$

The filter is stable when the input of the Miller integrator is fed by the negative feedback loop provided by the unity-gain inverter if:

 $R_4 = R_5 = R.$

The Ackerberg-Mossberg topology in Figure 1 allows for an arbitrary notch below the resonant frequency of the ultrasonic transducer. A notch may be needed to filter out interference from a nearby source e.g. CCFL. This notch does not affect the poles of the transfer function and is applied by feeding a portion of the input signal into the virtual ground node of the Miller integrator and the non-inverting integrator. It is governed by:

 $C_1=aC$ and $R_1=R/c$.

Sensitivity To External Components

The notch frequency is:

$$f_{\text{zero}} = f_0 \sqrt{\frac{c}{a}}$$

where:

a determines the high-frequency gain and

(3)

(1)

(4)



www.ti.com

c determines the low-frequency gain.

Resistor R₂=QR sets the selectivity factor. The component values are summarized in Table 1.

(6)

Component	Value	For resonant frequency	Description
R	1	7.860k	Set the cut-off frequency.
	$2\pi Cf_0$		
С	1	100pF	
	$\overline{2\pi Rf_0}$		
<i>C</i> ₁	aC	1 nF	Sets the high-frequency gain.
f _{zero}	$f_0\sqrt{\frac{c}{a}}$	60kHz	notch for EMI of CCFL
R ₁	R⁄c	7.00 kΩ	Sets the low-frequency gain.
<i>R</i> ₂	QR	66 kΩ	Sets the selectivity factor.

Table 1. Summarzied Component Values for the Åckerberg-Mossberg Topology.

4 Stability

In Figure 1, the non-inverting actively compensated integrator may become unstable due to the second parasitic pole of the LMV881. It is crucial to maintain the selectivity factor Q independent of the limited amplifier bandwidth while at the same time decreasing the phase-lead introduced by the non-inverting integrator. In this case, for the LMV881, let:

R_C=2.00 kΩ

(7)

5 Interface with the TDC1000

Although the LMV881 introduces a maximum input offset voltage of 1mV, an AC coupling interface is recommended to ensure optimum performance of the zero-cross detect comparator in the TDC1000 as shown below:

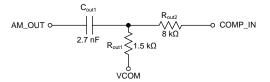


Figure 2. AC Coupling to Ensure Optimum Performance of the Zero-cross Detect Comparator in the TDC1000.

Figure 2 shows a high-pass filter that should not affect typical transducer resonant frequencies. Resistor R_out2 stabilizes the VCOM reference when the input capacitance of the zero-cross detect comparator discharges in the TDC1000.

6 Measured Results

Measured magnitude and phase responses are shown in Figure 3. The measured gain at 200kHz is 42.3dB with 3dB corners at 194kHz and 210kHz; the notch at 60kHz is at -40dB with 3dB corners deviating less than 1kHz away.

3



www.ti.com

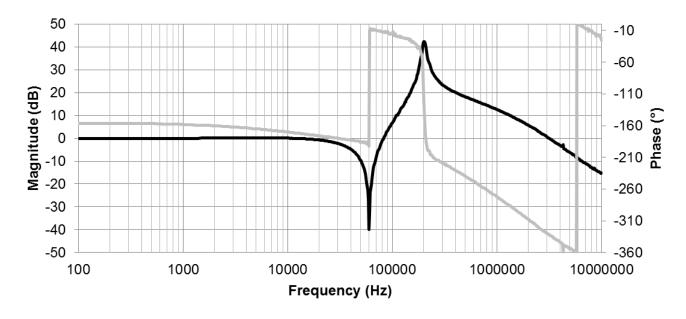


Figure 3. Measured Magnitude Response Using Component Values In Table 1

7 References

- D. Akerberg and K. Mossberg, "A versatile active RC building block with inherent compensation for the finite bandwidth of the amplifier," IEEE Trans. on Circuits and Systems, vol. CAS-21, pp. 75-78, Jan. 1974.
- 2. Martin, Ken and S. Sedra, Adel, "On the Stability of the Phase-Lead Integrator," IEEE Trans. On Circuits and Systems, vol. CAS-24, NO. 6, June 1977.
- 3. Soderstrand, M. A. et al, "Modern Active Filter Design". John Wiley & Sons Inc. Dec 31. 1981.



www.ti.com

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Cł	nanges from Original (December 2015) to A Revision	Page	ļ
•	Changed figure 1	2	2

5

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have *not* been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products		Applications	
Audio	www.ti.com/audio	Automotive and Transportation	www.ti.com/automotive
Amplifiers	amplifier.ti.com	Communications and Telecom	www.ti.com/communications
Data Converters	dataconverter.ti.com	Computers and Peripherals	www.ti.com/computers
DLP® Products	www.dlp.com	Consumer Electronics	www.ti.com/consumer-apps
DSP	dsp.ti.com	Energy and Lighting	www.ti.com/energy
Clocks and Timers	www.ti.com/clocks	Industrial	www.ti.com/industrial
Interface	interface.ti.com	Medical	www.ti.com/medical
Logic	logic.ti.com	Security	www.ti.com/security
Power Mgmt	power.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video
RFID	www.ti-rfid.com		
OMAP Applications Processors	www.ti.com/omap	TI E2E Community	e2e.ti.com
Wireless Connectivity	www.ti.com/wirelessconne	ctivity	

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2016, Texas Instruments Incorporated