

Cost-Optimized Opamp Window Comparator for Ultra-low Power PIR Motion Detectors

Bahram Mirshab, Analog Signal Chain



A window comparator is a combination of a noninverting and an inverting comparators along with two reference voltages, Vref_A and Vref_B as shown in Figure 1. When the signal at the input of the window comparator crosses either thresholds, the corresponding output changes state to an opposite voltage level at the output.

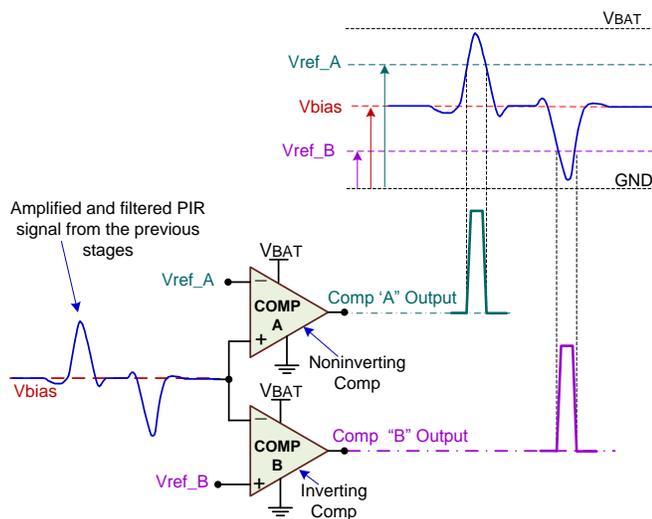


Figure 1. A Window Comparator Including a Noninverting and an Inverting Comparator and the Corresponding Inputs and Outputs

Passive Infrared (PIR) Motion Detector

An example of a system using a window comparator is a PIR motion detector shown in the block diagram of Figure 2.

Battery-powered wireless PIR motion detector sensor nodes are used in industrial, commercial and residential [Smart Building Monitoring](#) systems. They require ultra-low power analog-front-end (AFE) interface to amplify and filter small and noisy output signal of the sensor. The AFE includes a window comparator which signals a microcontroller unit (MCU) in the system the presence of motion in the sensor's field of view.

In the "gain/bandpass" stages, the PIR signal amplifies by about 96 dB in two similar sections, each having a bandpass filter with cut-off frequencies of 0.7 Hz and 10 Hz respectively.

Event-driven Sampling of PIR Sensor Signal

In some detectors, the MCU digitizes the signal for post processing and having a window comparator in the AFE circuit seems unnecessary. However, it must cycle on and off while the AFE maintains "on" continuously to save power. In this case, the comparator can be used to implement event-driven sampling. That is, the MCU starts sampling only when it receives wake-up signals from the comparator at the beginning of changes in the signal due to crossing of objects in the field of view.

A Cost-optimized Opamp Window Comparator

Normally a wireless motion monitoring network includes many sensor nodes and it is essential to design the nodes with minimal cost-optimized electronic components.

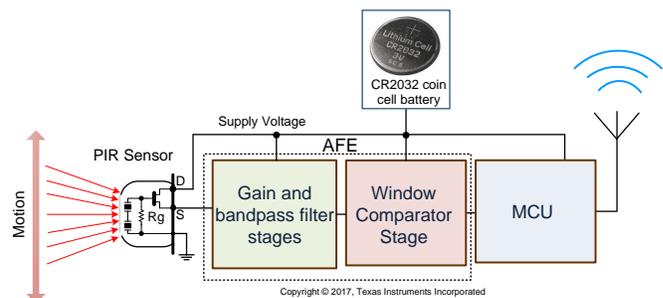


Figure 2. Block Diagram of a Typical Wireless Battery Operated PIR Motion Detector

Traditionally, the AFE is designed with a dual opamp amplifier, two individual comparator ICs and some additional passive components. However, considering PIR's low frequency signal, it is feasible to design the entire analog interface with a new 4 channel nanopower amplifier such as TLV8544— see application note [SNAA301](#).

The [TLV8544](#) has 4 channels, two opamps in the package can be used in the "gain/bandpass" stages of the AFE circuit, the remaining two (spares) can replace the individual comparator devices in the window comparator circuit as shown in [Figure 3](#).

It should be mentioned that an amplifier cannot be used as a comparator interchangeably in all applications because of amplifier's relatively long recovery time from output saturation and relatively long propagation delay due to internal

compensation. Particularly, nanopower opamps have very slow slew rate, limiting their usage as a comparator in only applications with very low frequency input signal such as PIR motion detector application.

The new nanopower **TLV8544** opamp performance, namely; rail-to-rail input/output operation, nanopower per channel current consumption (500 nA typ), very low input offset voltage (500 μ V typ), very low offset voltage drift with temperature (1.5 μ V/ $^{\circ}$ C), ultra-low input bias current (100 fA typ), ultra-low input offset current (100 fA) and optimal cost, makes it a suitable choice for the application. The input signal is biased at mid-rail to allow input signal to swing up or down from the center.

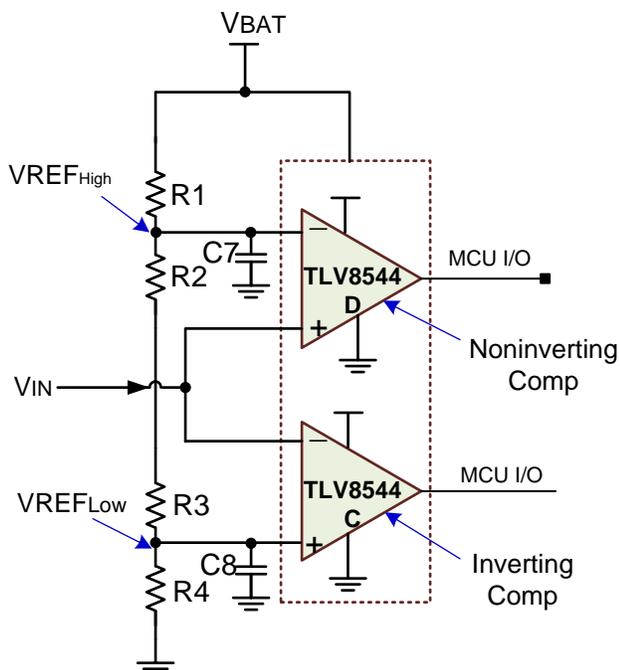


Figure 3. The Window Comparator Stage Implemented by the TLV8544 "C" and "D" Opamps

Reference Voltage Generator


Referring to [Figure 3](#), the reference voltages "VREF_{High}" and "VREF_{Low}" are generated by the divider network R1, R2, R3, and R4, where R_x = 15 M Ω . The ultra-low input bias and offset current of the TLV8544 enables choice of very large resistor values in the circuit, reducing static current consumption in the reference voltage generator circuit.

The equations for calculating the reference threshold voltages are:

$$VREF_{High} = \left(\frac{R2+R3+R4}{R1+R2+R3+R4} \right) V_{BAT}$$

$$VREF_{Low} = \left(\frac{R4}{R1+R2+R3+R4} \right) V_{BAT}$$

A PIR motion detector board, **BOOSTXL-TLV8544PIR**, is available from TI website for hands on experiment. The plots of [Figure 4](#) and [Figure 5](#) were generated using data captured from the booster board.

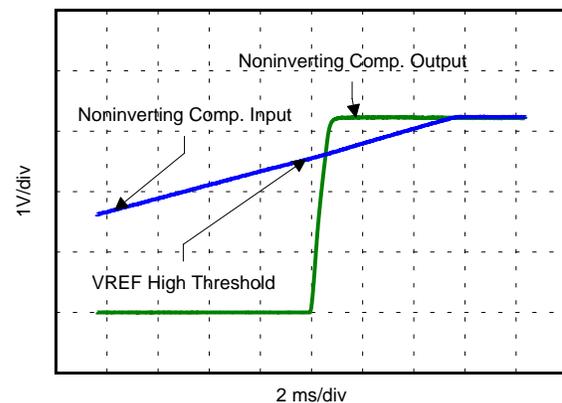


SNA4

Figure 4. Scope Plot of the Upper Cycle of the PIR Signal and the Output of the Noninverting Comparator

In [Figure 4](#), the upper cycle of the PIR signal and the output of the noninverting comparator are shown. In the circuit, the "VREF_{High}" is fixed at about 0.75 x V_{BAT} (~2.48V). As the input signal crosses the 2.48V threshold, the output of the opamp comparator changes from cutoff (slightly above ground) to saturation (slightly below V_{BAT}) in about 637 μ S,

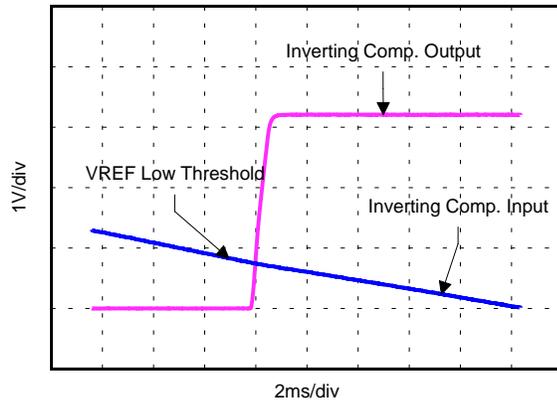The lower cycle of the PIR signal and the output of the inverting comparator are given in [Figure 5](#). In the circuit, the "VREF_{Low}" is fixed at about 0.25 x V_{BAT} (about 0.83V). As the signal crosses the 0.83V threshold, the output of the opamp comparator changes from cutoff to saturation in about the same amount time as the noninverting comparator.



SNAA

Figure 5. Scope Plot of the Lower Cycle of the PIR Signal and the Output of the Inverting Comparator

Table 1. Nanopower Amplifiers Family

Family	Channel Count	IQ/Ch	Vos (max)	Vsupply
TLV8544	4	500 nA	3.1 mV	1.7 to 3.6 V
TLV880x	1, 2	320 nA	4.5 mV	1.7 to 5.5 V
LPV81x	1, 2	425 nA	0.3 mV	1.6 to 5.5 V

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated