

# LP8863-Q1 External Component Selection Guide

Sung Ho Yoon

## ABSTRACT

The LP8863-Q1 device is an automotive LED driver with a boost or SEPIC converter to support infotainment display, automotive cluster, and lighting applications. Automotive displays often require high brightness for better visibility under bright ambient conditions; therefore, LED drivers that support automotive displays also require high output power, which often causes high voltage ripple, current limitation, and instability of the boost loop. Automotive applications also require a wide input voltage of the boost converter, making the selection of boost components difficult. This application note provides the information for boost components recommended for various LP8863-Q1 application conditions.

## Contents

1	Typical Application .....	2
2	External Components of LP8863-Q1 .....	3
3	Summary .....	10
4	References .....	10

## List of Figures

1	Simplified Schematic for LP8863-Q1 Application.....	2
2	LP8863-Q1 Feedback Divider.....	7

## List of Tables


1	Inductance Values for Switching Frequencies .....	3
2	Recommended Capacitance for Each Application Condition $C_{OUT}(\mu F)$ – Effective Output Capacitance .....	5
3	Boost Current Sense Resistor Values for Various Load Conditions (Maximum $R_{SENSE} (m\Omega)$ ) .....	9
4	Component List for LP8863Q1EVM Evaluation Board .....	10

## Trademarks

All trademarks are the property of their respective owners.

## 1 Typical Application

Figure 1 shows a connection diagram for a typical LP8863-Q1 application. The LP8863-Q1 device uses an external switching FET with gate drive controlled internally to support high power conditions. Switching FET (Q1), inductor (L1), Schottky diode (D1), and output capacitors ( $C_{OUT}$ ) are required to form a boost converter topology. The LP8863-Q1 needs more components to configure boost characteristics and device operation such as a power-line FET (Q2), input current-sensing resistor ( $R_{ISENSE}$ ), boost current-sense resistor ( $R_{SENSE}$ ), input capacitors ( $C_{IN}$ ), boost feedback resistors ( $R_{FB1}$ ,  $R_{FB2}$ ), charge-pump flying ( $C_{2X}$ )/output ( $C_{PUMP}$ ) capacitors, SD pulldown resistor ( $R_{SD}$ ) for power-line FET, and bypass capacitors ( $C_{VDD}$ ,  $C_{LDO}$ ) for power rails. Section 2 shows how to calculate the required rating of each component or generic values commonly used.

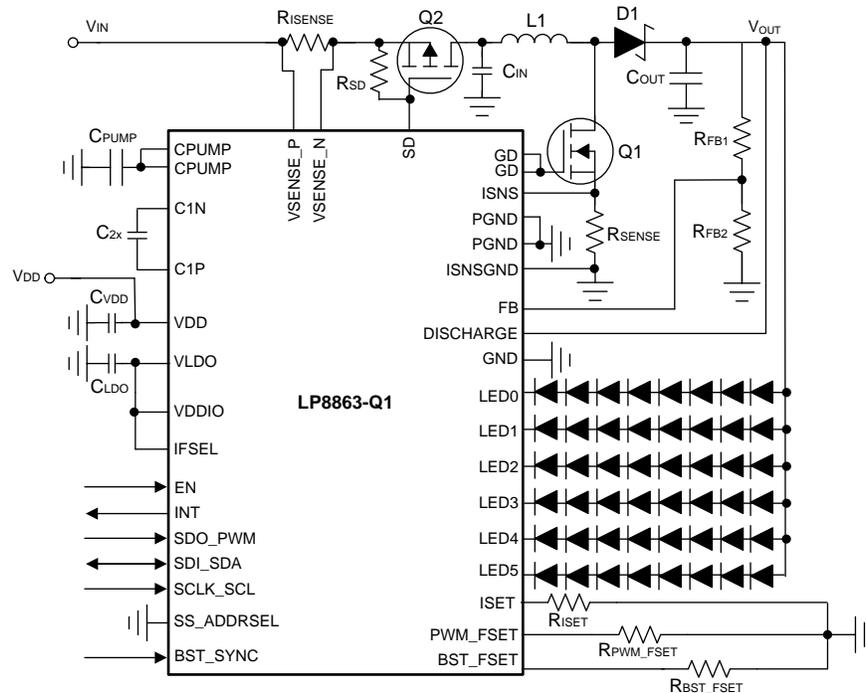

Copyright © 2017, Texas Instruments Incorporated

**Figure 1. Simplified Schematic for LP8863-Q1 Application**

## 2 External Components of LP8863-Q1

### 2.1 Inductor Selection

There are a few things to consider when selecting inductors including inductance, current rating, and DCR.

Inductance of the LP8863-Q1 circuit is provided by [Table 1](#), and all boost compensation controls are set automatically depending on switching frequency. Current rating can be calculated as following:

$$D = 1 - \frac{V_{IN(min)} \times \eta}{V_{OUT}}$$

where

- D = boost duty cycle
- $V_{IN(min)}$  = minimum input voltage
- $V_{OUT}$  = desired output voltage
- $\eta$  = efficiency of the converter, estimated at 80%. This efficiency varies with load condition, switching frequency, and components, but 80% is a good estimation to start. (1)

Maximum switching current of the boost is calculated with [Equation 2](#):

$$I_{SW(max)} = \frac{\Delta I_L}{2} + \frac{I_{OUT(max)}}{1 - D}$$

where

- $\Delta I_L$  = inductor ripple current
- $I_{OUT(max)}$  = maximum output current necessary in the application. (2)

$\Delta I_L$  can be calculated with a given inductor value:

$$\Delta I_L = \frac{V_{IN(min)} \times D}{f_s \times L}$$

where

- $f_s$  = minimum switching frequency (3)

The current rating of the inductor must be at least 25% higher than the maximum switching frequency of the boost calculated with [Equation 2](#).

The  $DCR_{(max)}$  must be lowest possible to minimize DC loss, but package size increases for lower DCR inductor. Consideration between package size and DCR is required for inductor selection.

[Table 1](#) shows the recommended inductor values for each frequency selection. The inductor values were selected from simulation/calculation results. Maximum current rating must be still calculated by preceding equations. Switching frequency is the most dominant factor when considering selection of inductor value.

**Table 1. Inductance Values for Switching Frequencies**

SWITCHING FREQUENCY (kHz)	INDUCTANCE ( $\mu$ H)
300	22
400	22
600	15
800	15
1000	10
1250	10
1667	10
2222	10

## 2.2 Output Capacitor Selection

The voltage rating of the capacitors must be at least 25% higher than output voltage level to consider the variation of each component (50% or higher is recommended). Output capacitance required for a desired output voltage ripple is shown in [Equation 4](#):

$$C_{\text{OUT}(\text{min})} = \frac{I_{\text{OUT}(\text{max})} \times D}{f_s \times \Delta V_{\text{OUT}}}$$

where

- $C_{\text{OUT}(\text{min})}$  = minimum capacitance
  - $I_{\text{OUT}(\text{max})}$  = maximum output current of the application
  - $D$  = duty cycle calculated with [Equation 1](#)
  - $f_s$  = minimum switching frequency of the converter
  - $\Delta V_{\text{OUT}}$  = desired output voltage ripple
- (4)

The ESR of the output capacitor (generally electrolytic capacitors) adds more ripple with [Equation 5](#):

$$\Delta V_{\text{OUT}(\text{ESR})} = \text{ESR} \times \left( \frac{I_{\text{OUT}(\text{max})}}{1 - D} + \frac{\Delta I_L}{2} \right)$$

where

- $\Delta V_{\text{OUT}(\text{ESR})}$  = additional output voltage ripple due to ESR of capacitor
  - ESR = equivalent series resistance of the used output capacitor
  - $I_{\text{OUT}(\text{max})}$  = maximum output current of the application
- (5)

Output capacitors also affect boost stability as well as inductor value. High enough capacitance results in decent (> 45 to 50 degrees) phase/gain margin. As a typical value, TI recommends using 2 × 33-μF electrolytic capacitors and 2 × 10-μF ceramic capacitors for most application conditions; these components were used on LP8863-Q1EVM. 2 × 33-μF electrolytic capacitors ensure high enough capacitance to reduce voltage ripple and increase boost stability. Electrolytic capacitors must support high ripple current of boost output stage, which can be a few Amps depending on load conditions. Generally, Al-polymer capacitors support higher ripple current compared to regular Al electrolytic capacitors. This ripple current must be checked on capacitor manufacturer's data sheet for best selection.

Capacitance of ceramic capacitors degrade linearly with DC bias voltage. Therefore, TI recommends using ceramic capacitors with high enough (50% to 100% higher) voltage rating compared to application conditions. [Table 2](#) shows recommended capacitor values for each application condition. These are simulated values to make high enough stability (phase margin > 45 to 50 degrees) when the correct boost-current-sensing resistor values for each application condition are used, which is explained in [Section 2.7](#). These values can be used as initial references and increased to better support warm or cold crank conditions. Effective capacitance must be considered for ceramic capacitors, which is de-rated by bias voltages. Actual required capacitance required is more than calculated values. Two 10-μF ceramic capacitors help reduce the ESR effect of electrolytic capacitors, which can affect voltage ripple.

**Table 2. Recommended Capacitance for Each Application Condition**  
**C<sub>OUT</sub> (μF) – Effective Output Capacitance**

V <sub>IN</sub> (V)	V <sub>OUT</sub> (V)	I <sub>LOAD</sub> (A)	SWITCHING FREQUENCY (kHz)			
			300/400	600/800	1000/1250	1650/2220
INDUCTOR			22 μH	15 μH	10 μH	10 μH
6 to 9	20 to 27	0.4	3 × 10	3 × 10	3 × 10	3 × 10
		0.6				
		0.9				
	28 to 35	0.4	3 × 10	3 × 10	3 × 10	3 × 10
		0.6				
		0.9				
	36 to 43	0.4	3 × 10 (V <sub>IN</sub> 6 V – 4 × 10)	3 × 10	4 × 10	4 × 10
		0.6				
		0.9				
10 to 15	20 to 27	0.4	2 × 10	2 × 10	2 × 10	2 × 10
		0.6				
		0.9				
	28 to 35	0.4	2 × 10	2 × 10	2 × 10	2 × 10
		0.6				
		0.9				
	36 to 43	0.4	2 × 10	2 × 10	2 × 10	2 × 10
		0.6				
		0.9				
16 to 21	21 to 27	0.4	1 × 10	1 × 10	2 × 10	2 × 10
		0.6				
		0.9				
	28 to 35	0.4	2 × 10	2 × 10	2 × 10	2 × 10
		0.6				
		0.9				
	36 to 43	0.4	2 × 10	2 × 10	2 × 10	2 × 10
		0.6				
		0.9				
22 to 27	28 to 35	0.4	1 × 10	1 × 10	2 × 10	2 × 10
		0.6				
		0.9				
	36 to 43	0.4	1 × 10	1 × 10	2 × 10	2 × 10
		0.6				
		0.9				

### 2.3 Input Capacitor Selection

The voltage rating of capacitors must be at least 25% higher than output voltage level to consider the variation of each component (50% or higher is recommended for ceramic capacitors). Input capacitance is not critical for boost operation, but it must support enough filtering for input power and charges for both normal operation and transition state such as warm/cold crank conditions. TI recommends same capacitance with output capacitance for a simple application, but input capacitance can be reduced monitoring input power requirements.

## 2.4 Output Diode Selection

The voltage rating of the output diode must be at least 25% higher than the output voltage level to consider the variation of each component. A diode with short transition/recovery time and low forward voltage, such as a Schottky diode, must be selected to reduce power loss. The forward voltage of Schottky diodes is lower than regular PN-junction diodes. It is important to make sure that the forward voltage of a Schottky diode at maximum current at application is as low as possible. Forward voltage itself affects power loss by  $P = V \times I$ , and if this increases with load current, reverse recover time is also increased, which often causes high switching current across the switching FET. A forward voltage  $< 0.5\text{ V}$  for all target conditions is necessary.

## 2.5 Switching FET Selection

The switching FET is a critical component to decide power efficiency of boost DC-DC converter. A few things to consider when selecting a switching FET are switching voltage, current rating,  $R_{\text{DS(on)}}$ , power dissipation, thermal resistance, input capacitance, rise/fall time, total gate charge, Miller voltage, and gate-input resistance.


- Voltage rating must be at least 25% higher than boost output voltage.
- Current rating of switching FET can be obtained from the calculation of maximum switching current for inductor selection. Current rating of switching FET must be at least 25% higher than calculated value.
- $R_{\text{DS(on)}}$  must be as low as possible. Typical value used for LP8863-Q1 applications is  $< 20\text{ m}\Omega$ .
- Maximum power dissipation must be at least a few times higher than expected power loss on the FET
- Thermal resistance (for example,  $R_{\theta(\text{JA})}$ ) must be also low to dissipate heat from power loss on switching FET, but lower thermal resistance means a larger package size, thus this trade-off must be considered.
- Input capacitance, rise/fall time, total gate charge, and Miller voltage affect switching speed of switching FET. Typical ranges of each parameter are:
  - Input capacitance:  $< 1000\text{ pF}$
  - Rise/fall time: a few ns — approximately  $1 \times \text{ns}$
  - Total gate charge: a few nC — approximately  $1 \times \text{nC}$
  - Miller voltage:  $2\text{ V}$  to  $3\text{ V}$
- Input resistance of switching FET must be considered not to make gate drive current higher than 2.5 A. Gate drive current can be calculated by  $V_{\text{GD}} / (G_{\text{DRDS(on)}} + \text{total resistance to gate input of SW FET})$ . If gate drive current is higher than 2.5 A with switching FET, add a series resistor on gate drive path to lower current.

## 2.6 Power-Line FET Selection

A power-line FET can be used to protect boost components in case of any fault conditions such as an overcurrent state. The power-line FET disconnects input power from boost input, therefore prevents excessive current flow into LP8863-Q1 device itself and other boost components. A P-type MOSFET is used for power-line FET and there are no requirements for switching speed. The voltage rating of a power-line FET must be at least 25% higher than input voltage range. Low  $R_{\text{DS(on)}}$  is important to reduce power loss on the FET. Typical value is  $< 20\text{ m}\Omega$ .
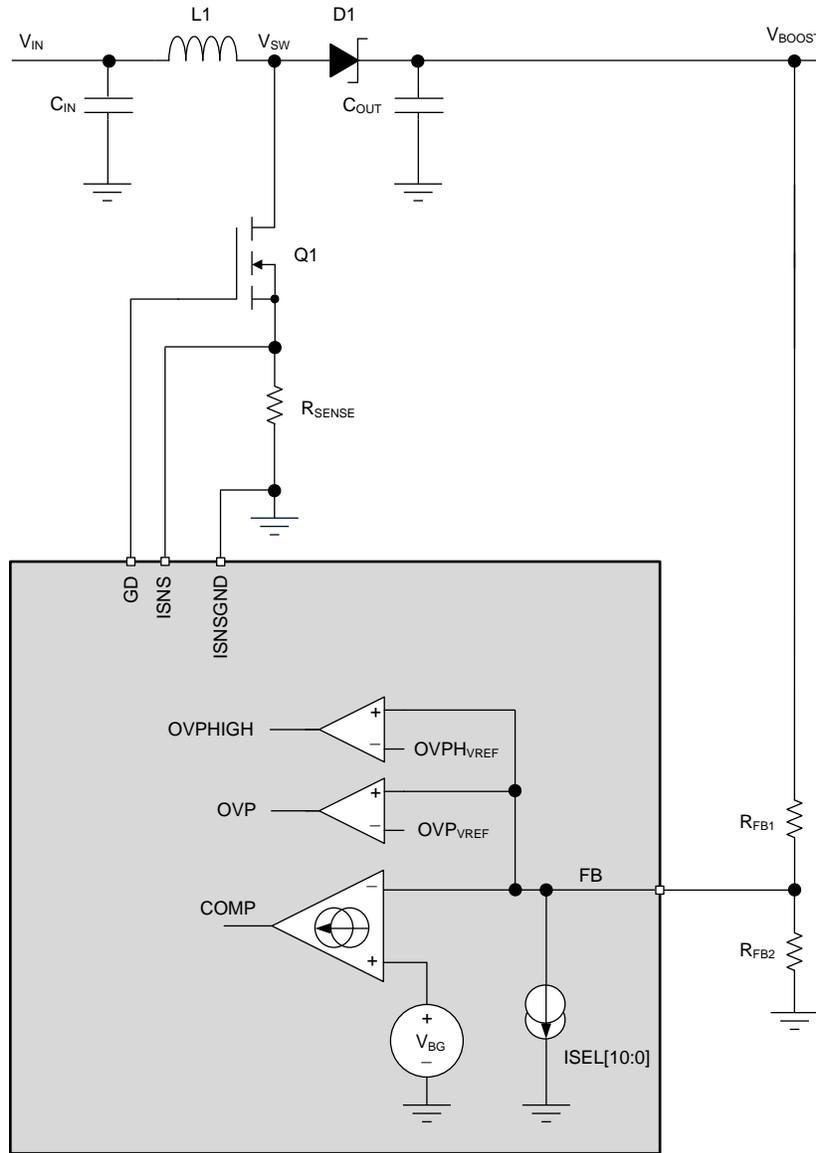
## 2.7 Boost Feedback Divider Resistor Selection

Two resistor values on the FB input of the LP8863-Q1 device determine maximum boost output voltage. [Figure 2](#) shows the structure of the feedback input block.



Copyright © 2017, Texas Instruments Incorporated

**Figure 2. LP8863-Q1 Feedback Divider**

Equation 6 and Equation 7 show calculations for maximum output voltage:

$$V_{OUT\_MAX} = \left( \frac{V_{BG}}{R_{FB2}} + I_{SEL\_MAX} \right) \times R_{FB1} + V_{BG} \quad (6)$$

$$V_{OUT\_MIN} = \left( \frac{V_{BG}}{R_{FB2}} + I_{SEL\_MIN} \right) \times R_{FB1} + V_{BG}$$

where

- $V_{BG} = 1.21 \text{ V}$
  - $I_{SEL\_MAX} = 38.381 \text{ } \mu\text{A}$
  - $I_{SEL\_MIN} = 0 \text{ } \mu\text{A}$
- (7)

For example, default values on the EVM are:

$R_{FB1} = 910 \text{ k}\Omega$  and  $R_{FB2} = 100 \text{ k}\Omega$ ;  $V_{OUT\_MAX} = 47.15 \text{ V}$ ,  $V_{OUT\_MIN} = 12.22 \text{ V}$ .

## 2.8 SD Pulldown Resistor Selection

SD is the pulldown signal to enable the power-line FET to connect external power source to boost input. SD current through resistor between source and gate makes voltage difference ( $V_{GS}$ ) to turn on the FET. The typical value of SD pulldown current is  $292 \text{ } \mu\text{A}$ , and  $V_{GS} = 292 \text{ } \mu\text{A} \times R_{SD}$  must be higher than the maximum  $V_{GS}$  specification of the power-line FED to turn it on correctly.

## 2.9 Input Current Sense Resistor Selection

The input current sense resistor ( $R_{ISENSE}$ ) is used as a sensor to detect input overcurrent fault. An overcurrent condition is detected when the voltage across the sensor resistor is higher than  $230 \text{ mV}$ . Typical sense resistor value is  $20 \text{ m}\Omega$ , so the overcurrent limit becomes  $11.5 \text{ A}$ . This sense resistor value can be increased to lower the overcurrent limit as needed for each application; for example,  $230 \text{ mV/OCP limit} = \text{sense resistor value}$ .

## 2.10 Boosting Switch Current Sense Resistor Selection

Boost current sense resistor ( $R_{SENSE}$ ) is used as a sensor to decide boost overcurrent condition (not a fault) for every boost switching cycle. The typical resistor value is  $15 \text{ m}\Omega$  for maximum current condition  $13.5 \text{ A}$ , and this sense resistor value can be increased to lower overcurrent limit. Be careful when increasing resistor value because it affects the maximum duty cycle of boost. [Table 3](#) shows boost current sense resistor values for various load conditions.

**Table 3. Boost Current Sense Resistor Values for Various Load Conditions  
(Maximum  $R_{SENSE}$  (m $\Omega$ ))**

$V_{IN}$ (V)	$V_{OUT}$ (V)	$I_{LOAD}$ (A)	SWITCHING FREQUENCY (kHz)			
			300/400	600/800	1000/1250	1650/2220
INDUCTOR			22 $\mu$ H	15 $\mu$ H	10 $\mu$ H	10 $\mu$ H
6 to 9	20 to 27	0.4	50	59	62	60
		0.6	40	45	45	42
		0.9	27	30	28	28
	28 to 35	0.4	40	47	46	45
		0.6	30	33	31	30
		0.9	23	25	22	21
	36 to 43	0.4	36	40	36	35
		0.6	25	28	24	23
		0.9	15	20	16	15
10 to 15	20 to 27	0.4	72	90	91	98
		0.6	58	65	65	68
		0.9	40	45	45	47
	28 to 35	0.4	51	70	71	75
		0.6	45	50	51	52
		0.9	34	38	35	35
	36 to 43	0.4	50	59	59	61
		0.6	40	45	41	42
		0.9	30	32	31	28
16 to 21	21 to 27	0.4	90	120	128	145
		0.6	79	94	96	105
		0.9	60	69	69	74
	28 to 35	0.4	76	96	98	110
		0.6	60	72	73	80
		0.9	45	53	53	56
	36 to 43	0.4	65	79	81	90
		0.6	50	59	60	65
		0.9	38	42	43	45
22 to 27	28 to 35	0.4	90	113	122	143
		0.6	76	92	94	105
		0.9	56	69	70	76
	36 to 43	0.4	76	94	97	114
		0.6	60	73	75	84
		0.9	45	55	56	60

### 2.11 Charge-Pump Flying/Output Capacitor Selection

An integrated charge pump can be used to supply high gate-drive voltage of switching FET. To use the charge pump, a 2.2- $\mu$ F capacitor is required as a flying capacitor between C1P and C1N, and a 10- $\mu$ F capacitor is required for the charge-pump output to hold the energy for the gate drive. Voltage rating of both capacitors must be at least 25% higher than the gate-drive level of switching FET (50% or higher is recommended)

### 2.12 Bypass Capacitor Selection for VDD/VLDO/VDDIO

TI recommends at least 1- $\mu$ F capacitance for VDD and VDDIO, and 4.7  $\mu$ F for VLDO near the pins. The voltage rating of each capacitor must be at least 25% higher than each voltage level (50% or higher is recommended).

### 2.13 Components on Evaluation Board

Table 4 shows the components are used on the LP8863-Q1EVM evaluation board as examples. All components listed in Table 4 support operation temperature  $-40^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$ , and all capacitors are X7R type.

**Table 4. Component List for LP8863Q1EVM Evaluation Board**

COMPONENTS	SW FREQUENCY = 300/400 kHz	SW FREQUENCY = 600/800 kHz	SW FREQUENCY = 1000/1250 kHz	SW FREQUENCY = 667/2222 kHz
Boost inductor	SRP1770TA-220M (22 $\mu$ H)	IHLP6767GZER150MA1 (15 $\mu$ H)	IHLP5050FDER100M01 (10 $\mu$ H)	IHLP5050FDER100M01 (10 $\mu$ H)
Boost input capacitors	EEH-ZC1J330P $\times$ 2 (2 $\times$ 33- $\mu$ F electrolyte) C5750X7S2A106M230KB $\times$ 2 (2 $\times$ 10- $\mu$ F ceramic)			
Boost output capacitors	EEH-ZC1J330P $\times$ 2 (2 $\times$ 33- $\mu$ F electrolyte) C5750X7S2A106M230KB $\times$ 2 (2 $\times$ 10- $\mu$ F ceramic)			
Output diode	FSV10100V (Schottky, 100 V, 10 A)			
Switching FET	NVMFS5C682NLT3G (60 V, 25 A)			
Power-line FET	SQJ461EP (60 V, 30 A)			
Boost feedback-divide resistors	R1 (upper): RC0603FR-07910KL (910 k $\Omega$ , 0.1 W); R2 (lower): RC0603FR-07100KL (100 k $\Omega$ , 0.1 W)			
SD pull-down resistor	CRCW06030K0FKEA (20 k $\Omega$ , 0.1 W)			
Input current-sense resistor	CRA2512-FZ-R020ELF (20 m $\Omega$ , 3 W)			
Boost current-sense resistor	CRA2512-FZ-R015ELF (15 m $\Omega$ , 3 W)			
Charge-pump flying capacitor	GRM21BR71E225KA73L (2.2 $\mu$ F, 25 V)			
Charge-pump output capacitor	C3216X7R1C106M (10 $\mu$ F, 16 V)			
Bypass capacitor - VDD	LMK212B7475KG-T (4.7 $\mu$ F, 10 V)			
Bypass capacitor - VLDO	GRM21BR71A106KE51L (2.2 $\mu$ F, 25 V)			
Bypass capacitor - VDDIO	0603ZK475KAT2A (4.7 $\mu$ F, 10 V)			

## 3 Summary

Recommended external component values for the LP8863-Q1 device can be selected by input/output voltages, load current, and other component values, accordingly, as previously explained. It is very important to note that these values are only simulated or calculated values, not tested for entire use cases. User can refer to these recommended values as a starting point and must consider extra margins of characteristics for each component.

## 4 References

- TI Application Report [Basic Calculation of a Boost Converter's Power Stage](#)
- Simulation results for the LP8863-Q1 device

---

## Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

<b>Changes from Original (April 2017) to A Revision</b>	<b>Page</b>
• First public release to WEB .....	<b>1</b>

---

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated