

# ***Inverting Application for the LMZM33602/3***

Jimmy Hua

*Power Modules Applications*

## **ABSTRACT**

The LMZM33603 is a 3-A rated synchronous step-down power module from Texas Instruments that features a wide operating input range from 4 V to 36 V with adjustable output voltage options from 1 V to 18 V. Furthermore, the LMZM33603 can be configured in an inverting buck-boost (IBB) topology with the output voltage inverted or negative with respect to ground. This application report shows how the conventional non-inverting evaluation board for the LMZM33603 can be configured for an inverting application without the need to spin the PCB if EN and PGOOD pins are not required. If EN and PGOOD pins are required, additional level-shifter circuitry must be taken into account during for PCB spin. Note that the LMZM33602 is rated for 2 A and pin-to-pin compatible with the LMZM33603.

## **Contents**

1	Inverting Buck-Boost Topology .....	2
2	Design Considerations .....	5
3	External Components .....	11
4	Typical Performance .....	12
5	Conclusion .....	14
6	References .....	14

## **List of Figures**

1	Buck Topology .....	2
2	Inverting Buck Boost Topology .....	2
3	Buck-Boost Configuration .....	3
4	Recommended Maximum Output Current for LMZM33603 .....	4
5	Recommended Maximum Output Current for LMZM33602 .....	5
6	LMZM33603 Inverting Buck-Boost Schematic With Schottky Diode .....	6
7	EN Pin Level Shifter .....	7
8	EN Pin Level Shifter on Start-Up .....	8
9	EN Pin Level Shifter on Shutdown .....	8
10	PG Pin Level Shifter .....	9
11	PG Pin Level Shifter on Start-Up .....	10
12	PG Pin Level Shifter on Shutdown .....	10
13	SW Node Voltage During Start-Up .....	11
14	Schematic of Tested Circuit .....	12
15	Efficiency vs Load Current With $V_{IN} = 24\text{ V}$ .....	12
16	Load Range With $V_{IN} = 24\text{ V}$ .....	12
17	Start-Up on $V_{IN}$ With 1.5-A Load .....	12
18	Shutdown on $V_{IN}$ With 1.5-A Load .....	12
19	Load Transient Response, 0 mA to 1.5 A With $V_{IN} = 12\text{ V}$ .....	12
20	Output Voltage Ripple, $V_{IN} = 12\text{ V}$ , $V_{OUT} = 5\text{ V}$ , and $I_{OUT} = 1.5\text{ A}$ .....	12

## **Trademarks**

All trademarks are the property of their respective owners.

# 1 Inverting Buck-Boost Topology

## 1.1 Concept

In a standard buck configuration the positive connection ( $V_{OUT}$ ) is connected to the inductor, and the return connection is connected to the device ground.

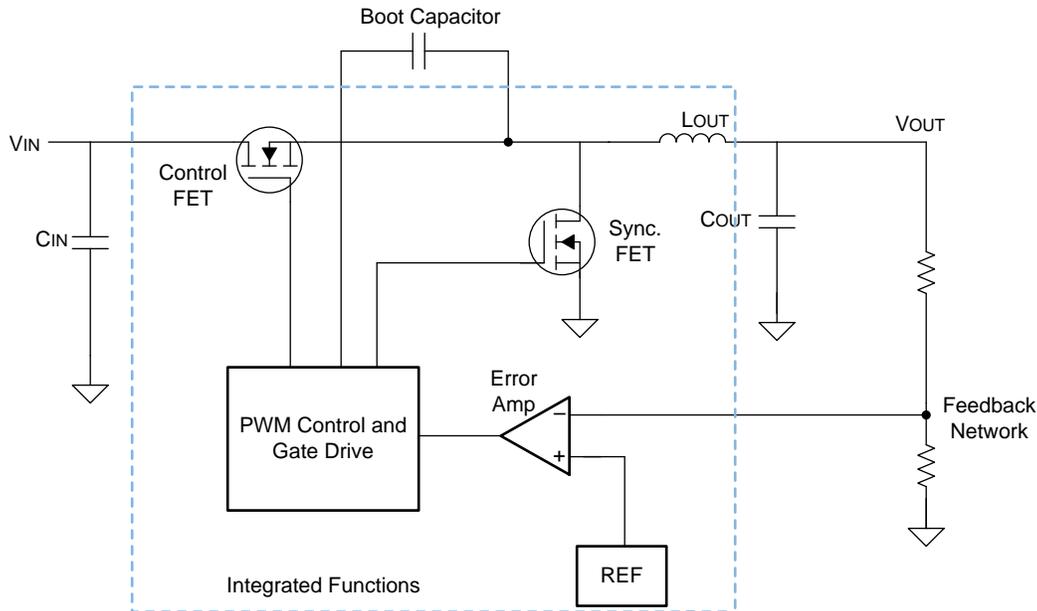


Figure 1. Buck Topology

In the IBB configuration, the device return is used as the negative output voltage pin (labeled as  $V_{OUT}$ ). The positive output in the buck configuration that was previously  $V_{OUT}$  is now referenced as ground (GND). This shift in topology allows the output voltage to be inverted with respect to the input voltage.


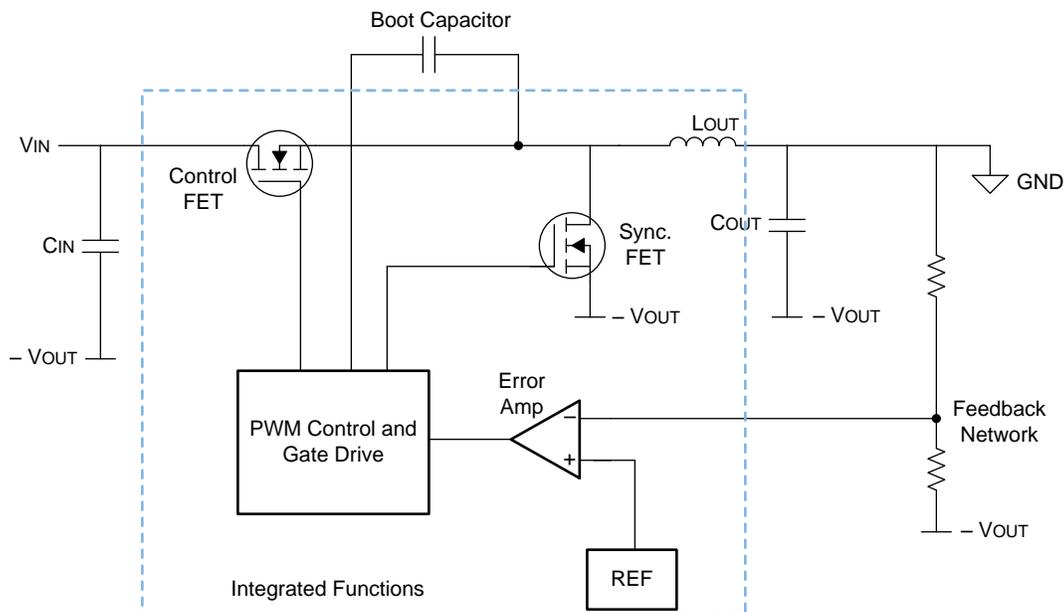


Figure 2. Inverting Buck Boost Topology

Though the components in an IBB topology are connected in the same way as with a buck topology, the output voltage terminals are reversed, as shown in (a) of [Figure 3](#). During the *on* time of the control MOSFET, as shown in (b) of [Figure 3](#), the inductor is energized with current, while the output capacitor supplies the load current. In this state, the inductor does not provide current to the load. During the *off* time of the control MOSFET and the *on* time of the synchronous MOSFET, as shown in (c) of [Figure 3](#), the inductor provides current to the load and the output capacitor. These changes affect many parameters, as discussed in the [Design Considerations](#) section.

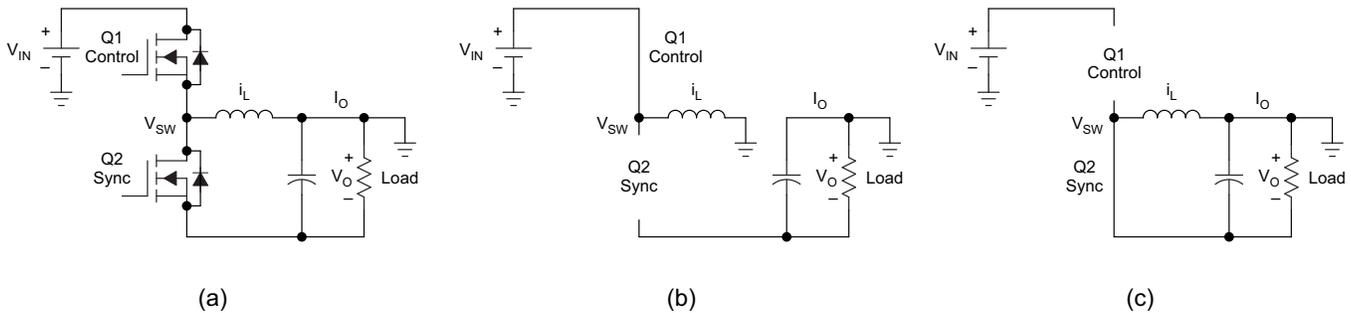

**Figure 3. Buck-Boost Configuration**

## 1.2 Output Current Calculations

By changing the buck configuration into an IBB configuration, the average inductor current is affected. In the buck configuration, the average inductor current equates to the average output current because the inductor is always supplying current to the load in both the *on* and *off* times of the high and low side FETs. In the inverting buck-boost configuration the output capacitor is completely disconnected from the inductor during the *on* time of the high-side FET and the inductor supplies current to both the output capacitor and the load during the *off* time.

The operating duty cycle for an inverting buck-boost converter can be found with [Equation 1](#):

$$D = \frac{V_{out}}{V_{out} - V_{in} * \eta} \tag{1}$$

**NOTE:**  $V_{OUT}$  in [Equation 1](#) is represented with a negative value.

The efficiency term in [Equation 1](#) adjusts the equations in this section for power conversion losses and yields a more accurate maximum output current result. Given that the IBB configuration yields an efficiency range of 70% to 85%, the conservative value of 70% is used for calculating the duty cycle. For example, given a  $-12\text{-V}$  output voltage,  $24\text{-V}$  input voltage, and  $3\text{-A}$  maximum current rating, [Equation 2](#) and [Equation 3](#) calculate the recommended maximum output current.

$$D = \frac{-12}{-12V - 24 * 0.7} = 0.4166 \tag{2}$$

The result of [Equation 2](#) is then used to calculate the maximum achievable output current:


$$I_{OUT} (IBB) = 3 \times (1 - 0.4166) = 1.75 \text{ A} \tag{3}$$

It is expected that the maximum output current for the LMZM33603 in the IBB topology will be lower than the typical buck topology due to the fact that the average inductor current is higher. [Table 1](#) provides a general idea of what to expect from the modified LMZM33603. Given that the switching frequency is set at  $450 \text{ kHz}$ , [Table 1](#) and [Figure 4](#) show the maximum output current for the LMZM33603 IBB configuration. [Table 2](#) and [Figure 5](#) show the maximum output current for the LMZM33602 IBB configuration.


**Table 1. Maximum Output Current Calculation for LMZM33603**

$V_{OUT}$ (V)	$V_{IN}$ (V)	$I_{L\_max}$ (A)	$\eta$	D	$I_{OUT}$ (A)
-2.5	24	3	0.7	0.129	2.6
-3.3	24	3	0.7	0.164	2.5
-5	24	3	0.7	0.229	2.3
-12	24	3	0.7	0.416	1.75

Figure 4 is a visual interpretation of the maximum output current table.

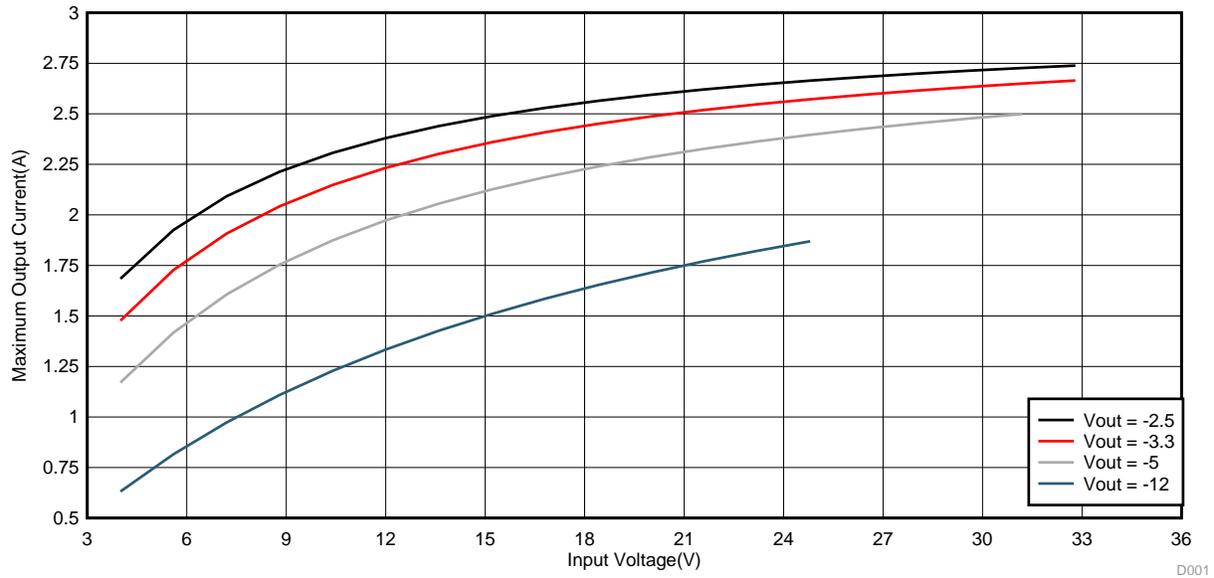
**Figure 4. Recommended Maximum Output Current for LMZM33603**
**Table 2. Maximum Output Current Calculation for LMZM33602/3**

$V_{OUT}$ (V)	$V_{IN}$ (V)	$I_{L\_max}$ (A)	$\eta$	D	$I_{OUT}$ (A)
-2.5	24	2	0.7	0.119	1.74
-3.3	24	2	0.7	0.151	1.67
-5	24	2	0.7	0.205	1.54
-12	24	2	0.7	0.392	1.16

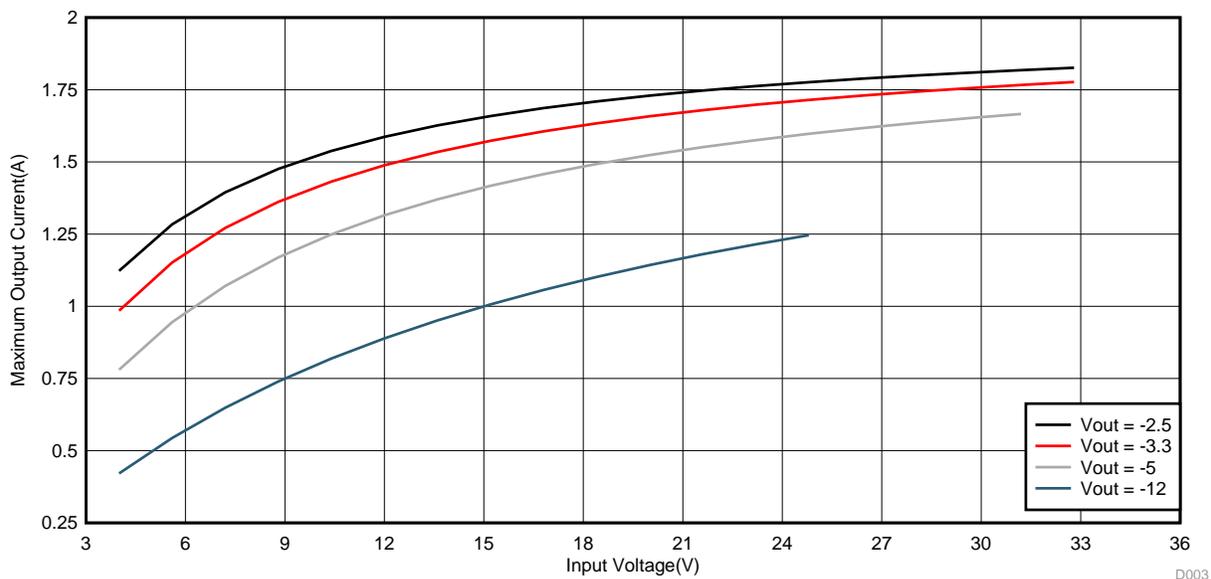

**Figure 5. Recommended Maximum Output Current for LMZM33602**

D003

### 1.3 $V_{IN}$ and $V_{OUT}$ Ranges

When configured in an IBB topology, the input voltage across the module is  $V_{IN}$  to  $V_{OUT}$ , not  $V_{IN}$  to ground. To illustrate this, the modified LMZM33603 has an input voltage range from 4 V to  $36 + V_{OUT}$ , where  $V_{OUT}$  is a negative value. The output voltage range in this topology is  $-1$  V to  $-18$  V because the expected output is now negative. Also consider that most DC-DC converter circuits have undervoltage lockout (UVLO) circuitry and that the minimum voltage to maintain operational start-up must be above the UVLO limit even with the modified topology.


## 2 Design Considerations

### 2.1 Additional Bypass Capacitor and Schottky Diode

Add a ceramic bypass capacitor,  $C_{BYP}$ , with a minimum capacitance of 10  $\mu$ F, as shown in [Figure 6](#). The voltage rating must be taken into consideration because this capacitor will experience stress equal to the full voltage difference between  $V_{IN}$  and  $V_{OUT}$ .

Consider that the inclusion of the  $C_{BYP}$  capacitor introduces an AC path from  $V_{IN}$  to  $V_{OUT}$  and might worsen the line transient response. When  $V_{IN}$  is initially applied, this  $dV/dt$  across the bypass capacitor creates a current that must return to ground to complete the loop. This current might flow through the internal low-side body diode of the MOSFET and the inductor to return to ground. For this case, TI recommends adding a Schottky diode between  $V_{OUT}$  and GND. If large line transients are expected, increase the output capacitance to keep the output voltage within acceptable levels.

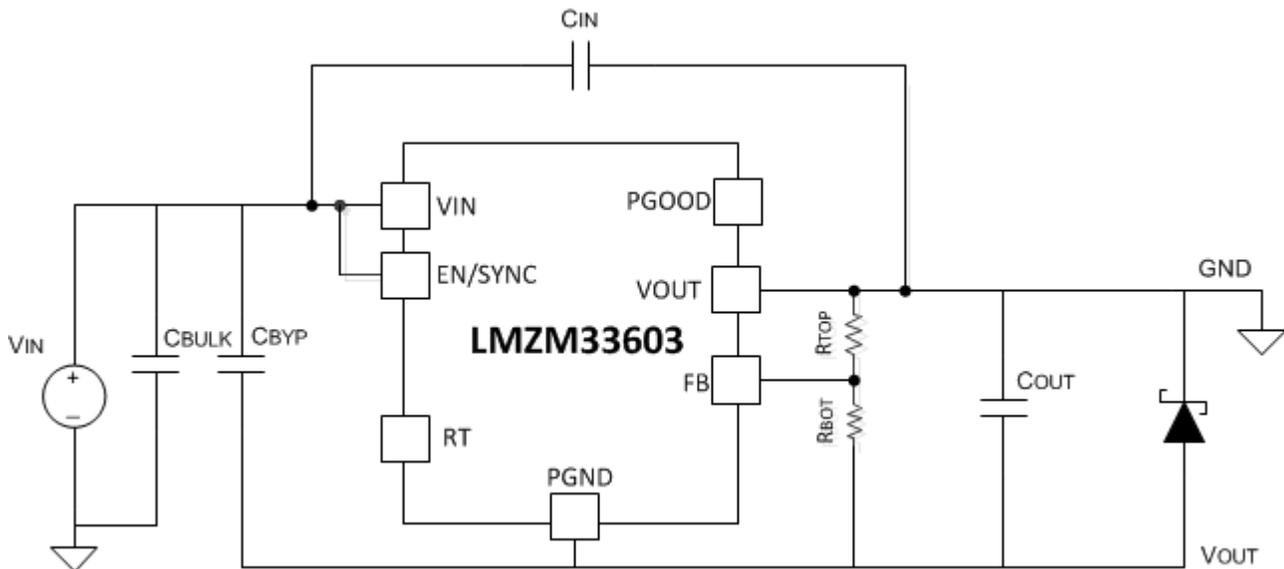Also note that in order for the system to be stable, there must be an input power supply capacitor to help dampen the high-frequency noise that can couple onto the circuit. When using the LMZM33603EVM, the  $C_{BULK}$  capacitor connection must be modified because the IC return is no longer ground.



Copyright © 2018, Texas Instruments Incorporated

**Figure 6. LMZM33603 Inverting Buck-Boost Schematic With Schottky Diode**

## 2.2 Bode Plot Stability

Output capacitance is an important factor when considering stability of the system. For stability the phase margin (PM) of at least 45° is typically desired. Below is a table that shows the measured PM data configured IBB LMZM33603 for both 12-V and 24-V inputs under maximum load for the given output voltages. Note that this dataset is valid for switching frequency of 450 kHz and output capacitance ( $4 \times 22 \mu\text{F}$ ) of the original LMZM33603EVM.

**Table 3. Measured Phase Margin of IBB Default EVM**

$V_{\text{IN}}$ (V)	$V_{\text{OUT}}$ (V)	$I_{\text{OUT}}$ (A)	$F_{\text{CROSS}}$ (kHz)	PM (°)
24	-2.5	2.6	58.15	46.1
24	-3.3	2.5	43.39	62.2
24	-5	2.35	28.02	73.7
24	-12	1.8	12.05	49.2

For the 24-V input voltage application, [Table 4](#) shows that using the output capacitance of the LMZM33603EVM will satisfy PM 45° for all negative output voltage selection. LMZM33603 features hiccup mode and will fault during a maintained over current condition on the output. During hiccup mode, the LMZM33603 shuts off both the high-side and low-side MOSFET and waits for a time interval before the LMZM33603 is turned back on. If the output capacitance is too high, the output voltage takes longer to stabilize to the regulated voltage and can trip hiccup. The table below shows the maximum output capacitance recommended for the IBB converted LMZM33603. Note that the output capacitance listed takes into account DC bias effects at each specific output voltage.

**Table 4. Recommended Output Capacitance For  $V_{\text{IN}} = 24 \text{ V}$** 


$V_{\text{IN}}$ (V)	$V_{\text{OUT}}$ (V)	$I_{\text{OUT}}$ (A)	$C_{\text{OUT\_MIN}}$ ( $\mu\text{F}$ )	$C_{\text{OUT\_MAX}}$ ( $\mu\text{F}$ )
24	-2.5	2.6	135	660
24	-3.3	2.5	97	530
24	-5	2.35	56	450
24	-12	1.8	22	70

## 2.3 Digital Pin Configurations
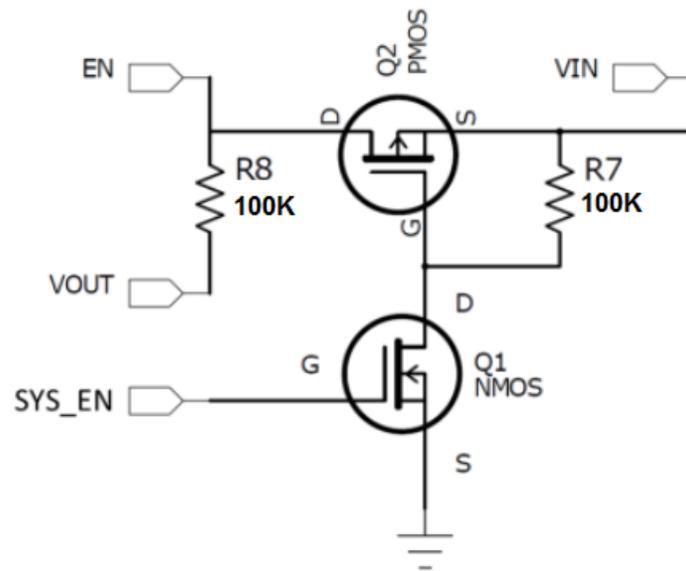
### 2.3.1 Digital Input Pin (EN)

Because  $V_{OUT}$  is the IC return in this configuration, the EN pin must be referenced to  $V_{OUT}$  instead of 0 V. In a buck configuration, the specified typical threshold voltage for the EN pin to be considered high is 1.55 V and 1.15 V is considered low. In the inverting buck-boost configuration, however, the  $V_{OUT}$  voltage is the reference; therefore, the high threshold is  $1.55\text{ V} + V_{OUT}$ , and the low threshold is  $1.15\text{ V} + V_{OUT}$ . For example, if  $V_{OUT} = -12\text{ V}$ ,  $V_{EN}$  is considered a high for voltages above  $-10.45\text{ V}$  and a low for voltages below  $-10.85\text{ V}$ .

This behavior can cause difficulties enabling or disabling the part, because in some applications the IC providing the EN signal may not be able to produce negative voltages. The level shifter alleviates any problems associated with the offset EN threshold voltages by eliminating the need for negative EN signals.



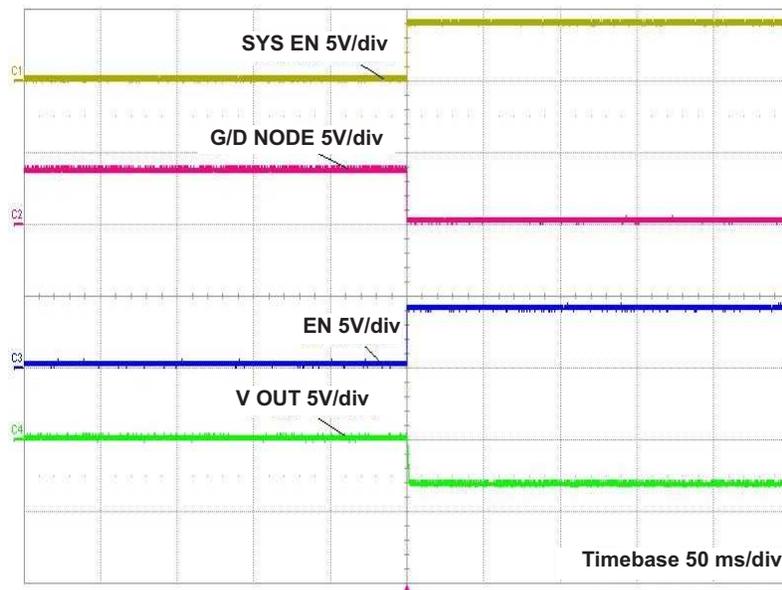
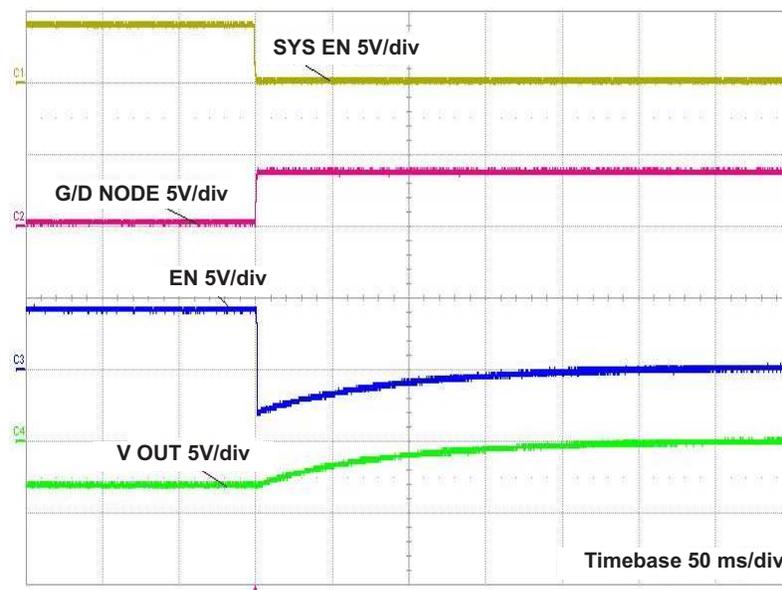
$V_{OUT}$  is the negative output voltage of the inverting buck-boost converter

**Figure 7. EN Pin Level Shifter**

The positive signal that originally drove EN is instead tied to the gate of Q1 (SYS\_EN). When Q1 is off (SYS\_EN grounded), Q2 detects 0 V across its  $V_{GS}$  and also remains off. In this state, the EN pin detects  $V_{OUT}$ , which is below the low level threshold and disables the device.

When SYS\_EN provides enough positive voltage to turn Q1 on (minimum  $V_{GS}$  as specified in the data sheet of the MOSFET), the gate of Q2 is pulled low through Q1. This drives the  $V_{GS}$  of Q2 negative and turns Q2 on. As a consequence,  $V_{IN}$  ties to EN through Q2, and the pin is above the high level threshold, causing the device to turn on. Ensure that the  $V_{GD}$  of Q2 remains within the ratings of the MOSFET ratings during both enabled and disabled states. Also ensure that  $V_{GS}$  and  $V_{DS}$  ratings are not exceeded. Failing to adhere to these constraints can result in damaged MOSFETs.

The SYS\_EN signal activates the enable circuit, and the G/D NODE signal represents the shared node between Q1 and Q2. The EN signal is the output of the circuit and goes from VIN to  $-V_{OUT}$  properly enabling and disabling the device.


**Figure 8. EN Pin Level Shifter on Start-Up**

**Figure 9. EN Pin Level Shifter on Shutdown**

### 2.3.2 Power-Good Pin

The LMZM33603 has a built-in power-good (PG) function to indicate whether the output voltage has reached its appropriate level or not. The PG pin is an open-drain output that requires a pullup resistor. Because  $V_{OUT}$  is the IC return in this configuration, the PG pin is referenced to  $V_{OUT}$  instead of ground, which means that the device pulls PG to  $V_{OUT}$  when it is low.

This behavior can cause difficulties in reading the state of the PG pin, because in some applications the IC detecting the polarity of the PG pin may not be able to withstand negative voltages. The level shifter circuit alleviates any difficulties associated with the offset PG pin voltages by eliminating the negative output signals of the PG pin. If the PG pin functionality is not needed, it may be left floating or connected to  $V_{OUT}$  without this circuit. Note that to avoid violating its absolute maximum rating, the PG pin must not be driven more than 12 V above the negative output voltage (IC return).


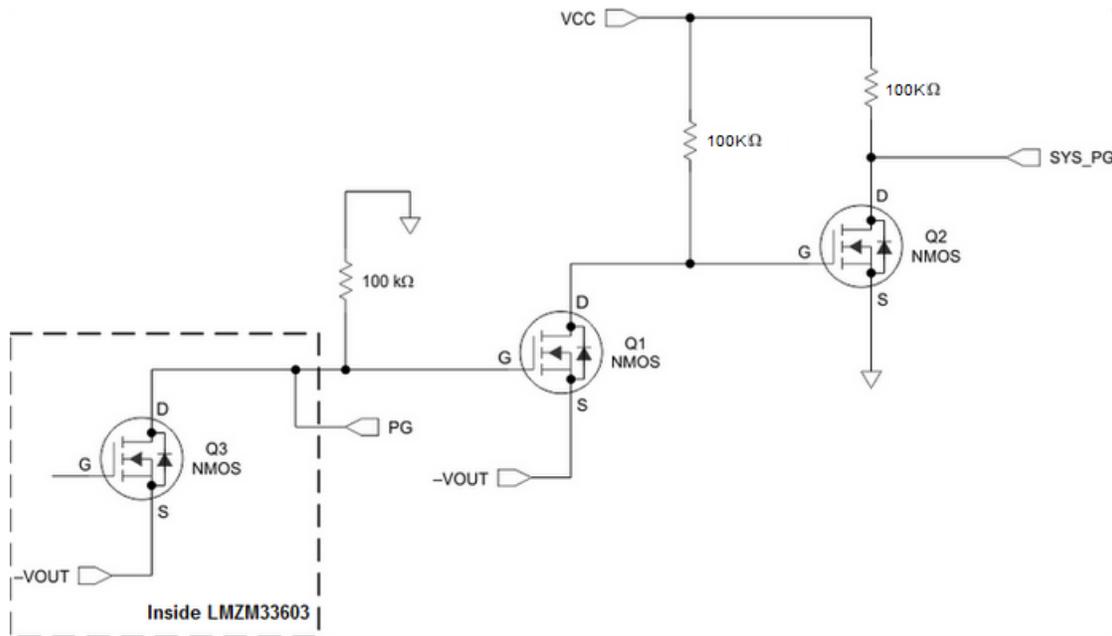


Figure 10. PG Pin Level Shifter

Inside these devices, the PG pin is connected to an N-channel MOSFET (Q3). By tying the PG pin to the gate of Q1, when the PG pin is pulled low, Q1 is off and Q2 is on because its  $V_{GS}$  detects  $V_{CC}$ . SYS\_PG is then pulled to ground.

When Q3 turns off, the gate of Q1 is pulled to ground potential turning it on. This pulls the gate of Q2 below ground, turning it off. SYS\_PG is then pulled up to the  $V_{CC}$  voltage. Note that the  $V_{CC}$  voltage must be at an appropriate logic level for the circuitry connected to the SYS\_PG net.

This PG pin level shifter sequence is illustrated in Figure 11 and Figure 12. The PG signal activates the PG pin level shifter circuit, and the GD Node signal represents the shared node between Q1 and Q2. This circuit was tested with a  $V_{CC}$  of 1.8 V and FemtoFET CSD15830F3. The SYS\_PG net is the output of the circuit that transitions between ground and 1.8 V and is easily read by a separate device.

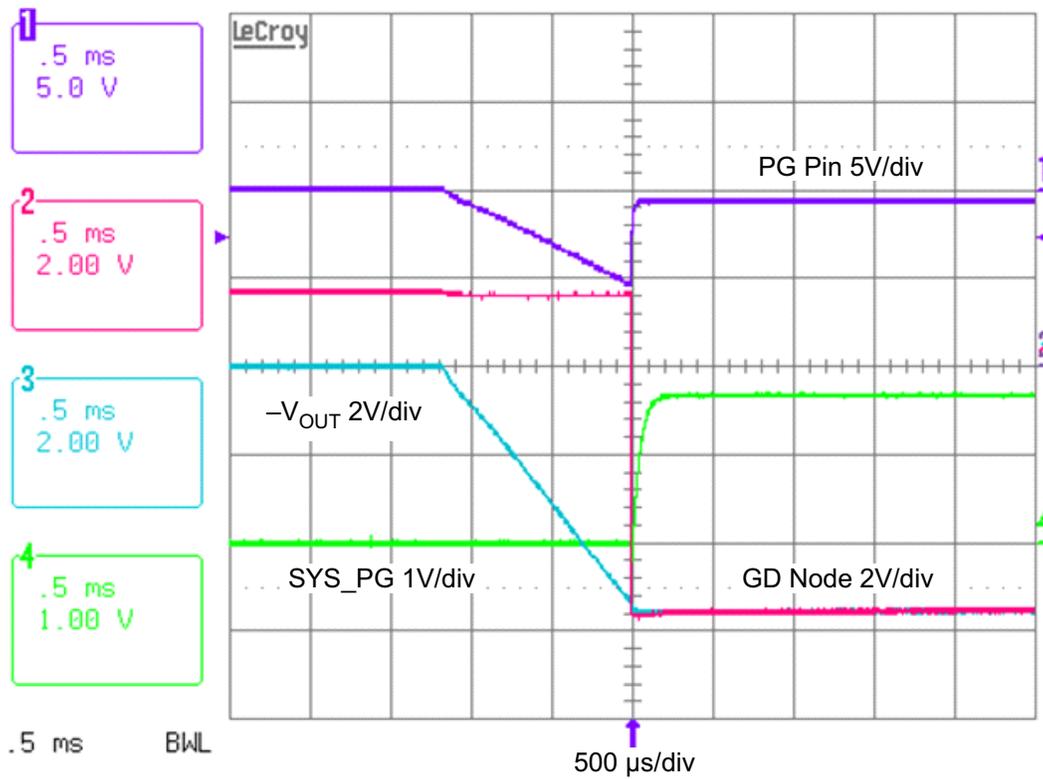

Note that the PG pin is with respect to system return.

Figure 11. PG Pin Level Shifter on Start-Up

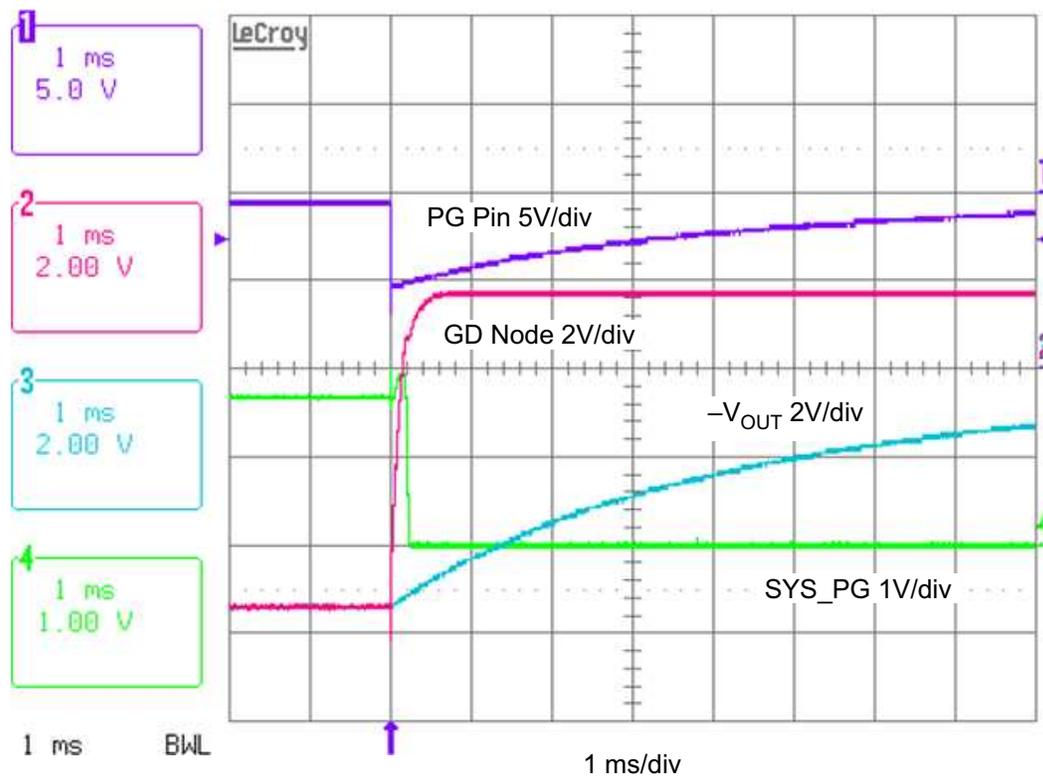


Figure 12. PG Pin Level Shifter on Shutdown

## 2.4 Start-up Behavior and Switching Node Consideration

The voltage on the SW pin switches from  $V_{IN}$  to  $V_{OUT}$  in an inverting topology instead of from  $V_{IN}$  to GND in a buck topology. When the high-side MOSFET is on, the SW node sees the input voltage. When low-side MOSFET is on, the SW node detects the device return, which is the output voltage. During start-up,  $V_{IN}$  rises to achieve the desired input voltage.  $V_{OUT}$  starts ramping down after the EN pin voltage exceeds its threshold level and  $V_{IN}$  exceeds its UVLO threshold. As  $V_{OUT}$  continues to ramp down, the SW node low level follows it down. Figure 13 shows the resulting normal and smooth start-up of the output voltage.

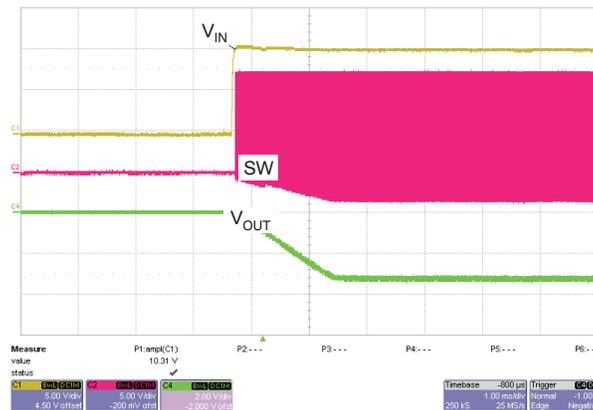


Figure 13. SW Node Voltage During Start-Up

## 3 External Components


The LMZM33603 power module integrates power MOSFETs and shielded inductor. As a result, this application only requires as few as four external components. TI recommends performing a load-transient test and frequency sweep to evaluate stability.

### 3.1 Capacitor Selection

TI recommends ceramic capacitors for low equivalent series resistance (ESR) to achieve low output voltage ripple criteria. X5R- or X7R-type dielectrics are recommended for the stable capacitance versus temperature characteristics and DC bias. The higher the DC voltage applied to the ceramic capacitor, the less the effective capacitance. TI recommends a minimum of 10- $\mu$ F capacitance for both  $C_{BYP}$  and  $C_{IN}$ . For the output capacitor, see *Table 1 - Required Component Values* in the [LMZM33603](#) data sheet. Making this capacitor value too great can prevent proper start-up operations. Evaluating the Bode plot can provide insight on the stability of the system.
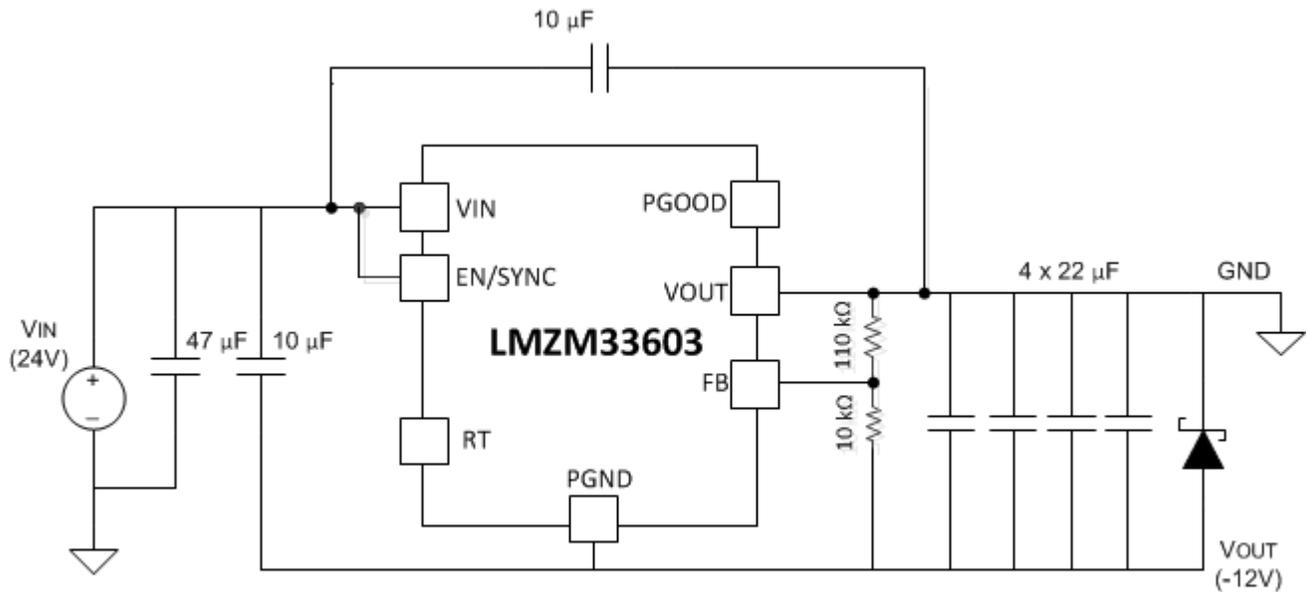
## 4 Typical Performance

The reference design shown in Figure 14 was used to generate the typical characteristic graphs presented in this section.



Copyright © 2018, Texas Instruments Incorporated

Figure 14. Schematic of Tested Circuit

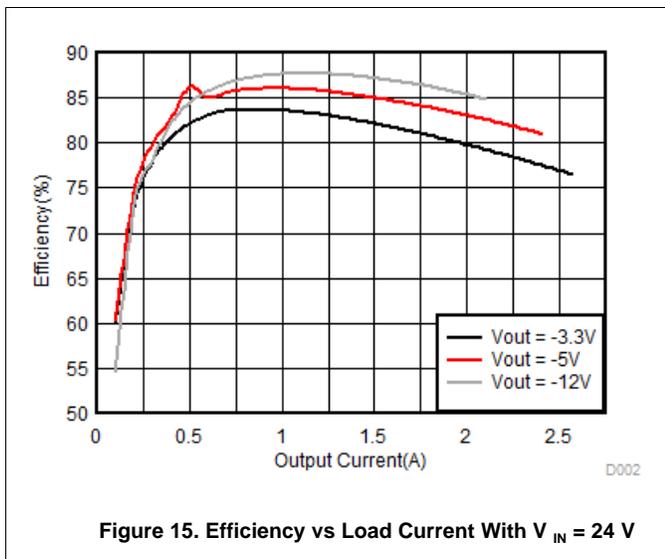


Figure 15. Efficiency vs Load Current With  $V_{IN} = 24\text{ V}$

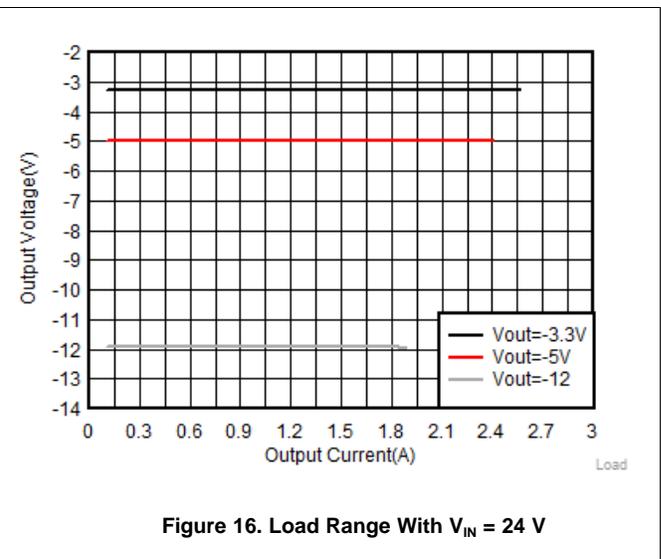


Figure 16. Load Range With  $V_{IN} = 24\text{ V}$

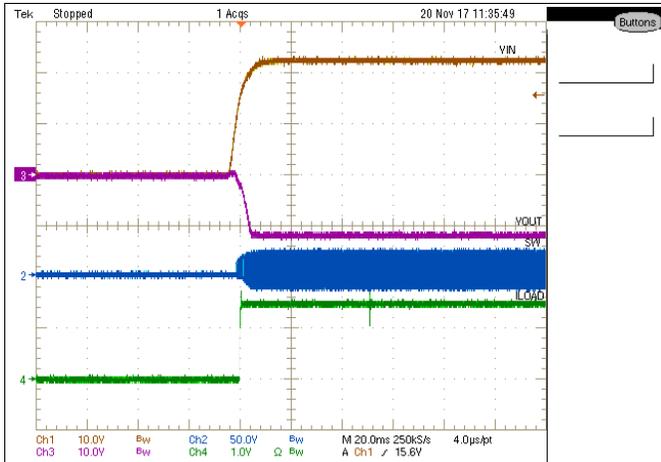


Figure 17. Start-Up on  $V_{IN}$  With 1.5-A Load

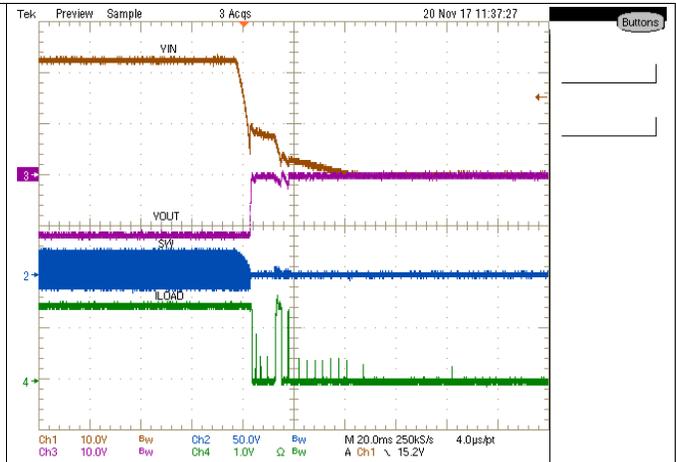


Figure 18. Shutdown on  $V_{IN}$  With 1.5-A Load

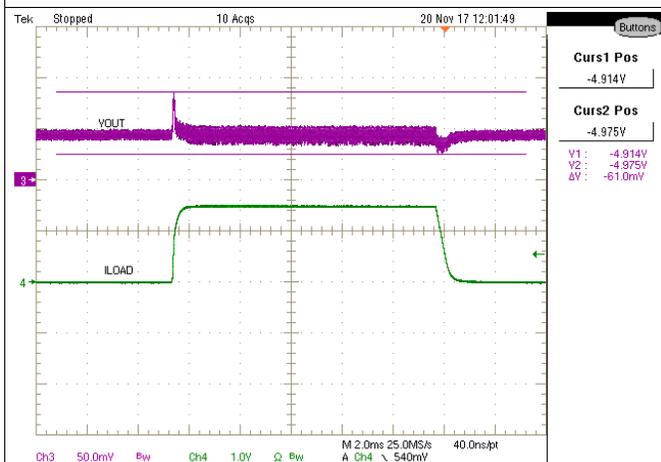


Figure 19. Load Transient Response, 0 mA to 1.5 A With  $V_{IN} = 12\text{ V}$

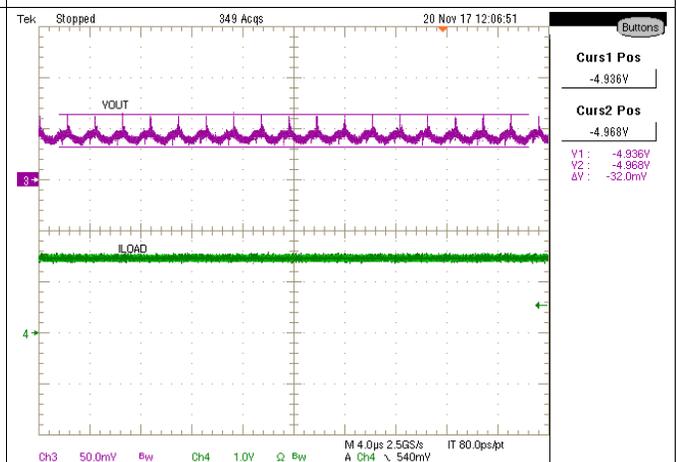


Figure 20. Output Voltage Ripple,  $V_{IN} = 12\text{ V}$ ,  $V_{OUT} = 5\text{ V}$ , and  $I_{OUT} = 1.5\text{ A}$

## 5 Conclusion

The LMZM33603 step-down power module can be configured in an IBB topology to generate a negative output voltage. This limits the system's input voltage range and maximum output current. The input voltage range is lowered because the device now has a reference point at negative output voltage rather than ground. Additionally, the inductor peak current is much higher effectively lowering the recommended maximum output current operating range. A spin of the PCB with additional level shifter circuitry is required if the EN and PG features are used.

## 6 References

The following documents are available for download from the [TI web site](#):

1. [Create an Inverting Power Supply From a Step-Down Regulator](#) .
2. [LMZM33603 4-V to 36-V Input, 3-A Step-Down DC-DC Power Module in QFN Package](#)
3. [Using a buck converter in an inverting buck-boost topology](#)
4. [Using the TPS5430 as an Inverting Buck-Boost Converter](#)

## Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

<b>Changes from A Revision (February 2018) to B Revision</b>	<b>Page</b>
• Changed duty cycle equation .....	3
• Changed duty cycle calculation .....	3
• Updated values in Table 1 .....	4
• Updated values in Table 2 .....	4

<b>Changes from Original (December 2017) to A Revision</b>	<b>Page</b>
• Added content to end of first paragraph .....	1
• Updated <a href="#">Figure 1</a> and <a href="#">Figure 2</a> .....	2
• Updated <a href="#">Figure 3</a> .....	3
• Changed efficiency from "0.87" to "0.85".....	3
• Updated values in Table 1 .....	3
• Changed titles of <a href="#">Table 1</a> and <a href="#">Figure 3</a> ; added and <a href="#">Figure 4</a> .....	4
• Changed diode symbol in <a href="#">Figure 6</a> to Schottky diode .....	5
• Deleted last sentence in <a href="#">Section 3</a> - information now elsewhere in app note; condensed <a href="#">Section 3.1</a> .....	11
• Changed diode symbol in <a href="#">Figure 14</a> to Schottky diode .....	12
• Deleted reference no. 5 .....	14

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2018, Texas Instruments Incorporated