

Simplify Your Bill of Materials with High-voltage Amplifiers



Kiernan Farmer

Engineers are often faced with the task of selecting multiple operational amplifiers (op amps) to fit the needs of each subsystem on their board, since op amp specifications often vary. This can complicate efforts from procurement to manufacturing.

However, it is possible to satisfy your system requirements with one op amp selection, which will help optimize your pricing and lower your design's overall cost. Let's look at how a single op amp can handle three common functions: current sensing, temperature sensing and comparator operation.

Current Sensing

Low-side current sensing is achieved by measuring the voltage drop across a shunt resistor placed between the load and ground, as shown in [Figure 1](#). Low-voltage (5-V) amplifiers typically handle this function. Just because an amplifier has a maximum supply voltage of 36 V or 40 V doesn't mean that it is limited to high-voltage supplies, however.


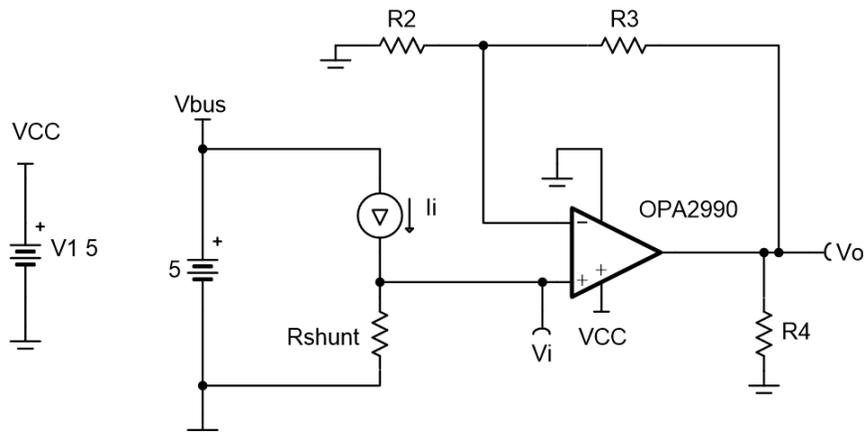


Figure 1. Single-supply Low-side Unidirectional Current-sensing Circuit

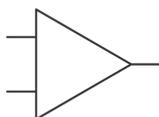High-voltage and highly versatile amplifiers



See TI's selection of high-voltage amplifiers providing a wide common mode range, high sensing capabilities and greater supply compatibility.

Low side-current sensing also often requires high-slew-rate op amps in case of a fault condition. Both the [OPA2990](#) and [OPA2191](#) have high slew rates for their respective power consumption: 4.5 V/ μ s for 120 μ A (the OPA2990), and 5.5 V/ μ s for 140 μ A (the OPA2191).

Since both of these op amps can operate at 36 V and 40 V, they are also a good fit for high-side current sensing functions. A key benefit of high-side current sensing when compared to low-side current sensing is the ability

to detect a short circuit. High-side current sensing uses a difference amplifier topology across a shunt resistor placed between the power supply and the load, as shown in [Figure 2](#).

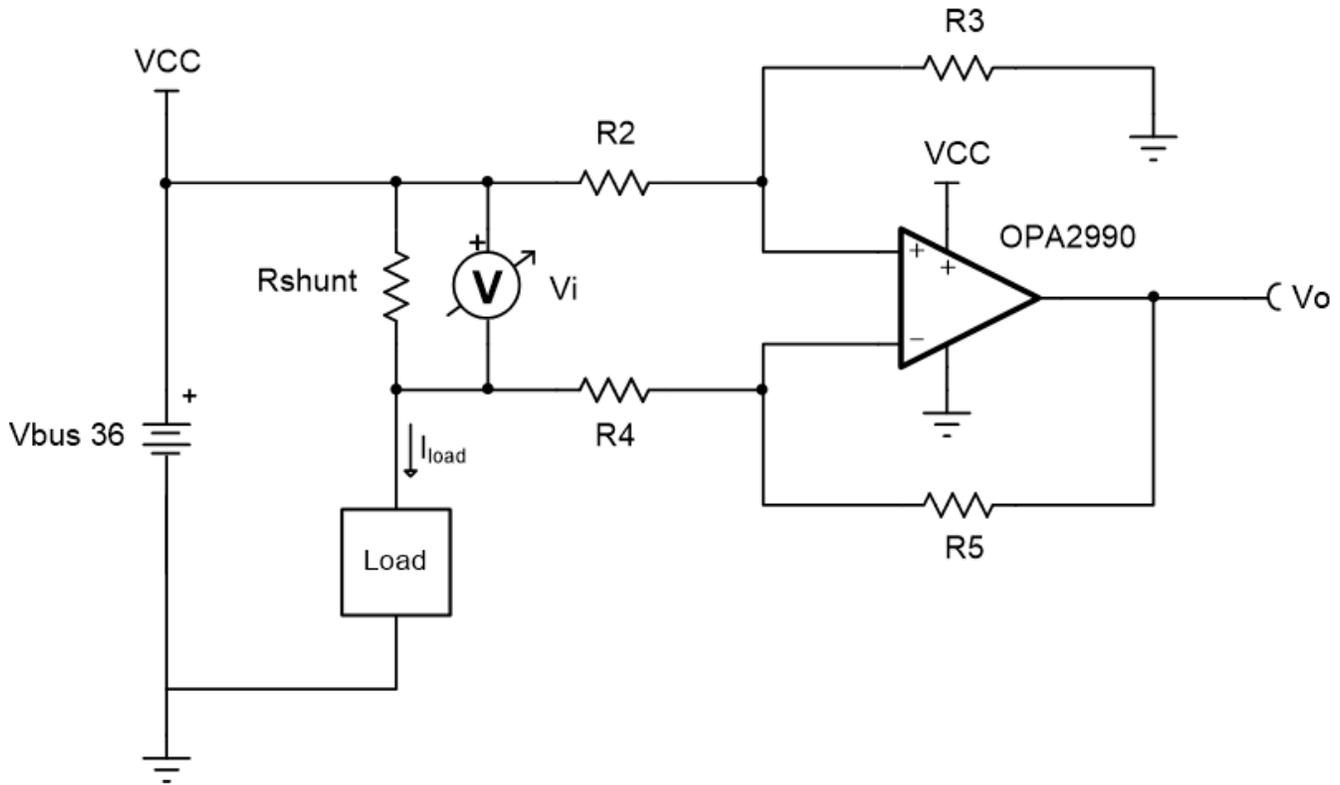


Figure 2. High-side Current-sensing Circuit

You must consider the common-mode voltage of the op amp when designing a high-side current-sensing circuit. The common-mode voltage is set by the bus voltage and the resistor divider formed by resistor R2 and R3 in [Figure 2](#). Because the common-mode voltage is typically equal to the bus voltage, amplifiers with rail-to-rail inputs and outputs are best for this function. Both the OPA2990 and OPA2191 have rail-to-rail common-mode input ranges and output swings across a wide 36-V (OPA2191) and 40-V (OPA2990) supply.

Temperature Sensing

Temperature sensing is critical in many applications in order to control environmental conditions or ensure safe operating conditions. Systems that measure temperature need to ensure accurate output measurements by scaling and amplifying sensor outputs to harness the full analog-to-digital converter (ADC) resolution. [Figure 3](#) shows how to configure an op amp to sense the resistive output of a positive temperature coefficient (PTC) thermistor and amplify that signal to an ADC.

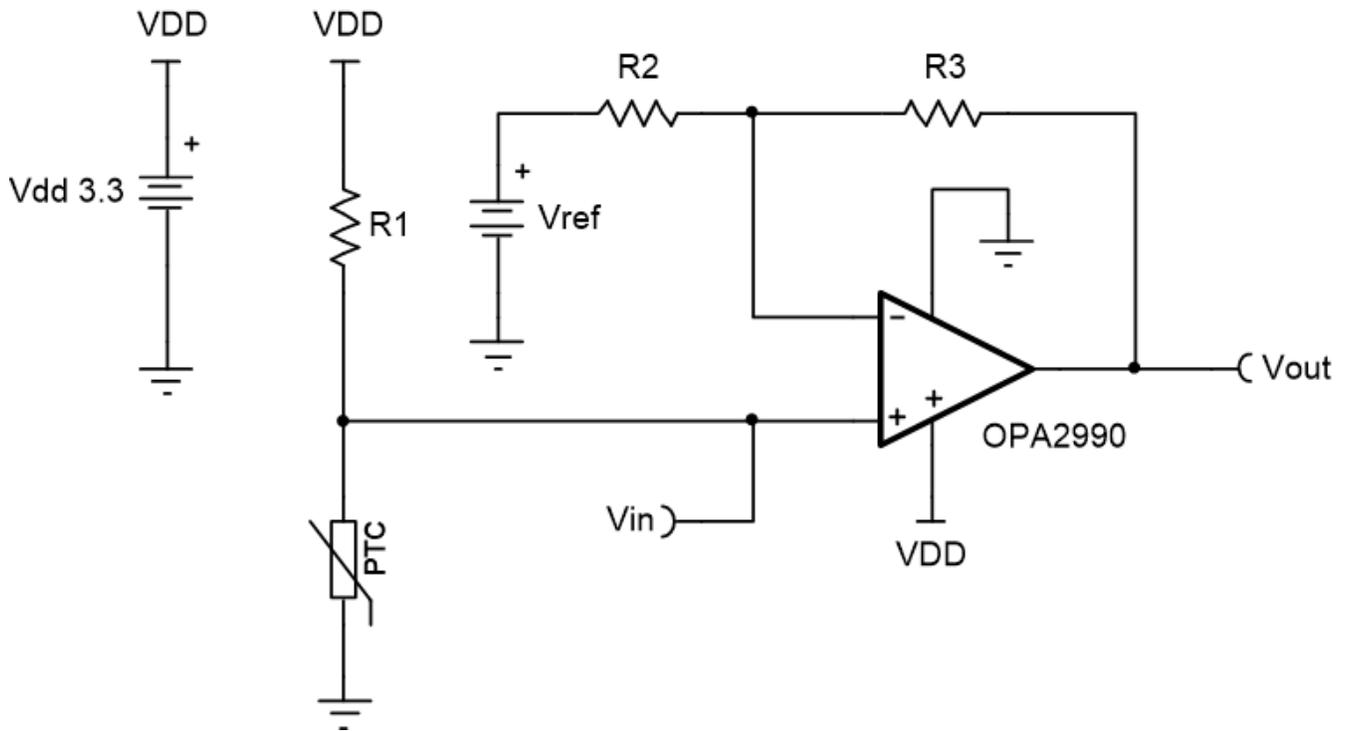


Figure 3. Temperature Sensing with PTC Circuit

The OPA2990 and OPA2191 can operate across a temperature range from -40°C to 125°C , which is useful for temperature-sensing functions in which the ambient temperature is expected to change significantly. This temperature range also emphasizes the importance of having low-drift op amps. For general-purpose applications, the OPA2990 has an offset drift of $0.5\ \mu\text{V}/^{\circ}\text{C}$. For a system that requires extremely accurate signals to the ADC, the OPA2191 has a drift of $0.15\ \mu\text{V}/^{\circ}\text{C}$.

Comparator Operation

Amplifiers with multiplexer-friendly inputs are designed so that they can properly interface with the large voltage transients characteristic of multiplexers. These amplifiers' internal input architecture does not use back-to-back diodes for electrostatic discharge protection, shown in Figure 4a. Instead, these multiplexer-friendly inputs allow for an input differential voltage that extends the full supply voltage range, which makes the OPA2990 and OPA2191 useful in both closed-loop as well as open-loop comparator-like topologies.

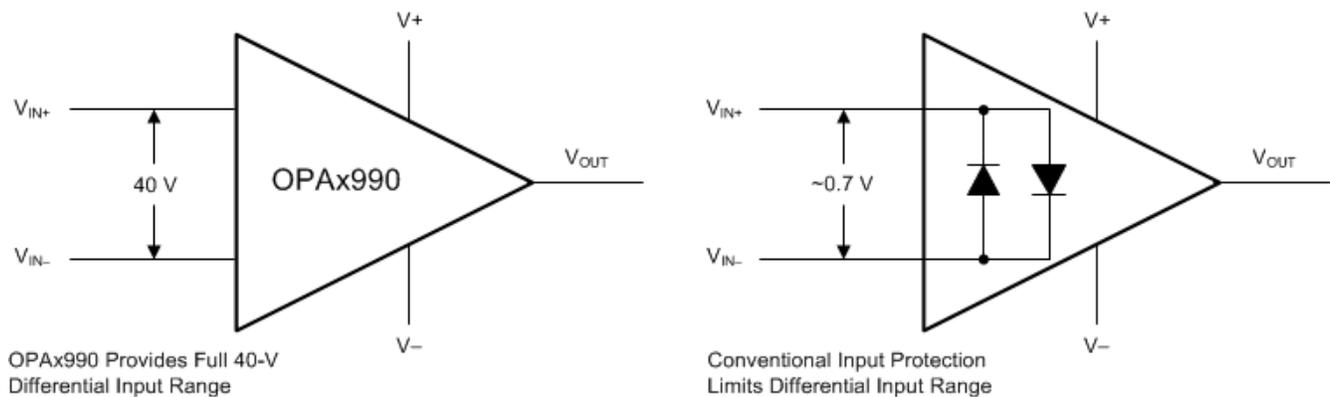


Figure 4. OPA2990 Input Protection Does Not Limit Differential Input Capability (a)

Conventional input protection limits differential input capability (b)

Choose the Amplifier Right for You

TI's new high-voltage amplifiers lower your device count and simplify your bill of materials while satisfying your system requirements with one single op-amp selection. Both the OPA2990 and OPA2191 have very flexible high-voltage options for systems requiring multiple op-amp functions. They can interface with a wide variety of other devices, including multiplexers, sensors and ADCs.

Additional Resources

- See a [comparison of specifications between the OPA2990 and OPA2191](#).
- Read the application note, "[MUX-Friendly Precision Operational Amplifiers](#)."
- Download the "[16-bit 400-KSPS Four-Channel Multiplexed Data Acquisition Reference Design for High-Voltage Inputs, Low Distortion](#)."

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated