

# Achieving Highly Accurate Full-scale Charge and Discharge Current Control for High-cell Li-ion Battery-formation Testing



Sean Zhou

The demand for lithium-ion (Li-ion) batteries is growing at an exponential pace, fueled by the increasing popularity of electric vehicles, personal electronics and grid systems. As consumer demand grows, so does the need for highly accurate battery-formation testing capabilities.

Battery-formation testing requires multiple charge and discharge cycles; achieving high accuracy during this process is necessary to maximize battery life and storage capacity. The battery current and voltage must be precisely controlled through every cycle, with many manufacturers requiring greater than 0.05% full-scale control accuracy. Maintaining such high accuracy becomes more challenging as the battery current requirements increase, however.

TI's [Battery Tester Reference Design for High Current Applications](#) leverages constant current (CC) and constant voltage (CV) calibration loops to achieve 0.01% full-scale charge and discharge current control accuracy. It supports charge and discharge rates as high as 50A and provides a modifiable platform for applications that need higher current or multiple phases. For example, the current specification of automotive cells is growing very sharply and may need even more than 50A.

As [Figure 1](#) shows, the reference design features the [LM5170-Q1](#), which regulates the current flowing into or out of the battery. The [INA188](#) implements and monitors the CC control loop, and because the current might flow in either direction, the [SN74LV4053A](#) multiplexer can adjust the inputs of the INA188 accordingly. The sensed current is compared to a precision reference generated by the [DAC80004](#) digital-to-analog converter (DAC), and both of these signals are fed into an error amplifier (EA) implemented with the [TLV07](#). The output of the EA is fed back to the ISETA analog current programming pin of the LM5170, which regulates the current flowing through the current-sense resistor to the current reference signal.


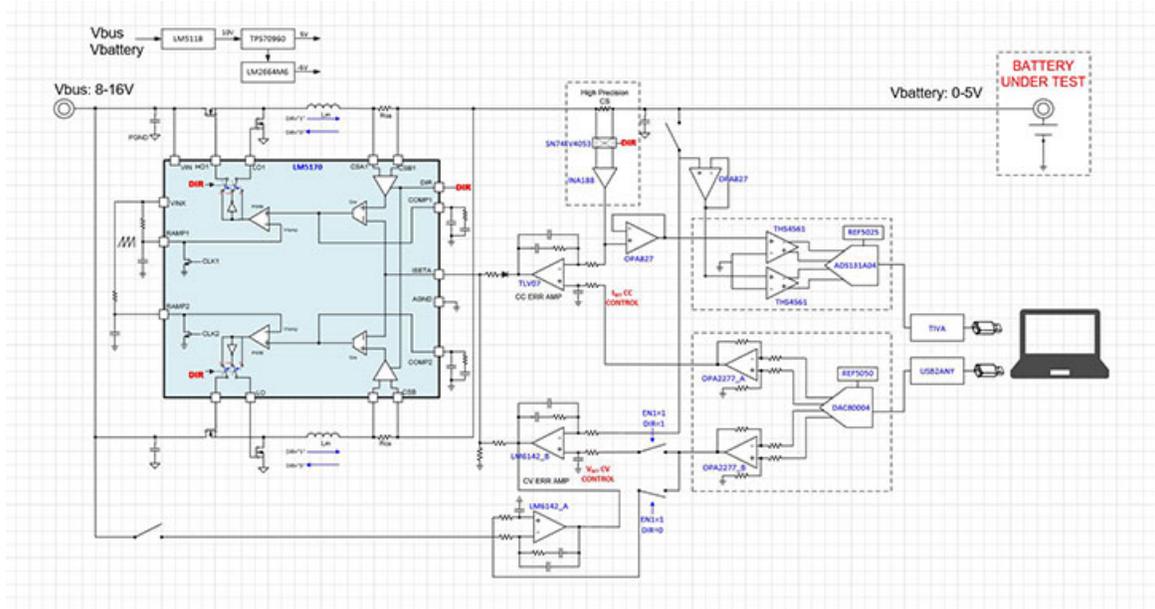


Figure 1. Block Diagram of the Battery Tester Reference Design

The CV control loop works in a similar fashion. The [ADS131A04](#) (24-Bit, 128kSPS, 4-Ch, Simultaneous-Sampling Delta-Sigma Analog-to-Digital Converter (ADC)), monitors both battery voltage and current, and the DAC80004 sets a highly accurate voltage reference for the CV control loop. The ADC monitoring the voltage and current of the battery and has a simple graphical user interface (GUI) through which you can observe the status of the battery. The DAC also provides a GUI to set the reference signals for different applications.


Many factors can affect system accuracy, including temperature drift, voltage drift and offset voltage. The battery tester reference design uses three-point calibration to account for different sources or any errors. [Figure 2](#) shows the full-scale accuracy achieved over a wide current range. The system works at buck mode when charging the battery and at boost mode when discharging the battery.

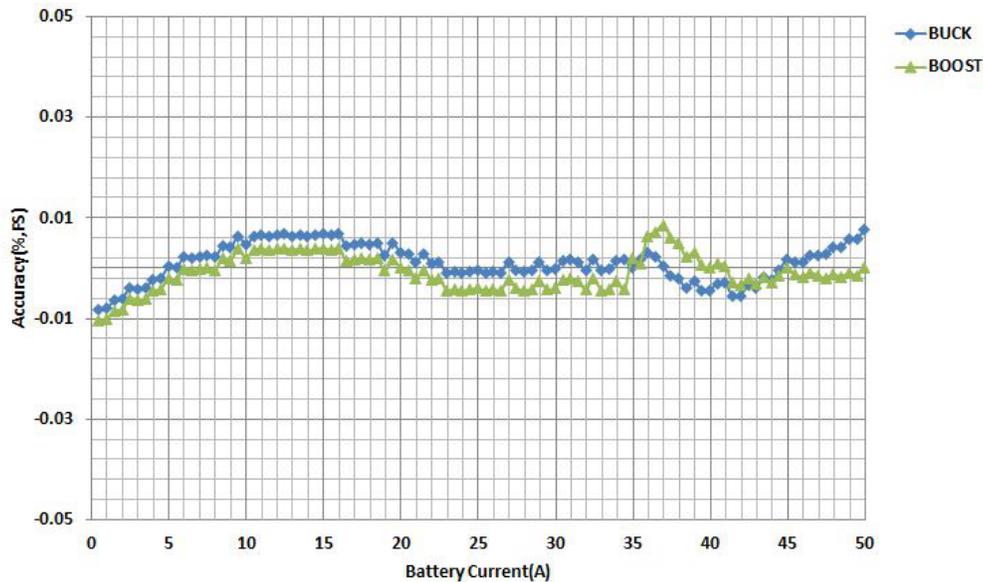

**Figure 2. Current Control Accuracy**


After power on, the CV control loop outputs a high voltage to the battery because of the low battery voltage. This output signal causes the CC loop to take the control of the system first. As the voltage of the battery rises, the system gradually transitions from CC control to CV control when it reaches the reference voltage level.

[Figure 3](#) shows the voltage control accuracy of the system with calibration when operating in buck mode.

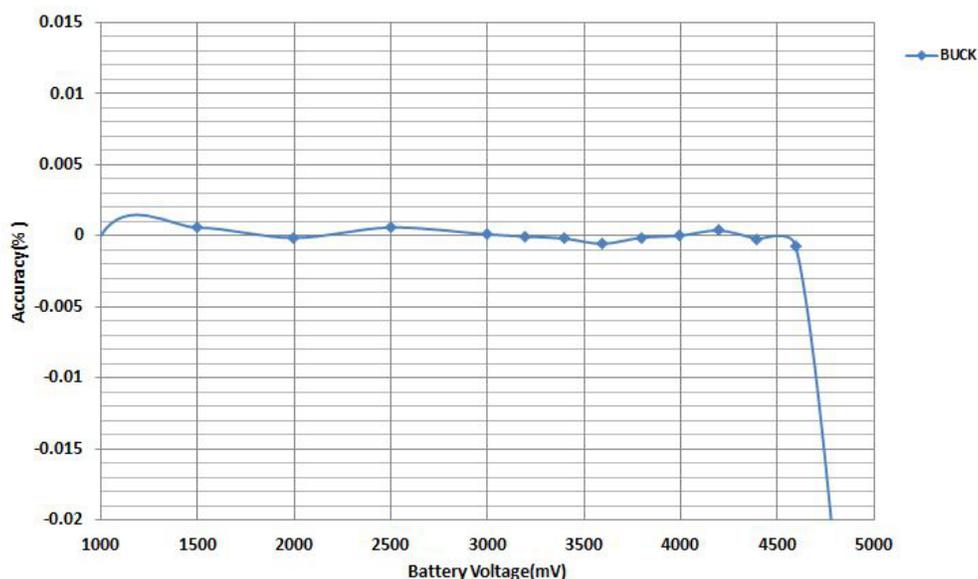


**Figure 3. Voltage Control Accuracy in Buck Mode**

Figure 4 shows the transition curve under different current conditions with the same voltage setting. The transition point in Figure 4 is different for different conditions because the voltage drop on the power transmission path increases with the increase of the current setting. Figure 5 shows the transition curve under different voltage conditions with the same current setting. These two curves show a smooth transition from CC to CV, indicating that the control system is stable.

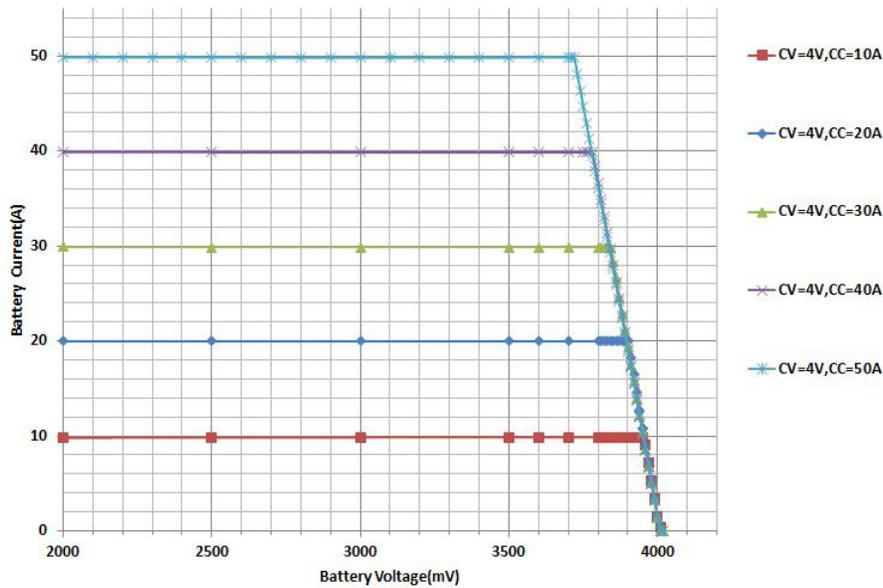

**Figure 4. CC/CV Transition with Different Current**

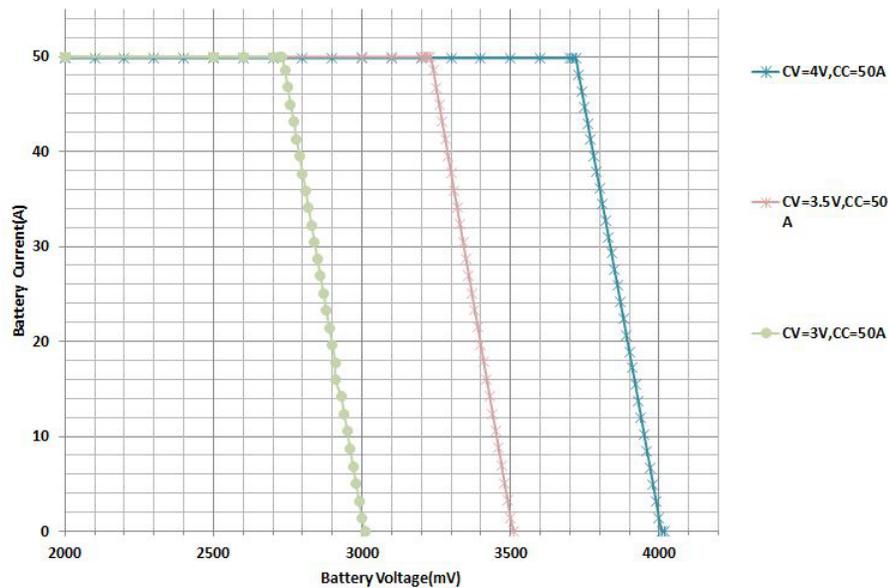

**Figure 5. CC/CV Transition with Different Voltage**

The reference design demonstrates how to achieve 0.01% full-scale charge and discharge current control accuracy leveraging CC and CV calibration loops, and it supports charge and discharge rates of up to 50A. For those needing to test 100-A applications, our [battery tester reference design for multi-phase high-precision 0.5 to 100-A battery formation](#) is a suitable alternative. That design is similar to our [battery tester reference design for high current applications](#) except that it uses two LM5170-Q1s to create four phases to reach the necessary 100 A while maintaining 0.02% current control accuracy.

---

## Additional Resources

- Read these other E2E™ Community blog posts:
  - [“How to charge and discharge battery test equipment.”](#)
  - [“How to choose the right charger for industrial batteries.”](#)
  - [“How to correctly lay out a 40A power supply: copper, vias and loop path.”](#)
- View [battery test equipment integrated circuits and reference designs](#).
- Check out these other TI Designs in the reference designs library:
  - [50A, 0.05% Current Accuracy Power Reference Design for Battery Test Systems](#).
  - [6A, 0.05% Current Accuracy Power Solution for Battery Test Systems Reference Design](#).

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated