

Harmeet Singh

Replacing existing meters (which still use technology developed decades ago), [smart meters](#) use a secure connection network to automatically and wirelessly send energy usage to utility companies. The heart of a smart meter is its switch-mode power supply (SMPS) using the low-cost flyback topology for both single- and three-phase smart meters.

The flyback converter shown in [Figure 1](#) operates by first storing energy from an input source into a transformer while the primary power switch is on. When the switch turns off, the transformer voltage reverses, forward-biasing the output catch diode(s) and delivering energy to the output(s). With a flyback topology, an output can be positive or negative (defined by a transformer polarity dot).

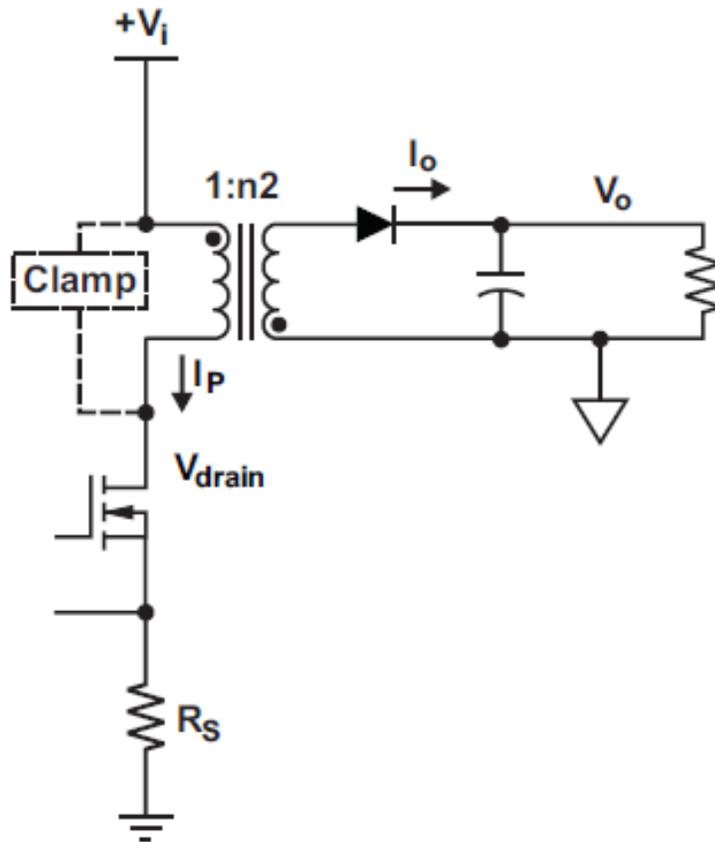


Figure 1. Basic Flyback Block Diagram

For multioutput, the technique is to have multiple windings on the transformer followed by a diode and capacitor circuit, as shown in [Figure 2](#).

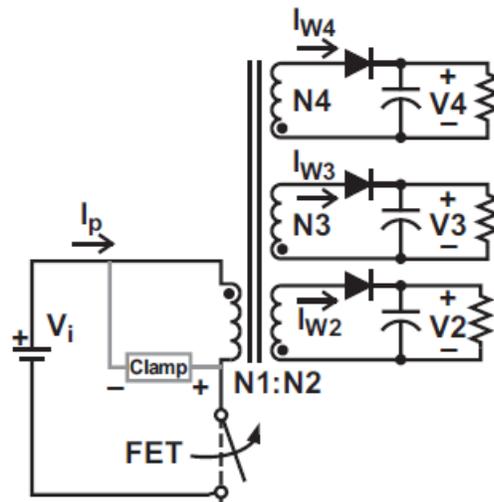


Figure 2. Multioutput Flyback Block Diagram

Figure 3 shows the block diagram of a single-/three-phase smart meter's SMPS scheme. The typical rails are:

- 3.3V for powering the microcontroller.
- 12V for latching relay for connection/disconnection.
- 6V-9V for isolated RS-485/RS-232 interfaces.
- 16V for programmable logic controller (PLC) communications.
- 3.8V-4.2V for Global System for Mobile Communications (GSM)/general packet radio service (GPRS) modem.
- 3.3V for the Sub-1 GHz radio-frequency (RF) module.
- 3.3V for the 2.4GHz RF module.

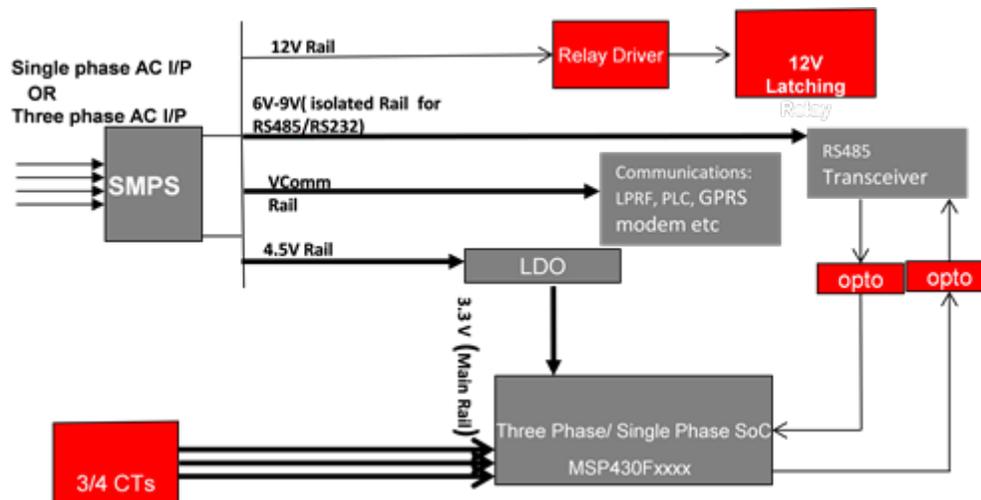


Figure 3. SMPS Scheme in a Smart Meter

In the multioutput flyback topology used in smart meters, one output is the master and the rest of the outputs are slaves. “One output is the master” means that the feedback loop is closed on that output; hence the master output is well regulated and the rest of the rails are quasi-regulated. Various techniques such as AC stacked winding, DC stacked winding and weighted feedback can improve regulation. But overload/short-circuit protection poses many challenges in a multioutput supply. The pulse-width modulation (PWM) controller will go into hiccup mode on overload or short circuit on any of the outputs. All of the voltage rails will collapse, as well as the main 3.3V rail powering the microcontroller. Because the microcontroller voltage rail has collapsed, it cannot measure energy, defeating the very purpose of a smart meter.

Figure 4 shows a proposed SMPS scheme with TI's electronic fuse (eFuse) to counter all of the issues and drawbacks mentioned in the present scheme. The TPS25921 can take care of the latching relay, PLC and RS-485/RS-232 interface rails, while the TPS25200 can take care of the Sub-1 GHz, zigbee® and GSM/GPRS modem communications rails.

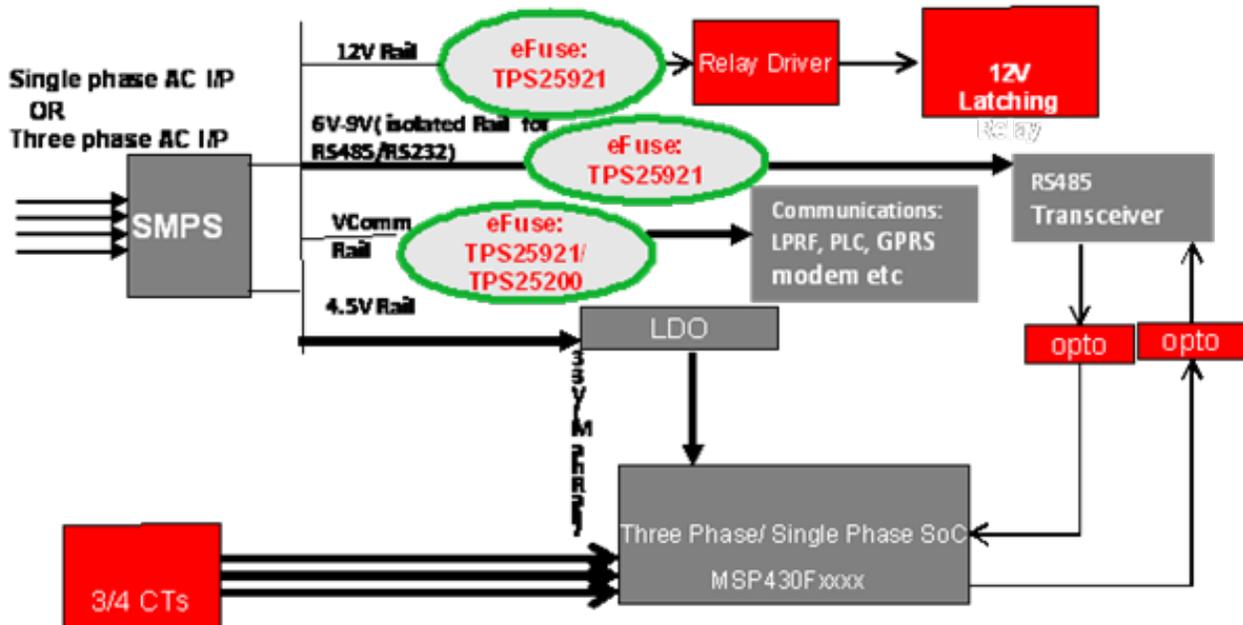


Figure 4. Proposed SMPS scheme in a smart meter

TI's eFuse is an active circuit protection device that will limit in-rush current and prevent load damage due to overcurrent events. It has an internal field-effect transistor (FET) to control the load current and integrates overcurrent and short-circuit protection. Figure 5 shows its block diagram.

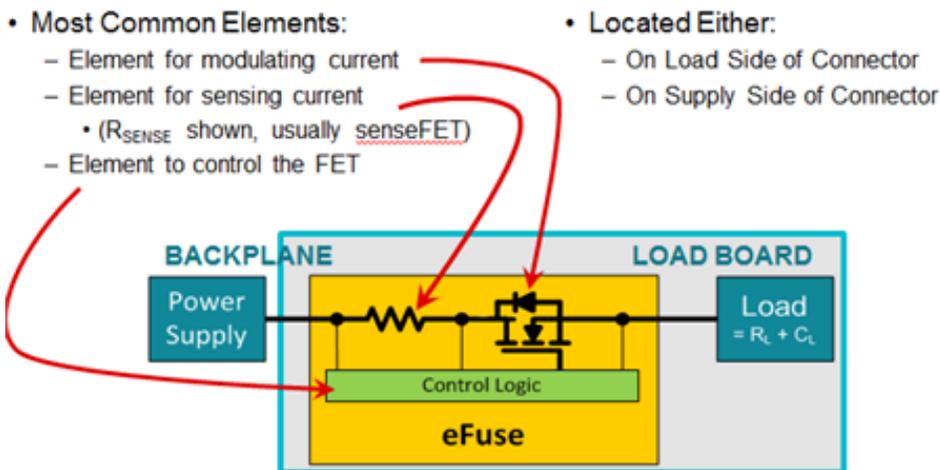


Figure 5. eFuse Block Diagram

The precision overcurrent limit helps minimize overdesign of the power supply, while the fast-response short-circuit protection immediately isolates the load from the input. These devices enable you to program the overcurrent limit threshold with an external resistor. Additional features include overtemperature protection to safely shut down in case of overcurrent and a choice of latched or automatic restart mode.

Thus, the eFuse device will help isolate a rail that experiences an overload or short-circuit event without affecting the main microcontroller rail (3.3V) that is measuring energy.

Additional Resources:

- Download the [Precision Power Limiting Solution](#) reference design
- Read the application report, “[UCC28722, Bias Supply Design Considerations for Intelligent eMeter Applications.](#)”
- Learn more about flyback SMPS design for smart meters with the [Snubberless, Non-Isolated AC/DC Flyback Converter Reference Design with Simplified Transformer](#)
- Check out these other E2E™ Community blog posts:
 - “[Solving the biggest challenges when designing smart meter power supplies.](#)”
 - “[Power Tips: Design considerations of high-voltage converters in a cascode MOSFET.](#)”
- Learn more about [electricity meter application](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated