

Shining a Light on Op Amps: Considerations in LED Lighting



Wen-Shin Wang

As a college student, I would often drive back to my dorm room very late at night. On my route, I would always have to drive on a long stretch of road with lots of overhanging trees on either side. It was beautiful by day but terrifying at night, as it seemed like other students would randomly pop out to walk right in front of my car.

Thankfully, my LED headlights were able to illuminate my fellow night owls. And behind the scenes, helping ensure that my headlights worked, was an often tiny but important device – the operational amplifier (op amp). In this blog post, I'll cover the key parameters to consider when choosing an op amp for an external lighting application.

Before we drill down on the op amp, let's summarize how LED lighting works. The current of the LED is the main consideration for lighting systems, as it controls the brightness and intensity of the light. The LED actually pulses a modulated light at above 200Hz – which the human eye averages out.

Because the LED current controls the brightness and intensity of the light, the op amp is often used as a current sense to help control the current going into the LEDs. High-current peaks in the pulse-width modulation (PWM) signal can overshoot the LED's specified current level and negatively impact its life span. [Figure 1](#) below shows the overall system block diagram of a LED headlight and where the op amp is used in the application.

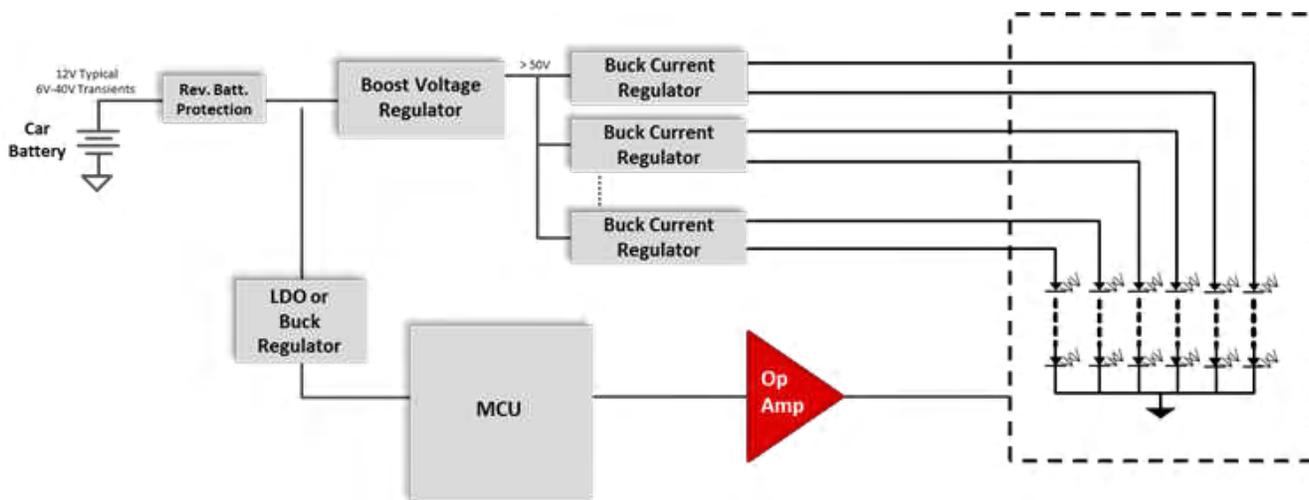


Figure 1. High-level System Block Diagram of LED Headlamp Lighting

To pick a suitable op amp as a current sense, it should have:

- Low offset voltage (V_{os}) to enable better accuracy for the current output to the LED
- Low drift over temperature to help the system achieve constant brightness over various temperature ranges.
- High output-current capability (in some cases) to drive the LED if the op amp directly connects to it (rather than to a buffer or transistor).
- Rail-to-rail capabilities to maximize the signal input and output, and avoid clipping.

As cost is always a strong factor in these systems, TI offers a wide range of op amps suitable for external lighting applications, such as the [TLC2272A-Q1](#) or [TLV2372-Q1](#). For higher-resolution needs, the [OPA365-Q1](#) is another option due to its wide bandwidth, very low offset and rail-to-rail output (RRO) features.

As the sun starts setting earlier, don't forget about these op amps when you turn on your headlights and drive home into the night. See TI's wide automotive op amp portfolio [here](#), and visit TI's body electronics and lighting overview page [here](#) for more information on system-level needs

Additional Resources

- For more information about the power considerations in LED lighting, see the following blog posts below:
 - [“Improving road safety by the headlight: LED matrix manager”](#) about the [TPS92661-Q1](#)
 - [“Lighting the road ahead: LEDs in automotive front lighting”](#) about the [TPS92515HV-Q1](#)
 - For other op amp alternatives in headlight, see [“Using dual high-current op amps to drive automotive LED lights”](#) about the [ALM2902-Q1](#)
 - View [TIDM-AUTO-DC-LED-LIGHTING](#) to see how op amps ([OPA4322-Q1](#) and [LM2902-Q1](#)) are used in headlight applications

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated