

# Power Tips: Simple PSRR Measurement with a Frequency Analyzer



Josh Mandelcorn

The power supply rejection ratio (PSRR) is the power supply's ability to reject ripple voltage applied at the input. This is normally done by adding a [high-current power amplifier](#) in series with the input source, driving it with a frequency-swept signal from a signal analyzer, and measuring the ratio of  $V_{IN}$  to  $V_{OUT}$  at each measured frequency. These power amplifiers are expensive, however, and easily damaged during testing. In this post, I'll explain how to dispense with the power amplifier by repurposing a voltage-loop analyzer and making a few low-cost modifications.

## Test Setup

See [Figure 1](#) below: I placed a small resistance in series with the input to apply a frequency-swept AC (Alternating Current) signal at  $V_{IN}$ , injected by a signal transformer. The signal is actually applied across the small resistance. I placed three  $0.15\Omega$  resistors in series, each rated at 3W, to get  $0.45\Omega$ . I adjusted the input to achieve the target 3.3V at the DC/DC (Direct Current to Direct Current) converter input.

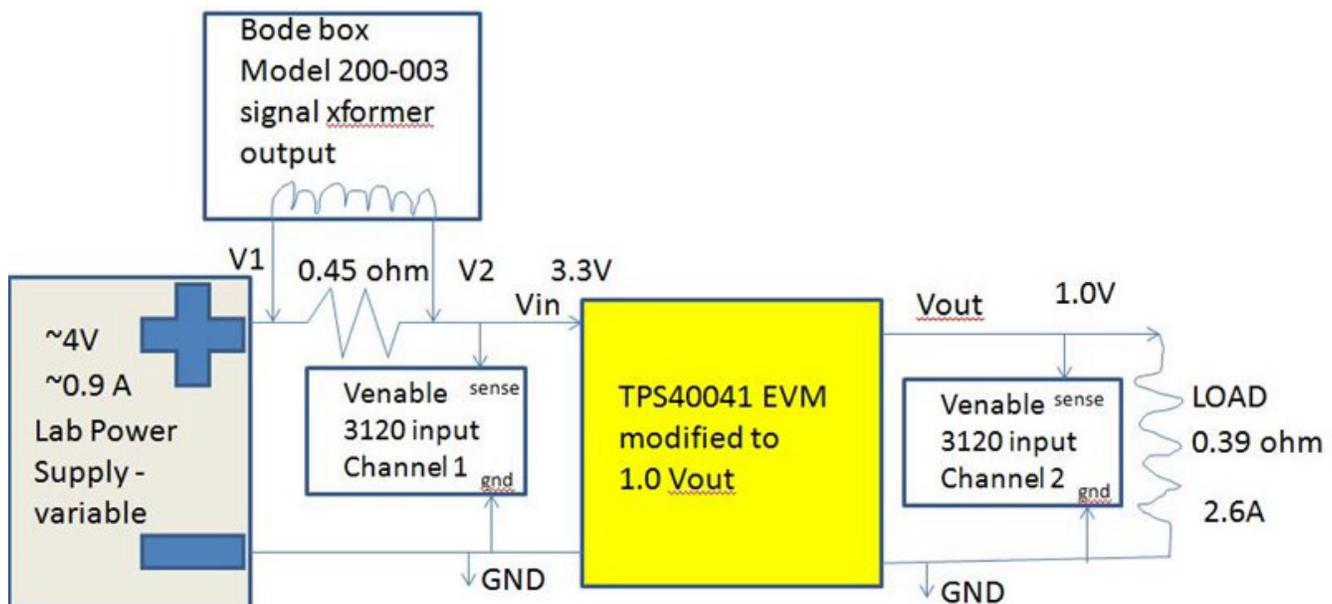


Figure 1. Test Setup

I used a Venable 3120 frequency analyzer with “Bode boxes” and made some modifications.

Typically, the Bode boxes are set up to inject an isolated signal between  $V1$  and  $V2$ , and to connect the  $V1$  and  $V2$  signals and ground from the converter under test to the  $V1$  and  $V2$  and ground inputs of the frequency analyzer. This enables one to measure loop gain with only three connections to the converter under test.

Using these same connections for both signal injection and measurement can introduce errors, however, as described in the post, [“Power Tips: How connection wires affect Bode plot measurements.”](#) Author Manjing Xie advises using the transformer connections only for injecting signals and having separate connections for measuring  $V1$  and  $V2$ .

With PSRR measurements where  $V_{OUT}$  is not connected to the injection transformer point, the V2 measurement would in any case need to be separate from the transformer connections. In my test, I injected signals through the Bode box, and had separate connections to measure both V1 ( $V_{IN}$ ) and V2 ( $V_{OUT}$ ).


I used the [TPS40041 EVM – 001](#) evaluation module with one modification of R5 from 10k to 30.1k to change  $V_{OUT}$  from 1.8V to 1.0V. Switching frequency was at 565-567kHz.

I tested at both no load and 2.6 A load off the 1.0V output.


I used the following generator settings and Bode boxes on the Venable 3120 for the different frequency ranges and took 20 points of data per frequency decade:

- For the 100Hz to 1kHz range I used the 100Hz to 10kHz Bode box (model 200-002) and 1V RMS (Root Mean Square) out of the generator.
- For the 1kHz to 100kHz range I used the 1kHz to 100kHz Bode box (model 200-003) and 1V RMS out of the generator.
- For the 100kHz to 1MHz range I used the 1kHz to 100kHz Bode box (model 200-003) and 10V RMS out of the generator.

The PSRR results are shown below in [Figure 2](#) for 2.6A load off the 1.0  $V_{OUT}$  and in [Figure 3](#) for no load. The ratio of  $V_{OUT}/V_{IN}$  in is shown in red in dB (decibels). The phase relationship is shown in blue in degrees.

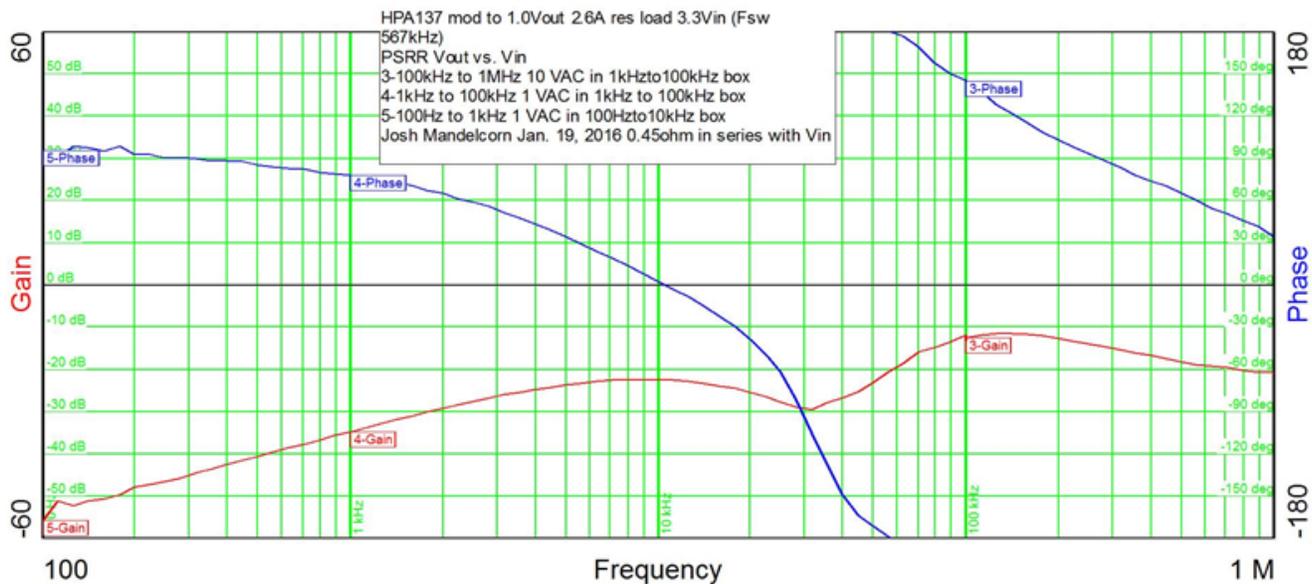

**Figure 2. PSRR of Modified TPS40041 EVM at a 2.6A Load**

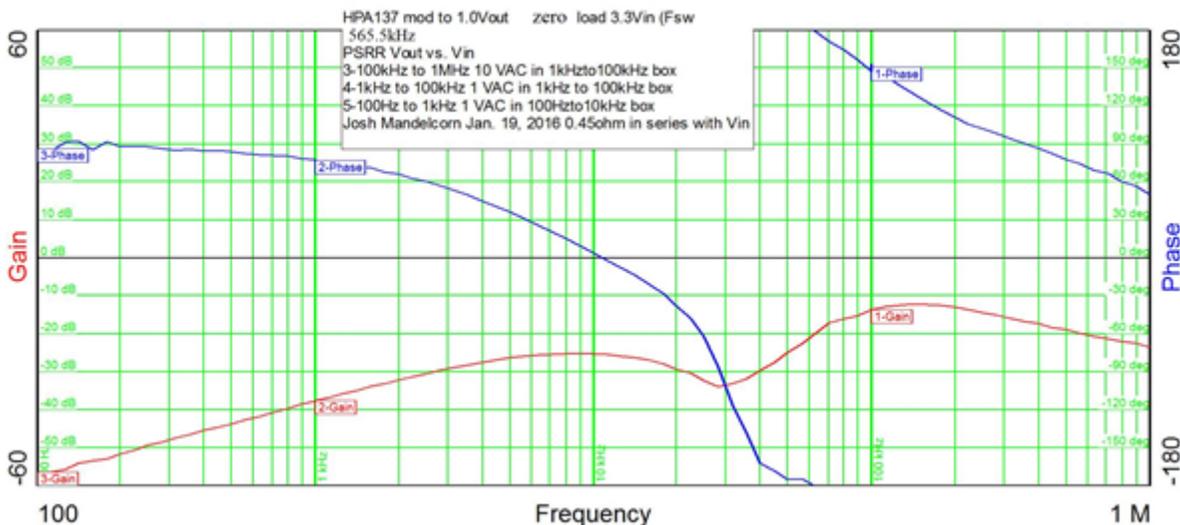

**Figure 3. PSRR of Modified TPS40041 EVM at No Load**

Gain and phase patterns are very similar for no load and 2.6A load with attenuation slightly better at no load by about 3 dB at most.

The [TPS40041](#) buck DC/DC controller does not have feed-forward input-voltage compensation in which the pulse-width modulator ramp is proportional to  $V_{IN}$  to improve input-voltage rejection. For controllers with feed-forward compensation such as the [TPS40170](#) PWM buck controller, you should expect an even more improved PSRR.

Now you should be able to eliminate the power amplifier by repurposing a voltage-loop analyzer and making a few low-cost modifications. Order the [TPS40041 evaluation module](#) or [TPS40170 evaluation module](#) and try conducting a similar test yourself.

#### Additional Resources

- Watch Power Tips [videos](#) to help with your design challenges.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated