

# Timing Is Everything: Improving Integer Boundary Spurs in Fractional PLL Synthesizers



Dean Banerjee

Have you ever done a phase-locked loop (PLL) design with a fractional synthesizer that looked great at integer channels, but then the spurs got much higher on frequencies that were just slightly offset from those integer channels? If so, you have experienced the integer boundary spur, which occurs at an offset from the carrier equal to the distance to the closest integer channel.

For instance, if the phase-detector frequency is 100 MHz and the output frequency is 2001 MHz, the integer boundary spur would be 1 MHz offset. In this case, 1 MHz might be tolerable. But when the offset gets too small, but is still nonzero, the fractional spurs are worse.

## Integer Boundary Spur Reduction Using a Programmable Input Multiple

The concept of the programmable multiplier is to shift the phase detector frequency so that the voltage-controlled oscillator (VCO) frequency is far from an integer boundary. Consider a 20-MHz input frequency used to generate an output frequency of 540.01 MHz, as shown in [Figure 1](#). The device has an output divider after the VCO, but both the output frequency and the VCO frequency are close to an integer multiple of 20 MHz. This setup would stress any PLL for fractional spurs.

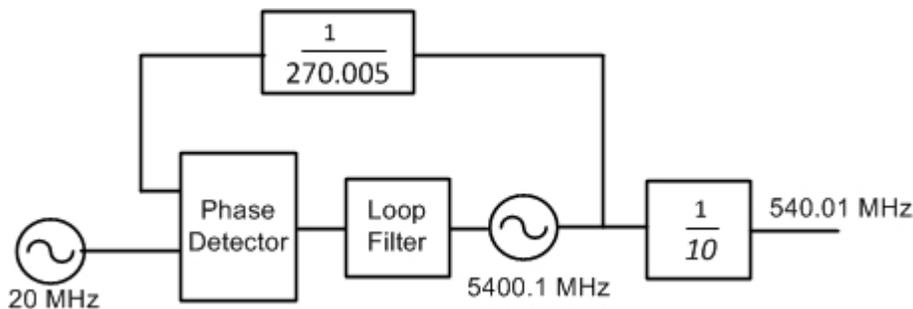


Figure 1. Integer Boundary Spur Example

If the device has a programmable input multiplier, then the configuration shown in [Figure 2](#) is possible.


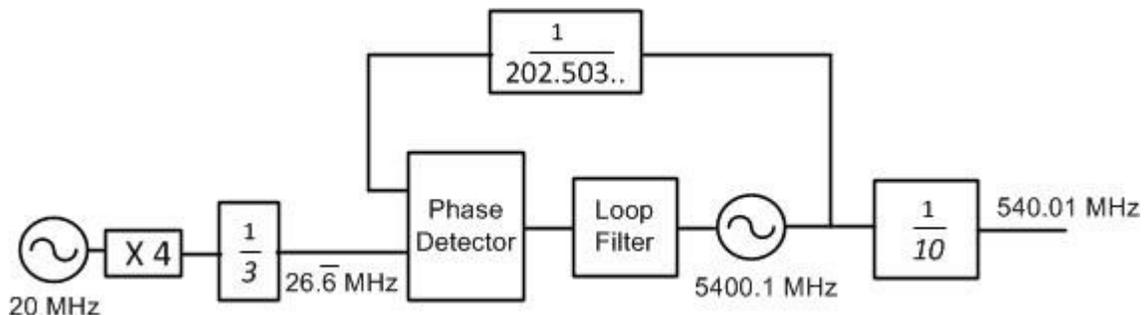


Figure 2. Avoiding Integer Boundaries Using a Programmable Multiplier

[Figure 3](#) shows the impact of the internal multiplier. Integer boundary spurs have multiple mechanisms, and it is difficult to completely eliminate them. But this method both reduces the integer boundary spur as well as other spurs that spawn from it.

The “spur-b-gone” trace in [Figure 3](#) shows the impact of using this programmable multiplier. There is an approximate 9-dB reduction in the integer boundary spur at 100 kHz, while substantially reducing other spurs at 50 kHz and 10 kHz.

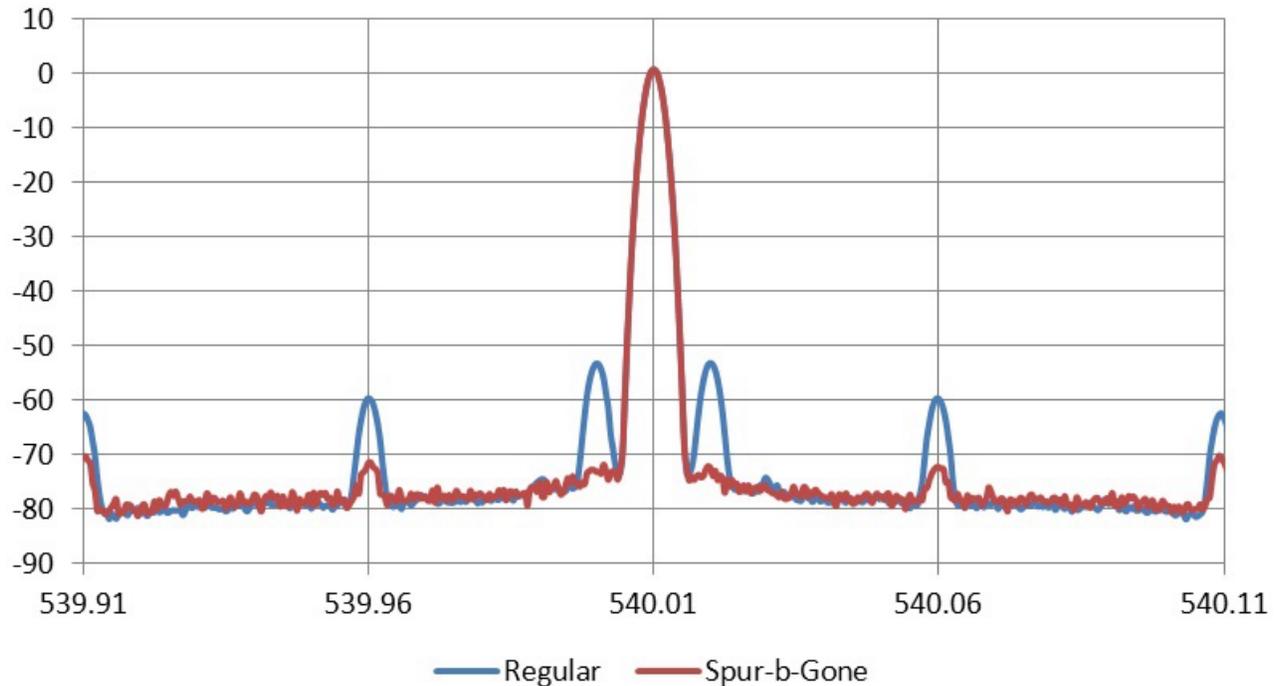

**Figure 3. Spur Comparison with and without Programmable Multiplier**

The examples shown were done with the TI’s [LMX2571](#) synthesizer, which includes a programmable multiplier that requires no external components. This device also features 39-mA current consumption, a PLL figure of merit of  $-231$  dBc/Hz, and a continuous output frequency range of 10–1344 MHz. It can support applications including land mobile radios, software-defined radios and wireless microphones.

#### Additional Resources

- View the [datasheet](#) for the [LMX2571](#).
- Watch the [demonstration video](#) for the [LMX2571](#).
- See TI’s entire portfolio of high-performance, low-jitter [clock and timing](#) ICs.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated