

Technical Article

Simple Circuit Drives TECs



Chris Glaser

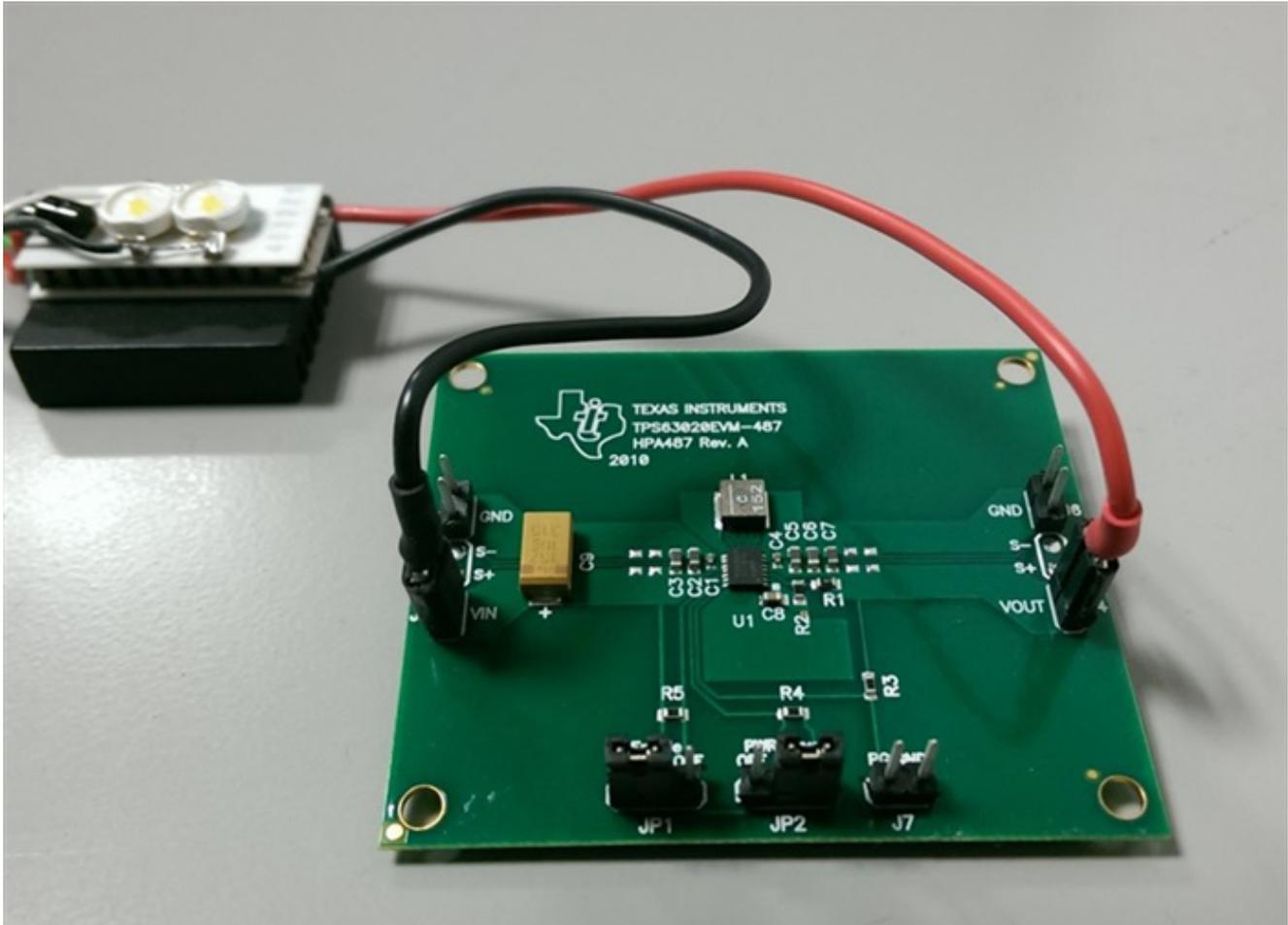


Figure 1. PMP9759 Is a Simple Circuit Which Drives TECs

In [optical networking modules](#) and other [communications systems](#), you may have to precisely control the temperature of a certain component. Lasers, for example, need a specific temperature in order to emit a certain wavelength of light. A thermoelectric cooler (TEC), shown in [Figure 1](#), is a common device used to either heat or cool a component in such systems.

Using a single element like a TEC for heating or cooling requires the power supply supplying the TEC to source and sink output current. Sourcing current through the TEC cools, while sinking current from the TEC heats. Using a TEC requires a bidirectional current flow, but only certain [power supplies](#) are configurable to both source and sink current. Even fewer power supplies are capable of sourcing and sinking the higher currents necessary for larger TECs. [TI Design](#) reference design [PMP9759](#) details the implementation of such a circuit, which is capable of sourcing up to 1.5A through the TEC.

In [PMP9759](#), the [TPS63020 buck-boost converter](#) is operated in forced pulse-width modulation (PWM) mode to achieve the ability to both source and sink. The [TPS63020](#) is a good fit for optical networking applications, which are frequently powered from 3.3V. As well, it has a wide output voltage range of 1.2V to 5.5V. Such a wide range

allows the most current flow through the TEC because it generates higher voltages across the TEC. Attaching the TEC from the input voltage to the output voltage instead of from the output voltage to ground enables a bidirectional current flow. Current flows in one direction to heat and the other to cool.

The onboard [microcontroller \(MCU\)](#) measures the temperature of the TEC and outputs either an analog or digital PWM signal to adjust the current sourced or sunk by the [TPS63020](#). Sending this signal into the feedback pin of the [TPS63020](#) adjusts the TEC current. Adjusting the current adjusts the temperature of the TEC, which is then fed back to the MCU, resulting in a [closed-loop system](#) that properly controls temperature. [Figure 2](#) shows the complete circuit.

In What Systems Do You Need Bidirectional Current Capability?

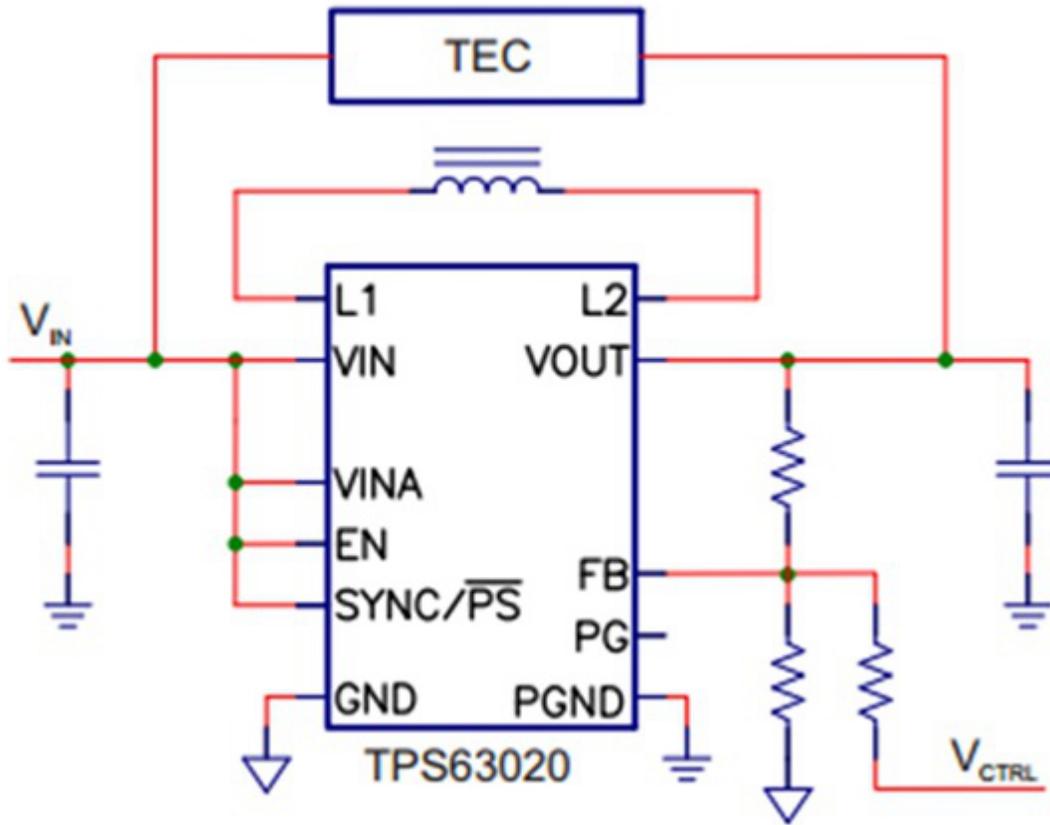


Figure 2. The [TPS63020](#) Simply Implemented as a TEC Driver

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated