

Test Report: PMP30603

-60 V Inverting buck-boost reference design




Description

This tiny reference design delivers -60 V output voltage from an input voltage around 5V typically generated by an automotive pre regulator. The controller in that circuit is LM5161-Q1 providing two internal MosFETs.

In general this converter is used as auxiliary supply for LiDAR applications. Due to duty cycle limitations some controllers are limited inverting 5V input to -60V output – PMP30602 and PMP30603 are offering cost effective solution to do so.

Features PMP30603:

- Small board space 35mm x 30mm, two layers, single side assembly
- Internal FETs providing synchronous rectification
- Capability to drive up to 40mA peak for pulsed applications
- Temperature rise less than +30K at full load
- Load regulation 30mV means only 0.05% output voltage deviation
- No switch node ringing results in low radiated emissions
- Output voltage ripple only around 100mVpp to supply sensitive load

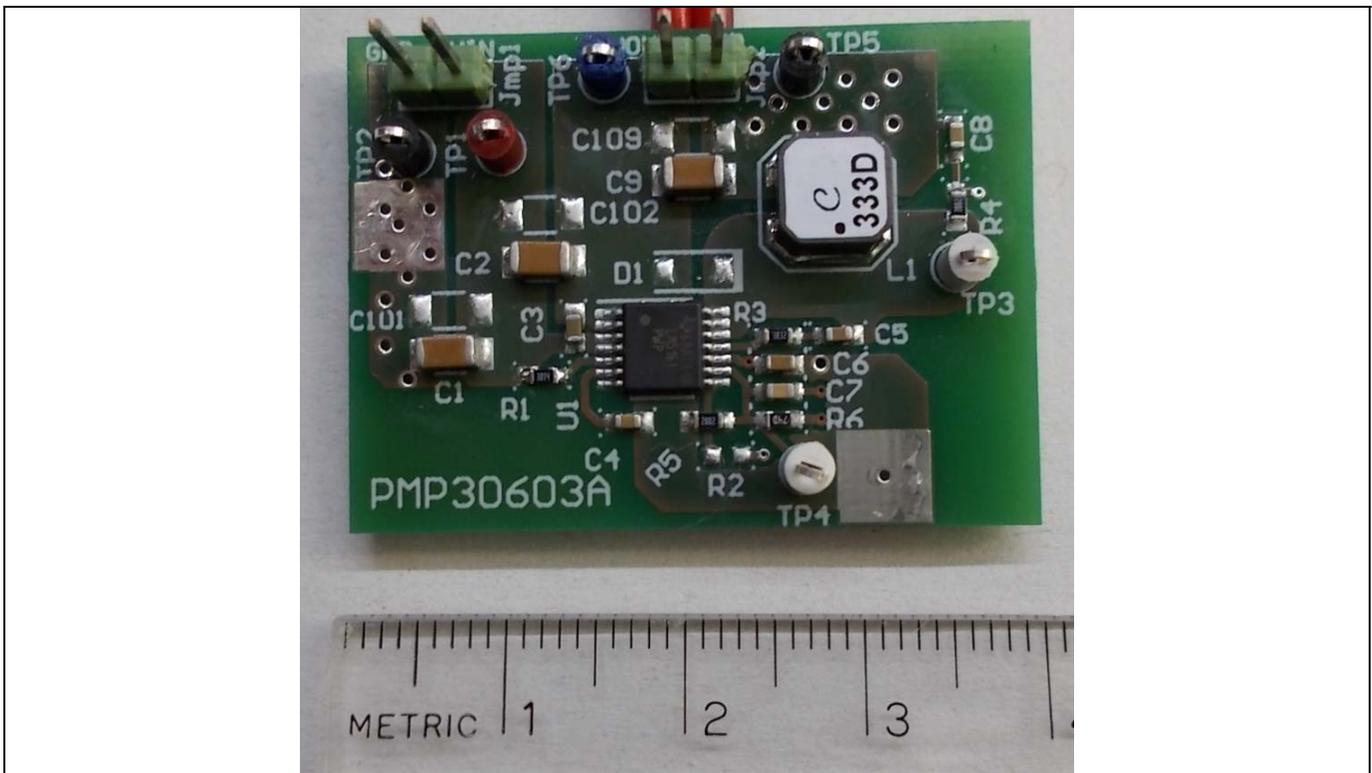

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements

| PARAMETER | SPECIFICATIONS |
|------------------------|----------------|
| Input Voltage Range | 4.5 V to 5.5 V |
| Output Voltage | -60 V |
| Maximum Output Current | 20 mA |

1.2 Considerations

The switching frequency is around 208 kHz.

Unless otherwise mentioned, all measurements were done with 5 V input voltage and 20 mA.

The circuit starts with switching with 4.5 V.

Resistors were used as load.

2 Testing and Results

2.1 Efficiency Graphs

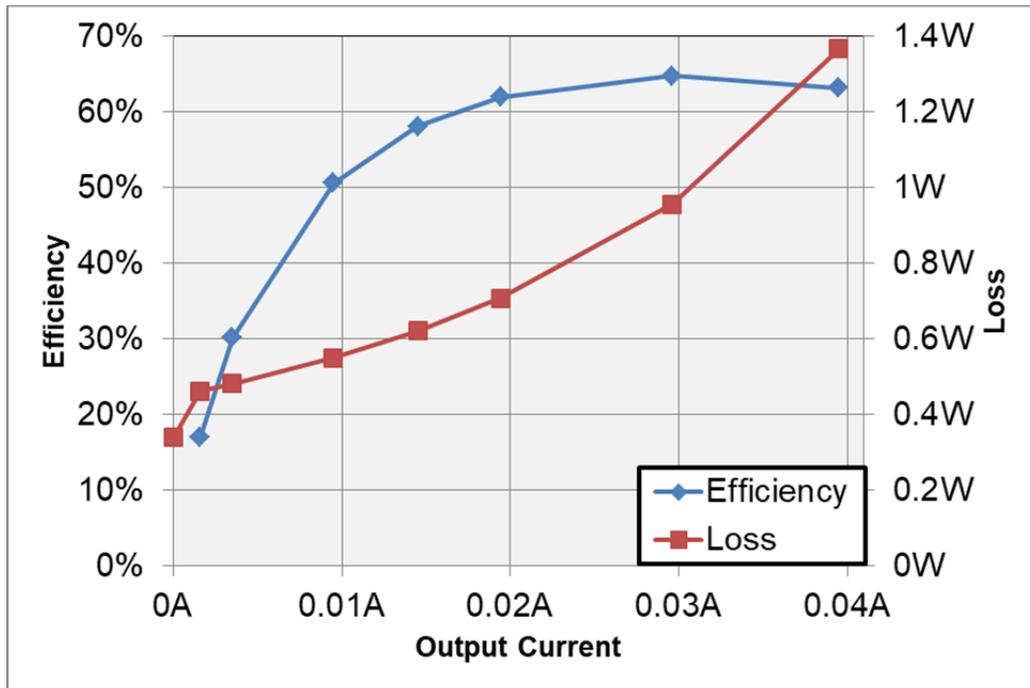


Figure 1 Efficiency and Loss vs Output Current

2.2 Load Regulation

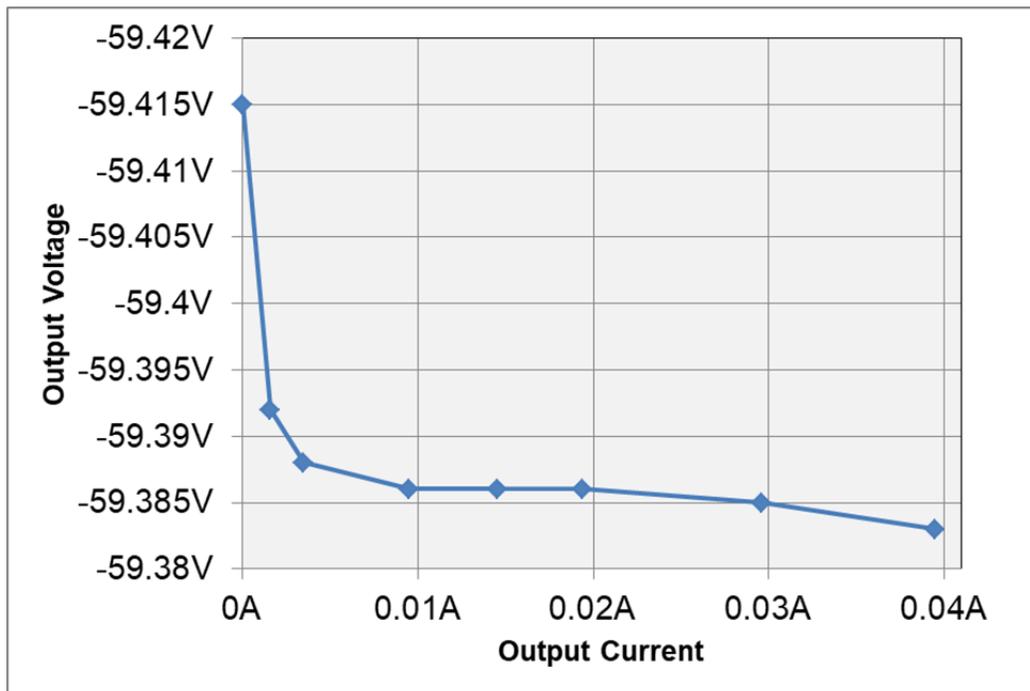


Figure 2 Output Voltage vs Output Current

2.3 Thermal Images

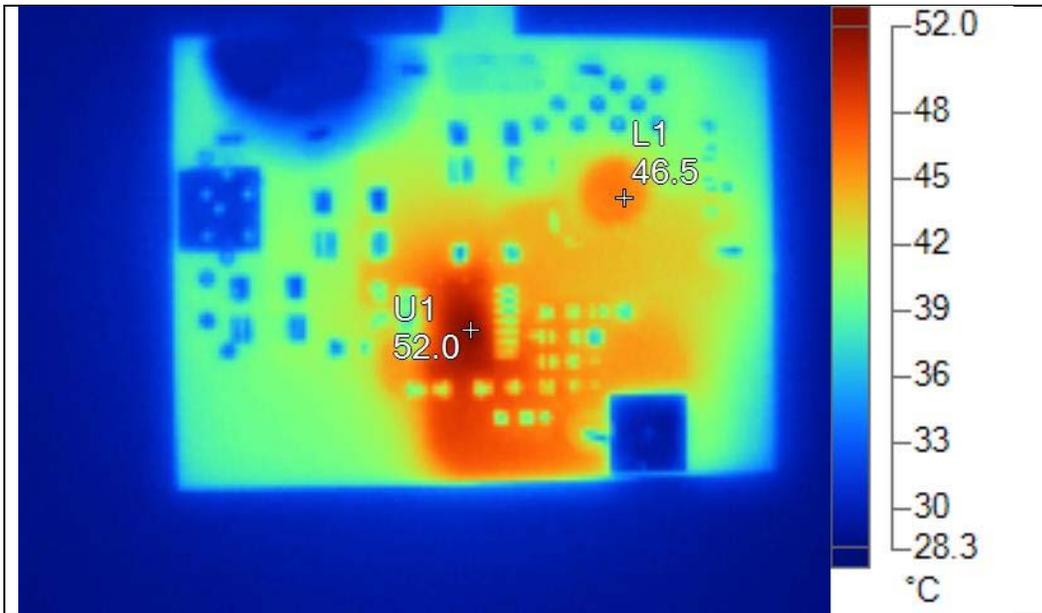


Figure 3 thermal IR-Foto

| Name | Temperature |
|------|-------------|
| L1 | 46.5°C |
| U1 | 52.0°C |

3 Waveforms

3.1 Switching

3.1.1 TP3 to GND

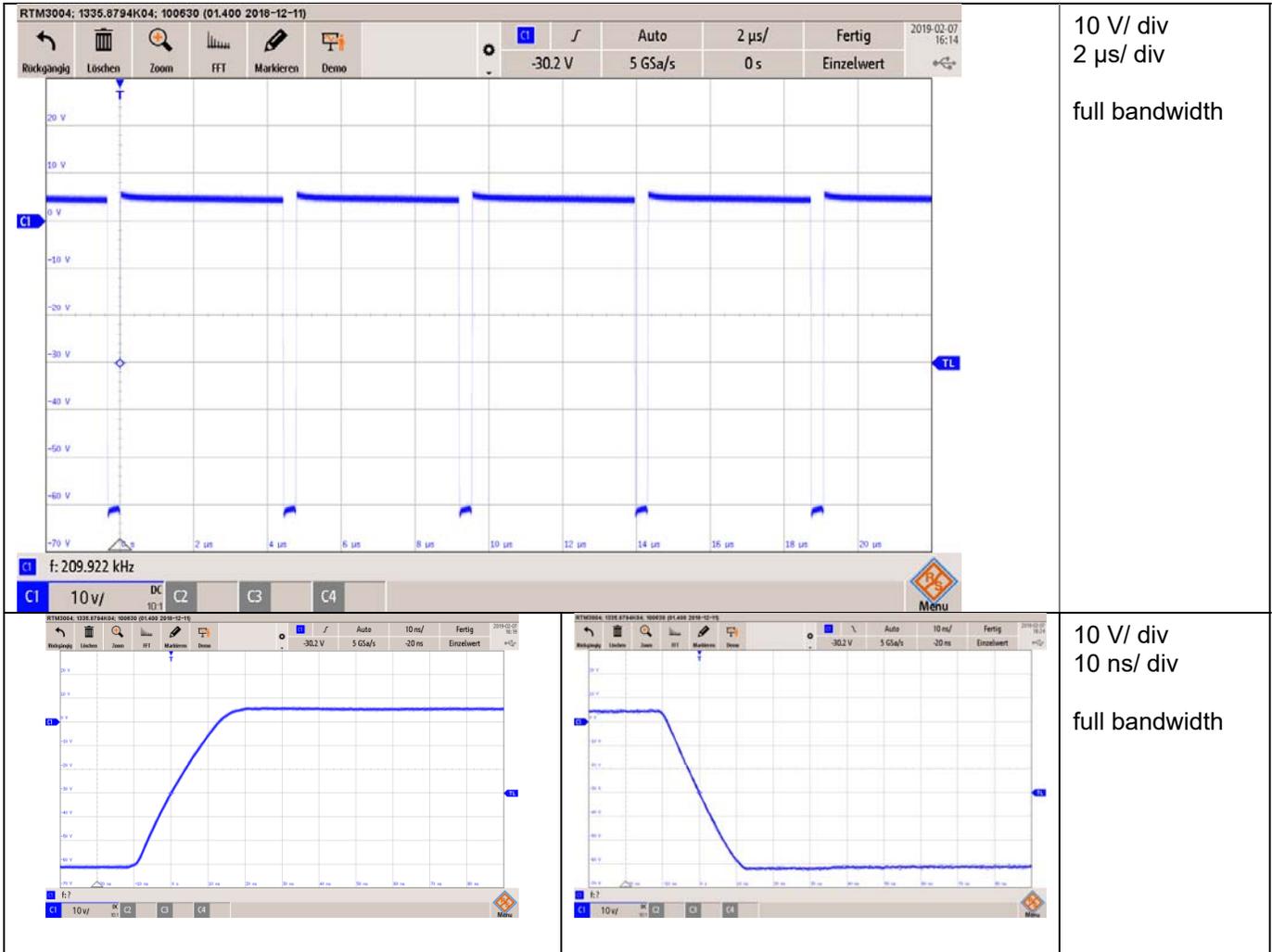


Figure 4 Switchnode (TP3)

3.2 Output Voltage Ripple

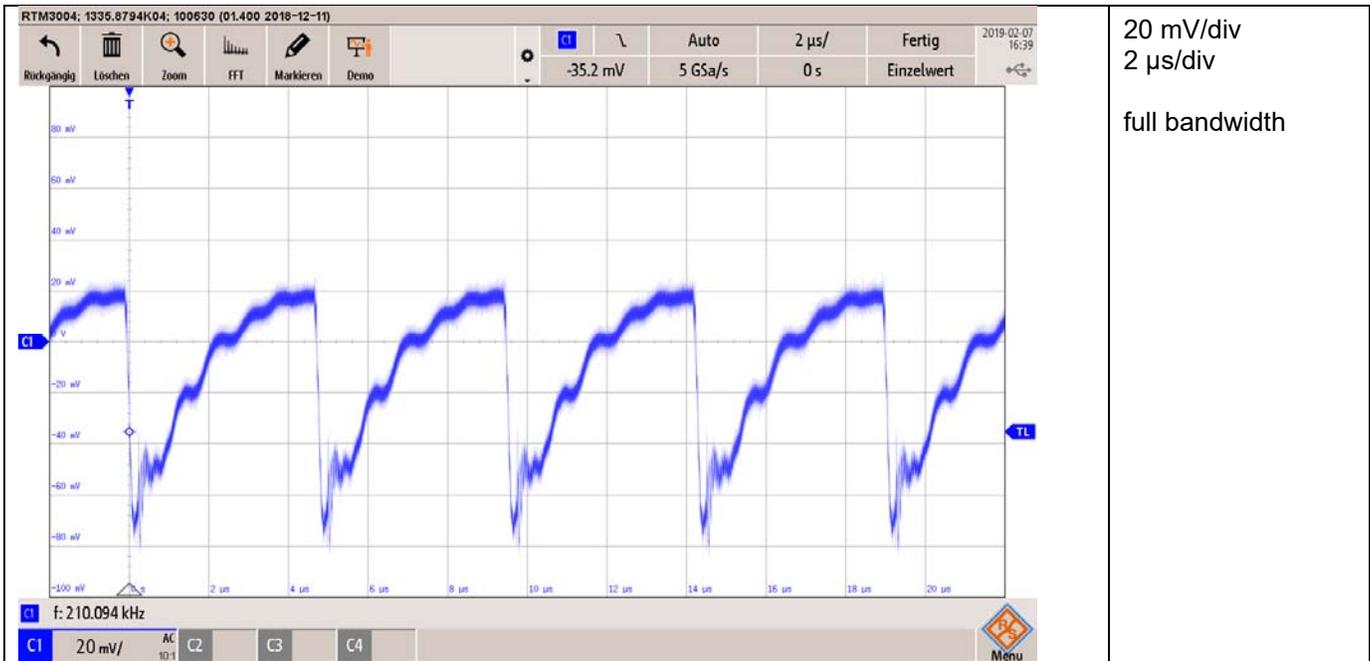


Figure 5 Output Voltage Ripple

3.3 Input Voltage Ripple



Figure 6 Input Voltage Ripple

3.4 Start-up Sequence

Power supply was plugged in.

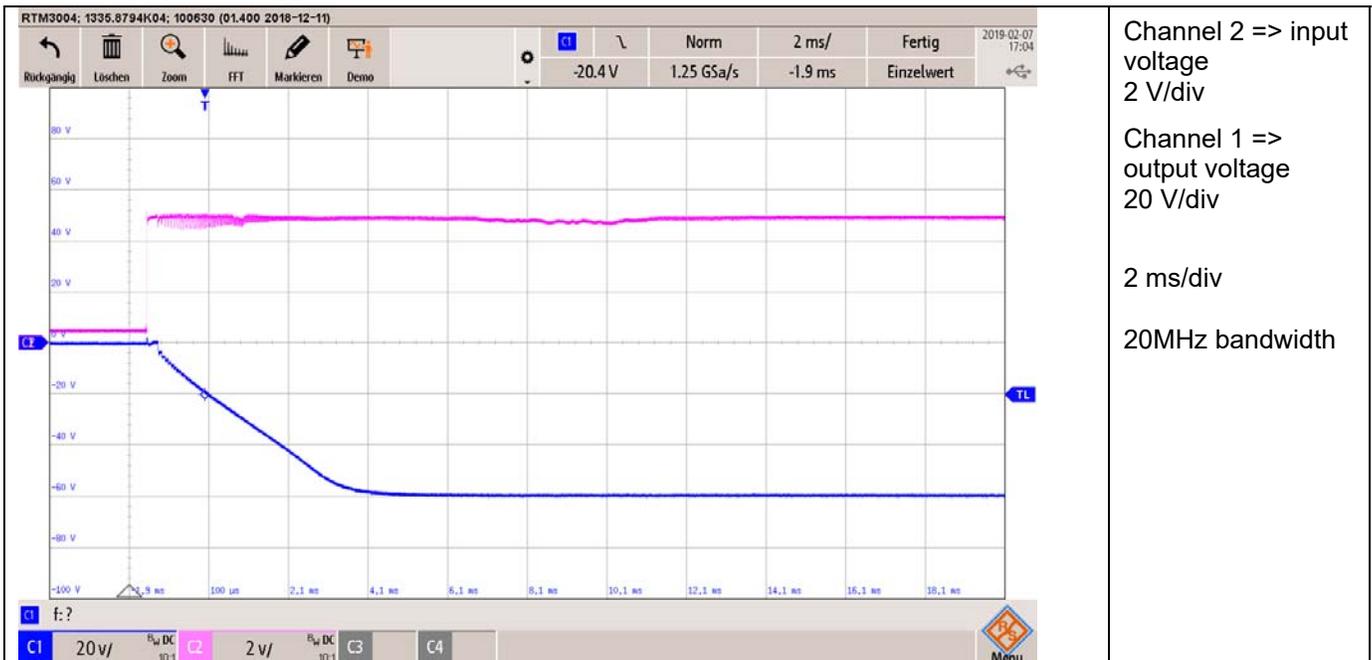


Figure 7 Start-up Sequence

3.5 Shutdown Sequence

Power supply was disconnected.



Figure 8 Shutdown Sequence

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated