

4-W Discontinuous Conduction Mode Primary Side Regulated Flyback Reference Design



Description

This tiny 4-W flyback converter with additional three isolated output windings generates four outputs in total. With a windings ratio of 1:1 in between the primary and auxiliary winding, the conventional RCD snubber could be replaced by an AC flying capacitor providing better efficiency and lower EMI, but this requires the lowest leakage inductance.

The input is in the automotive range of 7 V up to 42-V surge, three outputs are post-regulated by LDO to improve line and load regulation and power supply ripple rejection (PSRR).

A differential input filter has been added to attenuate conducted emissions, and a Schottky rectifier acts as reverse-polarity protection.

As for all multi-output primary-side regulated approaches using general purpose controllers *no load* at the auxiliary windings is a limitation for cross regulation.

Features


- Three isolated outputs \Rightarrow 12 V, 5 V, and 3.3 V and one single non-isolated output \Rightarrow 5 V
- Both 5-V outputs and the 3.3-V output are post-regulated for the lowest possible noise
- Differential input filter to prevent from reflected ripple
- Temperature rise less than +35 K at full load
- A table for all sixteen load combinations with light load and full load is provided

Applications

- [Automotive HVAC compressor module](#)



Board Photo (Top)

 

Board Photo (Bottom)

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

Parameter	Specifications
Input Voltage Range	7 V to 27 V, 42-V surge
Output Primary Side	5 V at 0.05 A _{max}
Output 1 Secondary Side	12 V _{nom} , 11 V to 14 V at 0.17 A _{max}
Output 2 Secondary Side	5 V at 0.05 A _{max}
Output 3 Secondary Side	3.3 V at 0.3 A _{max}
Switching Frequency	250 kHz

1.2 Considerations

Resistors were used as load.

Unless otherwise mentioned, the input voltage was adjusted to 12 V and the output current was determined by resistors. The resistor values were calculated for nominal output voltage for reaching the maximum output current for each single output.

1.3 Dimensions

The size of the board is 80 mm × 39.4 mm. The two-layer board was manufactured with 35-μm copper thickness on each layer.

2 Testing and Results

2.1 Efficiency Graphs

Efficiency is shown in [Figure 2-1](#).

 


Figure 2-1. Efficiency vs Percentage of Load

2.2 Loss

[Figure 2-2](#) shows the loss versus percentage of load graph.

 


Figure 2-2. Loss vs Percentage of Load

2.3 Load Regulation

All of the outputs in [Figure 2-3](#) through [Figure 2-7](#) are measured at the same percentage loading.

2.3.1 5-V Output Voltage

 


Figure 2-3. 5-V Output Voltages vs Output Current at LDO Output

Note

[Figure 2-4](#) illustrates LDO inputs at 5 V.

 


Figure 2-4. Voltages at 5-V LDO Inputs vs Output Current

2.3.2 3.3-V Output Voltage

 


Figure 2-5. Output Voltage vs Output Current

Note

Figure 2-6 illustrates LDO inputs at 3.3 V.


 


Figure 2-6. Voltage at 3.3-V LDO Input vs Output Current

2.3.3 12-V Output Voltage

 

Due to peak detection at **zero** load, this output needs to be clamped by Zener diode or minimum load.

Figure 2-7. 12-V Output Voltage vs Output Current

2.4 Line Regulation

The input voltage was varied from 7 V to 27 V.

2.4.1 5-V Outputs

 


Figure 2-8. 5-V Output Voltages vs Input Voltage

Figure 2-9 shows voltages measured before the corresponding LDOs.

Note

Figure 2-9 illustrates LDO inputs at 5 V.

 


Figure 2-9. 5-V LDOs Input Voltages vs Input Voltage

2.4.2 3.3-V Output Voltage


 


Figure 2-10. 3.3-V Output Voltage vs Input Voltage

2.4.3 12-V Output Voltage

 

Due to peak detection at **zero** load, this output needs to be clamped by Zener diode or minimum load.

Figure 2-11. 12-V Output Voltage vs Output Current

2.4.4 Efficiency and Loss in Dependence of Input Voltage

 


Figure 2-12. Efficiency vs Input Voltage

 


Figure 2-13. Loss vs Input Voltage

2.5 Cross Regulation Light Load and Full Load

2.5.1 Bias Current 1 mA

Table 2-1. Cross Regulation With Bias Current set to 1 mA

primary			secondary							
5 V	LDO in	LDO out	3.3 V	LDO out	LDO in	5 V	LDO out	LDO in	12 V	out
0	6.142	4.98	0	3.3	3.899	0	4.995	6.134	0	11.93
0	6.141	4.979	0	3.3	3.59	0	4.994	5.645	1	10.581
0	6.14	4.979	0	3.3	3.84	1	4.98	5.736	0	11.79
0	6.14	4.979	0	3.3	3.511	1	4.98	5.313	1	10.369
0	6.14	4.979	1	3.123	3.187	0	4.994	5.659	0	11.248
0	6.139	4.978	1	2.995	3.056	0	4.994	5.18	1	9.752
0	6.139	4.978	1	3.11	3.173	1	4.978	5.245	0	11.043
0	6.138	4.978	1	2.939	3	1	4.822	4.887	1	9.563
1	6.14	4.964	0	3.301	4.168	0	4.994	6.532	0	12.7
1	6.139	4.963	0	3.3	4.015	0	4.992	6.28	1	11.8
1	6.138	4.963	0	3.3	4.116	1	5.023	6.165	0	12.57
1	6.138	4.962	0	3.3	3.995	1	5.019	6.044	1	11.75
1	6.137	4.962	1	3.3	3.653	0	4.991	6.283	0	12.38
1	6.137	4.962	1	3.299	3.689	0	4.99	6.149	1	11.62
1	6.136	4.961	1	3.299	3.653	1	4.974	5.963	0	12.3
1	6.136	4.961	1	3.299	3.678	1	4.974	5.915	1	11.58
max. 10V					max. 6V			max. 10V	11V..14V	
RevE:					out of range					
flyback configuration										
xfmr A6154Rev3										
bias current 1mA										
bias voltage 6.14V										
2x rectifier at 12Vout										

2.5.2 Bias Current 5 mA

Table 2-2. Cross Regulation With Bias Current set to 5 mA

primary 5 V	LDO in	LDO out	secondary 3.3 V	LDO out	LDO in	5 V	LDO out	LDO in	12 V	out
0	6.766	4.979	0	3.301	4.36	0	4.993	6.822	0	13.29
0	6.765	4.979	0	3.3	4.102	0	4.993	6.413	1	12.06
0	6.764	4.978	0	3.3	4.308	1	4.976	6.43	0	13.16
0	6.763	4.978	0	3.3	4.041	1	4.976	6.099	1	11.89
0	6.763	4.977	1	3.299	3.67	0	4.99	6.408	0	12.7
0	6.762	4.976	1	3.3	3.586	0	4.991	6.009	1	11.35
0	6.764	4.978	1	3.3	3.669	1	4.975	6.012	0	12.55
0	6.763	4.978	1	3.3	3.527	1	4.976	5.696	1	11.196
1	6.762	4.96	0	3.301	4.603	0	4.99	7.184	0	13.99
1	6.762	4.96	0	3.3	4.429	0	4.989	6.9	1	13.01
1	6.763	4.961	0	3.301	4.547	1	4.973	6.8	0	13.85
1	6.763	4.961	0	3.301	4.41	1	4.972	6.653	1	12.98
1	6.762	4.96	1	3.3	4.067	0	4.989	6.922	0	13.65
1	6.762	4.96	1	3.301	4.095	0	4.988	6.769	1	12.84
1	6.762	4.96	1	3.301	4.064	1	5.011	6.599	0	13.57
1	6.761	4.96	1	3.301	4.083	1	5.009	6.534	1	12.8
	max. 10V					max. 6V			max. 10V	11V..14V
RevE:										
flyback configuration										
xfmr A6154Rev3										
bias current 5mA										
bias voltage 6.76V										
2x rectifier at 12Vout										

2.6 Thermal Images

The PMP30921 thermal image is shown in the following figure.

 


Figure 2-14. Thermal Image

Name	Temperature
D1	54.3°C
D2	52.5°C
D5	51.6°C
D5	52.9°C
D8	57.1°C
D9	44.6°C
Q1	50.6°C
T1	58.1°C
U3	54.7°C
U4	50.7°C

2.7 Bode Plots

The PMP30921 bode plot is shown in the following figure.

 


Figure 2-15. Frequency Response for 7.2-V Input Voltage

V_{IN}	7.2 V
Bandwidth (kHz)	8.16
Phase margin	61°
Slope (20 dB / decade)	-1.3
Gain margin (dB)	-22.8
Slope (20 dB / decade)	-1.9
Freq (kHz)	51.6

3 Waveforms

3.1 Switching

3.1.1 Q1 Drain to GND

 


Figure 3-1. Switchnode (Q1 Drain to GND)

3.1.2 Q1 Gate to GND

 


Figure 3-2. Switching (Q1 Gate to GND)

3.1.3 D1 Anode to 12 V_{OUT}

 


Figure 3-3. D1 (Anode to 12 V_{OUT})

3.2 Input Voltage Ripple

 


Figure 3-4. Input Voltage Ripple

The input filter is attenuating the reflected ripple (= conducted emissions).

To attenuate RF spikes further a ferrite bead (600 Ω at 100 MHz) could be added to the input.

 


Figure 3-5. Input Ripple (Jmp1 Zoomed and Full Bandwidth)

3.3 Output Voltage Ripple

3.3.1 5-V Output Voltage (Primary)

 


Figure 3-6. Output Voltage Ripple (5 V_p)

3.3.2 5-V Output Voltage (Secondary)

 


Figure 3-7. Output Voltage Ripple (5 V_s)

3.3.3 3.3-V Output Voltage

 


Figure 3-8. Output Voltage Ripple (3.3 V)

3.3.4 12-V Output Voltage

 


Figure 3-9. Output Voltage Ripple (12 V)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated