

Test Report: PMP30833

# 30-W Two-Switch Buck-Boost Reference Design With 24-V or 48-V Output



## Description

This two-switch buck boost controlled by the LM5118 device is stepping up and stepping down an input voltage range of 30 V to 60 V to either 24-V or 48-V output voltage. Jumper #3 at the digital-to-analog converter (DAC) is used to decide for 24  $V_{OUT}$  or 48  $V_{OUT}$  – with jumper 48  $V_{OUT}$ , without 24  $V_{OUT}$ .

For the final application, the 48-V output voltage is just needed for short term use < 1 s. For test purposes the power stage withstands this power level continuously, so the power stage itself could be shrunk for the final application.


Modify the loop bandwidth from between 600 Hz, 1200 Hz, and 2400 Hz – the default is 1.2 kHz. The final application adds a reactive load to the output and needs to be adapted; this prototype supports three different tested variants.

## Features

- Supports 48-V start-up output voltage and 24-V continuous output voltage
- The prototype itself supports continuous 48-V output operations at full load, 600 mA for test purposes
- Three control variants support various reactive load types
- Control scheme supports switched output voltage, load transient, and line transient

## Applications

- [Appliances pumps and fans](#)

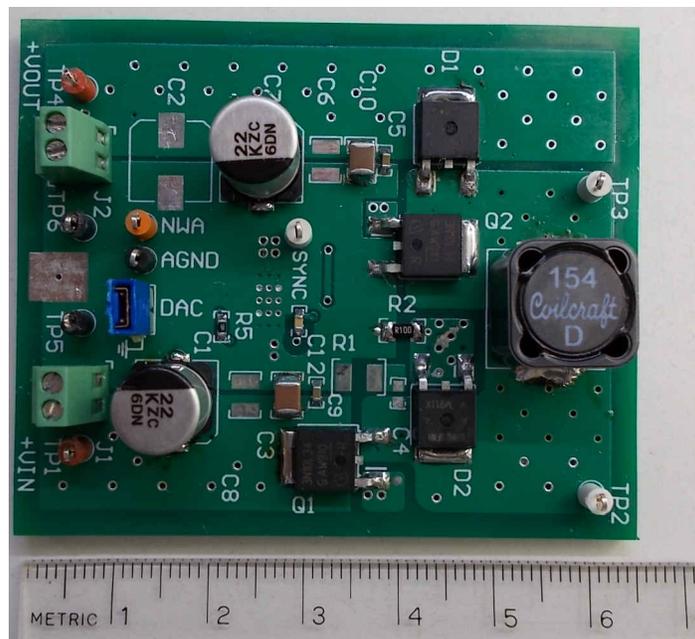

Top Photo

## 1 Test Prerequisites

### 1.1 Voltage and Current Requirements

**Table 1-1. Voltage and Current Requirements**

Parameter	Specifications
Input Voltage Range	30 V to 60 V, 65 V <sub>MAX</sub>
Output Voltage	24 V or 48 V
Maximum Output Current	0.6 A at 48 V <sub>OUT</sub>
Switching Frequency	300 kHz

### 1.2 Considerations

Unless otherwise indicated, all measurements were done by 0.6 A adjusted by a variable resistor.

The circuit starts with switching at 28 V and stops with switching around 25.7 V.

The prototype worked at a measured switching frequency of 300 kHz and soft start set to 12 ms.

---

#### Note

By inserting the jumper J3, the output voltage can be switched from 24 V to 48 V.

---

### 1.3 Dimensions

The outline of the board [PMP30520 Rev. A](#) is 53 mm × 64 mm. This PCB is a two-layer board with 2-oz copper thickness on each layer.

## 2 Testing and Results

### 2.1 Efficiency Graphs

#### 2.1.1 24-V Output Voltage

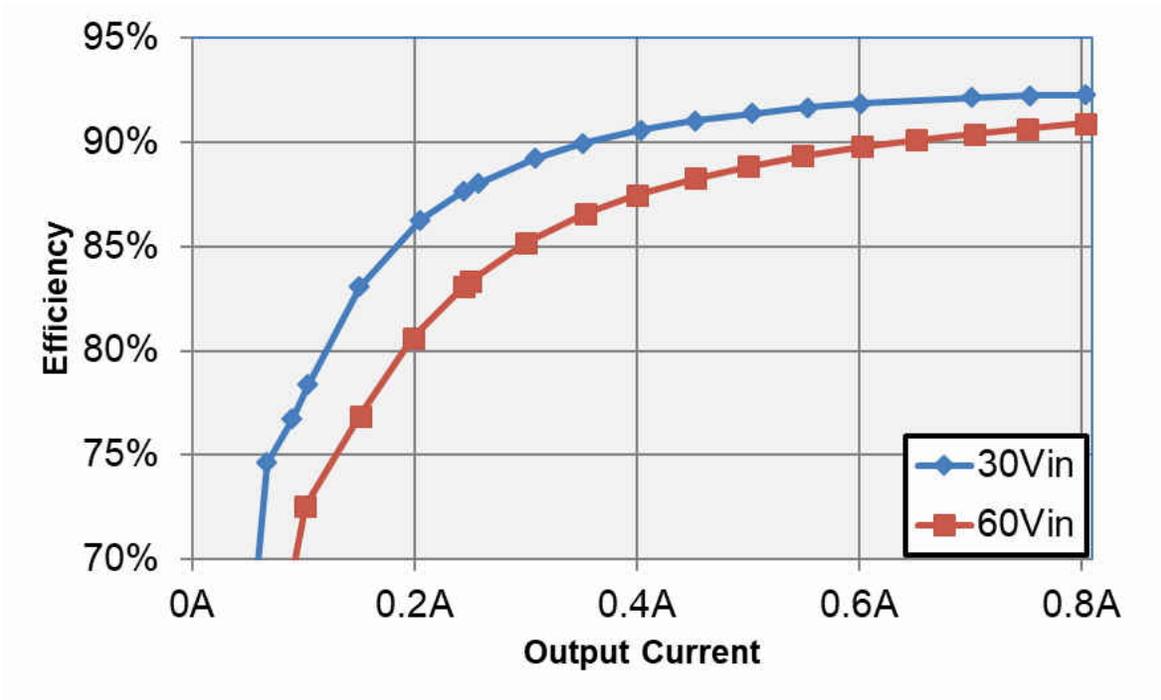


Figure 2-1. Efficiency vs Output Current

#### 2.1.2 48-V Output Voltage

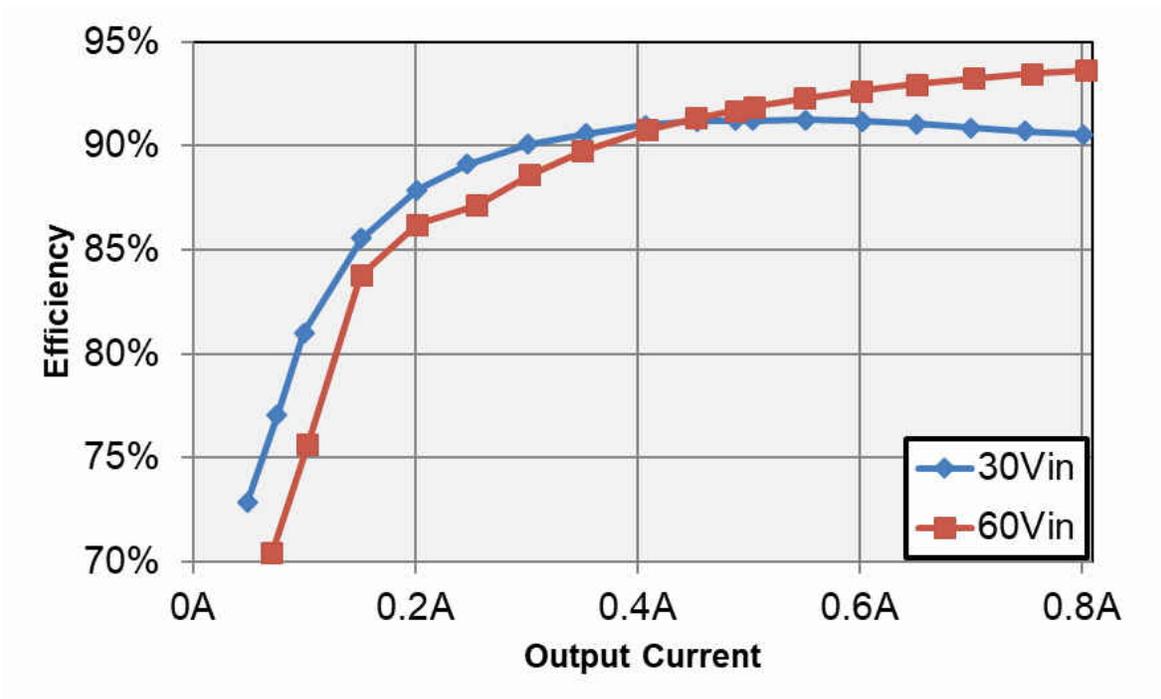


Figure 2-2. Efficiency vs Output Current

## 2.2 Loss Graphs

### 2.2.1 24-V Output Voltage

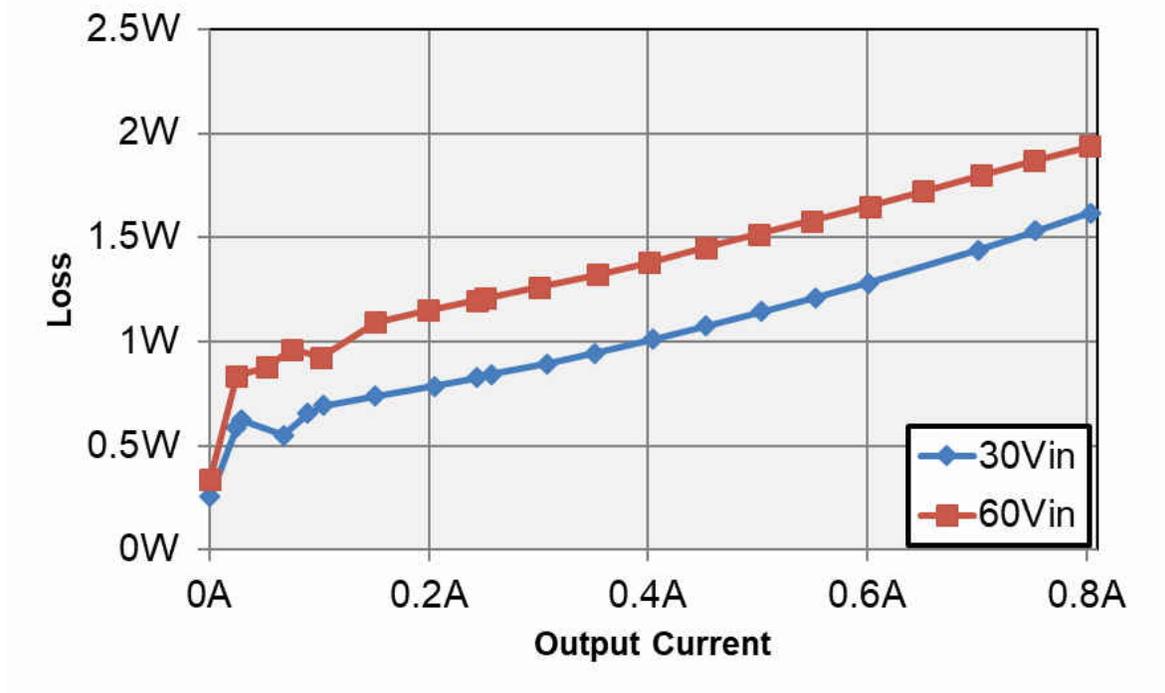


Figure 2-3. Loss vs Output Current

### 2.2.2 48-V Output Voltage

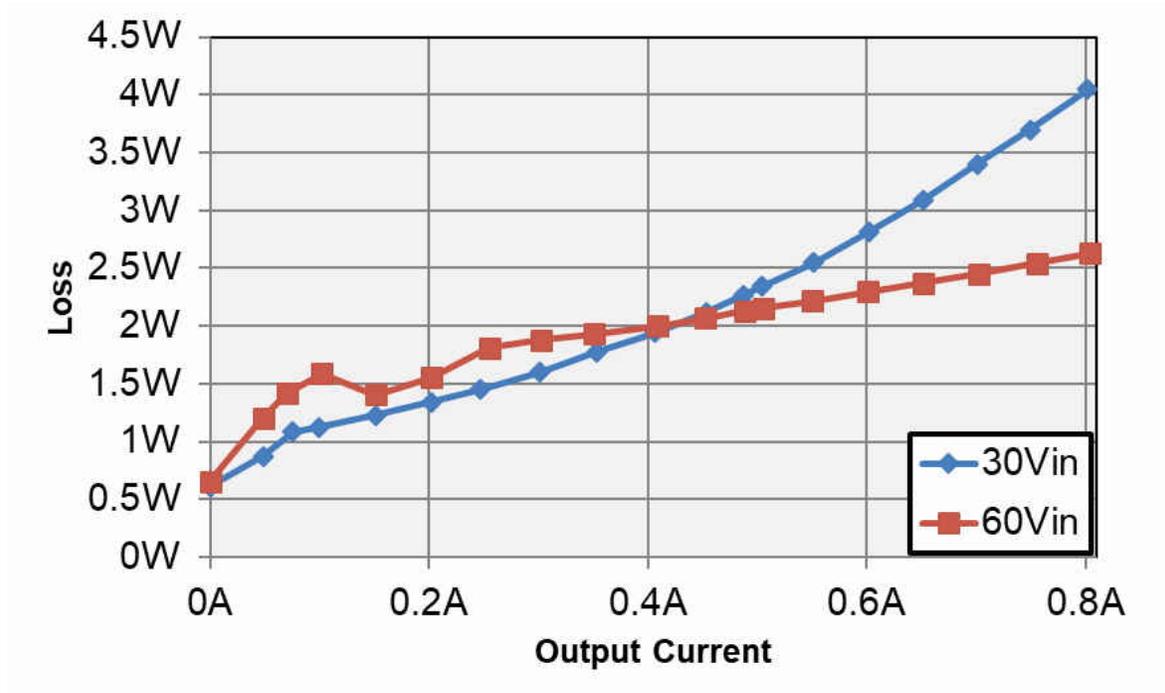


Figure 2-4. Loss vs Output Current

## 2.3 Load Regulation

### 2.3.1 24-V Output Voltage

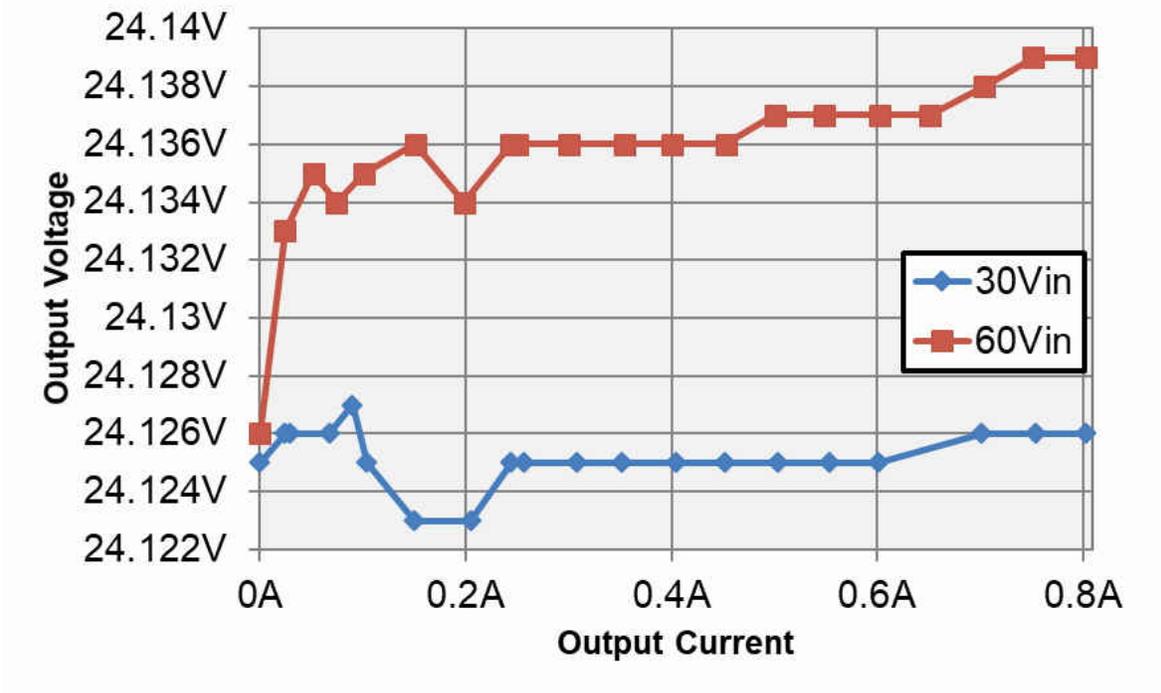


Figure 2-5. Output Voltage vs Output Current

### 2.3.2 48-V Output Voltage

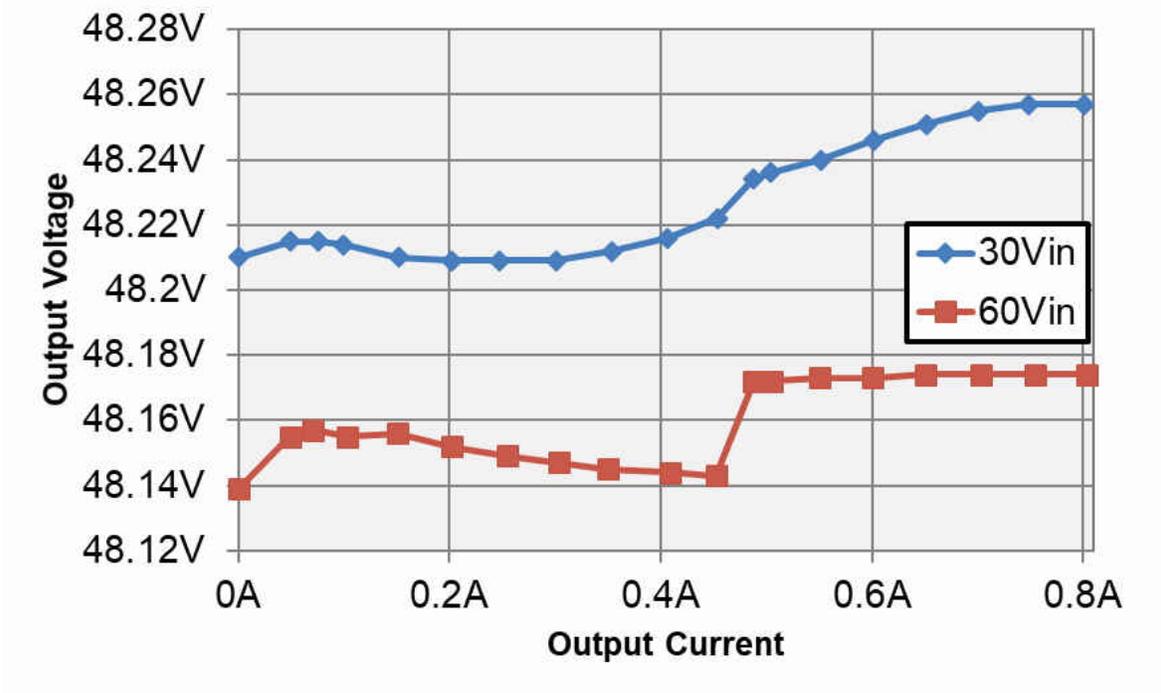


Figure 2-6. Output Voltage vs Output Current

## 2.4 Line Regulation

### 2.4.1 24-V Output Voltage

Figure 2-7 shows the output voltage depending on the input voltage.

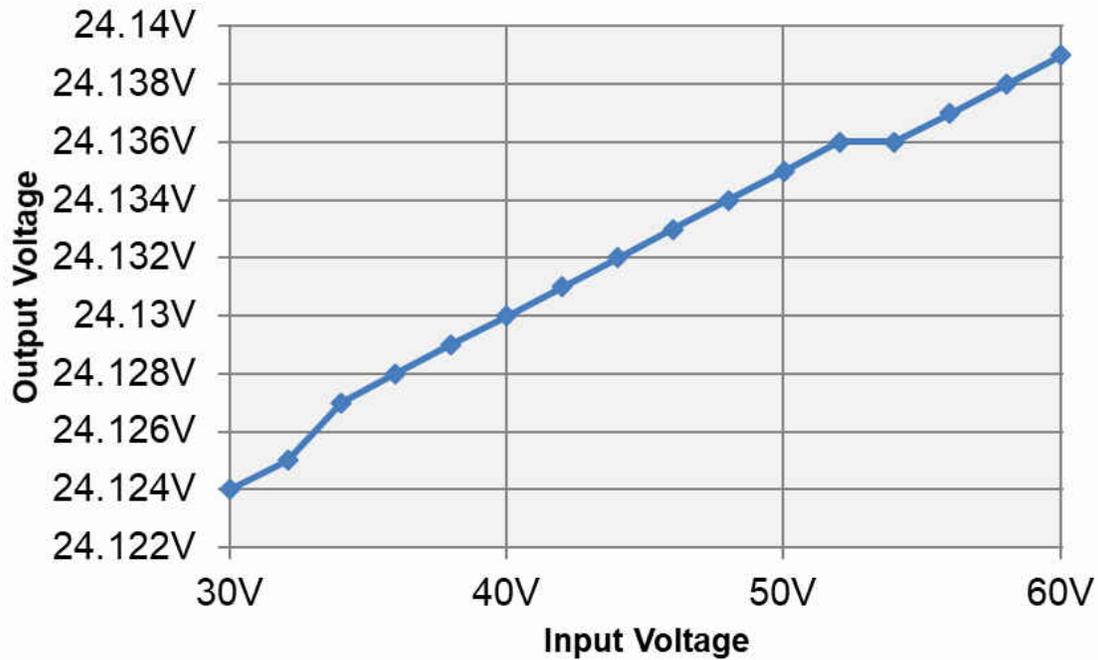


Figure 2-7. Output Voltage vs Input Voltage

Efficiency and loss were also calculated.

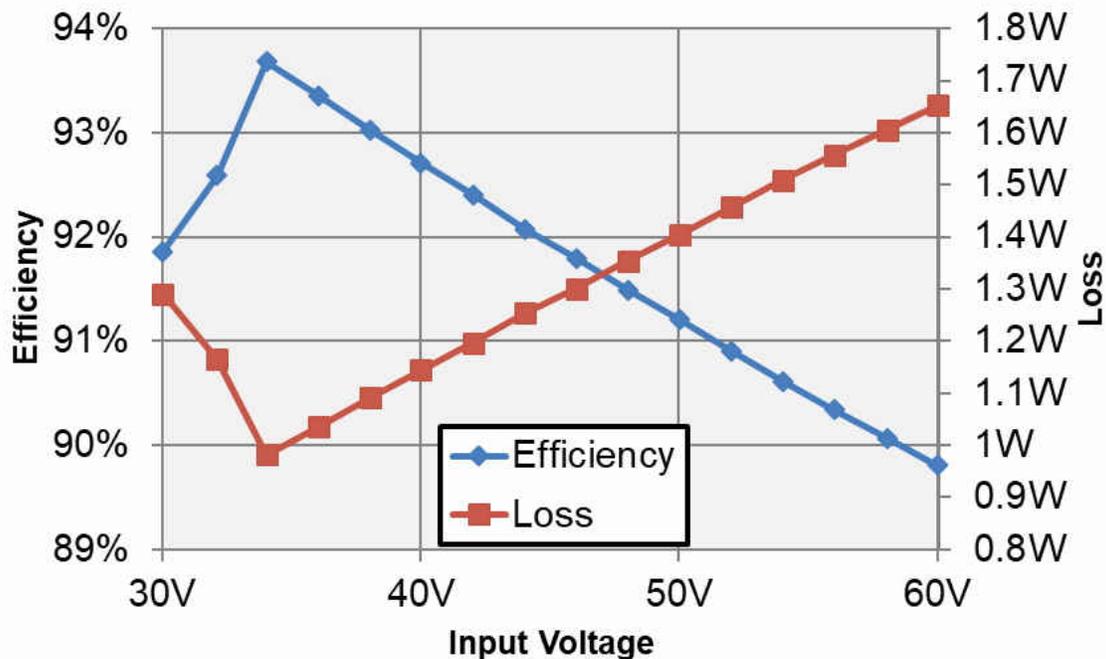


Figure 2-8. Loss and Efficiency vs Input Voltage

### 2.4.2 48-V Output Voltage

The dependency of output voltage to the input voltage is shown in [Figure 2-9](#).

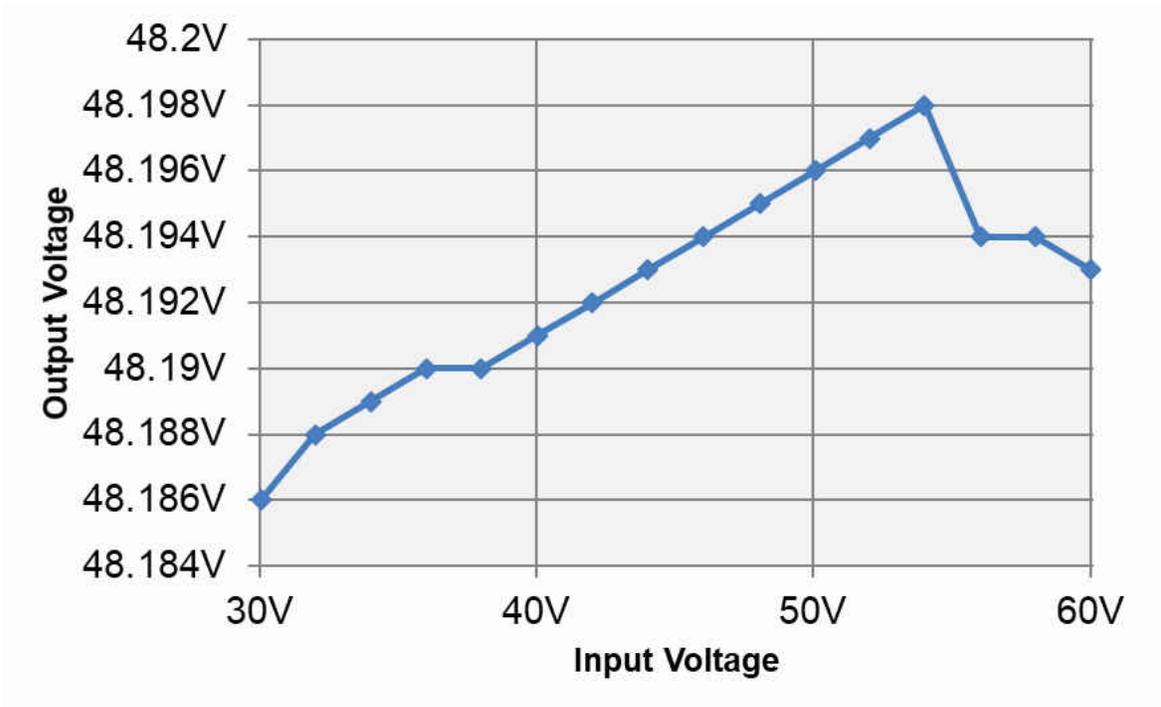


Figure 2-9. Output Voltage vs Input Voltage

[Figure 2-10](#) shows the efficiency and loss data.

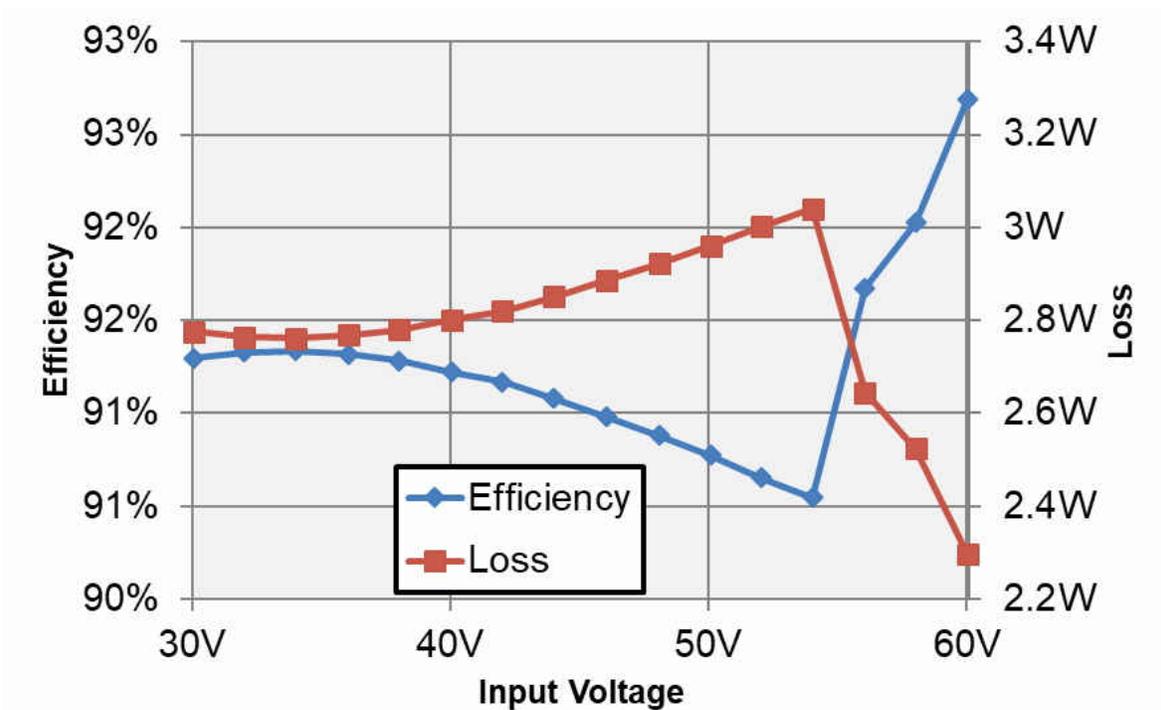



Figure 2-10. Loss and Efficiency vs Input Voltage

## 2.5 Thermal Images

These images have been taken after 30 minutes of operation at full load and 600 mA each.

### Note

For the final application, 48-V output voltage is just needed for less than one second.

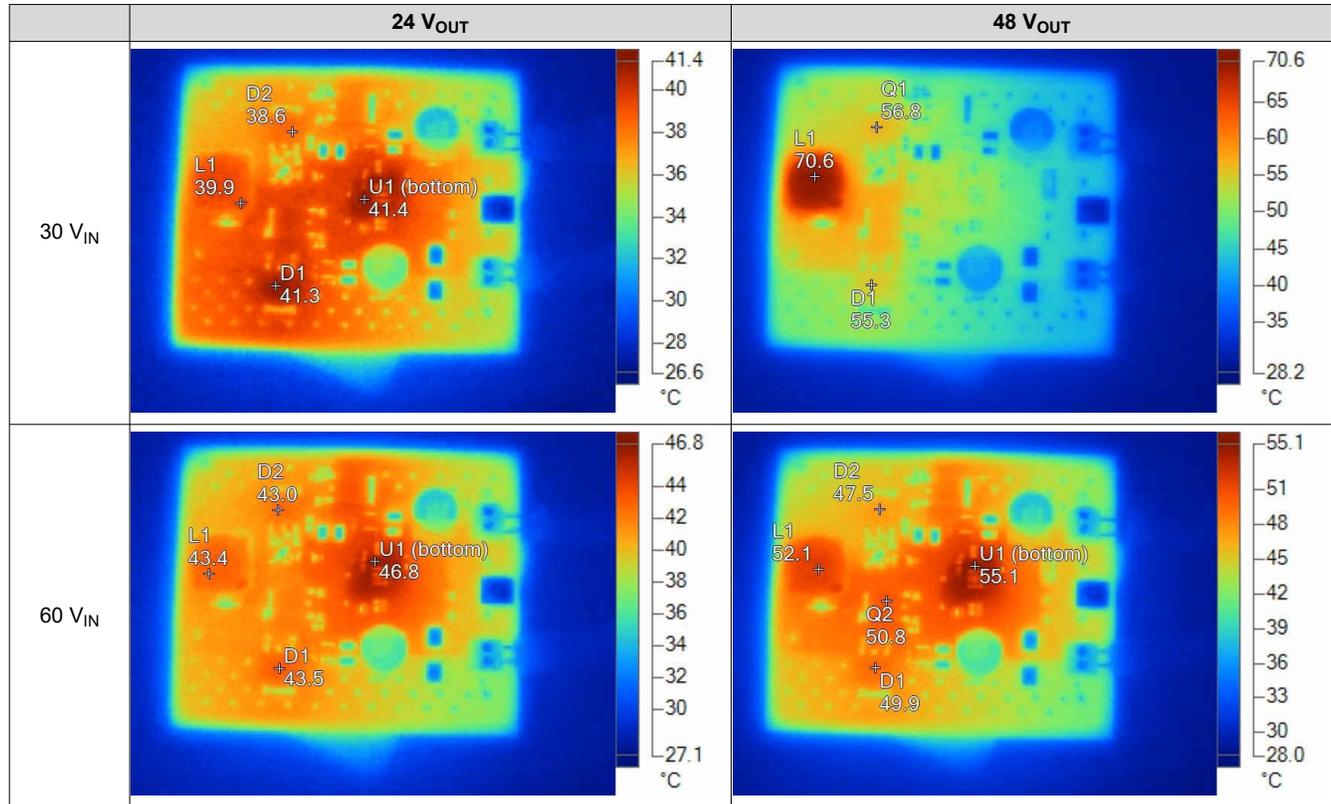

**Table 2-1. Temperature Comparison**

Name	30 V <sub>IN</sub> 24 V <sub>OUT</sub>	60 V <sub>IN</sub> 24 V <sub>OUT</sub>	30 V <sub>IN</sub> 48 V <sub>OUT</sub>	60 V <sub>IN</sub> 48 V <sub>OUT</sub>
D1	41.3°C	43.5°C	55.3°C	49.9°C
D2	38.6°C	43.0°C		47.5°C
L1	39.9°C	43.4°C	70.6°C	52.1°C
Q1			56.8°C	
Q2				50.8°C
U1 (bottom)	41.4°C	46.8°C		55.1°C

## 2.6 Bode Plots

### 2.6.1 60-V Input Voltage and 24-V Output Voltage

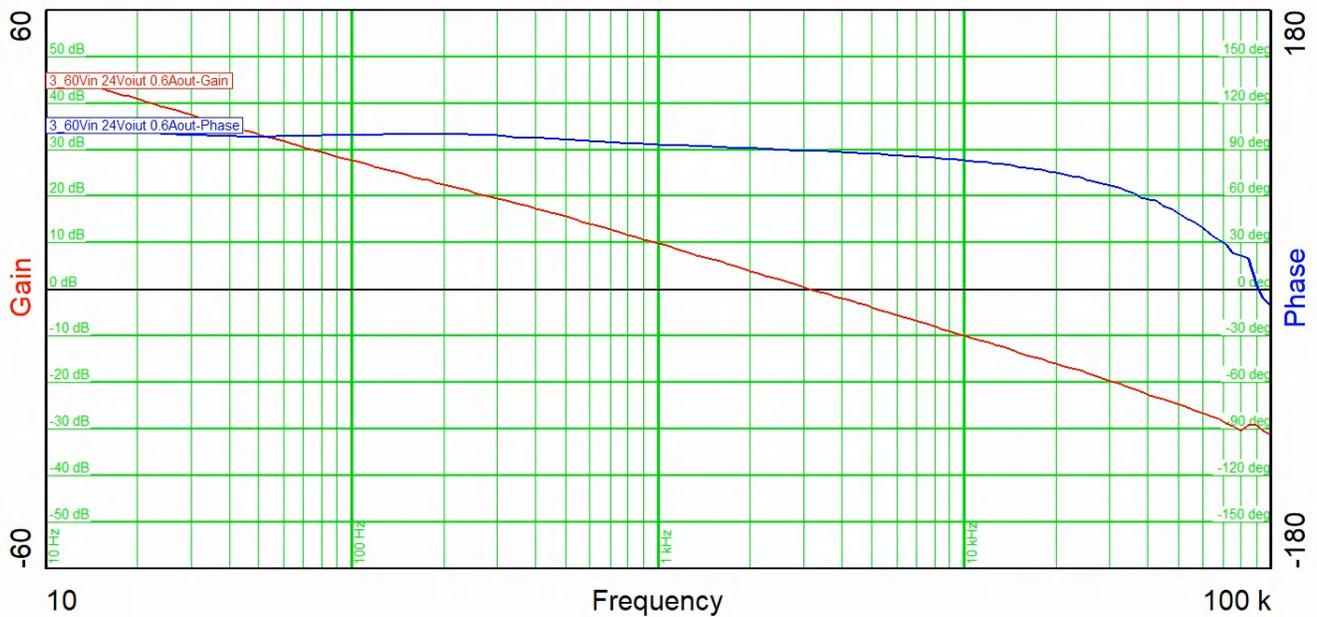


Figure 2-11. Bode Plot for 24 V<sub>OUT</sub> and 60 V<sub>IN</sub>, Buck mode

Parameter	Value
Bandwidth (kHz)	3.18
Phase margin	89°
Slope (20 dB / decade)	-1
Gain margin (dB)	-29.6
Slope (20 dB / decade)	-2.6
Freq (kHz)	91

### 2.6.2 30-V Input Voltage and 48-V Output Voltage

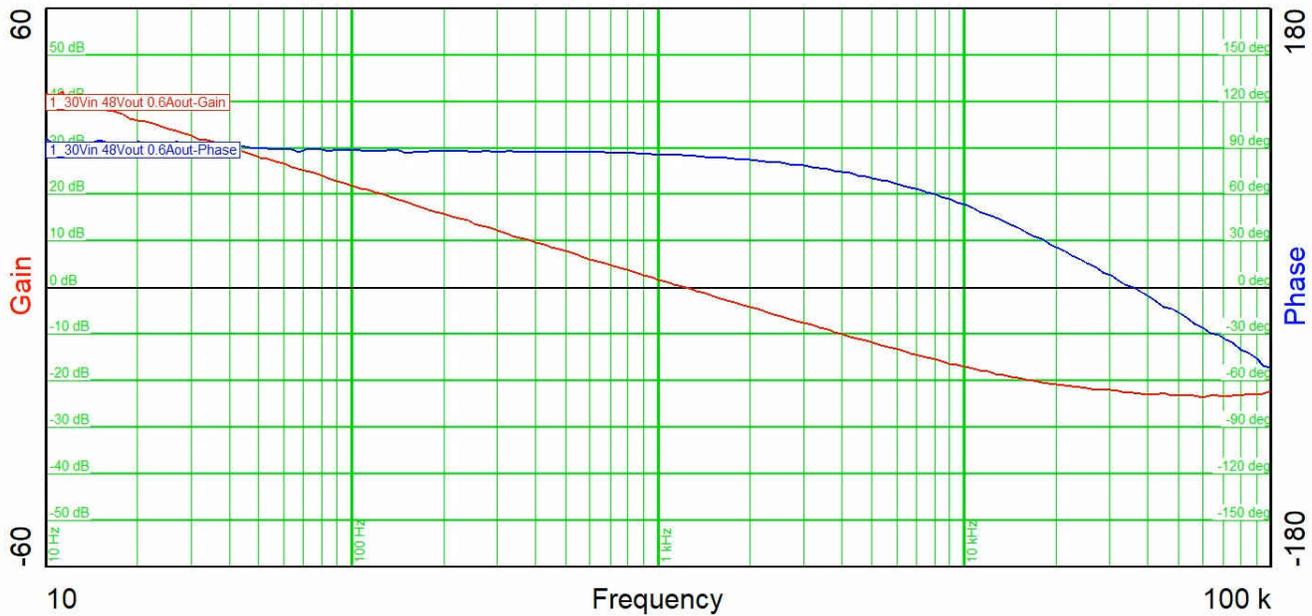


Figure 2-12. Bode Plot for 48 V<sub>OUT</sub> and 30 V<sub>IN</sub>, Boost mode - RHPZ at 32 kHz

Parameter	Value
Bandwidth (kHz)	1.23
Phase margin	85°
Slope (20 dB / decade)	-0.98
Gain margin (dB)	-22.6
Slope (20 dB / decade)	-0.49
Freq (kHz)	35.8

### 2.6.3 Loop Variants

- Rev. A (R12 = 10 kΩ , C15 = 100 nF , C16 = 100 pF) reduces to 600-Hz loop bandwidth
- Rev. B (R12 = 20 kΩ , C15 = 47 nF , C16 = 47 pF) 1200-Hz (default)
- Rev. C (R12 = 40.2 kΩ , C15 = 22 nF , C16 = 22 pF) boosts to 2400 Hz; using loop C for F<sub>co</sub> 2.4 kHz still provides phase margin > 70 degrees and gain margin -15 dB

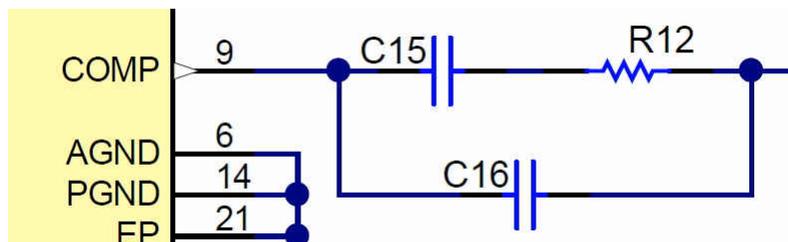


Figure 2-13. Schematic Detail


### 3 Waveforms

#### 3.1 Switching

**Note**


With duty cycle greater than 75%, the controller steps into buck-boost mode.

##### 3.1.1 24-V Output Voltage, 30-V Input Voltage (Duty Cycle 80%)

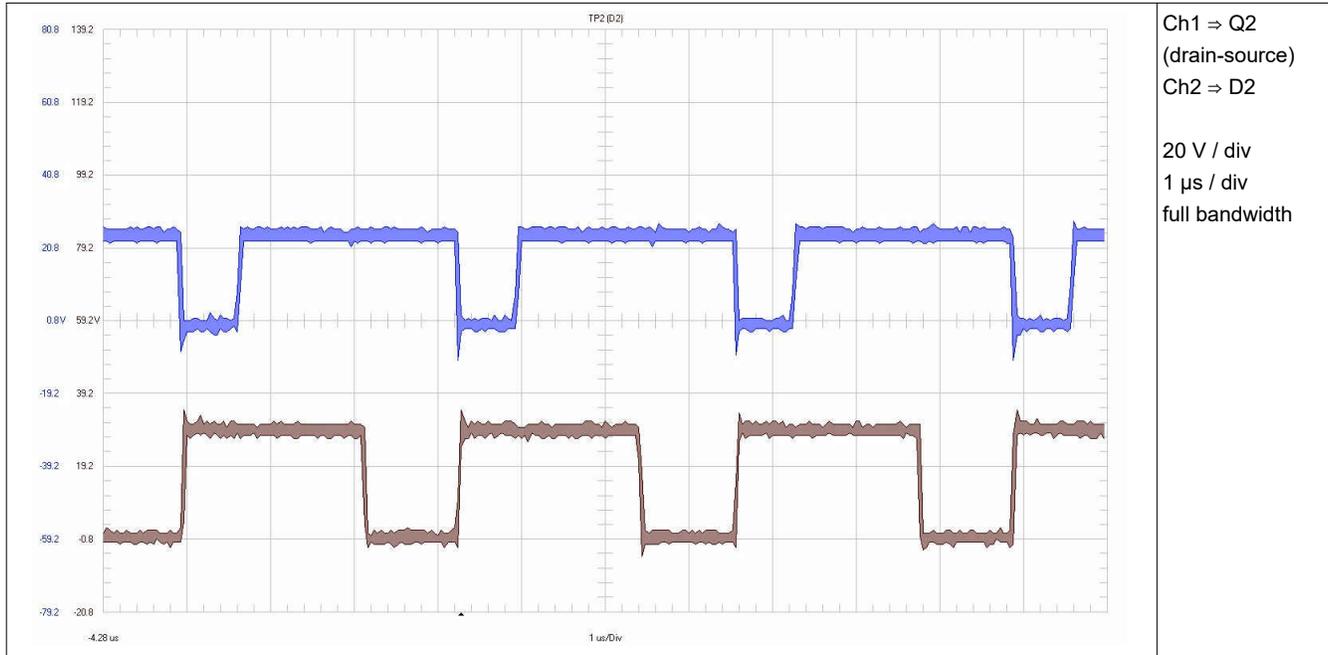

**Figure 3-1. Transistor Q2 Drain (TP3) to GND; Diode D2 (TP2) to GND**


**3.1.1.1 Diode D1**

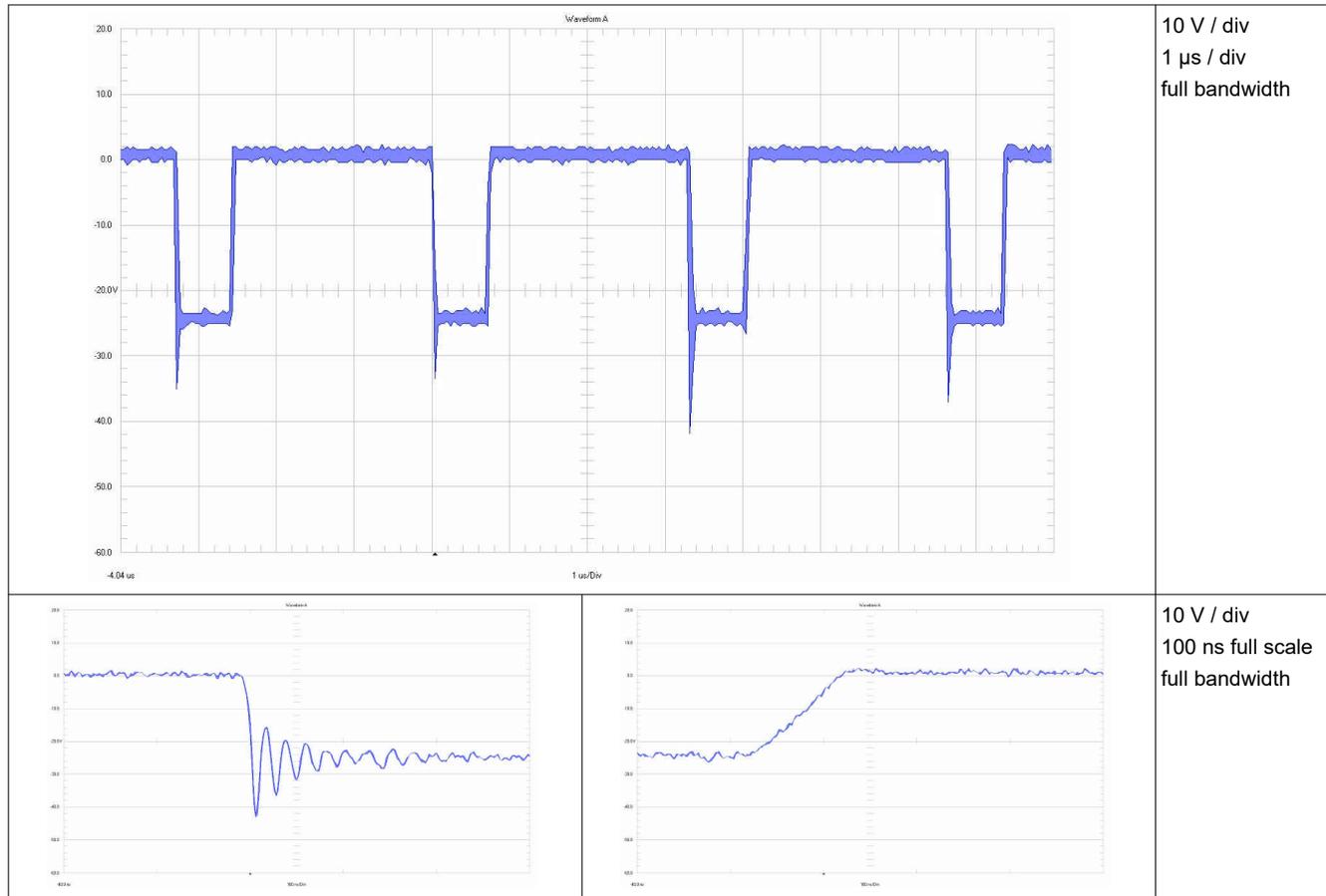

**Figure 3-2. Diode D1 Referenced to  $V_{OUT}$**

### 3.1.1.2 Transistor Q2

#### 3.1.1.2.1 Drain - GND

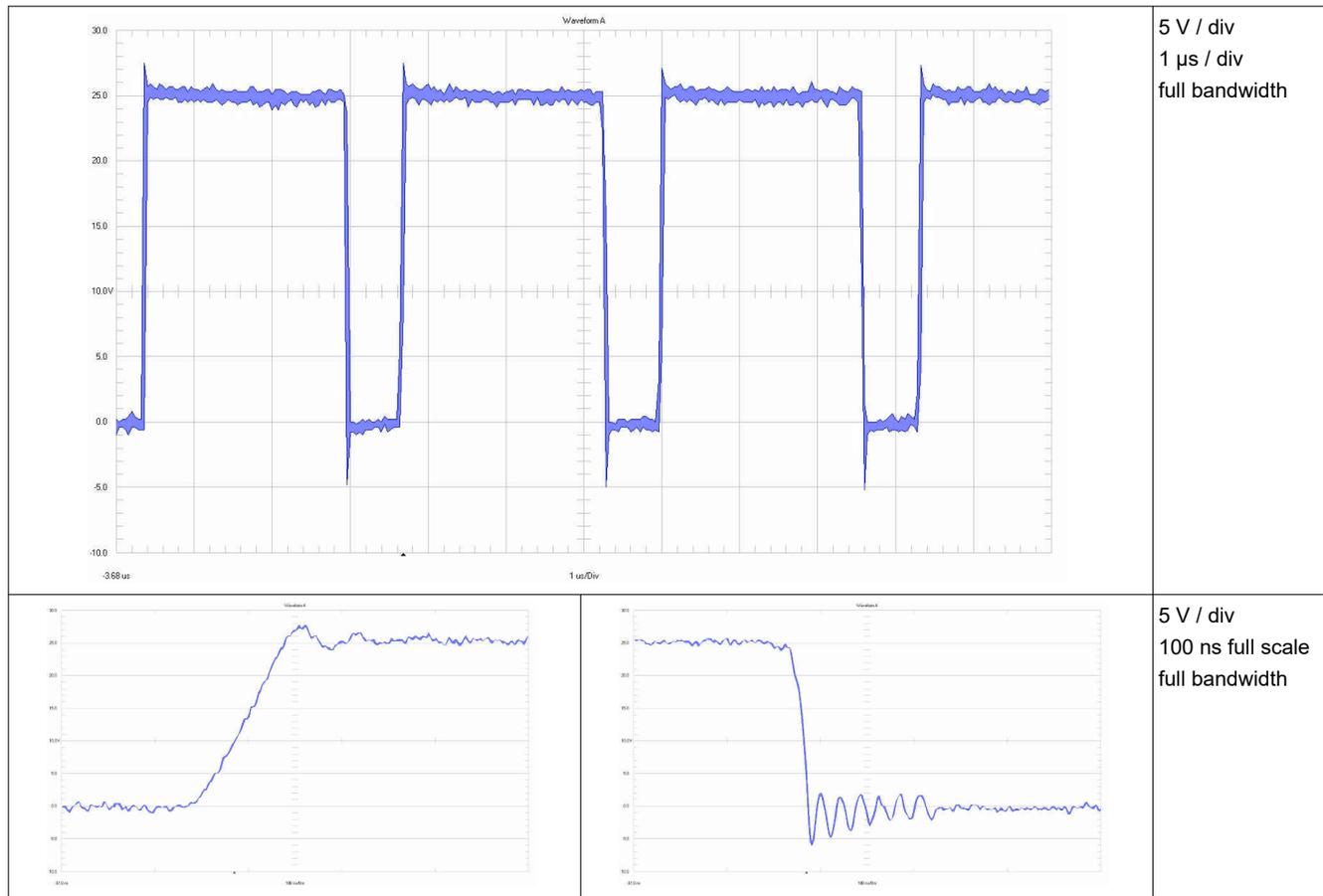


**Figure 3-3. Transistor Q2 Drain - GND**

3.1.1.2.2 Gate - GND

**Note**

The final application uses FETs with much lower gate charge QG. A gate resistor (3.3 Ω to 4.7 Ω) might reduce the ringing on the gate.

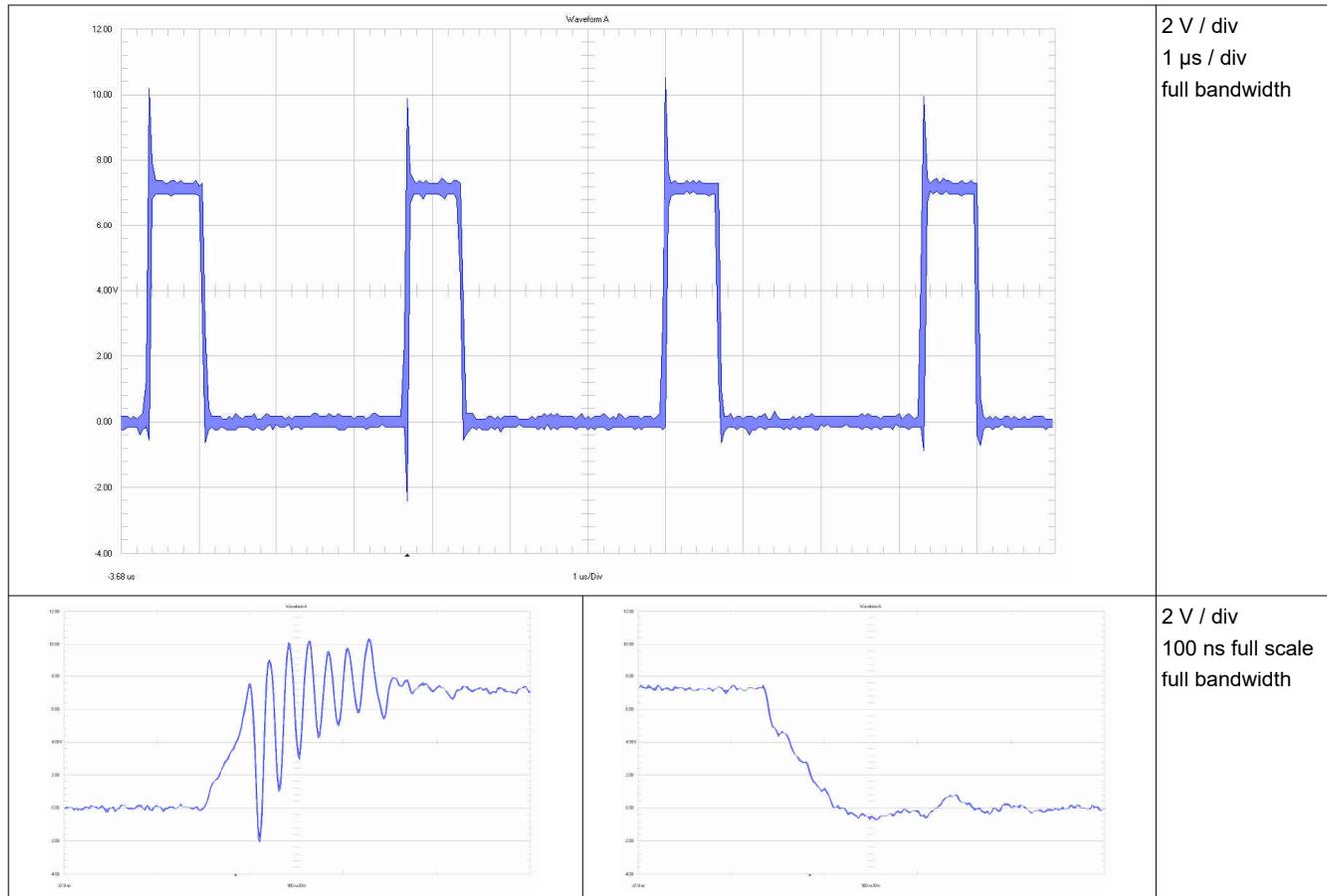

**Figure 3-4. Transistor Q2 Gate - GND**

### 3.1.1.3 Diode D2

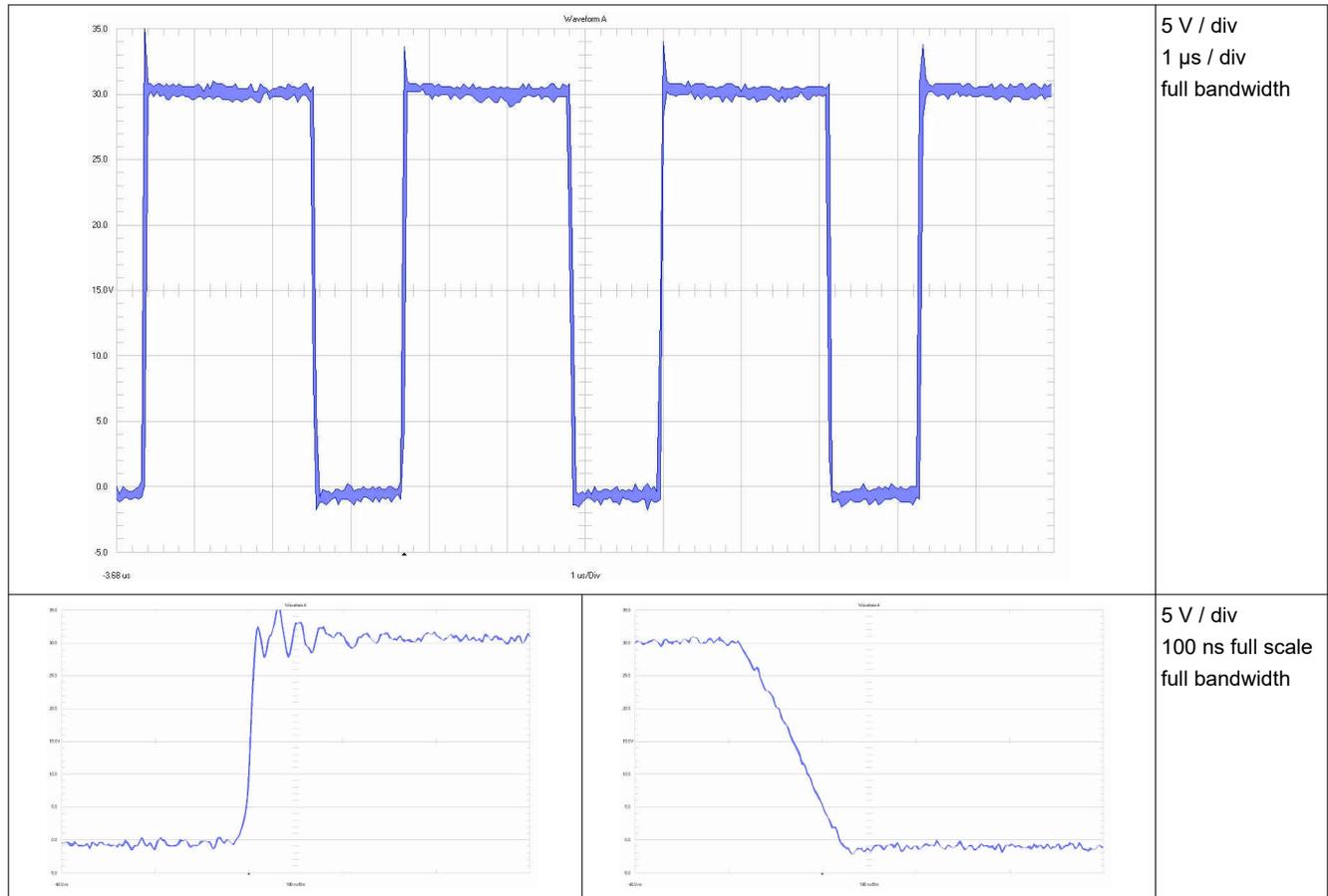


Figure 3-5. Diode D2

### 3.1.1.4 Transistor Q1

#### 3.1.1.4.1 Source - $V_{IN}$

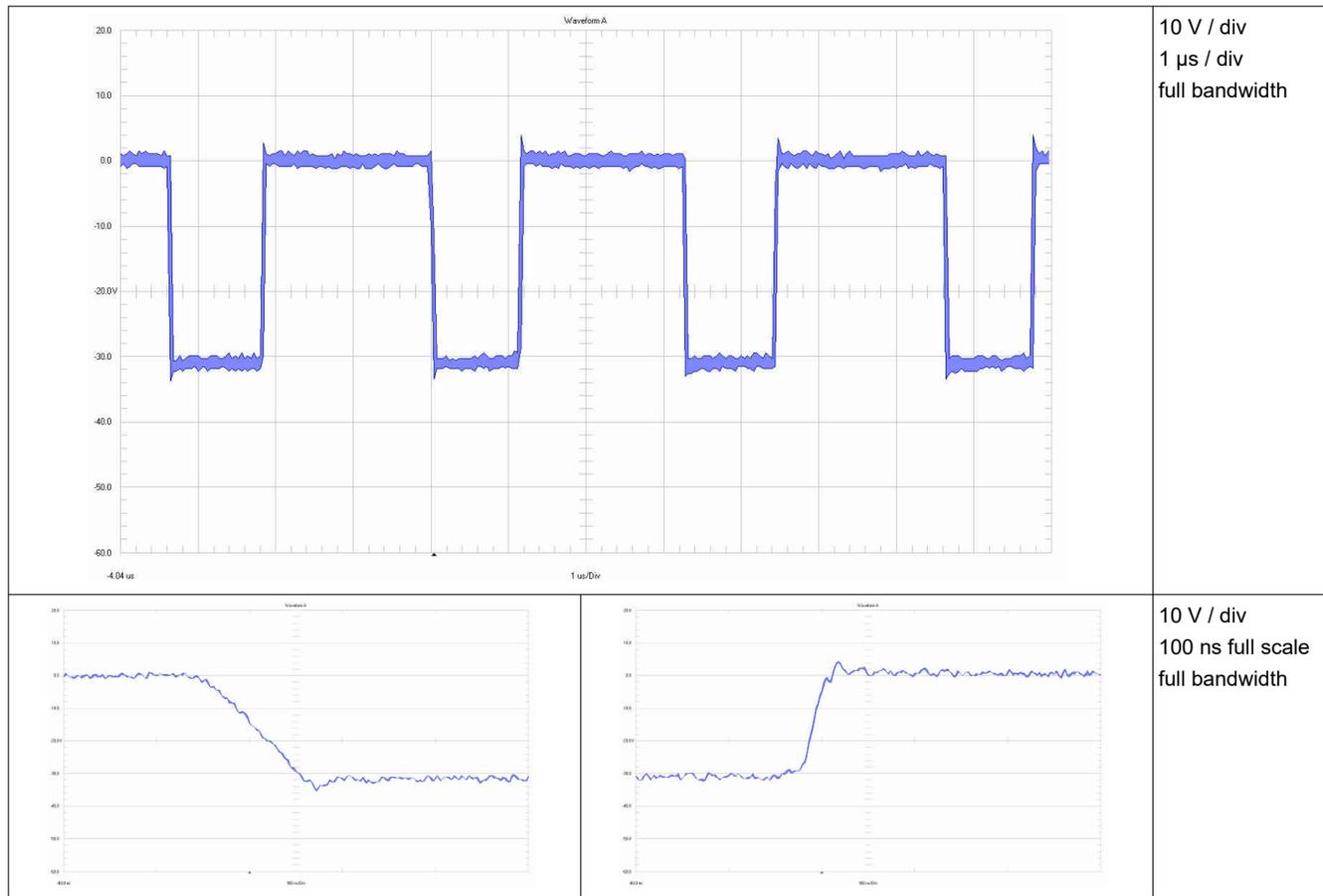


Figure 3-6. Transistor Q1 Source - Drain (Referenced to  $V_{IN}$ )

3.1.1.4.2 Gate - Source


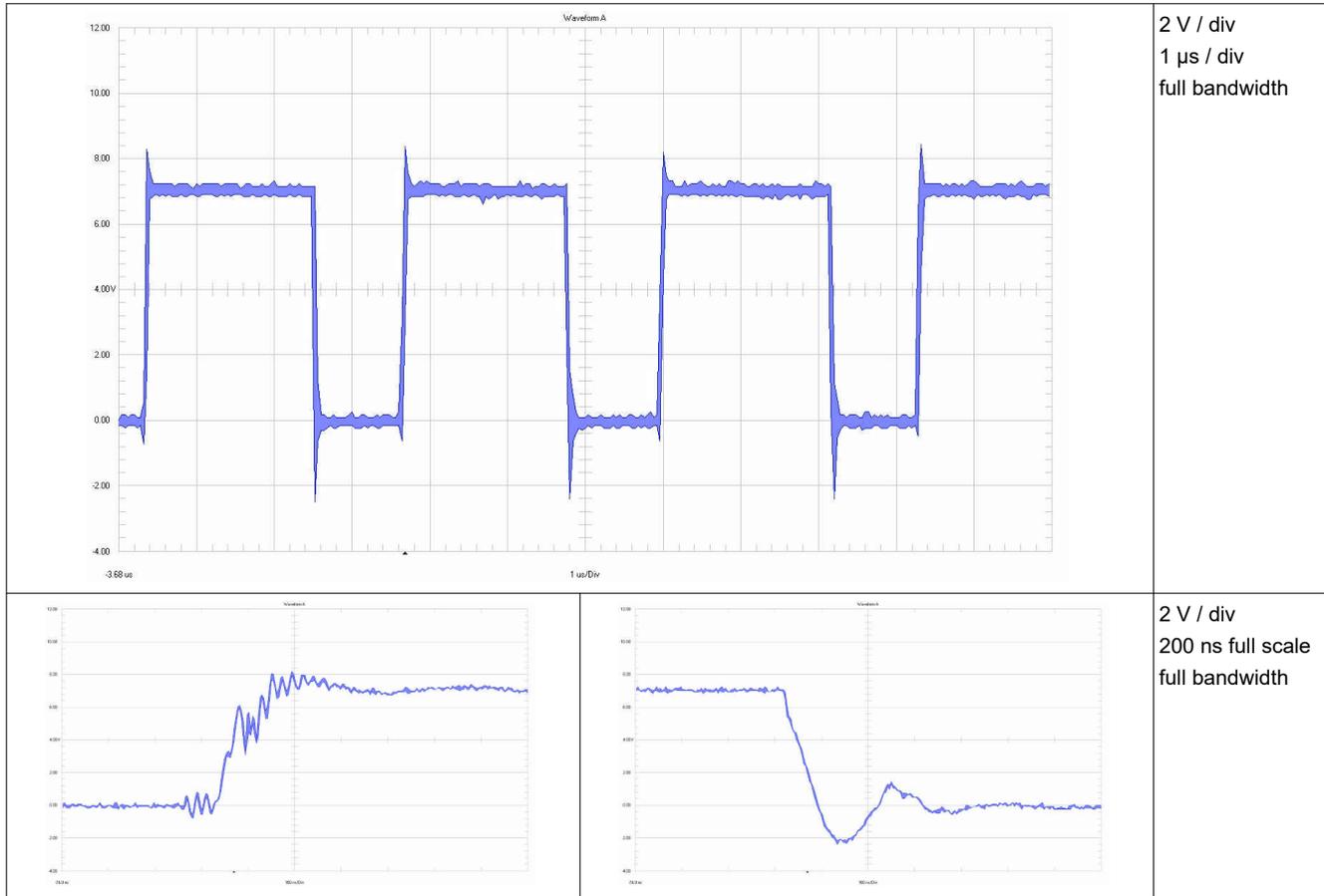


Figure 3-7. Transistor Q1 Gate - Source
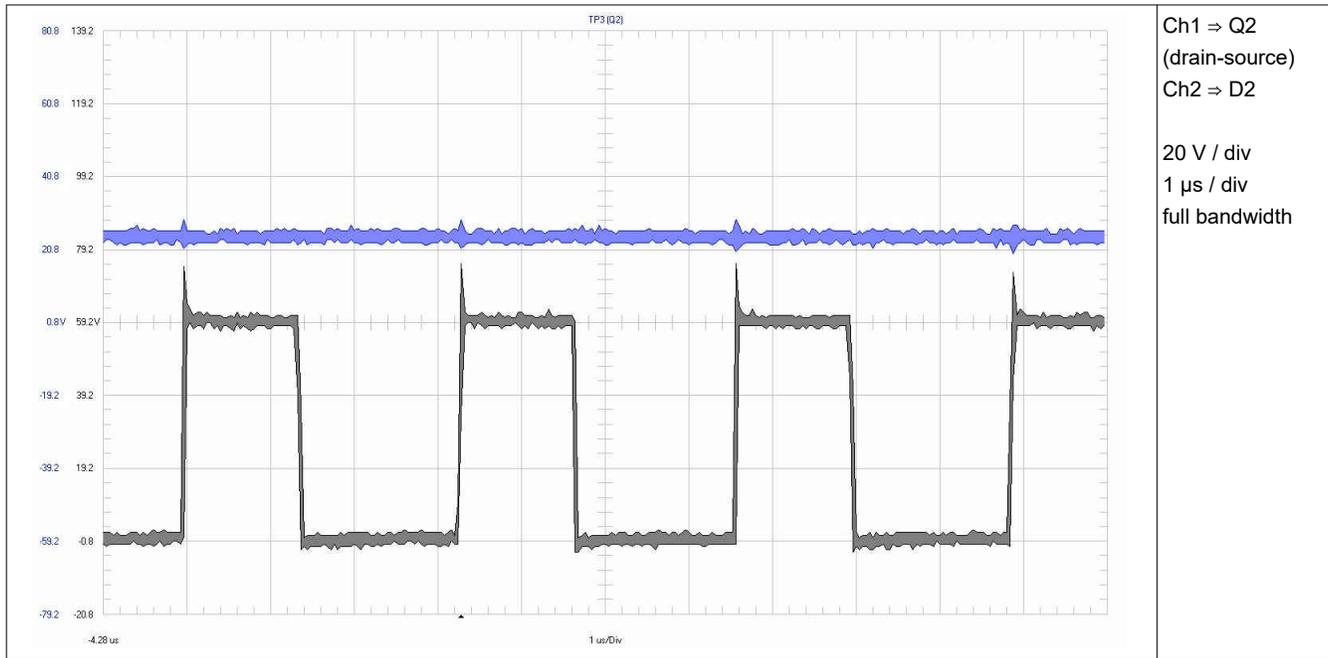
### 3.1.2 24-V Output Voltage; 60-V Input Voltage



The duty-cycle is 40%. The circuit works in pure buck mode.

**Figure 3-8. Transistor Q2 Drain (TP3) to GND; Diode D2 (TP2) to GND**

### 3.1.2.1 Diode D2


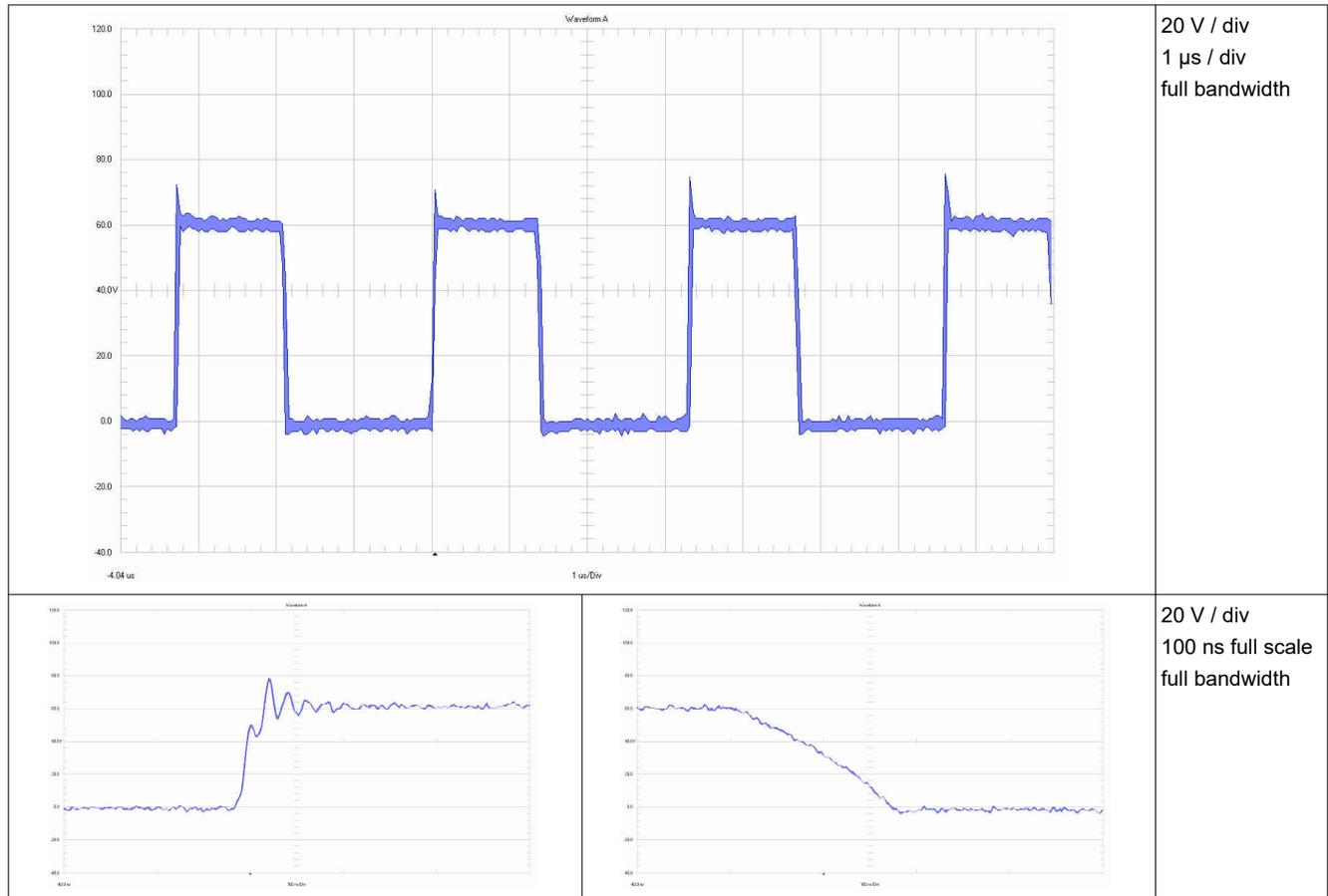


Figure 3-9. Diode D2

### 3.1.2.2 Transistor Q1

#### 3.1.2.2.1 Source - $V_{IN}$

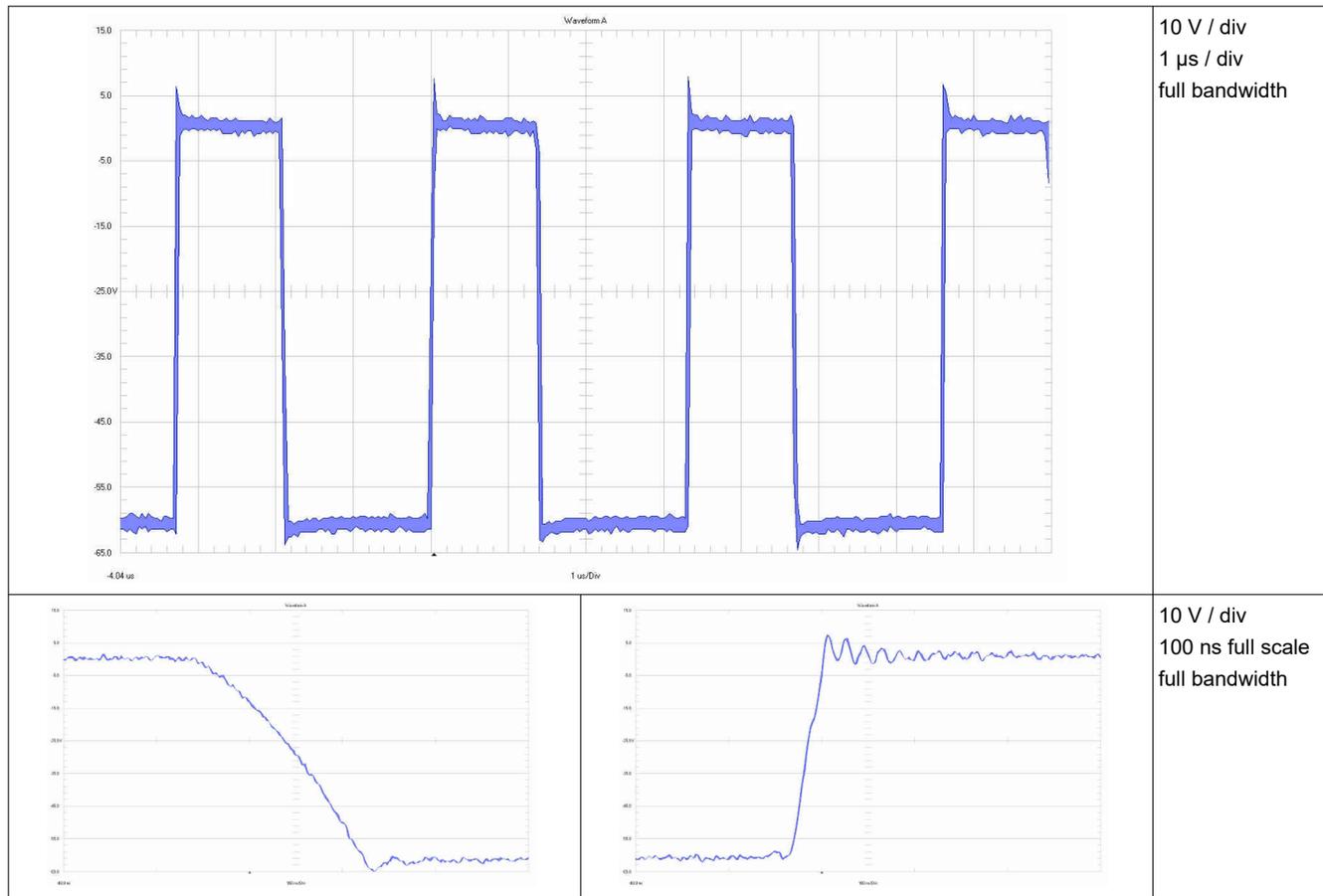

**Figure 3-10. Transistor Q1 Source - Drain (Referenced to  $V_{IN}$ )**

3.1.2.2.2 Gate-Source

**Note**

The final application uses FETs with much lower gate charge QG. A gate resistor (3.3 Ω to 4.7 Ω) might reduce the ringing on the gate.


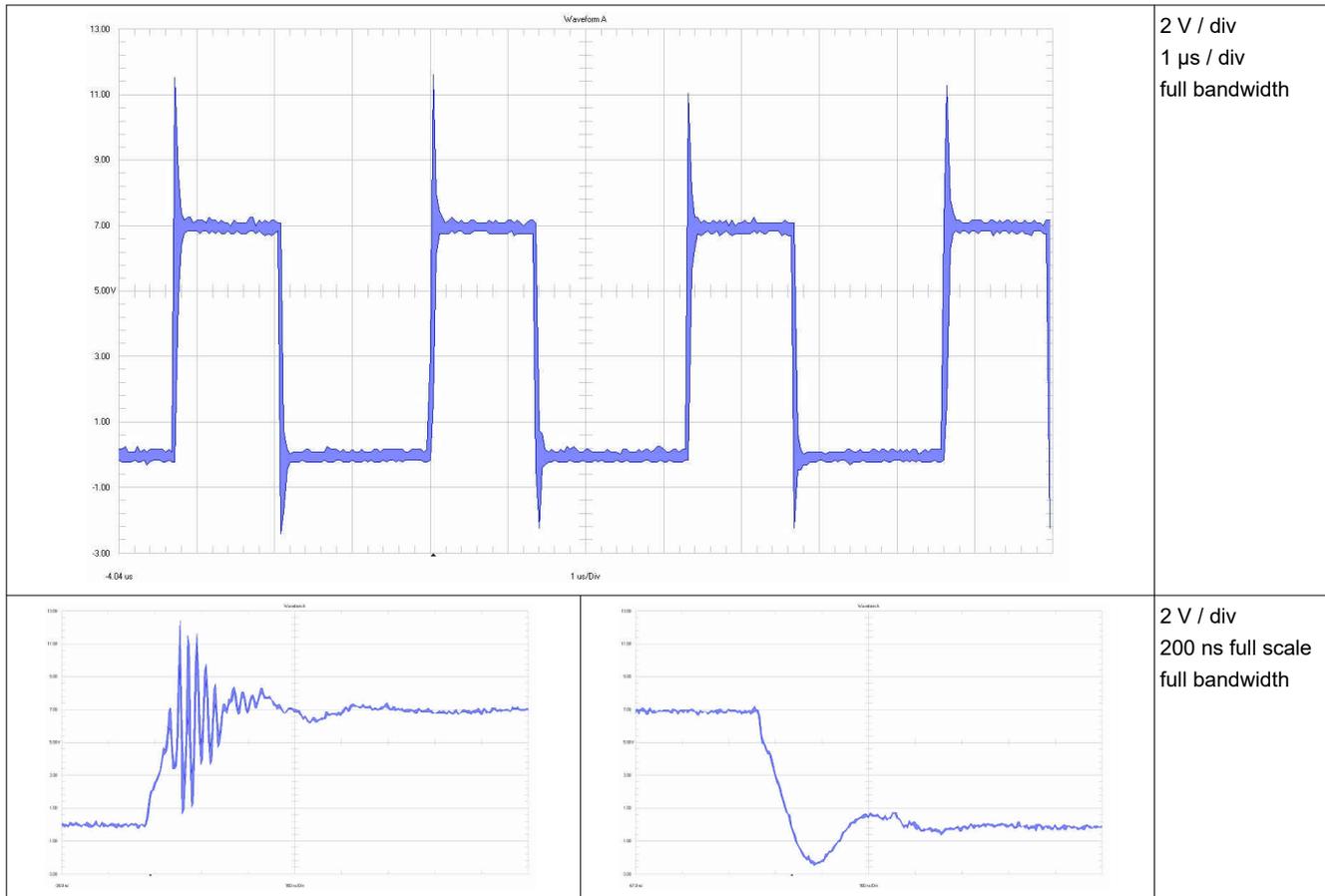


Figure 3-11. Transistor Q1 Gate - Source

### 3.1.3 48-V Output Voltage; 30-V Input Voltage (Maximum Stress)

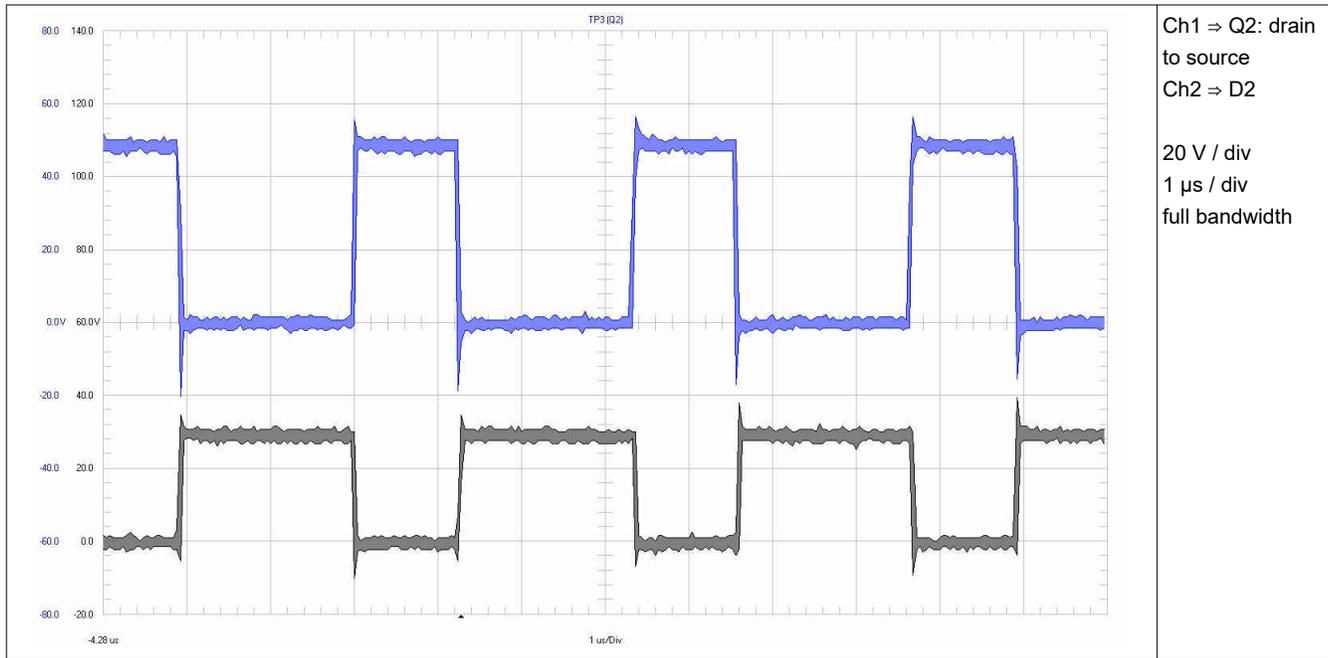

**Figure 3-12. Transistor Q2 Drain (TP3) to GND; Diode D2 (TP2) to GND**

### 3.1.3.1 Diode D1


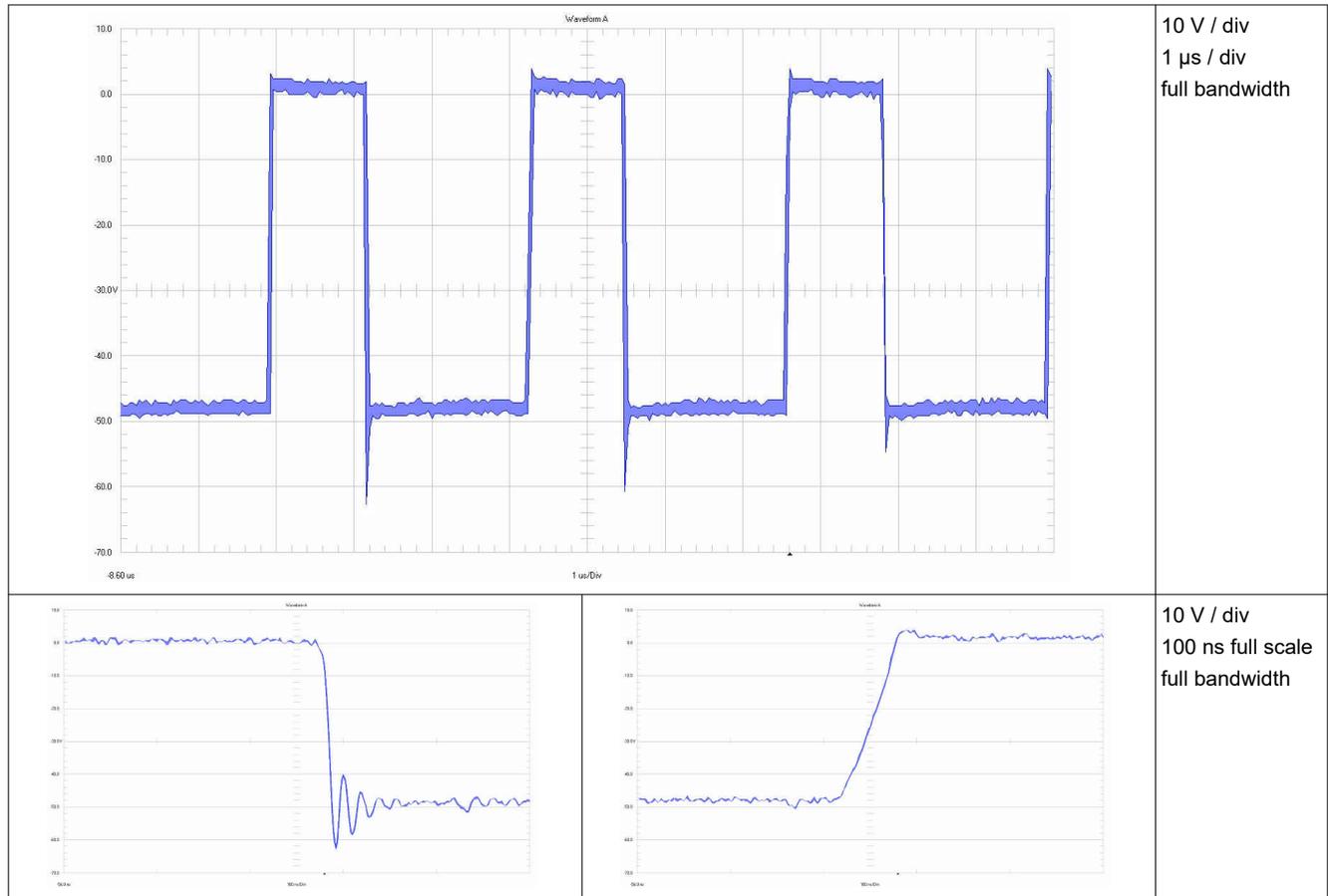


Figure 3-13. Diode D1

### 3.1.3.2 Transistor Q2

#### 3.1.3.2.1 Drain-GND

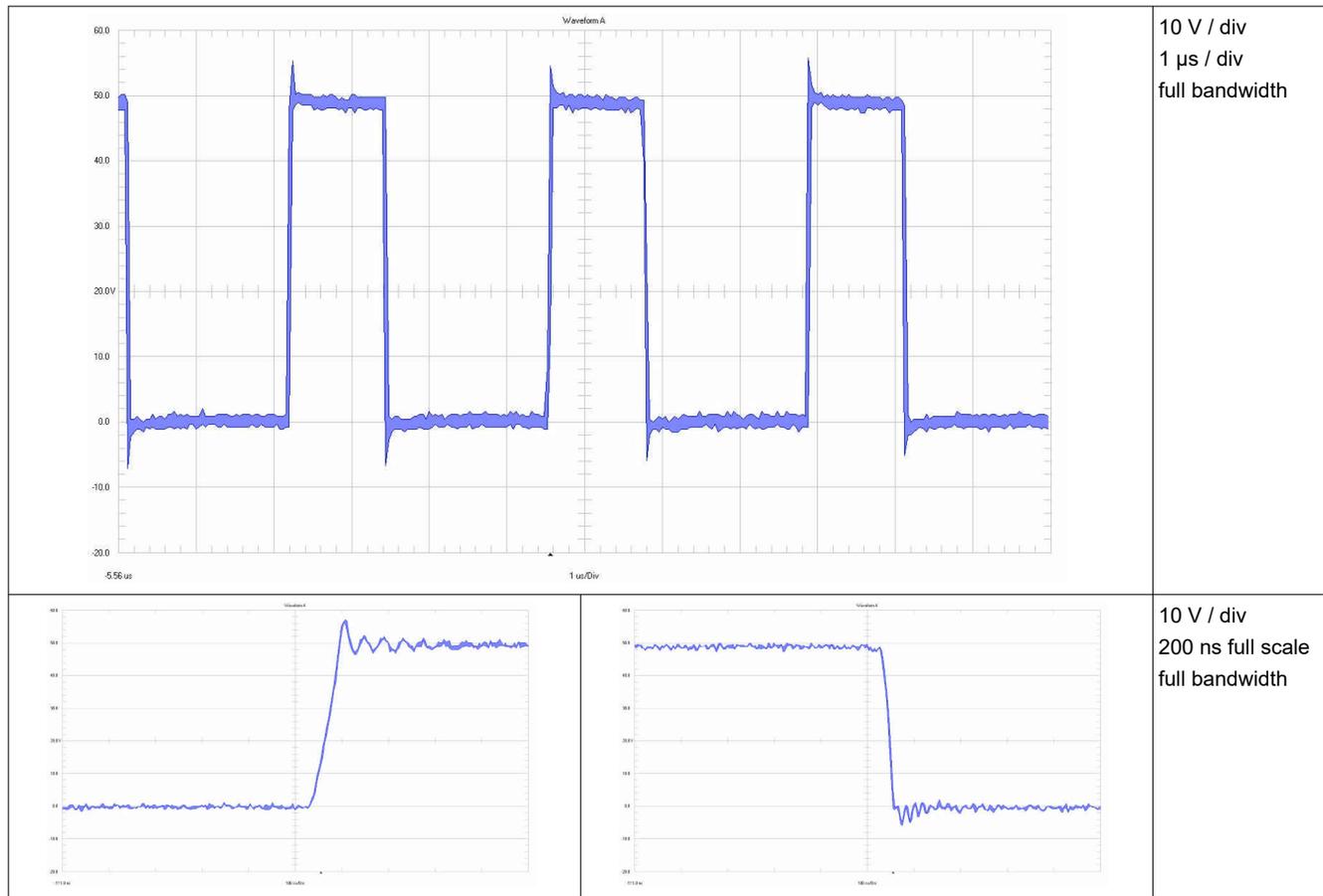

**Figure 3-14. Transistor Q2 Drain - GND**

3.1.3.2.2 Gate-GND

**Note**

The final application uses FETs with much lower gate charge QG. A gate resistor (3.3 Ω to 4.7 Ω) might reduce the ringing on the gate.


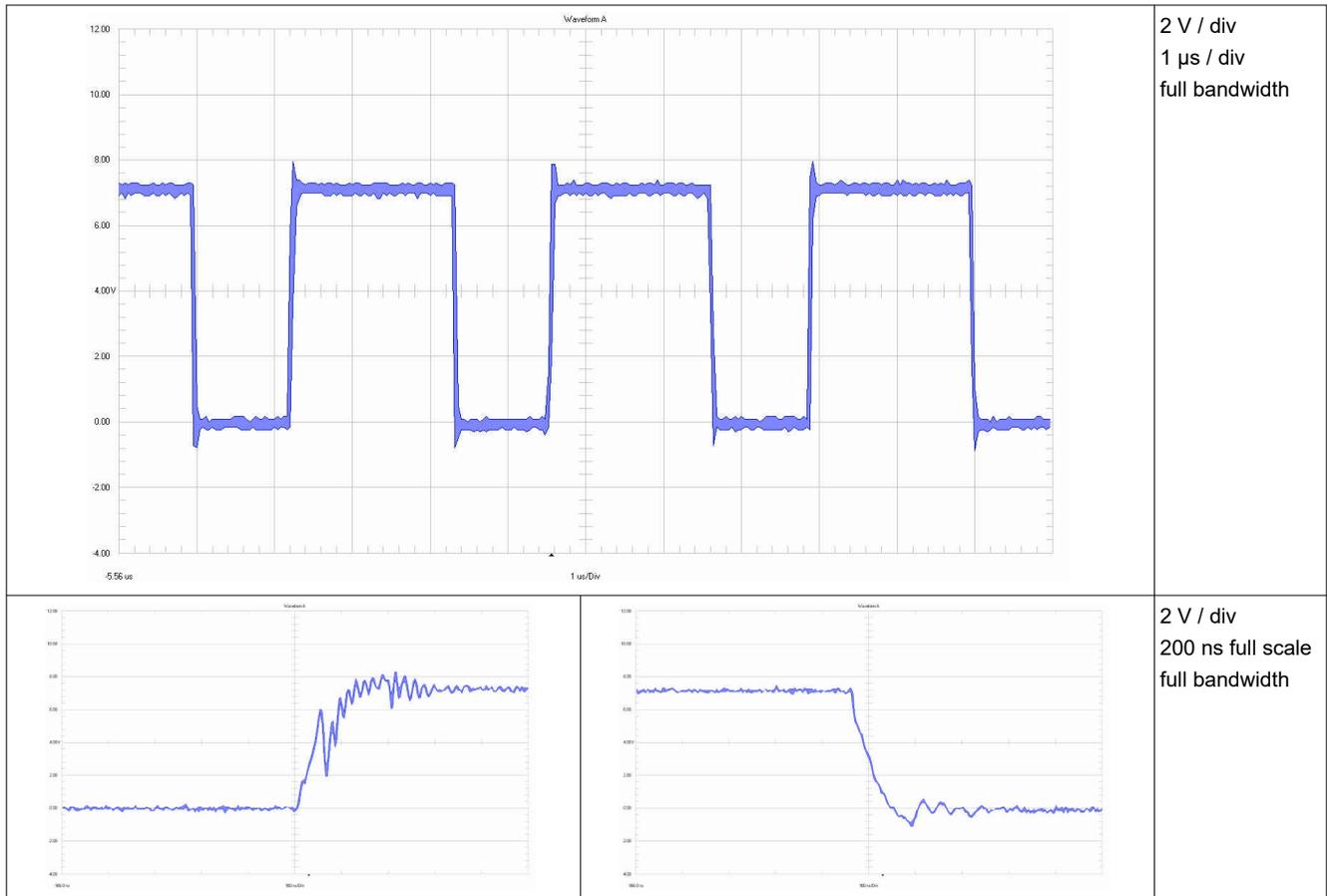


Figure 3-15. Transistor Q2 Gate - GND

**3.1.3.3 Diode D2**

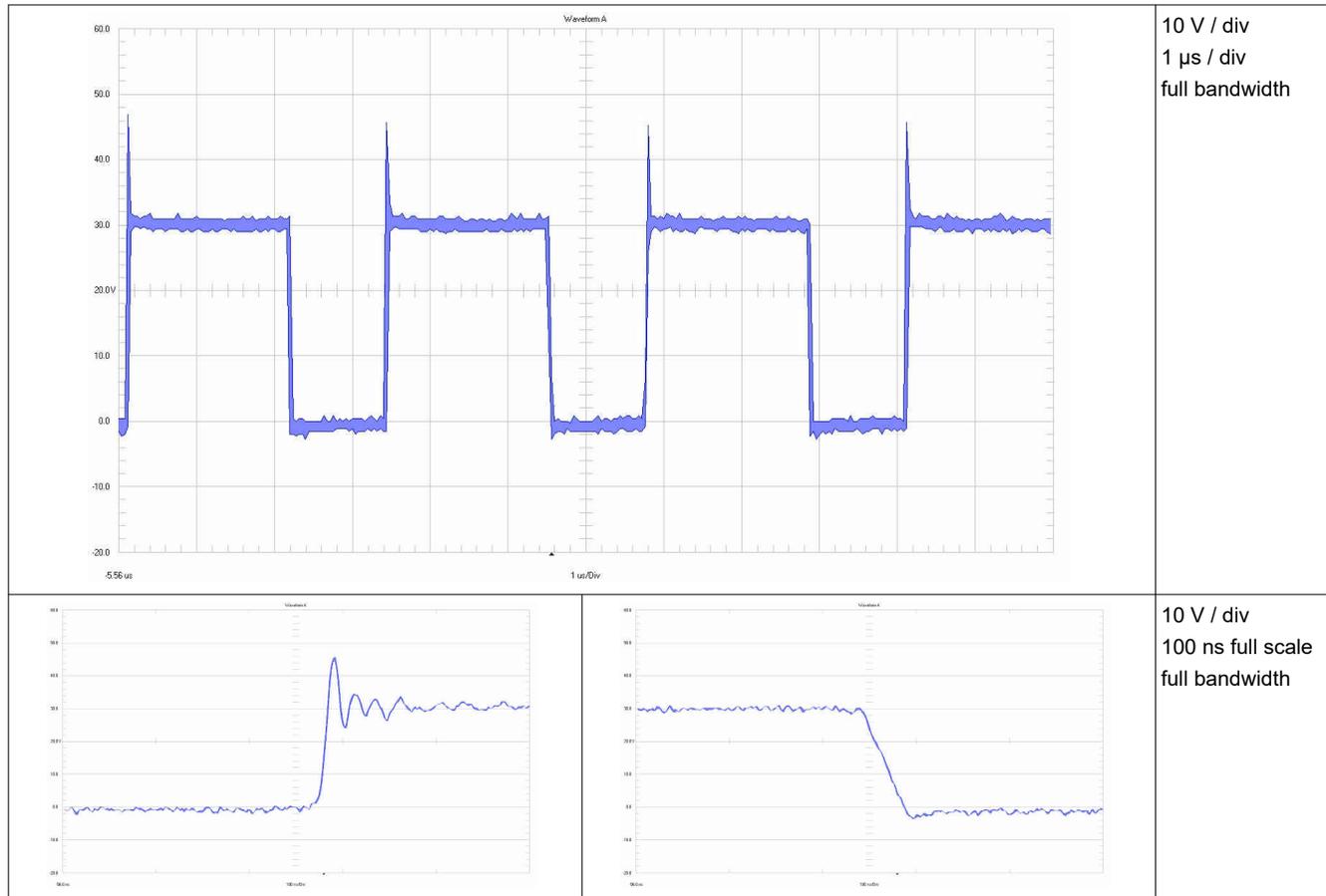

**Figure 3-16. Diode D2**

### 3.1.3.4 Transistor Q1

#### 3.1.3.4.1 Source - $V_{IN}$

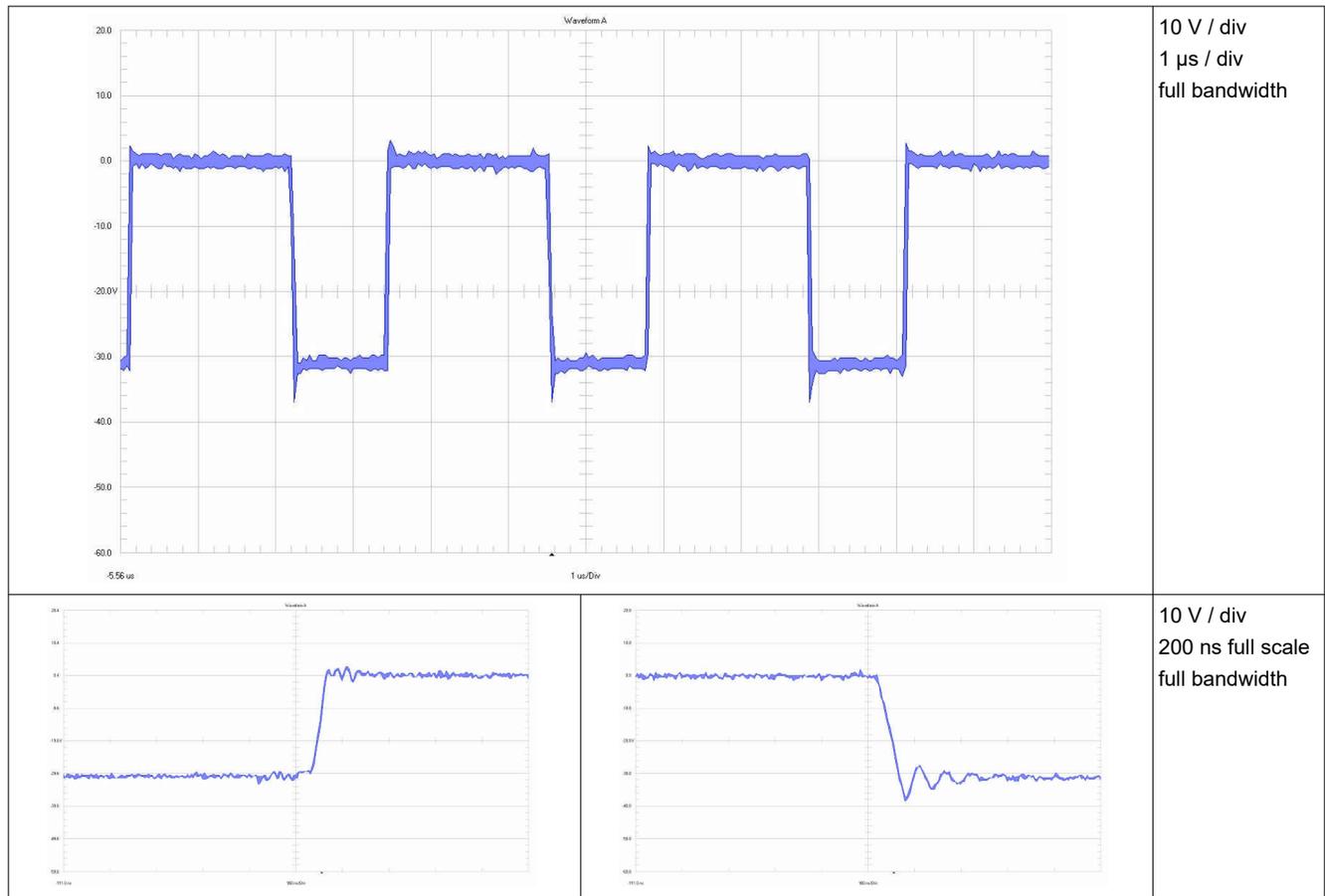


Figure 3-17. Transistor Q1 Source-Drain (referenced to  $V_{IN}$ )

3.1.3.4.2 Gate - Source

**Note**

The final application uses FETs with much lower gate charge QG. A gate resistor (3.3 Ω to 4.7 Ω) might reduce the ringing on the gate.


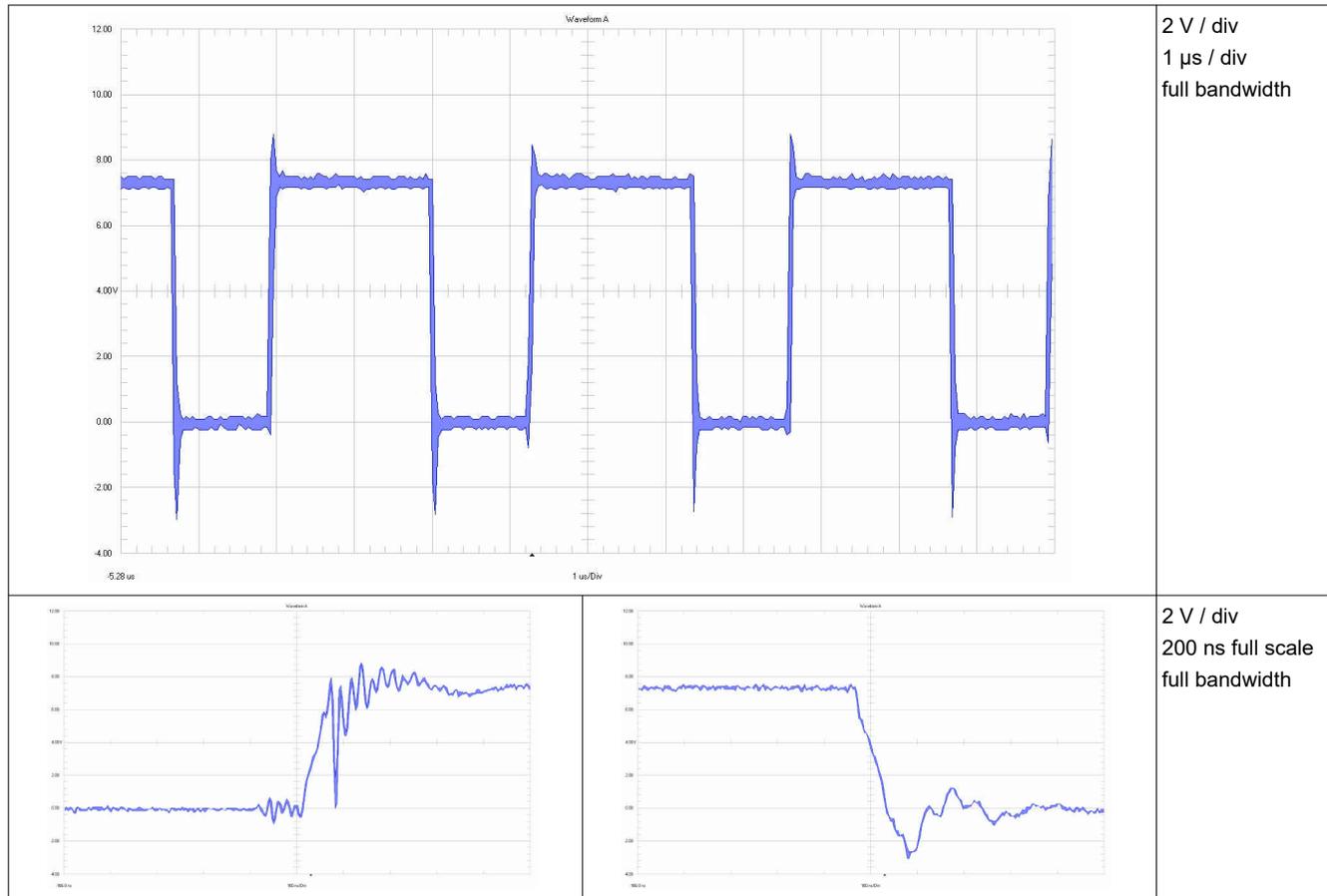



Figure 3-18. Transistor Q1 Gate - Source

### 3.1.4 48-V Output Voltage; 60-V Input Voltage

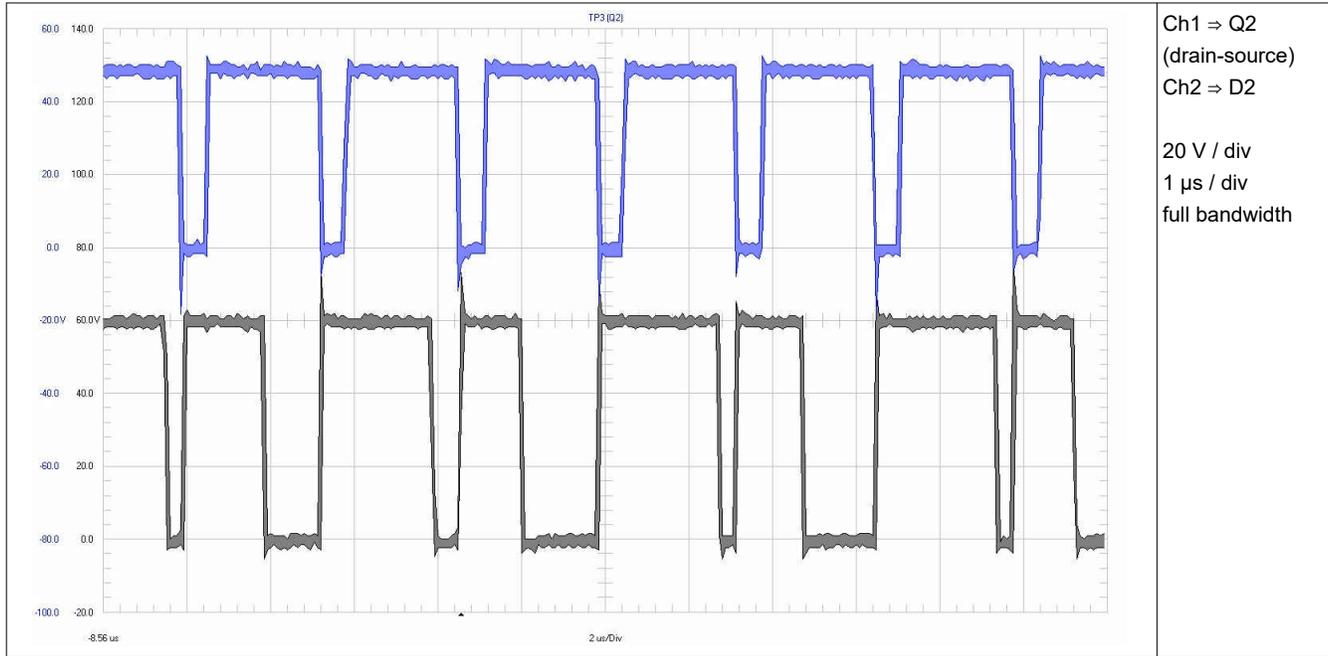

**Figure 3-19. Transistor Q2 Drain (TP3) to GND; Diode D2 (TP2) to GND**


**3.1.4.1 Diode D1**

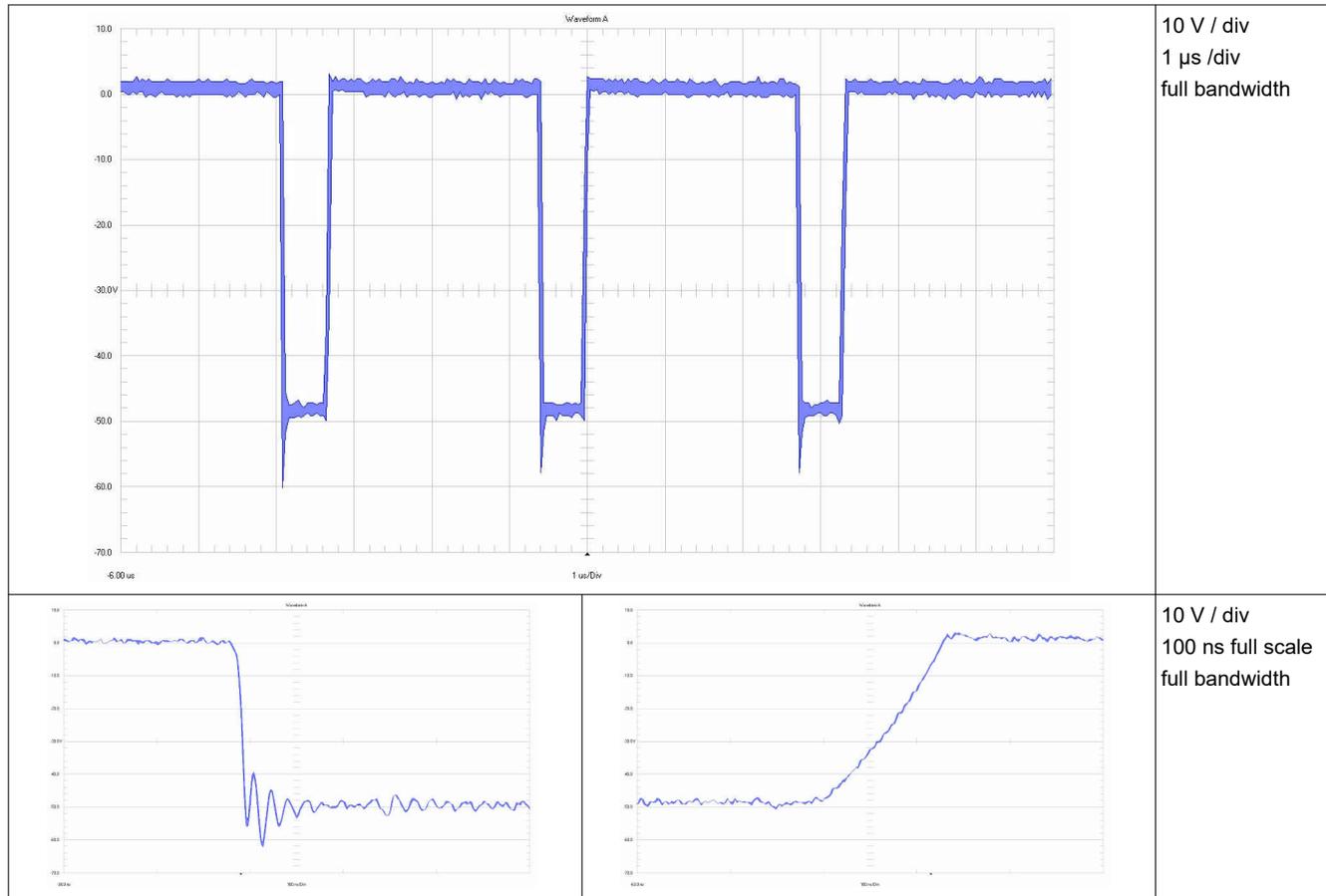

**Figure 3-20. Diode D1**

### 3.1.4.2 Transistor Q2

#### 3.1.4.2.1 Drain - GND

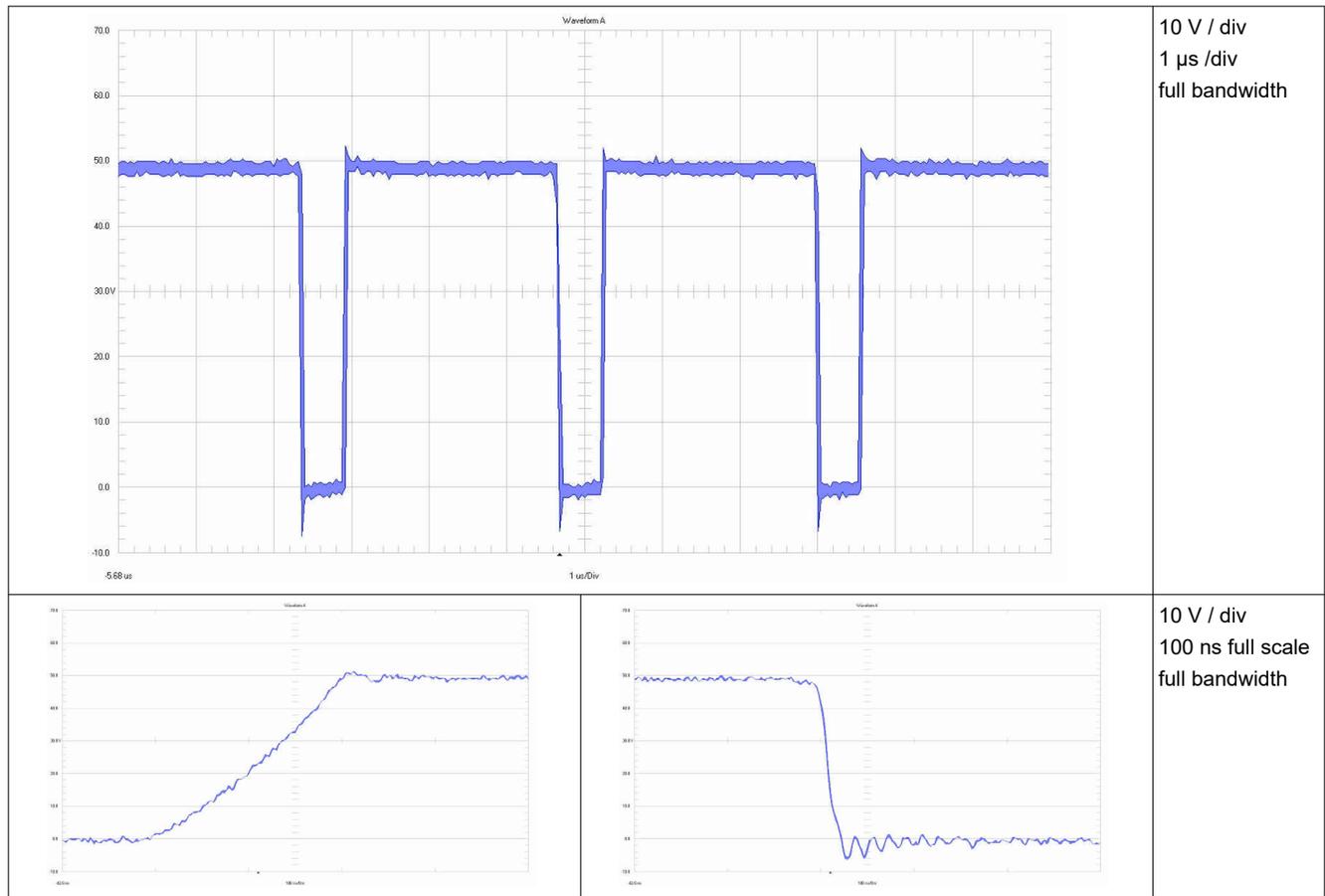


**Figure 3-21. Transistor Q2 Drain - GND**

3.1.4.2.2 Gate - GND

**Note**

The final application uses FETs with much lower gate charge QG. A gate resistor (3.3 Ω to 4.7 Ω) might reduce the ringing on the gate.

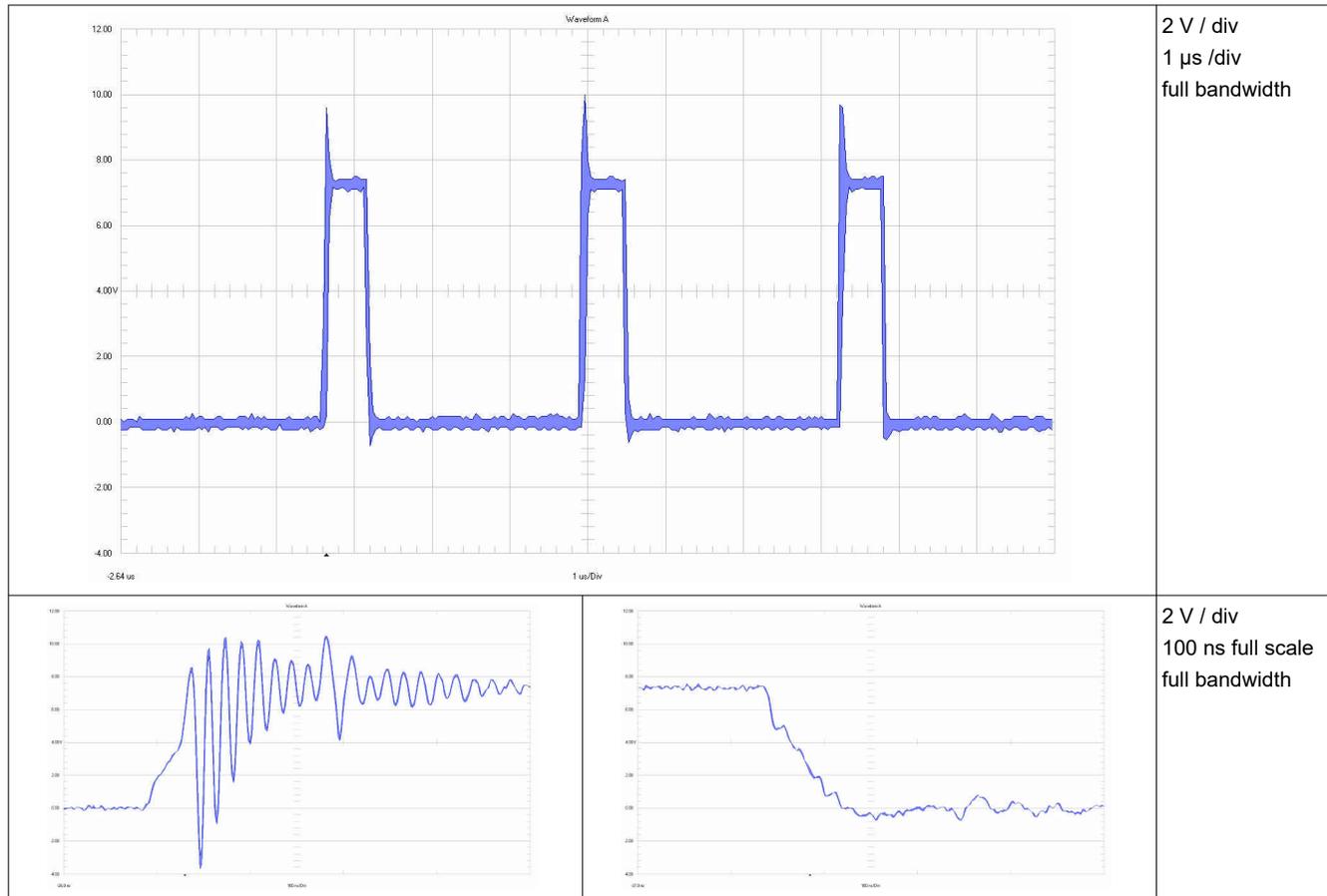

**Figure 3-22. Transistor Q2 Gate - GND**

### 3.1.4.3 Diode D2


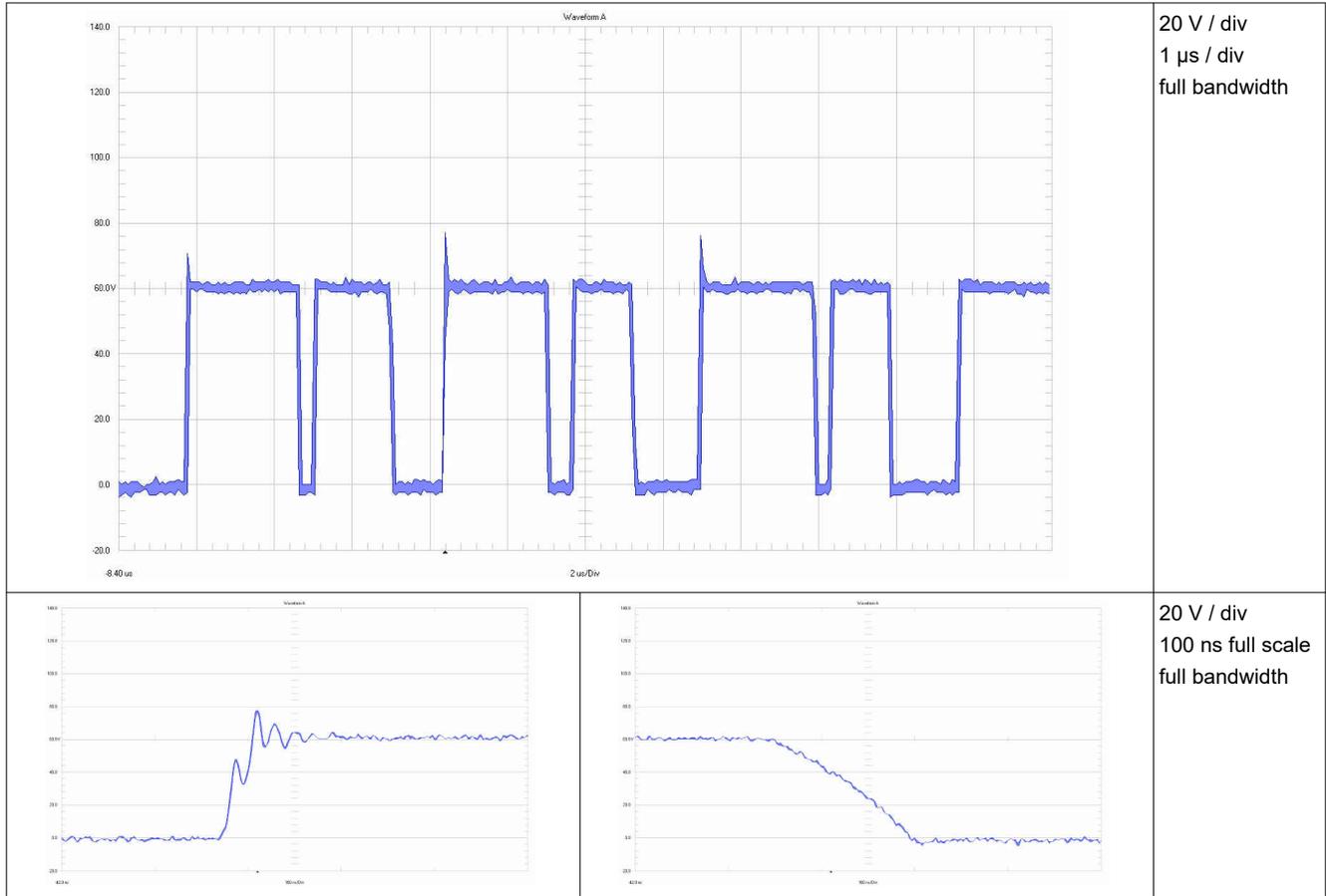


Figure 3-23. Diode D2

### 3.1.4.4 Transistor Q1

#### 3.1.4.4.1 Source - $V_{IN}$

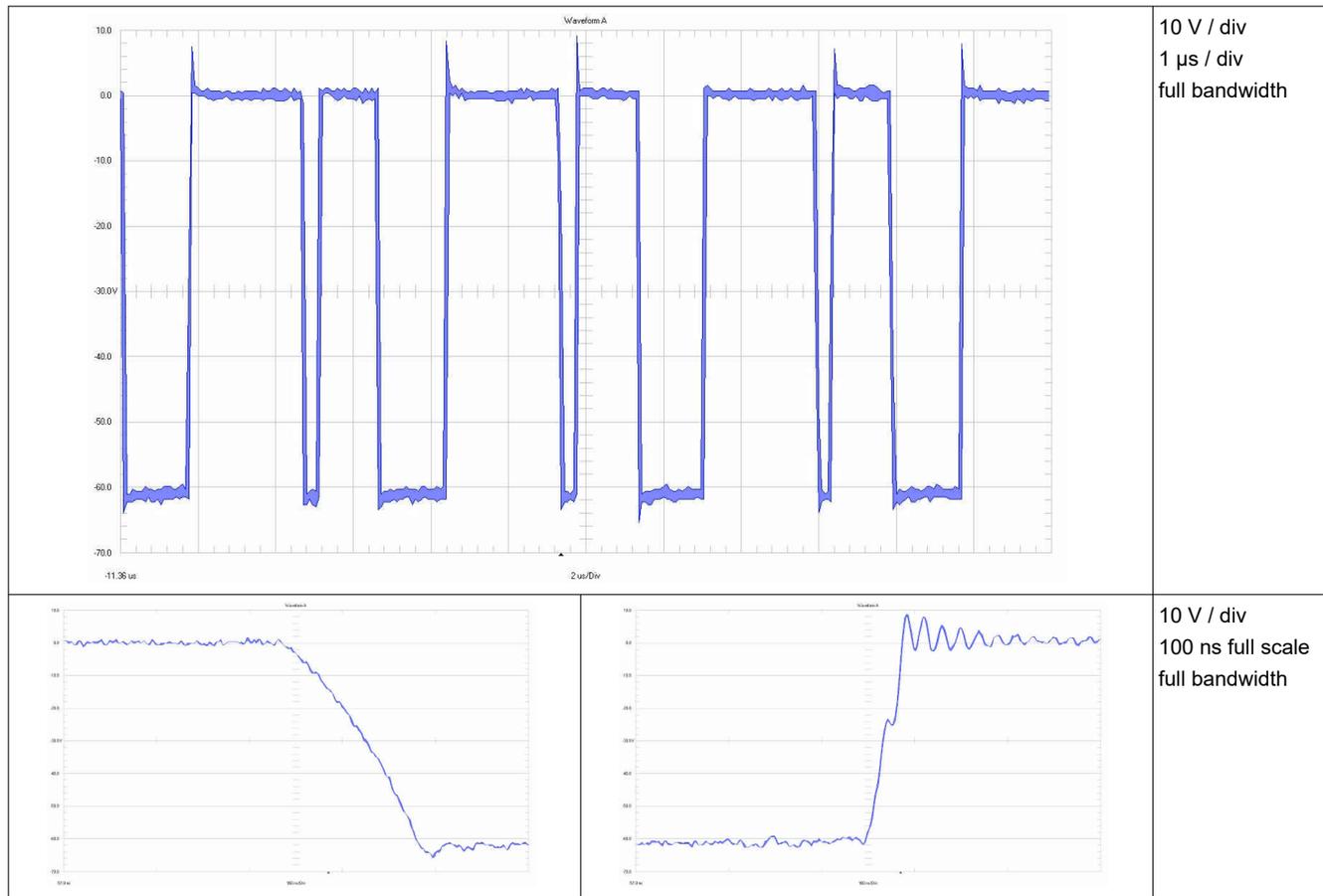

**Figure 3-24. Transistor Q1 Source - Drain (Referenced to  $V_{IN}$ )**

3.1.4.4.2 Gate - Source

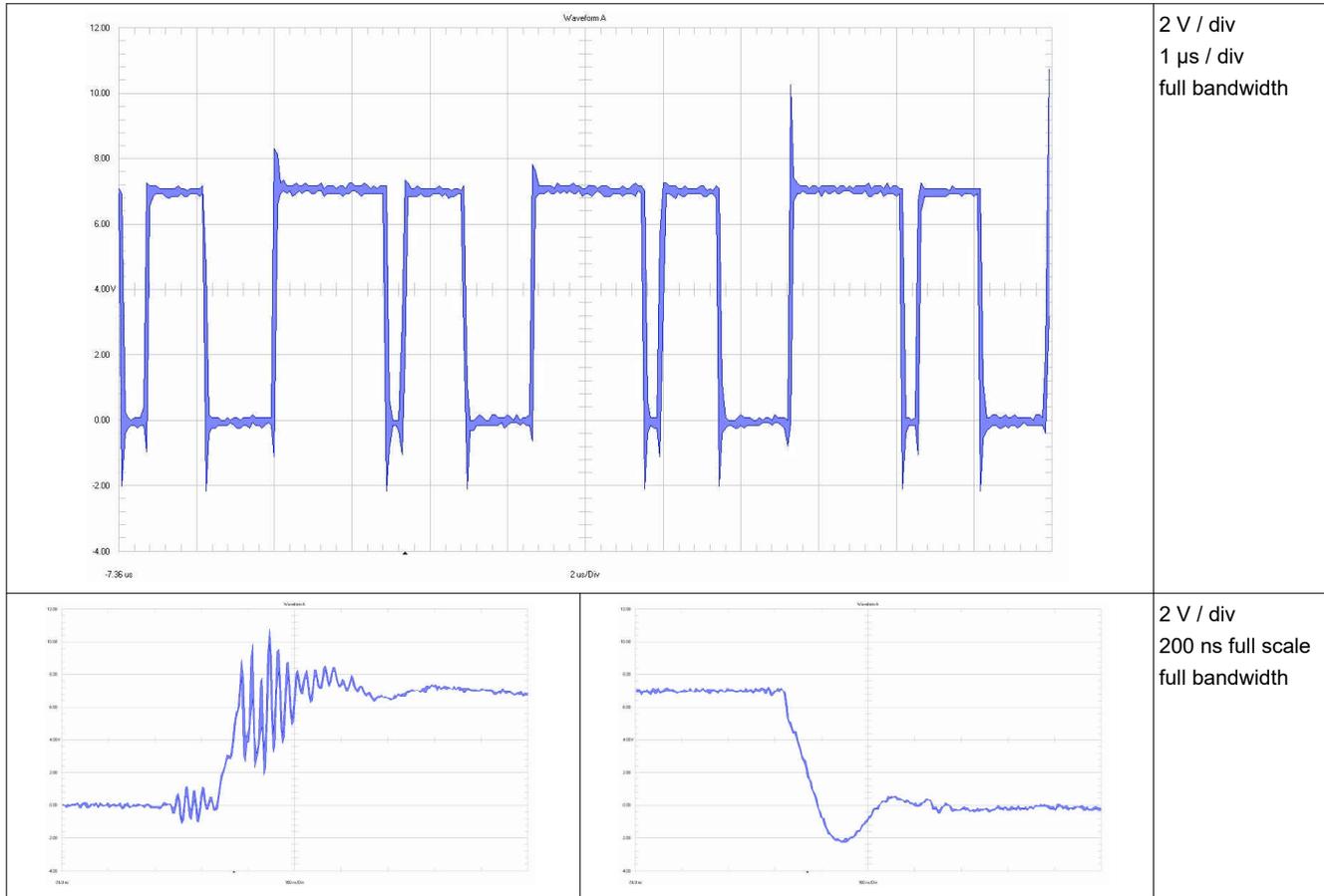


Figure 3-25. Transistor Q1 Gate - Source

### 3.2 Output Voltage Ripple

#### Note

Each trace in [Figure 3-26](#) and [Figure 3-27](#) was measured separately.

#### 3.2.1 24-V Output Voltage

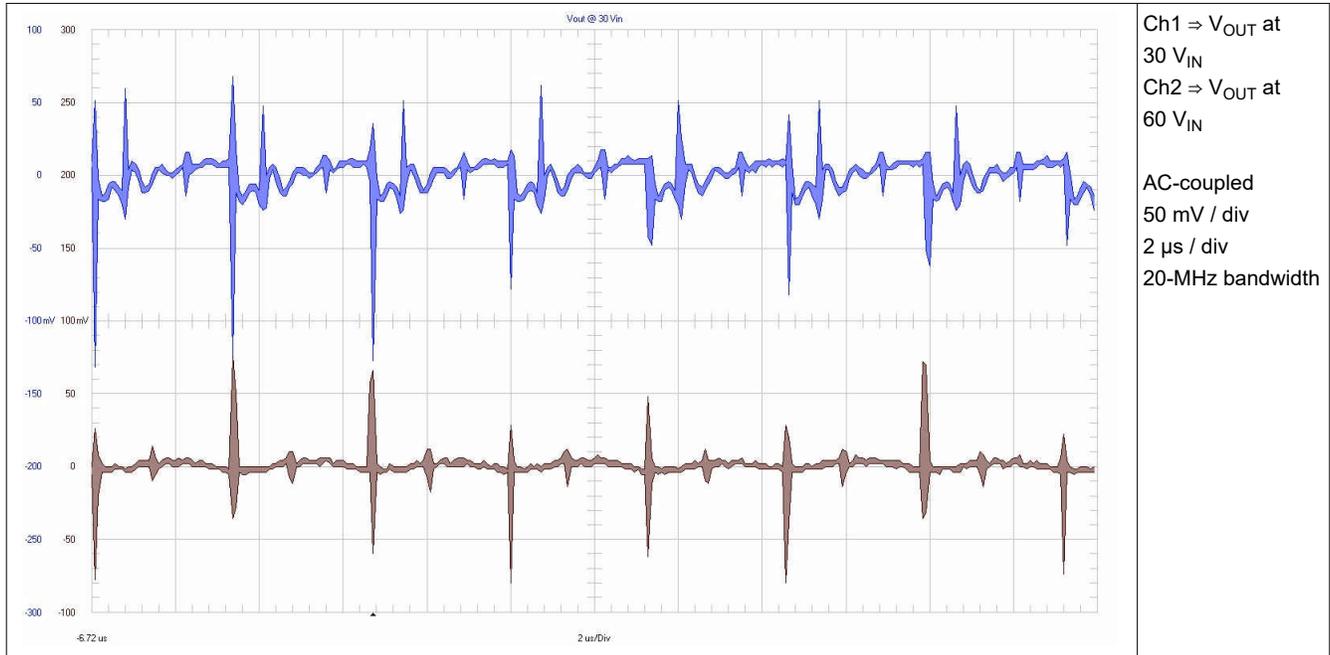


Figure 3-26. Output Voltage Ripple for 24  $V_{OUT}$

#### 3.2.2 48-V Output Voltage

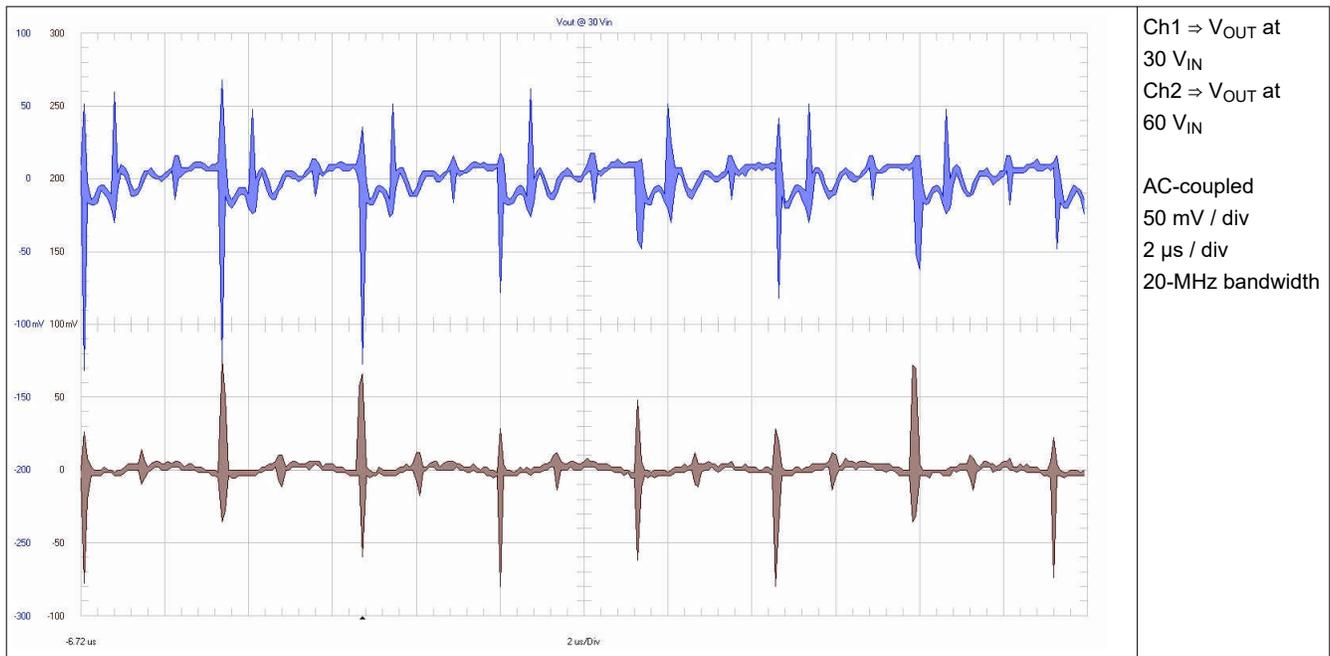


Figure 3-27. Output Voltage Ripple for 48  $V_{OUT}$

### 3.3 Input Voltage Ripple

**Note**

Each trace in [Figure 3-28](#) and [Figure 3-29](#) was measured separately.

#### 3.3.1 24-V Output Voltage

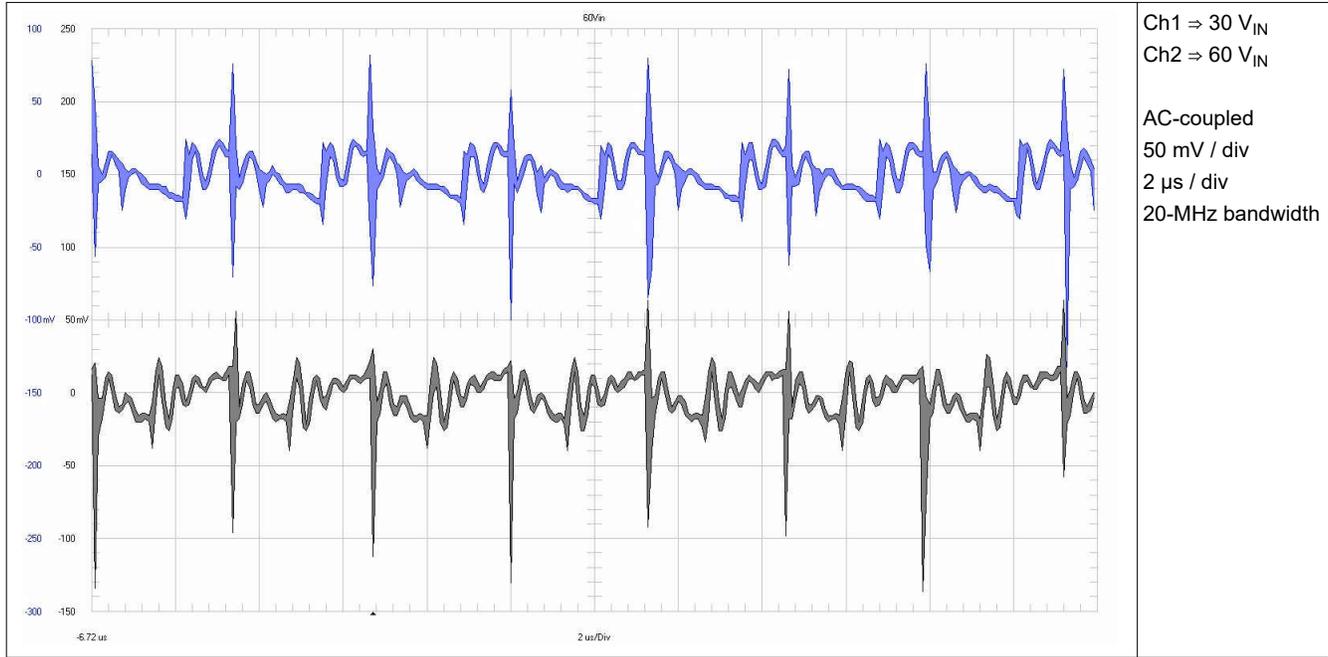


Figure 3-28. Input Voltage Ripple for 24 V<sub>OUT</sub>

#### 3.3.2 48-V Output Voltage

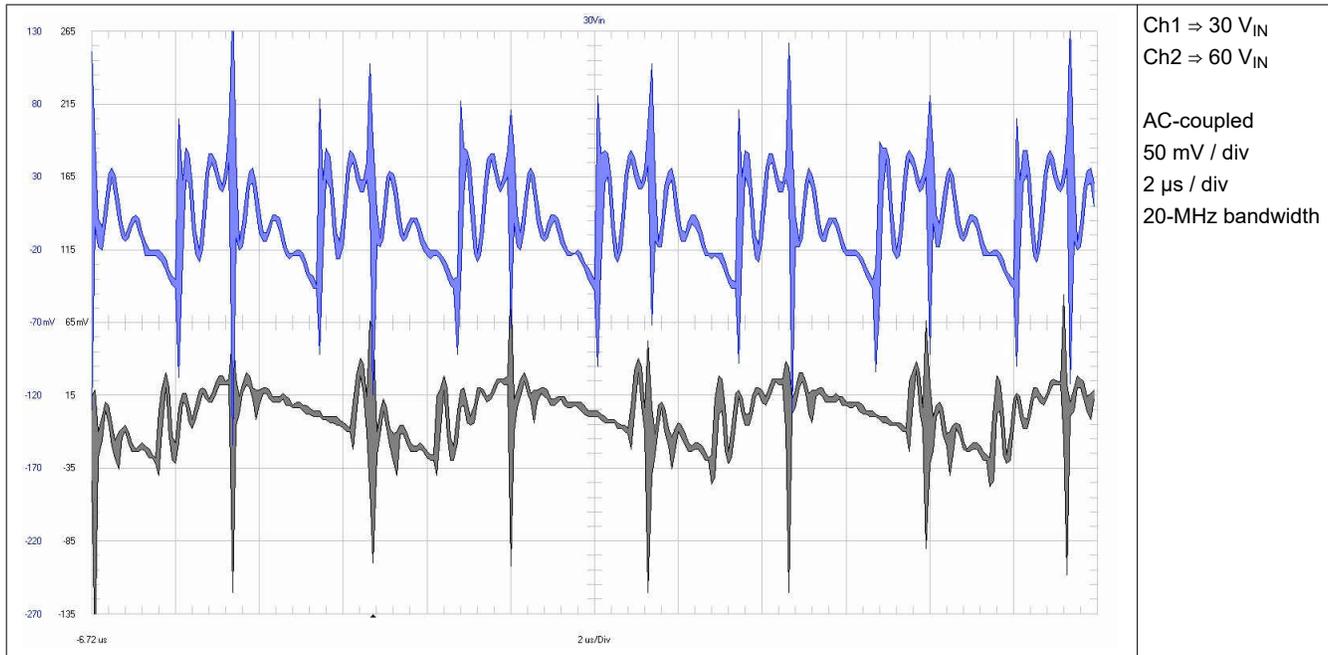


Figure 3-29. Input Voltage Ripple for 48 V<sub>OUT</sub>

### 3.4 Load Transients

The electronic load switches between 0.3 A and 0.6 A with a frequency of 75 Hz.

#### 3.4.1 24-V Output Voltage

##### 3.4.1.1 30-V Input Voltage

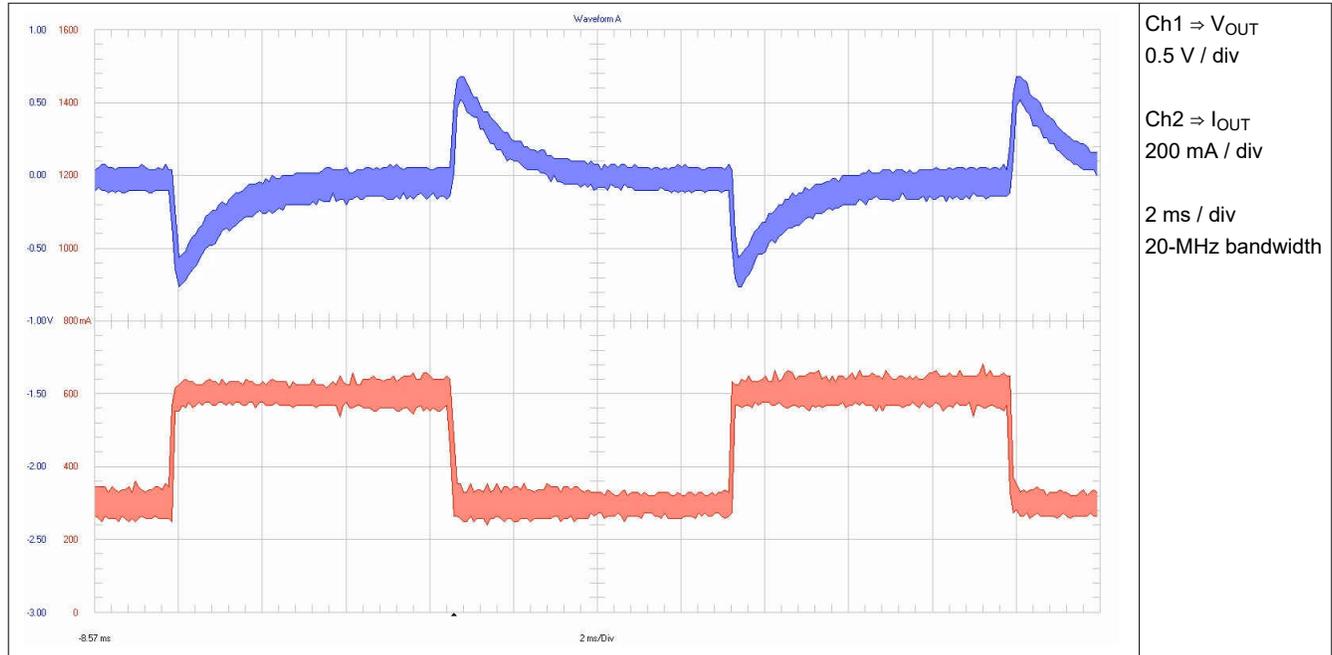


Figure 3-30. Transient at 30 V<sub>IN</sub> and 24 V<sub>OUT</sub>

##### 3.4.1.2 60-V Input Voltage

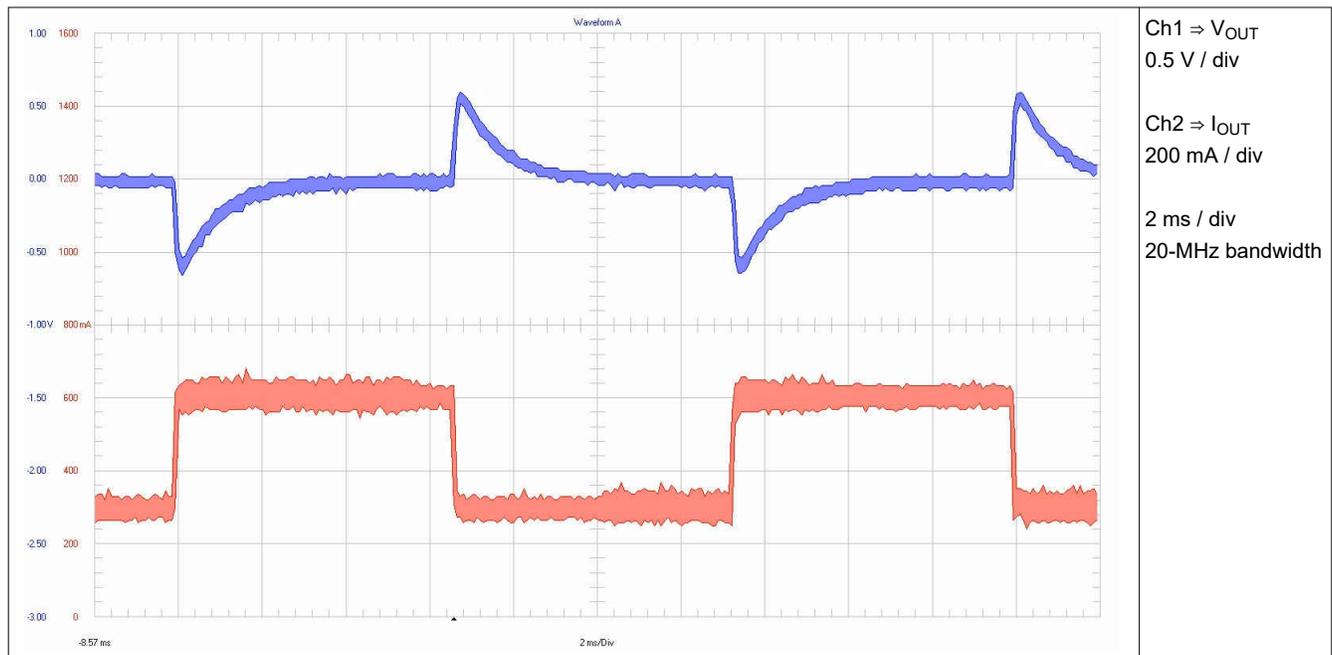


Figure 3-31. Transient at 60 V<sub>IN</sub> and 24 V<sub>OUT</sub>

### 3.4.2 48-V Output Voltage

#### 3.4.2.1 30-V Input Voltage

**Note**

This voltage combination is the worst case in boost mode due to *Right Half-Plane Zero (RHPZ)*.


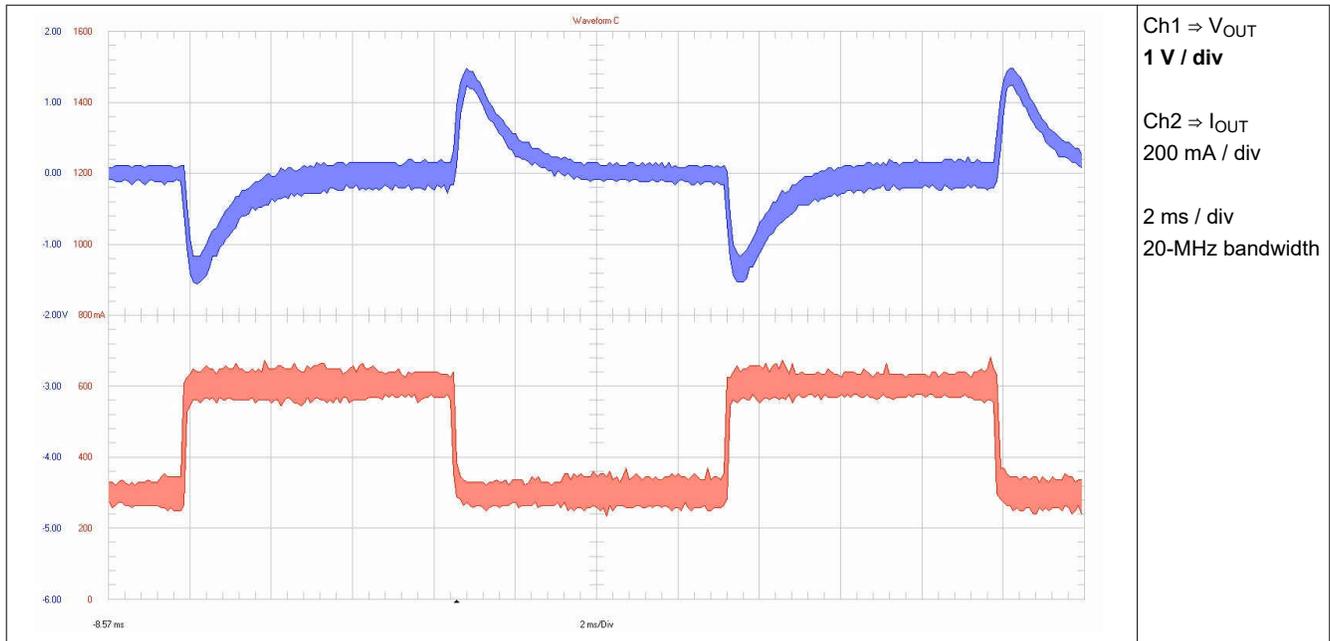


Figure 3-32. Transient at 30  $V_{IN}$  and 48  $V_{OUT}$

#### 3.4.2.2 60-V Input Voltage

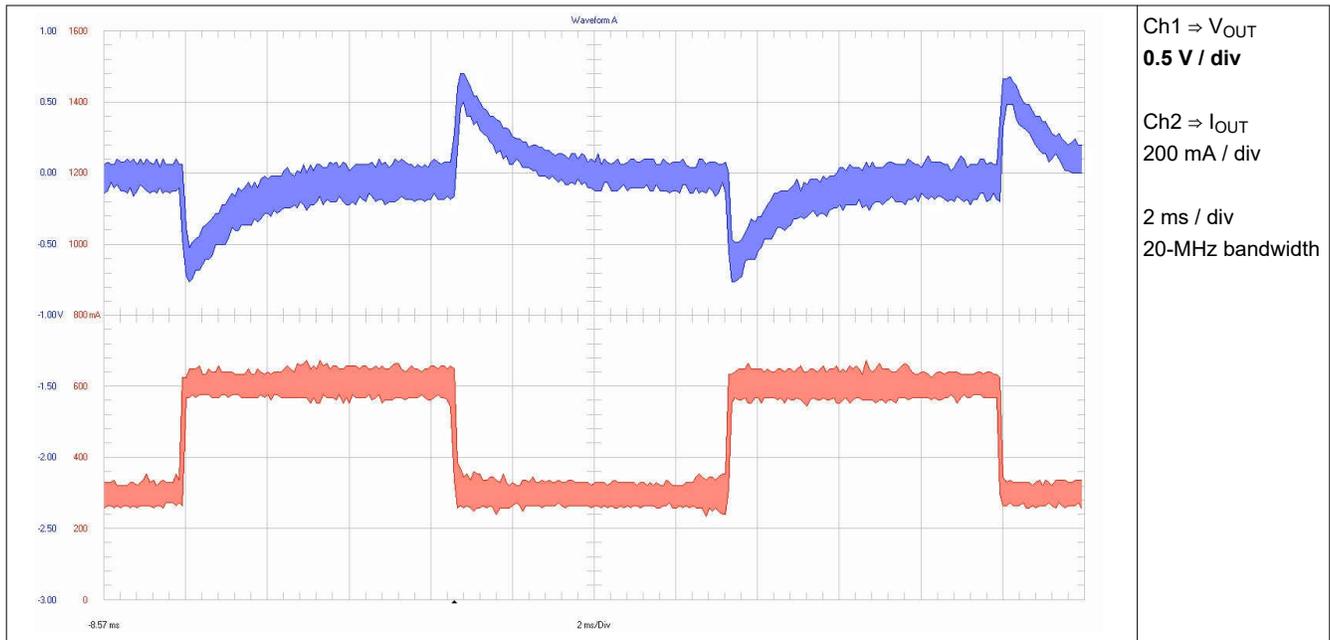

Loop compensation according to [Rev. B](#) ( $F_{co}$  1.2 kHz) shows transient response differential voltage (dv) < 3% for load transient 50%

Figure 3-33. Transient at 60  $V_{IN}$  and 48  $V_{OUT}$

### 3.5 Start-Up Sequence

#### 3.5.1 24-V Output Voltage

##### 3.5.1.1 30-V Input Voltage

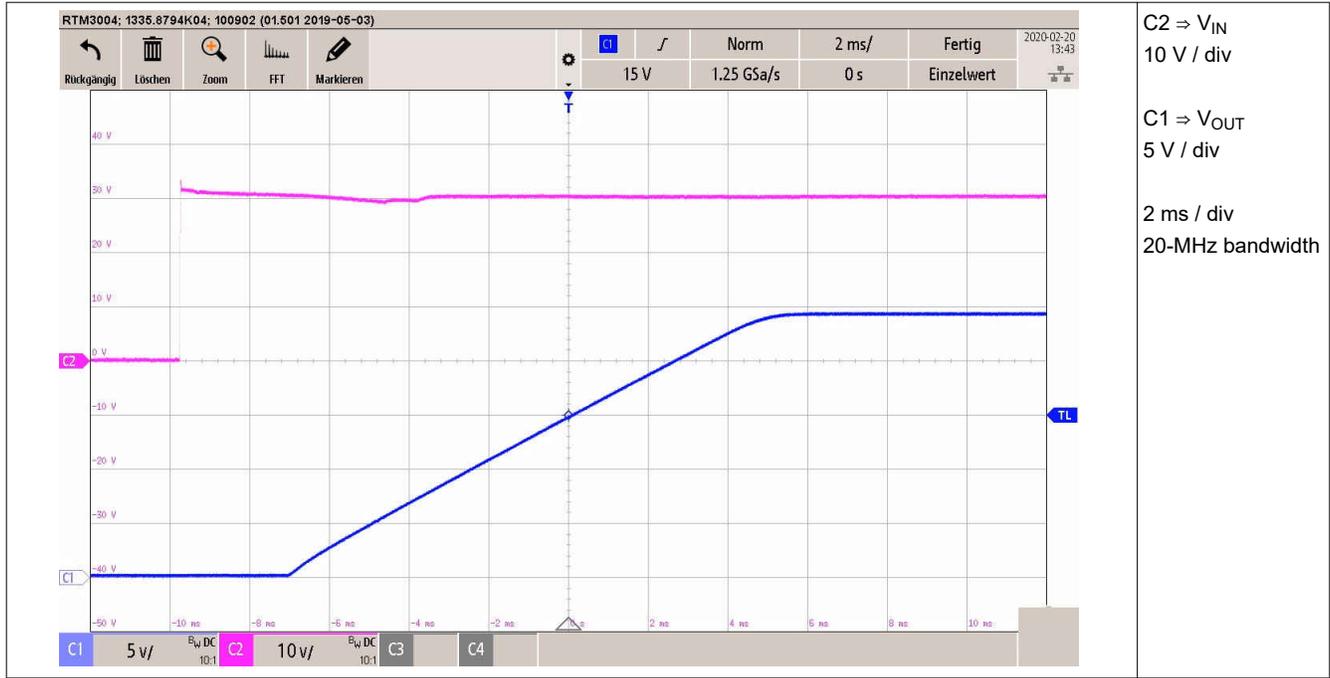


Figure 3-34. Start-up at 30 V<sub>IN</sub> and 24 V<sub>OUT</sub>

##### 3.5.1.2 60-V Input Voltage

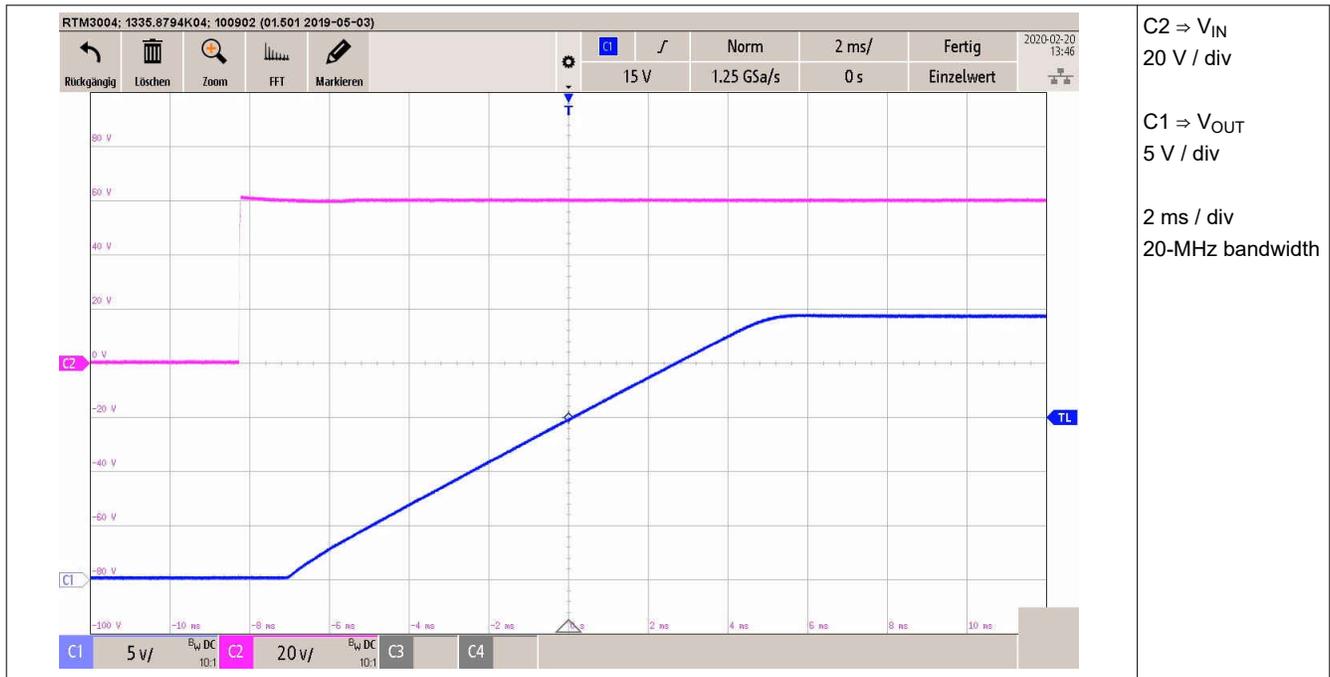


Figure 3-35. Start-up at 60 V<sub>IN</sub> and 24 V<sub>OUT</sub>

### 3.5.2 48-V Output Voltage

#### 3.5.2.1 30-V Input Voltage


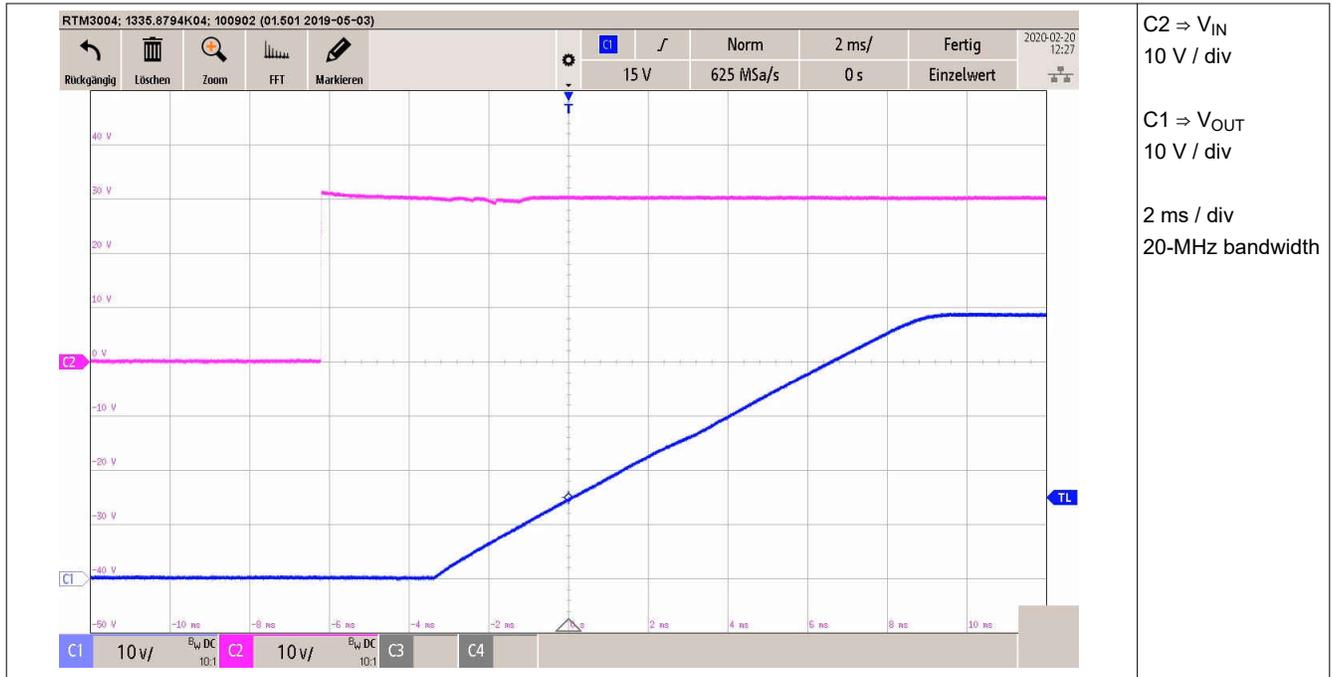


Figure 3-36. Start-up at 30 V<sub>IN</sub> and 48 V<sub>OUT</sub>

#### 3.5.2.2 60-V Input Voltage

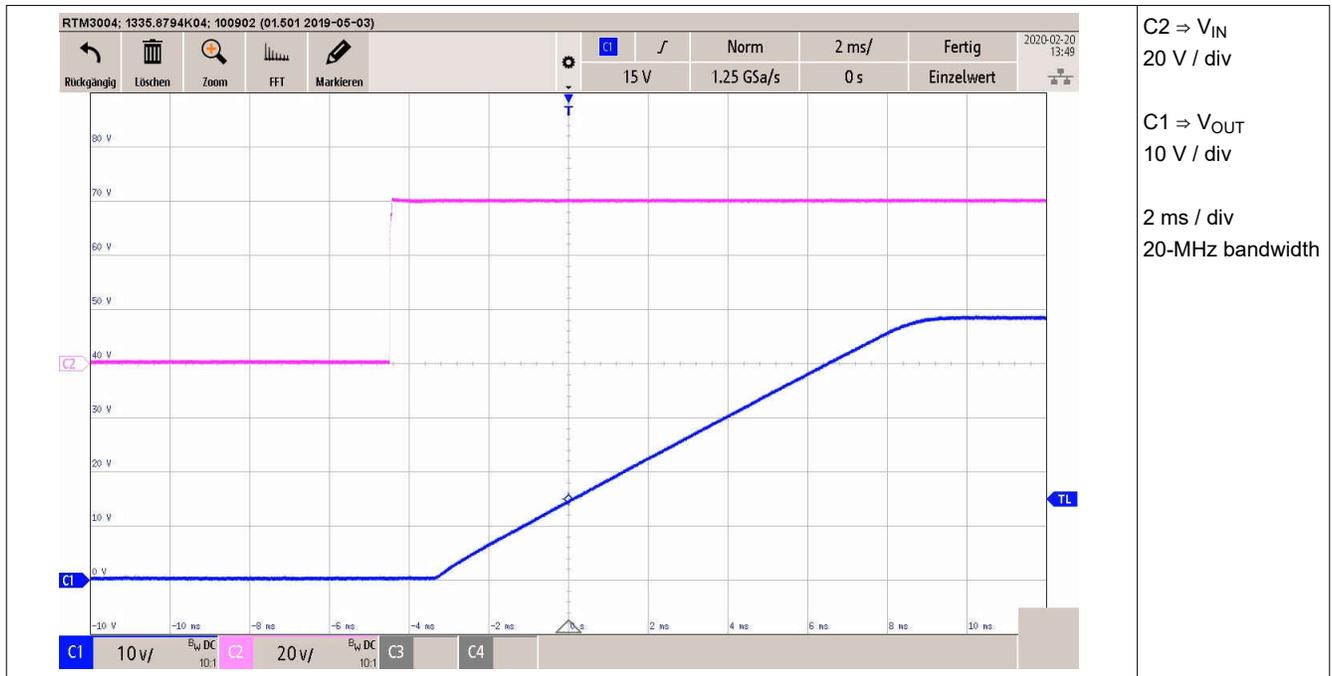

Soft-start capacitor C18, 100 nF results in soft-start time of 12 ms.

Figure 3-37. Start-up at 60 V<sub>IN</sub> and 48 V<sub>OUT</sub>

### 3.6 Shutdown Sequence

#### 3.6.1 24-V Output Voltage

##### 3.6.1.1 30-V Input Voltage

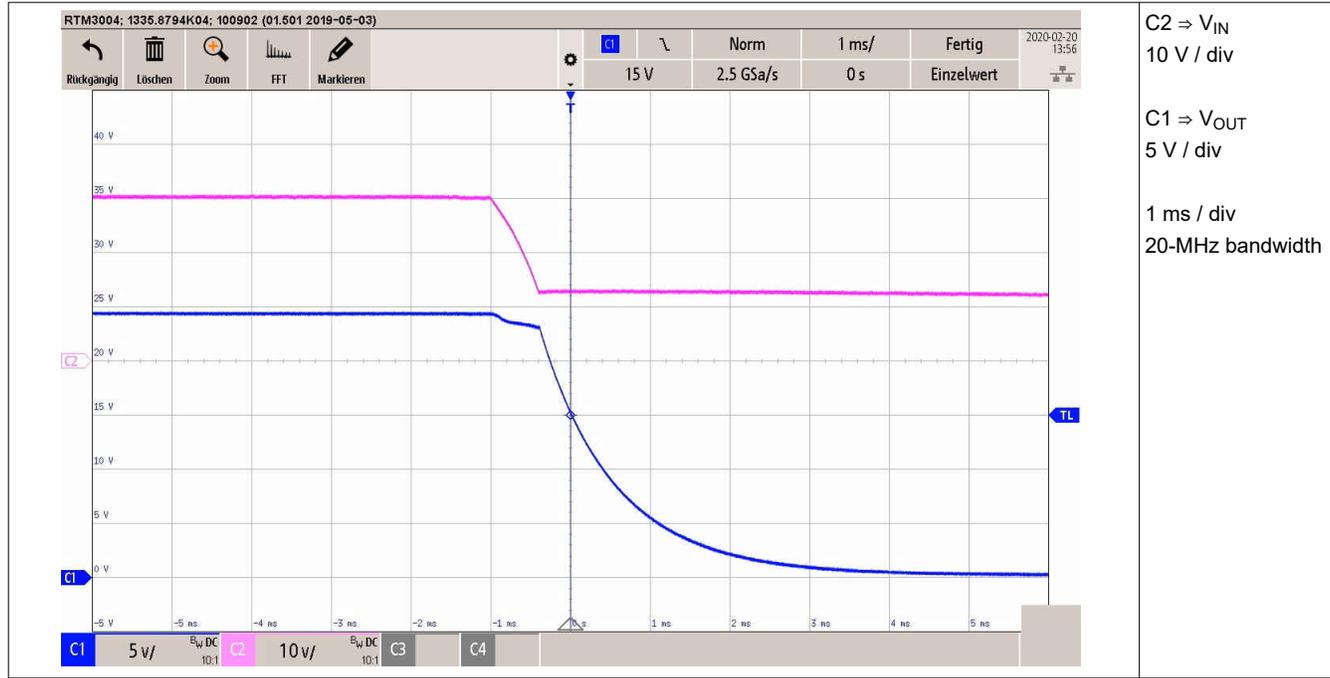


Figure 3-38. Shutdown at 30 V<sub>IN</sub> and 24 V<sub>OUT</sub>

##### 3.6.1.2 60-V Input Voltage

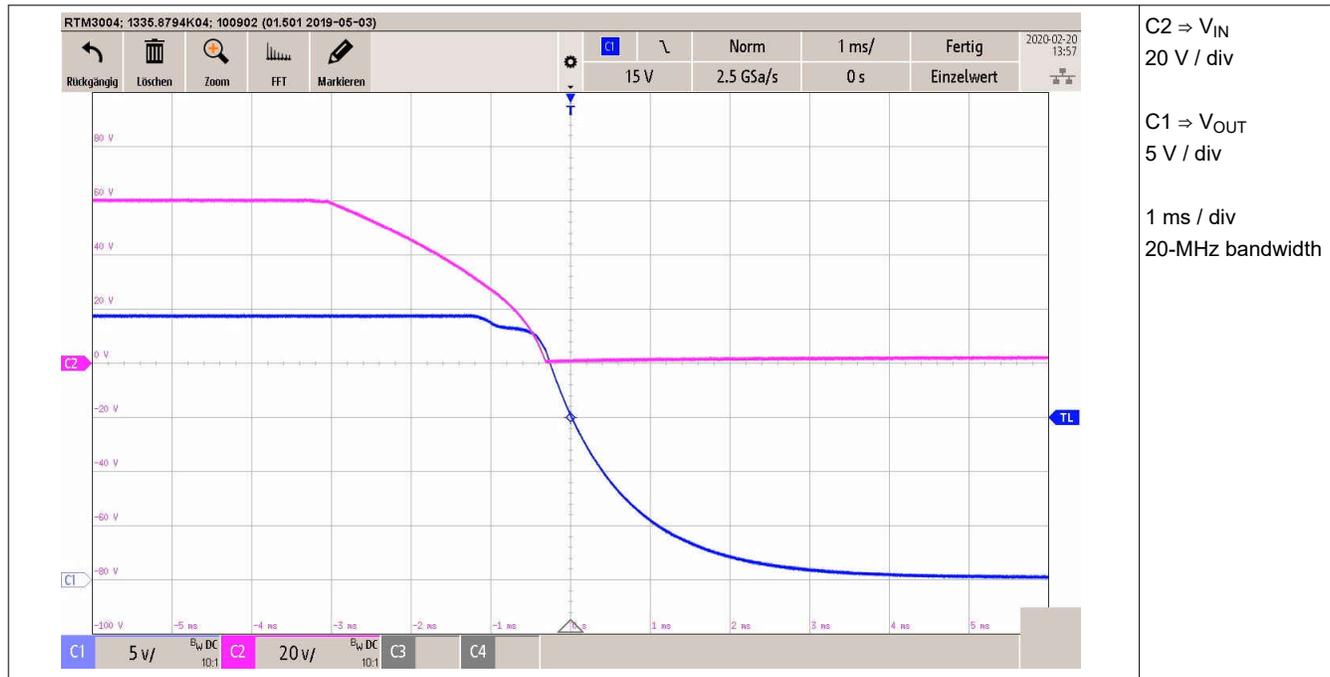


Figure 3-39. Shutdown at 60 V<sub>IN</sub> and 24 V<sub>OUT</sub>

### 3.6.2 48-V Output Voltage

#### 3.6.2.1 30-V Input Voltage

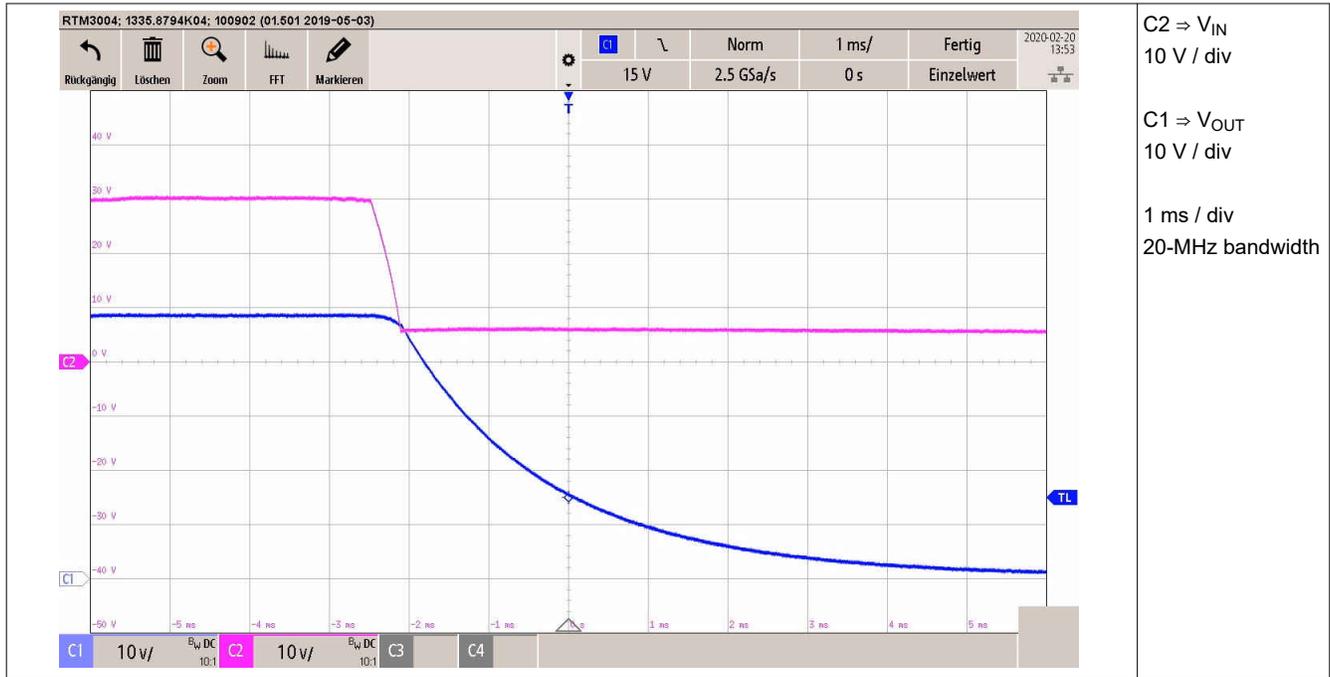


Figure 3-40. Shutdown at 30 V<sub>IN</sub> and 48 V<sub>OUT</sub>

#### 3.6.2.2 60-V Input Voltage

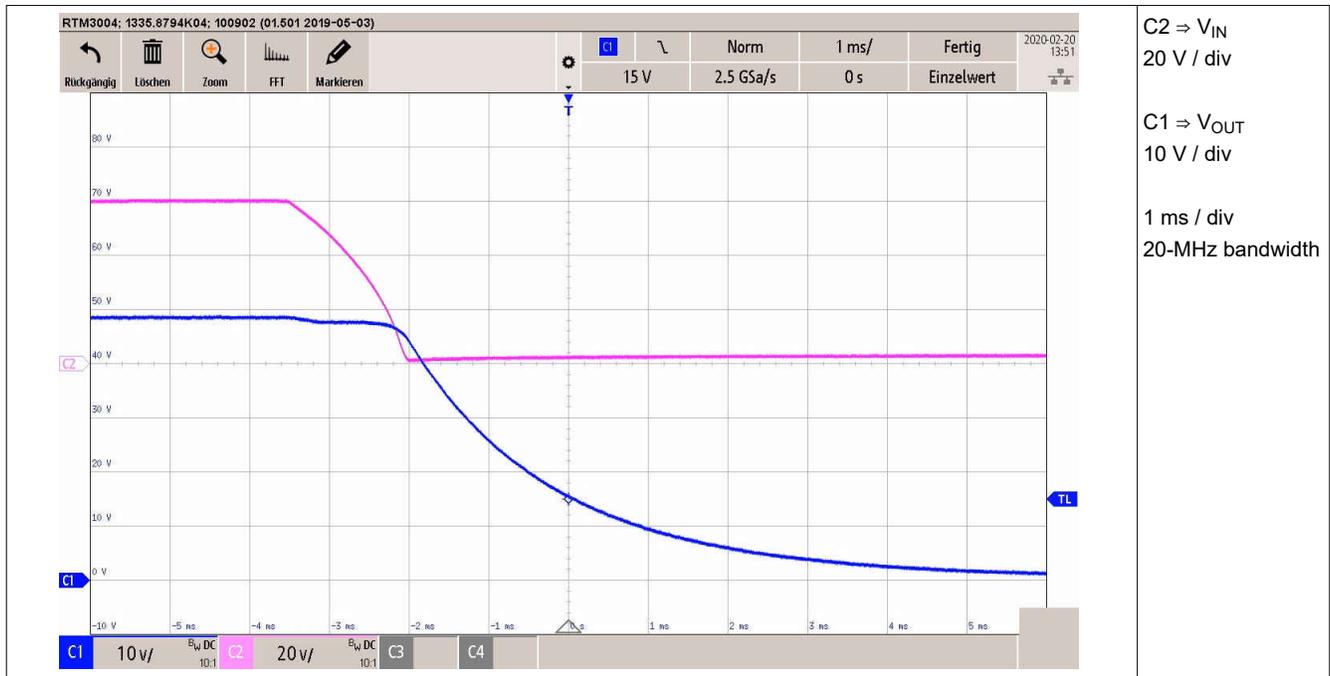


Figure 3-41. Shutdown at 60 V<sub>IN</sub> and 48 V<sub>OUT</sub>

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated