

# 24-W, Low-Input Voltage Synchronous Boost Converter Reference Design



## Description


This reference design uses the LM51521-Q1 boost controller to supply an 8-V, 3-A load and has been optimized to operate from a single-cell supercapacitor at the input. The converter can discharge a supercapacitor as low as 1.0 V to leverage as much of the stored energy as possible to open a car door in an emergency situation, where the KL30 car battery voltage is no longer present.

## Features


- Converter can operate from a single-cell supercapacitor and deliver 24 W of output power
- Operates down to 1.0-V input voltage enabling deep discharge of a supercapacitor
- High-efficiency conversion due to use of synchronous rectification
- Starts up from as low as 1.25 V
- Design has been built and tested
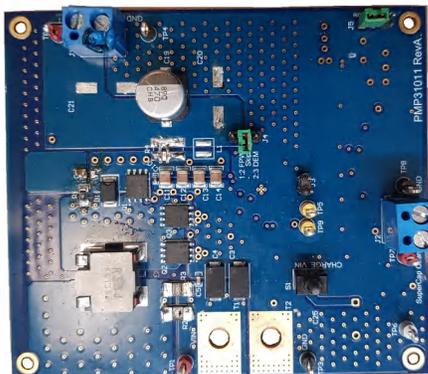
## Applications


- [Automotive door module](#)
- [Automotive sliding door module](#)



Top Photo

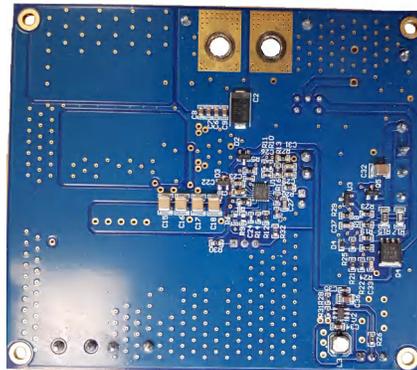

Bottom Photo

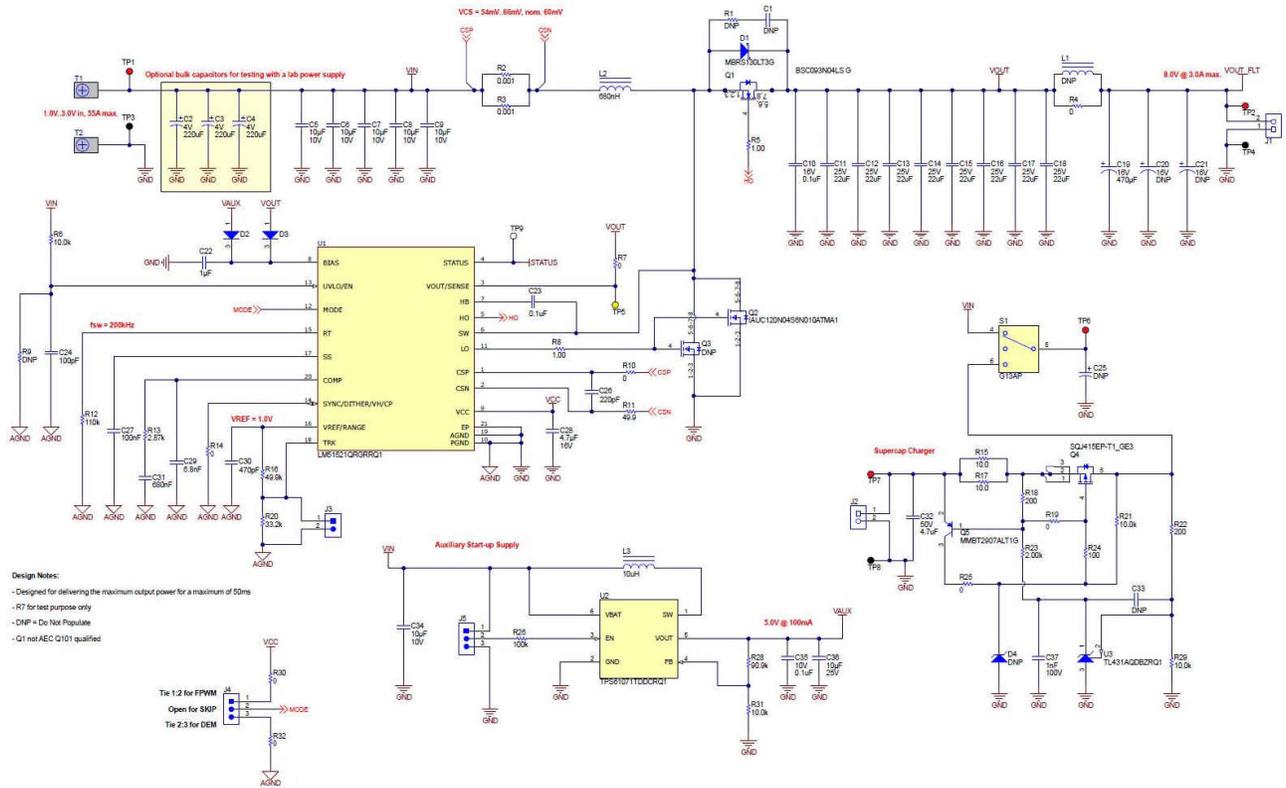

Schematic

## 1 Test Prerequisites

### 1.1 Voltage and Current Requirements

**Table 1-1. Voltage and Current Requirements**

Parameter	Specifications
Input Voltage	1.0 V to 3.0 V
Output Voltage	8.0 V
Output Current (maximum)	3.0 A
Isolation	no

### 1.2 Considerations

The lab power supply must be connected to the printed-circuit board (PCB). Make this connection with very short cables ( $\leq 30$  cm) to avoid resonances between the output of the lab power supply and the input circuit on the PCB, which can influence the look and results of the frequency analysis.

The copper thickness on the PCB must be a minimum of 70  $\mu\text{m}$ . The tested PCB had 105  $\mu\text{m}$  for the top and bottom layer. Measurements, including efficiency, were taken at room temperature without forced-air cooling.

Unless otherwise indicated:

- The board was assembled with two low-side FETs (Q2, Q3) and a 330-nH inductor L2
- The output current was adjusted to 3.0 A

The circuit switches on at 1.10 V and off at about 0.45 V ( $V_{\text{EN-Falling}}$  level). This individual circuit switches around 200 kHz.

The converter works in continuous conduction mode (CCM) at low input voltage and in discontinuous conduction mode (DCM) at higher input voltage. Under light load conditions the converter was operating in skip mode.

The transfer region DCM to CCM can be seen around:

- 1  $V_{\text{IN}} \Rightarrow 0.57 A_{\text{OUT}}$
- 2  $V_{\text{IN}} \Rightarrow 2.1 A_{\text{OUT}}$
- > 2.48  $V_{\text{IN}} \Rightarrow 3 A_{\text{OUT}}$

### 1.3 Dimensions

The size of the four-layer board is 83.5 mm  $\times$  95.3 mm. The copper thickness of the outer layer is 105  $\mu\text{m}$  and the inner layer is 35  $\mu\text{m}$ .

## 2 Testing and Results

### 2.1 Efficiency Graphs

#### 2.1.1 One Low-Side FET , 680-nH Coil , 1.0 V<sub>IN</sub> – 1.5 V<sub>IN</sub>

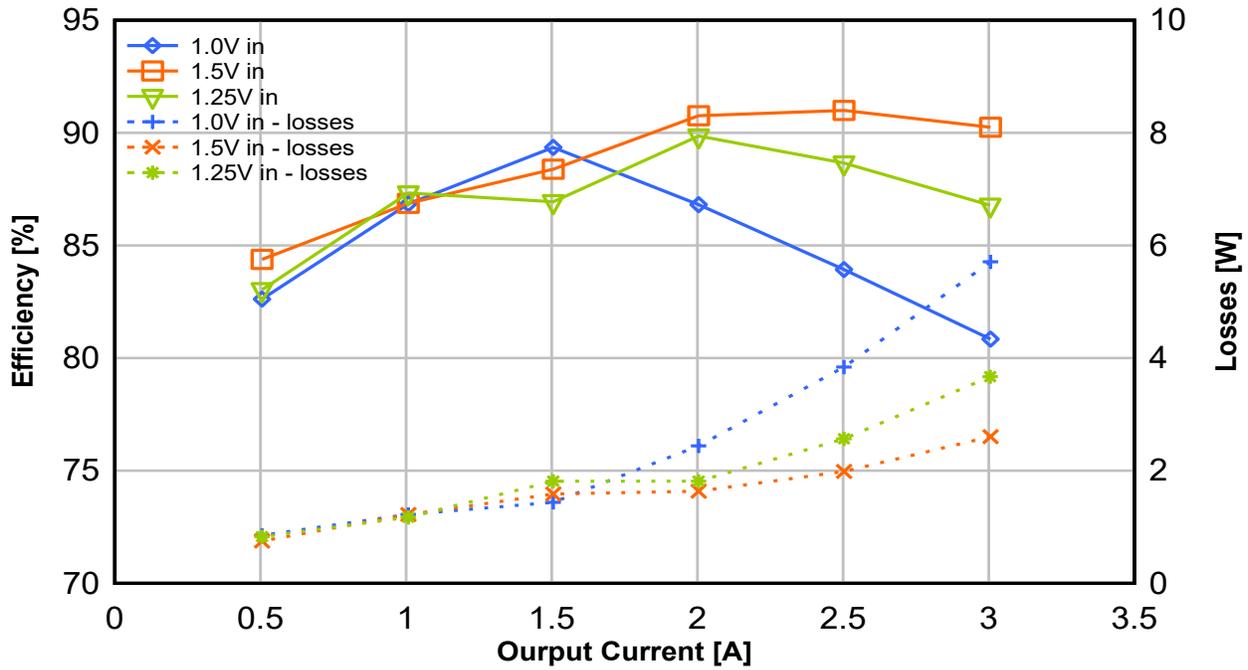


Figure 2-1. Efficiency and Losses vs Output Current From 1-V to 1.5-V Input Voltage

#### 2.1.2 One Low-Side FET , 680-nH Coil , 2.0 V<sub>IN</sub> – 3.0 V<sub>IN</sub>

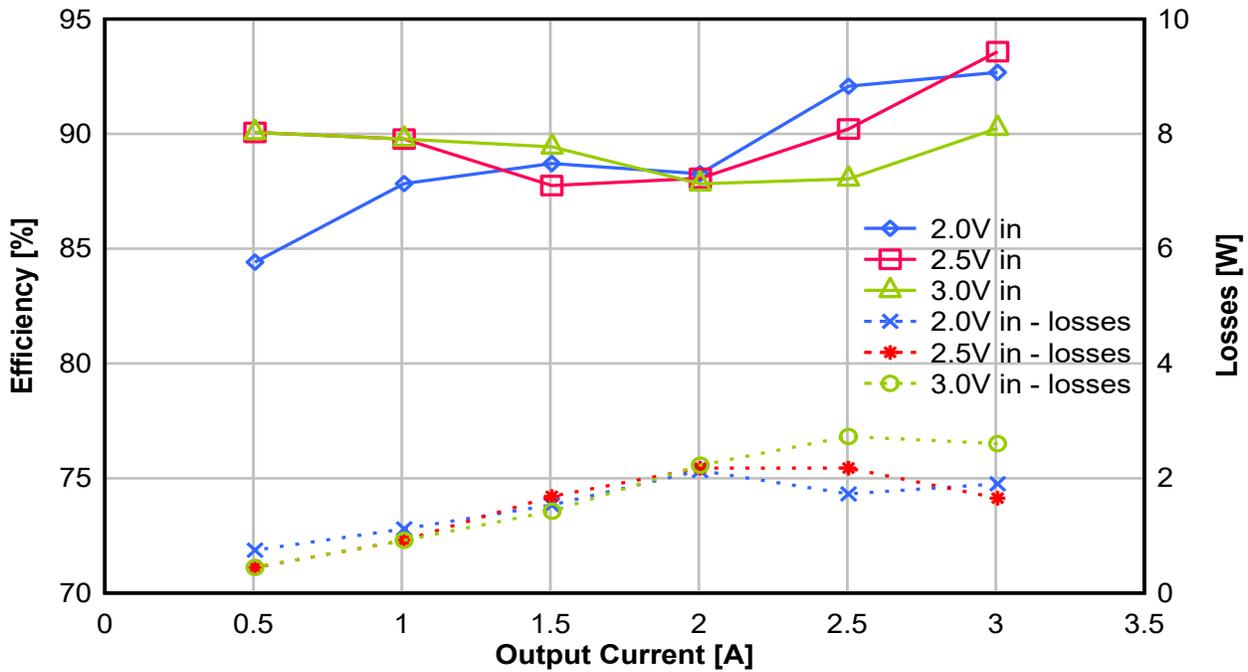


Figure 2-2. Efficiency and Losses vs Output Current from 2-V to 3-V Input Voltage

## 2.2 Load Regulation

### 2.2.1 One Low-Side FET, 680-nH Coil, 1.0 V<sub>IN</sub> – 1.5 V<sub>IN</sub>

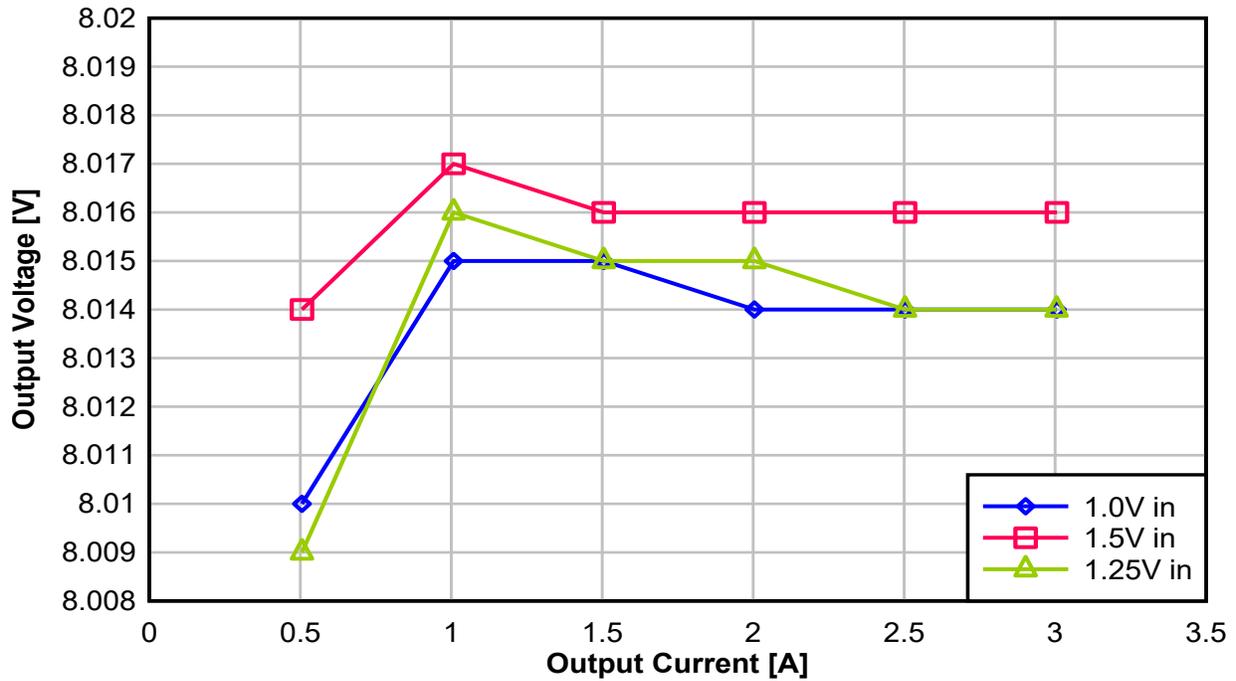


Figure 2-3. Load Regulation From 1-V to 1.5-V Input Voltage

### 2.2.2 One Low-Side FET, 680-nH Coil, 2.0 V<sub>IN</sub> – 3.0 V<sub>IN</sub>

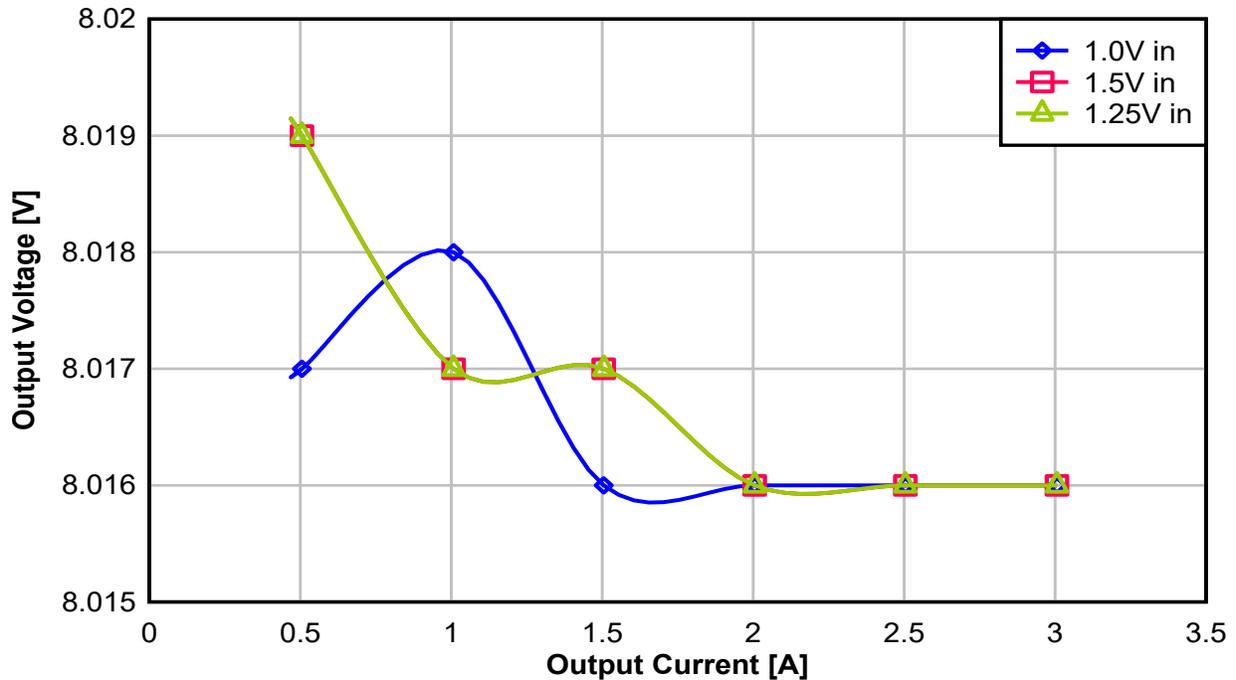


Figure 2-4. Load Regulation From 2-V to 3-V Input Voltage

## 2.3 Thermal Images

### 2.3.1 1.0-V Input Voltage – Full Load 3.0 A

#### 2.3.1.1 Two Low-Side FETs, 330-nH Coil

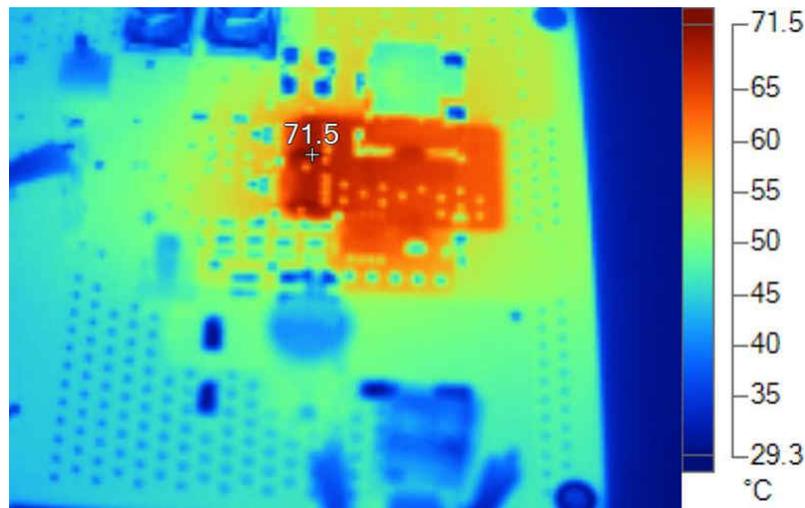


Figure 2-5. IR Photo for 1.0-V Input Voltage, 2 Low-Side FETs and 330-nH Coil

Name	Temperature
Q2, Q3	71.5°C

#### 2.3.1.2 One Low-Side FET, 680-nH Coil

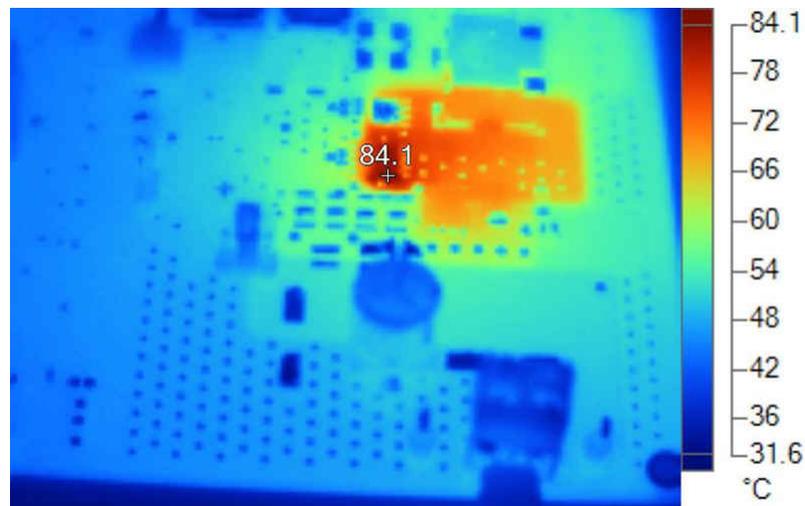


Figure 2-6. IR Photo for 1.0-V Input Voltage, One Low-Side FET and 680-nH Coil

Name	Temperature
Q2, Q3	84.1°C

### 2.3.2 2.0-V Input Voltage, Full Load 3.0 A

#### 2.3.2.1 Two Low-Side FETs, 330-nH Coil

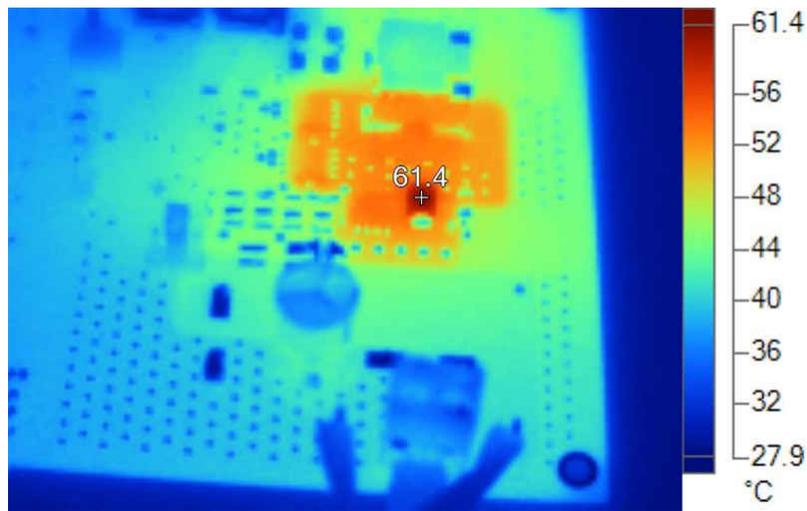


Figure 2-7. IR Photo for 2.0-V Input Voltage

Name	Temperature
D1	61.4°C

### 2.3.3 3.0-V Input Voltage, Full Load 3.0 A

#### 2.3.3.1 Two Low-Side FETs, 330-nH Coil

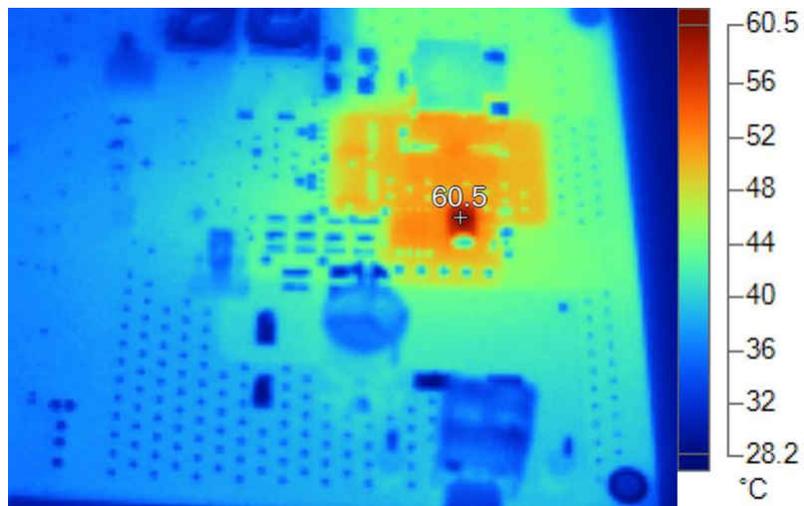


Figure 2-8. IR Photo for 3.0-V Input Voltage

Name	Temperature
D1	60.5°C


## 2.4 Bode Plots

This section includes a summary of the bode plots in Table 2-1 and Figure 2-9 through Figure 2-11 illustrate the bode plots at various input voltages.

**Table 2-1. Summary of the Bode Plots**

	1.0 V <sub>IN</sub>	2.0 V <sub>IN</sub>	3.0 V <sub>IN</sub>
Bandwidth (Hz)	524	1224	1030
Phase Margin	81.66	88.3	92,8
Slope (20 dB/decade)	-0.962	-1.05	-1.03
Gain margin (dB)	-15.37	-34	-35.6
Slope (20 dB/decade)	-0.468	-6.93	-6.6
Frequency (kHz)	4.4kHz	30.5	30.02

### 2.4.1 1.0-V Input Voltage

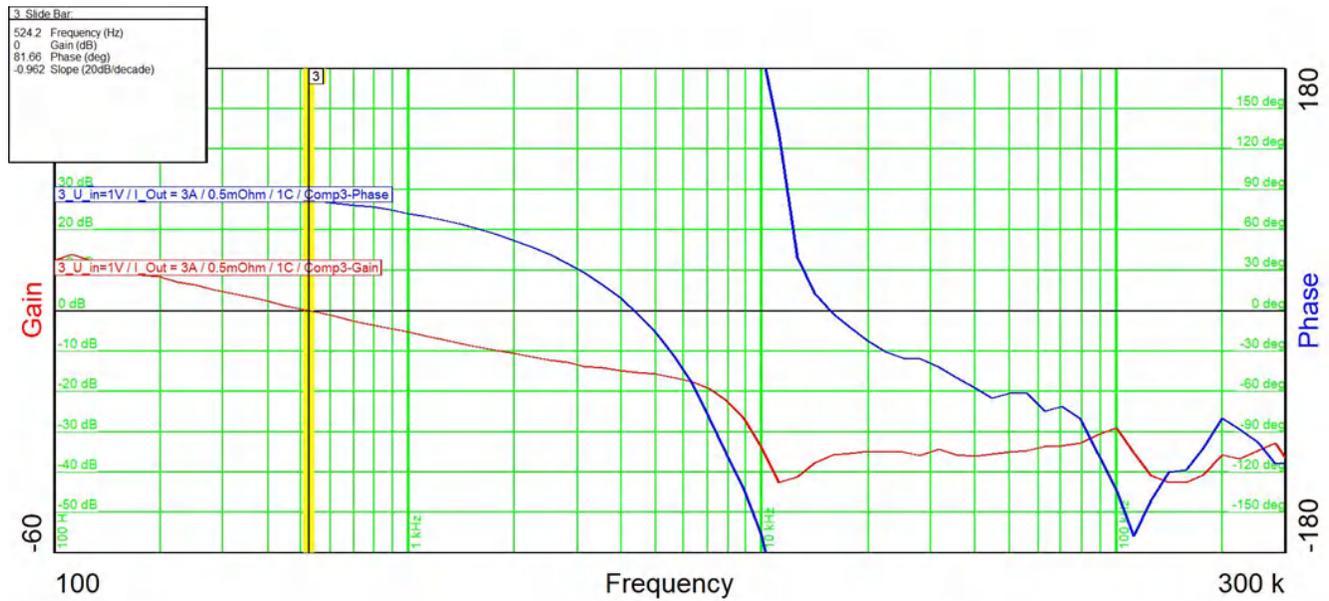

**Figure 2-9. Bode Plot for 1.0-V Input Voltage**

### 2.4.2 2.0-V Input Voltage

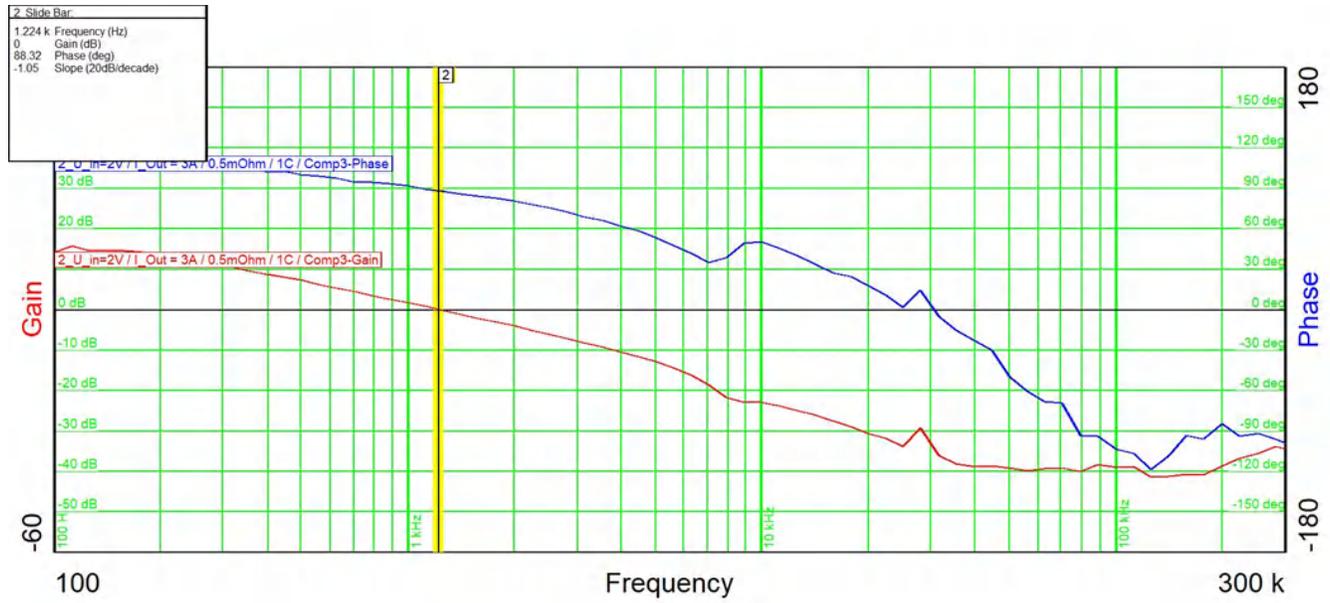


Figure 2-10. Bode Plot for 2.0-V Input Voltage

### 2.4.3 3.0-V Input Voltage

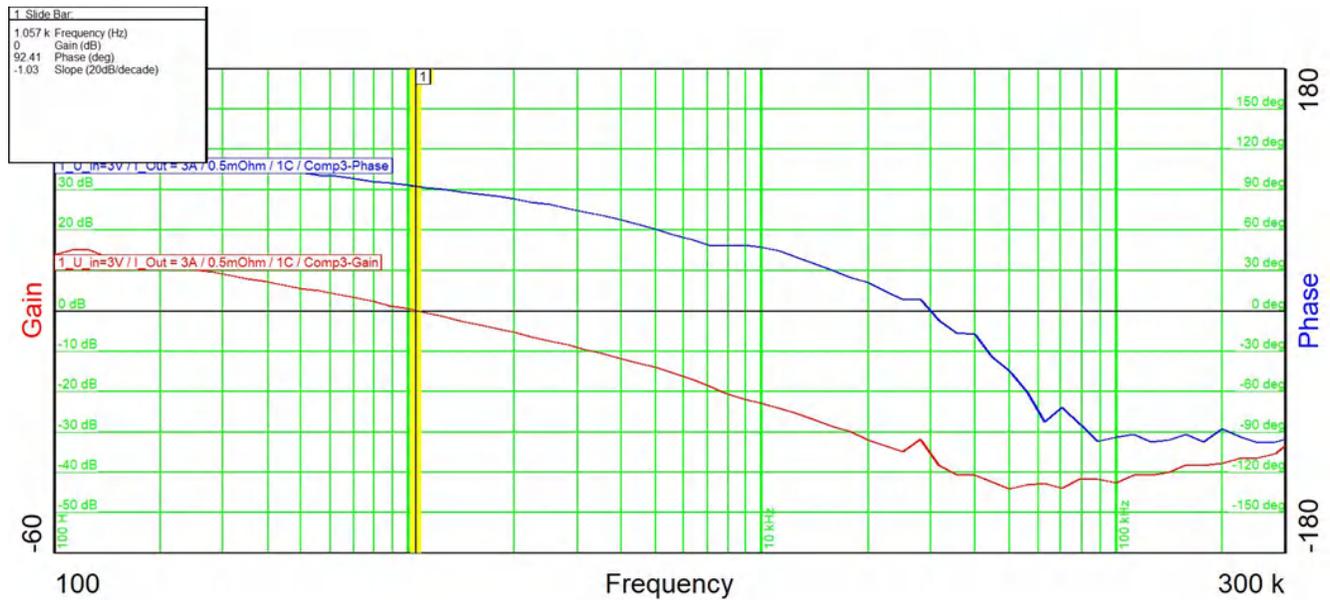


Figure 2-11. Bode Plot for 3.0-V Input Voltage

### 3 Waveforms

#### 3.1 Switching Q2 FET (Drain to Source)

##### 3.1.1 1.0-V Input Voltage

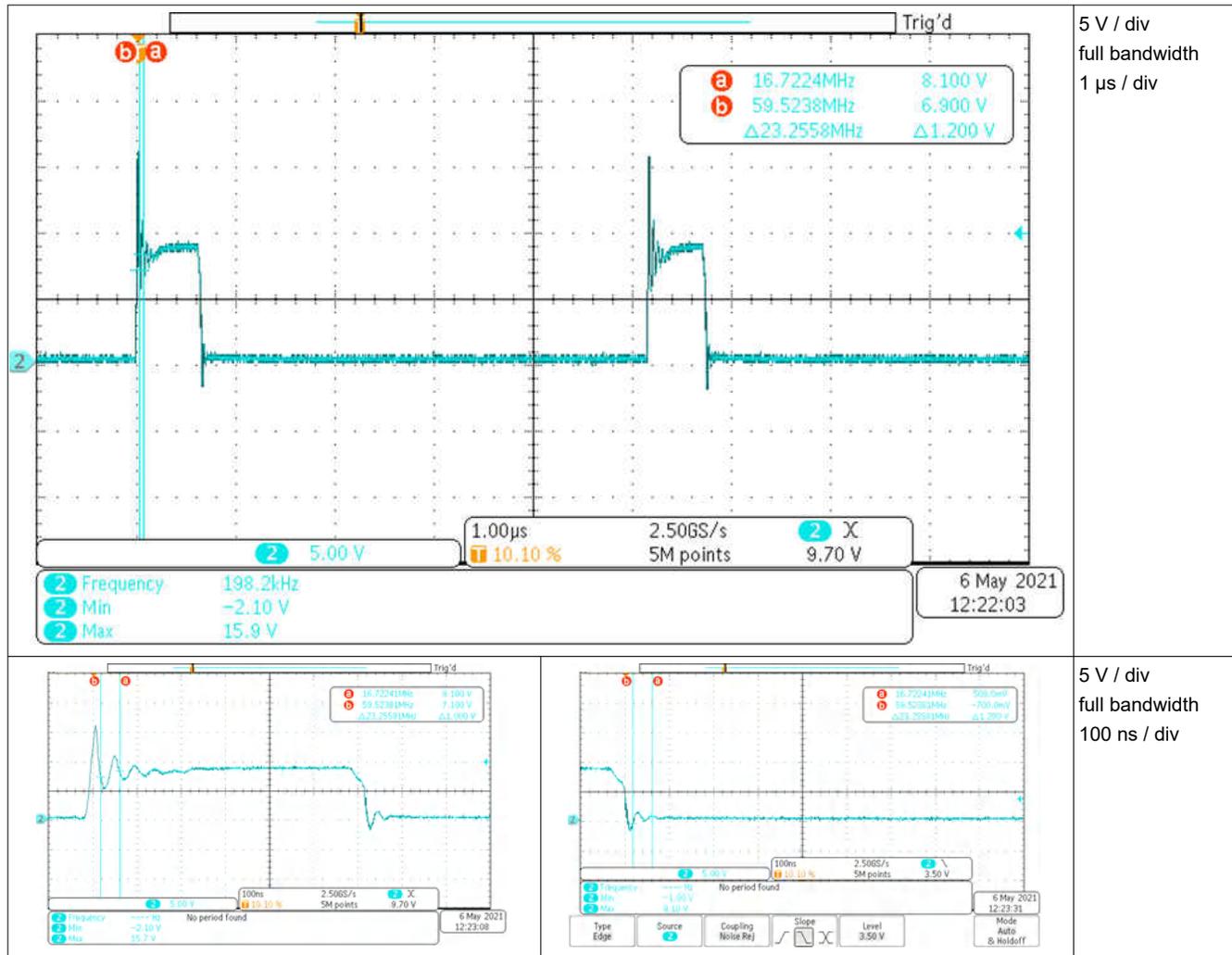


Figure 3-1. Switching Node Q2 at 1.0-V Input Voltage

### 3.1.2 3.0-V Input Voltage

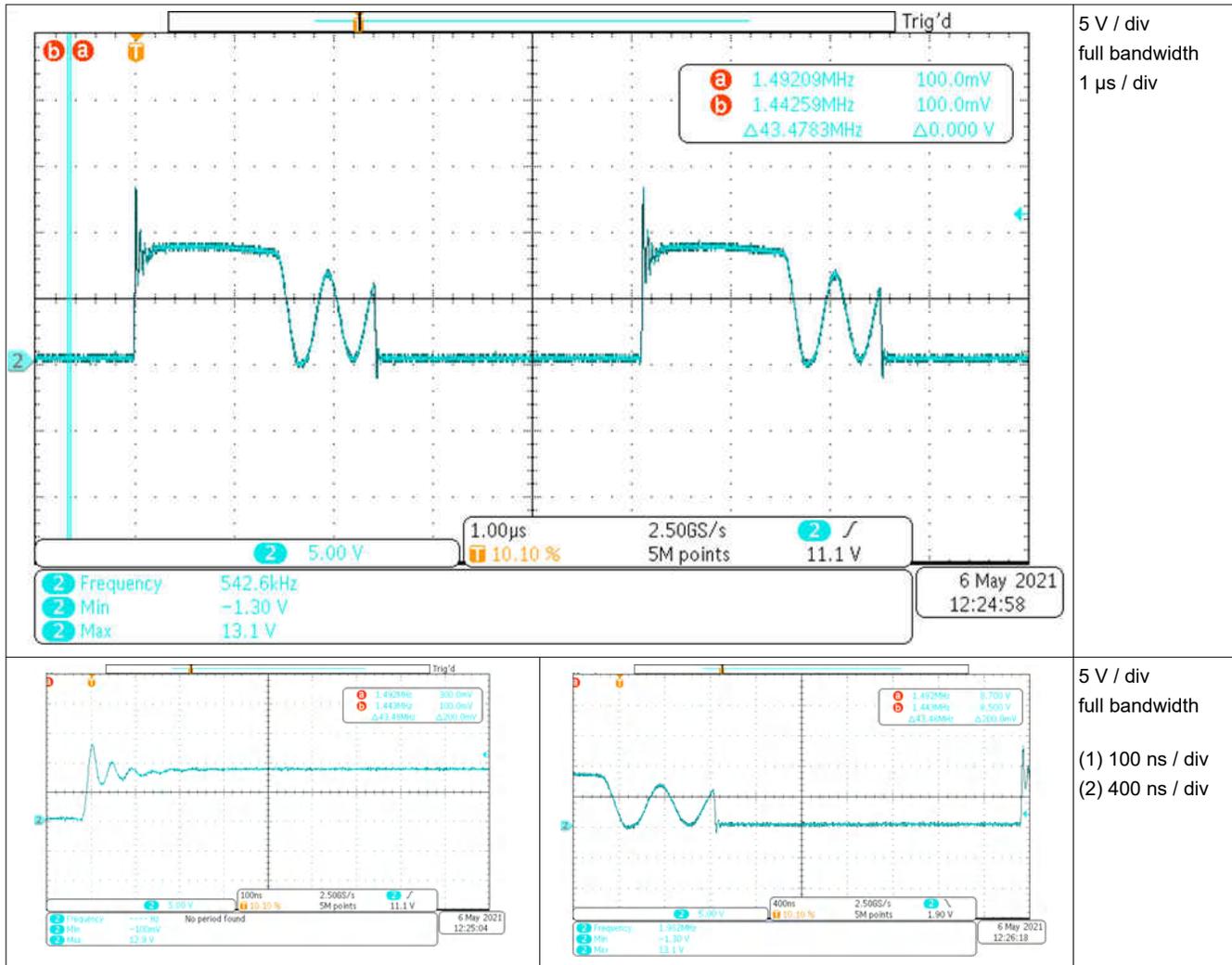


Figure 3-2. Switching Node Q2 at 3.0-V Input Voltage

### 3.2 Output Voltage Ripple

#### 3.2.1 1.0-V Input Voltage

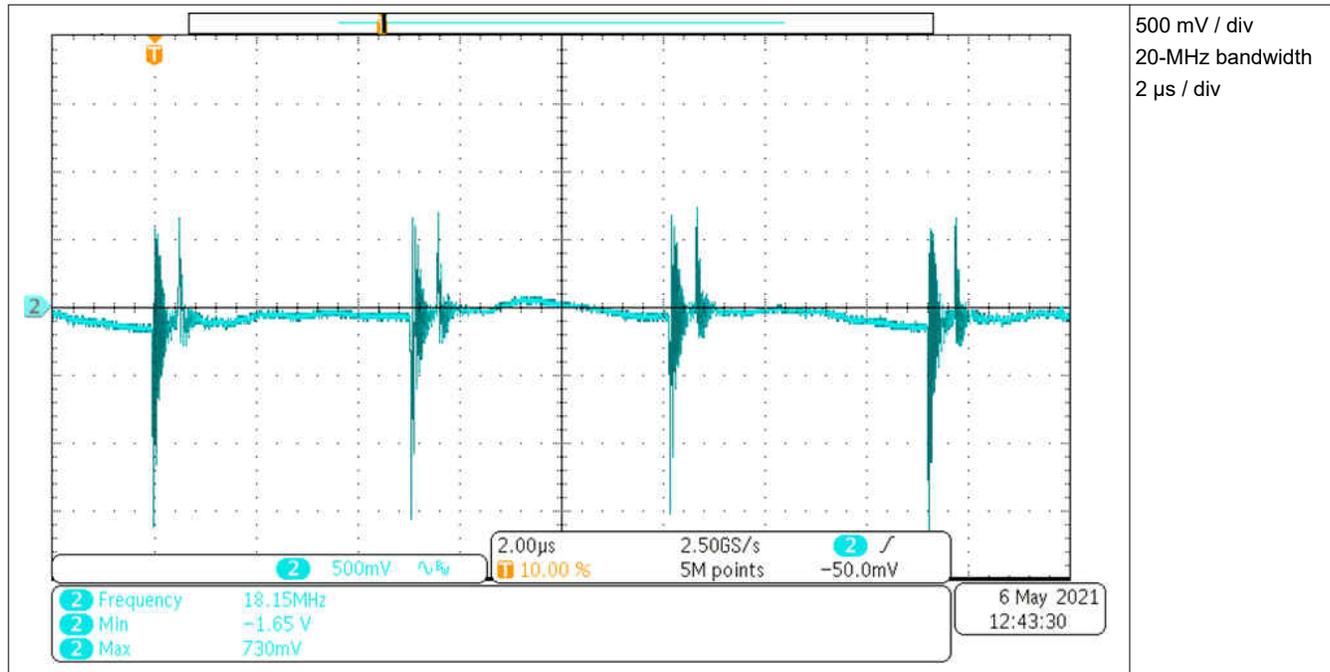


Figure 3-3. Output Voltage Ripple (1.0-V Input Voltage)

#### 3.2.2 3.0-V Input Voltage

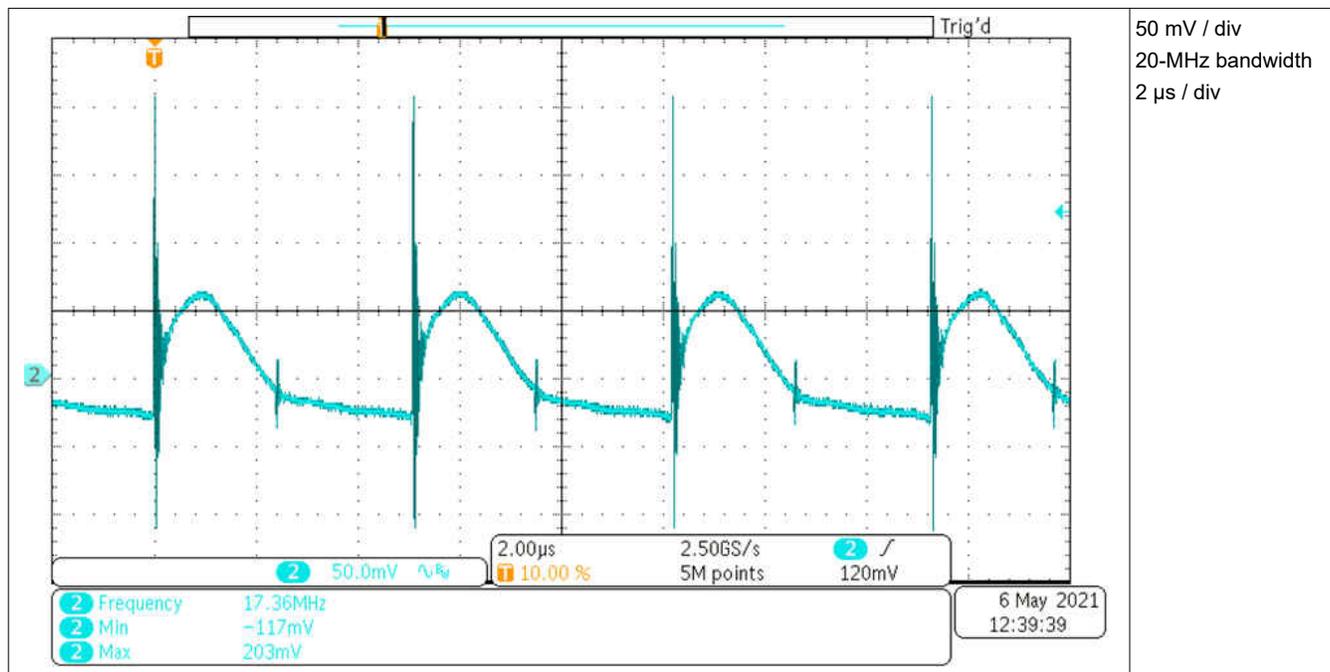


Figure 3-4. Output Voltage Ripple (3.0-V Input Voltage)

### 3.3 Input Voltage Ripple

#### 3.3.1 1.0-V Input Voltage

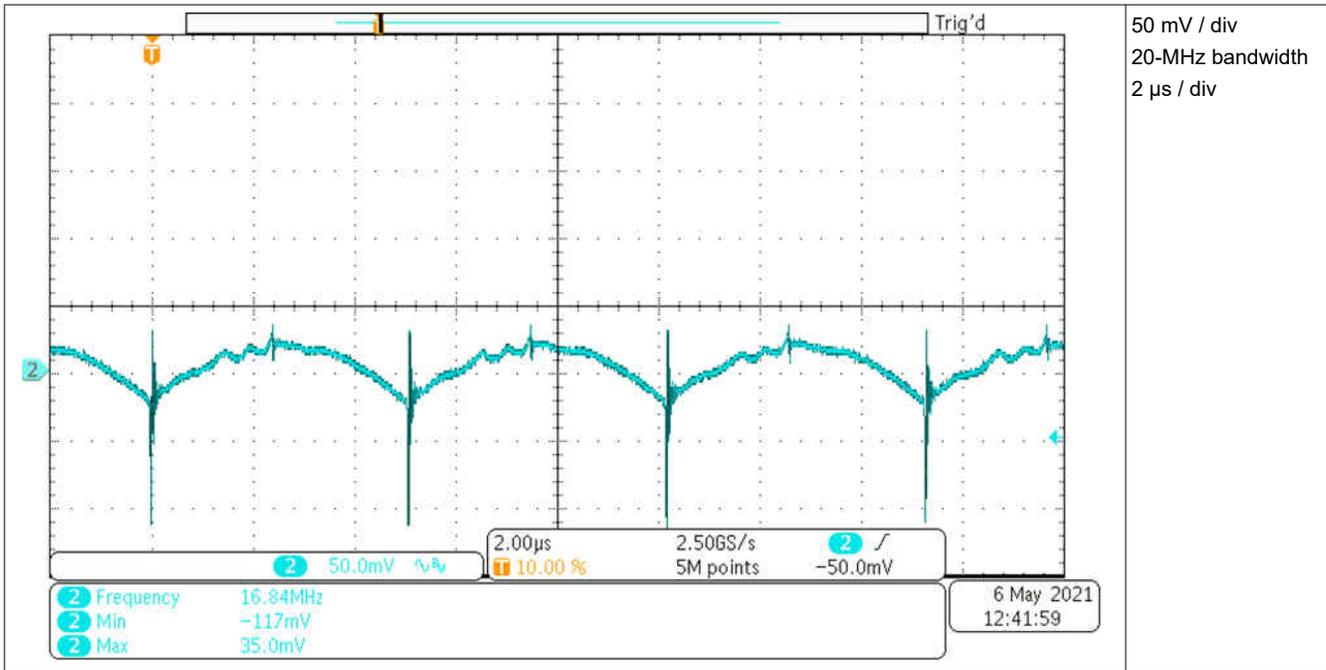


Figure 3-5. Input Voltage Ripple (1.0-V Input Voltage)

#### 3.3.2 3.0-V Input Voltage

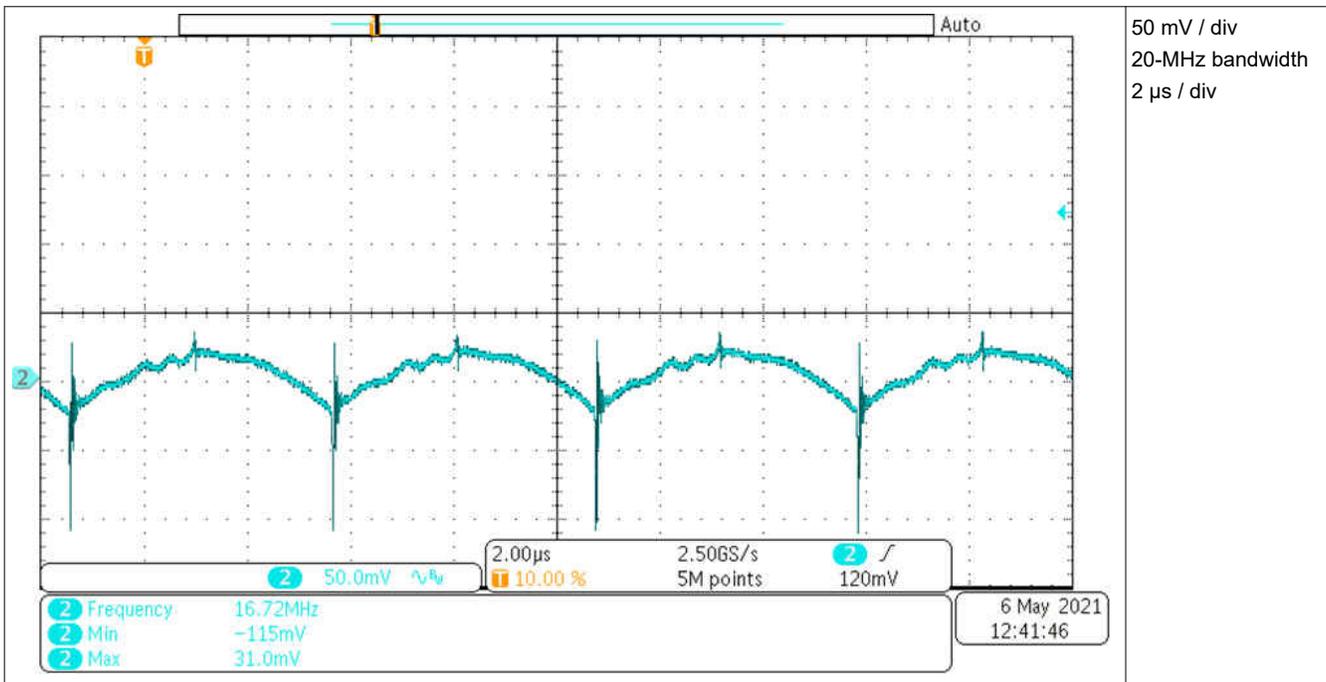


Figure 3-6. Input Voltage Ripple (3.0-V Input Voltage)

### 3.4 Load Transients

#### 3.4.1 Load Steps of 1.5 A to 3 A

Electronic load was used to create the load steps of 1.5 A to 3.0 A (30 Hz).

##### 3.4.1.1 1.0-V Input Voltage

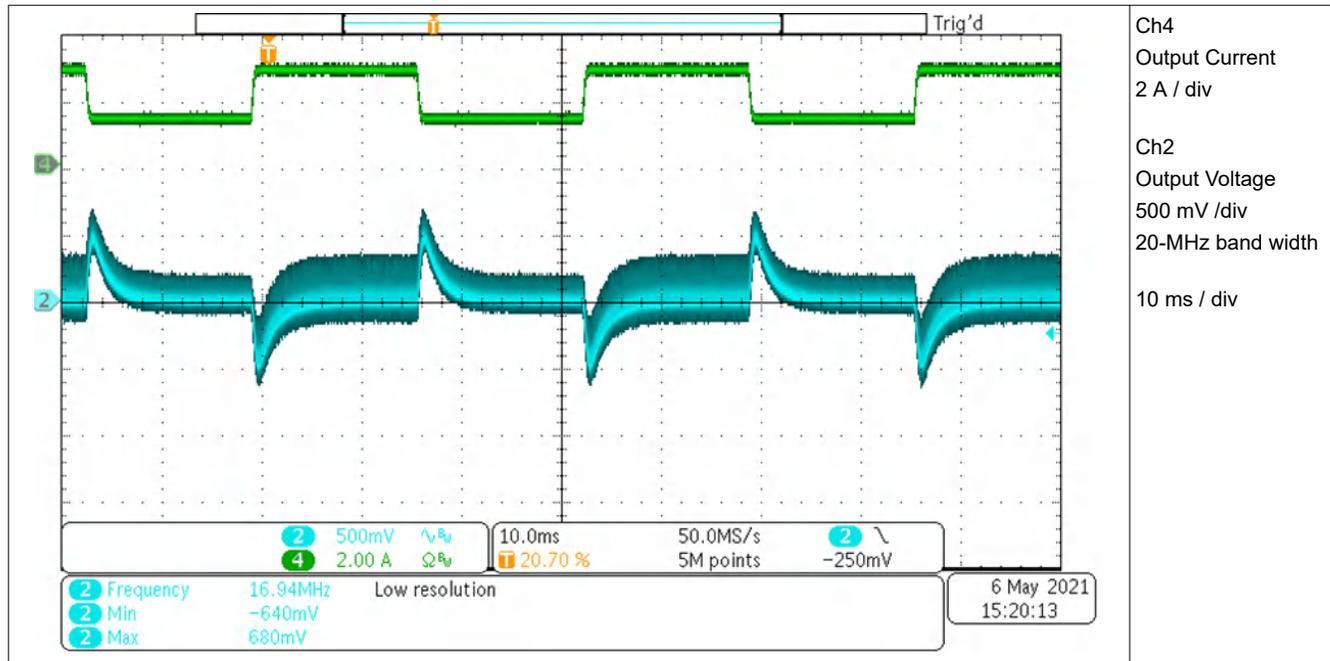


Figure 3-7. 1.5-A to 3-A Load Transient With 1.0-V Input Voltage

##### 3.4.1.2 3.0-V Input Voltage

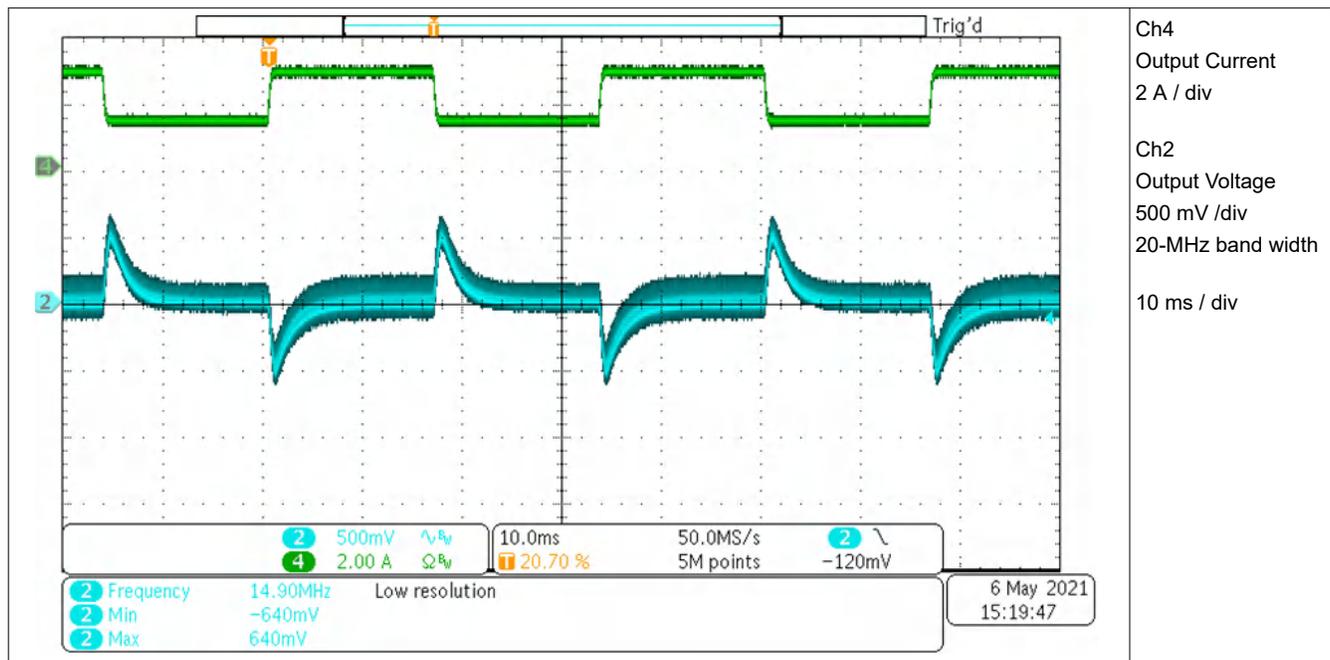


Figure 3-8. 1.5-A to 3-A Load Transient With 3.0-V Input Voltage

### 3.4.2 Load Steps of 0.2 A to 3 A

Electronic load has been used to create the load steps of 0.2 A to 3.0 A (30 Hz).

#### 3.4.2.1 1.0-V Input Voltage

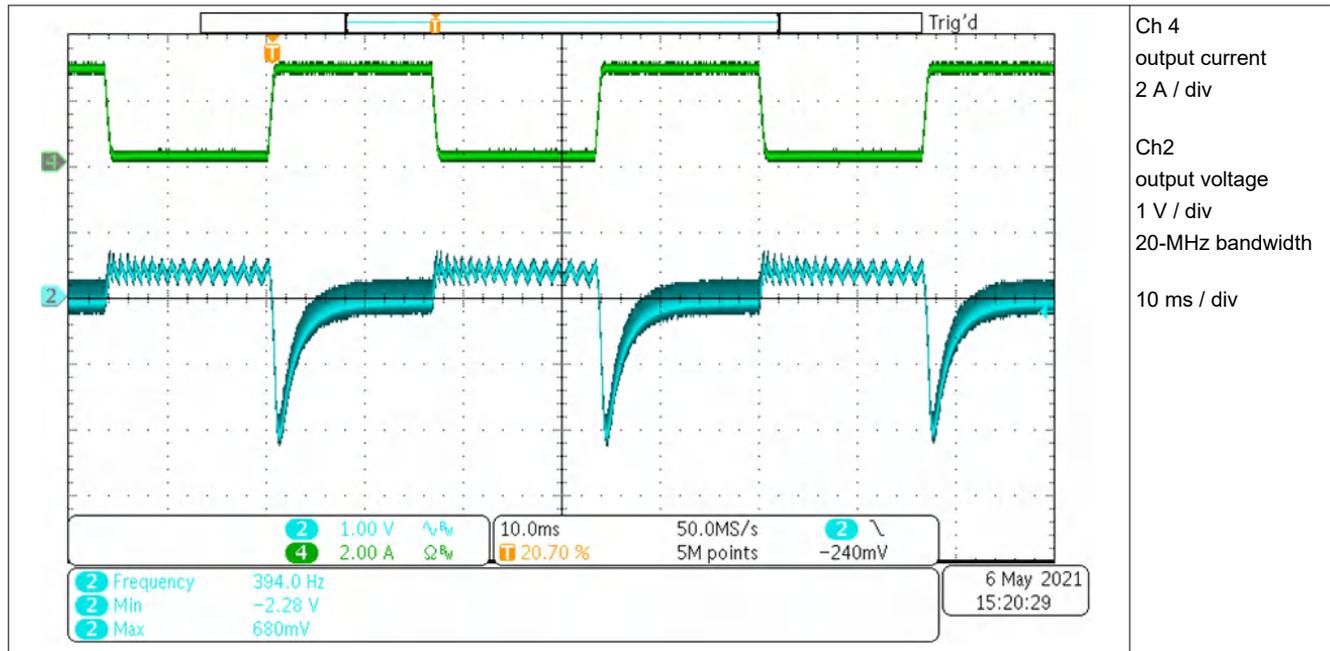


Figure 3-9. 0.2-A to 3-A Load Transient With 1.0-V Input Voltage

#### 3.4.2.2 3.0-V Input Voltage

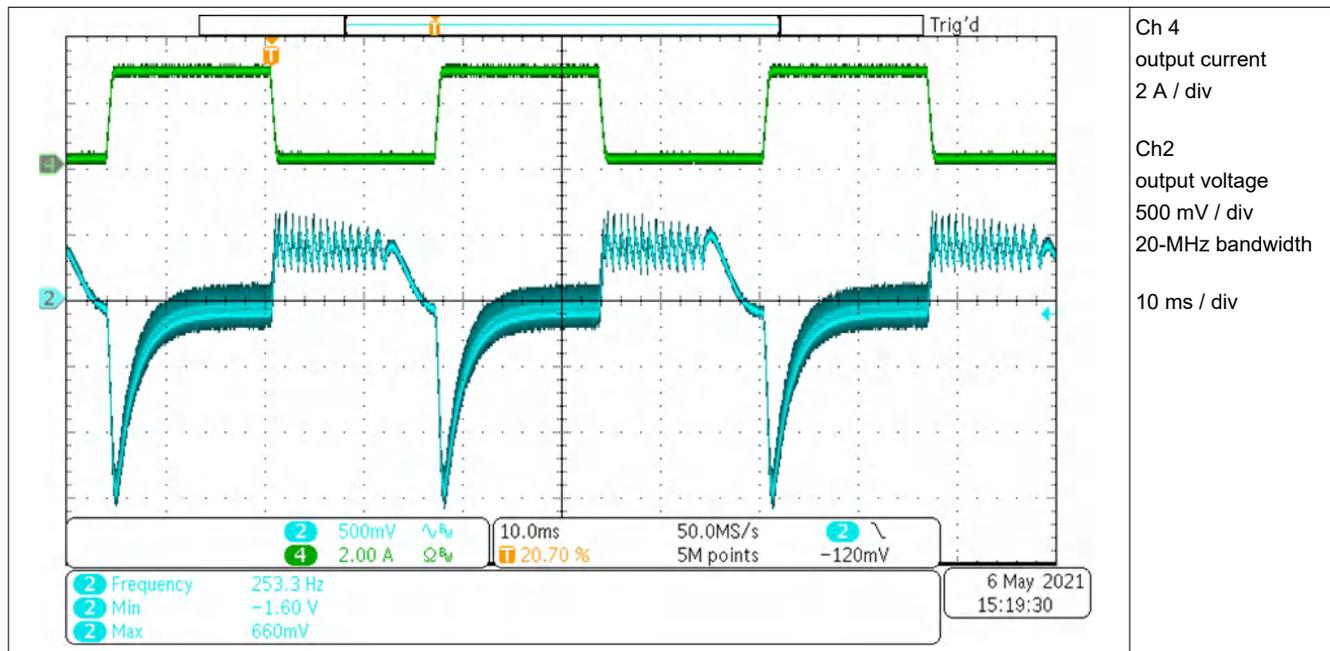


Figure 3-10. 0.2-A to 3-A Load Transient With 3.0-V Input Voltage

### 3.5 Start-Up Sequence

#### 3.5.1 1.0-V Input Voltage

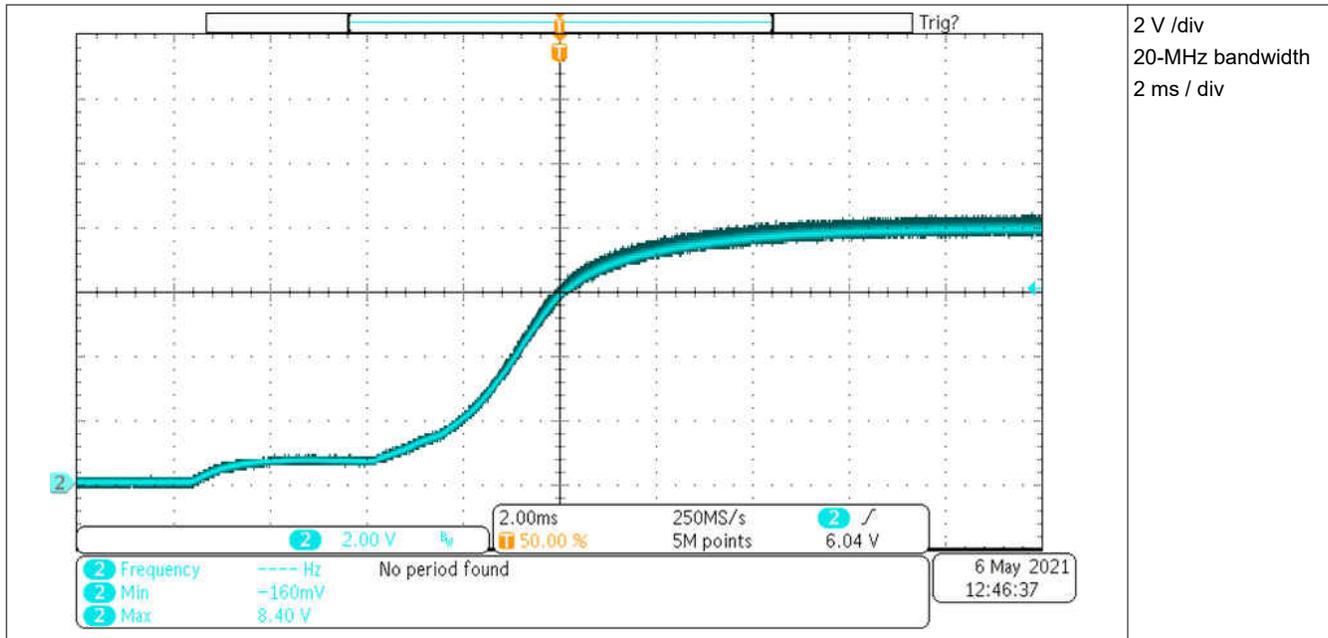


Figure 3-11. Start-Up With 1.0-V Input Voltage

#### 3.5.2 3.0-V Input Voltage

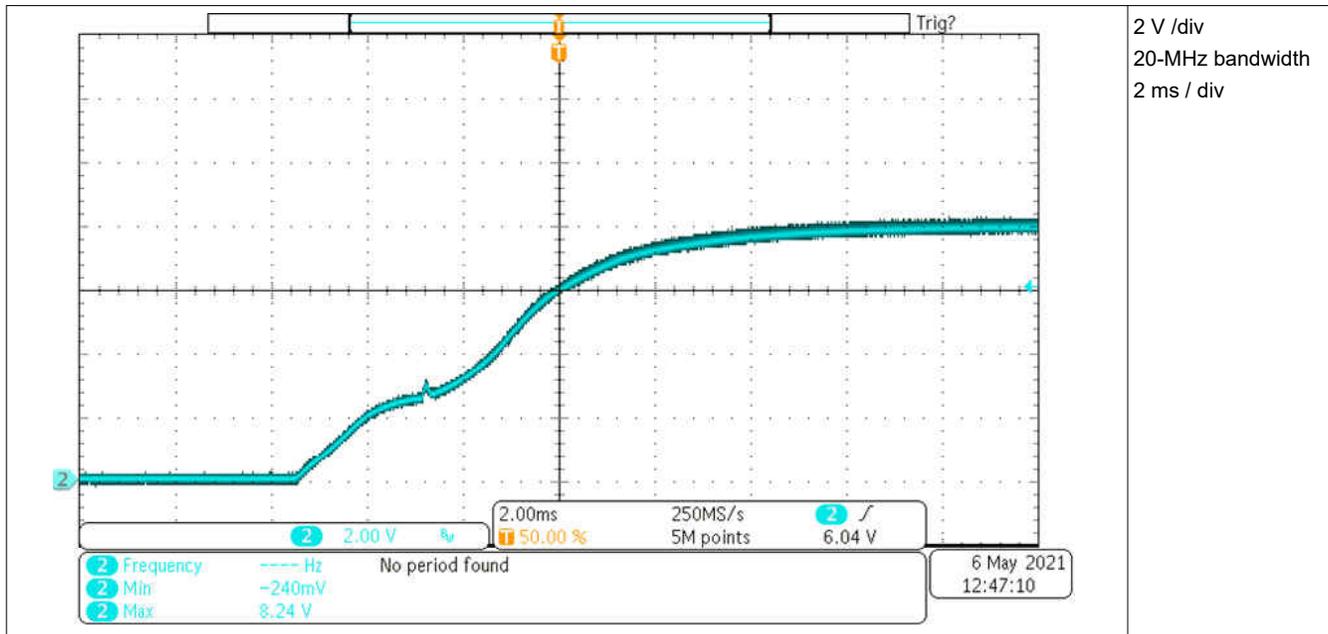


Figure 3-12. Start-Up With 3.0-V Input Voltage

### 3.6 Shutdown Sequence

#### 3.6.1 1.0-V Input Voltage

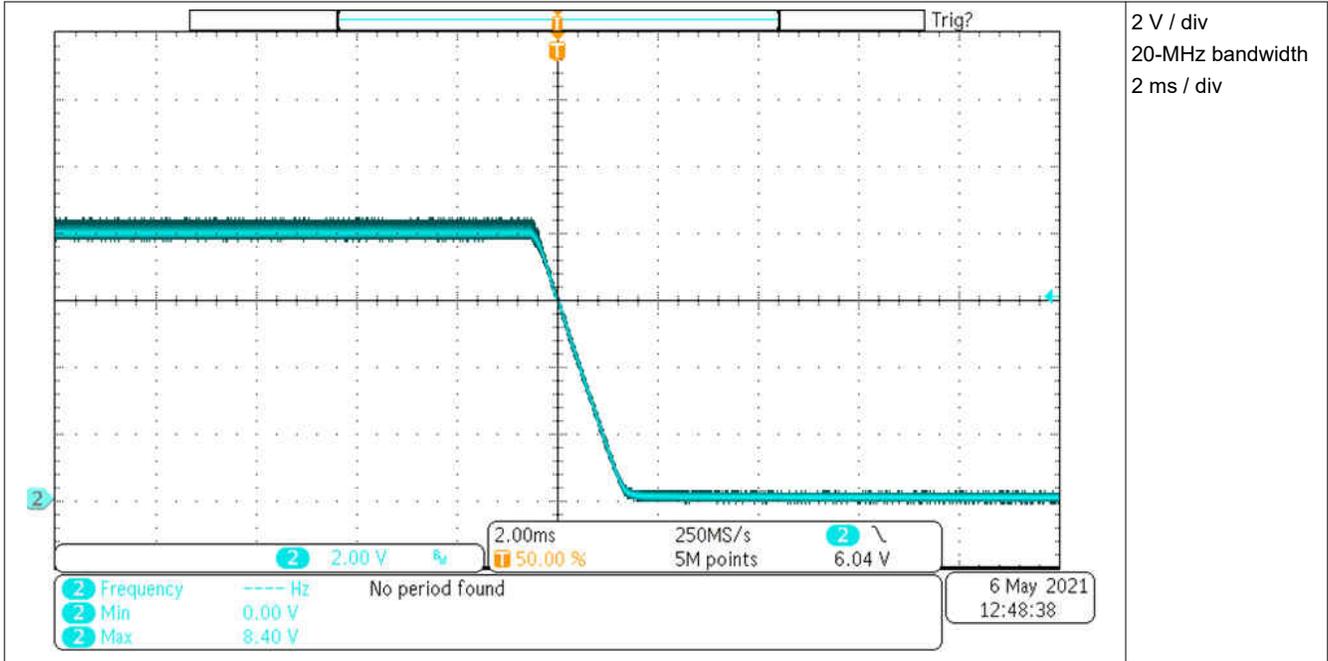


Figure 3-13. Shutdown With 1.0-V Input Voltage

#### 3.6.2 3.0-V Input Voltage

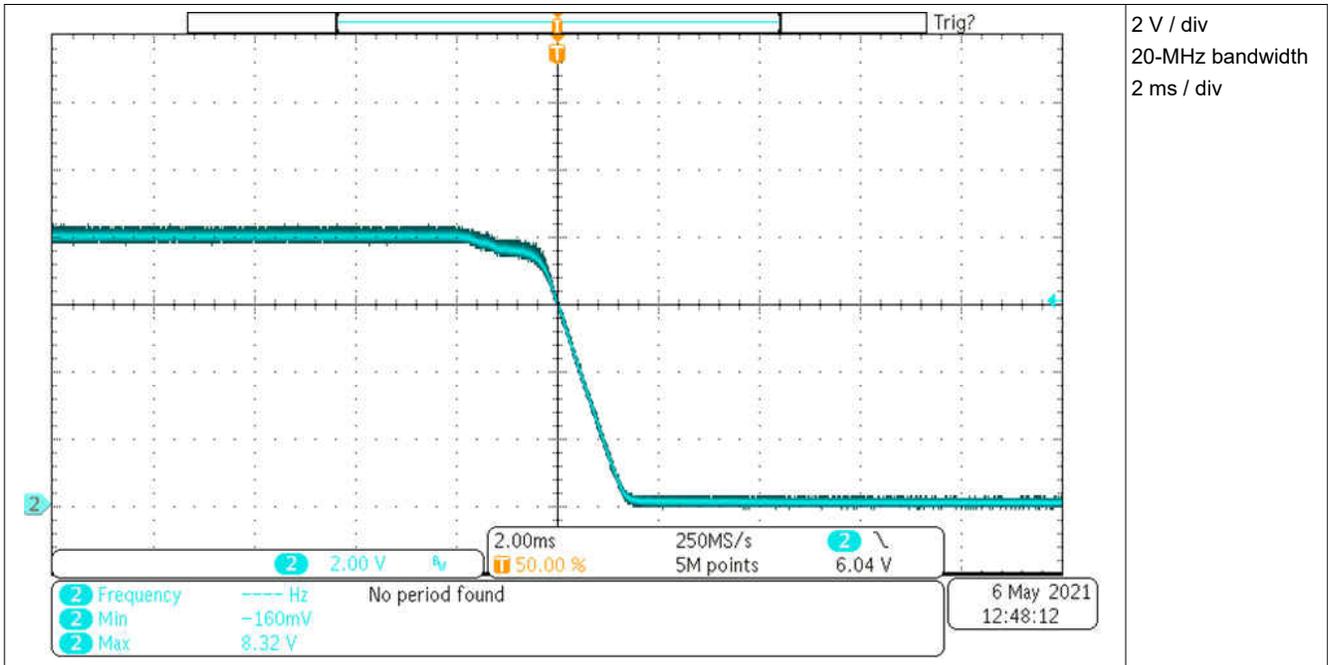


Figure 3-14. Shutdown With 3.0-V Input Voltage

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated