

SEPIC Reference Design Fitting for Battery Chargers



Description

This reference design shows the use of a Buck-Boost capability of a single-ended primary-inductor converter (SEPIC) converter. Since the input and output are separated by a capacitor, this topology can be used to charge a battery with variable V_{IN} as well as variable V_{OUT} . A synchronous peak-current mode controller LM5122 is employed; this IC can drive the high-side sync-FET by means of level shift (RCD network). By applying 9-V to 36-V input, this board can be used to charge two batteries in series with a voltage range of 8 V to 28 V, up to 2-A charging current, or simply used as standard constant-voltage power supply. Both setpoints of output voltage and current are defined by means of two trimmers, even though both references can also be replaced by employing two digital-to-analog converters.

Features

- Can be used as battery charger or standard power supply
- Synchronous SEPIC topology with external high-side field-effect transistors (FETs) and low-side FETs
- Constant charging current: adjustable in the range 0 A to 2 A
- Constant supply voltage : adjustable in the range 8 V to 28 V
- $\pm 2\%$ charging voltage accuracy and $\pm 2.5\%$ charging current accuracy
- Selectable Forced PWM Mode or Diode Emulation Mode for efficiency improvement at light load

Applications

- Appliances: battery charger



Top of Board



Bottom of Board



Angled View of Board

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

Parameter	Specifications
Input Voltage Range	9 V to 36 V
Output Voltage	8 V to 28 V (24 V nominal)
Maximum Output Current	2 A (adjustable)
IC	LM5122
Topology	SEPIC

1.2 Required Equipment

The following equipment is required for testing this design:

- Bench power supply with output voltage range 0–36 V, current limit up to 10 A
- Electronic load 0–30 V, 0–3 A, settable in constant-current and constant-voltage regulation

1.3 Dimensions

The size of the board is 104.1 mm × 73.2 mm. The board was manufactured with 4 copper layers. The outer layers are 70 μm and the inner layers are 35-μm copper thickness.

1.4 Test Setup

To avoid mistakes that can lead to unwanted behavior of this SEPIC charger (like setting a current limit threshold on this board less than the constant-current sink set to your electronic load), please observe the following procedure during testing:

1. Supply the board with the bench PSU (V_{IN}) on J1 (pin 1 positive)
2. Connect a constant current load to the output on J2 (positive on pin 2)
3. **If this power supply is used as standard PSU (therefore not charging a battery)** set “Mode select” on J3 by placing a jumper between pins 1 and 2 (Forced PWM)
4. **Please use “diode emulation mode” as the battery charger**
5. Set the constant current setpoint (I_{LOAD}) of the load to 0.1 A
6. Set V_{IN} to 24 V and the current limit to 1 A
7. Turn on V_{IN} and check the output voltage
8. Rotate the trimmer R22 (V_{OUT} Adjust) so that V_{OUT} is 26 V
9. If the output voltage does not reach 26 V, then R30 is set to very low current; in this case rotate R30 until V_{OUT} increases. As V_{OUT} increases, then rotate R22 to reach 26 V
10. Now increase the current limit of the bench PSU V_{in} to 8 A
11. Change the electronic load into “constant voltage” and set the voltage at 24 V
12. At this point the output current is dependent on the position of R30, while V_{OUT} is fixed by the load to 24 V
13. Now rotate R30 until the output current is 2 A
14. Start measuring the standard parameters as desired, versus output current
15. **Please remember that if you are using this charger with a battery, the converter must be set in “diode emulation mode” by moving the jumper over J3 from pins 1-2 to 2-3; in this case keep the diode emulation mode always on**

2 Testing and Results

2.1 Efficiency Graph

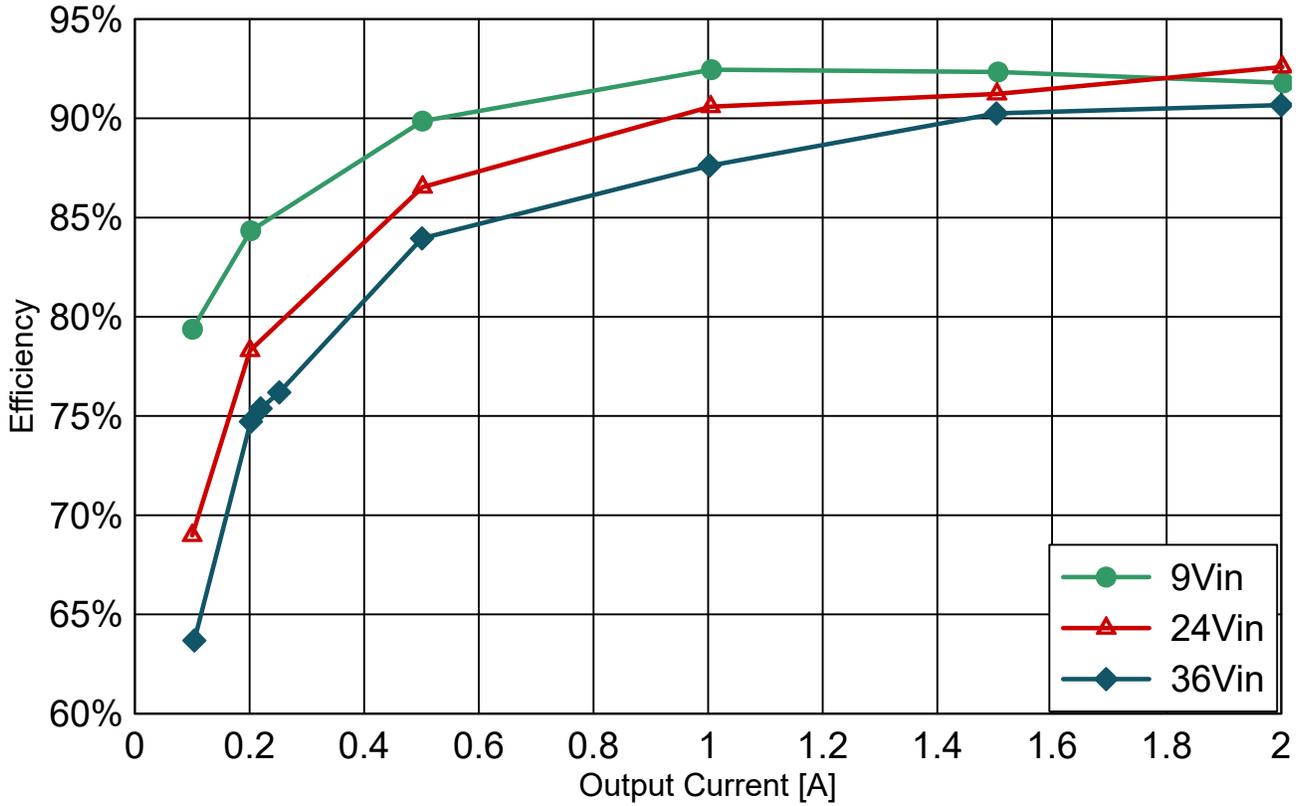


Figure 2-1. Efficiency Graph

2.2 Thermal Images

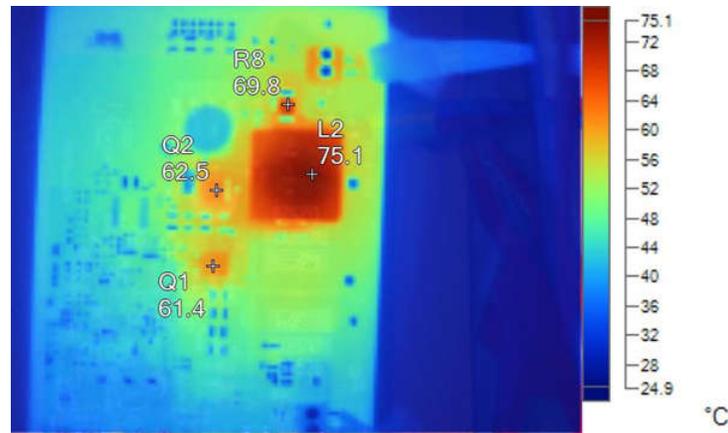


Figure 2-2. Thermal Image (9-V Input voltage, 24-V Output Voltage, 2-A Output Current)

Temperature Values

Name	Temperature
L2	75.1°C
Q1	61.4°C
Q2	62.5°C
R8	69.8°C

2.3 Bode Plots

2.3.1 Bode Plot With Battery

Three different bode plot measurements were taken. This first one refers to a connection of two 12-V valve regulated lead–acid (VRLA) batteries in series, model Yuasa NPH5-12 (12 V, 5 Ah).

2.3.1.1 Bode Plot With Battery During Recharging Phase (Constant Current)

For this measurement the battery did not reach the charge voltage; therefore, the SEPIC converter runs in constant-current mode. V_{IN} was set to 15 V, 18 V, and 26 V. Charge current is 1 A, while the battery voltage was 25 V. The line with dots in Figure 2-3 refers to $V_{IN} = 24$ V

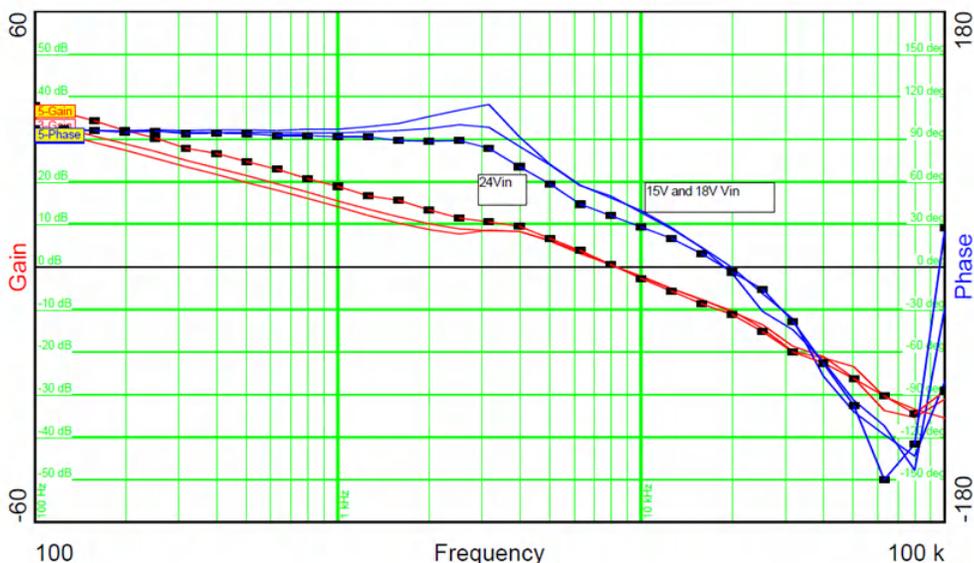


Figure 2-3. Bode Plot With Battery During Recharging Phase

2.3.1.2 Bode Plot With Battery at Constant Battery Voltage

Figure 2-4 shows where the battery reached the charge voltage set point; in this case the SEPIC converter runs in constant-voltage mode. V_{IN} was set to 24 V, V_{OUT} to 26 V (on the charger) and the charge current is 0.8 A

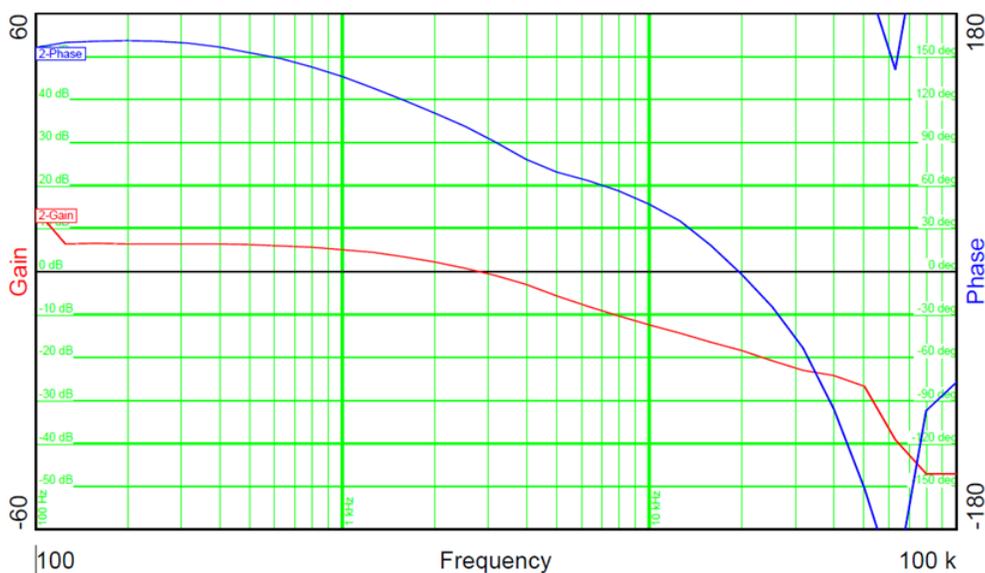


Figure 2-4. Bode Plot With Battery at Constant Battery Voltage

2.3.2 Bode Plot With Electronic Load

For this measurement the electronic load has been set to constant-current at 800 mA. V_{IN} was set to 24 V and V_{OUT} to 26 V (on the charger).

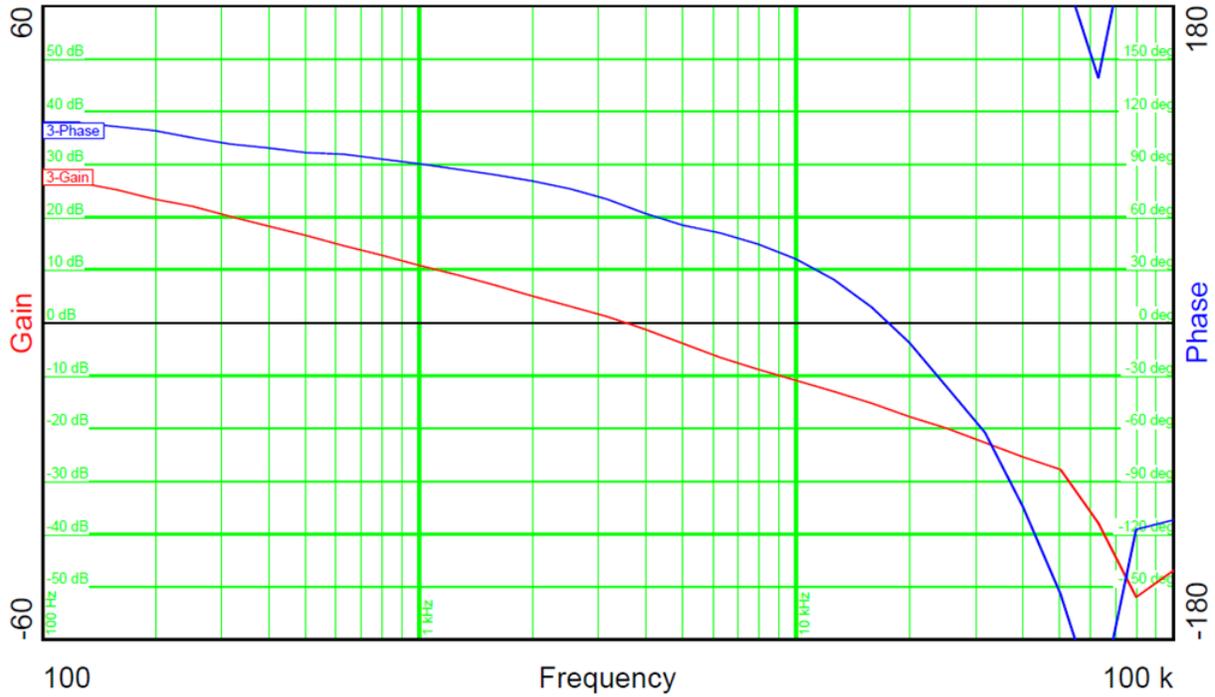


Figure 2-5. Bode Plot With Electronic Load

3 Waveforms

3.1 Switching

The measurements were done at 2-A output current and 24-V output voltage. The electronic load works in constant voltage mode.

3.1.1 Transistor Q2 Drain to Source

3.1.1.1 9-V Input Voltage

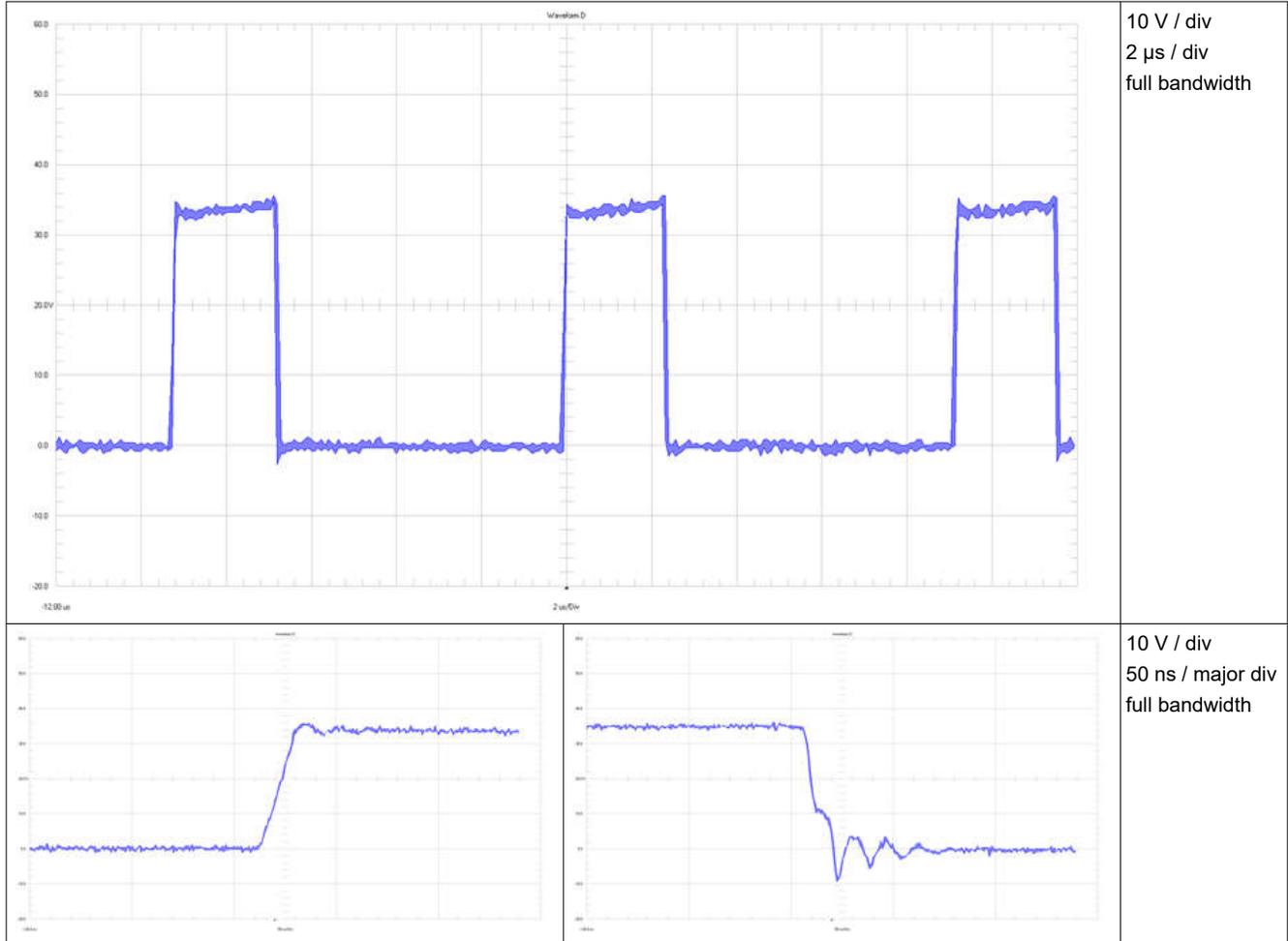


Figure 3-1. Switching Q2 at 9-V Input Voltage

3.1.1.2 36-V Input Voltage

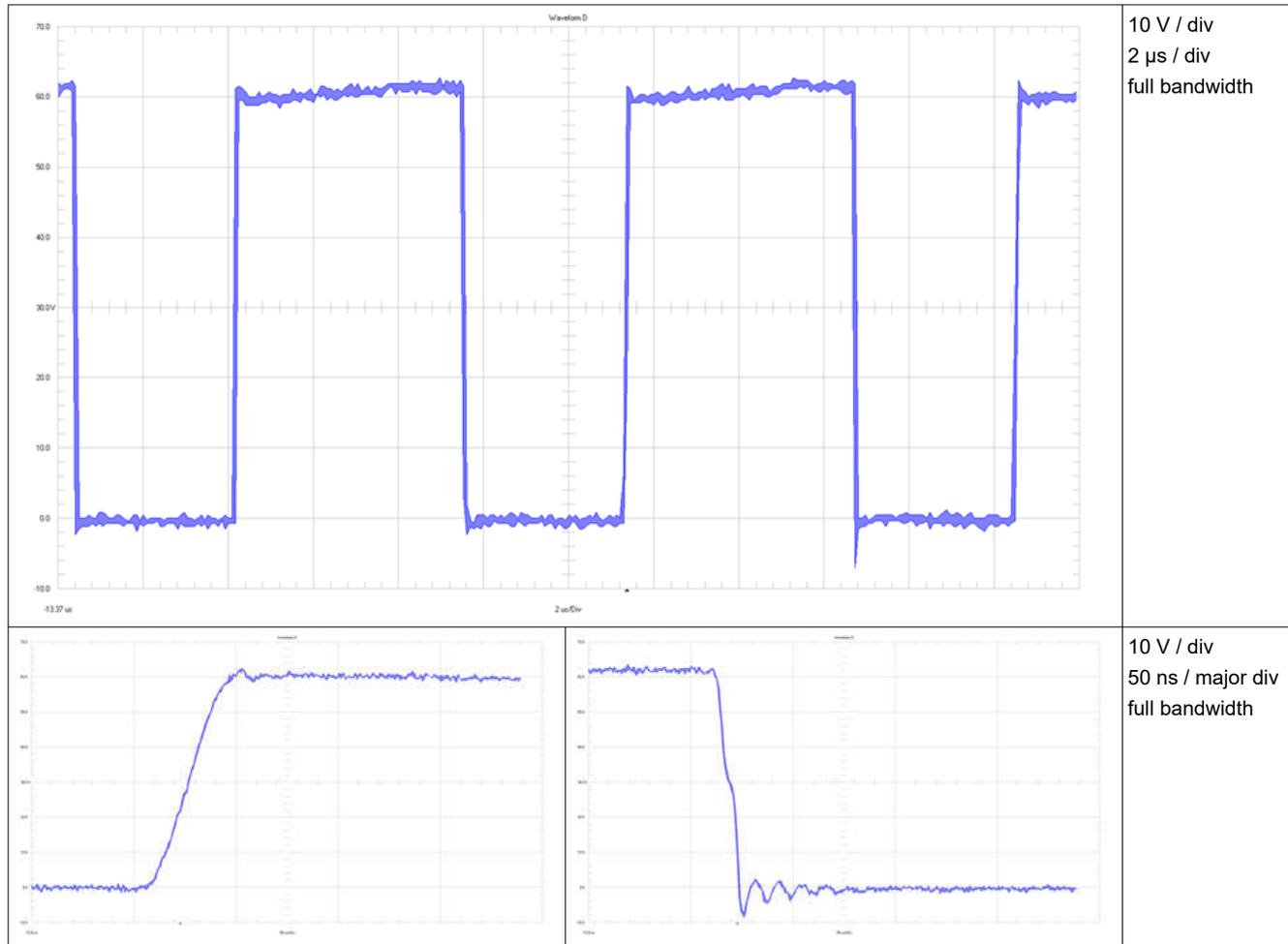


Figure 3-2. Switching Q2 at 36-V Input Voltage

3.1.2 Transistor Q1 Source to Drain

Note

On the falling edge the first overshoot is more than 80 V. The FET is rated for 80 V. Please introduce a snubber circuit or use a FET with a higher voltage rating.

3.1.2.1 9-V Input Voltage

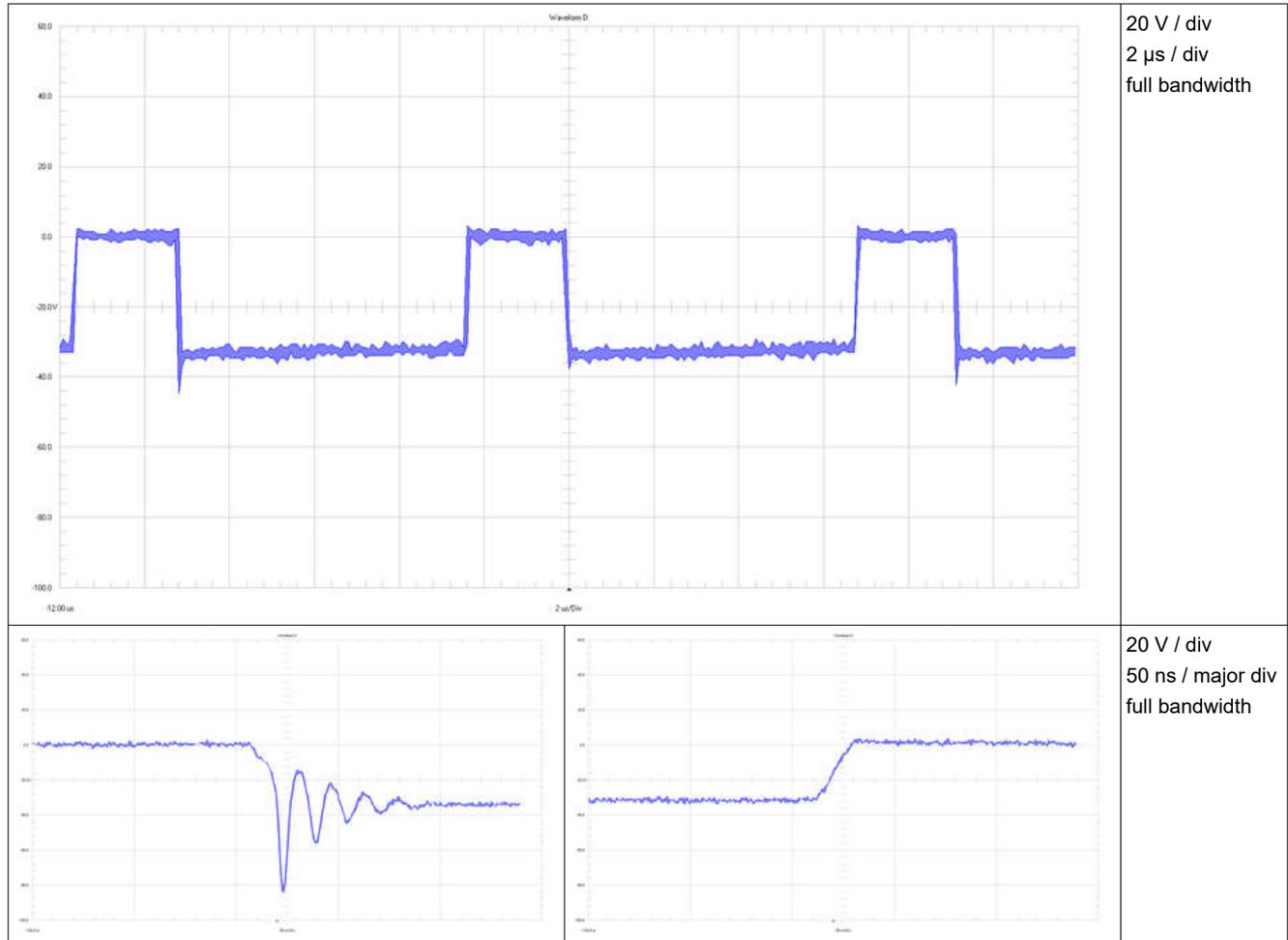


Figure 3-3. Switching Q1 at 9-V Input Voltage

3.1.2.2 36-V Input Voltage

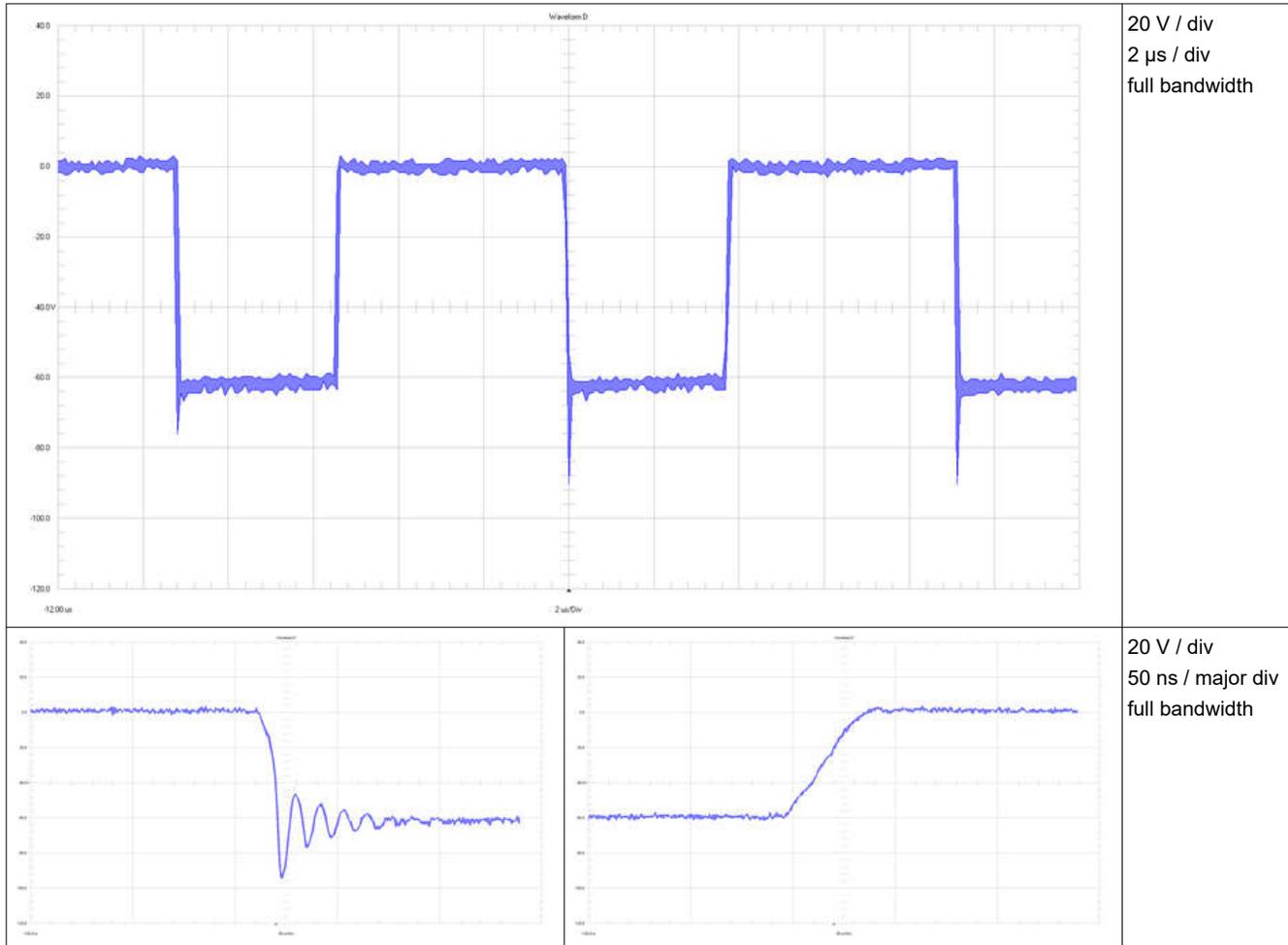


Figure 3-4. Switching Q1 at 36-V Input Voltage

3.2 Output Voltage Ripple

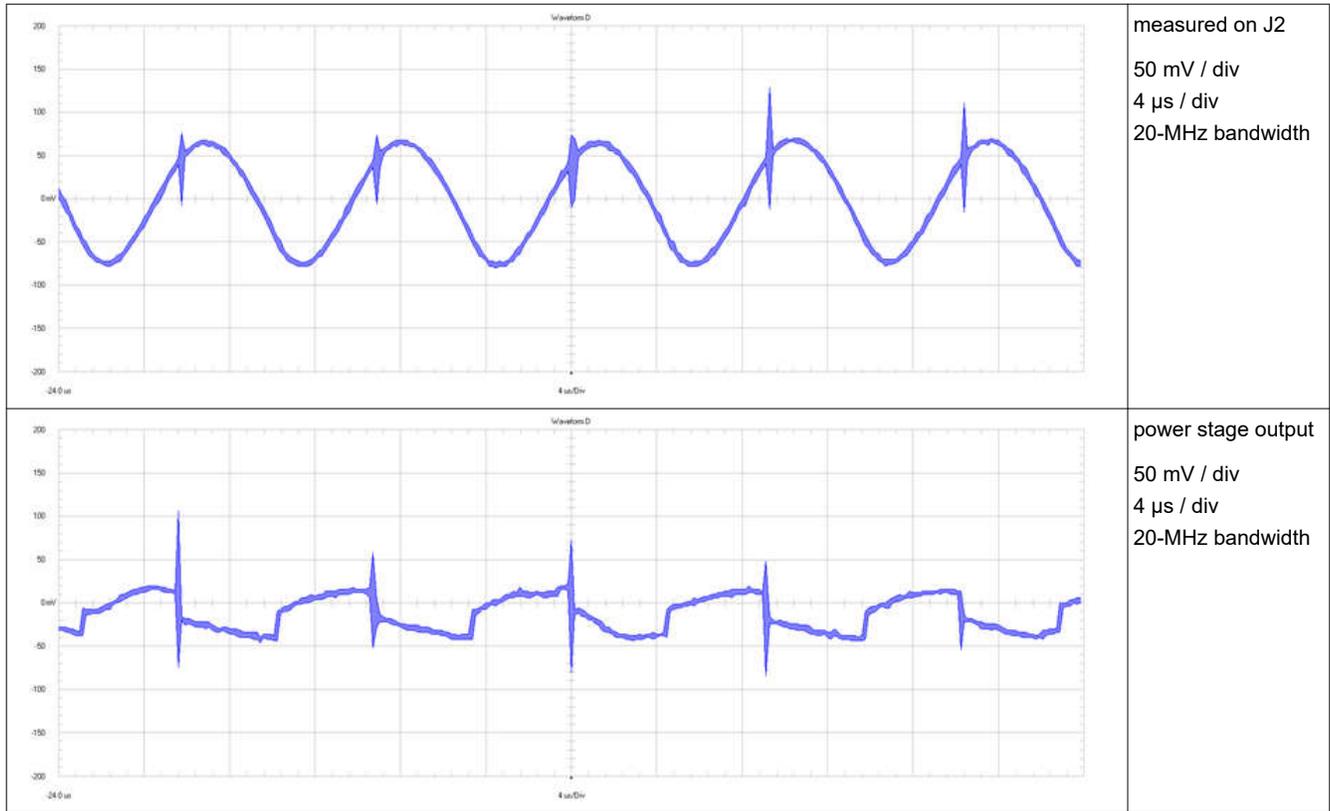


Figure 3-5. Output Voltage Ripple

3.3 Load Transients

The electronic load operates in constant-current mode. The current is switched from 0.5 A to 1.5 A with a frequency of 25 Hz. The input voltage was set to 24 V.

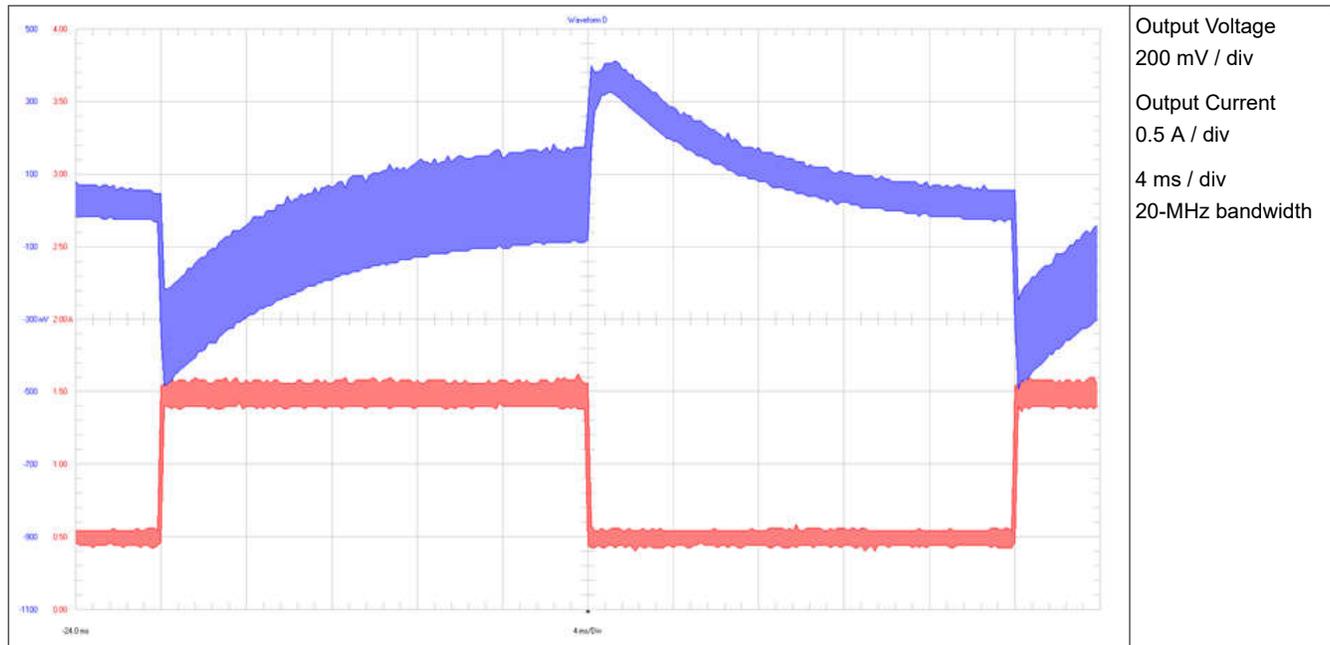


Figure 3-6. Load Transient 0.5 A to 1.5 A

3.4 Start-Up Sequence

Start-up behavior is shown in the following figure.

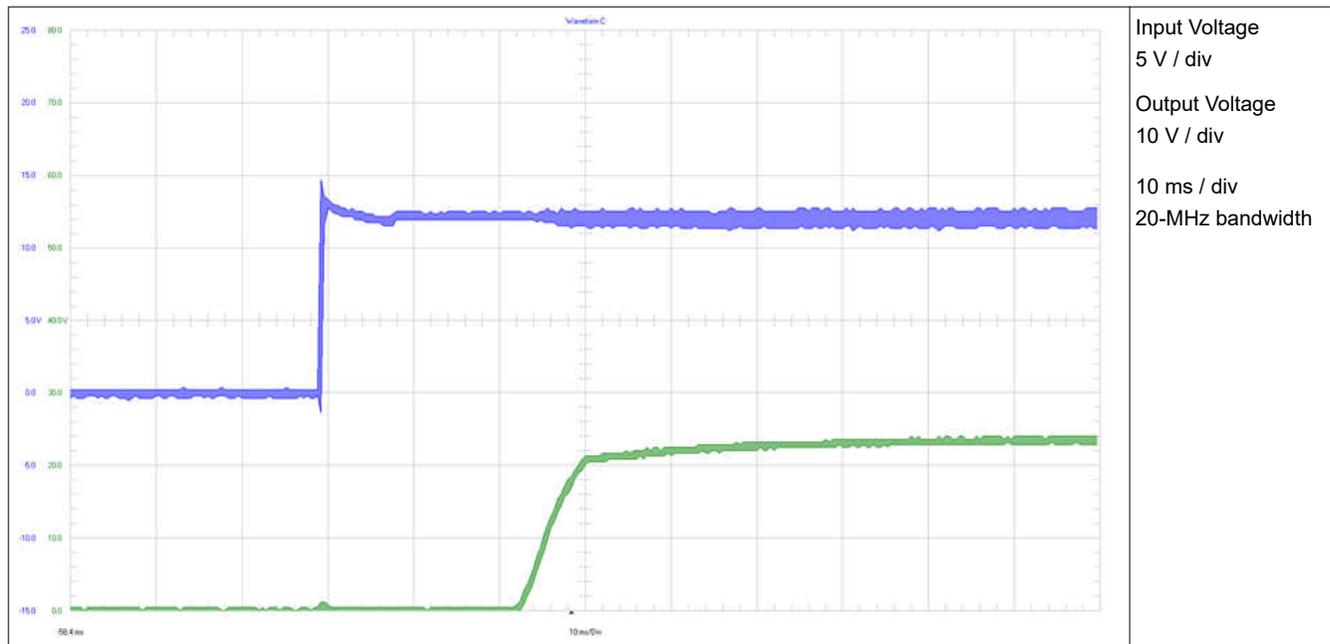


Figure 3-7. Start-up With 12-V Input Voltage

3.5 Shutdown Sequence

Shutdown behavior is shown in the following figure.

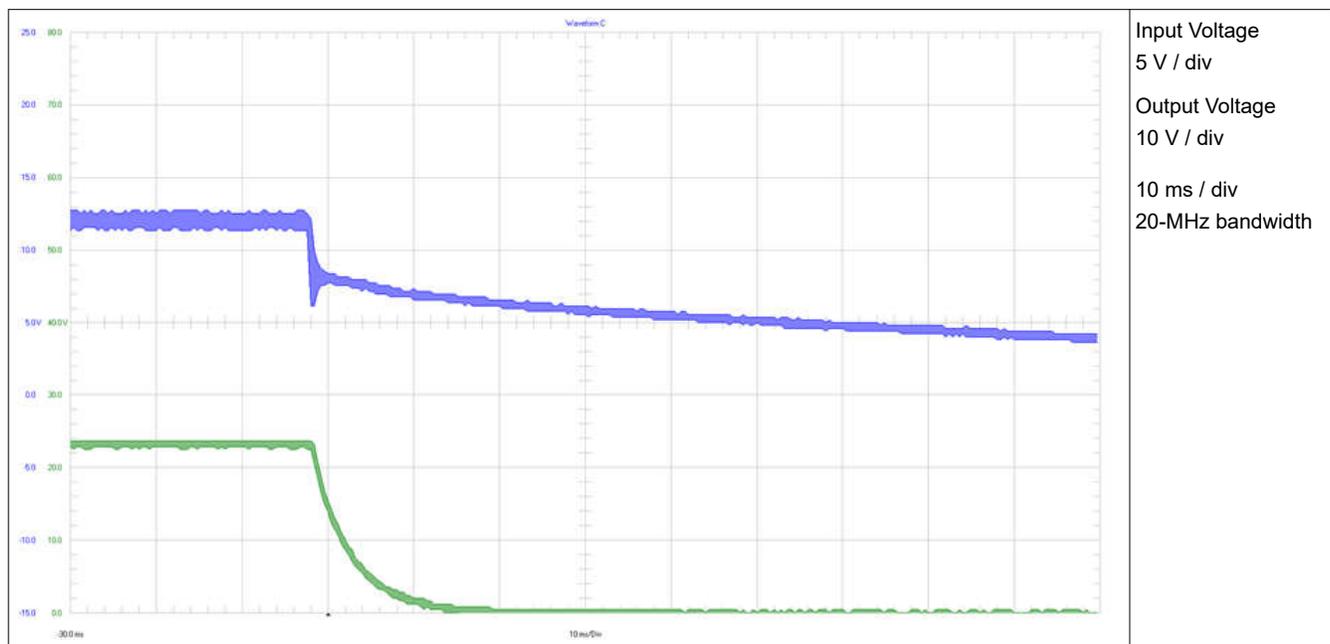


Figure 3-8. Shutdown With 12-V Input Voltage

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated