

Texas Instruments Inc.

High Performance Analog

High Speed Products

High Speed Amplifiers

Design Guide

Low power fully differential PGA using OPA2683

Ranji C. Bhola

Contents

- List of Figures 3

- Abstract..... 4

- Reference Design: Schematic..... 5

- Reference Design: Test Circuit 6

- Performance: Frequency Response 7

- Performance: Harmonic Distortion..... 10

- Performance: Power Consumption vs. Gain 11

- Results..... 12

- Conclusion..... 13

List of Figures

Figure 1 – Reference Design Schematic

Figure 2 – Test Circuit

Figure 3 – Gain = $2V/V$; $V_{\text{output}} = 2V_{\text{pp}}$ Frequency Response

Figure 4 – Gain = $21V/V$; $V_{\text{output}} = 2V_{\text{pp}}$ Frequency Response

Figure 5 – Gain = $50V/V$; $V_{\text{output}} = 2V_{\text{pp}}$ Frequency Response

Figure 6 – Gain = $70V/V$; $V_{\text{output}} = 2V_{\text{pp}}$ Frequency Response

Figure 7 – Gain = 2, 21, 50, $70V/V$; $V_{\text{output}} = 2V_{\text{pp}}$ Frequency Response

Figure 8 – Harmonic Distortion; $f = 300\text{kHz}$ & $f = 5\text{MHz}$

Figure 9 – Power Consumption vs Output Voltage vs Gain

Abstract

The objective of this reference design was to create a Low Power Fully Differential Programmable Amplifier. To accomplish this goal, the High Speed Current Feedback Amplifier OPA2683 was selected to provide a low power solution. The design is to provide a quick evaluation solution that provides the benefits of a PGA performance without the penalty on power consumption; within reason considering board design limitations.

A low power current feedback amplifier was selected to provide the drive capabilities required of a PGA with high dynamic range, high slew rate, and reduced bandwidth changes versus gain; gain and bandwidth are independent of each other, and the bandwidth is relatively constant with the R_f feedback resistor. With the OPA2683 we add the benefit of low power operation to the list of benefits. The OPA2683 provides many of the advantages of an ideal CFB with low power operation, there is also a closed-loop input stage buffer to provide low and linearized impedance at the inverting input. A deeper explanation of voltage feedback and current feedback amplifiers may prove useful, but is beyond the scope of this paper; a good resource would be the Texas Instruments Application note SLVA051^{*}.

Programmable gain amplifiers provide the benefit of adjustable gain without need to change external feedback resistors. These amplifiers are excellent for data acquisition systems, providing wide dynamic range based on input signal amplitude, allowing full use of the ADC input range.

Fully differential amplifiers provide excellent ADC drive performance with improved even order distortion performance, and increased dynamic range. So the combination of the two should prove to be a useful device.

Typically PGAs provide the relatively flat bandwidth across all gain settings, low distortion, and wide dynamic range versus gain. In PGAs that accomplish this, the power consumption is the cost for the performance. The increased power is due to the gain switching circuitry built into the amplifier, and the architecture requirements to provide flat response throughout gain settings. With this low power fully differential programmable reference design you have programmable gain control via analog circuitry and wide bandwidth at high gains with relatively low power consumption compared to current PGAs on the market.

** Voltage Feedback vs. Current Feedback Op Amps Application Note*

Reference Design: Schematic

The OPA2683 Dual Low Power amplifier was used in the following Programmable Gain Amplifier reference design. A low power switch may be utilized and is included in the reference design schematic, but for the purposes of this paper jumpers were used to switch between gain configurations. The schematic below has a switch in place, however it has been removed for testing as peaking was significantly detrimental to performance. A lower capacitance switch may be selected for use, or jumpers may be used between gain settings.

In selecting a switch for this type of configuration, the following should be considered. The switch should provide an isolated path when OFF and low resistance when ON. The other key to a stable design would be low capacitance in both states. For the OPA2683 it is recommended to have low parasitic capacitance $<2\text{pF}$ on the inverting input. External capacitance in excess of 2pF will start to peak the frequency response, in excess of 5pF on the inverting node, input stage oscillation that cannot be filtered by a feedback element adjustment will be present.

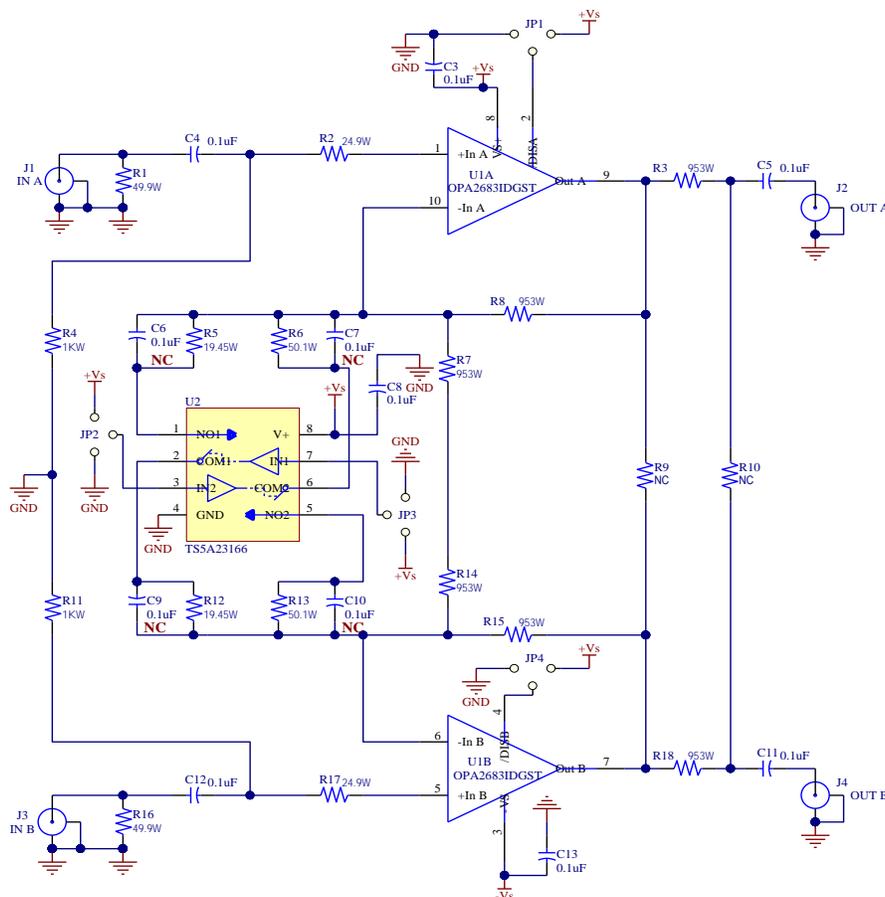


Figure 1: (Reference Design Schematic)

Reference Design: Test Circuit

The reference design was evaluated with the following test conditions:

Voltage Supply = +/-5V

G = 2, 21, 50, and 70 V/V

Load = 1kohm

Output Voltage = 2Vpp for Frequency Response and Harmonic Distortion measurements.

A THS4509 Fully Differential Amplifier in Single-ended to Differential conversion configuration was used to provide a single-end to differential conversion for the input signal. EVMs for this are available on the TI eStore.

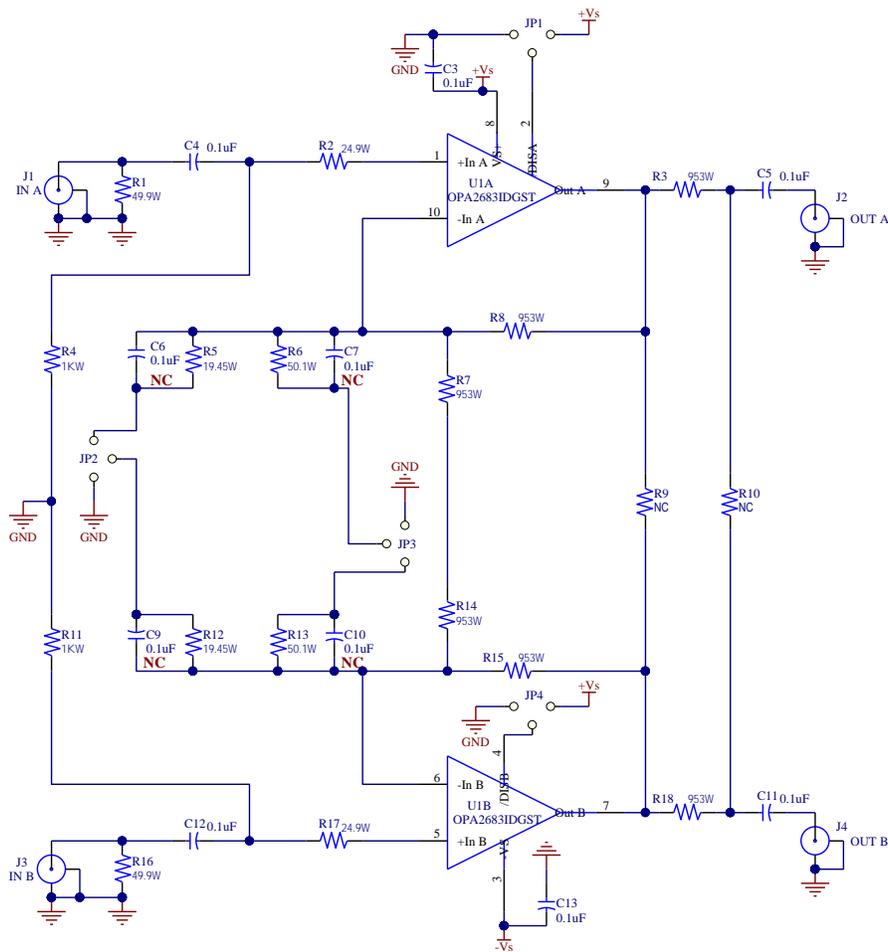


Figure 2: (Test Circuit)

Performance: Frequency Response

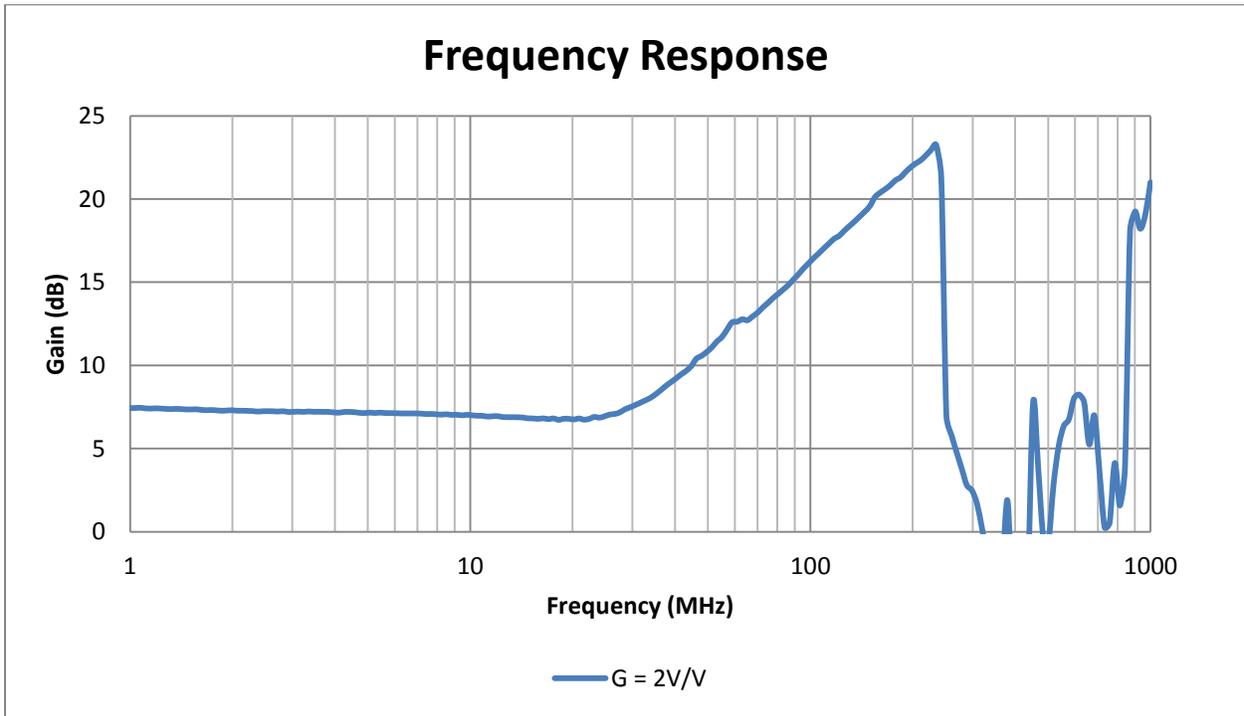


Figure 3: (G = 2V/V -3dB BW = 278MHz)

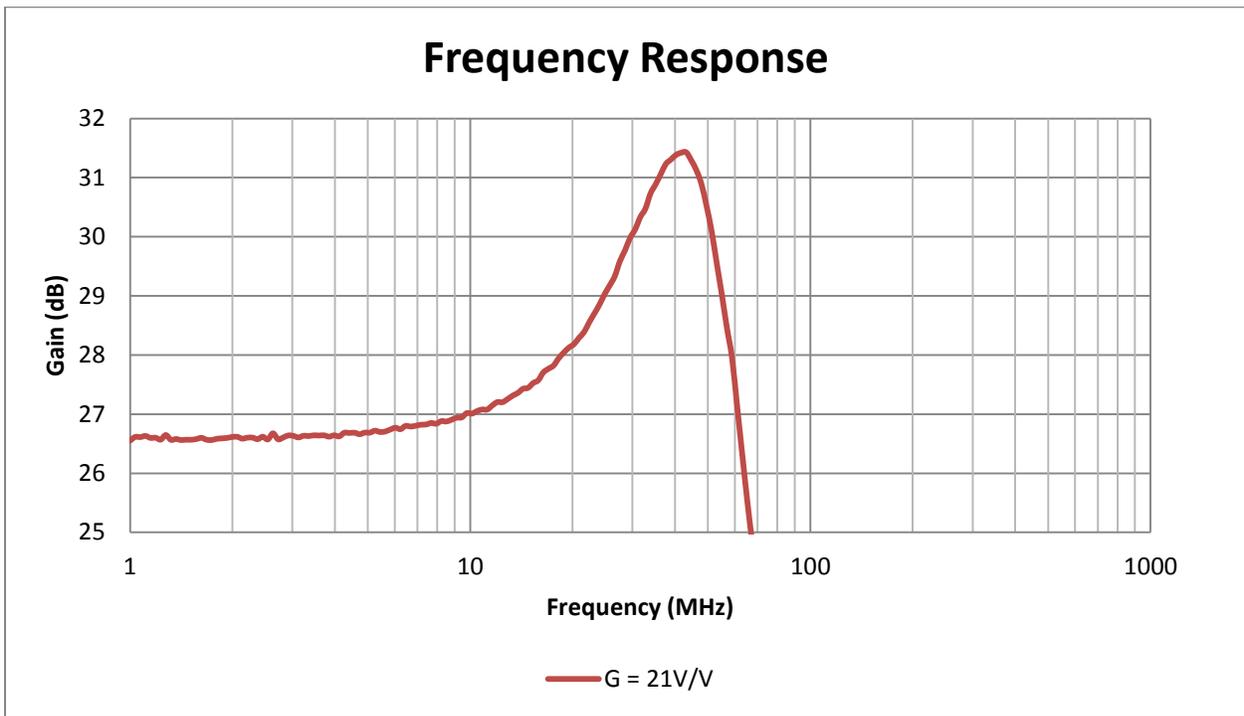


Figure 4: (G= 21V/V -3dB BW = 72MHz)

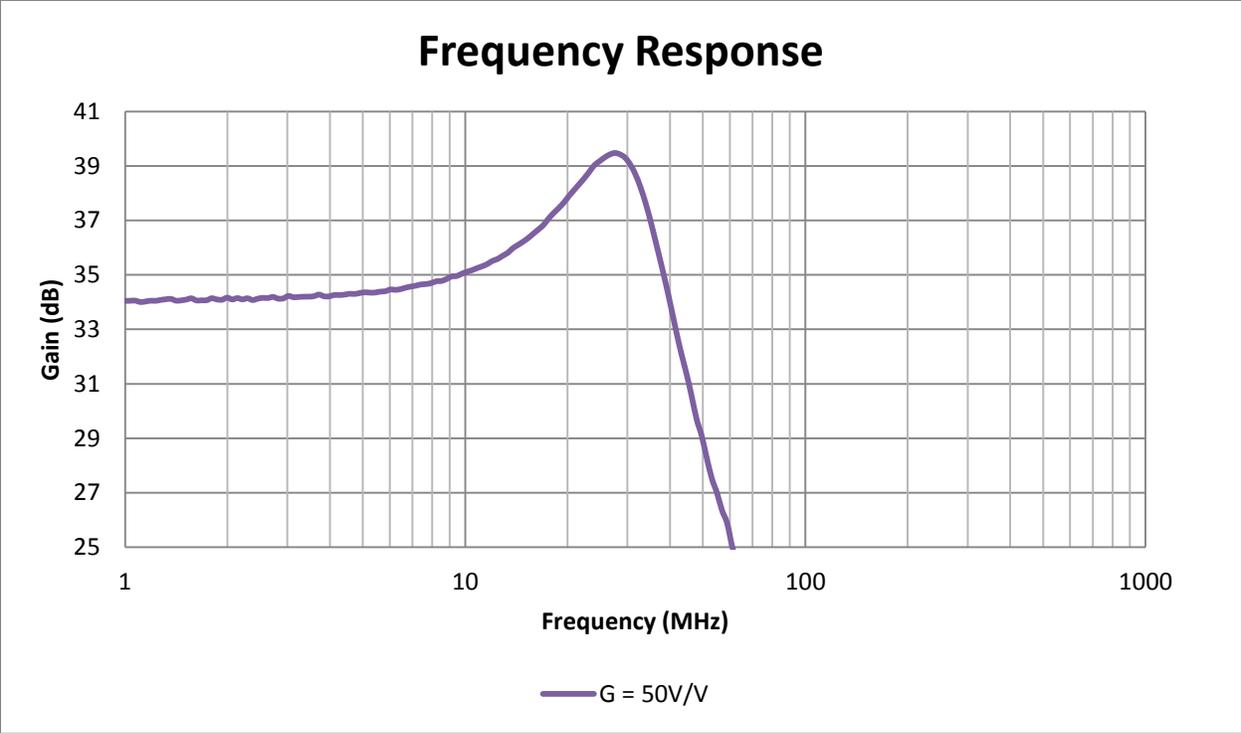


Figure 5: ($G = 50\text{V/V}$ -3dB BW = 45MHz)

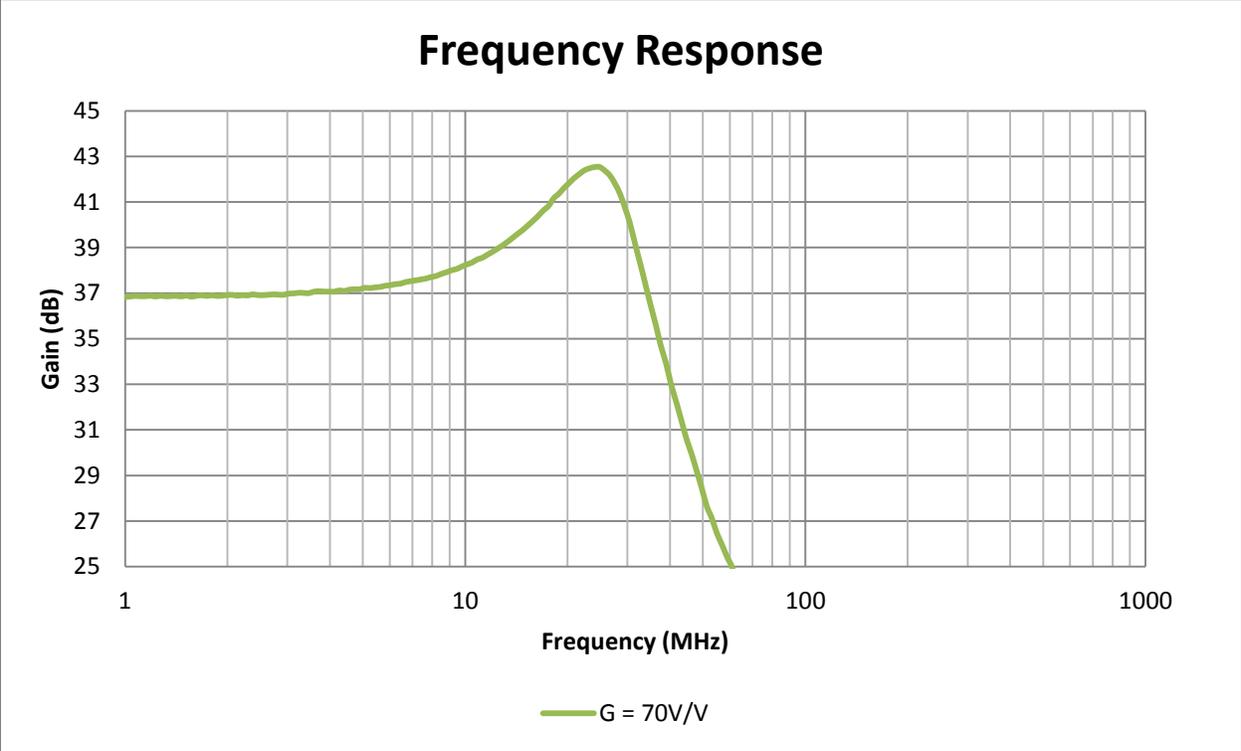


Figure 6: ($G = 70\text{V/V}$ -3dB BW = 40MHz)

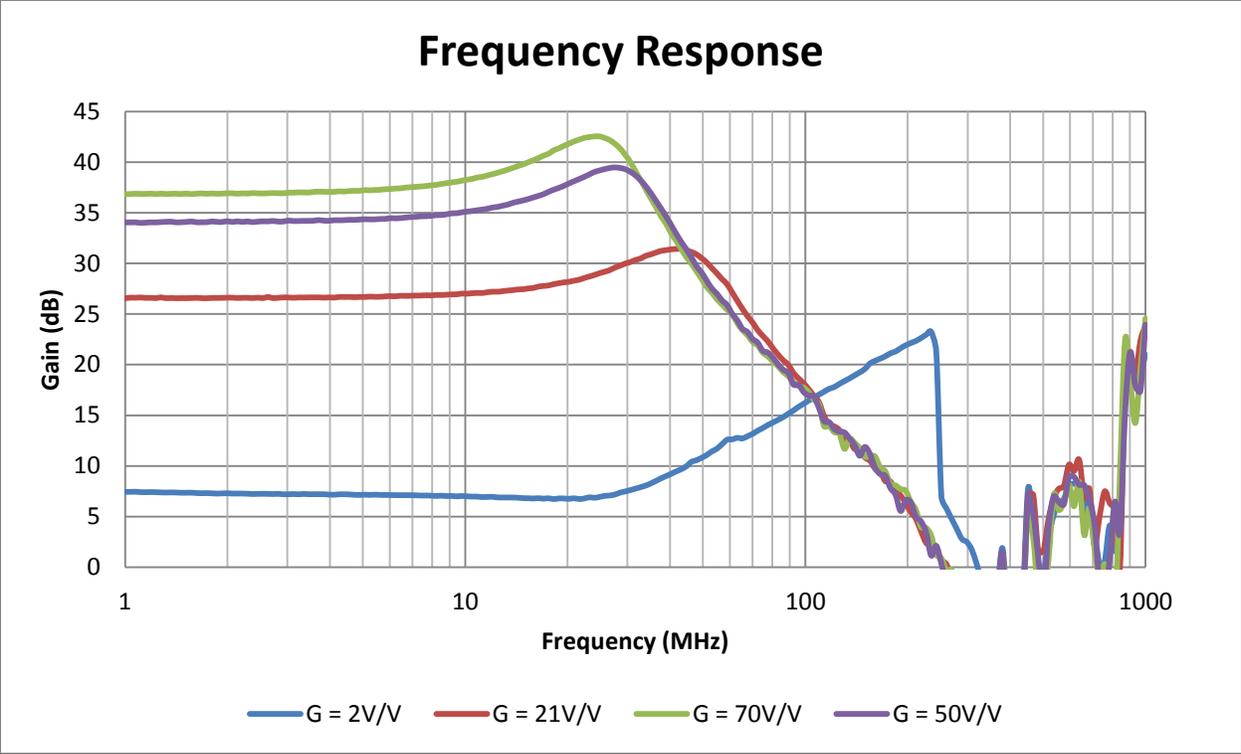


Figure 7: (All Gain Settings)

Performance: Harmonic Distortion

f = 300kHz		f = 5MHz	
600kHz	900kHz	10MHz	15MHz
HD2 (dBc)	HD3 (dBc)	HD2 (dBc)	HD3 (dBc)
-58.65	-31.15	-58.56	-30.85
-49.88	-28.55	21.33	49.88
-41.41	-28.41	13.00	41.41
-38.42	-28.20	10.22	38.42

Figure 8: Harmonic Distortion f = 300kHz & f = 5MHz

Performance: Power Consumption vs. Gain

The power consumption was tested with a 5MHz Sine wave with varying amplitude.

Load = 1kohms

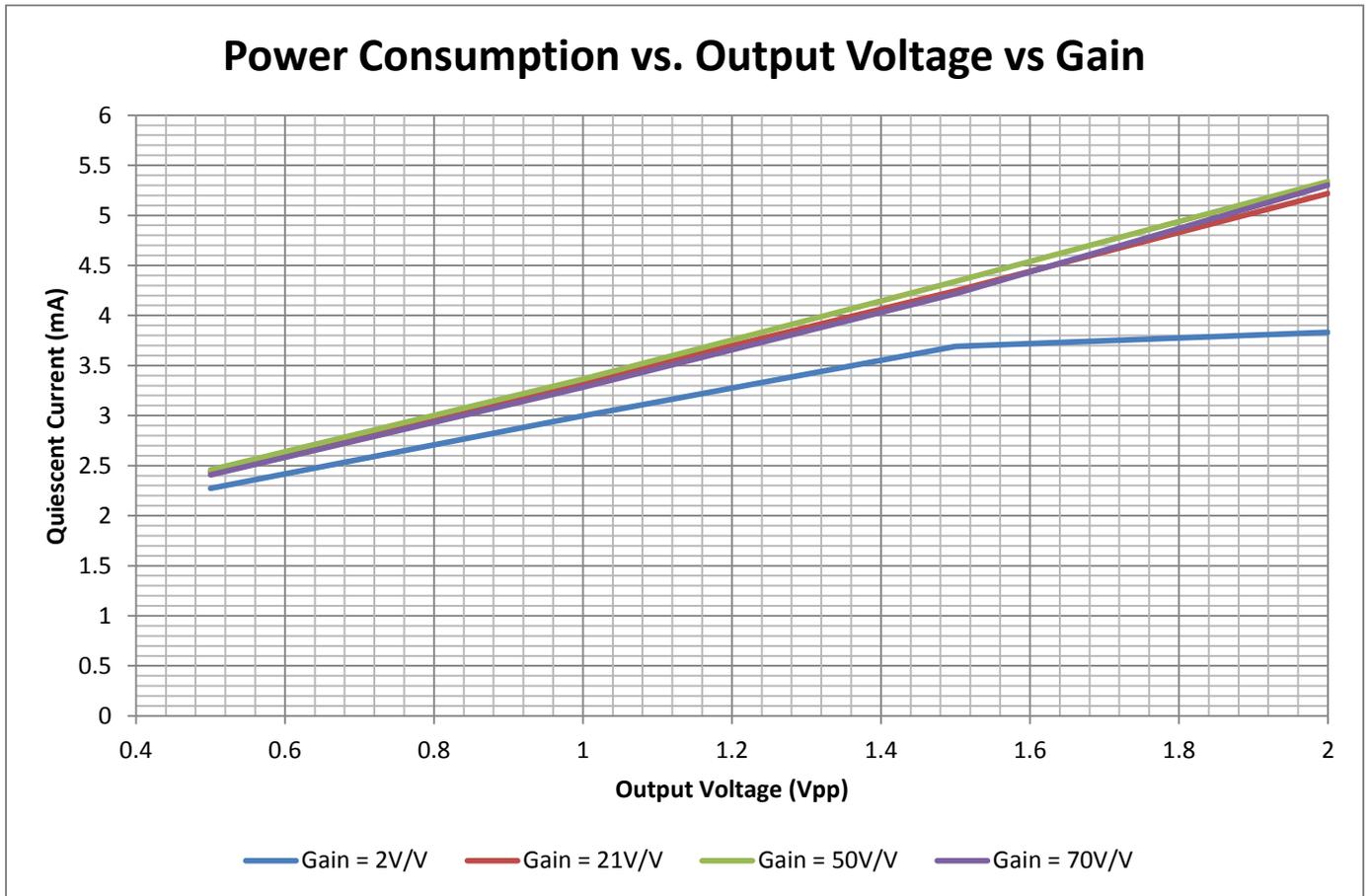


Figure 9: Power Consumption vs. Output Voltage vs. Gain

The plot shows the quiescent current of the reference design with varying output voltage at each gain setting. Gain of 2V/V shows the most differentiated change versus output voltage, with the higher gains being nearly negligible for power consumption difference.

Results

From the above frequency response plots we see significant peaking in the Gain of $2V/V$. This is due to the excess capacitance on the inverting input from the board and from the jumpers used for the test circuit. With decreased capacitance this peaking will diminish. The peaking is also noticeable in the higher gain settings, but this is reduced since the series resistance of R_g eliminates some of the stray capacitance on the inverting input when the jumper is closed.

Overall the bandwidth is reduced; as you would expect in higher gain configurations. Considering this is a low power part used in this configuration, the tradeoff is warranted by the goal. As with most amplifiers and overall analog designs, higher performance for flat wide bandwidth and low distortion comes at the price of consuming more power.

The distortion performance is also reduced for the configuration used in this reference design. This further proves the challenge in creating a programmable differential amplifier with the switchable gain done externally. Careful consideration must be taken to reduce stray capacitance on the sensitive feedback path as mentioned in an earlier section of this paper.

Another device which accomplishes the goal of this reference design is the LMH688x which is The World's First Programmable Differential Amplifier. The aforementioned device has excellent performance with higher power consumption, but for 2.4GHz bandwidth, this part does a superior job with low distortion, low noise and high bandwidth.

Conclusion

The OPA2683 provides the performance metrics necessary to accomplish the goal of a fully differential low power PGA solution. The OPA2683 demonstrates peaking at throughout gain settings; however this is to be expected, due to stray capacitance. The limitation of a low power solution for a fully differential programmable has been mitigated with this reference design. Performance and distortion are comparable relative to the power consumption for such a device configuration. For better performance higher power consumption is to be expected.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.