

TI Designs High-Efficiency IP Camera Power Module Design



TI Designs

TI Designs provide the foundation that you need including methodology, testing and design files to quickly evaluate and customize and system. TI Designs help **you** accelerate your time to market

Design Resources

SAT0027	Design Folder
TPS23753A	Product Folder
TPS54339	Product Folder
TPS5432	Product Folder
TPS63036	Product Folder
TPS3839G33	Product Folder
TPS3897A	Product Folder

Design Features

- Enables Class 1 PoE system power in a 1080p IP Camera.
- IP Camera solution power as low as 2.2 W for 1080p30 with 5-V input.
- 90% efficiency on 5-V operation. 78% efficient on PoE operation.
- Lower system heat generation simplifies package design.
- Cost effective compared with many PMIC solutions.

Featured Applications

- [DM385 IP Camera Reference Design](#)



[ASK Our Analog Experts](#)
[WebBench Calculator Tools](#)

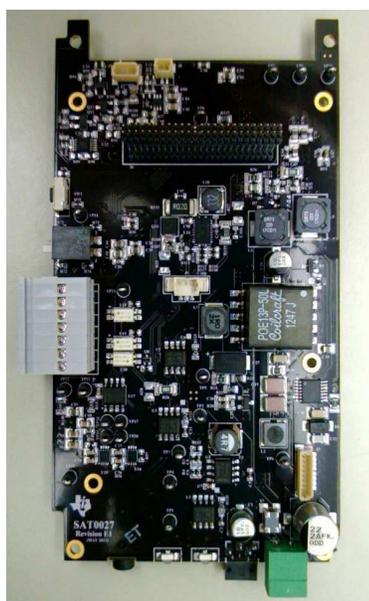


Figure 1. Power Module

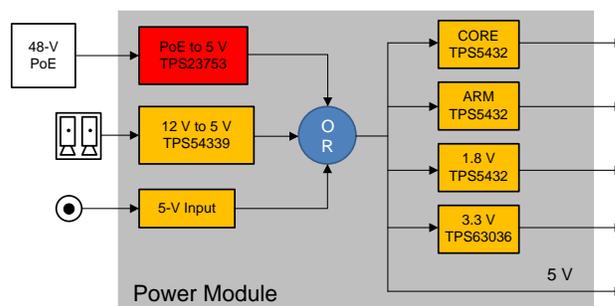


Figure 2. Power Module Block Diagram



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

All trademarks are the property of their respective owners.

1 System Description

The Low-Power Internet Protocol (IP) Net Camera Power-Module Reference Design is a highly efficient power supply design. The module forms a part of an IP-security camera based on the DM385 DaVinci™ Digital Media Processor ([DM385 IP Camera Reference Design](#)). The module can also be used for IP cameras based on similar application processors.

The power module features a Power over Ethernet (PoE) converter. The power module can also operate with a 5-V or a 12-V power input. The module supplies the Core, HDVICP, and ARM supplies for the DM385. Other supplies provided are 1.8 V, 3.3 V, and 5 V for IO and peripheral functions. The power module also contains circuits required for peripherals in the previously mentioned IP Net Camera: analog TV output, auto IRIS motor control, RS485 interface (PHY), LED indicators, and the alarm interface. The power module is built on a six-layer circuit board.

The Power Module was designed to allow low power consumption by the IP camera.

Table 1. System Performance Summary⁽¹⁾⁽²⁾

Sensor Type	Video Frame Rate	Ethernet Link Type	CORE and ARM Voltage	Input Supply	Power Consumption
AR0330	60 Hz	1000 Mb	1.35 V	5 V	3.59 W
	60 Hz	100 Mb	1.35 V	5 V	3.35 W
	30 Hz	100 Mb	1.35 V	5 V	2.51 W
	30 Hz	100 Mb	1.2 V	5 V	2.21 W

⁽¹⁾ The AR0330 sensor has an MIPI CSI2 output. Other types of sensor can be used with the DM385 IP camera. The total power consumption of the system is different when a different sensor is used.

⁽²⁾ Video output is three video streams: 1080P H.264, 1080P MPEG4, and standard definition (SD) video.

2 Design Analysis

This section is a circuit-by-circuit description of the power supplies on the Power Module and how they work together. [Figure 3](#) shows a block diagram of the power supplies on the power module. Refer to the power module schematic for the circuits. The power properties for each circuit are measured when used in the DM385 IP Camera Reference Design configuration or with a discrete load. Note that when the camera is operating it outputs three video streams to Ethernet: H.264 1080p, SD video (D1), and MPEG4 1080p. The frame rate is either 30 Hz or 60 Hz and is noted when a test result is reported. The power results are based on an AR331 Sensor Module with the ARM and Core voltages set for 1.35 V unless otherwise noted. In-system power was measured on a different unit than the one used to characterize each power supply and therefore some results differ between the two power results.

The following sections describe the power circuitry. There are other circuits on the power module that are present to fulfil IP-Camera related functions but that are not part of the power supply function. These additional circuits are included to describe the full functionality for the IP-Camera.

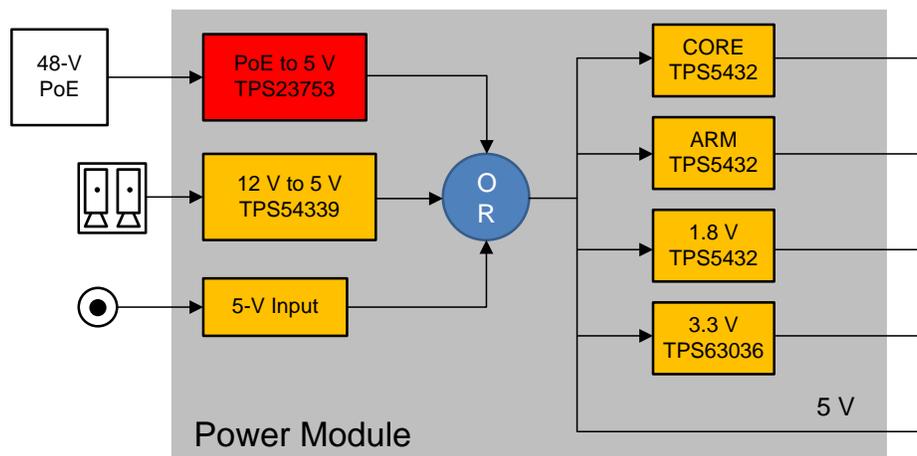


Figure 3. Power Module Block Diagram

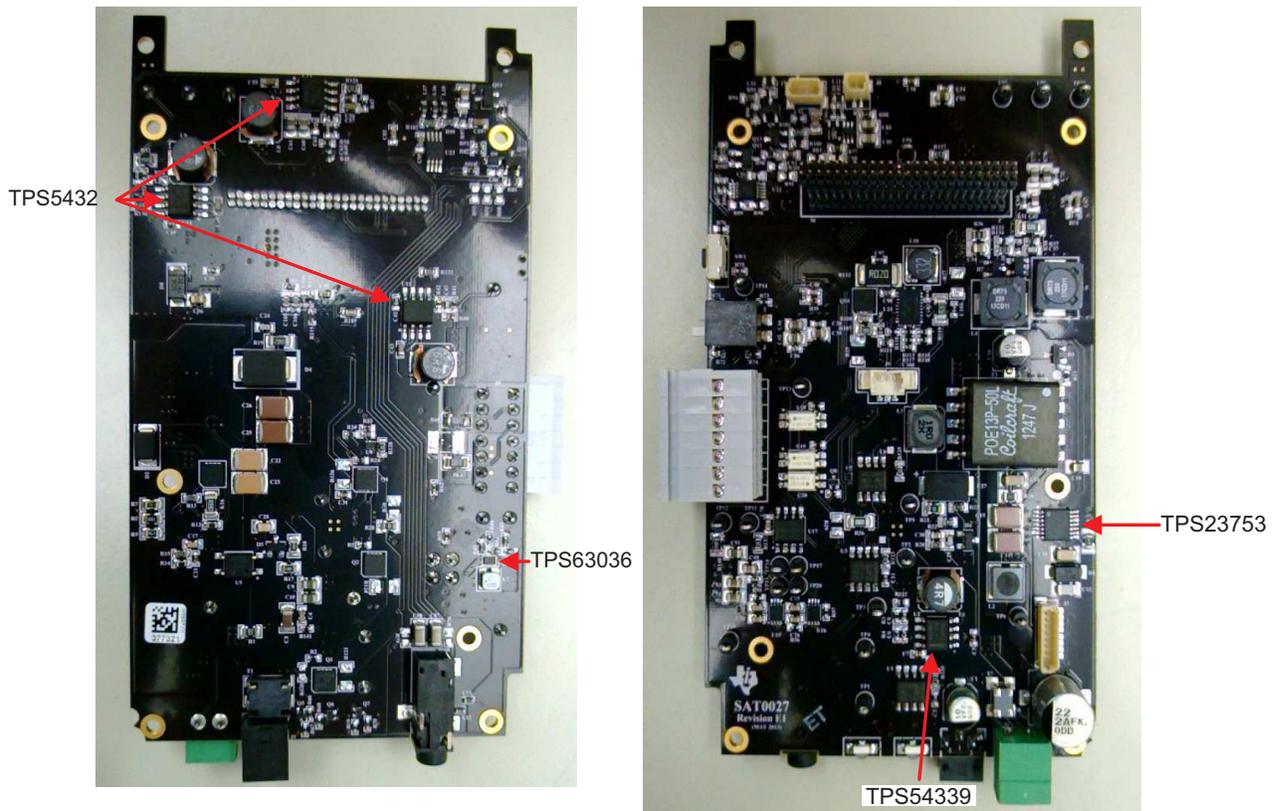


Figure 4. Power Module Board Design Showing Location of Major Components

2.1 Input Supplies

The three possible power inputs to the system are PoE, 12 V, and 5 V. The PoE and 12-V inputs are converted to 5 V. When converted, all of the possible 5-V sources are connected together through a power supply OR circuit. [Figure 5](#) shows the full circuit.

2.1.1 5-V Input

A barrel connector provides the 5-V input. The 5-V input is intended for use with an appropriately-sized DC supply. The input path incorporates a low-pass filter to reduce EMI from being conducted into or out of the camera. The external 5 V then connects to a TPS2419D power-supply OR controller (U1 plus Q1). The barrel connector has a switch that disengages when the barrel is inserted. This function ensures that the 12-V and PoE input OR controllers are disabled. See [Section 2.1.4](#) for additional information on this function. When the camera streams 1080p at 30 Hz the input power is 3.48 W with a 5-V input supply when using 1.35 V for the ARM and Core supplies and an AR331 image sensor is used.

2.1.2 12-V Input

A connector supplies the 12-V input that is converted to 5 V by a TPS54339 step-down, or buck, converter. This 5-V output is connected to a different TPS2419 OR controller (U3 plus Q2). The TPS54339 converter has an input voltage range of 4.5 to 23 V and a rated output current of 3 A. This converter was selected because of the good efficiency characteristics and a 5-V output over the expected current range. Refer to the efficiency graphs in the TPS54339 datasheet ([SLVSBT2](#)) for more information. The expected efficiency is above 90% for loads between 0.25 A and 3 A. When the circuit was tested with an external load and 12 V for an input, the efficiency result was similar to the values expected from the data sheet as shown in [Figure 6](#).

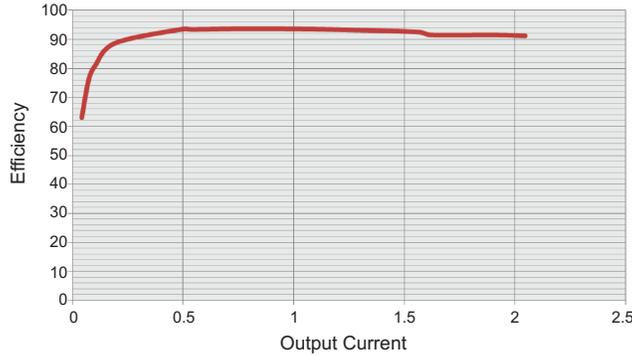


Figure 6. Measured Efficiency Versus Output Current

As shown in [Figure 7](#), the load regulation of the circuit is also good.

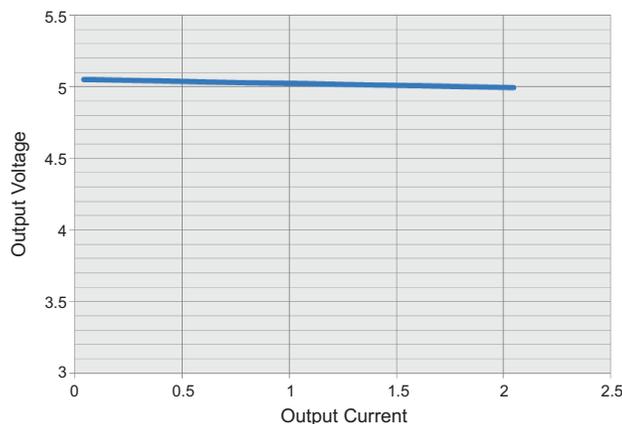


Figure 7. Output Voltage Versus Load Current

When tested with the camera operating at a 1080-P 30-Hz output-stream to Ethernet, the supply output was 5.03 V, 692 mA, 3.48 W. The input power to the TPS54339 device was 3.82 W, therefore the efficiency was 91%.

2.1.3 PoE Supply

The PoE input is converted to 5 V by a TPS23753 PoE interface and controller. This controller conforms to the IEEE802.3at standard for a type 1, 13-W powered device (PD). The controller provides the PoE detection signature required by the specification. The 5-V output is isolated from the Ethernet input by T3, a Coilcraft PoE13P-50L. A different board in the system supplies the input. This board is called the SUB board (SAT0007) and contains the Ethernet connector and transformers. Figure 8 shows the Ethernet-power input section of the SUB board.

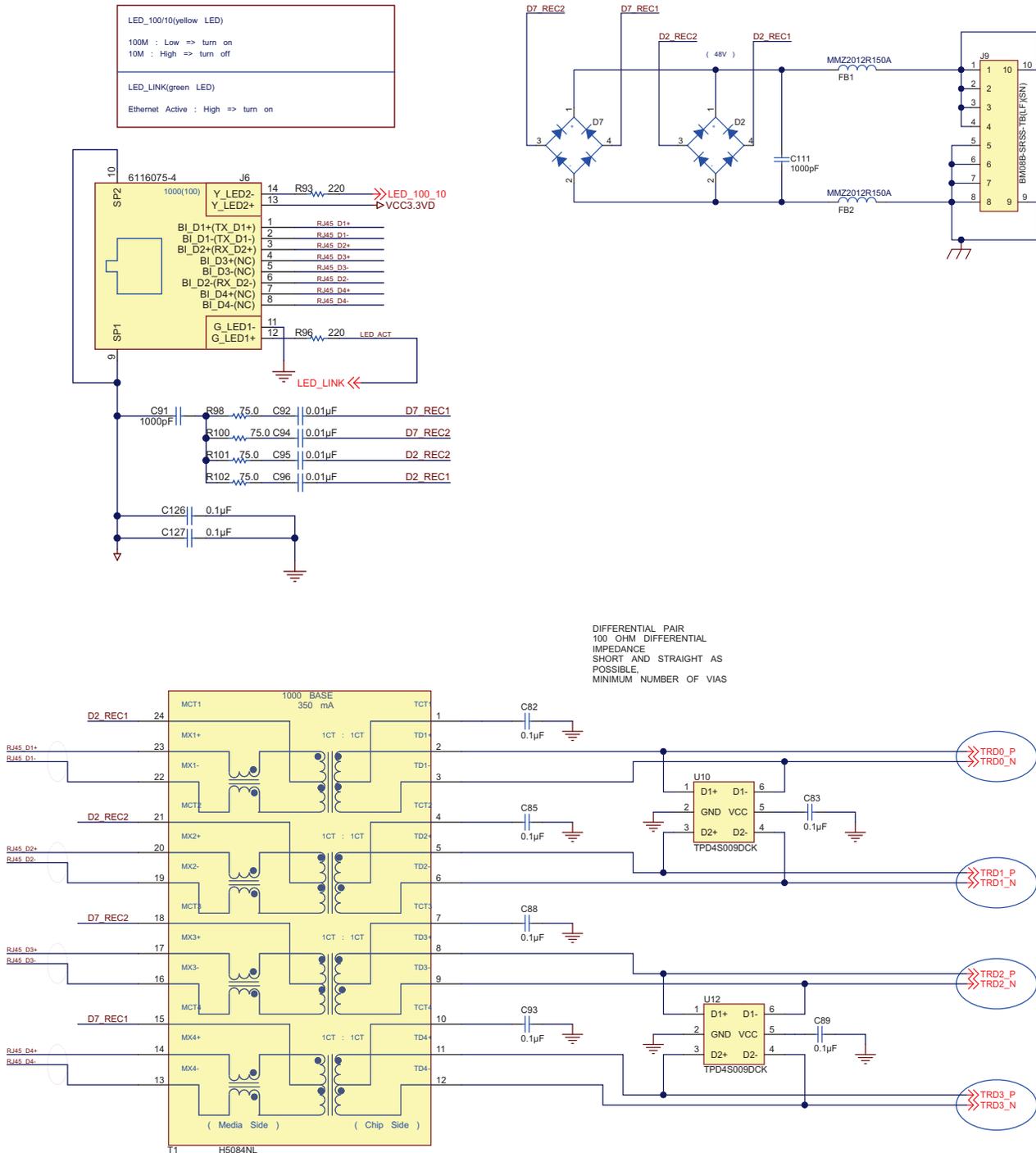


Figure 8. Ethernet Power Input Section of SUB Board

The Ethernet power is supplied from the centers of the Ethernet isolation transformer input and routes to two bridge rectifiers. These bridge rectifiers connect in turn through connectors J9 on the SUB Board, J3 on the Power Module.

Because of the additional circuitry in this supply, specifically the transformers, there are more losses in this circuit than in the 12-V to 5-V supply. Efficiency for this supply is reasonably good. The efficiency with a 50-V PoE input is shown in [Figure 9](#).

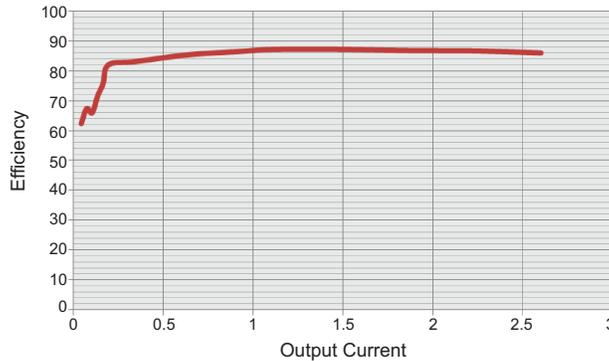


Figure 9. PoE — TPS23753A Rail (No Other Rails Enabled)

As shown in [Figure 10](#), load regulation for this circuit is very good.

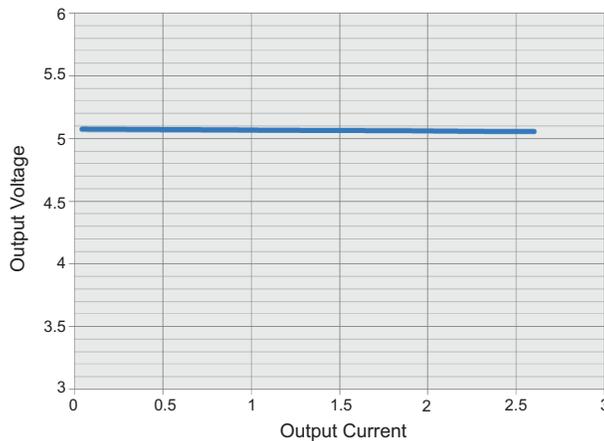


Figure 10. Output Voltage Versus Load Current

When used in the system with the camera producing 1080p 30 Hz, the output was 5.05 V, 634 mA for an output power of 3.2 W. The input was 47.1 V, 80 mA, 3.768 W, therefore the efficiency is 85%. The output of this circuit also feeds a TPS2419 OR controller (U6 and Q4).

2.1.4 OR Controllers

The TPS2419 OR controllers are the interface between the various 5-V supplies and the remainder of the system. The outputs of the PoE-to-5-V and 12-V-to-5-V converters are set at slightly different voltages to ensure that the 12-V OR controller is off when PoE is present. The 5-V input ranges from 4.75 to 5.25 V. Because of this voltage range, the OR controller can source current from either the 5-V input or one of the other inputs depending on whether the other inputs are present and whether the voltage at the 5-V input is below the output of the PoE or 12-V-to-5-V converter.

When only one input voltage is available, there can be some leakage through the OR controller circuits back into the other inputs. Because of this leakage, the 5-V input connector controls additional circuitry. If a 5-V input barrel-connector is present, the signal *PoE_12V_OFF_CONT* is pulled high. Pulling the signal high turns on Q15 and Q16 which then disable the OR controllers U3 and U6. To ensure that only one input supplies the camera at a time and that there is a preference order for the inputs, additional circuitry could be added. The output of the OR controller circuitry is a single 5-V power supply *VOUT_POE*.

2.2 Electronics Supply Rails

After the OR controller circuit, there is a common 5-V supply for the rest of the system. This signal supplies all other power conversion in the system, including the DDR supply on the processor board (SAT0008) and the IRIS controller on the Power Module. The following sections describe the individual power supply circuits in the order that the supplies are enabled. All performance tests listed in Section 2.2.1 through Section 2.2.4 were performed with a 5-V input.

2.2.1 1.8-V Supply

The 1.8-V supply, the Core supply, and the ARM supply are all very similar designs. The only difference in the designs is the output voltage setting. These supplies use the TPS5432 converter. This converter has an input range of 2.95 to 6 V which is typical for a system that runs on a Lithium-Ion battery. The TPS5432 device is rated for up to 3 A and therefore can supply a wide range of output loads. The use this controller provides flexibility of the Power Module design. The loads required by the DM385 IP Camera Reference Design are well within the ratings of this device, and the loads presented are in a range where the TPS5432 device has the best efficiency. Without a change in the design, a more highly integrated processor can be used with these supplies. The only adjustment required to use a more integrated processor is to adjust the output voltages for the Core and ARM supplies. Using the same controller for all of these supplies has the benefit of reducing the number of items in the bill of material.

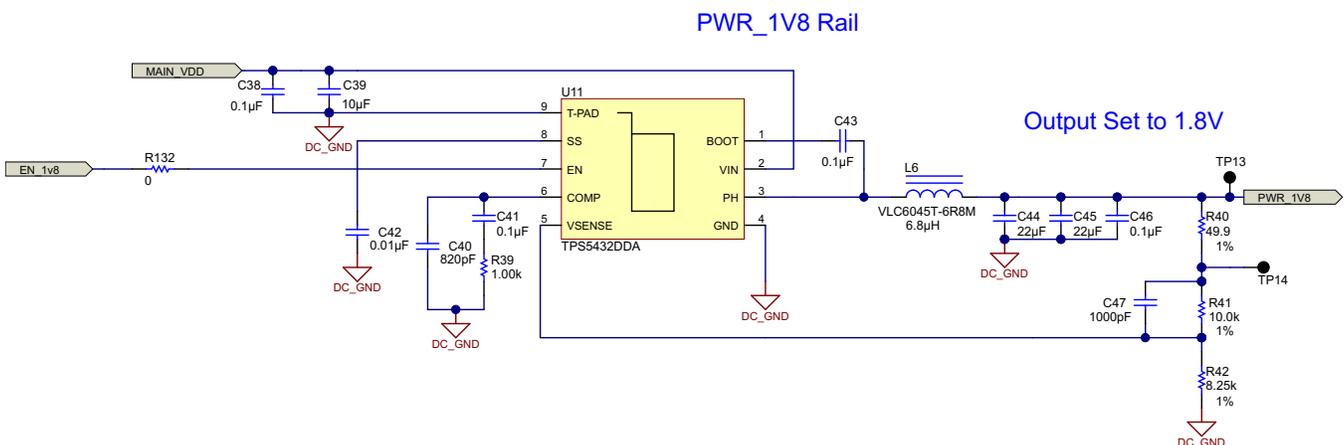


Figure 11. Power Module 1.8-V Circuit

The TPS5432 device is very efficient in the in the range of output voltages and currents used in the DM385 IP Camera. For the loads in question (below 1 A), the efficiency is at or above 90% as shown in Figure 12. For more information on the TPS5432 device, see the data sheet [SLVSB89](#).

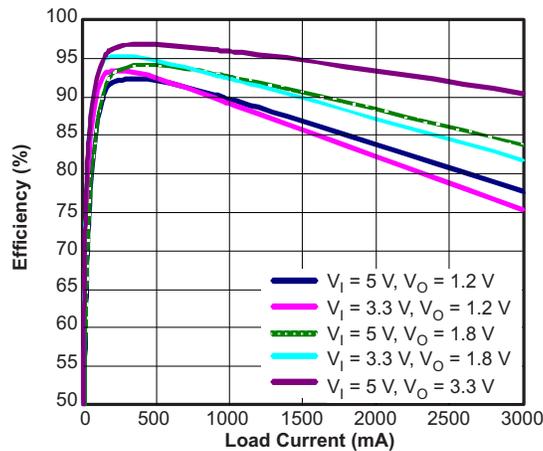


Figure 12. TPS5432 Efficiency Curve

When used in the power module, the 1.8-V supply results were similar to the TPS5432 efficiency curve as shown in Figure 13

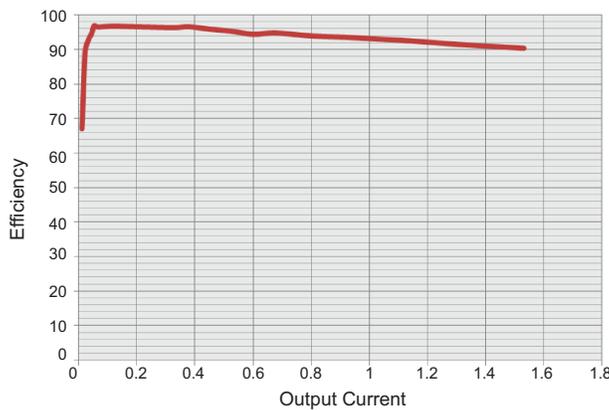


Figure 13. 1.8-V TPS5432 Rail (No Other Rails Enabled)

As show in Figure 14, load regulation for this circuit was also very good.

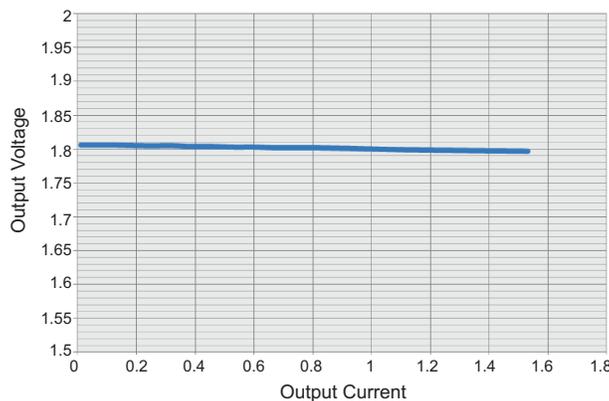


Figure 14. Output Voltage Versus Load Current

At system startup, the rise time for the 1.8-V supply is about 3.9 ms (see [Figure 15](#)).

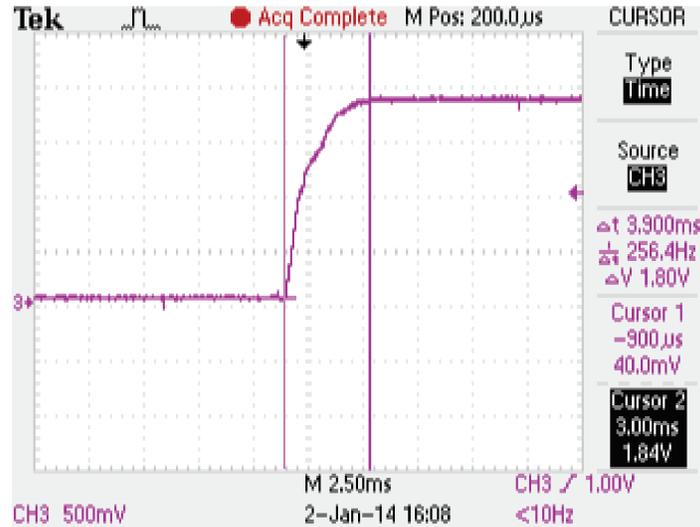


Figure 15. Rise Time — 1.8-V Supply

For a camera streaming 1080p 30-Hz video, the 1.8-V load is only 103 mA which is low for this supply. Output power is 185 mW, while the input power is 206 mW. Therefore the efficiency is 90%.

2.2.2 3.3-V Supply

The 3.3-V supply uses a TPS63036 buck-boost controller. A buck-boost controller is used to allow the main power supply rails for the camera processing to run from a Lithium Ion battery, if desired. With the battery, the input voltage can drop as low as 3 V. The buck-boost topology maintains the 3.3-V output voltage when the battery voltage drops to 3.3 V or below. In the standard application the TPS63036 stays in buck mode because a battery is not used. Figure 17 and Figure 18 show the TPS63036 efficiency curves for a 3.3-V output voltage with Power Save Mode enabled.

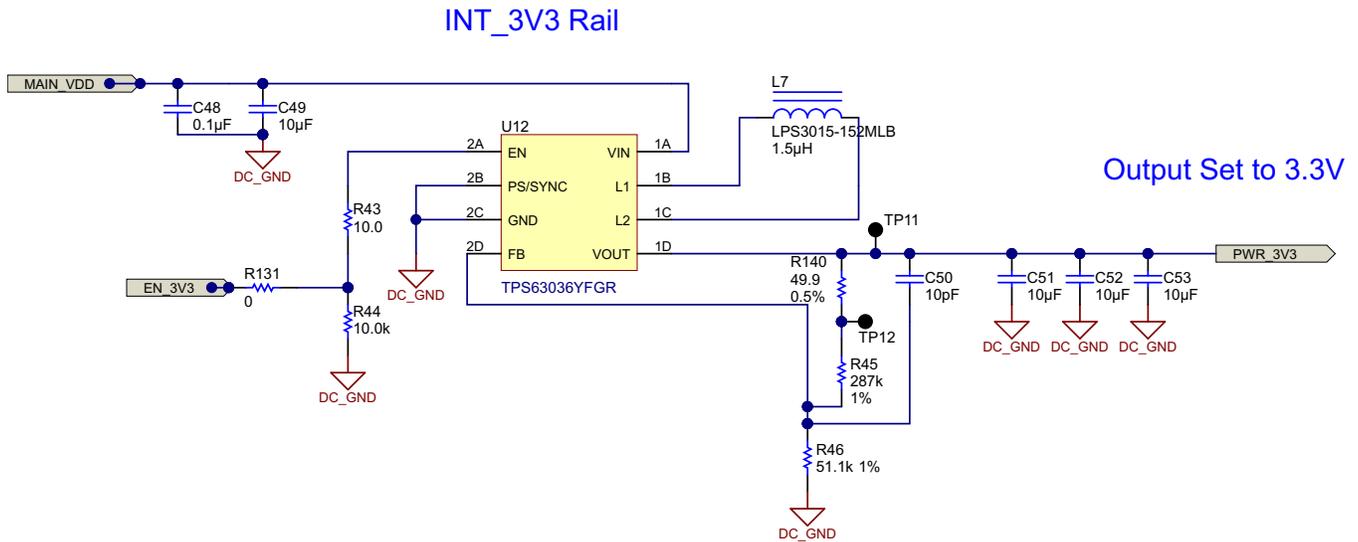


Figure 16. Power Module 3.3-V Circuit

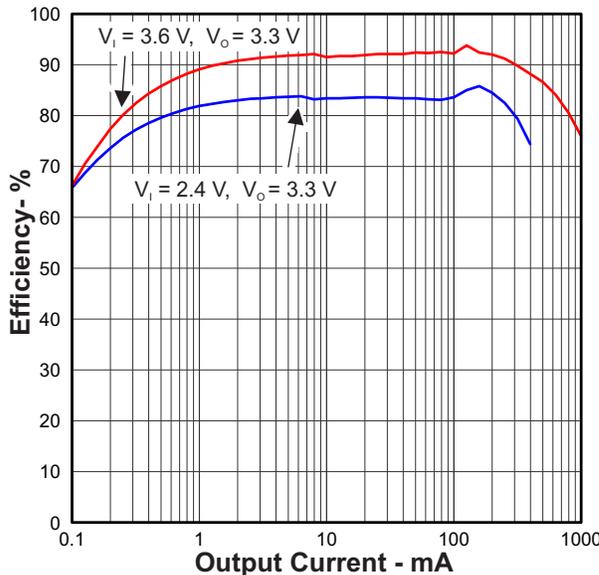


Figure 17. Efficiency vs Output Current

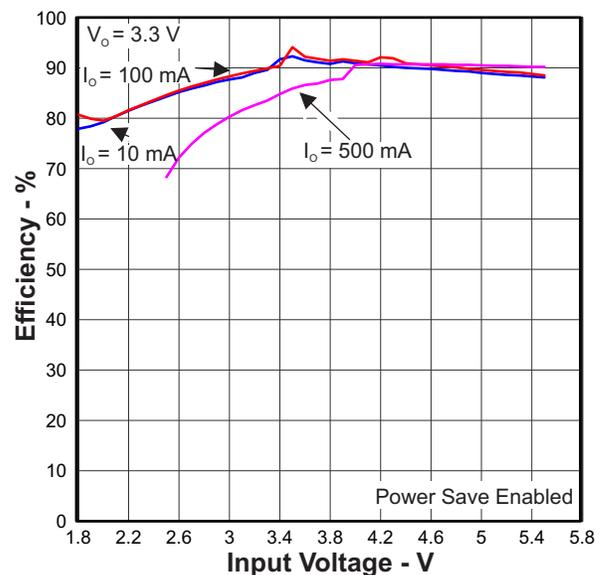


Figure 18. Efficiency vs Input Voltage

In-circuit performance results were good. As shown in Figure 19, efficiency is above 90% from about 125 mA to 600 mA.

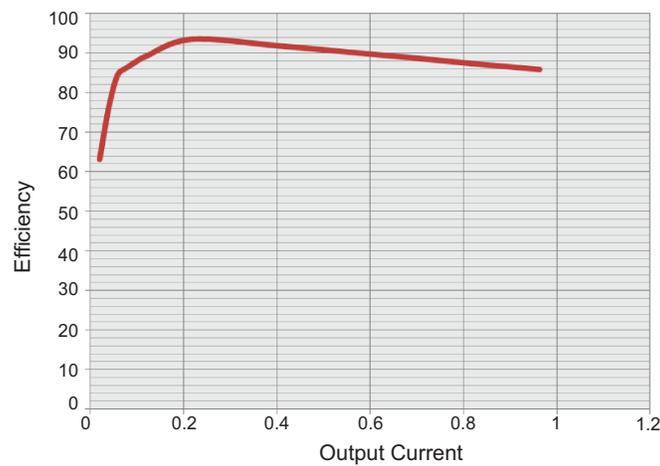


Figure 19. 3.3-V Supply — TPS63036 Rail (No Other Rails Enabled)

As shown in [Figure 20](#), output voltage regulation was very good.

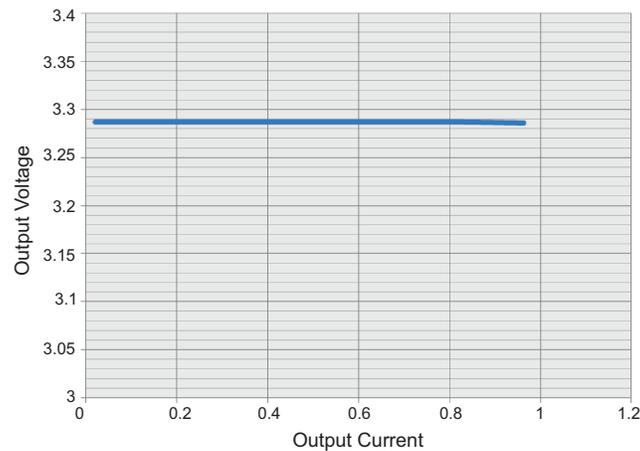


Figure 20. Output Voltage Versus Load Current

Note that the input voltage for the 3.3-V circuit test was 5 V.

At startup, the supply output rise time is very fast at approximately 760 ms as shown by the yellow trace in [Figure 21](#).

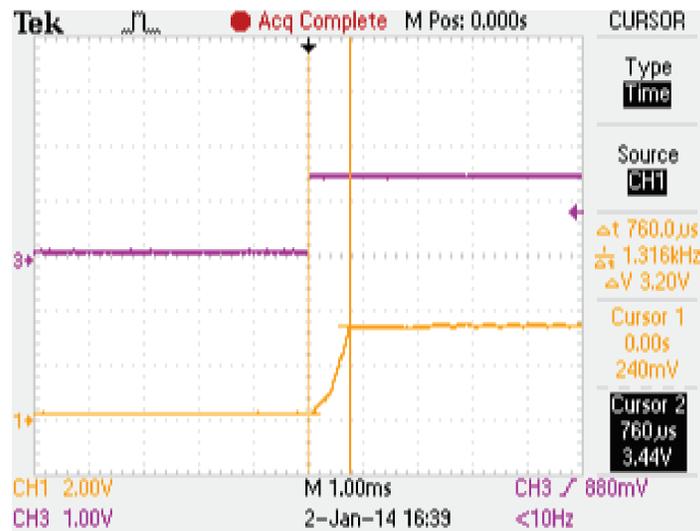


Figure 21. Rise Time — 3.3-V Supply

For a camera streaming 1080p 30-Hz video, the 3.3-V output measured 3.291 V at 336 mA for 1.106 W. Input power was 4.99 V, 246 mA, 1.228 W. The efficiency is 90%.

2.2.3 ARM and CORE Supplies

The ARM and CORE supplies use the TPS5432 as described [Section 2.2.1](#). These two supplies power different DM385 core power domains. The Core supply powers both the Core and HDVICP domains (CVDD and CVDD_HDVICP pins on the DM385), while the ARM supply powers the ARM domain (CVDD_ARM pins on the DM385). In this application, the two supplies can be set to different voltages depending upon the operating conditions. If the camera is used for both 30-Hz and 60-Hz frame rates, the two voltages are set at 1.35 V. If the camera is used only at the 30-Hz frame rate, the two supplies can be set for a 1.2-V output. With both supplies set for a 1.2-V output, the system saves a significant amount of power. In both cases, a resistor change is necessary.

NOTE: The LINUX® builds for the camera must be different. Some system clocks are lower for 30-Hz operation. The boot conditions for the clocks must also be slower for the lower voltages.

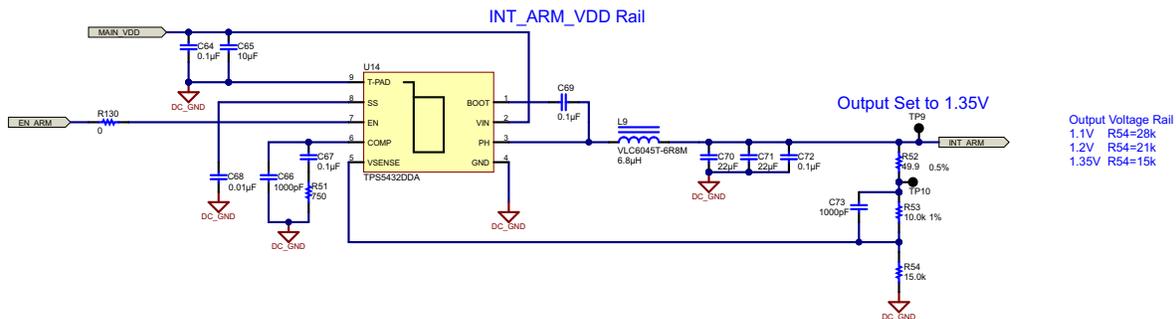


Figure 22. Power Module ARM Supply Circuit


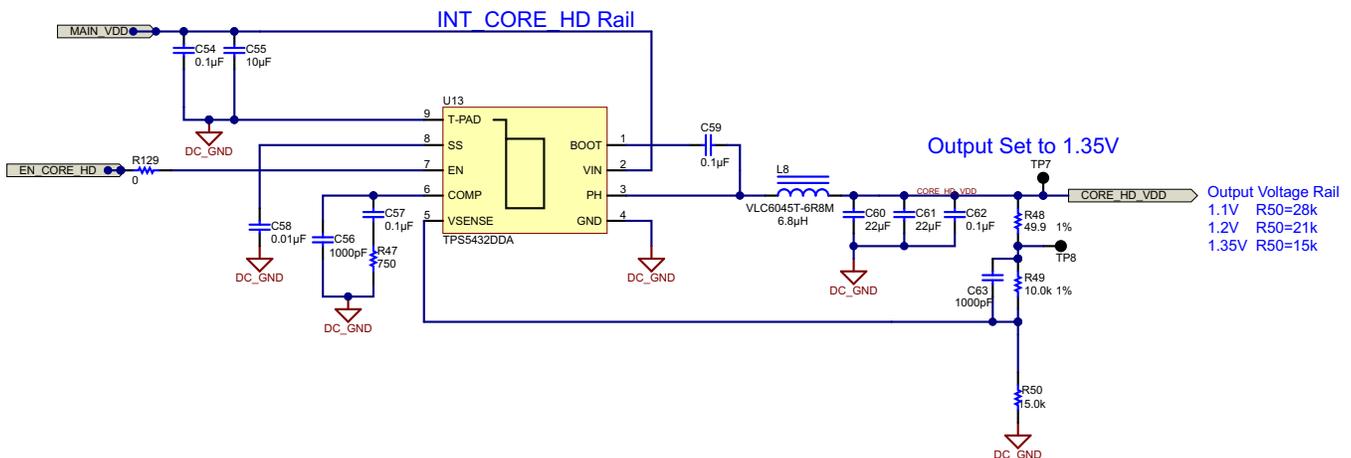


Figure 23. Power Module Core Supply Circuit

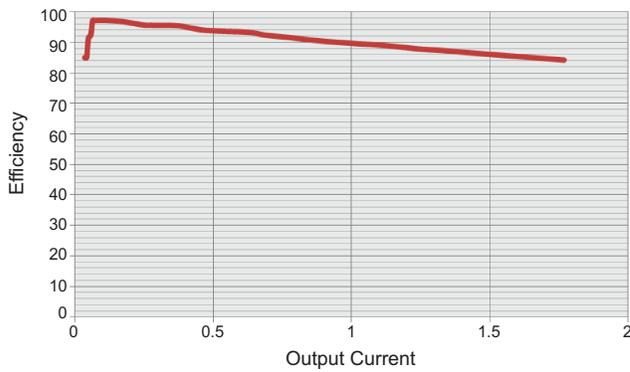
2.2.3.1 ARM Supply

The following graphs show the efficiency measurements for the ARM supply.




Output voltage = 1.2 V, input voltage = 5 V

Figure 24. ARM Supply Efficiency Versus Output Current

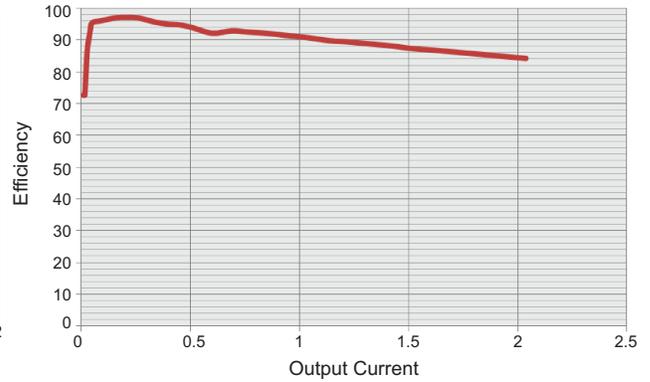


Output voltage = 1.35 V, input voltage = 5 V

Figure 25. ARM Supply Efficiency Versus Output Current

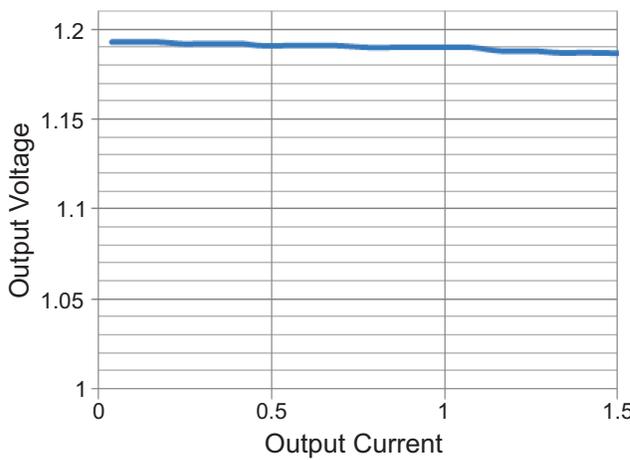

Output voltage = 1.2 V

Figure 26. Output Voltage Versus Load Current

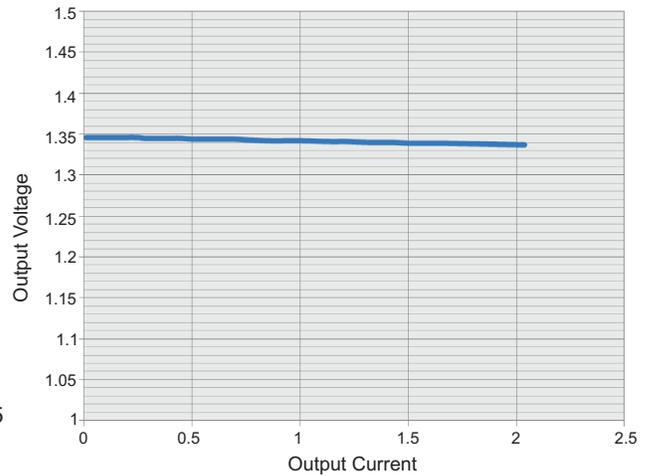


Output voltage = 1.35 V


Figure 27. Output Voltage Versus Load Current

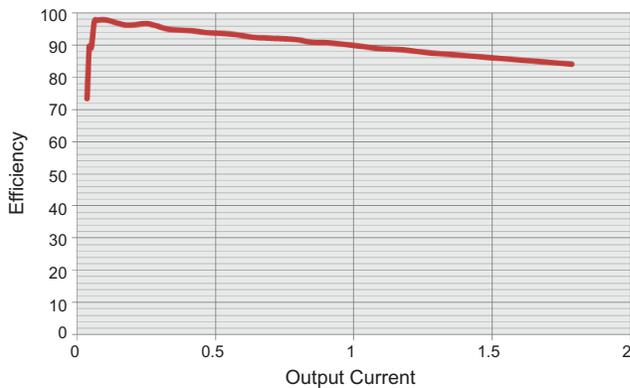2.2.3.2 Core Supply


The following graphs show the efficiency measurements for the Core supply.



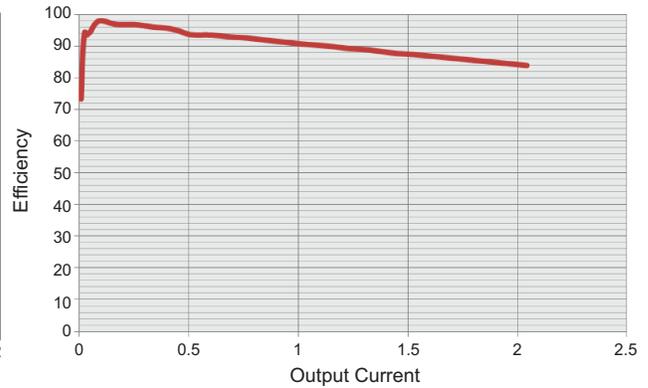
Output voltage = 1.2 V, input voltage = 5 V
Figure 28. Core Supply Efficiency Versus Output Current



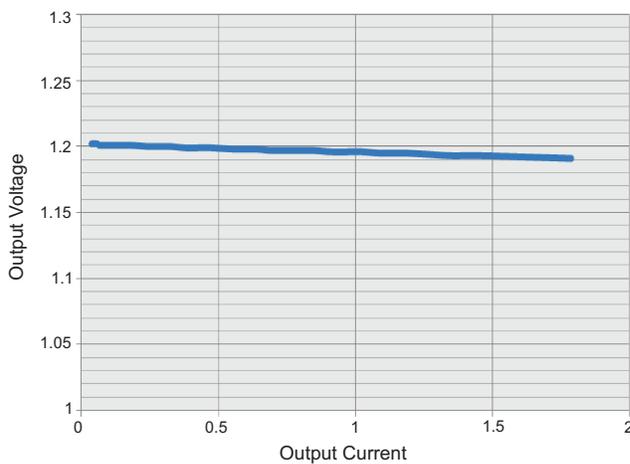Output voltage = 1.35 V, input voltage = 5 V
Figure 29. Core Supply Efficiency Versus Output Current



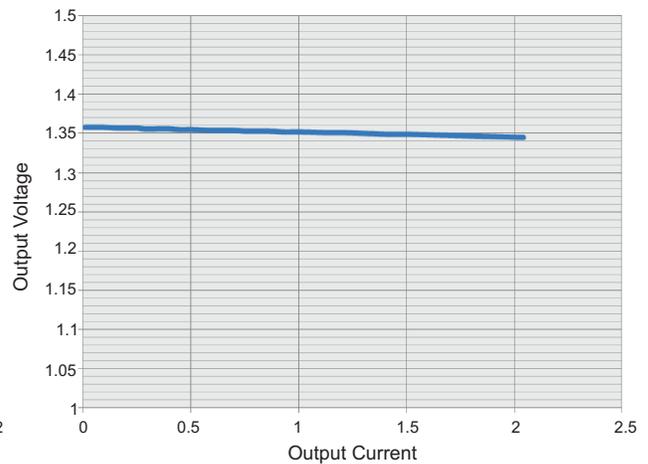Output voltage = 1.2 V
Figure 30. Output Voltage Versus Load Current



Output voltage = 1.35 V
Figure 31. Output Voltage Versus Load Current

The efficiencies for each circuit are about the same regardless of the output voltage setting. Output regulation is very good in all cases.

2.2.3.3 Rise Time

Rise Time for the Core supply is 3.2 ms and is 3.9 ms for the ARM supply.

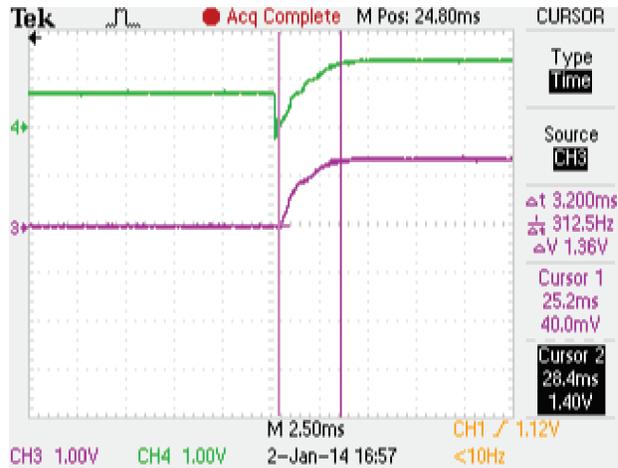


Figure 32. Rise Time — Core Supply

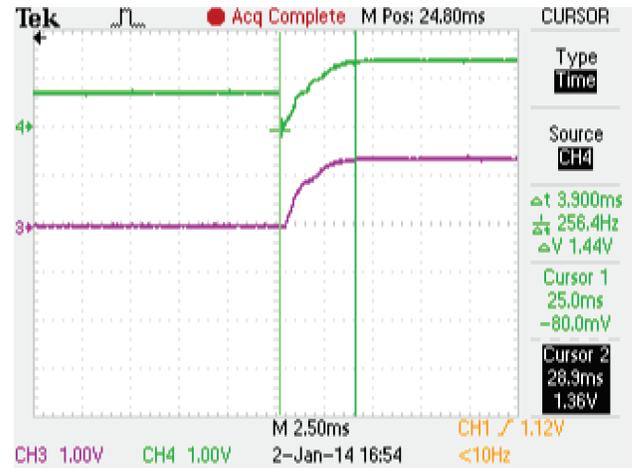


Figure 33. Rise Time — ARM Supply

2.2.3.4 In-System Performance

The two supplies have very different loads when the camera is operating. The Core supply has a larger load than the ARM supply. For a camera streaming 1080p at 30 Hz, the ARM supply output is 1.349 V, 160 mA, 0.216 W. The input power is 5.02 V, 46.5 mA, 0.233 W. ARM supply efficiency is 93%. For the Core supply, output power is 1.35 V, 726 mA, 0.98 W, while the input power was 5.02 V, 218 mA, 1.096 W. Core supply efficiency is 89%, which is in line with the value measured with a static load (see [Figure 29](#)). The two supplies could be combined into one supply circuit to save cost. The overall efficiency would be less because the higher load on one TPS5432 device.

2.2.4 Power Supply Sequencing

The DM385 device has a defined sequence for enabling the various power supplies. The DM385 device requires the supplies to be enabled in the following sequence:

1. 1.8-V IO supply
2. DDR supply
3. 3.3-V supply
4. Core and ARM supply

Several devices in the system create the power supply sequence. Part of this sequence occurs on the SAT0008 processor board because the DDR power supply is on that board. Figure 34 shows the DDR supply circuit.

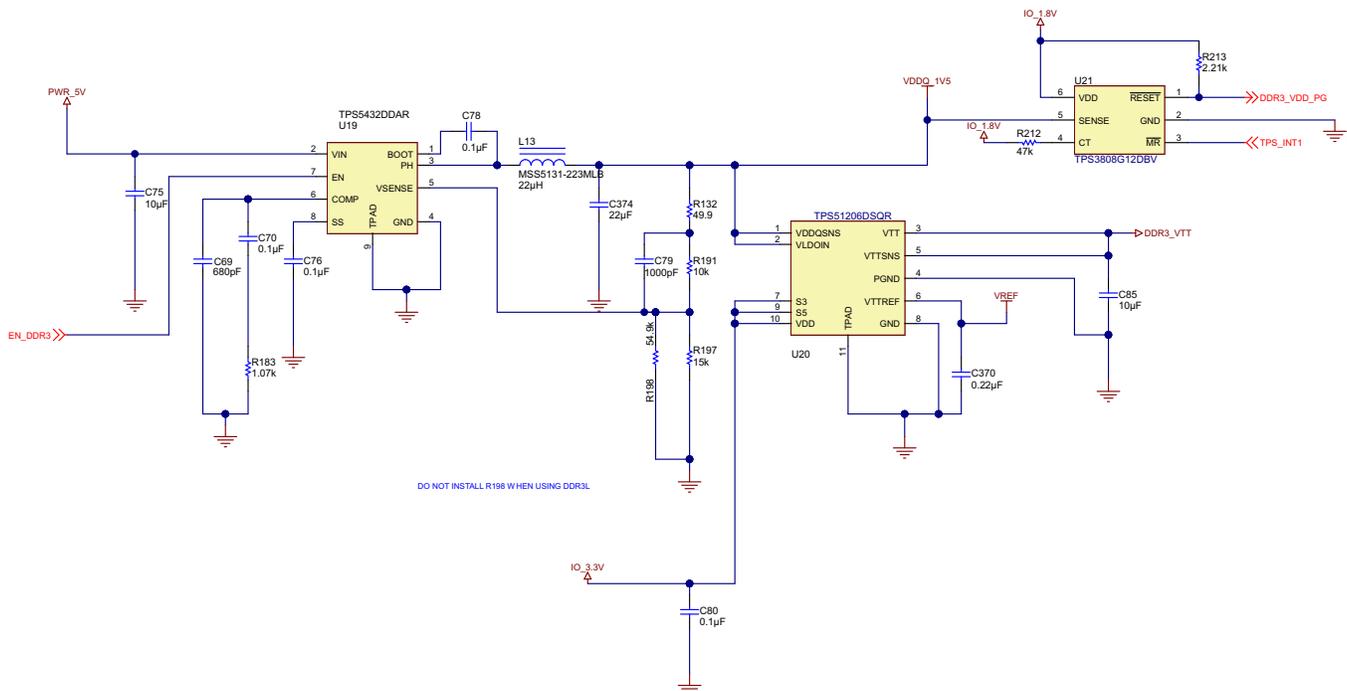


Figure 34. DDR3 Power Supply and Support Circuitry from the Processor Board

Figure 35 shows the portions of the sequencing circuit that are on the power module.

Several small supervisor components create the timing for the sequence. At the start, the common 5-V node (VOUT_POE) powers U7, a TPS3839G33 ultra-low power-supply voltage supervisor. This device has a threshold of 3 V (nominal). The nRESET output of U7 goes high between 120 ms and 300 ms after VOUT_POE reaches this threshold. nRESET going high enables the 1.8-V supply and supervisors U8 and U9, both of which are TPS3897-adjustable supervisor circuits. The output of U8 goes high when the SENSE pin reaches 0.5 V. U8 has a timing circuit that consists of R32, R33, and C32 connected to the 1.8-V output. This circuit delays the output of U8 for about 50 ms. After this 50-ms time delay, the SENSE_OUT pin, net EN_DDR3, goes high. This net connects through the boards to the enable pin on the DDR3 supply controller on the system processor board (see Figure 34). The DDR3 supply, featuring a TPS5432 controller and a TPS51206 DDR termination regulator, feeds the sense input of a TPS3808G12 programmable-delay supervisor (U21 on the processor board). The TPS3808G12 device has a 1.12-V threshold and can be programmed to have either a 300-ms delay (R212 = 47K as shown) or 20-ms (if R212 is not populated). The remaining output of this supervisor feeds back through the boards to enable the 3.3-V supply. When the 3.3-V supply turns on, U9 on the power module has a timing circuit consisting of R34, R35 and C33, similar to the U8 timing circuit previously described. This circuit delays the output of U9 for about 25 ms. When the output of U9 goes high, the Core and ARM supplies are enabled. When these supplies have stabilized, the DM385 begins to boot up. The whole process takes about 430 ms. The numbers in Figure 36 are based on measurements taken in an actual system.

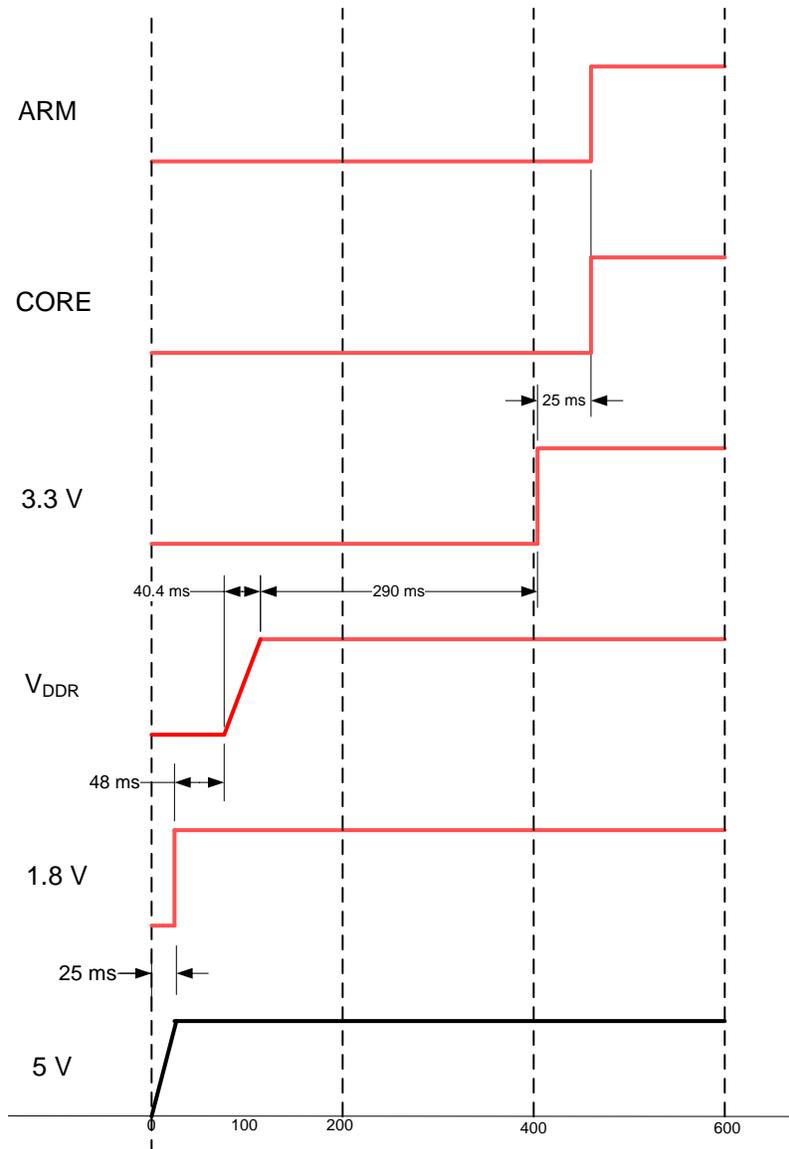


Figure 36. Power Supply Timing Sequence (Measured)

2.3 Other Circuits

There are several other circuits that make up the power module that provide specific peripheral functions for the DM385 IP Camera Reference Design. The following sections list these circuits.

2.3.1 RS485 Interface

Many security cameras are controlled by an RS485 two-wire serial interface. In this system, two SN74AVC2T45 level translators convert the 1.8-V signal level on the DM385 to the 3.3-V IO required by the SN65HVD11 RS485 transceiver. The output is on J5 which is shared with the alarm.

2.3.2 Alarm Interface

The alarm Interface has an optically-isolated output and two optically-isolated inputs. The optically-isolated inputs and output provide a means for the DM385 to send or receive interrupts to and from another device or camera.

2.3.3 Indicator Lights

The indicator lights are LEDs and associated power switches to indicate power ON, system errors, 1000-G Ethernet connection, or a LAN event.

2.3.4 TV Output

The TV output drives a BNC connector on the camera housing which allows the camera to be used as a standard definition security camera in an existing security system. The SD output is driven by an OPA360 device which is a low-power OPAMP designed specifically for driving a video output.

2.3.5 IRIS Driver

Two PWM signals from the DM385 control the IRIS output. The output is driven by a an LMV722 low-noise operational amplifier (op-amp).

2.3.6 Earphone Jack

The earphone jack is the audio output for the camera.

2.3.7 Battery Charger

A Lithium-Ion battery charger is included in the design for applications where a backup battery is desired. In the DM385 IP Camera Reference Design, this function is not used and the circuit is bypassed in the power module.

3 System Performance

System power consumption is the ultimate measure of a power supply design. For the DM385 IP Net Camera, the power consumption is very low although it is a function of the chosen image sensor module and the frame rate of the video. [Table 2](#) lists data received from three different image sensor modules, two different frame rates (30 Hz and 60Hz), and with the Core and ARM voltage set for 1.2-V for some of the 30-Hz tests. In all cases, the IP camera streams three video streams, 1080p H.264, 1080p MPEG4, and D1 30Hz. The image sensor modules are available from Leopard Imaging. These image modules are based on the Aptina AR0330 and AR0331 Imagers.

Table 2. System Performance⁽¹⁾

Sensor Type	Module Output Type	Video Frame Rate	Ethernet Link Type	CORE and ARM Voltage	Input Supply	Power Consumption
AR0330	MIPI	60 Hz	1000 Mb	1.35 V	5 V	3.59 W
		60 Hz	100 Mb	1.35 V	5 V	3.35 W
		30 Hz	100 Mb	1.35 V	5 V	2.51 W
		30 Hz	100 Mb	1.2 V	5 V	2.21 W
AR0331	LVDS	30 Hz	100 Mb	1.2 V	5 V	2.57 W
	FPGA	30 Hz	100 Mb	1.2 V	5 V	2.75 W
		30 Hz	100 Mb	1.35 V	5 V	3.13 W
		30 Hz	100 Mb	1.35 V	12 V	3.43 W
		60 Hz	1000 Mb	1.35 V	5 V	3.48 W
		60 Hz	1000 Mb	1.35 V	12 V	3.82 W
		60 Hz	1000 Mb	1.35 V	PoE	3.77 W

⁽¹⁾ The AR0331 LVDS sensor is module LI-CAM-AR0331-324-1.8 V1.1. The AR0331 FPGA sensor is module LI-CAM-AR0331-1.8 V1.0.

As listed in [Table 2](#), the best result is with the sensor module that has the MIPI, followed by LVDS and the FPGA version. The best power performance is with the 5-V input, 1.2-V Core and ARM voltages, the MIPI sensor module, and a frame rate of 30 Hz. The system power increases significantly for the Gigabit Ethernet connection: approximately 250 mW for the AR0330 case.

4 About the Author

Mark Knapp is a Systems Architect at Texas Instruments Incorporated where he is responsible for developing reference design solutions for the industrial segment. He has an extensive background in video camera systems and infrared imaging systems for Military, Automotive, and Industrial applications. Mark earned his BSEE at the University of Michigan-Dearborn and his MSEE at the University of Texas at Dallas.

EVALUATION BOARD/KIT/MODULE (EVM) ADDITIONAL TERMS

Texas Instruments (TI) provides the enclosed Evaluation Board/Kit/Module (EVM) under the following conditions:

The user assumes all responsibility and liability for proper and safe handling of the goods. Further, the user indemnifies TI from all claims arising from the handling or use of the goods.

Should this evaluation board/kit not meet the specifications indicated in the User's Guide, the board/kit may be returned within 30 days from the date of delivery for a full refund. THE FOREGOING LIMITED WARRANTY IS THE EXCLUSIVE WARRANTY MADE BY SELLER TO BUYER AND IS IN LIEU OF ALL OTHER WARRANTIES, EXPRESSED, IMPLIED, OR STATUTORY, INCLUDING ANY WARRANTY OF MERCHANTABILITY OR FITNESS FOR ANY PARTICULAR PURPOSE. EXCEPT TO THE EXTENT OF THE INDEMNITY SET FORTH ABOVE, NEITHER PARTY SHALL BE LIABLE TO THE OTHER FOR ANY INDIRECT, SPECIAL, INCIDENTAL, OR CONSEQUENTIAL DAMAGES.

Please read the User's Guide and, specifically, the Warnings and Restrictions notice in the User's Guide prior to handling the product. This notice contains important safety information about temperatures and voltages. For additional information on TI's environmental and/or safety programs, please visit www.ti.com/esh or contact TI.

No license is granted under any patent right or other intellectual property right of TI covering or relating to any machine, process, or combination in which such TI products or services might be or are used. TI currently deals with a variety of customers for products, and therefore our arrangement with the user is not exclusive. TI assumes no liability for applications assistance, customer product design, software performance, or infringement of patents or services described herein.

REGULATORY COMPLIANCE INFORMATION

As noted in the EVM User's Guide and/or EVM itself, this EVM and/or accompanying hardware may or may not be subject to the Federal Communications Commission (FCC) and Industry Canada (IC) rules.

For EVMs **not** subject to the above rules, this evaluation board/kit/module is intended for use for ENGINEERING DEVELOPMENT, DEMONSTRATION OR EVALUATION PURPOSES ONLY and is not considered by TI to be a finished end product fit for general consumer use. It generates, uses, and can radiate radio frequency energy and has not been tested for compliance with the limits of computing devices pursuant to part 15 of FCC or ICES-003 rules, which are designed to provide reasonable protection against radio frequency interference. Operation of the equipment may cause interference with radio communications, in which case the user at his own expense will be required to take whatever measures may be required to correct this interference.

General Statement for EVMs including a radio

User Power/Frequency Use Obligations: This radio is intended for development/professional use only in legally allocated frequency and power limits. Any use of radio frequencies and/or power availability of this EVM and its development application(s) must comply with local laws governing radio spectrum allocation and power limits for this evaluation module. It is the user's sole responsibility to only operate this radio in legally acceptable frequency space and within legally mandated power limitations. Any exceptions to this are strictly prohibited and unauthorized by Texas Instruments unless user has obtained appropriate experimental/development licenses from local regulatory authorities, which is responsibility of user including its acceptable authorization.

For EVMs annotated as FCC – FEDERAL COMMUNICATIONS COMMISSION Part 15 Compliant

Caution

This device complies with part 15 of the FCC Rules. Operation is subject to the following two conditions: (1) This device may not cause harmful interference, and (2) this device must accept any interference received, including interference that may cause undesired operation.

Changes or modifications not expressly approved by the party responsible for compliance could void the user's authority to operate the equipment.

FCC Interference Statement for Class A EVM devices

This equipment has been tested and found to comply with the limits for a Class A digital device, pursuant to part 15 of the FCC Rules. These limits are designed to provide reasonable protection against harmful interference when the equipment is operated in a commercial environment. This equipment generates, uses, and can radiate radio frequency energy and, if not installed and used in accordance with the instruction manual, may cause harmful interference to radio communications. Operation of this equipment in a residential area is likely to cause harmful interference in which case the user will be required to correct the interference at his own expense.

FCC Interference Statement for Class B EVM devices

This equipment has been tested and found to comply with the limits for a Class B digital device, pursuant to part 15 of the FCC Rules. These limits are designed to provide reasonable protection against harmful interference in a residential installation. This equipment generates, uses and can radiate radio frequency energy and, if not installed and used in accordance with the instructions, may cause harmful interference to radio communications. However, there is no guarantee that interference will not occur in a particular installation. If this equipment does cause harmful interference to radio or television reception, which can be determined by turning the equipment off and on, the user is encouraged to try to correct the interference by one or more of the following measures:

- Reorient or relocate the receiving antenna.
- Increase the separation between the equipment and receiver.
- Connect the equipment into an outlet on a circuit different from that to which the receiver is connected.
- Consult the dealer or an experienced radio/TV technician for help.

For EVMs annotated as IC – INDUSTRY CANADA Compliant

This Class A or B digital apparatus complies with Canadian ICES-003.

Changes or modifications not expressly approved by the party responsible for compliance could void the user's authority to operate the equipment.

Concerning EVMs including radio transmitters

This device complies with Industry Canada licence-exempt RSS standard(s). Operation is subject to the following two conditions: (1) this device may not cause interference, and (2) this device must accept any interference, including interference that may cause undesired operation of the device.

Concerning EVMs including detachable antennas

Under Industry Canada regulations, this radio transmitter may only operate using an antenna of a type and maximum (or lesser) gain approved for the transmitter by Industry Canada. To reduce potential radio interference to other users, the antenna type and its gain should be so chosen that the equivalent isotropically radiated power (e.i.r.p.) is not more than that necessary for successful communication.

This radio transmitter has been approved by Industry Canada to operate with the antenna types listed in the user guide with the maximum permissible gain and required antenna impedance for each antenna type indicated. Antenna types not included in this list, having a gain greater than the maximum gain indicated for that type, are strictly prohibited for use with this device.

Cet appareil numérique de la classe A ou B est conforme à la norme NMB-003 du Canada.

Les changements ou les modifications pas expressément approuvés par la partie responsable de la conformité ont pu vider l'autorité de l'utilisateur pour actionner l'équipement.

Concernant les EVMs avec appareils radio

Le présent appareil est conforme aux CNR d'Industrie Canada applicables aux appareils radio exempts de licence. L'exploitation est autorisée aux deux conditions suivantes : (1) l'appareil ne doit pas produire de brouillage, et (2) l'utilisateur de l'appareil doit accepter tout brouillage radioélectrique subi, même si le brouillage est susceptible d'en compromettre le fonctionnement.

Concernant les EVMs avec antennes détachables

Conformément à la réglementation d'Industrie Canada, le présent émetteur radio peut fonctionner avec une antenne d'un type et d'un gain maximal (ou inférieur) approuvé pour l'émetteur par Industrie Canada. Dans le but de réduire les risques de brouillage radioélectrique à l'intention des autres utilisateurs, il faut choisir le type d'antenne et son gain de sorte que la puissance isotrope rayonnée équivalente (p.i.r.e.) ne dépasse pas l'intensité nécessaire à l'établissement d'une communication satisfaisante.

Le présent émetteur radio a été approuvé par Industrie Canada pour fonctionner avec les types d'antenne énumérés dans le manuel d'usage et ayant un gain admissible maximal et l'impédance requise pour chaque type d'antenne. Les types d'antenne non inclus dans cette liste, ou dont le gain est supérieur au gain maximal indiqué, sont strictement interdits pour l'exploitation de l'émetteur.

【Important Notice for Users of EVMs for RF Products in Japan】

This development kit is NOT certified as Confirming to Technical Regulations of Radio Law of Japan

If you use this product in Japan, you are required by Radio Law of Japan to follow the instructions below with respect to this product:

1. Use this product in a shielded room or any other test facility as defined in the notification #173 issued by Ministry of Internal Affairs and Communications on March 28, 2006, based on Sub-section 1.1 of Article 6 of the Ministry's Rule for Enforcement of Radio Law of Japan,
2. Use this product only after you obtained the license of Test Radio Station as provided in Radio Law of Japan with respect to this product, or
3. Use of this product only after you obtained the Technical Regulations Conformity Certification as provided in Radio Law of Japan with respect to this product. Also, please do not transfer this product, unless you give the same notice above to the transferee. Please note that if you could not follow the instructions above, you will be subject to penalties of Radio Law of Japan.

Texas Instruments Japan Limited
(address) 24-1, Nishi-Shinjuku 6 chome, Shinjuku-ku, Tokyo, Japan

<http://www.tij.co.jp>

【無線電波を送信する製品の開発キットをお使いになる際の注意事項】

本開発キットは技術基準適合証明を受けておりません。

本製品のご使用に際しては、電波法遵守のため、以下のいずれかの措置を取っていただく必要がありますのでご注意ください。

1. 電波法施行規則第6条第1項第1号に基づく平成18年3月28日総務省告示第173号で定められた電波暗室等の試験設備でご使用いただく。
2. 実験局の免許を取得後ご使用いただく。
3. 技術基準適合証明を取得後ご使用いただく。

なお、本製品は、上記の「ご使用にあたっての注意」を譲渡先、移転先に通知しない限り、譲渡、移転できないものとします。

上記を遵守頂けない場合は、電波法の罰則が適用される可能性があることをご留意ください。

日本テキサス・インスツルメンツ株式会社

東京都新宿区西新宿 6 丁目 2 4 番 1 号

西新宿三井ビル

<http://www.tij.co.jp>

EVALUATION BOARD/KIT/MODULE (EVM) WARNINGS, RESTRICTIONS AND DISCLAIMERS

For Feasibility Evaluation Only, in Laboratory/Development Environments. Unless otherwise indicated, this EVM is not a finished electrical equipment and not intended for consumer use. It is intended solely for use for preliminary feasibility evaluation in laboratory/development environments by technically qualified electronics experts who are familiar with the dangers and application risks associated with handling electrical mechanical components, systems and subsystems. It should not be used as all or part of a finished end product.

Your Sole Responsibility and Risk. You acknowledge, represent and agree that:

1. You have unique knowledge concerning Federal, State and local regulatory requirements (including but not limited to Food and Drug Administration regulations, if applicable) which relate to your products and which relate to your use (and/or that of your employees, affiliates, contractors or designees) of the EVM for evaluation, testing and other purposes.
2. You have full and exclusive responsibility to assure the safety and compliance of your products with all such laws and other applicable regulatory requirements, and also to assure the safety of any activities to be conducted by you and/or your employees, affiliates, contractors or designees, using the EVM. Further, you are responsible to assure that any interfaces (electronic and/or mechanical) between the EVM and any human body are designed with suitable isolation and means to safely limit accessible leakage currents to minimize the risk of electrical shock hazard.
3. Since the EVM is not a completed product, it may not meet all applicable regulatory and safety compliance standards (such as UL, CSA, VDE, CE, RoHS and WEEE) which may normally be associated with similar items. You assume full responsibility to determine and/or assure compliance with any such standards and related certifications as may be applicable. You will employ reasonable safeguards to ensure that your use of the EVM will not result in any property damage, injury or death, even if the EVM should fail to perform as described or expected.
4. You will take care of proper disposal and recycling of the EVM's electronic components and packing materials.

Certain Instructions. It is important to operate this EVM within TI's recommended specifications and environmental considerations per the user guidelines. Exceeding the specified EVM ratings (including but not limited to input and output voltage, current, power, and environmental ranges) may cause property damage, personal injury or death. If there are questions concerning these ratings please contact a TI field representative prior to connecting interface electronics including input power and intended loads. Any loads applied outside of the specified output range may result in unintended and/or inaccurate operation and/or possible permanent damage to the EVM and/or interface electronics. Please consult the EVM User's Guide prior to connecting any load to the EVM output. If there is uncertainty as to the load specification, please contact a TI field representative. During normal operation, some circuit components may have case temperatures greater than 60°C as long as the input and output are maintained at a normal ambient operating temperature. These components include but are not limited to linear regulators, switching transistors, pass transistors, and current sense resistors which can be identified using the EVM schematic located in the EVM User's Guide. When placing measurement probes near these devices during normal operation, please be aware that these devices may be very warm to the touch. As with all electronic evaluation tools, only qualified personnel knowledgeable in electronic measurement and diagnostics normally found in development environments should use these EVMs.

Agreement to Defend, Indemnify and Hold Harmless. You agree to defend, indemnify and hold TI, its licensors and their representatives harmless from and against any and all claims, damages, losses, expenses, costs and liabilities (collectively, "Claims") arising out of or in connection with any use of the EVM that is not in accordance with the terms of the agreement. This obligation shall apply whether Claims arise under law of tort or contract or any other legal theory, and even if the EVM fails to perform as described or expected.

Safety-Critical or Life-Critical Applications. If you intend to evaluate the components for possible use in safety critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, such as devices which are classified as FDA Class III or similar classification, then you must specifically notify TI of such intent and enter into a separate Assurance and Indemnity Agreement.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2014, Texas Instruments Incorporated

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.