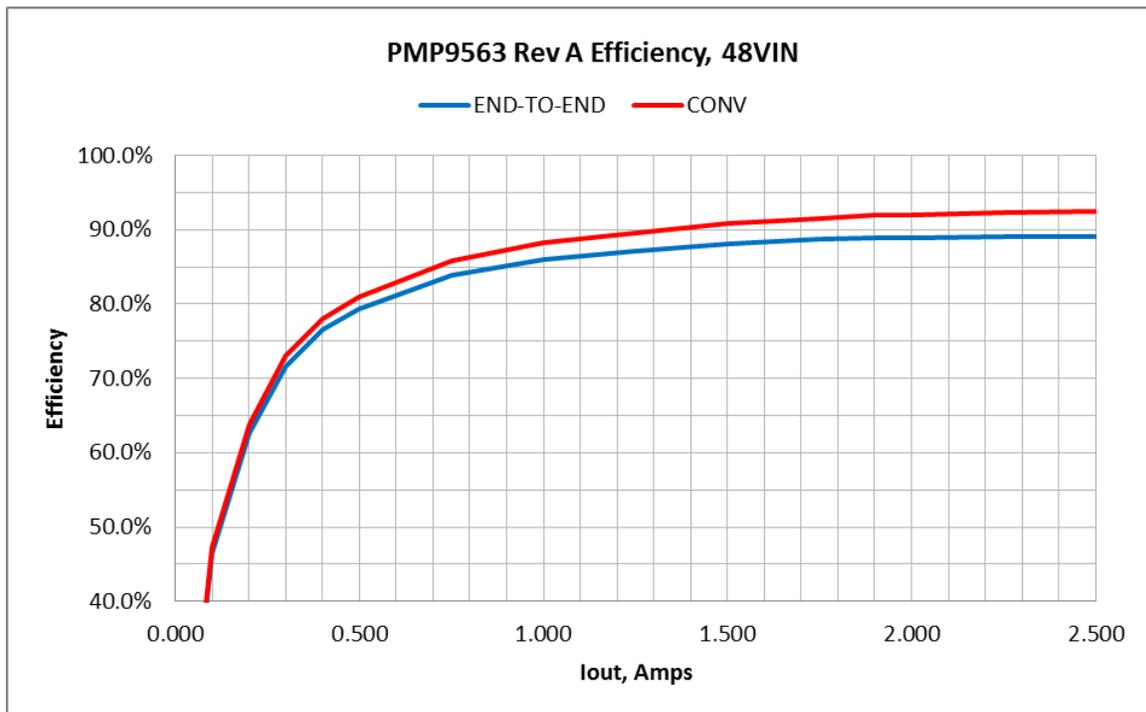


All testing performed with 48VIN, 1.9A load and 20MHz BW unless otherwise noted.

**Efficiency**


The efficiency is shown below:

<b>J4</b>	<b>J4</b>	<b>J1</b>	<b>J1</b>	<b>J1</b>	<b>CONV</b>	<b>CONV</b>
<b>Iout</b>	<b>Vout</b>	<b>Iin</b>	<b>Vin</b>	<b>Eff</b>	<b>Vin</b>	<b>Eff</b>
0.000	12.03	0.028	48.00	0.0%	47.29	0.0%
0.100	12.03	0.054	48.00	46.4%	47.22	47.2%
0.200	12.03	0.080	48.00	62.7%	47.16	63.8%
0.300	12.03	0.105	48.00	71.6%	47.11	73.0%
0.400	12.03	0.131	48.00	76.5%	47.07	78.0%
0.500	12.03	0.158	48.00	79.3%	47.02	81.0%
0.750	12.02	0.224	48.00	83.8%	46.91	85.8%
1.000	12.02	0.291	48.00	86.1%	46.81	88.2%
1.250	12.02	0.359	48.00	87.2%	46.70	89.6%
1.500	12.02	0.426	48.00	88.2%	46.60	90.8%
1.750	12.02	0.494	48.00	88.7%	46.50	91.6%
1.900	12.02	0.535	48.00	88.9%	46.43	91.9%
2.000	12.02	0.563	48.00	89.0%	46.38	92.1%
2.250	12.02	0.633	48.00	89.0%	46.30	92.3%
2.500	12.02	0.703	48.00	89.1%	46.22	92.5%



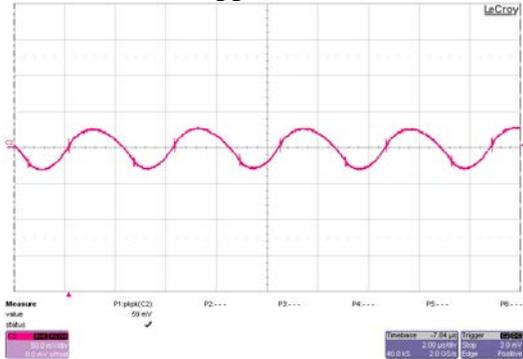
### Ripple and Noise

Output Ripple (C20), 50mV/div  
Measured 59mVpp:




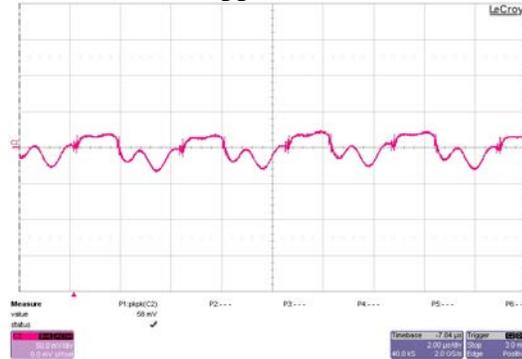Input Ripple (C7), 50mV/div  
Measured 58mVpp:


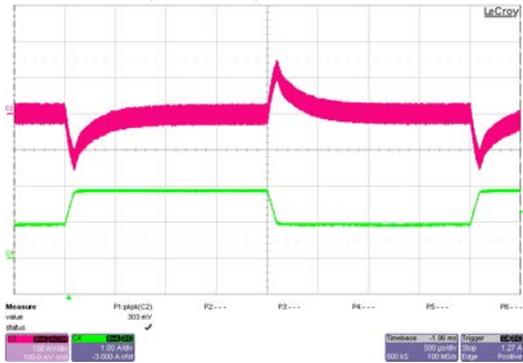
### Dynamic Loading

Output Load Step; 0.95A to 1.9A load step; Slew Rate = 10mA/usec  
100mV/div, 1A/div, 500usec/div: Measured 303mVpp across C20:




### Turn On Response

1.9A Load, 1msec/div, 2V/div:




0A Load, 1msec.div, 2V/div:

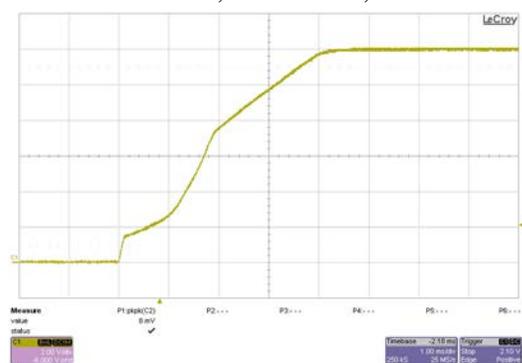

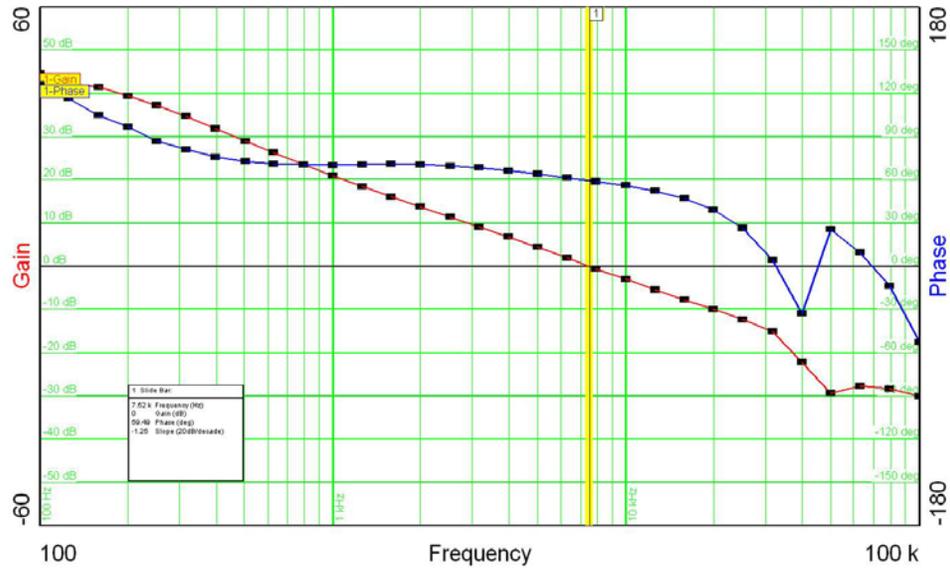**Loop Stability**

The measured Bode plot of the converter is shown below:




BW: 7.5KHz      PM: 59 deg      GM: 15dB


**Photo**

(Converter fits in 60x30mm area)

Top:

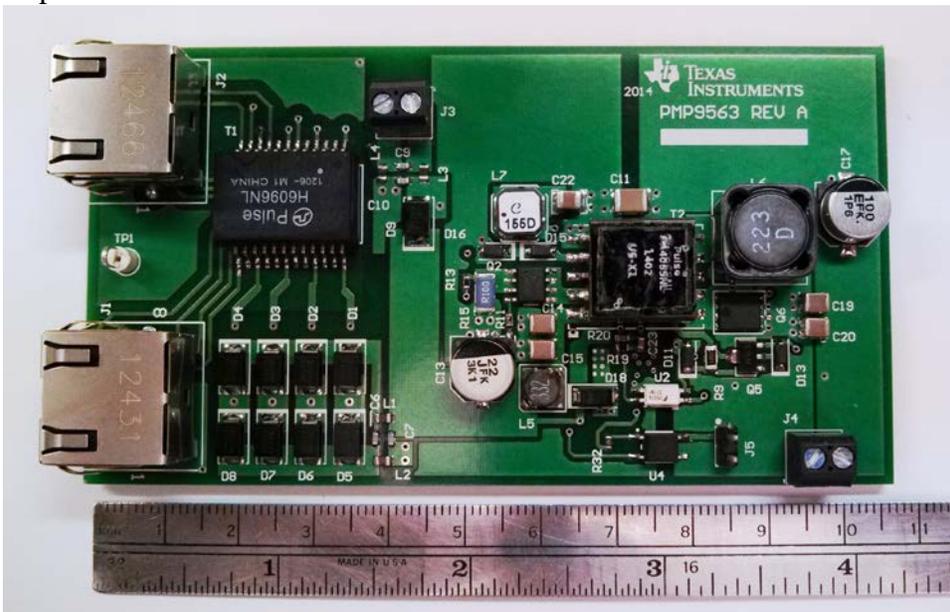

Bottom:

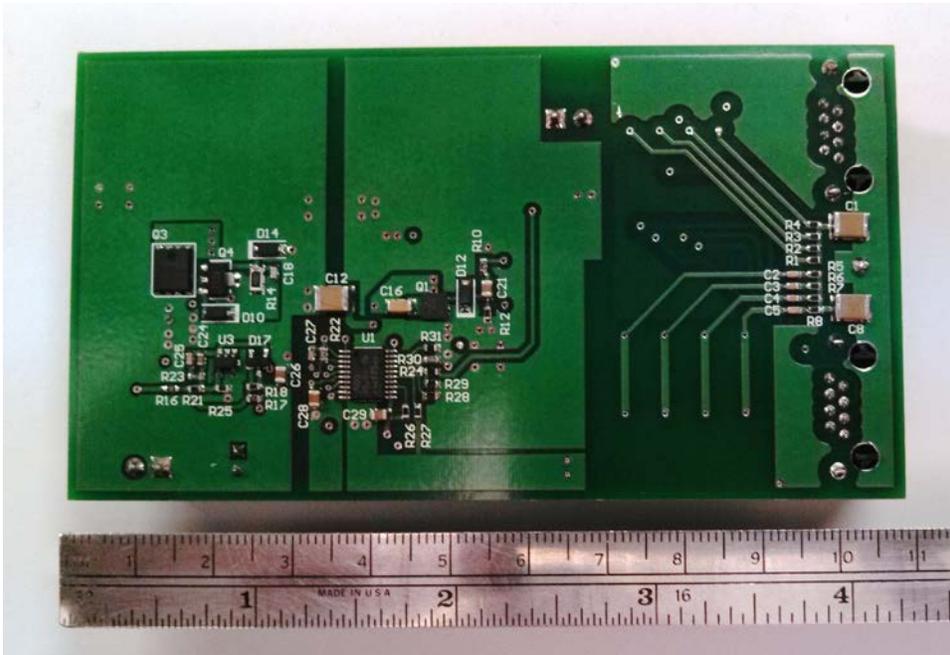

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated