

TIDA-00539 UPOE High-Efficiency Flyback Converter (19V/2.3A) for Forced 4-Pair PoE PD Applications

1 Introduction

TIDA-00539 is a high power four-pair solution for Power-over-Ethernet (PoE) applications requiring power in excess as defined in the current IEEE 802.3at standard. It is compliant with Cisco UPOE Forced Four-Pair designs.

2 Configurable features

1.1 Features

- Excellent efficiency, driven, synchronous flyback design.
- Forced Four-Pair UPOE compliant
- 19V @ 2.3A DC output (2.9A capable)

1.2 Applications

- Universal Power Over Ethernet (UPOE) Compliant Devices
- Video and VoIP telephones
- Multiband access points
- Security cameras
- Pico-base stations


3 Electrical specifications

TIDA-00539 Electrical and Performance Specifications

⁽¹⁾Per TPS2378 PD


Parameter	Condition	Min	Typ	Max	Units	
Power Interface						
Input Voltage	Applied to the power pins of connectors J1 or J3	42.5	-	57	Volts	
Operating Voltage ⁽¹⁾	After start up.	30	-	57		
Input UVLO, POE input J1 ⁽¹⁾	Rising input voltage	-	-	40		
	Falling input voltage	30	-	-		
Detection voltage ⁽¹⁾	@ device terminals	1.4	-	10.1		
Classification voltage ⁽¹⁾	@ device terminals	11.9	-	23.0		
Classification current ⁽¹⁾	Rclass = 63.4 ohms	38	-	42	mA	
Inrush current-limit ⁽¹⁾		100	-	180		
Operating current-limit ⁽¹⁾		850	-	1200		
DC/DC Converter						
Output Voltage	$42.5 \leq V_{in} \leq 57V$, ILOAD \leq ILOAD (max)	19V output	19.01	19.04	19.07	Volts
Output Current	$42.5 \leq V_{in} \leq 57V$	19V output	-	-	2.9	Amps
Output ripple voltage, pk-to-pk	$V_{in} = 48V$, ILOAD = 2.9A	19V output	-	225	-	mV
Efficiency, dc-dc converter	$V_{in} = 48V$, ILOAD = 2.9A	19V output	-	93	-	%
Efficiency, end-to-end	$V_{in} = 48V$, ILOAD = 2.9A	19V output	-	90	-	%
Switching frequency		225	-	270		kHz

4 Efficiency

 


5 Load Regulation

Load regulation is less than +/-20mV.

 


6 Line Regulation

 


7 Start up

 The below graph shows startup of the converter and subsequent current starting between the two PDs for a 26W output load.




8 Switch Node Waveforms

 The below waveform shows the primary FET gate drive voltage and VDS voltage at 48V input and 2.9A output current.




 The below waveform shows the synch FET gate drive voltage and VDS voltage at 48V input and 2.9A output current.



9 Output Ripple Voltage

 The 19V output ripple voltage is shown in the scope plot below. The waveform was taken with the output loaded to 2.9A. $V_{in} = 48V$.




10 Load Delay Circuit

IEEE standard requires at startup, the PD does not consume more than 13W for 80ms. Typically, there are provisions (startup delays) in the end-product load that satisfies this requirement.


Resistive loads are typically used for evaluation. The main purpose of the Load Delay Circuit is to delay a high-current resistive load and prevent PSE hiccup during startup.

 The 19V output voltage is shown in the scope plot below. There is 230ms delay before the load current is enabled. This can be adjusted through C39. The waveform was taken with the output loaded to 2.4A and the Load Delay Circuit enabled. $V_{in} = 48V$.



11 Load Transients

 
The scope plots below shows the 19V output voltage when the load current is pulsed from 0.29 to 2.9A at a 300A/ms slew rate. Vin = 48V.



12 Control Loop Gain / Stability

The table below shows the loop gain and phase margin. The output was loaded to 2.9A with a resistive load.

Input voltage	48VDC	
Gain/Phase	Crossover	Phase Margin
TIDA-00539	7kHz	80°

 

13 Thermal

The image below shows the thermal performance of TIDA-00539 at full load with 48V input.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated