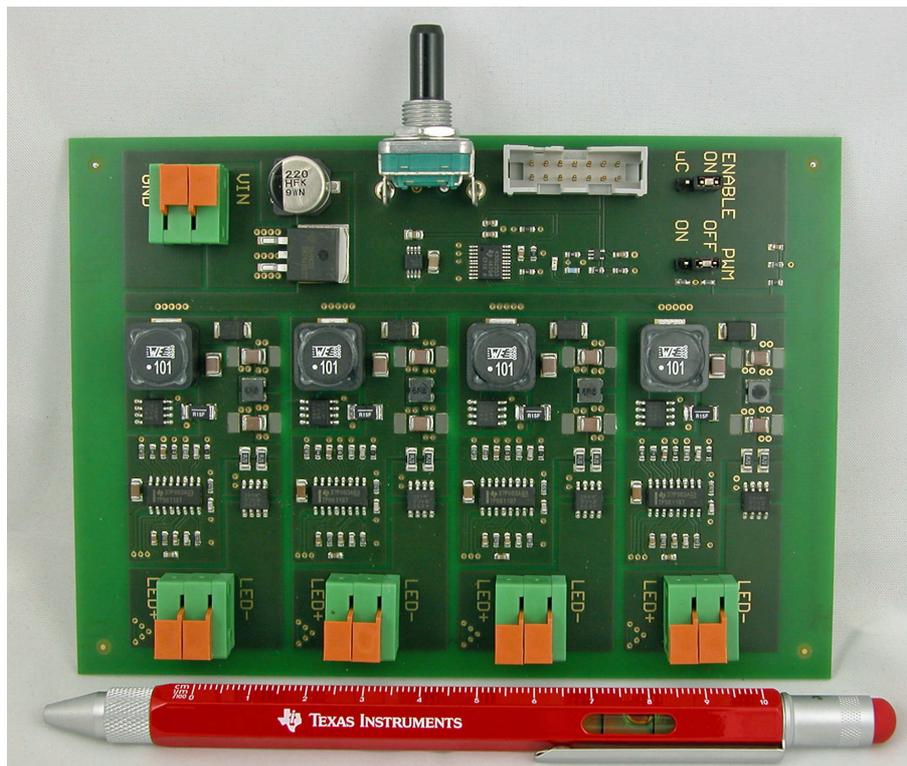


4-Channel Boost LED-Driver with Dimming

- Input 10..30V DC
- Output 4x 500mA @ 40V max.
- Controller TPS61197
- Free-Running switching frequency of 350 kHz
- Working in continuous conduction mode
- Reverse polarity protection with “ideal diode” SM74611
- PWM dimming signal generated by MSP430G2553



1 Startup

The startup waveform of a single converter is shown in Figure 1. The input voltage is set at 20.0V with 500mA @ 30V on the output.

Channel C1: **20.0V Input voltage**
5V/div, 5ms/div

Channel C2: **500mA Output current**
200mA/div, 5ms/div

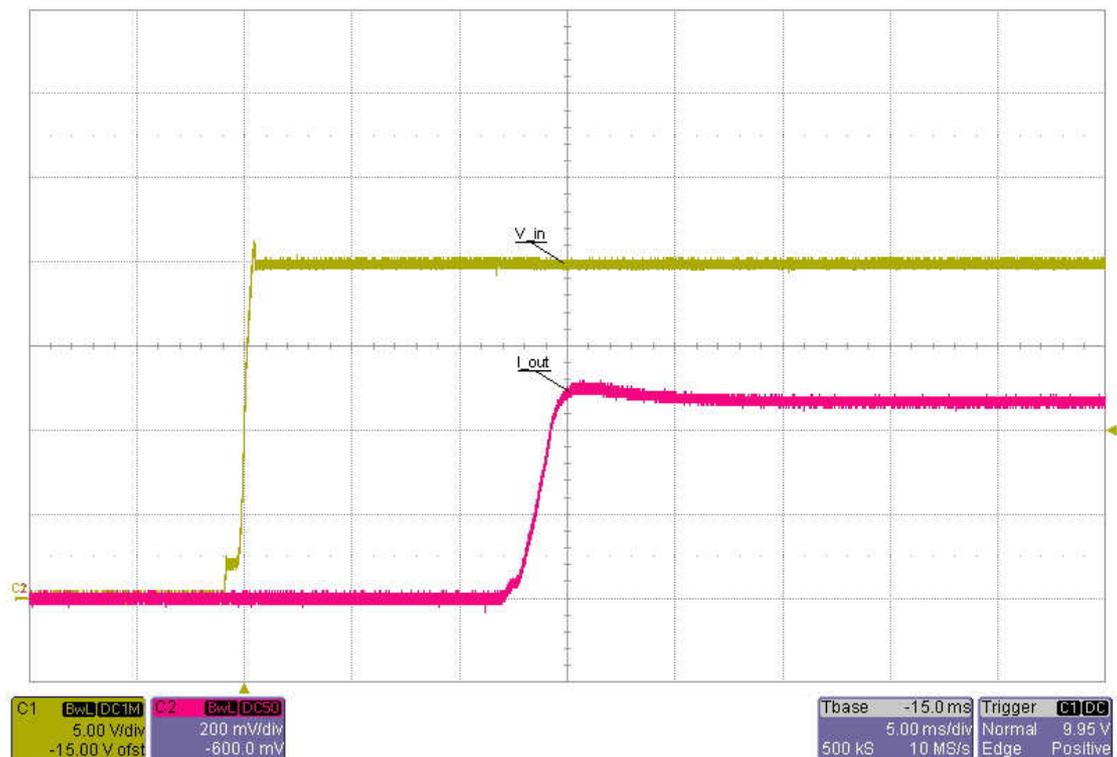


Figure 1

2 Shutdown

The shutdown waveform of a single converter is shown in Figure 2. The input voltage is set at 20.0V with 500mA @ 30V on the output.

Channel C1: **20.0V Input voltage**
5V/div, 5ms/div

Channel C2: **500mA Output current**
200mA/div, 5ms/div

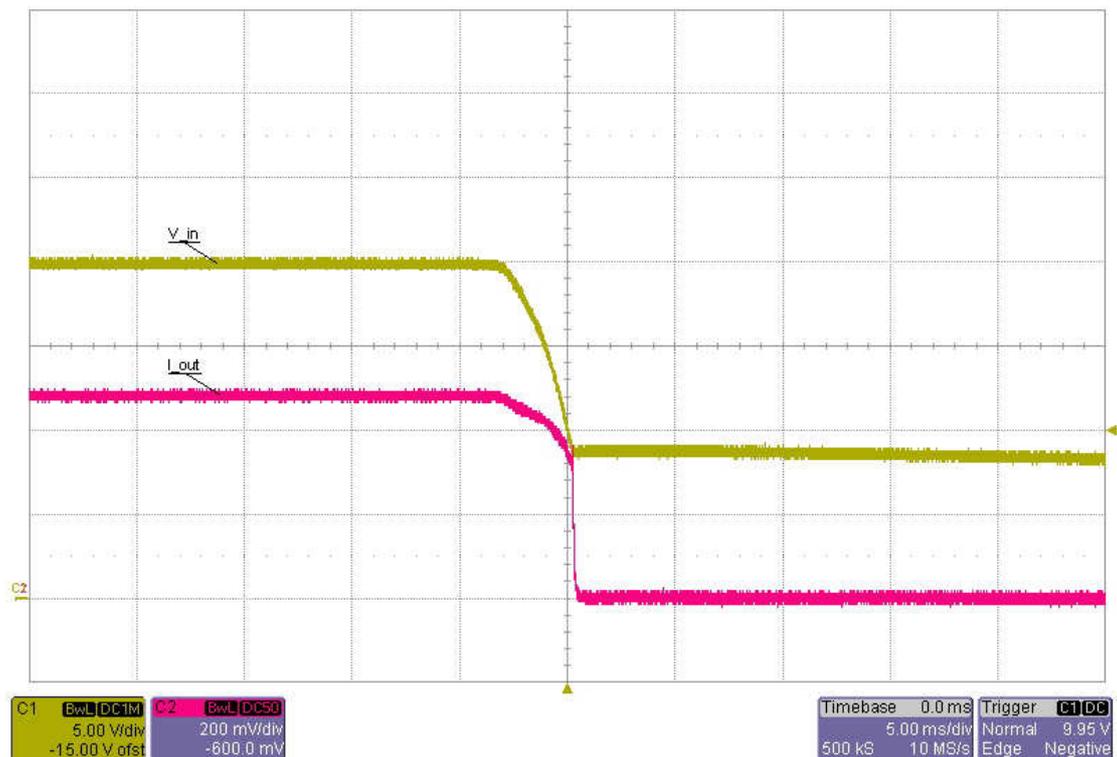


Figure 2

3 Efficiency & Load Regulation

The efficiency and load regulation of a single converter are shown in Figure 3 and Figure 4.

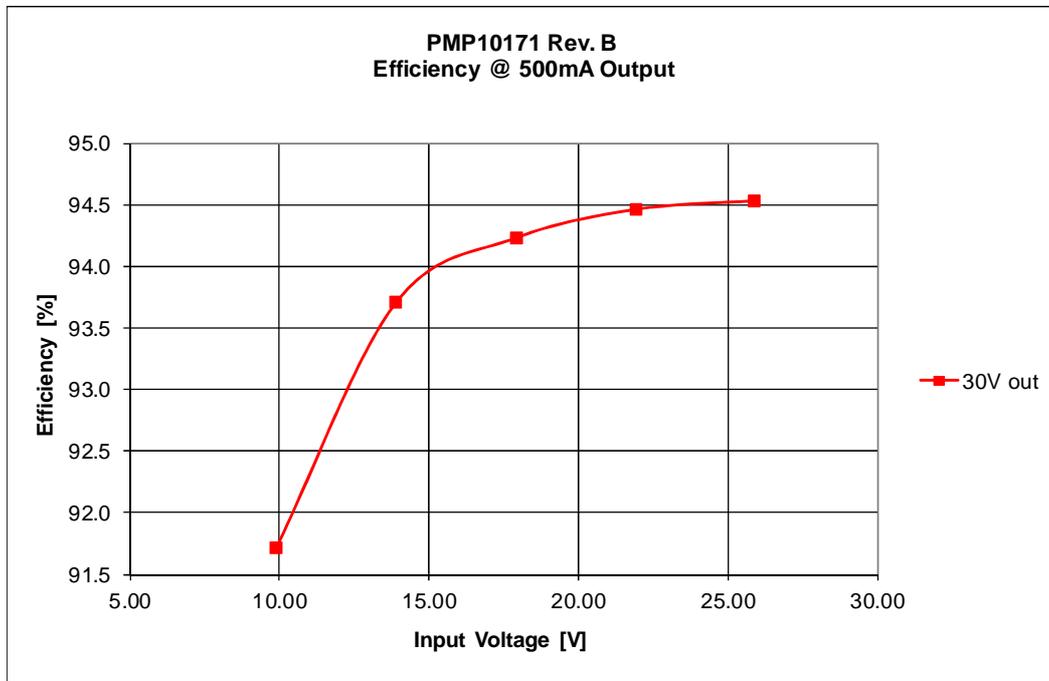


Figure 3

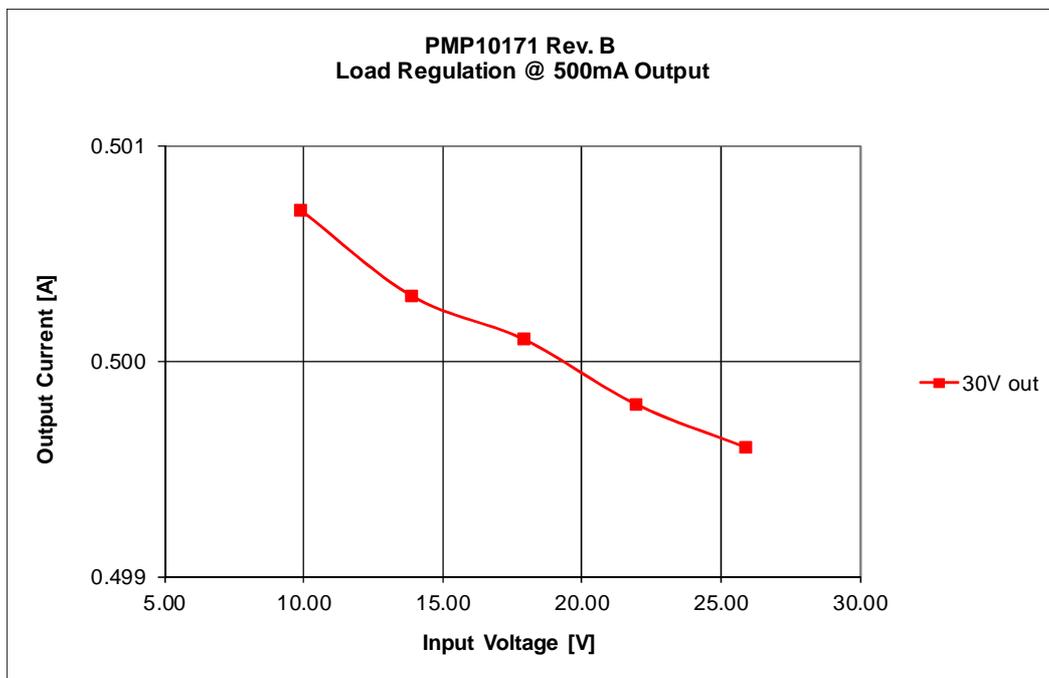


Figure 4

4 Input Ripple

The input ripple voltage for a single converter at 500mA @ 30V load is shown in Figure 5.

Channel M1: **Input voltage @ 10V input**, 30mV peak-peak (0.3%)
20mV/div, 2us/div, AC coupled

Channel M2: **Input voltage @ 24V input**, 25mV peak-peak (0.1%)
20mV/div, 2us/div, AC coupled

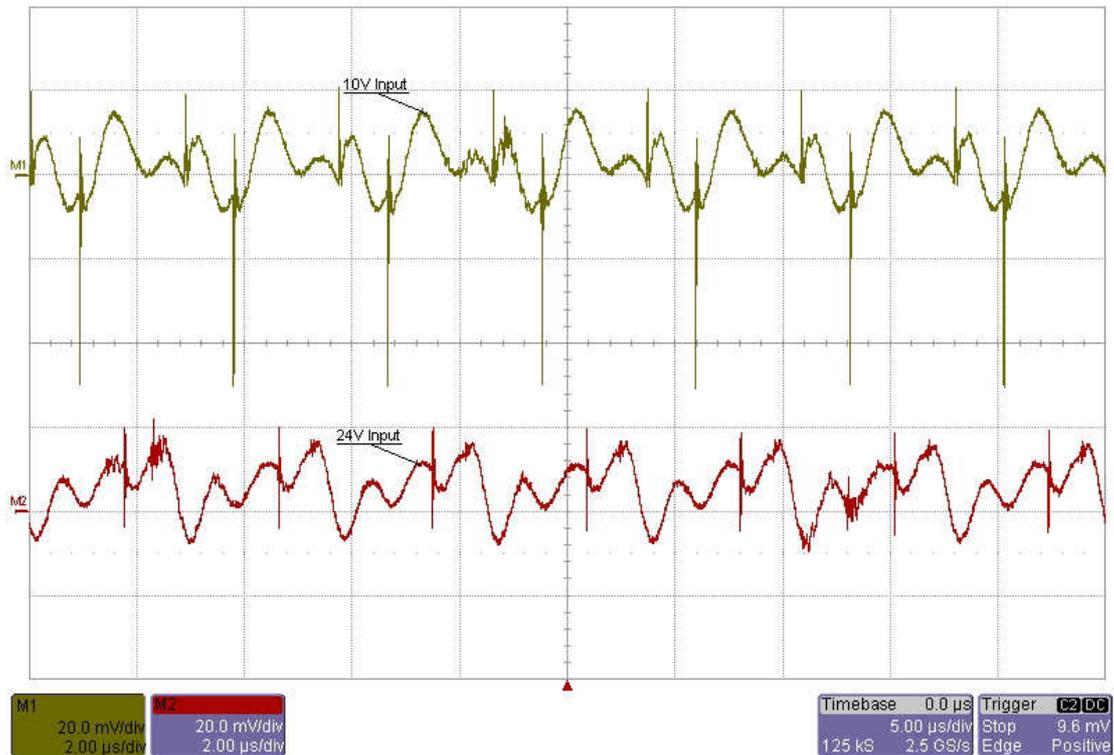


Figure 5

5 Output Ripple – Before Filter

The output ripple voltage for a single converter at 500mA @ 30V load before the post-filter is show in Figure 6.

Channel M1: **Output voltage @ 10V input**, 385mV peak-peak (1.2%)
100mV/div, 5us/div, AC coupled

Channel M2: **Output voltage @ 24V input**, 129mV peak-peak (0.4%)
100mV/div, 5us/div, AC coupled

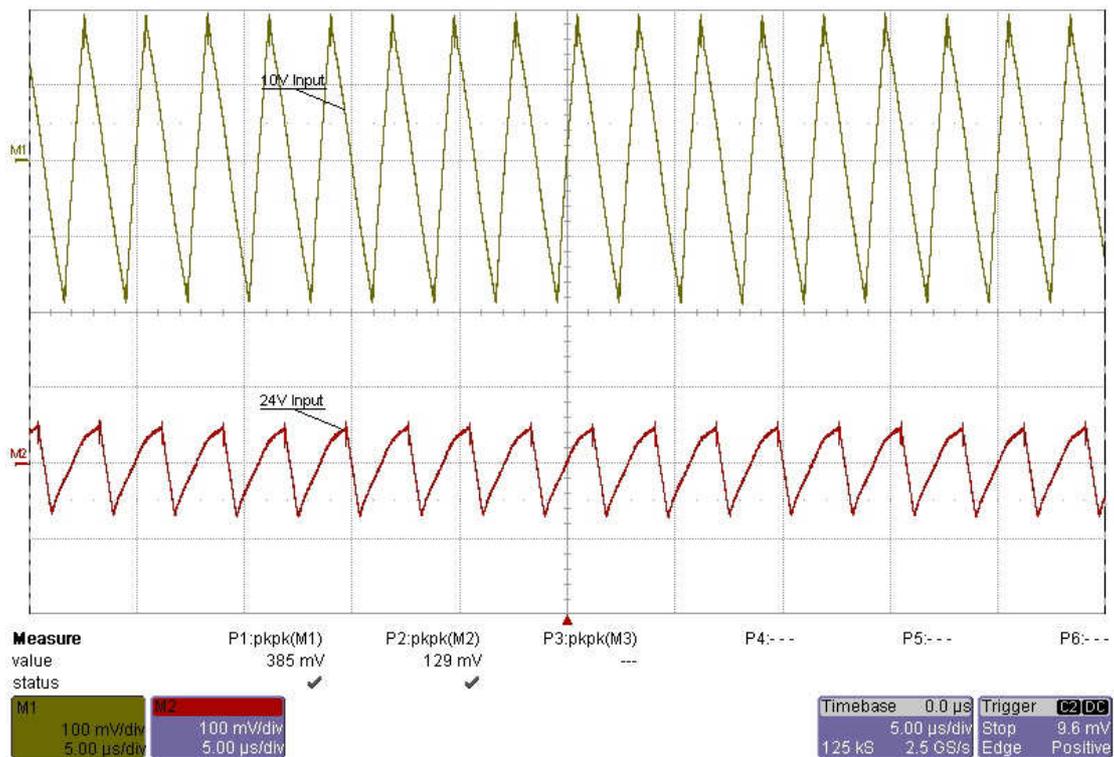


Figure 6

6 Output Ripple – After Filter

The output ripple voltage for a single converter at 500mA @ 30V load after the post-filter is show in Figure 7.

Channel M1: **Output voltage @ 10V input**, 8mV peak-peak (0.03%)
20mV/div, 5us/div, AC coupled

Channel M2: **Output voltage @ 24V input**, 5mV peak-peak (0.02%)
20mV/div, 5us/div, AC coupled

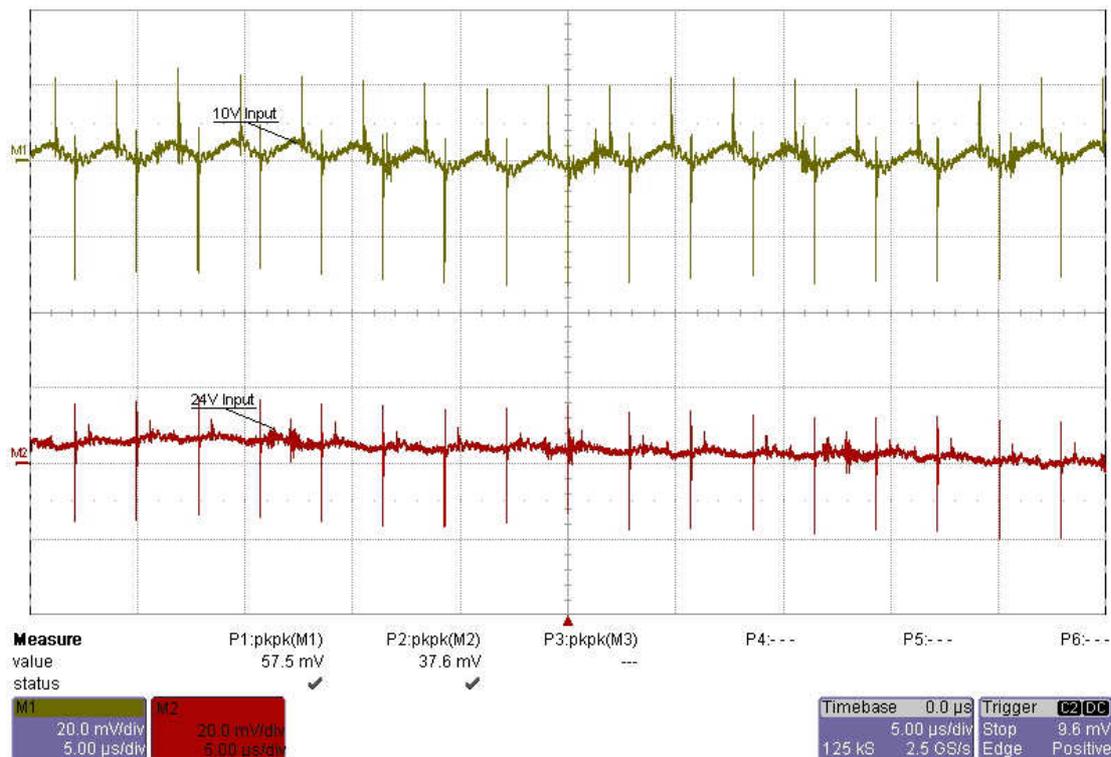


Figure 7

7 Dimming

Figure 8 shows dimming of the output current with 1 kHz and 40% duty cycle. The input voltage is set to 24V.

Channel M2: **Output current @ 24V input**
200mA/div, 500us/div, AC coupled

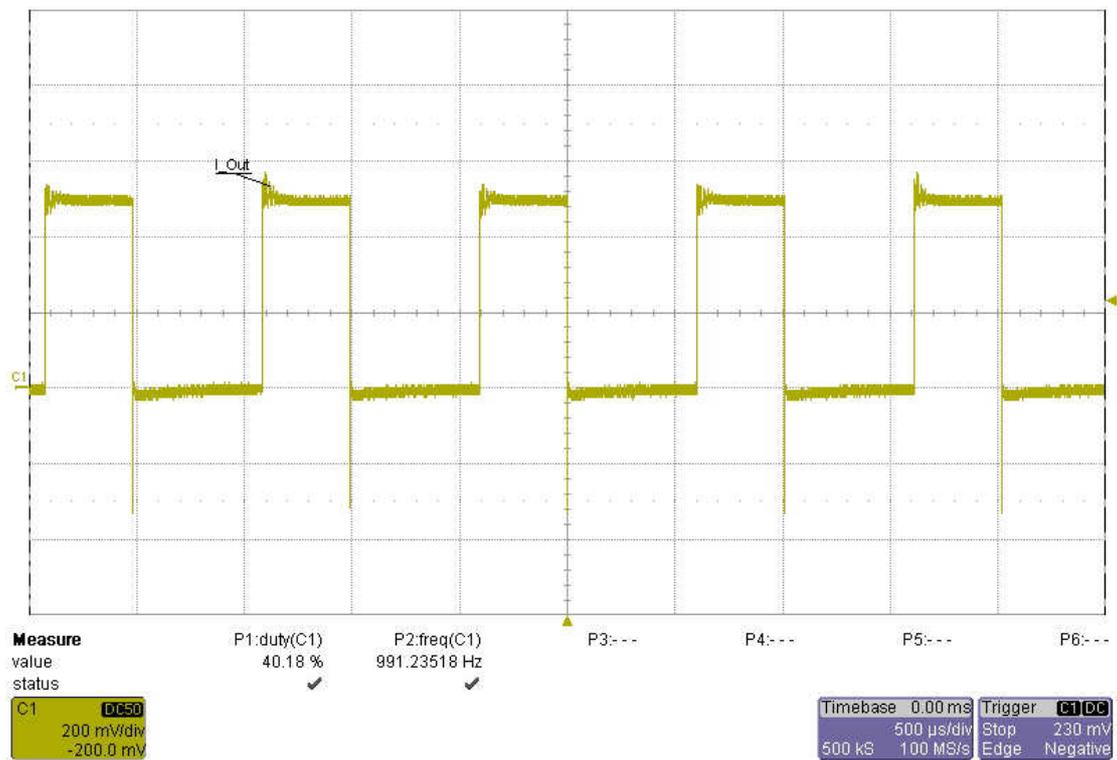


Figure 8

8 Switching Node

The drain-source voltage on the switching node is shown in Figure 9. The image was captured with 24V input and 500mA @ 30V load.

Channel C2: **Drain-source voltage**, -1.3V minimum voltage, 33.2V maximum voltage
5V/div, 2 μ s/div

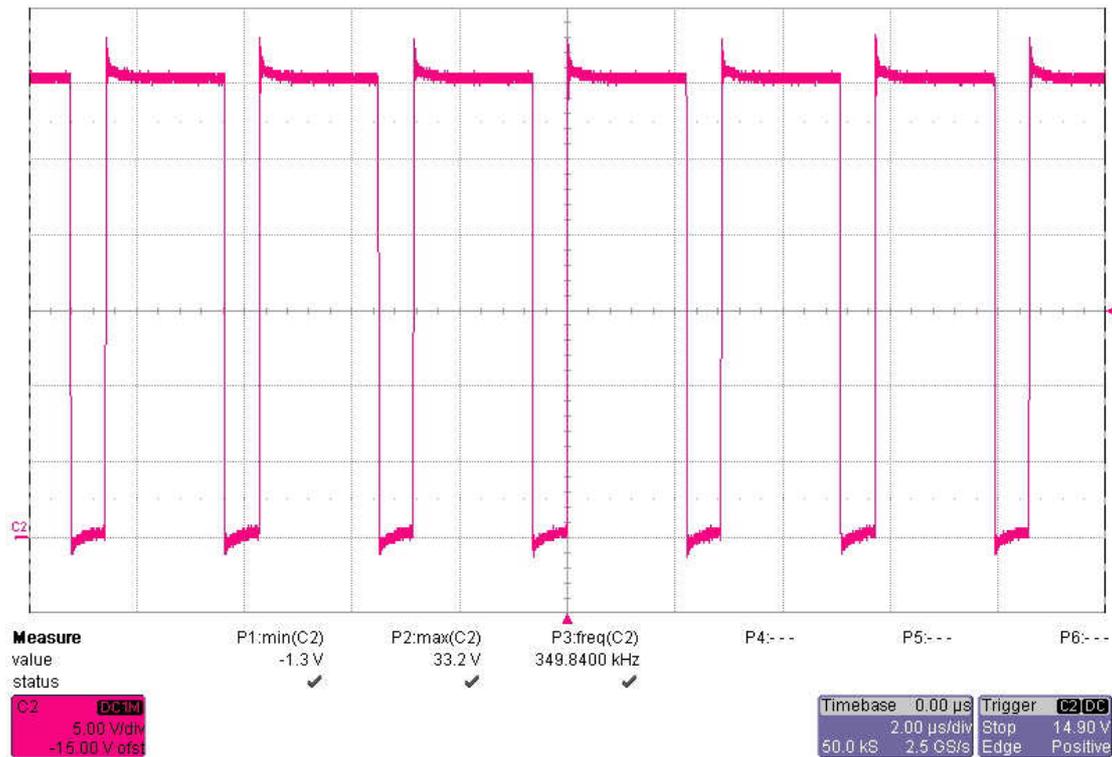


Figure 9

9 Thermal Measurement

The thermal image (Figure 10) shows the circuit at an ambient temperature of 21 °C with an input voltage of 24.0V and a load of 500mA @ 31V on each channel.

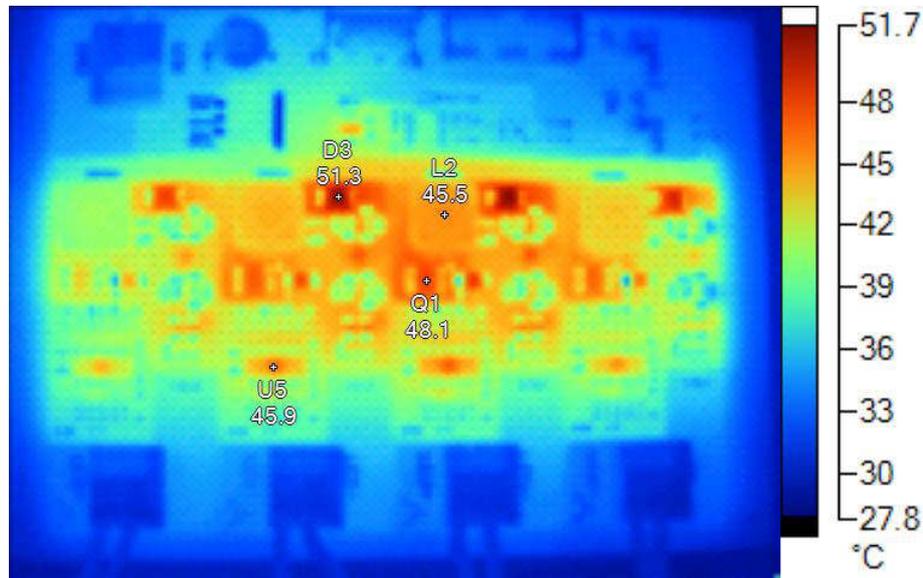


Figure 10

Markers

Label	Temperature	Emissivity	Background
U5	45.9 °C	0.95	21.0 °C
D3	51.3 °C	0.95	21.0 °C
Q1	48.1 °C	0.95	21.0 °C
L2	45.5 °C	0.95	21.0 °C

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated