

**Test Data
For PMP10748
09/20/2015**



Table of Contents

1. Design Specifications	2
2. Circuit Description.....	3
3. Block Diagram	4
4. Board Schematic	5
5. PMP10748 Board Photos	6
6. Adjustable Overcurrent Protection Test Results	8
4.2 Waveforms.....	8
4.2.1 20A+ Overcurrent Protection.....	8
4.2.2 20A Overcurrent Protection (Ramp input)	10
4.1 Thermal Data.....	11
5. Adjustable Overvoltage Protection Test Results.....	12
5.1 Waveforms.....	12
6. Under voltage-Lockout Test Result.....	13
6.1 UVLO Waveform	13
6.2 UVLO and OVP Waveform	14
7. Reverse Polarity Protection Test Result.....	15
7.1 Reverse Polarity Protection Waveform 1	15
7.2 Reverse Polarity Protection Waveform 2	16
8. OR-ing Solution with LM74610-Q1	17
8.1 Waveform 1	17
8.1 Waveform 2	18

1. Design Specifications

Vin Minimum	12V
Vin Maximum	36V
Vout	12VDC
Iout	20A
Reverse Polarity Protection	Yes
Over Voltage Range	36V
Under Voltage Lockout	Not Populated
Over Current Protection	20A+
OR-ing Controller	Yes

2. Circuit Description

PMP10748 is a complete front end system protection design with the following features:

1. Reverse Polarity Protection:

The LM74610-Q1 Smart diode controller is combined with SQJ422EQ N-Channel MOSFET to provide reverse current and reverse voltage protection. The LM74610-Q1 is used to provide gate drive to the external MOSFET, and to protect the load in the case of reverse polarity by shutting down the gate within 2usec.

2. Smart Diode OR-ing Controller:

The PMP10748 replaces diode ORing for redundant power supplies with LM74610-Q1 Smart Diode Controller solution. This solution makes the OR-ing Controller device 10x more efficient.

3. Over Voltage Protection:

The LM5060 provides an over voltage and series fault protection when the input voltage surges higher than 36V. OVP can be calculated using the following expression:

$$V_{INMAX} = OVP_{TH} + \frac{R_2 \times OVP_{TH}}{R_3}$$

4. Over Current Protection:

The LM5060 uses a sense resistor to provide over current protection when the output current exceeds 20A.

5. Under Voltage Lockout (optional):

This option is not populated, but the design included an under voltage lock out. By placing appropriate resistor values for Ru and Ro, the under voltage lockout can be set to any desired value. The resistor values for under voltage lockout can be calculated using the following expression:

$$R_u = \frac{V_{INMIN} - UVLO_{TH}}{\left(UVLO_{BIAS} + \frac{UVLO_{TH}}{R_o} \right)}$$


$$V_{INMIN} = UVLO_{TH} + \left[R_u \times \left(UVLO_{BIAS} + \frac{UVLO_{TH}}{R_o} \right) \right]$$

*Pick any value for Ro and R3 below 100kΩ


*UVLO_{BIAS} = 5.5μA, UVLO_{TH} = 1.6V

* OVP_{BIAS} = 0μA, OVP_{TH} = 2.0V

3. Block Diagram

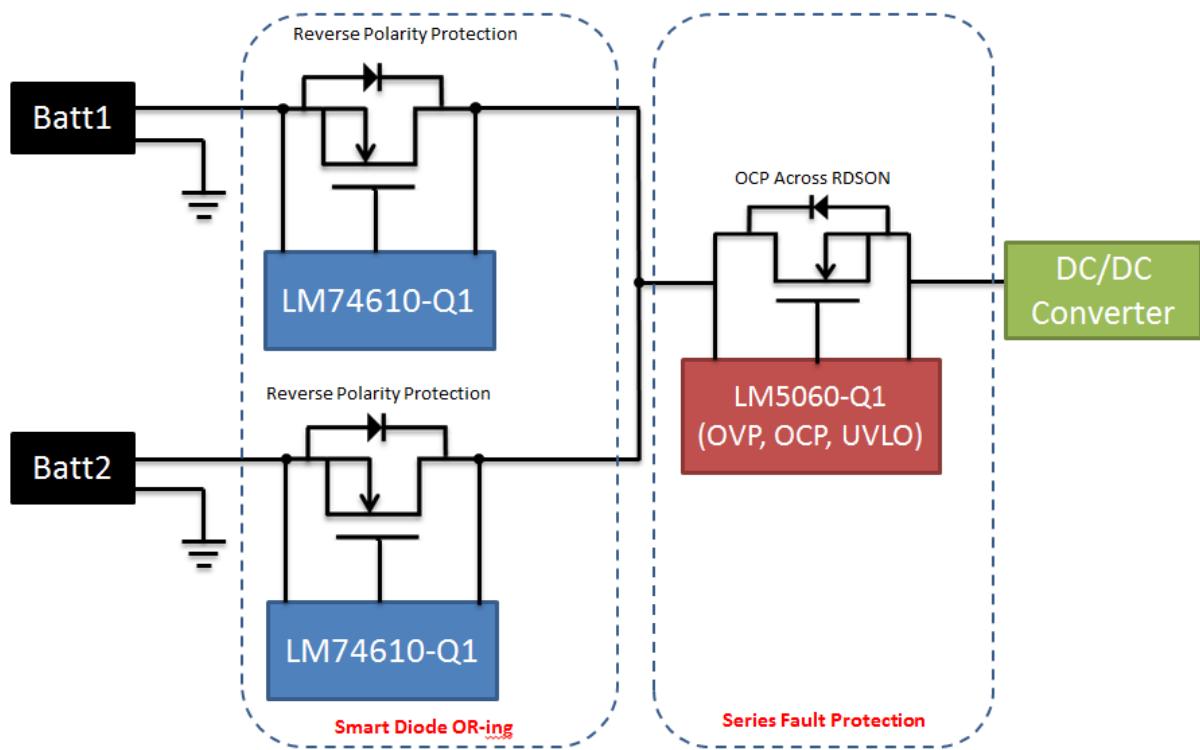


4. Board Schematic

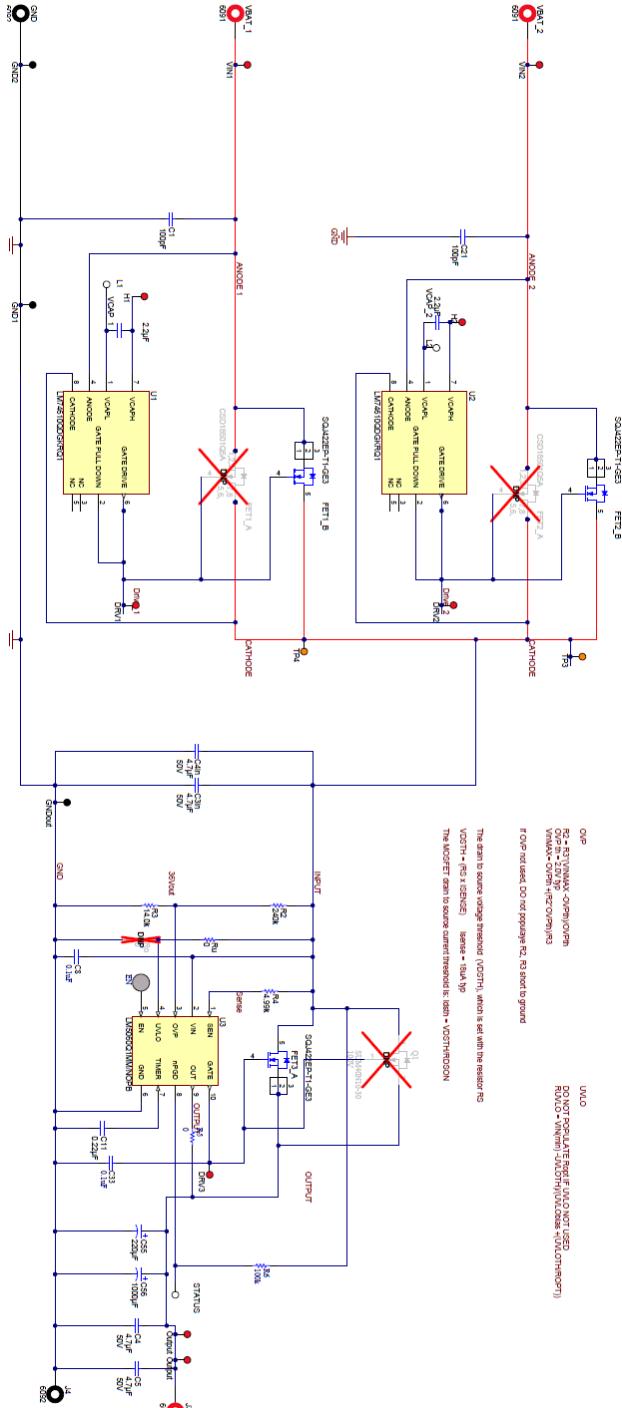



5. PMP10748 Board Photos

Board Dimensions: 4682mil *2840mil

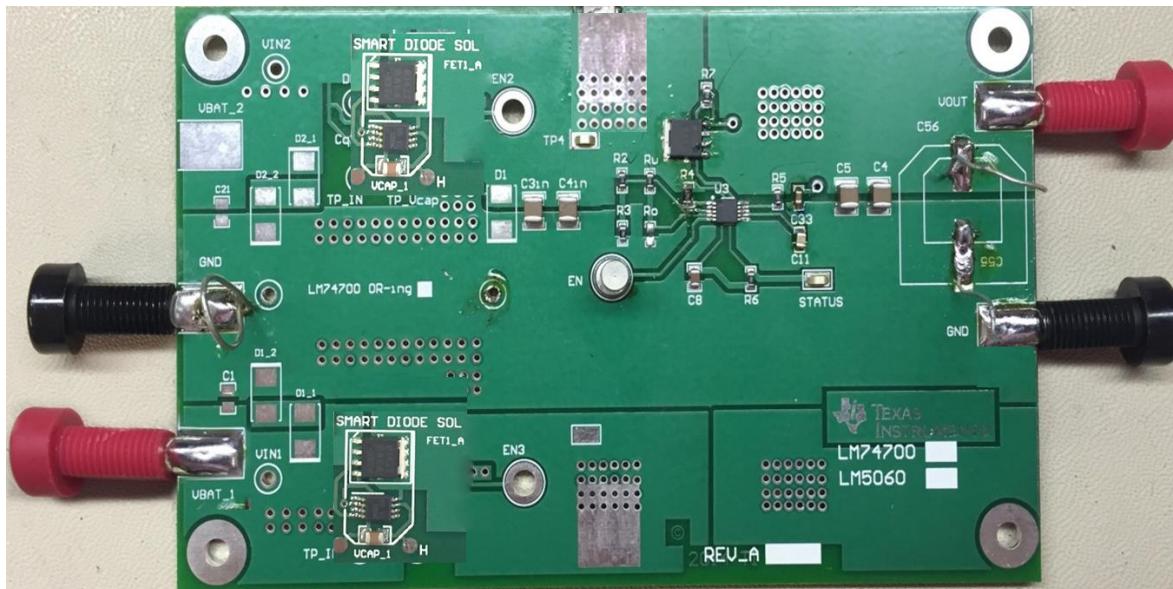


Board Photo (Top)

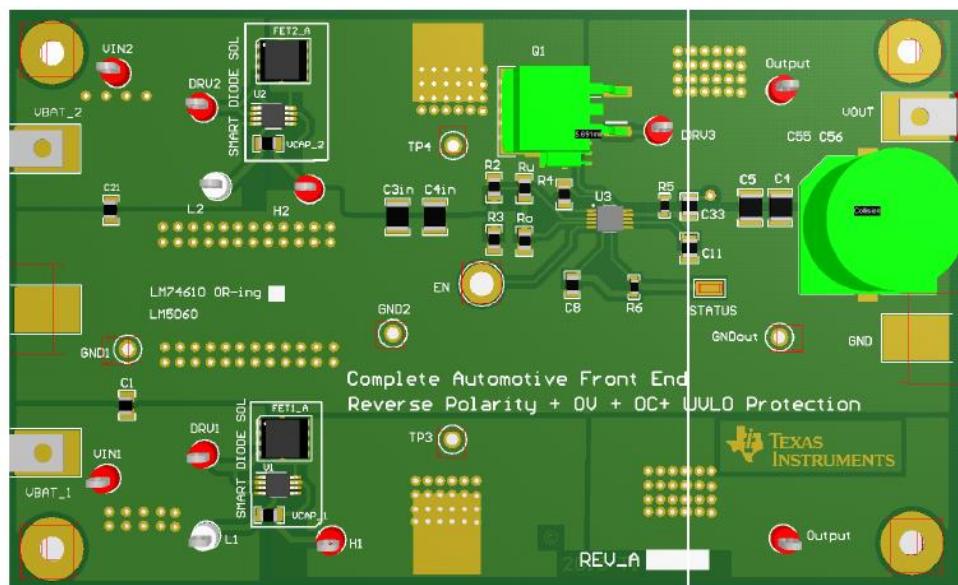

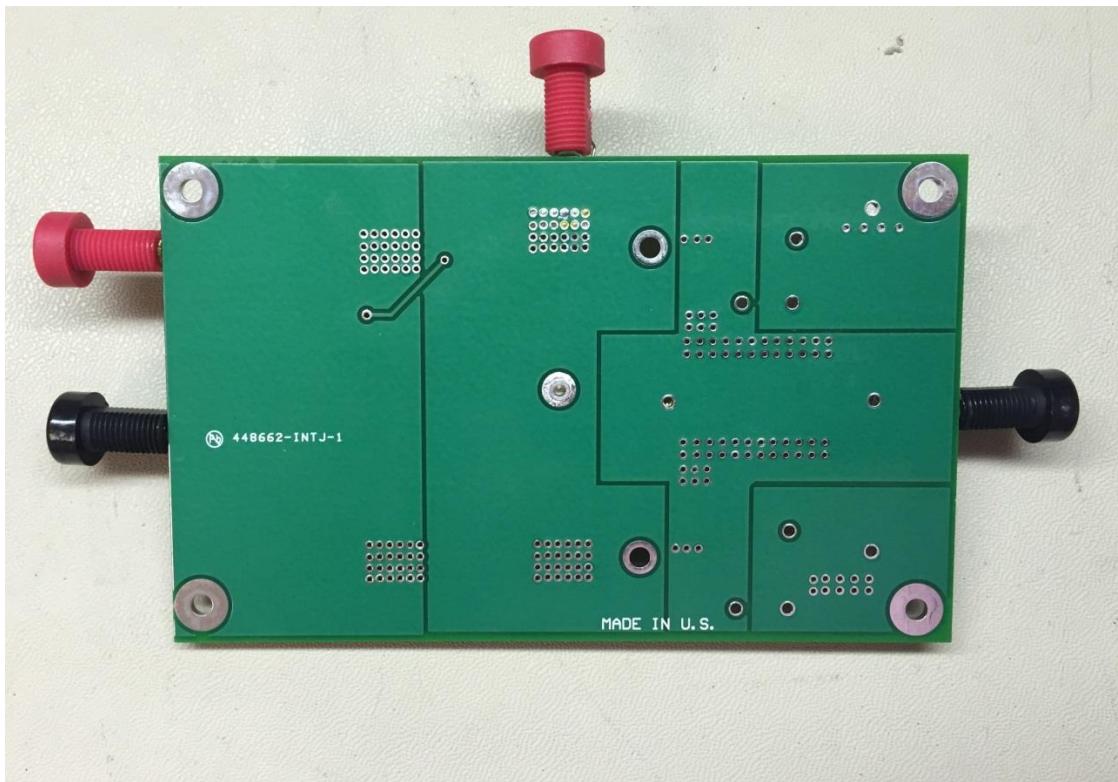

Board Photo (Bottom)

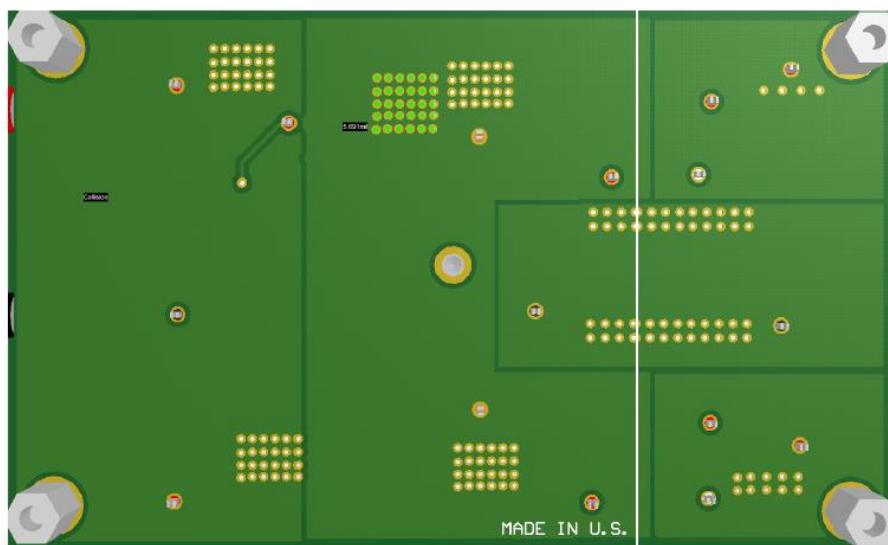


6. Adjustable Overcurrent Protection Test Results

For the test performed, the sense resistor was set at $5\text{k}\Omega$ which allowed the Overcurrent threshold to be set around 20A.

4.2 Waveforms

4.2.1 20A+ Overcurrent Protection

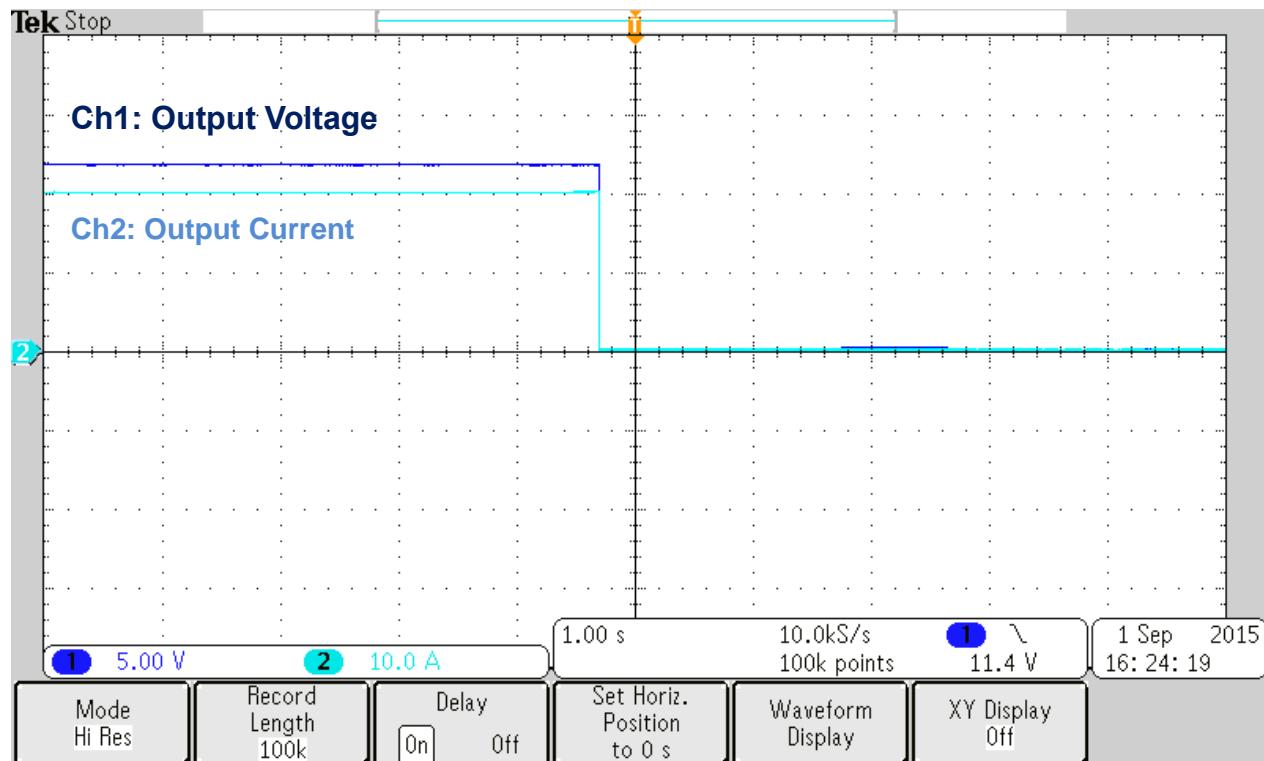


Overcurrent Protection Response: Current shift from 19.5A steady state to 20A.

$R_{sense} = 5\text{k}\Omega$.

Teal- I_{out}

Blue- V_{out}

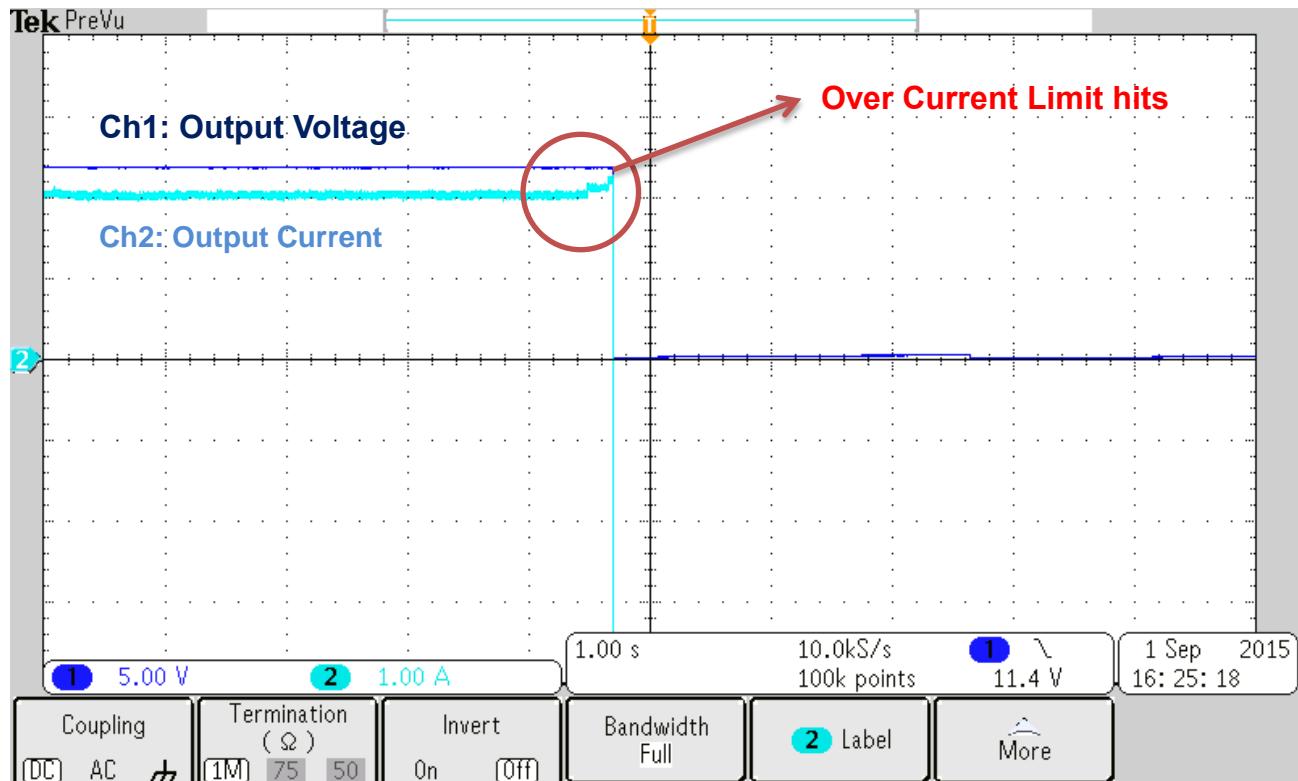

(Zoomed in)


Overcurrent Protection Response: Current shift from 19.5A steady state to 20A.

$R_{sense} = 5\text{k}\Omega$.

Teal- I_{out}

Blue- V_{out}

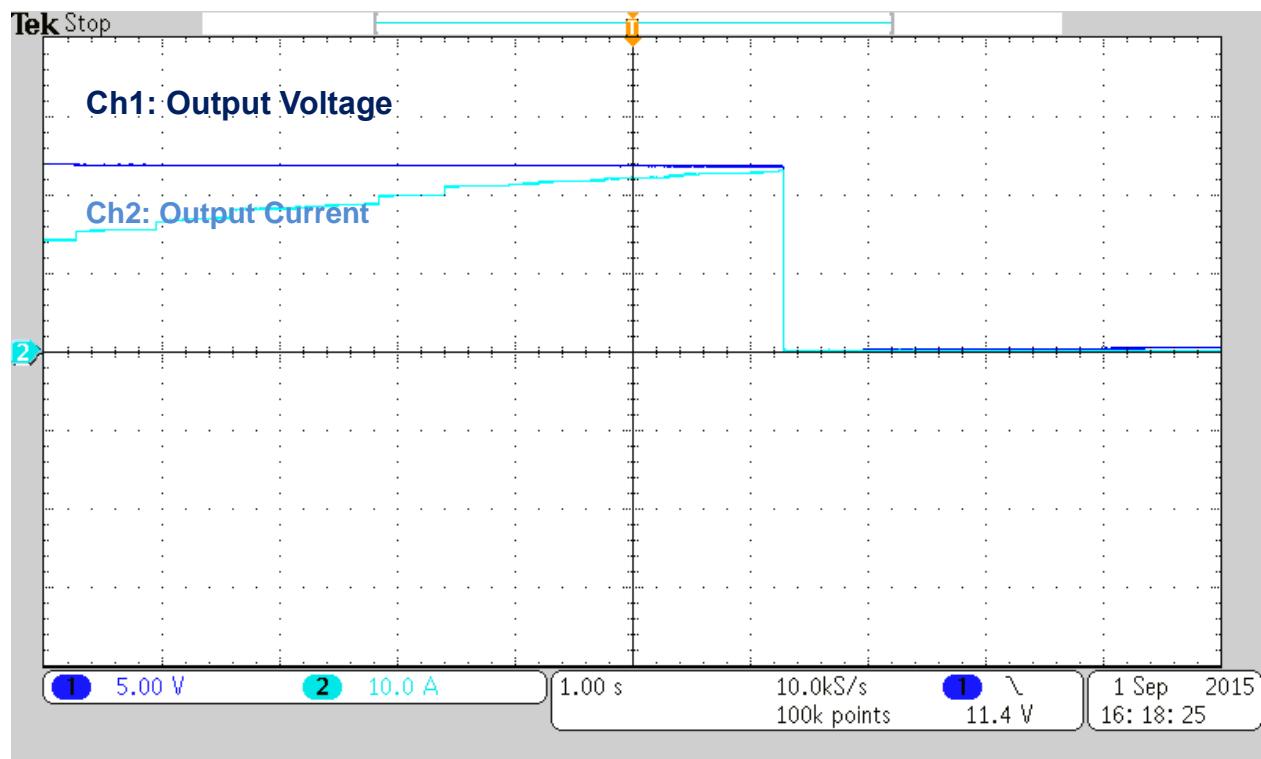4.2.2 20A Overcurrent Protection (Ramp input)




Overcurrent Protection Response: Current ramp from 0A to +20A.

$R_{sense} = 5\text{k}\Omega$.

Teal- I_{out}

Blue- V_{out}

4.1 Thermal Data

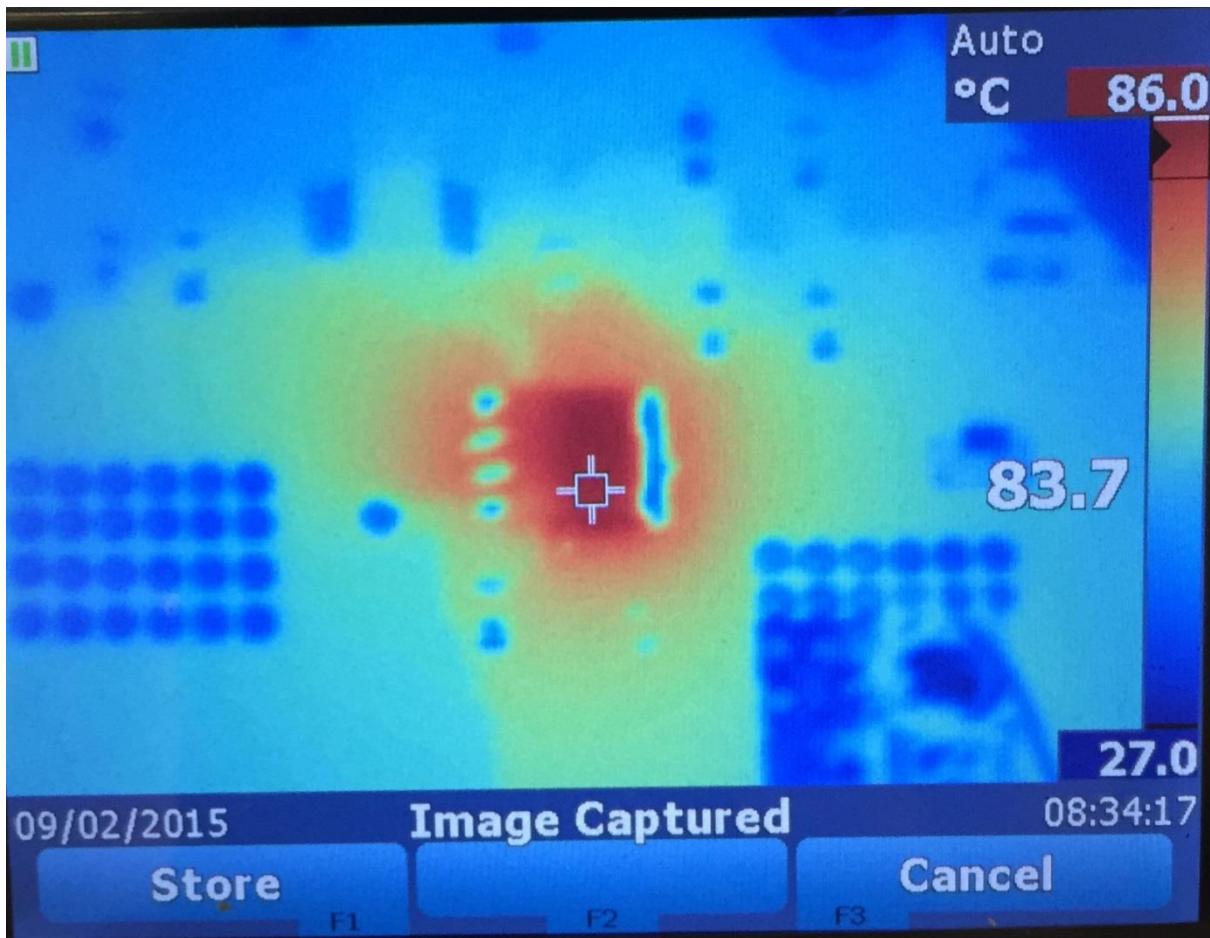


IR thermal image taken at steady state with 12V V_{in} and 20 A load.

5. Adjustable Overvoltage Protection Test Results

The Overvoltage threshold was set at 36V. This is done by.....

5.1 Waveforms

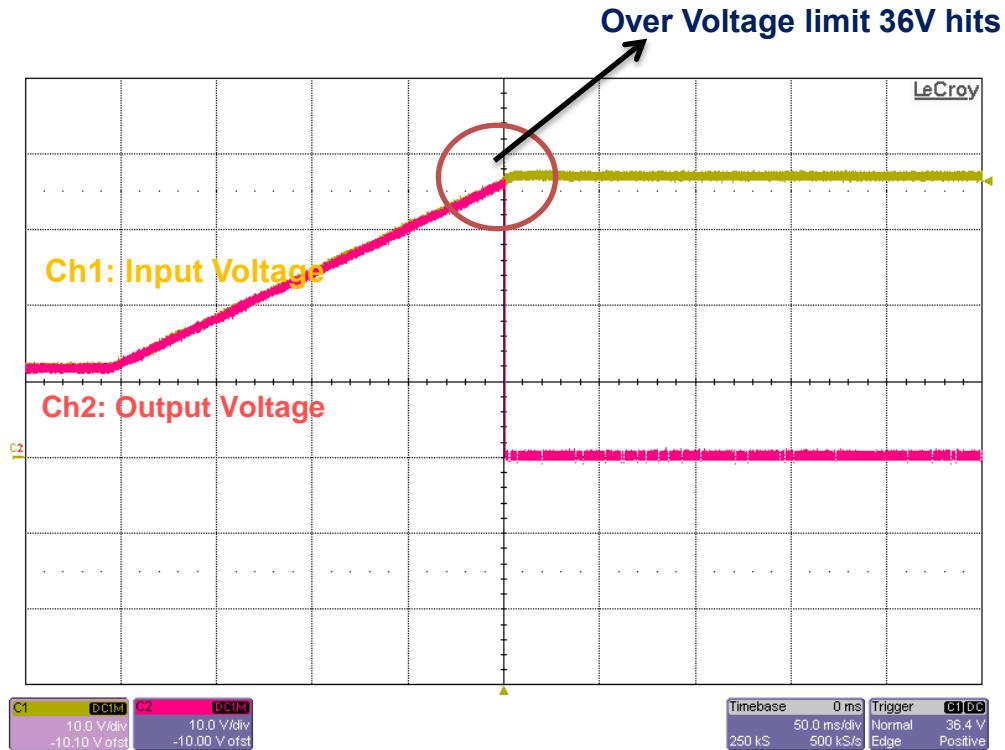

Overvoltage Protection Response: Voltage ramp from 0V to 36V.


Green- V_{in}

Red- V_{out}

6. Under voltage-Lockout Test Result

The board does not have under voltage lock out populated. The function is disabled by shorting Ru to Vin and not populating Ro, but the option is available.

6.1 UVLO Waveform

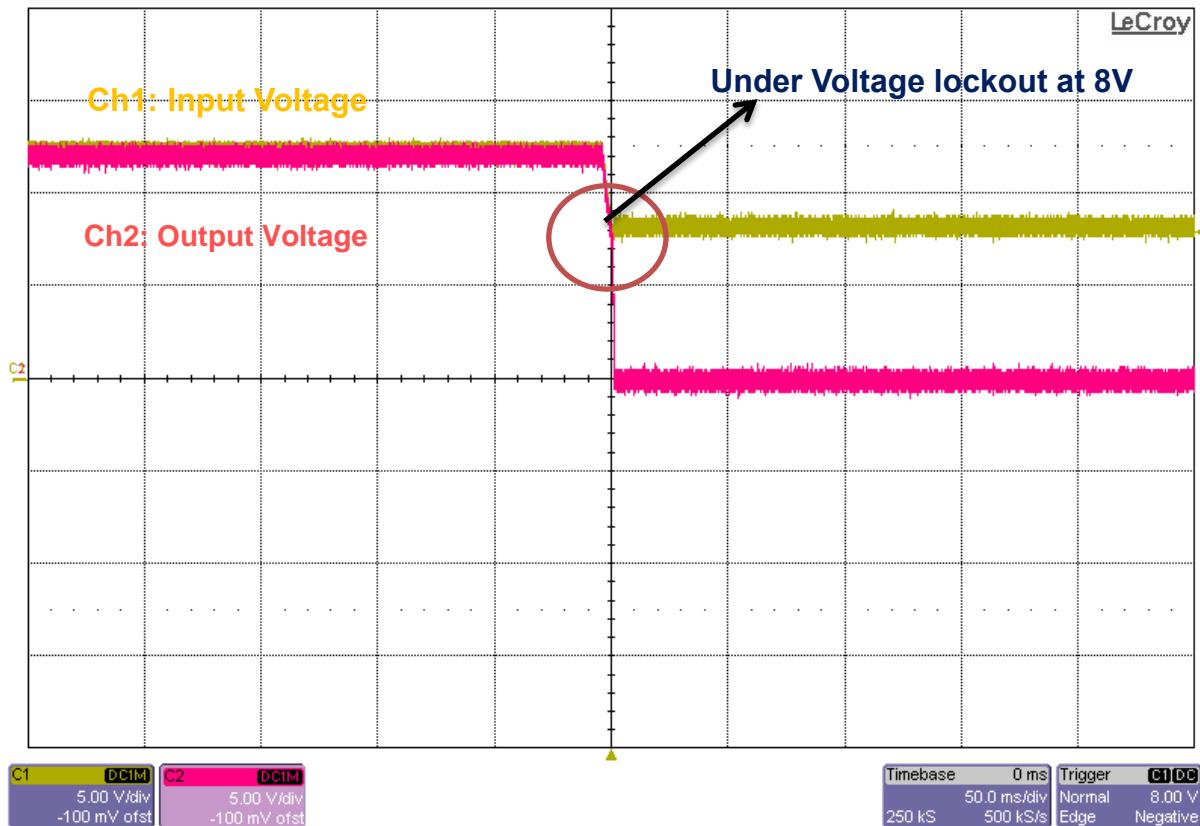


Undervoltage-Lockout Response: Voltage ramp from 12V to 8V.

Green- V_{in}

Red- V_{out}

6.2 UVLO and OVP Waveform

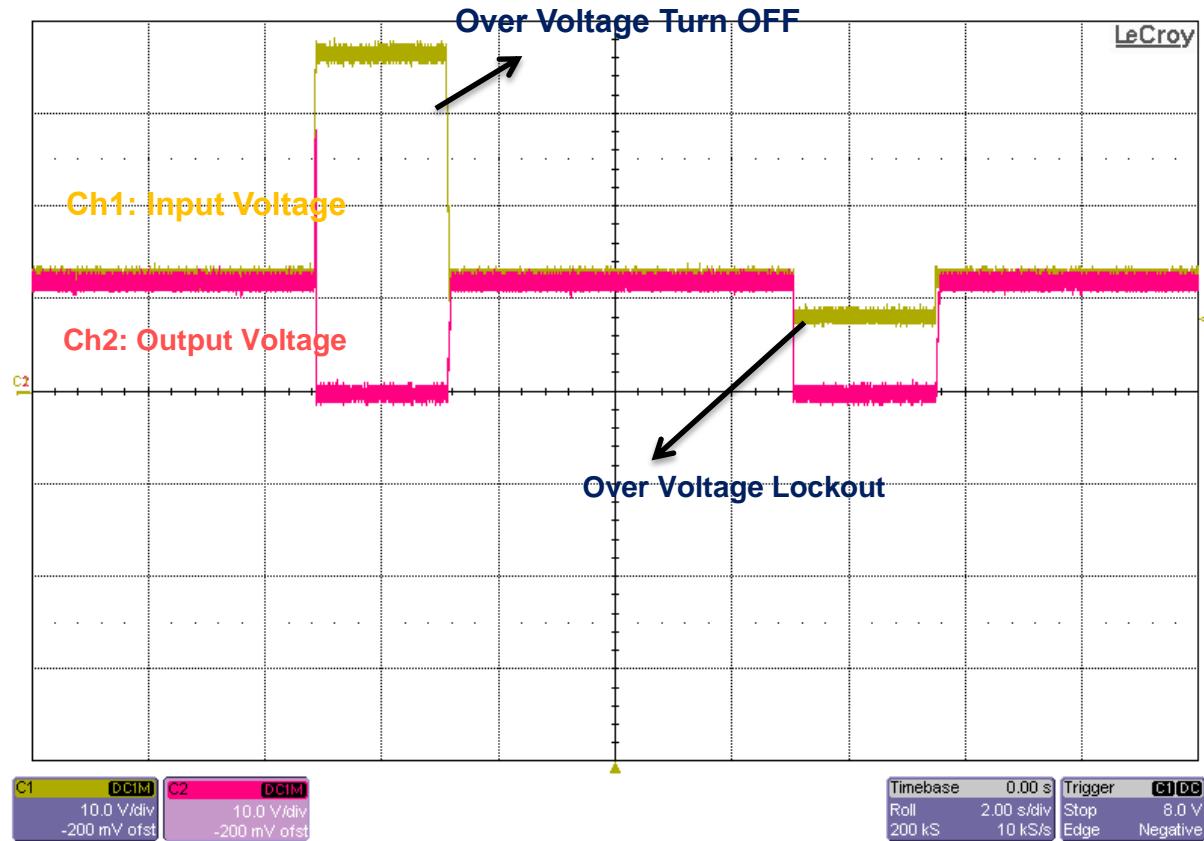

UVLO and OVP Response: Voltage pulse from 12V to 36V and a second pulse from 12V to 8V.


Green- V_{in}

Red- V_{out}

7. Reverse Polarity Protection Test Result

Using the LM74610-Q1 Smart diode in series with LM5060 the board is also given the ability to protect against reverse polarity.

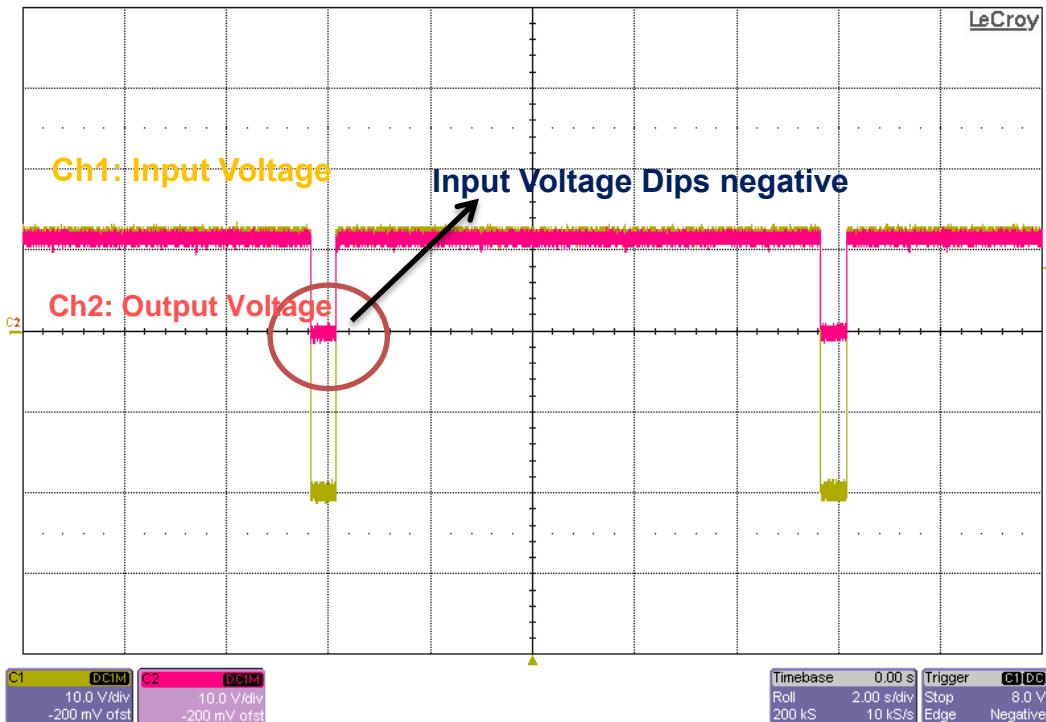7.1 Reverse Polarity Protection Waveform 1




Reverse Polarity Protection Response: Voltage pulse from 12V to -20V.

Green- V_{in}

Red- V_{out}

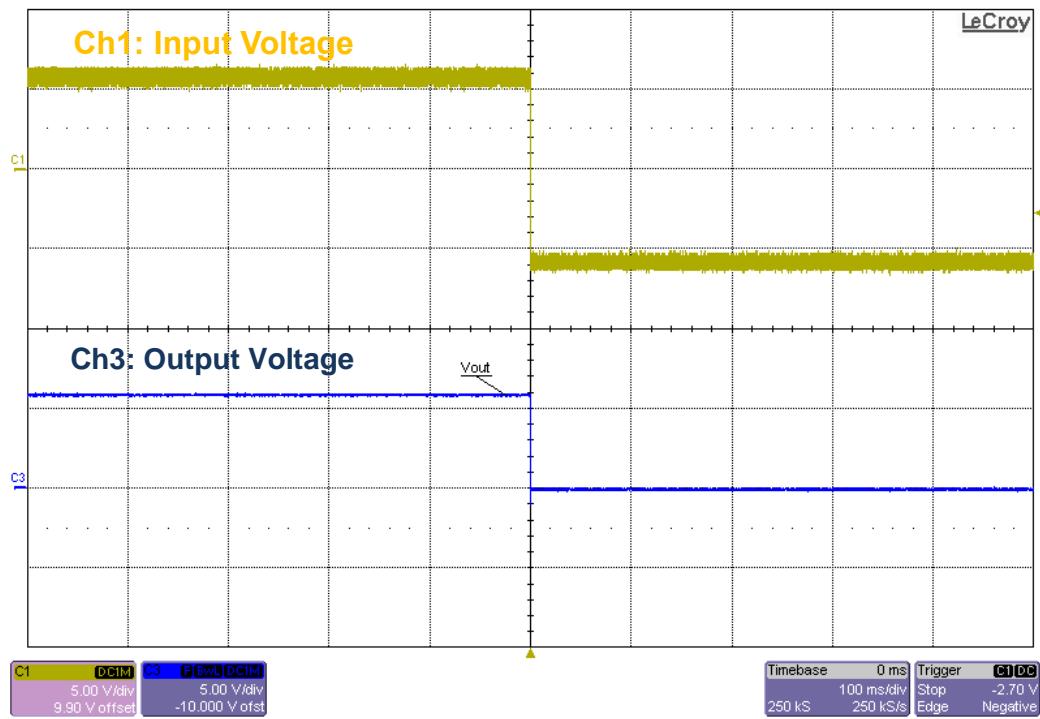7.2 Reverse Polarity Protection Waveform 2



Reverse Polarity Protection Response: Voltage pulse from 6V to -6V.


Green- V_{in}

Blue- V_{out}

8. OR-ing Solution with LM74610-Q1

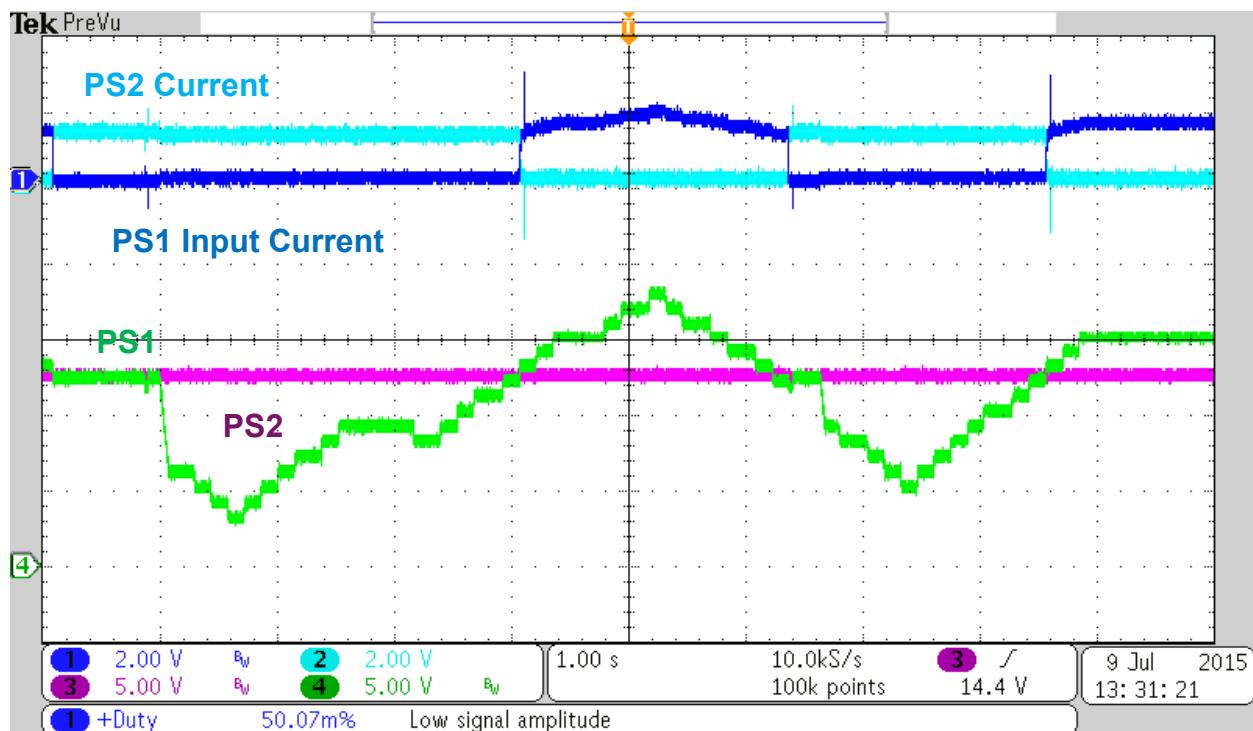8.1 Waveform 1

The following scope plot shows that changing the PS1 (Green) and PS2 (Pink) doesn't get affected. The output current is 1.5A for the following test. As the PS1 voltage increases, the input Current through PS2(light blue) immediately becomes zero after a negative current spike.



Power Supply OR-ing with PMP10748

Green- Supply 1


Pink- Supply 2

Blue- PS1 Input Current

Teal- PS3 Input Current

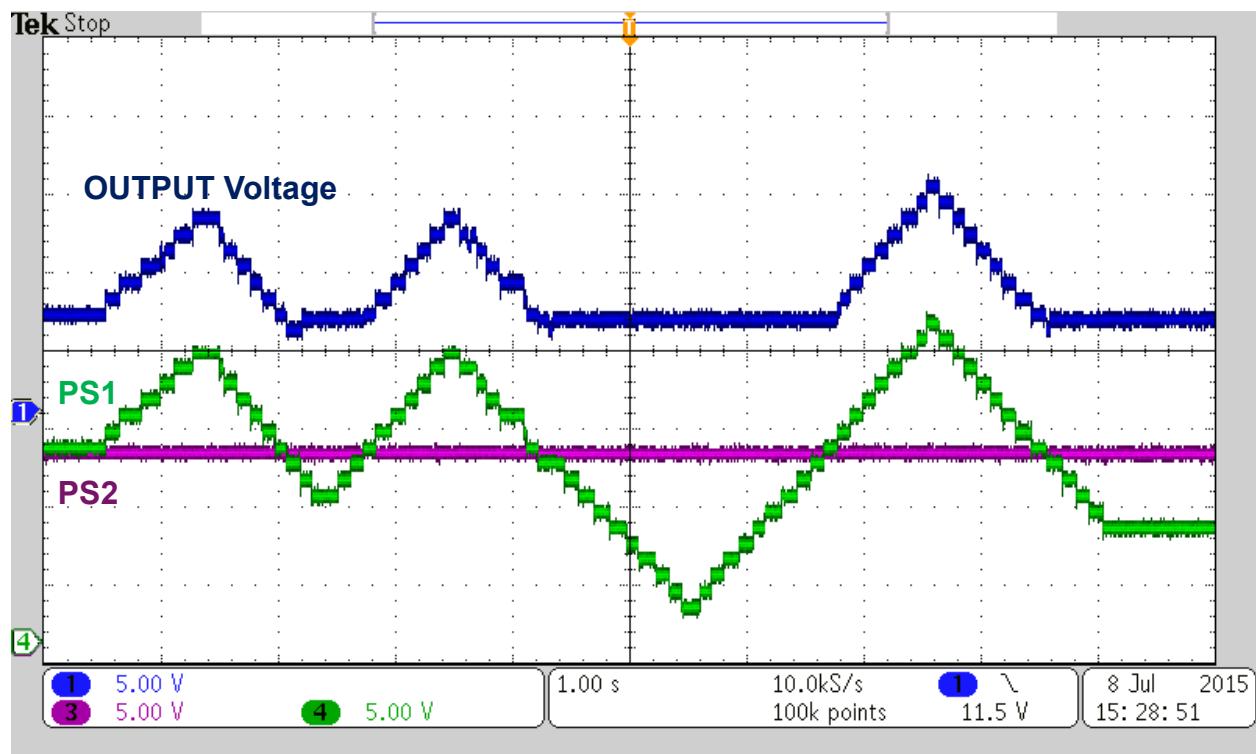8.1 Waveform 2

The following scope plot shows that voltage interruption at PS1 (Green) and PS2 (Pink) doesn't get affected. The output Voltage (Blue) follows the higher supply voltage similar to the diode ORing device. The output current is 1.5A for the following test.



Green- Supply 1

Pink- Supply 2

Blue- Output Voltage

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated