

**Test Report
For PMP10723
03/01/2016**




1. Design Specifications

V_{in} Min.	9VDC
V_{in} Max.	16VDC
V_{out}	53VDC
I_{out}	400mA max
Target Switching Frequency	230kHz

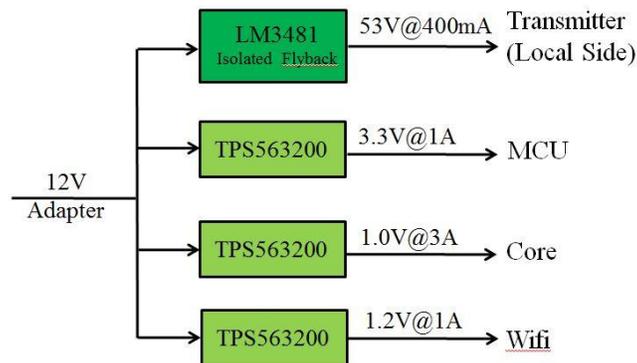2. Circuit Description


PMP10723 is an isolated flyback solution which accepts an input voltage of 9 to 16V_{IN} and provides an output of 53V output capable of supplying continuous 400mA of current to the load. With secondary control, it can achieve great load regulation performance. This LM3481 flyback reference design can be used for supplying the transmitter in the local side in home gateway application, as well as other isolated high voltage industrial application by changing the transformer parameters. The home gateway user side's power tree is as below.



3. Board Photos




Top

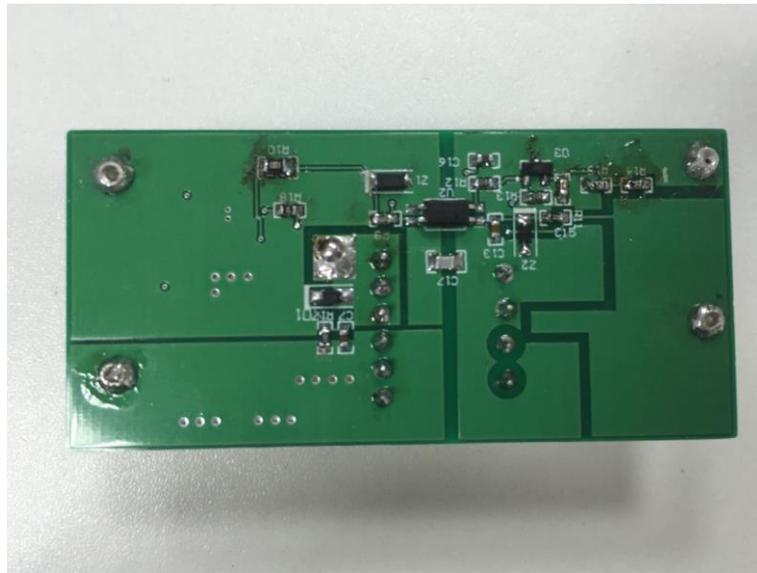


Bottom

4. Thermal Data

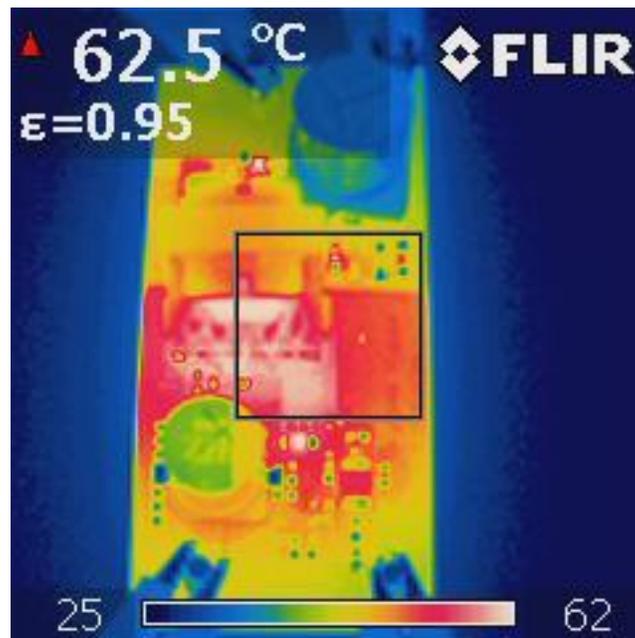

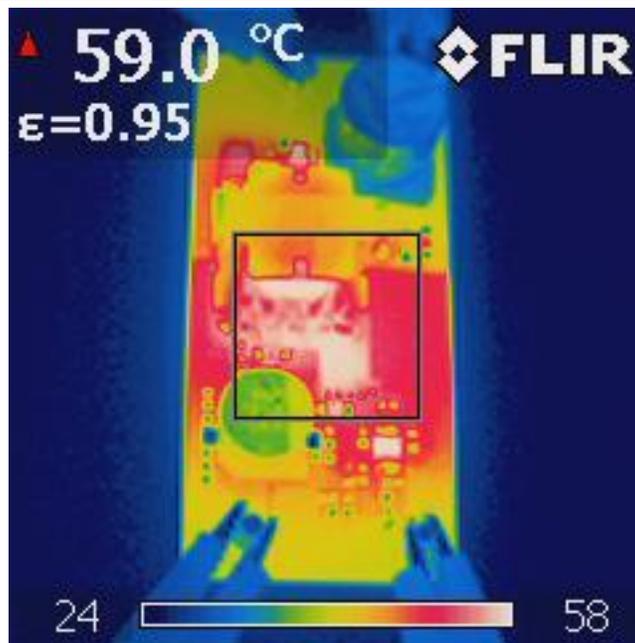
IR thermal image taken at steady state at 400mA load and VIN = 9.0V for two minutes with no airflow (4 Layer board, 1 Oz copper layer)




IR thermal image taken at steady state at 400mA load and VIN = 16V for two minutes with no airflow (4 Layer board, 1 Oz copper layer)

5. Efficiency and Regulation

5.1 Efficiency Chart


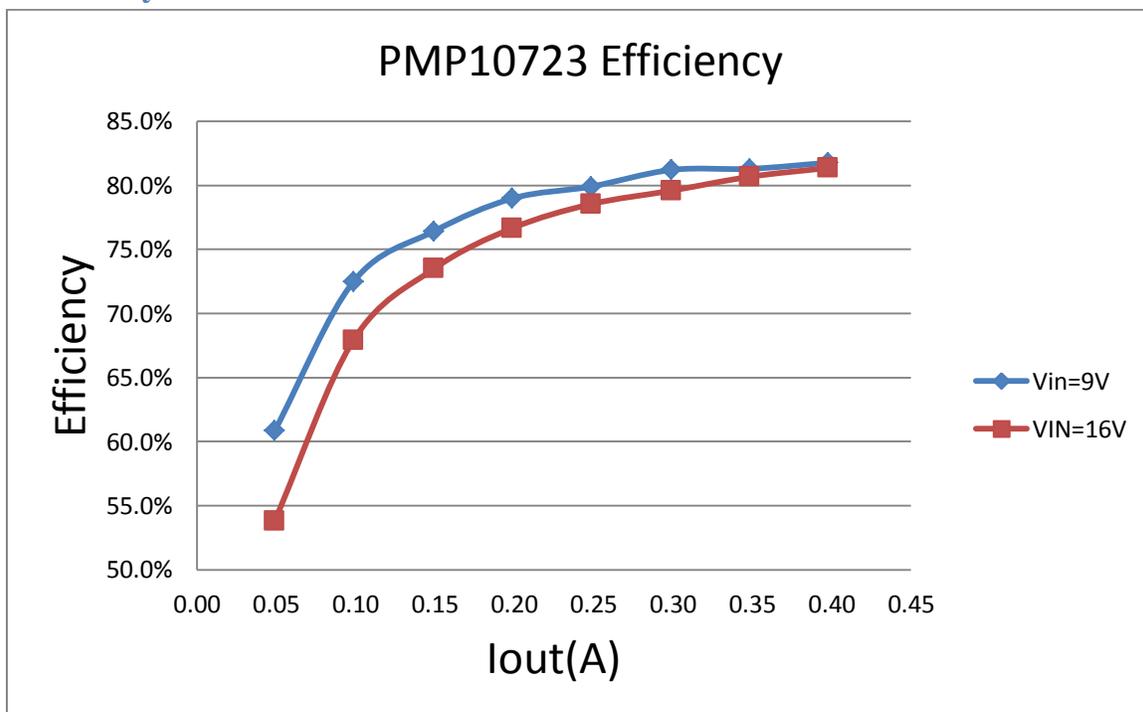



5.2 Regulation Chart

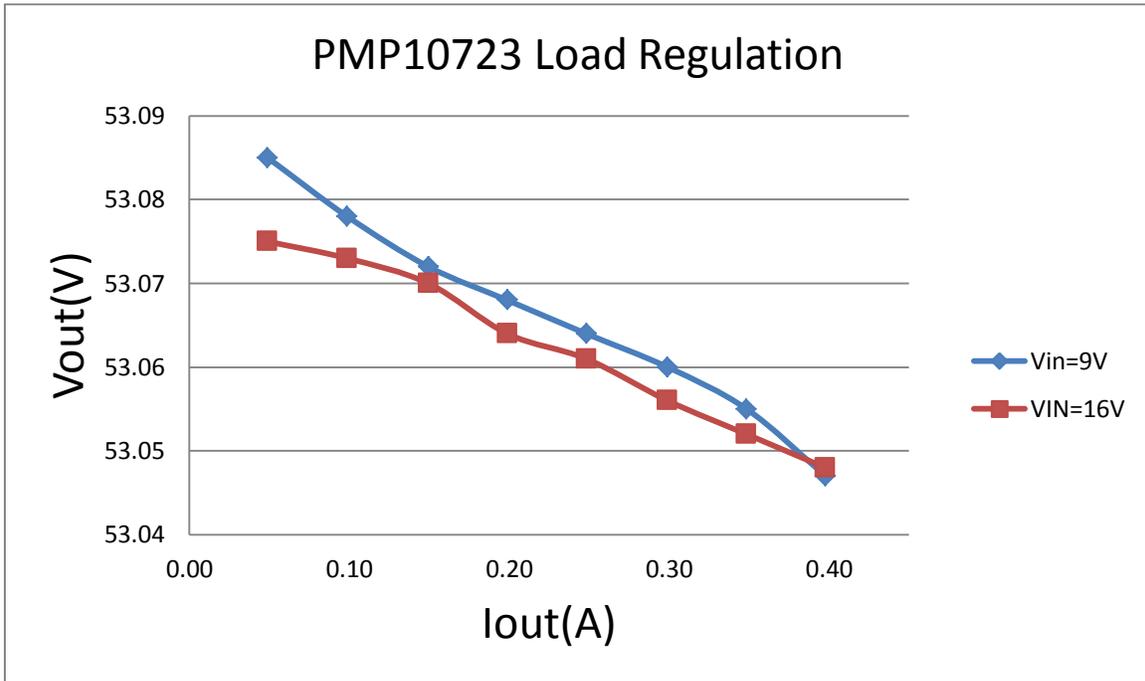


6. Waveform

6.1 Startup

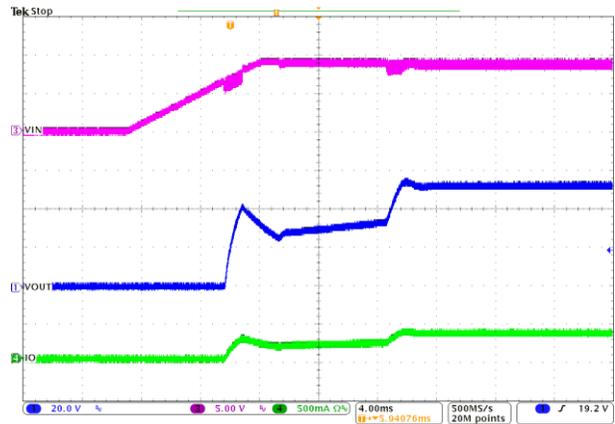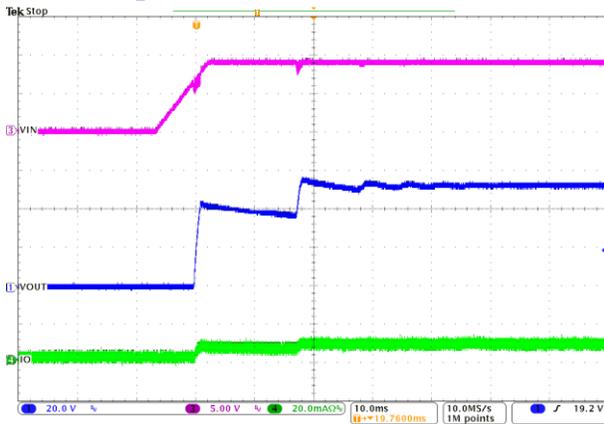

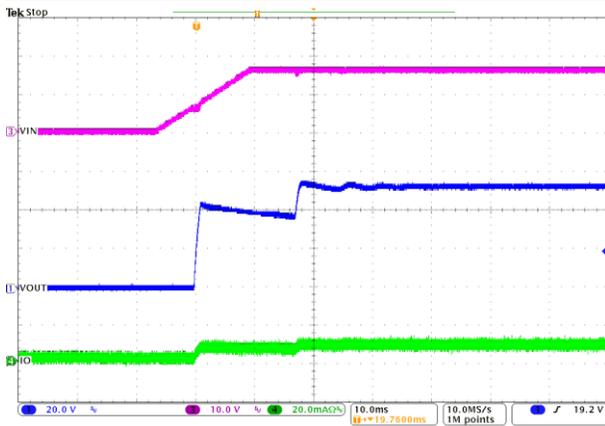


VIN=16V, Io=10mA

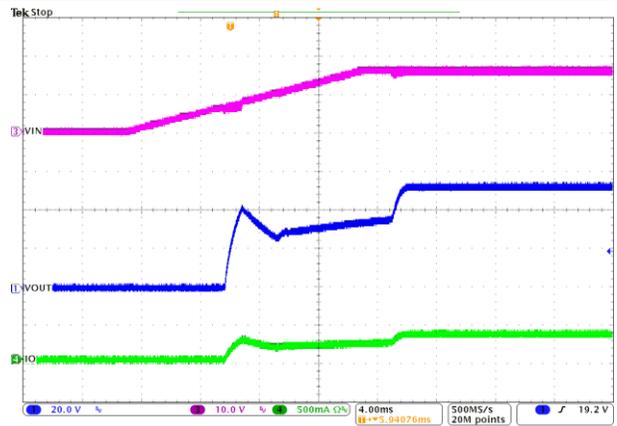


VIN=16V, Io=400mA


6.2 Shutdown

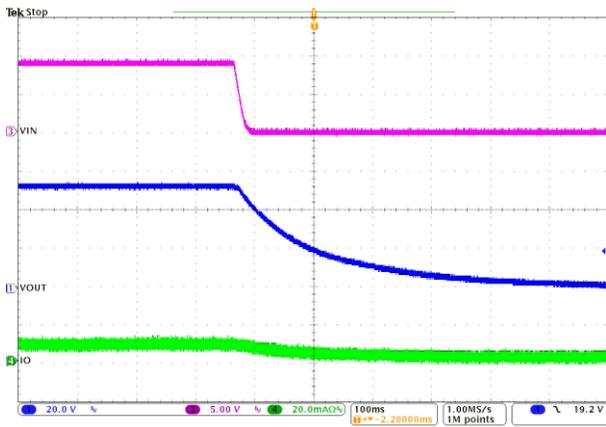


VIN=9V, Io=10mA

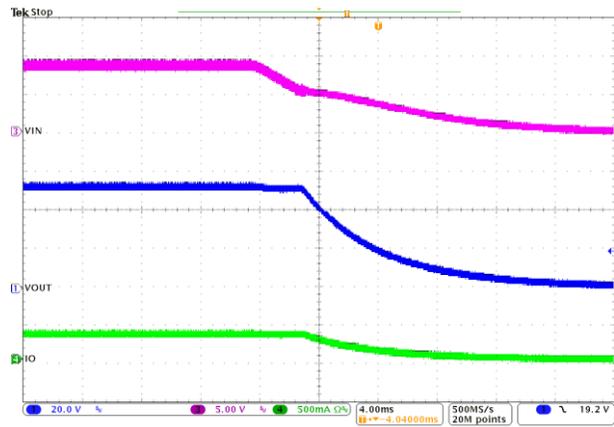

VIN=9V, Io=400mA

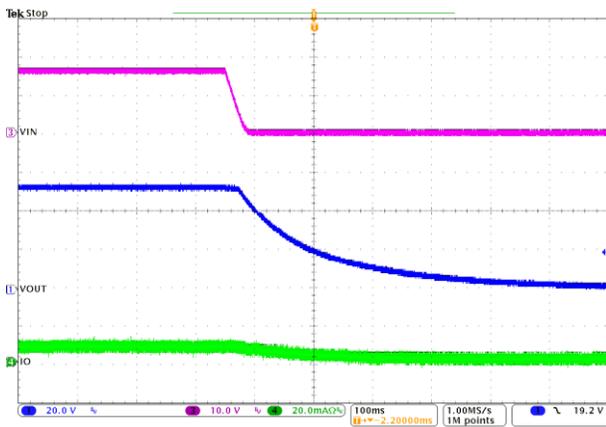


VIN=16V, Io=10mA

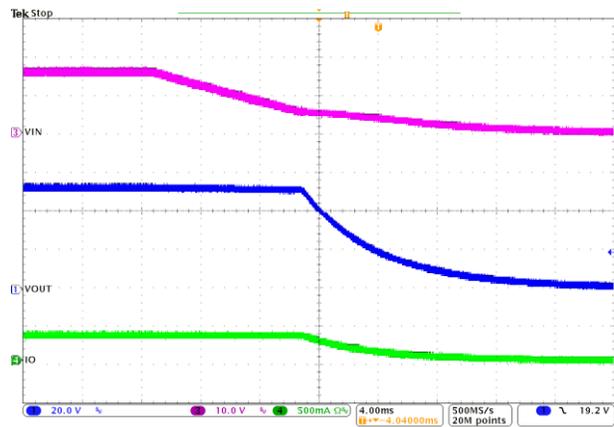


VIN=16V, Io=400mA


6.3 Ripple

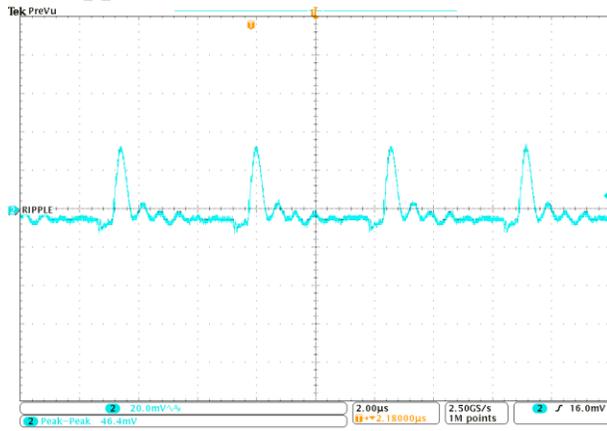


VIN=9V, Io=10mA

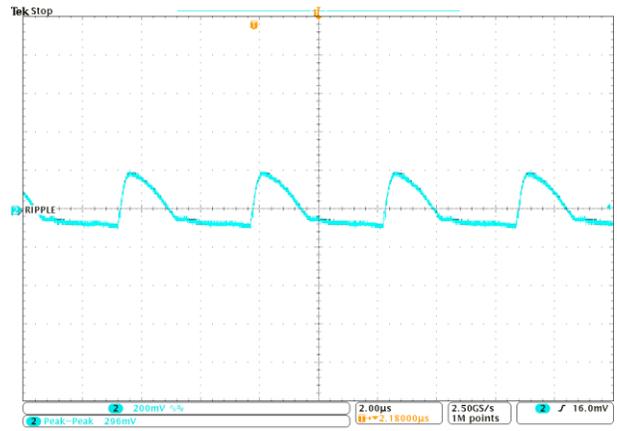

VIN=9V, Io=400mA

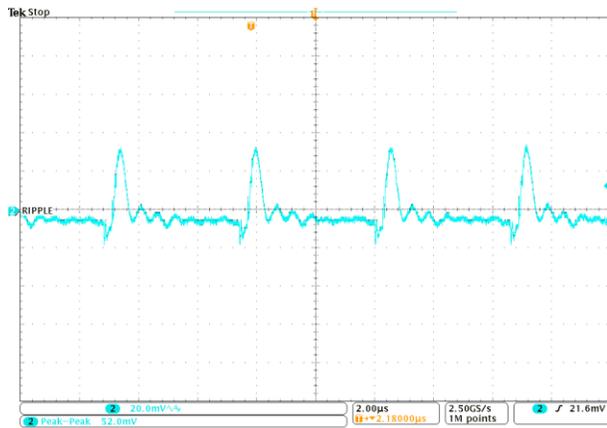


VIN=16V, Io=10mA

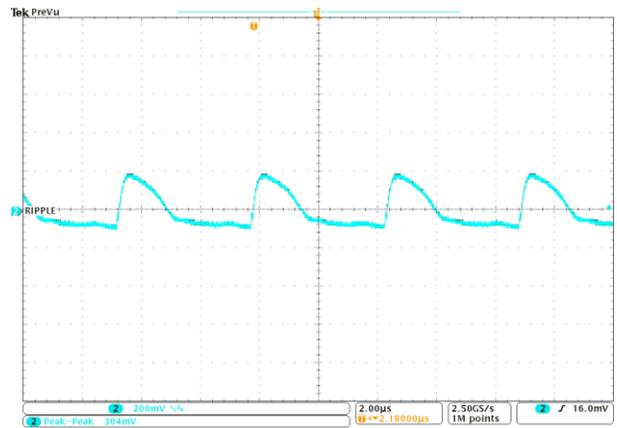


VIN=16V, Io=400mA


6.4 Switching

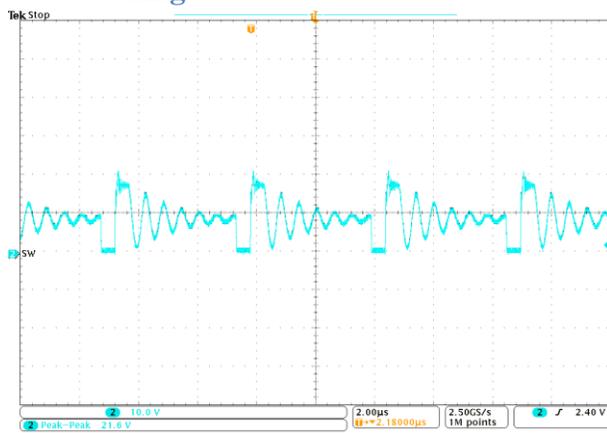


VIN=9V, Io=10mA

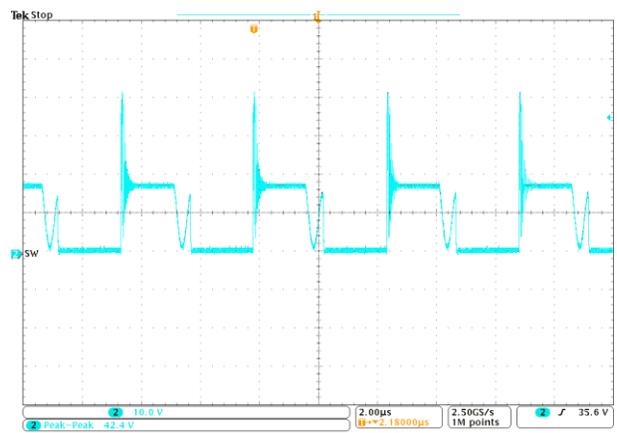

VIN=9V, Io=400mA

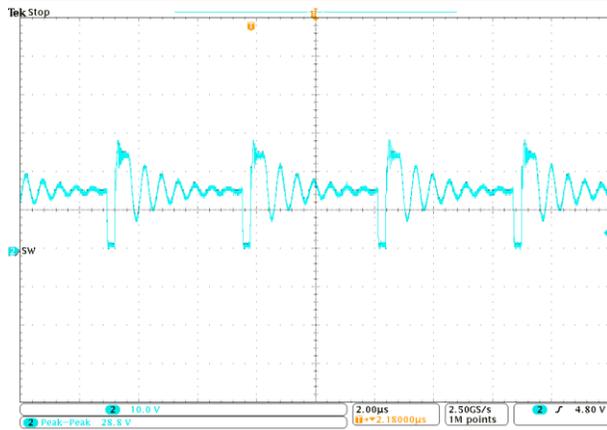


VIN=16V, Io=10mA

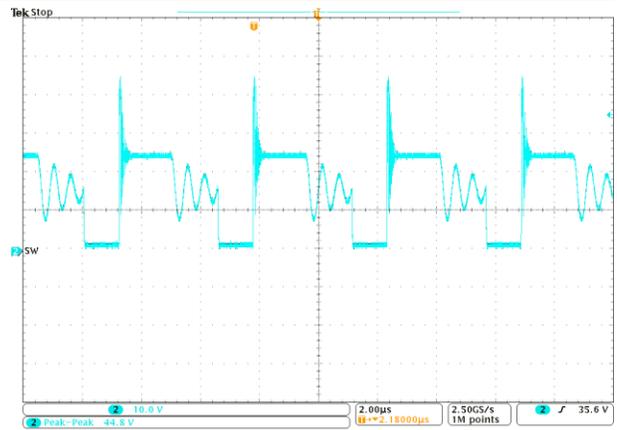


VIN=16V, Io=400mA


6.4 Diode Voltage

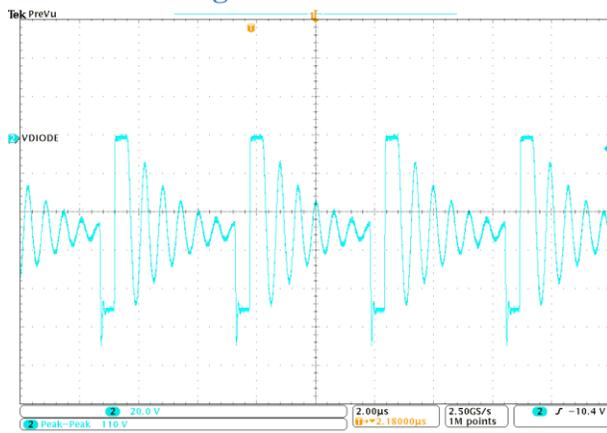


VIN=9V, Io=10mA

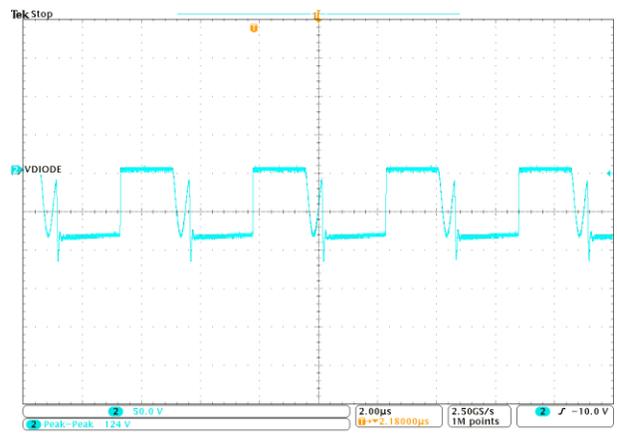

VIN=9V, Io=400mA

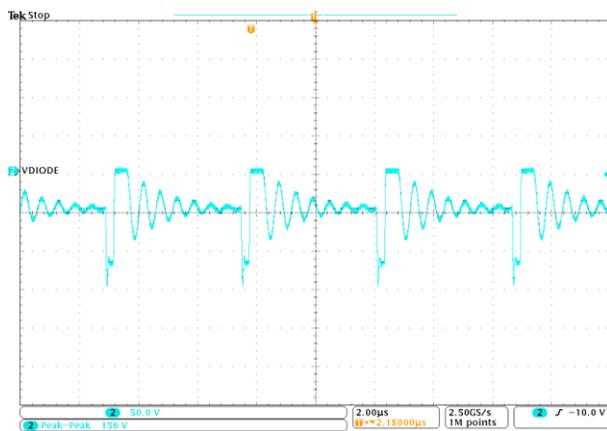

VIN=16V, Io=10mA

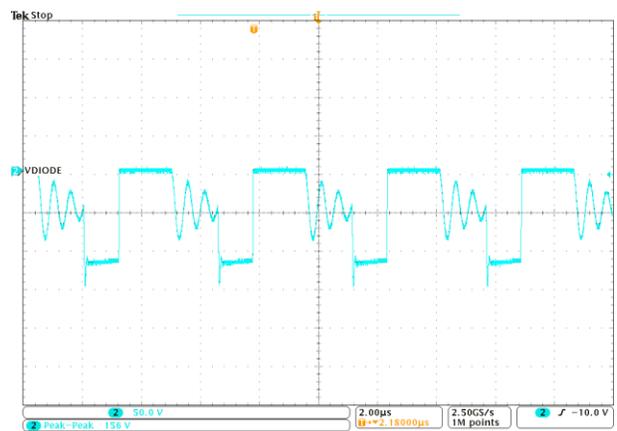

VIN=16V, Io=400mA

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated