

# LM25574,LM25576

?????40V????????????????????



Literature Number: ZHCA406

# POWER | *designer*

Expert tips, tricks, and techniques for powerful designs

No. 117

Feature Article.....1-7

Emulated Current Mode  
SIMPLE SWITCHER®  
Regulators .....2

WEBENCH® Tools for  
SIMPLE SWITCHER  
Designs .....4

PWM Buck Regulator.....6

Power Design Tools.....8

## Overcoming Challenges in Designing Step-Down Regulator Applications with $\geq 40V$ Input Voltage

— By Robert Bell, Applications Engineer

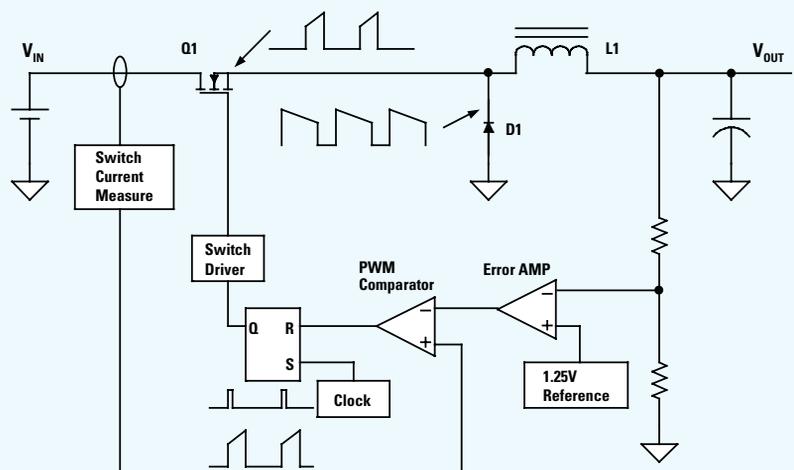


Figure 1. Buck Regulator Using Current Mode Control

Switching regulators are commonly used to step-down a higher level, unregulated input voltage to a regulated output voltage. In applications requiring DC-DC conversion from a relatively high input voltage, a switching regulator will dramatically improve conversion efficiency relative to linear regulator alternatives. Two of the most common transformer based DC-DC converter topologies are the Flyback and Forward. These topologies are very effective for high input to output step-down ratios since the transformer turns ratio can be set to accomplish the majority of the step-down conversion. For example, the conversion equation for a Forward converter is approximately:  $V_{OUT} = V_{IN} \times D \times N_s/N_p$

Where D is the duty cycle of the modulating switch, and  $N_s$  and  $N_p$  are the quantities of the transformer secondary and primary turns. For  $V_{IN} = 66V$


**NEXT ISSUE:**  
Powering Digital ICs

 **National  
Semiconductor**  
The Sight & Sound of Information



# Dial in Your Power Supply
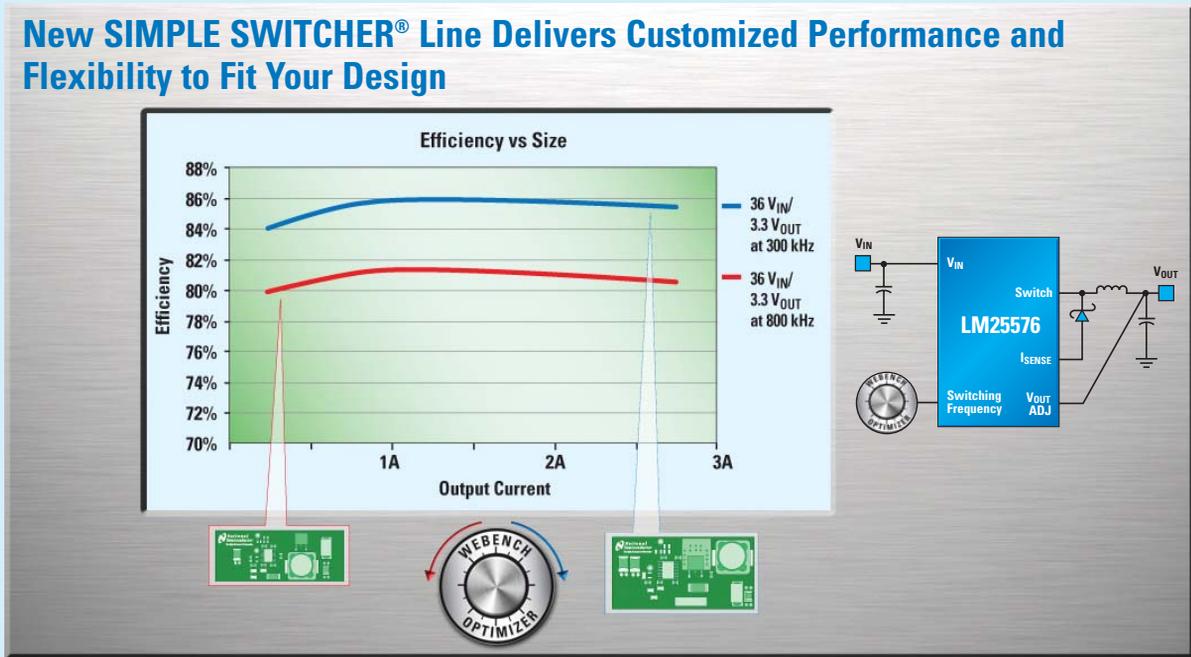
## New SIMPLE SWITCHER® Line Delivers Customized Performance and Flexibility to Fit Your Design



Product ID	Eval Board ID	V <sub>IN</sub> Range (V)	V <sub>OUT</sub> (V) Min	I <sub>OUT</sub> (A)	f <sub>SWITCH</sub> Range	Packaging
LM5576	LM5576EVAL	6 to 75	1.225	3	50 kHz to 500 kHz	TSSOP20-EP
LM25576	LM25576EVAL	6 to 42	1.225	3	50 kHz to 1 MHz	TSSOP20-EP
LM5575	LM5575EVAL	6 to 75	1.225	1.5	50 kHz to 500 kHz	TSSOP16-EP
LM25575	LM25575EVAL	6 to 42	1.225	1.5	50 kHz to 1 MHz	TSSOP16-EP
LM5574	LM5574EVAL	6 to 75	1.225	0.5	50 kHz to 500 kHz	TSSOP-16
LM25574	LM25574EVAL	6 to 42	1.225	0.5	50 kHz to 1 MHz	TSSOP-16

### New Emulated Current Mode (ECM) SIMPLE SWITCHER Line

- NEW!** • High V<sub>IN</sub> to low V<sub>OUT</sub> step-down ratios
- NEW!** • Superior transient response
- Fast design, guaranteed performance and flexibility

Ideal for when you need to quickly design a power supply optimized for your design that is guaranteed to work

For **FREE** samples, datasheets, and more information, visit [switcher.national.com](http://switcher.national.com)

## Design Challenges In Step-Down Regulator Applications

and  $V_{OUT} = 3.3$  (20:1 step down) the transformer turns ratio ( $N_s/N_p$ ) can be set to 1:10, requiring the modulation switch duty cycle to be 50%. For a 500 kHz operation, the 50% duty cycle equates to a switch on-time of 1  $\mu$ s. For applications that do not require ground isolation, a Buck regulator is a more desirable topology. The buck topology provides a lower cost solution since it does not require a transformer. The conversion equation for a buck regulator is simply:  $V_{OUT} = V_{IN} \times D$

Buck regulator applications with a high input to output step-down ratio require a small duty cycle. Coupled with high-frequency operation, the on-time for the modulating switch becomes very small. The high frequency and high step down ratio imposes significant challenges for the pulse-width modulation (PWM) controller. A buck regulator with  $V_{IN} = 66V$  and  $V_{OUT} = 3.3V$  operating at 500 kHz will require an on-time of 100 ns.

Common modulation control methods often used in buck regulators include Voltage Mode (VM), Current Mode (CM), and Constant On-Time (COT) control. Current-mode control provides ease of loop compensation and inherent line feed-forward compensation which make this method a favorite among power designers. Voltage-mode control is typically less noise sensitive but under-performs current mode in transient response and ease of stabilization. Constant On-Time control eliminates most of the stability-related issues and responds well to line and load transients. However, COT controlled regulators do not operate at constant switching frequency and cannot be synchronized to an external clock.

*Figure 1* shows the block diagram of a buck regulator utilizing the current-mode control method. The output voltage is monitored and

compared to a reference, with the resulting error signal applied to the PWM. The origin of the modulating ramp is where voltage mode and current mode control differ. The modulating ramp used in current mode control is a signal proportional to the buck switch current. The inductor current flows through the buck switch during the switch on-time. During this time, the inductor current waveform has a positive slope of  $(V_{IN} - V_{OUT})/L$ . An accurate, fast measurement of the buck switch current is necessary to create the modulating ramp signal. The main disadvantage of current-mode control is the difficulties encountered creating the buck switch current signal.

Propagation delays and noise susceptibility make it almost impossible to use conventional current-mode control for high input voltage, large step-down buck regulator applications where very small on-times are required. Measuring the buck switch current is challenging. The measurement techniques commonly used are, make a voltage measurement across a shunt resistor or the buck switch 'on' resistance or use a current mirror circuit coupled to the buck switch. Each method requires a level shift to transpose the measured signal down to the ground reference for application to the PWM comparator. Even with the best design practices, current sense and level shift circuits will add a significant propagation delay. Another challenge is, when the buck switch is turned on, the free-wheel diode (D1) will turn off. A reverse recovery current will flow through the diode and the buck switch, causing a leading edge current spike and an extended ringing period. This spike can cause the PWM comparator to prematurely trip, causing erratic operation. The most common solution is to add filtering or leading edge blanking to the current sense signal. Attempts to filter or

# WEBENCH® Online Design Environment Makes SIMPLE SWITCHER® Designs Flexible

## LM2575x and LM5575x SIMPLE SWITCHER Regulators Offer Performance and Flexibility that's Easy to Use

### 1. Choose a part

- Input your design requirements
- Choose a recommended part from a customized list

### 2. Optimize your design

- Exchange parts to compare performance, size, and cost
- Use recommended components or create a custom BOM
- Adjust components and exercise operating values


### 3. Analyze it

- Simulate your circuit and evaluate performance using electrical and thermal simulations
- Overlay alternate circuits and compare results to get optimal performance

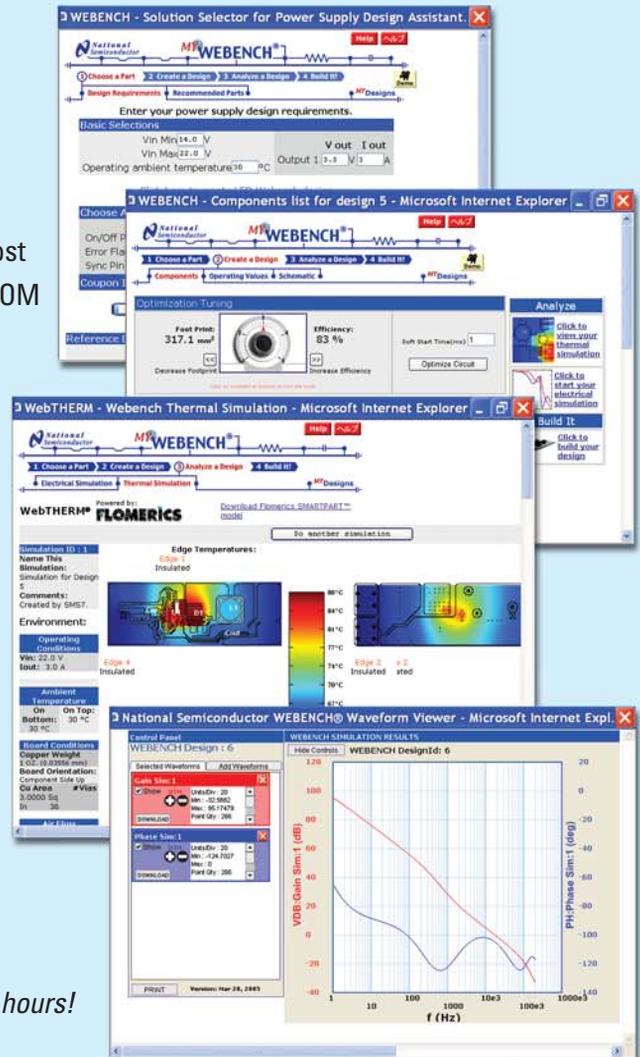
### 4. Build it

- Request samples and purchase parts or demo boards
- Receive your custom prototyping kit the next business day
- Download your automatically generated CAD files, assembly details, test instructions, and complete performance characteristics— instantly!

*Go from a design idea to a completed prototype in just 24 hours!*



**24 HOUR DELIVERY!**

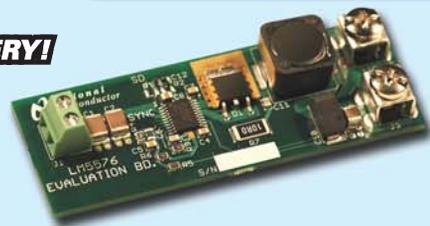

For FREE samples, datasheets, and more information on the SIMPLE SWITCHER family, contact us today at:

[switcher.national.com](http://switcher.national.com)

## Design Challenges In Step-Down Regulator Applications

blank this leading-edge spike increase the minimum controllable on-time of the buck switch.

### Creating an Emulated Current Sense Signal

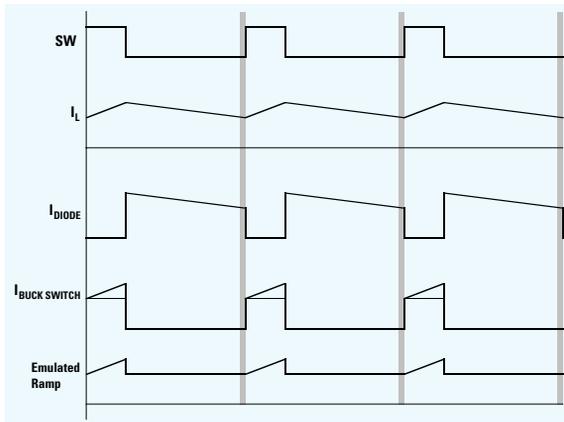


Figure 2. Buck Regulator Waveforms

The challenge of accurate and fast buck switch current measurement can be avoided with a new method that emulates the buck switch current without actually measuring the current. In a buck regulator, the inductor current is the sum of the buck switch current and free-wheel diode current, as shown in *Figure 2*. The buck switch current waveform can be broken down into two parts, a base or pedestal and a ramp. The pedestal represents the minimum inductor current value (or valley) over the switching cycle. The inductor current is at its minimum the instant the free-wheel diode turns off, as the buck switch turns on. The buck switch and the diode have the same minimum current value, occurring at the valley of the inductor current. A sample-and-hold measurement of the free-wheel diode current, sampled just prior to the turn-on of the buck switch can be used to capture the pedestal level information.

The other part of the buck switch current waveform is the ramp portion of the signal. The voltage across the inductor is the difference between the input ( $V_{IN}$ ) and output ( $V_{OUT}$ ) voltages when the buck switch is on. This voltage forces a positively ramping current through the inductor and the buck switch. The ramping current slope is equal to:  $di/dt = (V_{IN} - V_{OUT}) / L$ . An equivalent signal can be created with a voltage controlled current source and a capacitor. The rising voltage slope of a capacitor ( $C_{RAMP}$ ) driven by a current source ( $I_{RAMP}$ ) is equal to:  $dv/dt = I_{RAMP} / C_{RAMP}$ . If the current source is set proportional to the difference between the input and output voltages the capacitor ramp slope is equal to:  $dv/dt = K \times (V_{IN} - V_{OUT}) / C_{RAMP}$ , where  $K$  is a scale factor for the current source and  $C_{RAMP}$  is the ramp capacitor. The value of  $C_{RAMP}$  can be selected to set the capacitor voltage slope proportional to the inductor current slope.

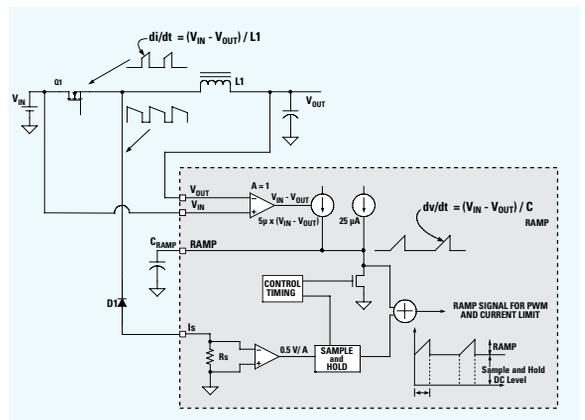


Figure 3. Emulated Current Mode Control Ramp Generator

*Figure 3* presents the block diagram of the LM25576, one of six new integrated buck regulators that implement the emulated current mode control scheme described above. The top portion

# ±1% Accurate, Ultra-High Precision PWM Buck Regulator


## LM3495 Controller Provides Design Flexibility and Reliable Protection Features for Sensitive Sub-Micron Processors

### LM3495 Features


- Input voltage from 2.9V to 18V
- Adjustable output from 0.6V to 5.5V
- Feedback accuracy: ±1% over temperature
- Switch node fault protection
- Hiccup mode current limit protection for reduced thermal design
- Internal soft-start with tracking capability
- 200 kHz to 1.5 MHz switching frequency, synchronizable to control system noise
- Available in TSSOP-16 packaging

AVAILABLE  
LEAD-FREE

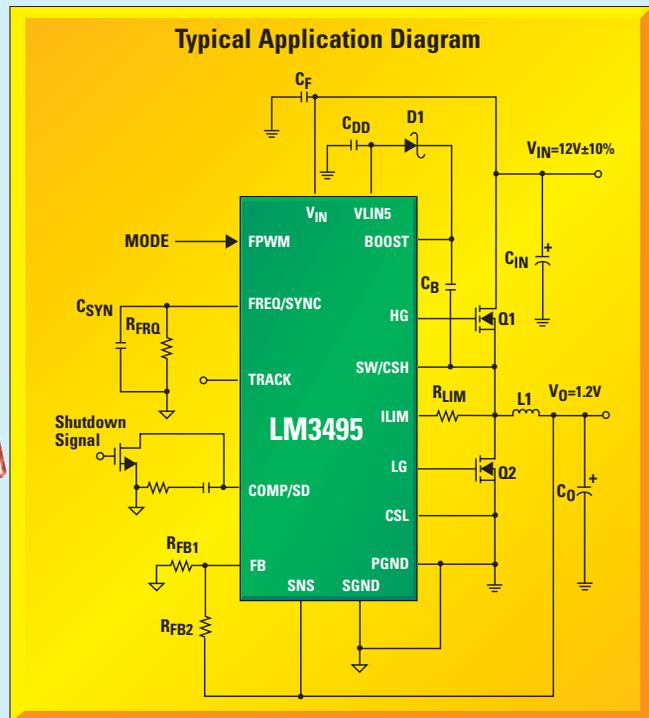Ideal for use in ASICs, FPGAs, DSPs, embedded controller power supplies, industrial applications, and high output current power modules


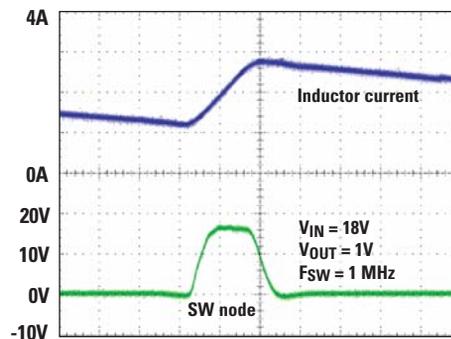
### Unique Emulated Peak Current-Mode Control Architecture Enables Jitter-Free Operation with Very Small On-Times



For FREE samples, datasheets and more go to  
[www.national.com/pf/LM/LM3495.html](http://www.national.com/pf/LM/LM3495.html)

## Design Challenges In Step-Down Regulator Applications

of the diagram shows the normal buck regulator power switching components. The free-wheel diode anode is connected to ground through the controller. A small value current sense resistor and amplifier are used to measure the diode current. The sample-and-hold circuit triggers each cycle, just prior to the turn-on of the buck switch, providing the pedestal portion of the emulated current sense signal.

The LM25576 senses the input voltage and the output voltage to generate a current source that charges an external ramp capacitor ( $C_{RAMP}$ ). Each cycle when the buck switch is turned on, the capacitor voltage rises linearly. When the buck switch is turned off, the ramp capacitor is discharged. For proper operation, the ramp capacitor is set proportional to the value of the output inductor. A good starting point is to select  $C_{RAMP} = L \times 10^{-5}$ , where the units of L are Henrys and  $C_{RAMP}$  are Farads. The last step necessary to complete the generation of the emulated buck switch current signal is to sum the pedestal information (from the sample and hold) to the ramp capacitor voltage signal. The final result is a controller that behaves like peak current mode control but without the delay and transient effects in the current sensing signal.

For applications operating with duty cycles greater than 50 percent, peak current mode controlled regulators are subject to sub-harmonic oscillation. By adding an additional fixed slope voltage ramp signal (slope compensation) to the current sense signal, this oscillation can be avoided. Referring to the ramp generator circuit, an additional fixed 25  $\mu$ A offset current provides additional fixed slope to the capacitor voltage ramp signal. For very high duty cycle applications the 25  $\mu$ A current source can be supplemented with a pull-up resistor or the ramp capacitor value can be decreased to increase

the ramp slope, preventing sub-harmonic oscillation.

### Overload Protection

The LM25576 output overload protection is accomplished with a dedicated current limit comparator that limits the emulated peak current on a cycle-by-cycle basis. The emulated current mode method provides the added benefit of capturing the inductor current information prior to the buck switch turn-on. If the current pedestal exceeds the current limit comparator threshold, the buck switch skips cycles allowing the inductor current additional time to decay, preventing current run-away.

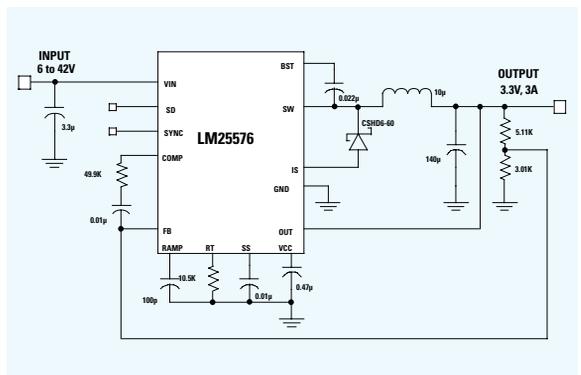


Figure 4. LM25576 Buck Regulator Schematic

Current-mode control offers many benefits. However in buck regulator applications requiring very short on-times the generation of the modulating ramp is very difficult. Through the use of an emulated ramp signal this challenge can be overcome. National has developed a new family of integrated regulators using the emulated current mode control technique.

For more information, visit [switcher.national.com](http://switcher.national.com) ■

# Power Design Tools

## Online Seminars

View the online seminar, "Integrated Buck Regulators Using ECM" at:


[www.national.com/onlineseminars](http://www.national.com/onlineseminars)


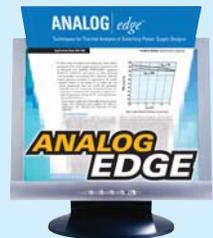
## Analog Edge<sup>SM</sup> App Note

National's monthly app note highlight

[edge.national.com](http://edge.national.com)



## Reference Designs

National's power reference design library provides a comprehensive library of practical reference designs to speed system design and time-to-market.

[www.national.com/refdesigns](http://www.national.com/refdesigns)




**National Semiconductor**  
2900 Semiconductor Drive  
Santa Clara, CA 95051  
1 800 272 9959

**Mailing address:**  
PO Box 58090  
Santa Clara, CA 95052

**Visit our website at:**  
[www.national.com](http://www.national.com)

**For more information,  
send email to:**  
[new.feedback@nsc.com](mailto:new.feedback@nsc.com)

## Don't miss a single issue!

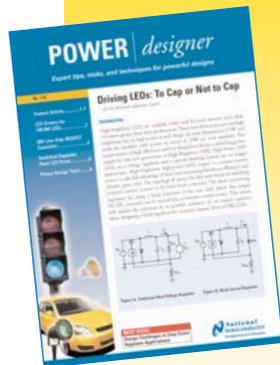

Subscribe now to receive email alerts when new issues of Power Designer are available:

[power.national.com/designer](http://power.national.com/designer)

Read our Signal Path Designer<sup>®</sup> online today at:

[signalpath.national.com/designer](http://signalpath.national.com/designer)



 **National  
Semiconductor**  
*The Sight & Sound of Information*

©2007, National Semiconductor Corporation. National Semiconductor, SIMPLE SWITCHER, WEBENCH, and Signal Path Designer are registered trademarks and Analog Edge is a service mark of National Semiconductor. All other brand or product names are trademarks or registered trademarks of their respective holders. All rights reserved.

550263-017

## 重要声明

德州仪器(TI) 及其下属子公司有权在不事先通知的情况下, 随时对所提供的产品和服务进行更正、修改、增强、改进或其它更改, 并有权随时中止提供任何产品和服务。客户在下订单前应获取最新的相关信息, 并验证这些信息是否完整且是最新的。所有产品的销售都遵循在订单确认时所提供的TI 销售条款与条件。

TI 保证其所销售的硬件产品的性能符合TI 标准保修的适用规范。仅在TI 保证的范围内, 且TI 认为有必要时才会使用测试或其它质量控制技术。除非政府做出了硬性规定, 否则没有必要对每种产品的所有参数进行测试。

TI 对应用帮助或客户产品设计不承担任何义务。客户应对其使用TI 组件的产品和应用自行负责。为尽量减小与客户产品和应用相关的风险, 客户应提供充分的设计与操作安全措施。

TI 不对任何TI 专利权、版权、屏蔽作品权或其它与使用了TI 产品或服务的组合设备、机器、流程相关的TI 知识产权中授予的直接或隐含权限作出任何保证或解释。TI 所发布的与第三方产品或服务有关的信息, 不能构成从TI 获得使用这些产品或服务的许可、授权、或认可。使用此类信息可能需要获得第三方的专利权或其它知识产权方面的许可, 或是TI 的专利权或其它知识产权方面的许可。

对于TI 的产品手册或数据表, 仅在没有对内容进行任何篡改且带有相关授权、条件、限制和声明的情况下才允许进行复制。在复制信息的过程中对内容的篡改属于非法的、欺诈性商业行为。TI 对此类篡改过的文件不承担任何责任。

在转售TI 产品或服务时, 如果存在对产品或服务参数的虚假陈述, 则会失去相关TI 产品或服务的明示或暗示授权, 且这是非法的、欺诈性商业行为。TI 对此类虚假陈述不承担任何责任。

TI 产品未获得用于关键的安全应用中的授权, 例如生命支持应用(在该类应用中一旦TI 产品故障将预计造成重大的人员伤亡), 除非各方官员已经达成了专门管控此类使用的协议。购买者的购买行为即表示, 他们具备有关其应用安全以及规章衍生所需的所有专业技术和知识, 并且认可和同意, 尽管任何应用相关信息或支持仍可能由TI 提供, 但他们将独力负责满足在关键安全应用中使用其产品及TI 产品所需的所有法律、法规和安全相关要求。此外, 购买者必须全额赔偿因在此类关键安全应用中使用TI 产品而对TI 及其代表造成的损失。

TI 产品并非设计或专门用于军事/航空应用, 以及环境方面的产品, 除非TI 特别注明该产品属于“军用”或“增强型塑料”产品。只有TI 指定的军用产品才满足军用规格。购买者认可并同意, 对TI 未指定军用的产品进行军事方面的应用, 风险由购买者单独承担, 并且独力负责在此类相关使用中满足所有法律和法规要求。

TI 产品并非设计或专门用于汽车应用以及环境方面的产品, 除非TI 特别注明该产品符合ISO/TS 16949 要求。购买者认可并同意, 如果他们在汽车应用中使用任何未被指定的产品, TI 对未能满足应用所需要求不承担任何责任。

可访问以下URL 地址以获取有关其它TI 产品和应用解决方案的信息:

	产品		应用
数字音频	<a href="http://www.ti.com.cn/audio">www.ti.com.cn/audio</a>	通信与电信	<a href="http://www.ti.com.cn/telecom">www.ti.com.cn/telecom</a>
放大器和线性器件	<a href="http://www.ti.com.cn/amplifiers">www.ti.com.cn/amplifiers</a>	计算机及周边	<a href="http://www.ti.com.cn/computer">www.ti.com.cn/computer</a>
数据转换器	<a href="http://www.ti.com.cn/dataconverters">www.ti.com.cn/dataconverters</a>	消费电子	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
DLP® 产品	<a href="http://www.dlp.com">www.dlp.com</a>	能源	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
DSP - 数字信号处理器	<a href="http://www.ti.com.cn/dsp">www.ti.com.cn/dsp</a>	工业应用	<a href="http://www.ti.com.cn/industrial">www.ti.com.cn/industrial</a>
时钟和计时器	<a href="http://www.ti.com.cn/clockandtimers">www.ti.com.cn/clockandtimers</a>	医疗电子	<a href="http://www.ti.com.cn/medical">www.ti.com.cn/medical</a>
接口	<a href="http://www.ti.com.cn/interface">www.ti.com.cn/interface</a>	安防应用	<a href="http://www.ti.com.cn/security">www.ti.com.cn/security</a>
逻辑	<a href="http://www.ti.com.cn/logic">www.ti.com.cn/logic</a>	汽车电子	<a href="http://www.ti.com.cn/automotive">www.ti.com.cn/automotive</a>
电源管理	<a href="http://www.ti.com.cn/power">www.ti.com.cn/power</a>	视频和影像	<a href="http://www.ti.com.cn/video">www.ti.com.cn/video</a>
微控制器 (MCU)	<a href="http://www.ti.com.cn/microcontrollers">www.ti.com.cn/microcontrollers</a>		
RFID 系统	<a href="http://www.ti.com.cn/rfidsys">www.ti.com.cn/rfidsys</a>		
OMAP 机动性处理器	<a href="http://www.ti.com/omap">www.ti.com/omap</a>		
无线连通性	<a href="http://www.ti.com.cn/wirelessconnectivity">www.ti.com.cn/wirelessconnectivity</a>		
	德州仪器在线技术支持社区		<a href="http://www.deyisupport.com">www.deyisupport.com</a>

邮寄地址: 上海市浦东新区世纪大道 1568 号, 中建大厦 32 楼 邮政编码: 200122  
Copyright © 2011 德州仪器 半导体技术 (上海) 有限公司