

LM3152,LMZ14201,LMZ14202,LMZ14203

????????????????????????????



Literature Number: ZHCA412

Comparing the Merits of Integrated Power Modules versus Discrete Regulators

— By Rich Rosen, Field Applications Engineer

Introduction

Modern integration technologies have brought about improvements to the modular DC-DC voltage regulator. Time to market, cost, size constraints, reliability, and design capabilities are among the motivating factors in choosing modular power versus a traditional controller plus external components design. Each approach has its advantages and disadvantages. And often times, it is not possible to predict which choice will better satisfy the list of design criteria until the design process has been completed for each approach.

What is a Modular Voltage Regulator?

The basic building blocks of a simple, non-isolated DC-DC switching voltage regulator can be seen in the schematics shown in **Figure 1**. PWM control, current switching, inductance, and capacitance for storing energy are all required. The modular regulator integrates the current switches and inductor while these are separate entities in a discrete design. Since the values of the energy-storing capacitors tend to be well over 1 μf , they are integrated less often into a monolithic package.

How to Choose between Discrete and Modular Power

Typically, the tradeoff is between cost of ownership, design effort, and performance.

The cost of ownership is the bill of materials (BOM) cost in addition to power designer labor fees plus test, potential redesign labor fees, and finally manufacturing/assembly costs. Other potential costs can include those associated with quality issues with an improperly designed supply.

Clearly, the design effort behind using a fully integrated power module is less than that of a discrete supply. But within the discrete regulator designs available, there exists a range of integration. For example, some regulators have built-in FET switches that remove the task of choosing the FETs and gate drive considerations. Controller ICs are the most flexible of choices but require a more expert level of design capability. Should one decide to tackle a non-modular approach, they should further investigate how “discretely” they wish to dive into the design. Fortunately, there are excellent tools available such as National Semiconductor’s WEBENCH® online design tool, that allow novice power supply designers to easily assemble discrete supply designs.

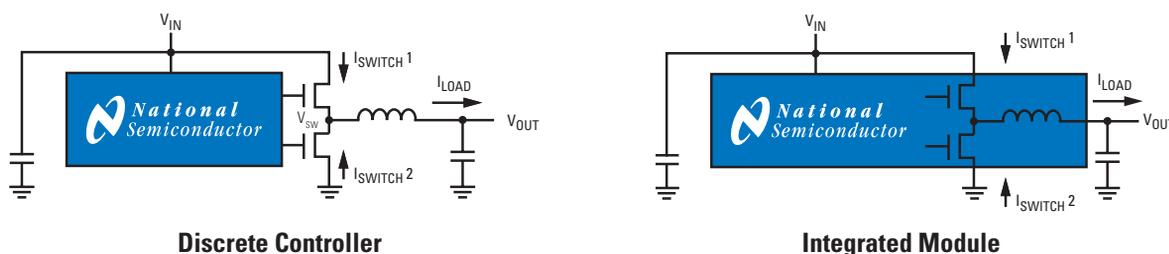


Figure 1. DC-DC Buck Regulator Integration Levels

DESIGN MADE EASY




EXPLORE & LEARN COMPARE & SELECT DESIGN & BUILD

Save time. Design with Ease.

New SIMPLE SWITCHER® Power Modules

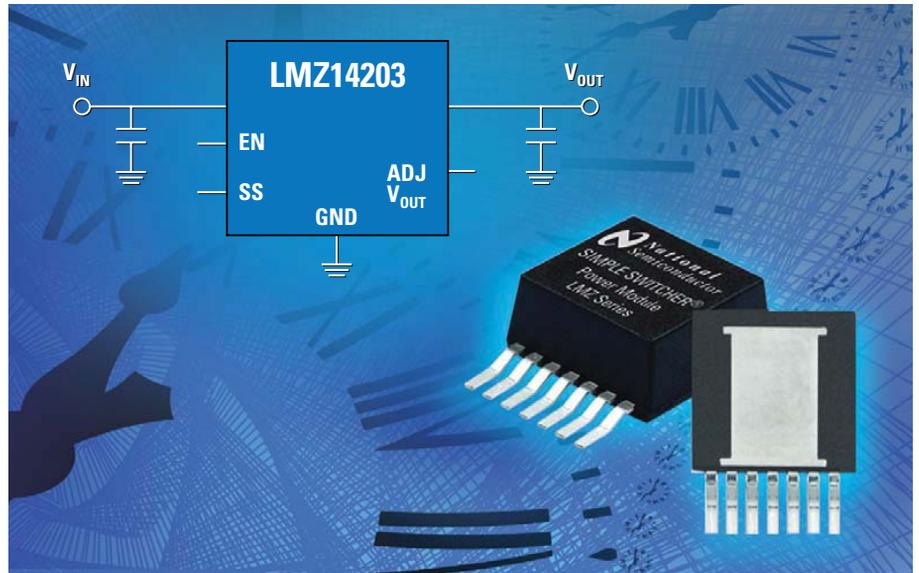SIMPLE SWITCHER power modules deliver a highly efficient, all-in-one power solution with superior EMI and thermal performance in an innovative package.



New, Industry-Leading Integrated Package

The easy-to-use package provides a single copper bottom for superior thermal performance and simplified prototyping and manufacturing. Load currents within each series are pin-to-pin and footprint-compatible for greater design ease.

Excellent EMI

Ideal for noise-sensitive applications, the LMZ series of power modules provide excellent radiated EMI performance and comply with CISPR22 Class B radiated emissions standards.

Superior Thermal Performance

Thermal performance with no airflow required, combined with low operating temperature and low system heat generation, make the power modules reliable and robust. Efficient heat dissipation technology eliminates the need for external heat sinks or fans that can add complexity and cost.

Comparing the Merits of Integrated Power Modules versus Discrete Regulators

Integrated modules streamline design and layout challenges but do not completely eliminate the process. At a minimum, the designer must evaluate the power specification of the design; this includes assessing requirements of input and output voltage, current, allowed temperature rise, noise issues, safety and emissions, and possibly other considerations. Even the simplest modular solution is not exempt from careful planning.

Circuit performance is multifaceted and application dependent. Where output noise might be most critical in an RF circuit supply, temperature rise and size of the circuit can be the driving specifications in a hearing aid.

Design Example


It would be impossible to examine the pros and cons of each approach with all possible values of voltage and current, but the following design analysis will expose the benefits and drawbacks of a modular design versus a design with a discrete controller IC for a common set of parameters. The design specifications will be the same between the two approaches:

- $V_{IN} = 24V$
- $V_{OUT} = 3.3V$
- Output Current = 3.0A maximum
- Ambient Temperature = 55°C

To demonstrate the relative ease of design between the two approaches, National's WEBENCH design tool will be used to design circuits around the LM3152 3.3V SIMPLE SWITCHER® controller and LMZ14203 SIMPLE SWITCHER power module. The easy-to-use WEBENCH tool offers too large a complement of design tools to highlight at this time, but it can be thoroughly examined online at national.com/webench. The desired output will focus on the schematic, BOM costs, component land area of the PCB, output noise analysis, efficiencies, and thermal simulation.

Schematics and Bill of Materials


Figure 2 shows the discrete design using the LM3152 3.3V controller. This design was accomplished using the WEBENCH tool and took about 30 minutes, including a few part changes to optimize for cost savings and some design simulation to verify proper operation. Design without the aid of a CAD program might take anywhere from a couple of hours to an entire day for circuit calculations and component searches.

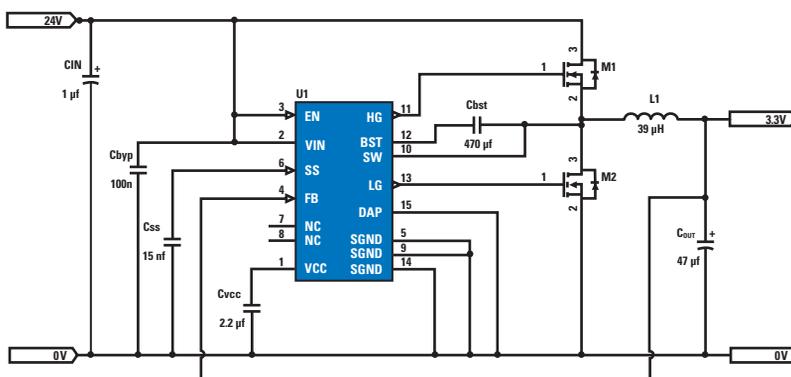

Part	Attribute	Price
Cbst	470 nF/16V	\$ 0.02
Cbyp	100 nF/50V	\$ 0.01
CIN	1 µF/50V	\$ 0.05
COUT	47 µF/16V	\$ 0.41
CSS	15 nF/50V	\$ 0.01
CVCC	2.2 µF/10V	\$ 0.02
L1	10 µH/4A	\$ 0.54
M1	80V/30 mΩ	\$ 0.39
M2	80V/30 mΩ	\$ 0.39
U1	LM3152MH-3.3	\$ 2.30
	Total BOM	\$ 4.14

Figure 2. Discrete Design—LM3152 3.3V Controller and Bill of Materials

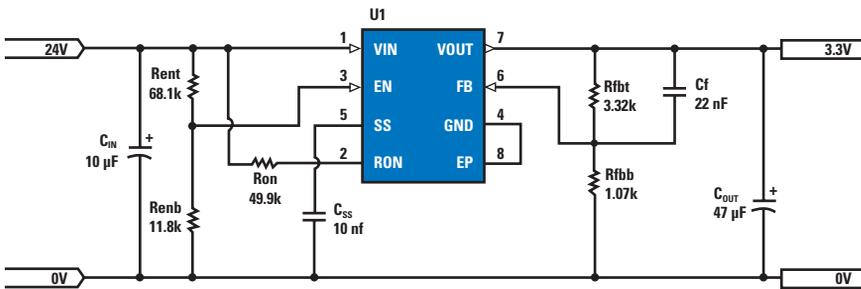Comparing the Merits of Integrated Power Modules versus Discrete Regulators



Part	Attribute	Price
Cf	22 nF/50V	\$ 0.01
CIN	10 µF/50V	\$ 0.43
COUT	47 µF/6.3V	\$ 0.18
CSS	10 nF/50V	\$ 0.02
Renb	11.8 KΩ	\$ 0.01
Rent	68.1 KΩ	\$ 0.01
Rfbb	1.07 KΩ	\$ 0.01
Rfbb	3.32 KΩ	\$ 0.01
Ron	49.9 KΩ	\$ 0.01
U1	LMZ14203	\$ 9.50
Total BOM		\$ 10.19

Figure 3. Modular Design—LMZ14203 Integrated Power Module and Bill of Materials

Figure 3 shows the schematic of the modular design using the LMZ14203 integrated power module. With fewer design choices to make, and limited opportunities for error, the design process is almost instantaneous with the WEBENCH design tool. The data sheet provides instruction on choosing the capacitors and resistors. The task of searching through catalogs for the FETs and the inductor is eliminated.

Comparing the BOM cost between the two designs, there is clearly a cost benefit to the discrete design. Note that the power module price is based on a 500-piece list price, whereas the controller price is based on a 1000-quantity list price. All costs shown are generated by the WEBENCH tool and are published catalog prices, typically at 1000-unit or cut-tape quantities.

Simplicity of PCB Layout

Figure 4 shows evaluation boards that represent the current design examples. The “art” of laying out a switching regulator lies in reducing the length and size of the high-current, high-frequency nodes, as well as properly managing the paths of the return currents. Any PCB CAD operator can put together a “working” supply. Ensuring the supply is robust and operating with minimal noise emissions requires careful planning and knowledge of the circuit operation. It should be intuitively obvious that the modular design is far less prone to layout mistakes.

Another advantage of the PCB layout for some modular designs is the ability to route an unbroken top copper plane underneath the die. Maximum heat conduction between the die and the top copper plane is always an important goal to keep the junction temperatures as



Integrated Power Module



Discrete Controller

Figure 4. Evaluation Boards for Modular and Discrete Solutions

Design Type	WEBENCH® Footprint (Single-Side Layout)	50% Packing Factor	Eval Board Comparison (Single-Side Layout)
Discrete	526 mm ² / 0.815 in ²	1.22 in ²	1.4 in ²
Modular	374 mm ² / 0.58 in ²	0.87 in ²	0.902 in ²

Figure 5. Component Land Area Comparison Table

cool as possible. In the case of National’s LMZ family of power modules, a large-geometry exposed pad of ground potential is spatially separated from the other signal pins. The LMZ14203 evaluation board in **Figure 4** illustrates the ease of providing unbroken top copper to the exposed pad underneath the module.

Component Land Area

Component PCB “footprint” is given in units of mm² by the WEBENCH tool. It includes a 1 mm per-side margin to allow for clearance. The table in **Figure 5** summarizes the total component footprint and adds an additional 50% packing factor to include traces and open spaces. All dimensions are for single-side layout.

Efficiency and Thermal Simulation

The WEBENCH thermal simulator outputs represent operating conditions of 24 V_{IN}, 3.3 V_{OUT}, 3A output current, 55°C ambient temperature, no fan, and 1.5 oz copper on both sides. Thermal graphs show a generic layout and do not represent the maximum packing density possible.

It is clear from the efficiency plots and the thermal images in **Figures 6** and **7** that the discrete design is more efficient and will operate with less heat dissipation compared to the modular design. Of course, this is just one operating point.

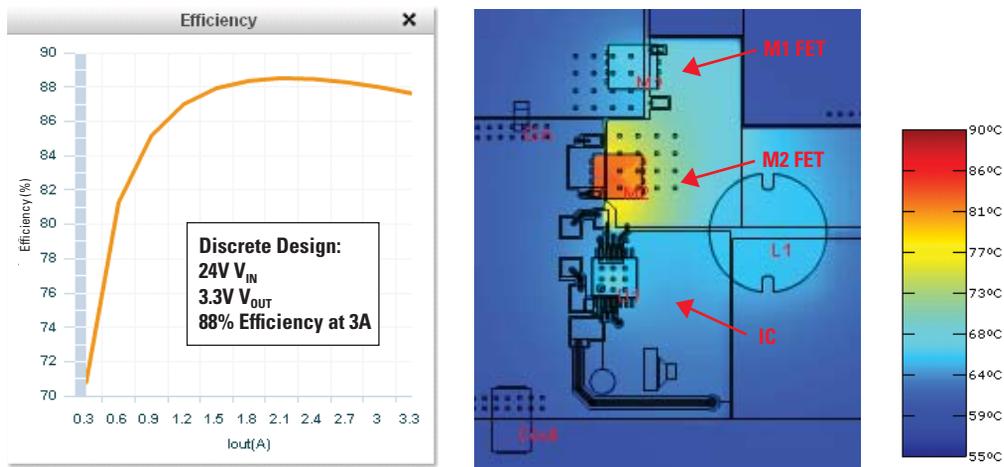


Figure 6. WEBENCH Simulation Output for a Discrete Design

Comparing the Merits of Integrated Power Modules versus Discrete Regulators

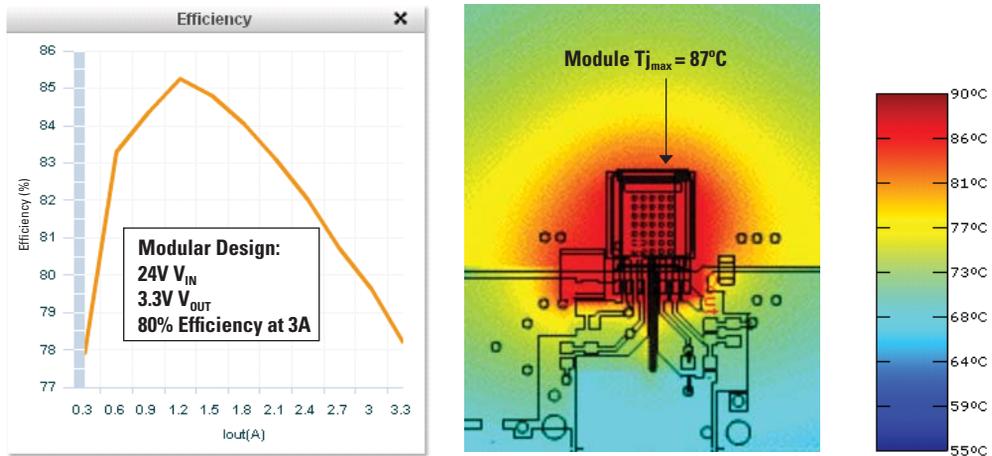


Figure 7. WEBENCH Simulation Output for a Modular Design

An advantage of the discrete design is the ability to optimize the FET selection for the specified operating voltage and output current. Also, it is important to remember that these temperatures are at 55°C raised ambient. With a maximum T_j of 125°C, there remains an additional 38°C of safety buffer for the modular design.


Output Noise and Emissions

Since there are many ways to quantify noise generated from switching supplies, this discussion will be limited to comparing the output voltage noise between the two designs. In addition, it would be an erroneous assumption to say that one approach is always noisier

than the other. Factors such as inductor size, input voltage, switching frequency, and capacitor Equivalent Series Resistance (ESR) play dominant roles in the resultant output voltage ripple.

There is, however, a distinct advantage in modular designs since the circuit traces connecting the regulator components are minimized far more than is possible in a discrete design.

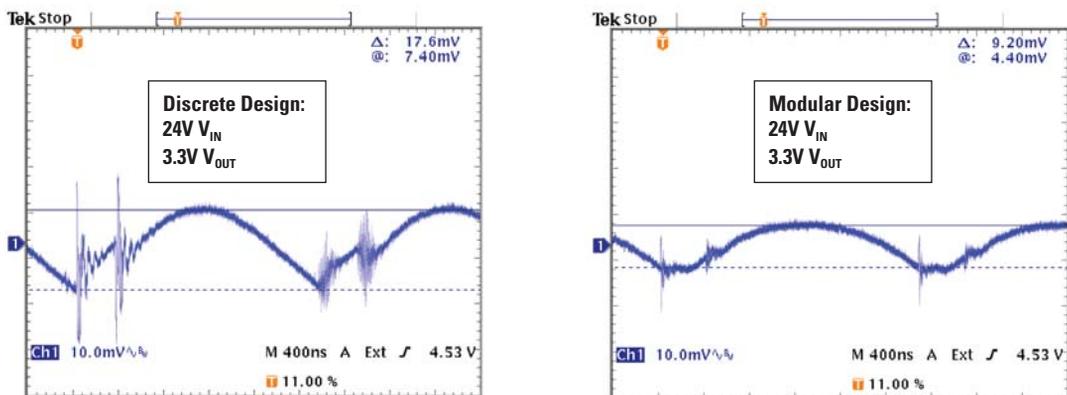The LMZ family of integrated modules utilizes a three-dimensional stack of silicon and shielded inductor to minimize trace length and inductance. Scope plots of the output voltages are shown in **Figure 8**.



Note: AC-coupled output noise. BW = 150 MHz. Very low inductance probe across output capacitors.

Figure 8. Output Ripple Noise Measurement Taken from Evaluation Boards

For both of these outputs, it is possible to realize even lower voltage ripple by lowering the total capacitor ESR. This can be achieved by obtaining a more expensive capacitor or adding more capacitance in parallel. The difference to notice is the amount of very-high-frequency noise “spikes” that appear in the discrete design. All of the additional parasitic inductance and capacitance of the trace elements create high-frequency spikes that occur in the output and also as conducted and radiated noise that can fail noise emissions tests.

Reliability Considerations

Circuit failures of a working power supply design can be grouped into three categories—initial assembly errors, lack of protection against misuse (overloaded outputs, excessive input voltages, etc.), and shortened lifetime component failures. Both discrete and modular designs are subject to all three categories, but it is often the case where the modular design incorporates a more extensively thought-out set of protection

mechanisms since the entire circuit is “planned” by a designer and the module manufacturer will subject the circuit to a much more rigorous set of testing than the typical end user will expose to their supply.

Modular designs have a significant advantage when it comes to comparing the likelihood of assembly errors such as incorrect components, unstuffed components, and bad solder joints. The modules are always tested before they are sold for assembly into a printed circuit board.

Summary

The pros and cons of discrete versus modular voltage regulator design for the previous design example are summarized in the following table. This “scorecard” will generally hold true for many DC-DC regulator applications. Exceptions to this example will occur often, especially since design specifications often deviate from common voltage and current ranges.

Consideration		Modular Approach	Discrete Approach	Comment
Costs	Cost of Design		✓	Initial cost much less for discrete design Time to market might offset differences significantly
	Reliability of Design	✓		Assembly errors greatly reduced in modular design Modular design subject to higher levels of testing
	Cost of Ownership	Depends upon factors such as quantities, quality of assembly line, and purchasing consistency		
Ease of Design	Design Simplicity	✓		Always easier, especially if CAD tool unavailable
	Simplicity of PCB Layout	✓		Always easier, difficult to make mistakes
	Design Effort	Schematic, parts sourcing, and PCB layout are all easier		
Performance	Design Size	✓		Usually smaller with modular design
	Thermal Advantages		✓	Ability to optimize components allows flexibility in design
	Output Noise, Ripple	✓	✓	For this design, modular was quieter, but there is control over ripple noise with choice of component value
	Output Voltage, RF	✓		Modular designs are inherently quieter due to small node length/size
	RF Emissions / Compliance	✓		As above, National’s SIMPLE SWITCHER power modules are predesigned to pass EN55022 and equivalent compliance testing
	Circuit Performance	More performance metrics available, but not listed above; extremely application dependent		

Visit national.com/power to learn more about National’s complete family of power modules and controllers.

Power Design Tools



Design, build, and test analog circuits in this online design and prototyping environment.
national.com/webench



Expand your knowledge and understanding of analog with our free online educational training tool.
national.com/training



National's monthly analog design technical journal.
national.com/edge

Reference Design Library

Access the complete library of reference designs covering an array of applications and topologies supporting National's wide range of analog solutions.

national.com/refdesigns

National Semiconductor
2900 Semiconductor Drive
Santa Clara, CA 95051
1 800 272 9959

Mailing address:
PO Box 58090
Santa Clara, CA 95052

Visit our website at:
national.com

**For more information,
send email to:**
new.feedback@nsc.com

Don't miss a single issue!

Subscribe now to receive email alerts when new issues of Power Designer are available:

national.com/powerdesigner

Read our Signal Path Designer® online today at:

national.com/spdesigner



重要声明

德州仪器(TI) 及其下属子公司有权在不事先通知的情况下, 随时对所提供的产品和服务进行更正、修改、增强、改进或其它更改, 并有权随时中止提供任何产品和服务。客户在下订单前应获取最新的相关信息, 并验证这些信息是否完整且是最新的。所有产品的销售都遵循在订单确认时所提供的TI 销售条款与条件。

TI 保证其所销售的硬件产品的性能符合TI 标准保修的适用规范。仅在TI 保证的范围内, 且TI 认为有必要时才会使用测试或其它质量控制技术。除非政府做出了硬性规定, 否则没有必要对每种产品的所有参数进行测试。

TI 对应用帮助或客户产品设计不承担任何义务。客户应对其使用TI 组件的产品和应用自行负责。为尽量减小与客户产品和应用相关的风险, 客户应提供充分的设计与操作安全措施。

TI 不对任何TI 专利权、版权、屏蔽作品权或其它与使用了TI 产品或服务的组合设备、机器、流程相关的TI 知识产权中授予的直接或隐含权限作出任何保证或解释。TI 所发布的与第三方产品或服务有关的信息, 不能构成从TI 获得使用这些产品或服务的许可、授权、或认可。使用此类信息可能需要获得第三方的专利权或其它知识产权方面的许可, 或是TI 的专利权或其它知识产权方面的许可。

对于TI 的产品手册或数据表, 仅在没有对内容进行任何篡改且带有相关授权、条件、限制和声明的情况下才允许进行复制。在复制信息的过程中对内容的篡改属于非法的、欺诈性商业行为。TI 对此类篡改过的文件不承担任何责任。

在转售TI 产品或服务时, 如果存在对产品或服务参数的虚假陈述, 则会失去相关TI 产品或服务的明示或暗示授权, 且这是非法的、欺诈性商业行为。TI 对此类虚假陈述不承担任何责任。

TI 产品未获得用于关键的安全应用中的授权, 例如生命支持应用(在该类应用中一旦TI 产品故障将预计造成重大的人员伤亡), 除非各方官员已经达成了专门管控此类使用的协议。购买者的购买行为即表示, 他们具备有关其应用安全以及规章衍生所需的所有专业技术和知识, 并且认可和同意, 尽管任何应用相关信息或支持仍可能由TI 提供, 但他们将独力负责满足在关键安全应用中使用其产品及TI 产品所需的所有法律、法规和安全相关要求。此外, 购买者必须全额赔偿因在此类关键安全应用中使用TI 产品而对TI 及其代表造成的损失。

TI 产品并非设计或专门用于军事/航空应用, 以及环境方面的产品, 除非TI 特别注明该产品属于“军用”或“增强型塑料”产品。只有TI 指定的军用产品才满足军用规格。购买者认可并同意, 对TI 未指定军用的产品进行军事方面的应用, 风险由购买者单独承担, 并且独力负责在此类相关使用中满足所有法律和法规要求。

TI 产品并非设计或专门用于汽车应用以及环境方面的产品, 除非TI 特别注明该产品符合ISO/TS 16949 要求。购买者认可并同意, 如果他们在汽车应用中使用任何未被指定的产品, TI 对未能满足应用所需要求不承担任何责任。

可访问以下URL 地址以获取有关其它TI 产品和应用解决方案的信息:

	产品		应用
数字音频	www.ti.com.cn/audio	通信与电信	www.ti.com.cn/telecom
放大器和线性器件	www.ti.com.cn/amplifiers	计算机及周边	www.ti.com.cn/computer
数据转换器	www.ti.com.cn/dataconverters	消费电子	www.ti.com/consumer-apps
DLP® 产品	www.dlp.com	能源	www.ti.com/energy
DSP - 数字信号处理器	www.ti.com.cn/dsp	工业应用	www.ti.com.cn/industrial
时钟和计时器	www.ti.com.cn/clockandtimers	医疗电子	www.ti.com.cn/medical
接口	www.ti.com.cn/interface	安防应用	www.ti.com.cn/security
逻辑	www.ti.com.cn/logic	汽车电子	www.ti.com.cn/automotive
电源管理	www.ti.com.cn/power	视频和影像	www.ti.com.cn/video
微控制器 (MCU)	www.ti.com.cn/microcontrollers		
RFID 系统	www.ti.com.cn/rfidsys		
OMAP 机动性处理器	www.ti.com/omap		
无线连通性	www.ti.com.cn/wirelessconnectivity		
	德州仪器在线技术支持社区		www.deyisupport.com

邮寄地址: 上海市浦东新区世纪大道 1568 号, 中建大厦 32 楼 邮政编码: 200122
Copyright © 2011 德州仪器 半导体技术 (上海) 有限公司