

**说明**

此参考设计可产生用于评估转换器稳定性所需的快速负载瞬态信号。电路板包含三个可经过调节或未经调节的负载瞬态发生器，并能够支持不同的负载配置。负载可以是以地为基准的负载或是浮动负载。

资源

TIDA-01379
CSD17304Q3
CSD25404Q3
CSD18534Q5A
OPA365

设计文件夹
产品文件夹
产品文件夹
产品文件夹
产品文件夹

特性



- 快速瞬态
- 浮动负载和以地为基准的负载
- 稳压
- 隔离式

应用

- 电源测试



咨询我们的 E2E 专家

  



该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

1 System Description

Power supplies are present in all electronic devices where they power the needed supply rails. These rails need to be maintained at a certain level under the specified operating conditions, including load transient events. A load transient event happens when the load current changes suddenly from one level to another. The response of a converter to such changes permits to assess its stability.

The TIDA-01379 design board includes three different circuits that are used to perform load transient measurements for different load configurations. These circuits provide faster rise and fall times than commercial transient generators at a lower cost.

1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Load current	$\geq 500 \text{ mA}$
Rise and fall time	$< 1 \mu\text{s}$
Maximum load output voltage	20 V

2 System Overview

2.1 Block Diagram

 


图 1. TIDA-01379 Block Diagram

2.2 **Highlighted Products**

2.2.1 CSD17304Q3

The CSD17304Q3 device is a 30-V, N-channel, NexFET™ power MOSFET with the following features:

- Optimized for 5-V gate drive
- Ultra-low Q_g and Q_{gd}
- Low thermal resistance
- Avalanche rated
- Pb-free terminal plating

For further details, see the [CSD17304Q3 product page](#).

2.2.2 CSD25404Q3

The CSD25404Q3 device is a -20-V, P-channel, NexFET power MOSFET with the following features:

- Ultra-low Q_g and Q_{gd}
- Low thermal resistance
- Low $R_{DS(on)}$
- Halogen free
- RoHS compliant

For further details, see the [CSD25404Q3 product page](#).

2.2.3 CSD18534Q5A

The CSD18534Q5A device is a 60-V, N-channel NexFET power MOSFET with the following features:

- Ultra-low Q_g and Q_{gd}
- Low thermal resistance
- Avalanche rated
- Logic level
- Pb-free terminal plating

For further details, see the [CSD18534Q5A product page](#).

2.2.4 OPA365

The OPA365 device is a rail-to-rail input and output operational amplifier with a gain bandwidth of 50 MHz. This amplifier has a slew rate of 25 V/ μ s and can settle to 0.01% in 0.3 μ s.

The OPA365 has the following features:

- Gain bandwidth: 50 MHz
- Zerø-crossover distortion topology:
 - Excellent THD+N: 0.0004%
 - CMRR: 100 dB (minimum)
 - Rail-to-rail input and output
 - Input 100 mV beyond supply rail

- Low noise: 4.5 nV/ $\sqrt{\text{Hz}}$ at 100 kHz
- Slew rate: 25 V/ μs
- Fast settling: 0.3 μs to 0.01%
- Precision:
 - Low offset: 100 μV
 - Low input bias current: 0.2 pA
- 2.2- to 5.5-V operation

For further details, see the [OPA365 product page](#).

2.3 System Design Theory

The following sections present three ways to generate fast transient signals for converter stability tests. These designs provide transient signals with a rise and fall time of less than 1 μs for load steps from 0 to 500 mA with a limited bill of materials.

2.3.1 Open-Loop Load Transient Generator

[图 2](#) and [图 3](#) are open-loop load transient generators for ground-referenced positive or negative outputs. These generators are mainly composed of the following:

- An NMOS transistor for positive outputs
- A PMOS transistor for negative outputs
- A sense resistor to measure the load current

The transistors Q1 and Q2 are operated in their linear regions as variable resistors. The adjustment of the gate voltage permits to control the value of the resistance between drain and source, thereby setting the load current. A pulse waveform with the right levels must be applied on the IN pin to get the required load step. A pulse signal with a low duty cycle must be used to optimize the power dissipation on the transistor and the sense resistor and to avoid overheating of the board. Because this simple transient generator is always stable, it is recommended to use it for the first stability assessment of a converter when it is unknown if the converter is stable or not.

 


图 2. Open-Loop Load Transient Generator for Positive Outputs

 


图 3. Open-Loop Load Transient Generator for Negative Outputs

2.3.2 Regulated Load Transient Generator

The circuits presented in [节 2.3.1](#) are unregulated, and the user needs to estimate and set the gate voltage input that is needed for each required load steps. To avoid this manual tuning, the regulated load transient generator on [图 4](#) is used. It is composed of mainly the following:

- An NMOS transistor
- An operational amplifier that is driving the gate of the transistor
- A transformer for galvanic isolation
- A sense resistor to measure the load current step

The gate of the transistor is driven by the amplifier and the feedback loop is between the transistor's source and the negative input of the amplifier. The transient load that is applied to the device under test (DUT) is then proportional to the sense resistor value and the amplifier input voltage. In this TI Design, $R_{SENSE} = 1 \Omega$, which means that this design has a 1:1 equivalence between the control input voltage and the load step value.

A 1:1 transformer is added to isolate the input from the signal generator and to give the possibility to apply a transient to ground-referenced DUTs as well as floating DUTs. Adding this transformer creates overshoots and undershoots on the input signal applied to the non-inverting input of the amplifier. These are damped with the addition of a resistor ($10 \text{ k}\Omega$) across the transformer's secondary, which leads to some power loss.

To avoid that the transformer enters into saturation and a distortion of the input signal, 50% duty cycle pulse signals with symmetrical positive and negative levels must be used as input.

To select the amplifier, consider the following parameters to meet requirements in [表 1](#):

- Bandwidth $f_{3dB} > 0.35/tr$, with tr being the rise time of the input signal
- Slew rate that must be high enough to support the maximum rate of change of the amplifier's output
- Supply voltage range that shall permit to reach the expected amplifier's output voltage for the required maximum load
- Amplifier's output load capability

Consider the following parameters when selecting the transformer:

- Input level that must allow to transmit the input signal without distortion
- Frequency range of operation and volt-microsecond rating. There must be enough time between the rising and falling edges of the pulse input signal to see the complete converter response.

 


图 4. Closed-Loop Load Transient Generator

3 Hardware, Testing Requirements, and Test Results

3.1 Hardware

The TIDA-01379 design board is composed of three different load transient generators that can be split up and used separately.

3.1.1 Connectors, Jumpers, and Test Points

表 2, 表 3, and 表 4 give an overview of the connector and jumper connections of the evaluation board.

表 2. Connector Overview Circuit 1 ⁽¹⁾

CONNECTOR		SIGNAL	PIN	DESCRIPTION
J1	Positive power supply	VCC+	1, 2	Positive power supply
J2	Ground	GNDB	1, 2	Secondary ground or DUT negative output
J3	Negative power supply	VCC-	1, 2	Negative power supply
J4	DUT output voltage	OUTP OUTN	1, 2, 3 4, 5, 6	DUT positive output DUT negative output
J5	Input	VIN GNDA	1, 2 3, 4	Signal generator input Primary ground
J6	Load transient voltage	V_MEAS GNDB	1 2	Load transient voltage Secondary ground or DUT negative output

⁽¹⁾ Circuit 1 corresponds to the top part of the board with the title "Pos_Neg_Output"

表 3. Connector Overview Circuit 2 ⁽¹⁾

CONNECTOR		SIGNAL	PIN	DESCRIPTION
J7	DUT output voltage	VOUT	1, 2, 3, 4	Negative output
		S-	5	Negative output sense
		GND	6, 7, 8, 9, 10	Ground
J8	DUT output voltage sense	S- GND	1 2	Negative output sense Ground
J9	Gate drive input	VIN	—	Signal generator input
J10	Load transient voltage	V_MEAS	—	Load transient voltage

⁽¹⁾ Circuit 2 corresponds to the middle part of the board with the title "Neg_Output"

表 4. Connector Overview Circuit 3 ⁽¹⁾

CONNECTOR		SIGNAL	PIN	DESCRIPTION
J11	DUT output voltage	VOUT	1, 2, 3, 4	Positive output
		S+	5	Positive output sense
		GND	6, 7, 8, 9, 10	Ground
J12	DUT output voltage sense	S+ GND	1 2	Positive output sense Ground
J13	Gate drive input	VIN	—	Signal generator input
J14	Load transient voltage	V_MEAS	—	Load transient voltage

⁽¹⁾ Circuit 3 corresponds to the bottom part of the board with the title "Pos_Output"

3.2 Testing and Results

The three different circuits are used to evaluate the load transient response of the TPS65632 device. The TPS65632 is a triple-output (V_{POS} , V_{NEG} , and $AVDD$) power supply used to drive AMOLED displays.

3.2.1 Test Setup

To evaluate the different circuits, a signal generator, an oscilloscope, and a power supply are required.

3.2.2 Test Results

3.2.2.1 Positive Output

The circuit in [图 2](#) is used to evaluate the transient response of the VPOS boost converter. The load is connected between VPOS and GND as shown in [图 5](#). [图 6](#) shows that the converter is stable when a 500-mA load step with a rise and fall time of less than 250 ns is applied to it.

 


图 5. Board 3 Connection

 


图 6. Transient Response—Load Between VPOS and GND

3.2.2.2 Negative Output

The circuit in 图 3 is used to test the transient response of the VNEG inverting buck-boost converter as shown in 图 7. The load transient signal has an amplitude of 500 mA and a rise and fall time of less than 250 ns.

 


图 7. Board 2 Connection

 


图 8. Transient Response—Load Between VNEG and GND

3.2.2.3 Positive and Negative Outputs

The circuit in 图 4 permits to generate a load transient signal for ground referenced loads as well as floating loads. It is used to test the stability of the TPS65632 converters when a 500-mA load step is applied between VPOS and GND, between VNEG and GND, and between VPOS and VNEG. 图 9 shows how to connect the different loads. 图 10, 图 11, and 图 12 show that the 500-mA load step has different rise and fall times values of 25 ns and 320 ns, respectively.

 


图 9. Board 1 Connection

 


图 10. Transient Response—Load Between VPOS and GND

 


图 11. Transient Response—Load Between VNEG and GND

 


图 12. Transient Response—Load Between VPOS and VNEG

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [TIDA-01379](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01379](#).

4.3 Layout Prints

To download the layer plots, see the design files at [TIDA-01379](#).

4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01379](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01379](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01379](#).

5 Related Documentation

1. Texas Instruments, [TPS65632 Triple-Output AMOLED Display Power Supply](#), TPS65632 Datasheet (SLVSCY2)
2. Texas Instruments, [AN-1733 Load Transient Testing Simplified](#), SNOA507 Application Report (SNOA507)

5.1 商标

NexFET is a trademark of Texas Instruments.

All other trademarks are the property of their respective owners.

有关 TI 设计信息和资源的重要通知

德州仪器 (TI) 公司提供的技术、应用或其他设计建议、服务或信息，包括但不限于与评估模块有关的参考设计和材料（总称“TI 资源”），旨在帮助设计人员开发整合了 TI 产品的应用；如果您（个人，或如果是代表贵公司，则为贵公司）以任何方式下载、访问或使用了任何特定的 TI 资源，即表示贵方同意仅为该等目标，按照本通知的条款进行使用。

TI 所提供的 TI 资源，并未扩大或以其他方式修改 TI 对 TI 产品的公开适用的质保及质保免责声明；也未导致 TI 承担任何额外的义务或责任。TI 有权对其 TI 资源进行纠正、增强、改进和其他修改。

您理解并同意，在设计应用时应自行实施独立的分析、评价和判断，且应全权负责并确保应用的安全性，以及您的应用（包括应用中使用的所有 TI 产品）应符合所有适用的法律法规及其他相关要求。你就您的应用声明，您具备制订和实施下列保障措施所需的一切必要专业知识，能够（1）预见故障的危险后果，（2）监视故障及其后果，以及（3）降低可能导致危险的故障几率并采取适当措施。您同意，在使用或分发包含 TI 产品的任何应用前，您将彻底测试该等应用和该等应用所用 TI 产品的功能。除特定 TI 资源的公开文档中明确列出的测试外，TI 未进行任何其他测试。

您只有在为开发包含该等 TI 资源所列 TI 产品的应用时，才被授权使用、复制和修改任何相关单项 TI 资源。但并未依据禁止反言原则或其他法理授予您任何 TI 知识产权的任何其他明示或默示的许可，也未授予您 TI 或第三方的任何技术或知识产权的许可，该等产权包括但不限于任何专利权、版权、屏蔽作品权或与使用 TI 产品或服务的任何整合、机器制作、流程相关的其他知识产权。涉及或参考了第三方产品或服务的信息不构成使用此类产品或服务的许可或与其相关的保证或认可。使用 TI 资源可能需要您向第三方获得对该等第三方专利或其他知识产权的许可。

TI 资源系“按原样”提供。TI 兹免除对 TI 资源及其使用作出所有其他明确或默认的保证或陈述，包括但不限于对准确性或完整性、产权保证、无屡发故障保证，以及适销性、适合特定用途和不侵犯任何第三方知识产权的任何默认保证。

TI 不负责任何申索，包括但不限于因组合产品所致或与之有关的申索，也不为您辩护或赔偿，即使该等产品组合已列于 TI 资源或其他地方。对因 TI 资源或其使用引起或与之有关的任何实际的、直接的、特殊的、附带的、间接的、惩罚性的、偶发的、从属或惩戒性损害赔偿，不管 TI 是否获悉可能会产生上述损害赔偿，TI 概不负责。

您同意向 TI 及其代表全额赔偿因您不遵守本通知条款和条件而引起的任何损害、费用、损失和/或责任。

本通知适用于 TI 资源。另有其他条款适用于某些类型的材料、TI 产品和服务的使用和采购。这些条款包括但不限于适用于 TI 的半导体产品 (<http://www.ti.com/sc/docs/stdterms.htm>)、评估模块和样品 (<http://www.ti.com/sc/docs/samptersms.htm>) 的标准条款。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122
Copyright © 2017 德州仪器半导体技术（上海）有限公司