

# TI Designs: TIDA-01253

## 符合 CISPR 25 4 类标准的汽车类双路远程和本地 USB 端口参考设计



### 说明

此汽车媒体端口设计充分利用了符合 AEC-100 标准的模拟集成电路 (IC) 所组成的完整参考设计，能够帮助客户加快媒体端口系统开发速度。此参考设计专为同时需要本地端口和远程端口支持的汽车媒体端口（采用 USB BC1.2 规范）而设计。此设计打造了一款可靠灵活的解决方案，可让系统同时为两个端口充电，而且仍然可解决远程端口上的电压降问题。

### 资源

<a href="#">TIDA-01253</a>	设计文件夹
<a href="#">LM74610-Q1</a>	产品文件夹
<a href="#">LMS3655-Q1</a>	产品文件夹
<a href="#">TPS254900-Q1</a>	产品文件夹
<a href="#">TPS2511</a>	产品文件夹
<a href="#">LM358</a>	产品文件夹
<a href="#">CSD16408Q5C</a>	产品文件夹

### 特性


- LM74610-Q1 智能二极管模拟理想的二极管整流器，并在反极性情况下为下游器件提供保护
- TPS254900 和 TPS2511 分别通过 D+/D- 线路提供远程端口和本地端口协商，从而为电缆补偿的端口或典型的本地端口进行充电
- 系统中的组件提供了针对高达 40V 输入瞬态电压的电池短路保护和负载突降保护
- 汽车级 LMS3635-Q1 通过 AM 和 FM 频带外的可调开关频率来优化电源，并通过提供高达 5.5A 的连续电流支持两个端口，无需外部二极管或 MOSFET

### 应用


- 具有远程显示的汽车音响主机
- 远程媒体集线器



咨询我们的 E2E 专家

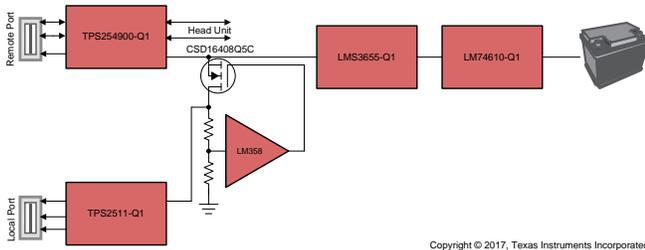

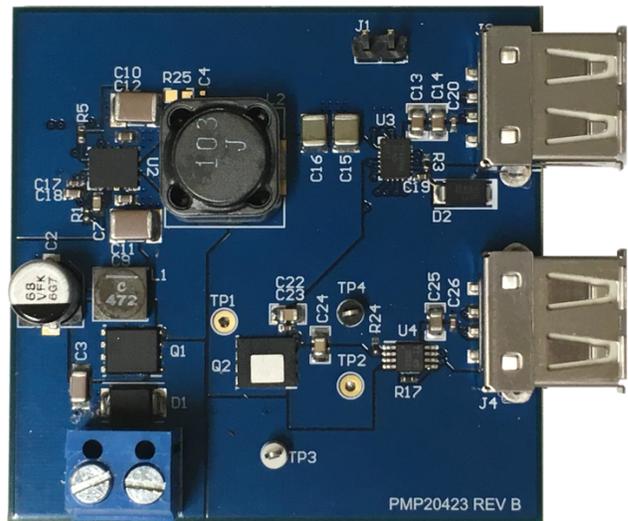Copyright © 2017, Texas Instruments Incorporated



该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

## 1 System Overview

### 1.1 System Description

This system is designed to allow a dual-USB type-A port from a head unit to provide cable compensation to a remote port while still operating within tight USB specifications on the local port. One port is a dedicated charging port (DCP) and the other is a charging downstream port (CDP) that allows the USB 2.0 data to pass to the head unit. A common challenge when trying to design for both a local and remote port using one input voltage is when the feedback loop for the remote port adjusts the voltage to compensate for the voltage drop across the long cable. This adjustment puts the local port voltage outside the required tolerances. To overcome this issue, use a very-low dropout regulator to maintain the local port regulation.


### 1.2 Key System Specifications

This design is specified to use a car battery input between 5.5 V and 36 V with a nominal voltage typically around 12 V to 14.5 V. Both USB type-A outputs ultimately support 5-V nominal; however, this design was created specifically such that the local port is within  $\pm 2.5\%$  of 5 V and the remote port is within  $\pm 2.5\%$  of 5 V after 2 m to 3 m of cable. The following 表 1 presents the key specifications for this design.

表 1. Key System Specifications

PARAMETER	COMMENTS	MIN	TYP	MAX	UNIT
<b>SYSTEM OPERATION</b>					
$V_{IN}$	Input voltage of system	5.5	14.5	36	V
$F_{sw}$	Switching frequency of DC-DC	—	400	—	kHz
$R_{DS(ON)-Remote}$	ON-resistance of power switch (TPS254900)	—	50	—	m $\Omega$
$R_{DS(ON)-local}$	ON-resistance of power switch (TPS2511)	—	70	120	m $\Omega$
$I_{OS-Remote}$	Short-circuit current limit of TPS254900	2.42	2.59	2.760	A
$I_{OS-Local}$	Short-circuit current limit of TPS2511	2.11	2.3	2.5	A
<b>OUTPUT VOLTAGES</b>					
$V_{Remote}$	Remote port voltage	5.081	5.087	5.092	V
$V_{Local}$	Local port voltage	4.875	5.00	5.125	V
$V_{BUS}$	Output of LM73605 with cable compensation adjustment	5.0	5.1	5.6	V
<b>OUTPUT CURRENT</b>					
$I_{OUT-Remote}$	VBUS load current of remote port	—	2.4	—	A
$I_{OUT-Local}$	VBUS load current of local port	—	2.4	—	A

### 1.3 Block Diagram

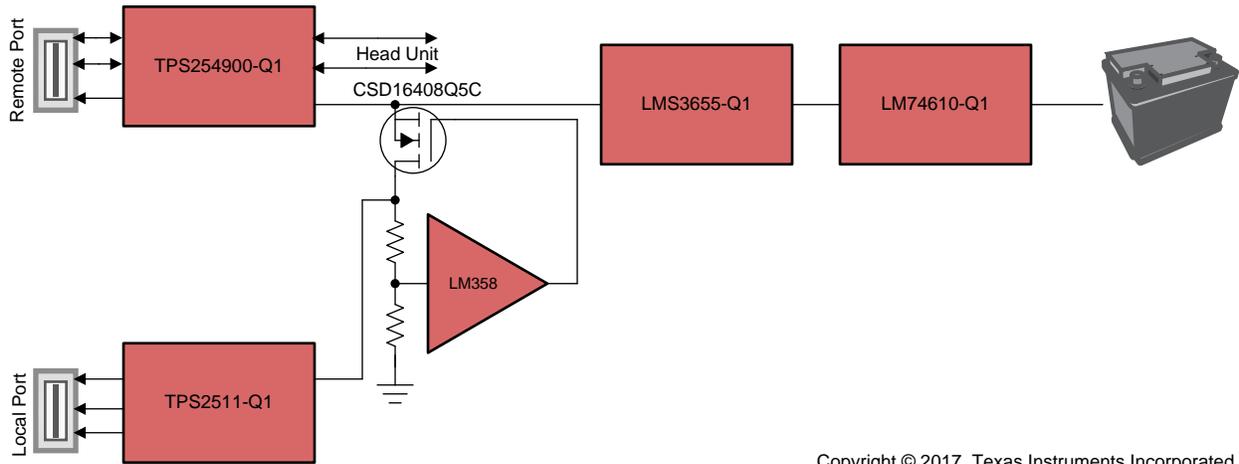


Copyright © 2017, Texas Instruments Incorporated

图 1. TIDA-01253 Block Diagram



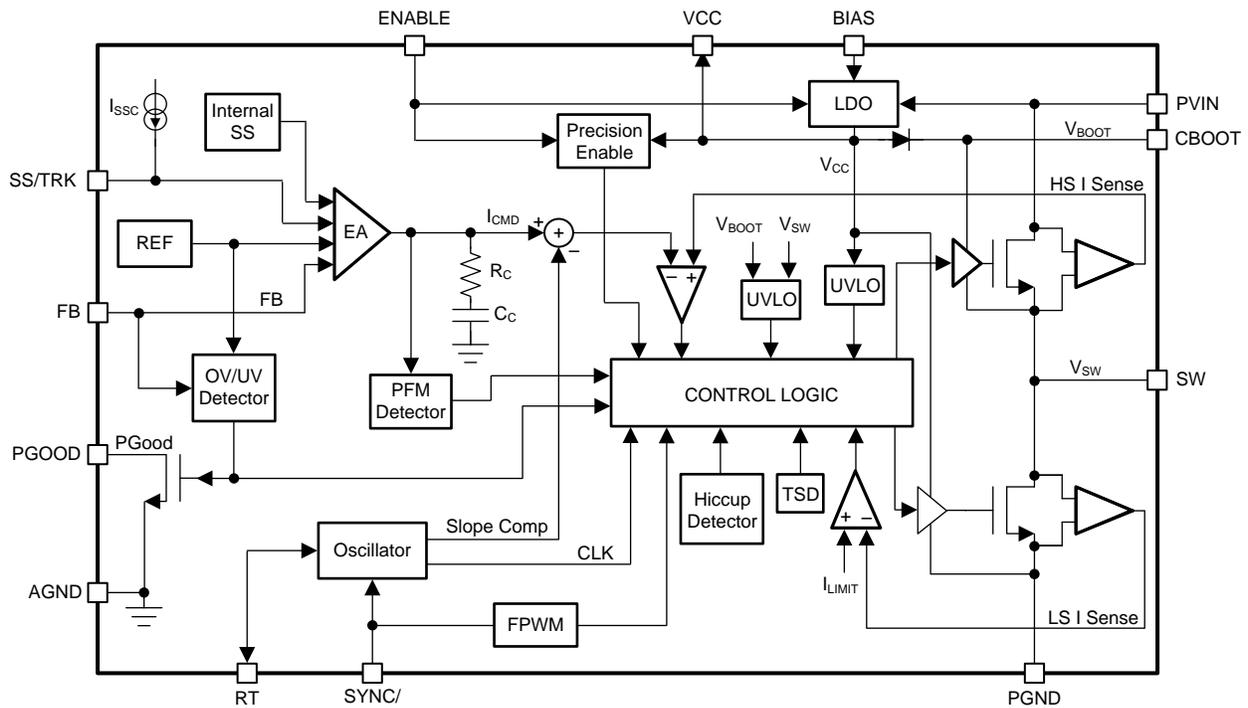
### 1.4.2 LMS3635-Q1 to 36-V, 5.5-A, 400-kHz Synchronous Step-Down Voltage Converter

The LMS3655 synchronous buck regulators are optimized for high-performance applications, providing an adjustable output of 1 V to 15 V. Seamless transition between PWM and PFM modes, along with a low quiescent current, ensures high efficiency and superior transient responses at all loads. Advanced high-speed circuitry allows the LMS3655 to regulate an input of 24 V to an output of 3.3 V at a fixed frequency of 400 kHz while also enabling a continuous load current of 5.5 A. An innovative frequency foldback architecture allows this device to regulate a 3.3-V output from an input voltage of only 3.5 V. The input voltage can range up to 36 V, with transient tolerance up to 42 V, easing input surge protection design. An open-drain reset output, with built-in filtering and delay, provides a true indication of system status. This feature negates the requirement for an additional supervisory component, saving cost and board space.



Copyright © 2017, Texas Instruments Incorporated

图 4. LMS3655-Q1 Functional Block Diagram

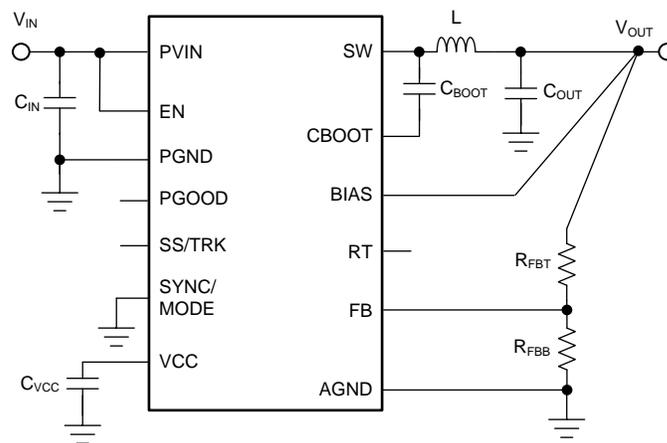

Copyright © 2017, Texas Instruments Incorporated

**图 5. LMS3655-Q1 Simplified Schematic**


### 1.4.3 TPS254900-Q1 Automotive Charging Port Controller and Power Switch With Short-to-Battery Protection

The TPS254900-Q1 (图 6 and 图 7) is a USB charging port controller and power switch with short to-battery protection. The TPS254900-Q1 provides protection on the OUT, DM\_IN, and DP\_IN pins. These three pins withstand voltages up to 18 V. Upon a short-to-battery incident, an internal MOSFET quickly disconnects the pin. This feature provides protection to the power supply of the TPS254900-Q1, the upstream processor, or the upstream HUB.

The TPS254900-Q1 50-m $\Omega$  power switch has two selectable, programmable current limits that support port power management by providing a lower current limit that can be used when adjacent ports experience heavy loads. This feature is important in a system with multiple ports and the upstream supply is unable to provide full current to all ports simultaneously.

The TPS254900Q1 has a current-sense output that is able to control an upstream supply. This output control allows it to maintain 5 V at the USB port even during heavy charging currents. This feature is important in systems with long USB cables where significant voltage drops can occur while fast-charging portable devices. The unique IMON feature allows the system to register the load current by monitoring the IMON voltage and is used for dynamic port-power management.

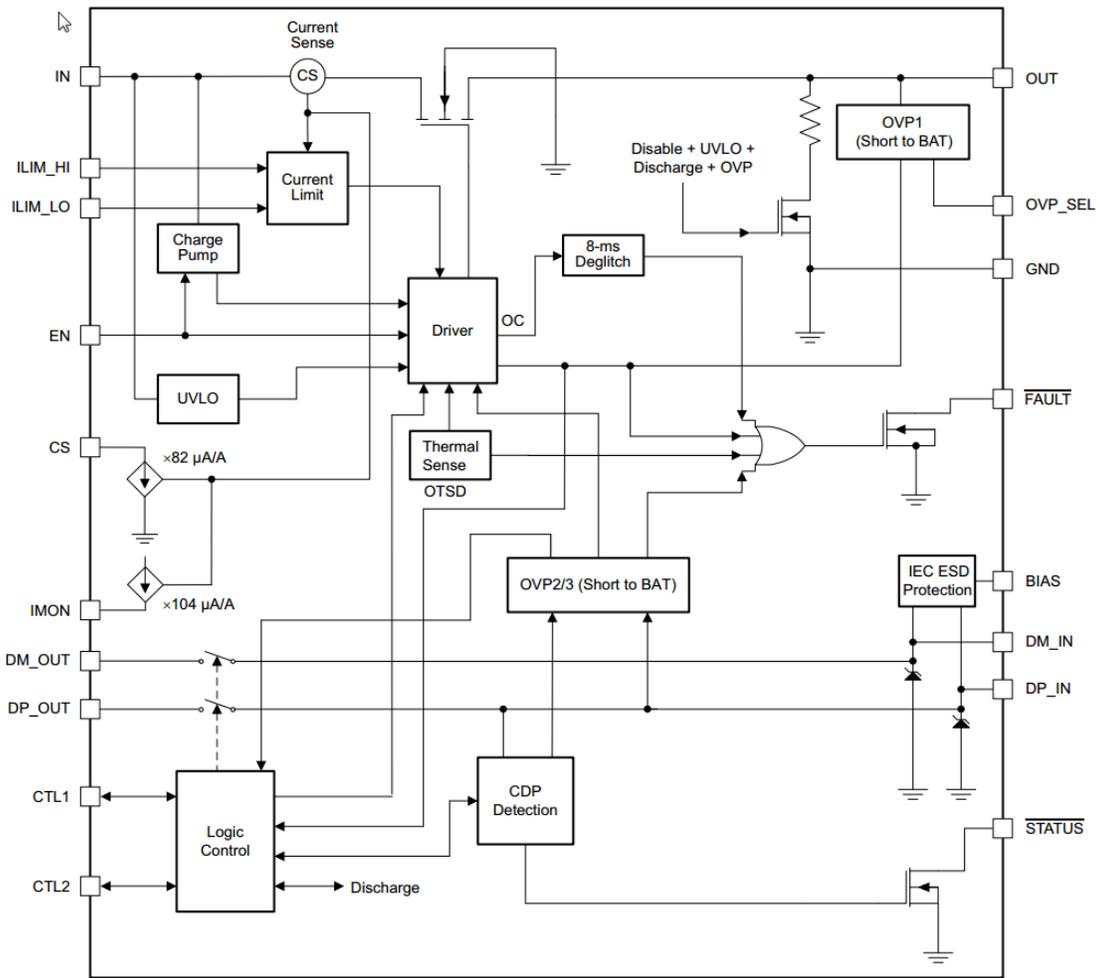To save space in the application, the TPS254900-Q1 also integrates IEC 61000-4-2 compliant protection from electrostatic discharge (ESD).



Copyright © 2016, Texas Instruments Incorporated

图 6. TPS254900-Q1 Functional Block Diagram



The TPS2511-Q1 supports three of the most common protocols:

- USB battery charging specification, revision 1.2 (BC1.2)
- Chinese Telecommunications Industry Standard YD/T 1591-2009
- Divider mode

These protocols utilize three types of charging ports which are defined to provide different charging current to client-side devices. These charging ports are defined as:

- Standard downstream port (SDP)
- Charging downstream port (CDP)
- Dedicated charging port (DCP)

The BC1.2 specification defines a charging port as a downstream-facing USB port that provides power for charging portable equipment.


The following 表 2 shows different port operating modes according to the BC1.2 specification.

**表 2. Operating Modes Table**

PORT TYPE	SUPPORTS USB 2.0 COMMUNICATION	MAXIMUM ALLOWABLE CURRENT DRAWN BY PORTABLE EQUIPMENT
SDP (USB 2.0)	Yes	0.5 A
SDP (USB 3.0)	Yes	0.9 A
CDP	Yes	1.5 A
DCP	No	1.5 A

The BC1.2 specification defines the protocol necessary to allow portable equipment to determine what type of port it is connected to so that it can allot its maximum allowable current drawn. The handshaking process consists of two steps. During step one, the primary detection, the portable equipment outputs a nominal 0.6-V output on its D+ line and reads the voltage input on its D– line. The portable device concludes that it is connected to the charging port if the D– voltage is greater than the nominal data-detect voltage of 0.3 V and less than 0.80 V.

The second step, the secondary detection, is necessary for portable equipment to determine between a CDP and DCP. The portable device outputs a nominal 0.6-V output on its D– line and reads the voltage input on its D+ line. The portable device concludes it is connected to a CDP if the data line being read remains less than the nominal data detect voltage of 0.3 V. The portable device concludes it is connected to a DCP if the data line being read is greater than the nominal data-detect voltage of 0.3 V and less than 0.8 V.

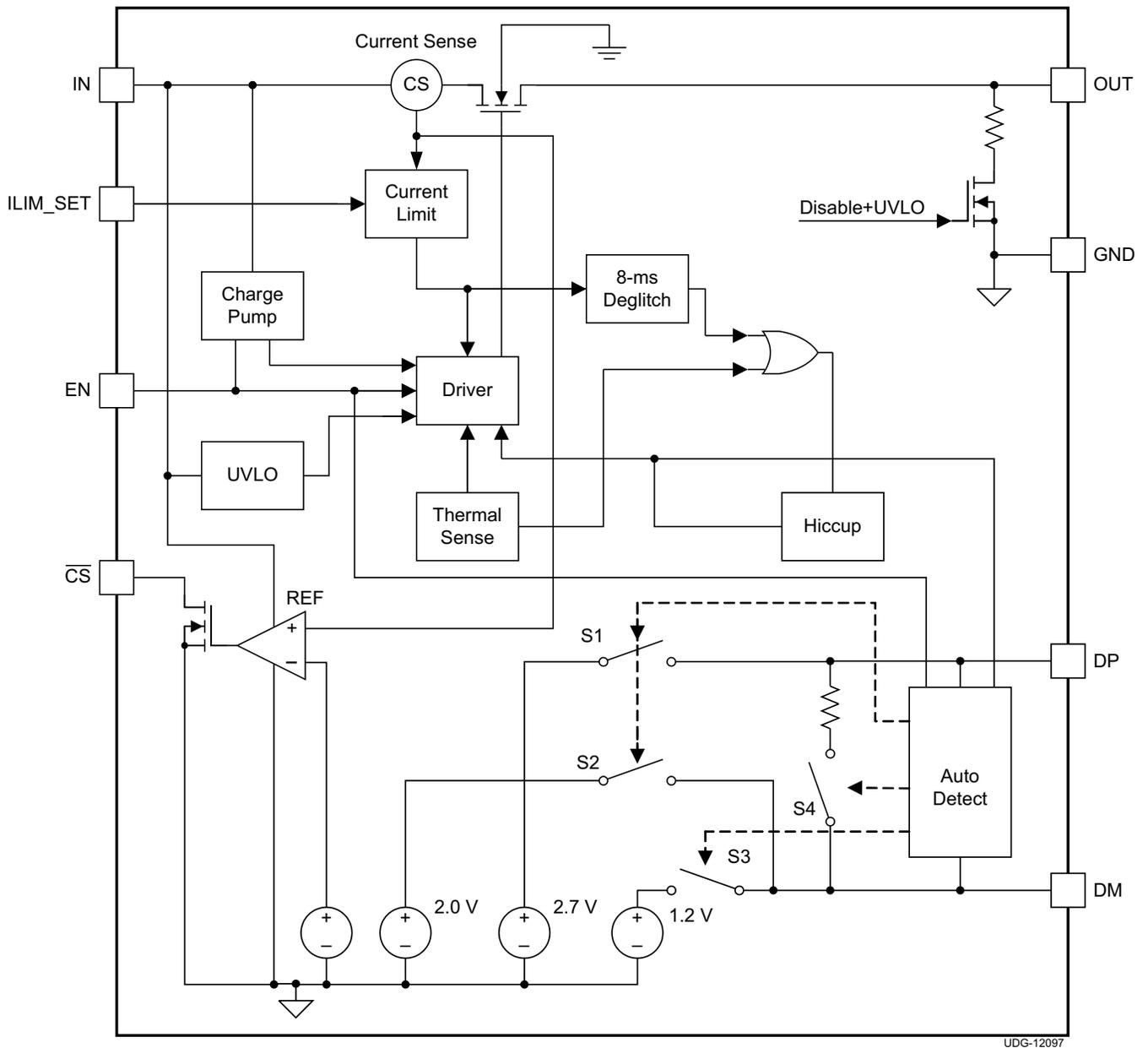

Copyright © 2017, Texas Instruments Incorporated

图 8. TPS2511-Q1 Functional Block Diagram

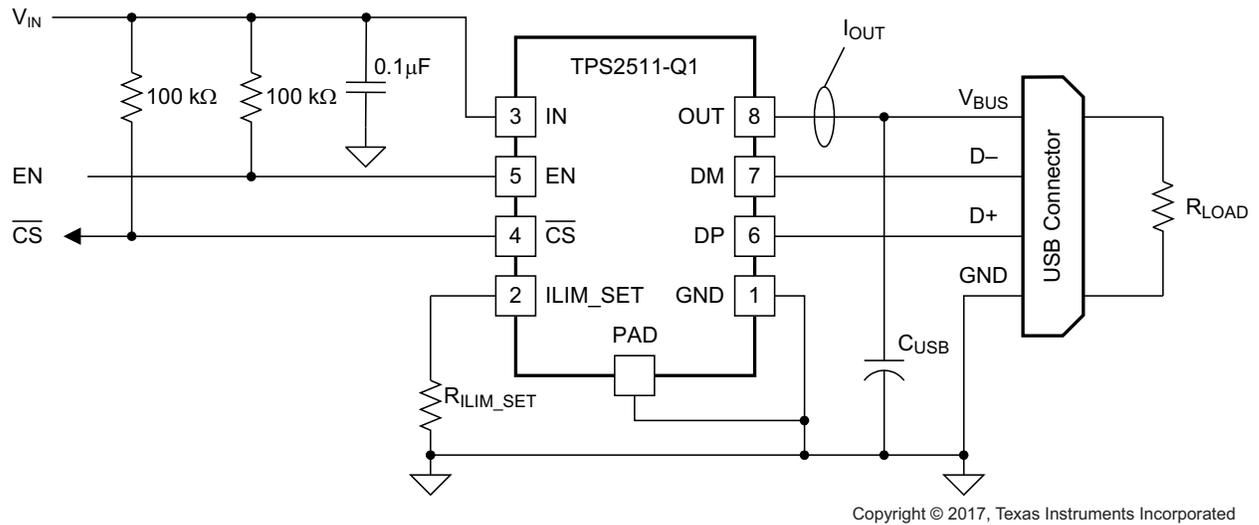



图 9. TPS2511-Q1 Simplified Schematic

#### 1.4.5 LM358 Dual Operational Amplifiers

These devices consist of two independent, high-gain frequency-compensated operational amplifiers (op amps) designed to operate from a single supply over a wide range of voltages. Operation from split supplies is also possible if the difference between the two supplies is 3 V to 32 V (3 V to 26 V for the LM2904 device) and VCC is at least 1.5 V more positive than the input common-mode voltage. The low supply-current drain is independent of the magnitude of the supply voltage.


Applications include transducer amplifiers, DC amplification blocks, and all the conventional op-amp circuits that can now be implemented more easily in single-supply voltage systems. For example, these devices can be operated directly from the standard 5-V supply used in digital systems and can easily provide the required interface electronics without additional  $\pm 5\text{-V}$  supplies.

图 10 shows the functional block diagram of the LM358 and 图 11 shows the simplified schematic.

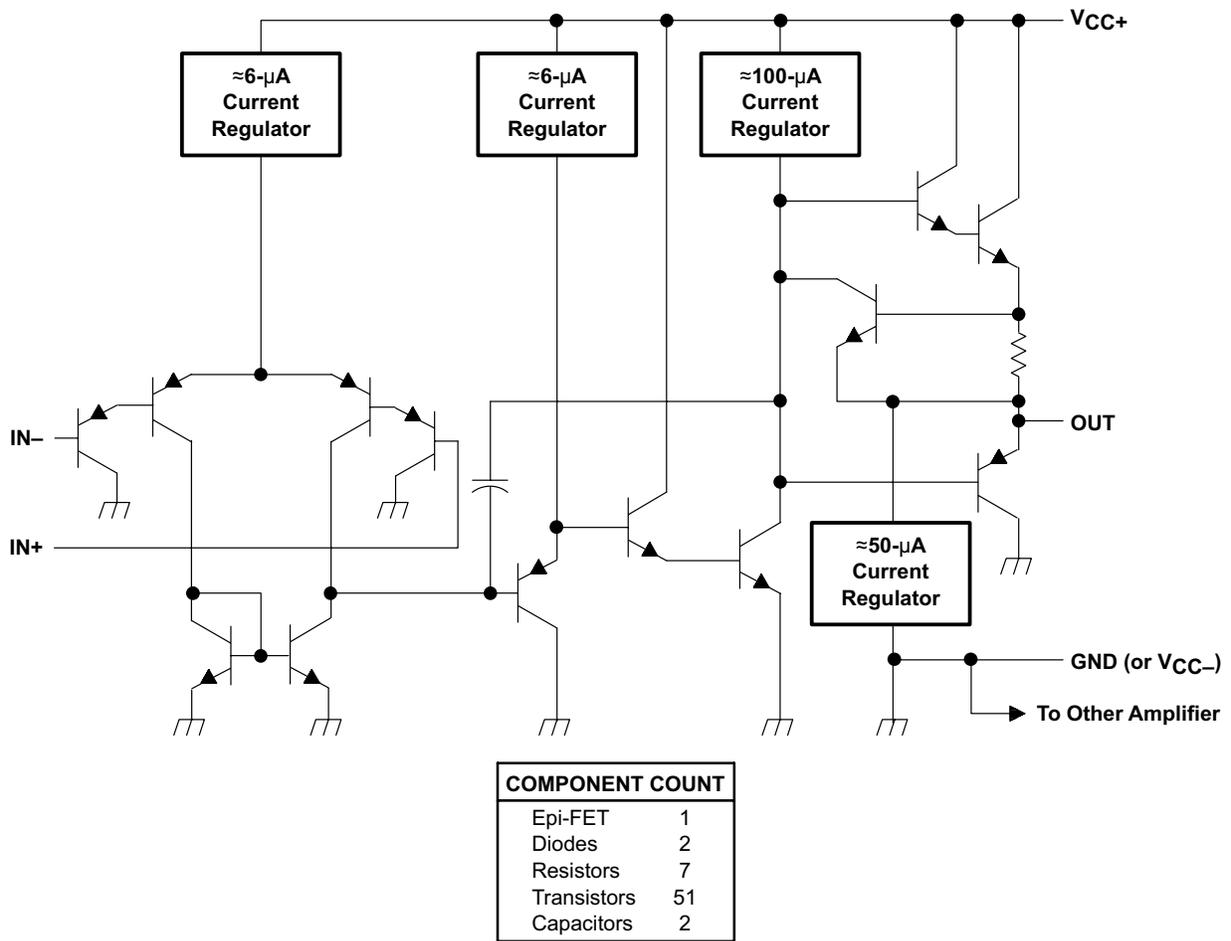

Copyright © 2017, Texas Instruments Incorporated

图 10. LM358 Functional Block Diagram

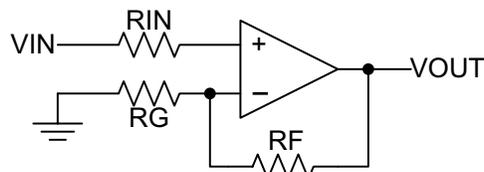

Copyright © 2017, Texas Instruments Incorporated

图 11. LM358 Simplified Schematic

### 1.4.6 CSD16408Q5C DualCool™ N-Channel NexFET™ Power MOSFET

The NexFET™ power MOSFET has been designed to minimize losses in power conversion applications with ultra-low  $Q_g$  and  $Q_{gd}$ . While utilizing the DualCool™ packaging, the devices are optimized for two-sided cooling and have low thermal resistance, all while being avalanche rated (see 图 12).


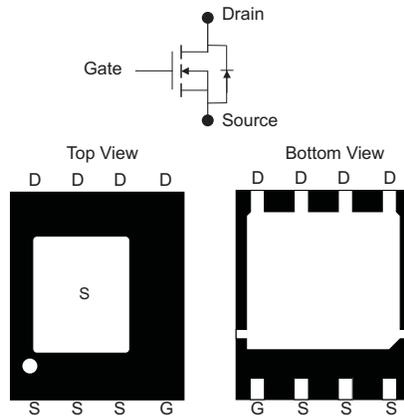


图 12. CSD16408Q5C Package and Symbol

## 2 System Design Theory
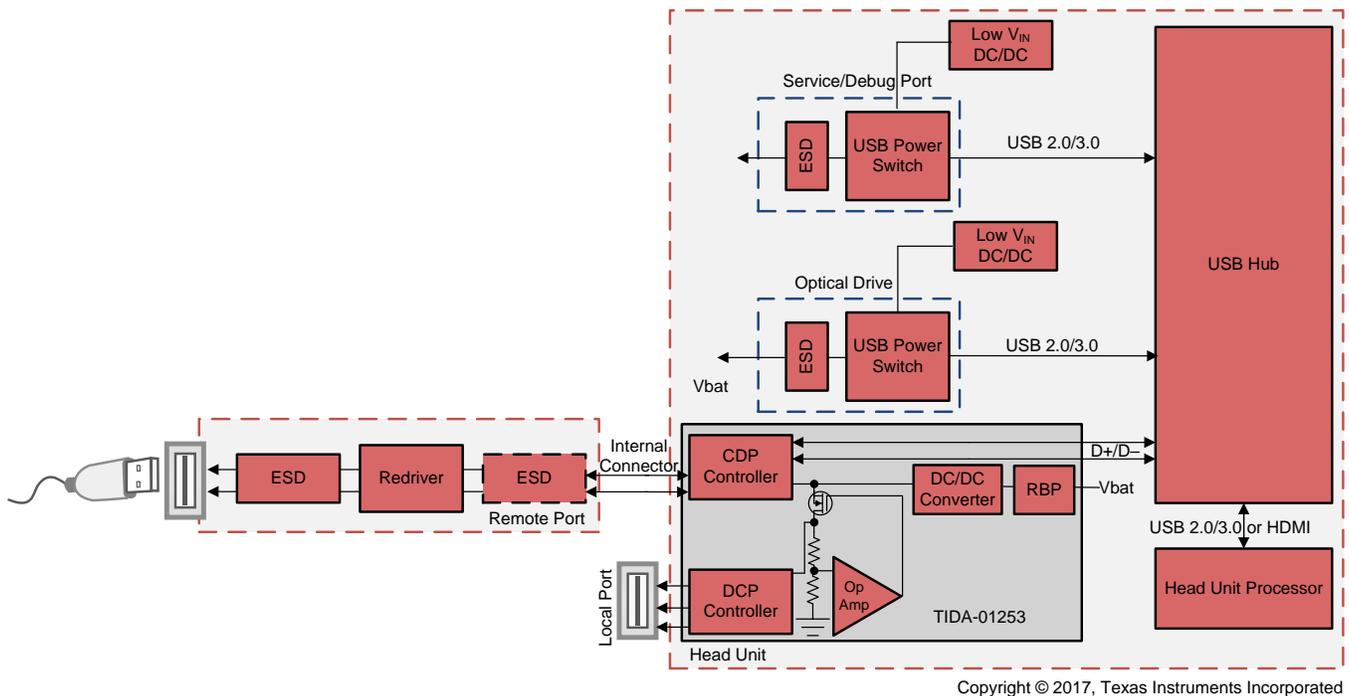
### 2.1 Introduction

The TIDA-01253 reference design has been designed to support two USB type-A ports: one port operating in CDP mode and the other operating in DCP mode as specified by USB BC1.2 specification (see 图 13). The purpose of this design is to show dual-port functionality while using one power supply. The challenge, however, is when supporting a remote port, cable compensation is required due to the voltage drop across wires. This challenge requires additional voltage to compensate for the loss; however, the difficulty is providing an extra voltage for the remote port while also maintaining adequate voltage for the local port. The following subsections address this issue. As 图 1 shows, the TIDA-01253 is a media interface subsystem that could be integrated in a head unit while supporting a remote port. This TI Design has been specifically designed to meet automotive standards and uses parts that are already released or, at the time of this writing, planned to be released as automotive Q-100 grade-qualified. When designing a subsystem for automotive infotainment, satisfying relevant protection standards as required by automotive original-equipment manufacturers (OEMs) is important. In this TI Design, parts have been selected to support typical protection requirements such as reverse battery protection, current limiting, short-to-battery protection, as well as ESD protection. Additionally, power supplies typically require a spread spectrum to mitigate EMI and switching frequency outside of AM band operation while supporting wide input off-battery operation. In the circuit board layout (see 图 1), care has been taken to improve thermal dissipation and EMI to ultimately pass CISPR-25 class-5 standards. The following sections explain each system subsection.




Copyright © 2017, Texas Instruments Incorporated

图 13. System Integration Concept

## 2.2 Power Supply
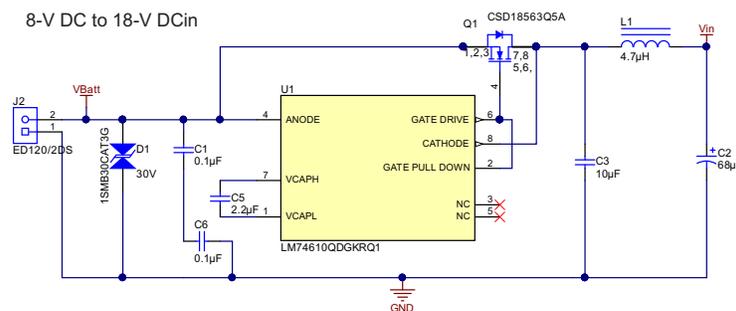
### 2.2.1 Reverse Battery Protection

The reverse battery protection that 图 14 shows is a requirement for every electronic subsystem in a vehicle recognized by OEM standards as well as load dump protection standards ISO 16750-2. The LM74610 device is used to control the NFET to protect the load in a negative polarity condition. This device is used to emulate an ideal diode by using an NFET in series with the battery supply. This configuration has the advantage of a highly effective and efficient substitute for reverse battery protection to the traditional rectifier. The LM74610 has no power pin and no ground reference which means that it requires zero  $I_Q$  and reduces standby current drawn from the battery. Additionally, the voltage drop across the field-effect transistor (FET) is so inconsequential that it allows the wide  $V_{IN}$  buck regulator to operate at even lower battery input voltages. This feature is an advantage for scenarios such as cold crank when the battery voltage temporarily drops to as low as 3.5 V. A traditional diode solution usually has a 700-mV voltage drop, so the buck converter is incapable of maintaining the 5- $V_{OUT}$  system voltage. With the smart diode solution, the buck still receives close to 5 V during this condition and can continue to operate.



Copyright © 2016, Texas Instruments Incorporated

图 14. Schematic of Reverse Battery Protection

#### 2.2.1.1 MOSFET

The LM74610-Q1 product folder has tools to help simulate using the WEBENCH® Design simulator tool. The data sheet also outlines MOSFET selection in the LM74610-Q1 data sheet [1]. Some important characteristics that the data sheet recommends to design around are:

- Continuous drain current ( $I_D$ )
- Maximum drain-to-source voltage ( $V_{DS(MAX)}$ )
- Gate-to-source threshold voltage ( $V_{GS(TH)}$ )
- Drain-to-source ON-resistance ( $R_{DS(ON)}$ )

The rating for  $I_D$  must exceed the load current, which is 6 A ( $I_D > I_{LOAD}$ ) in this system, and the body diode maximum current  $I_S \geq I_D$ . Also, the gate-to-source threshold voltage must be  $V_{GS(TH)} \leq 3$  V. The NFET outlined in the following 表 3 has been selected for this application.

表 3. MOSFET Parameters

AUTOMOTIVE N-CHANNEL 40-V (D-S) 175°C MOSFET (SQJ422EP)					
PARAMETER	COMMENTS	MIN	TYP	MAX	UNIT
$I_D$	Drain-to-source current	—	—	75	A
$V_{DS}$	Drain-to-source voltage	—	—	40	V
$V_{GS(TH)}$	Gate-to-Source voltage	1.5	2.5	2.5	V

**表 3. MOSFET Parameters (continued)**

AUTOMOTIVE N-CHANNEL 40-V (D-S) 175°C MOSFET (SQJ422EP)					
PARAMETER	COMMENTS	MIN	TYP	MAX	UNIT
$R_{DS(ON)}$	Drain-to-source ON resistance	—	4.3	—	m $\Omega$

### 2.2.1.2 Input Capacitors

Due to the possibility of this subsystem PCB flexing, the likelihood of mechanical short increases. If a mechanical short does occur, then a short transpires between the two terminals of the battery. To mitigate any chance of this short, the two input capacitors are placed in series but rotated 90° to one another in case the vibration in an automotive system causes one capacitor to crack. Some component manufacturers offer options for an integrated solution using automotive-grade multilayer ceramic capacitors (MLCC); but for this solution, discrete components have been used.

### 2.2.1.3 TVS Diodes

Although the transient voltage suppression (TVS) diodes used in this TI Design are not required by the LM74610-Q1 (as outlined in the LM74610-Q1 data sheet [1]), they are used to clamp the positive and negative voltage surges that may occur in the input. These transients are outlined in the ISO specification ISO 7637-2:2004 pulses 1 and 2a. An LC filter is also used downstream. This TI Design focuses on maintaining a fully functional system while transients may be present because this system must remain in operation during such transient conditions. Two specifications that must be considered are breakdown voltage and clamping voltage:

- Breakdown voltage is the voltage when the TVS diode goes into an avalanche similar to a Zener diode and is specified at a low-current value (typically 1 mA).
- Clamping voltage is the voltage which the TVS diode clamps to in high-current pulse situations.

表 4 shows these parameters for the selected diodes.

**表 4. TVS Diode Parameters**

600-W PEAK-POWER ZENER TRANSIENT VOLTAGE SUPPRESSOR BIDIRECTIONAL (1SMB30CAT3G)					
PARAMETER	COMMENTS	MIN	TYP	MAX	UNIT
$V_{RWM}$	Reverse standoff voltage	—	30	—	V
$V_C$	Clamping voltage	—	48.8	—	V
$V_{BR}$	Breakdown voltage	33.3	35.06	36.8	V


Choose the diode breakdown voltage such that the transients are clamped at the voltages that protect the MOSFET and the rest of the system. D1 clamps above the double battery (jump-start) and clamped load-dump voltages, but lower than the maximum operating voltage of the downstream devices. In this case, the diode starts to clamp around 30 V but has a maximum clamp voltage just below 48 V. The ideal voltage is somewhere around 35 V, which is why D1 has been chosen for its maximum clamping voltage. In regard to power levels for TVS diodes, the particular package used is SMBJ, which supports 600-W peak-power levels. This package is sufficient for ISO 7637-2 pulses and suppressed load-dump case (ISO-16750-2 pulse B). For unsuppressed load dumps (ISO-16750-2 pulse A), higher power TVS diodes such as SMCJ or SMDJ may be required. Refer to the LM74610-Q1 data sheet [1] for more information about designing the TVS diodes for this application

### 2.2.2 DC-DC Converter

For this design, the LMS3655 has been chosen for its optimization for automotive applications. In this particular application, this device was used for its 5-A current capability. However, the LMS3655 also meets many of the requirements for automotive applications such as:

- Wide  $V_{IN}$  operation with transient tolerance up to 42 V
- Wettable flanks
- Switching frequency outside AM band
- Low EMI and switch noise
- External frequency synchronization
- AEC-Q100 automotive qualified

图 15 shows the DC-DC schematic of the LMS3655.

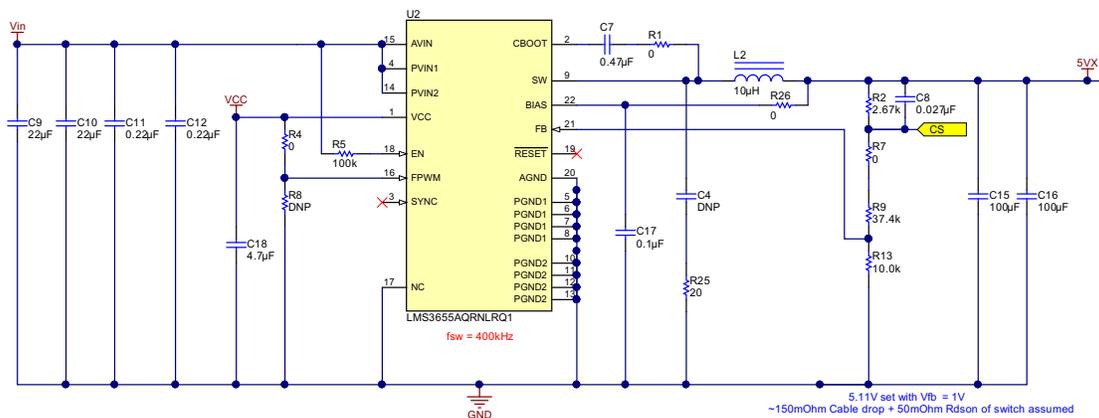

Copyright © 2016, Texas Instruments Incorporated

图 15. DC-DC Schematic

表 5. Spreadsheet Parameters of Power Supply Design

PARAMETER	COMMENTS	MIN	TYP	MAX	UNIT
<b>System Operation</b>					
$V_{IN}$	Input voltage	5.5	14.5	36	V
$F_{SW}$	Switching frequency	—	400	—	kHz
<b>Output Voltages</b>					
$V_{Remote}$	Remote port voltage	5.081	5.087	5.092	V
$V_{Local}$	Local port voltage	4.875	5.00	5.125	V
$V_{BUS}$	Output of LM73605 with cable compensation adjustment	5.0	5.1	5.6	V
<b>Output Current</b>					
$I_{OUT-Remote}$	VBUS load current of remote port	—	2.4	—	A
$I_{OUT-Local}$	VBUS load current of local port	—	2.4	—	A
<b>Component Values</b>					
$L_1$	Inductor	—	10	—	$\mu$ H
$C_{IN}$	Input capacitance	—	44.4	—	$\mu$ F
$C_{OUT}$	Output capacitance	—	200	—	$\mu$ F

### 2.2.2.1 Input Capacitors

Ceramic capacitors are typically used at the input of a power supply because they provide a low-impedance source to the regulator in addition to supplying ripple current and isolating switching noise from other circuits. Because the input of the regulator can encounter voltages up to 40 V, the rating of the capacitors must be able to accommodate these voltages (see 表 6). In addition, small high-frequency bypass capacitors connected directly between the VIN and GND pins are used to reduce noise spikes and aid in reducing conducted EMI. Additional high-frequency capacitors can be used to help manage conducted EMI or voltage spike issues that may be encountered. The following calculations help determine the right input capacitance to use.

表 6. Input Capacitor Selection

NOMINAL CAPACITANCE	VOLTAGE RATING	TYPE	PART NUMBER
2x22 $\mu$ F	25 V	X7R	C4532X7R1E226M250KC
0.22 $\mu$ F	50 V	X5R	GRM155R61H104ME14D

注: Following the recommendations from the DC-DC regulator is important; however, following the correlation of the input filter is also important to pass CISPR-25 EMI testing. The following calculations describe how the LC filter was calculated with respect to the system.

As 图 16 shows, the following parameters must be identified to calculate the ideal component selection.

- Board I/Os: Input voltage ( $V_{IN}$ ), output voltage ( $V_{OUT}$ ), and output current ( $I_{OUT}$ )
- Estimated efficiency
- Switching frequency ( $F_{SW}$ )
- Filter inductor ( $L_f$ )
- Input capacitance ( $C_{IN}$ ) and damping capacitor ( $C_d$ ) equivalent series resistance (ESR)
- Maximum noise ( $V_{MAX}$ )

With these parameters defined, the following calculations are conducted in 公式 1:

$$\text{Target attenuation} = 20 \times \text{LOG}(I_{OUT} / \pi^2 \times F_{SW} \times 1000 \times C_{IN} \times 1e - 6) \times \text{SIN}(\pi \times D) / 1e - 6 - V_{MAX} \quad (1)$$

where,

- Duty cycle  $D = V_{OUT} / V_{IN}$ .

After calculating the target attenuation, the filter capacitor ( $C_f$ ) can be calculated. Two options are available for calculating the  $C_f$  and the greater of the two options in 公式 2 and 公式 3 provides the value to select.


$$C_{fA} = C_{IN} \times 1e - 6 / (C_{IN} \times 1e - 6 \times L_f \times 1e - 6 \times (2 \times \pi \times F_{SW} \times 1000 / 10)^2 - 1) / 1e - 6 \quad (2)$$

$$C_{fB} = 1 / (L_f \times 1e - 6) \times (10^{(TA / 40)} / (2 \times \pi \times F_{SW} \times 1000))^2 / 1e - 6 \quad (3)$$

The two equations calculate to  $C_{fA} = 3.8 \mu\text{F}$  and  $C_{fB} = 27.7 \mu\text{F}$ , respectively. The 4.7- $\mu\text{F}$  value has been chosen for this design.

For  $C_d$ , the damping capacitor is recommended to be  $C_d \geq 4 \times C_{IN}$ , where  $C_{IN}$  is the input capacitance to the DC-DC and thus determined by the input ripple required for the switcher. This equation produces a rather large  $C_d$  of 108  $\mu\text{F}$  for this particular design. A standard high-frequency capacitor was chosen but note that adjusting these values based on the table in the following 图 16 can help change the impedance at the switching frequency and thus troubleshoot any EMI issues that may arise.

Enter input voltage:	$V_{IN} =$	14.5	V
Enter output voltage:	$V_{OUT} =$	5	V
Enter output current:	$I_{OUT} =$	5	A
Enter estimated efficiency:	EFF =	93%	
Enter switching frequency:	$F_{SW} =$	400	kHz
Enter the max noise level:	$V_{MAX} =$	40	dB $\mu$ V ( 45 dB $\mu$ V for CISPR 22)

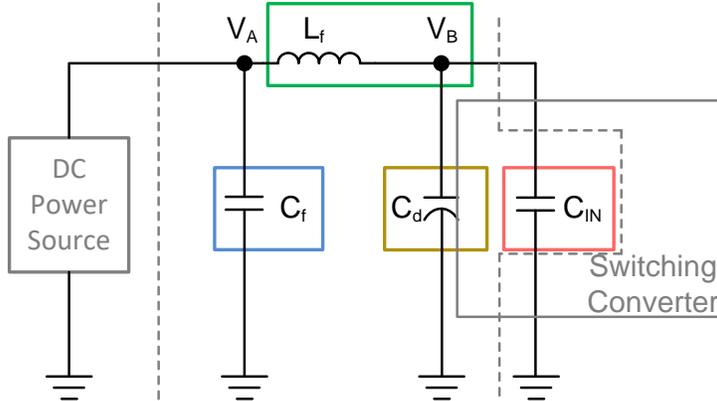

ENTER $L_f$ VALUE:	
$L_f =$	4.7 $\mu$ H
Suggested range between 1 $\mu$ H and 10 $\mu$ H	

ENTER $C_{IN}$ VALUE:	
$C_{IN} =$	40 $\mu$ F
$C_{IN}$ ESR =	0.005 $\Omega$

SUGGESTED MIN $C_f$ VALUE:
$C_f \geq$ 10 $\mu$ F
Note that $C_f$ must be a low ESR capacitor. If ceramic is used, take into account the capacitance drop at the $V_A$ bias voltage and add more caps in parallel if required.
ENTER ACTUAL VALUE:
$C_f =$ 10 $\mu$ F

SUGGESTED MIN $C_d$	
CAPACITANCE: $C_d \geq$	160 $\mu$ F
ENTER ACTUAL VALUES:	
$C_d =$	68 $\mu$ F
$C_d$ ESR =	0.4 $\Omega$

图 16. LC Filter Calculation

### 2.2.2.2 DC-DC Inductor Selection

There are two necessary criteria for selecting an output inductor:

- Inductance
- Saturation current rating

Inductance is usually calculated based on the desired peak-to-peak ripple current,  $\Delta IL$ , that flows in the inductor along with the load current. Two tradeoffs exist for this selection:

- Higher inductance means lower ripple current and lower ripple voltage at the output; however, this usually leads to a higher inductor cost.
- Lower inductance means a smaller package size and thus a more cost-effective device.

An estimate for peak-to-peak ripple current through the inductor should start between 0.2 to 0.4 of the maximum output current. From this range, the minimum inductance can be calculated in [公式 4](#) from this value:

$$L_{\min} = (V_{IN(\text{Max})} - V_{OUT}) / (f_{\text{sw}} \times \Delta IL) \times D \quad (4)$$

where,

- $V_{IN(\text{MAX})} = 14.5$ ,
- $V_{OUT} = 5.11$ ,
- $D = 0.352$ ,
- $F_{\text{SW}} = 400 \text{ kHz}$ ,
- $\Delta IL = 0.4$

For this design,  $L_{\text{MIN}} = 4.128 \mu\text{H}$  and a standard  $10 \mu\text{H}$  has been chosen for cost optimization.

The second criterion is inductor saturation current rating. The LMS3655 has an accurately-programmed valley current limit. During an instantaneous short, the peak inductor current can be very high due to a momentary increase in duty cycle. Because this current is limited by the high-side switch current limit, TI advises to select an inductor with a saturation current close to the high-side current limit, which is approximately 8 A; therefore, a saturation current can be chosen to match this value.

### 2.2.2.3 Output Voltage and Capacitor Selection

The output capacitor is responsible for filtering the output voltage and supplying load current during transients. Capacitor selection depends on application conditions as well as ripple and transient requirements. Best performance is achieved by using ceramic capacitors or combinations of ceramic and polymer capacitors. For high-output voltage conditions, such as 12 V and above, finding ceramic caps that are rated for an appropriate voltage can be challenging. In such cases, a low ESR SP™ or POSCAP™ type capacitor should be chosen. For those high  $V_{\text{OUT}}$  conditions, a low-value ceramic capacitor can be introduced in parallel so as to reduce the output ripple and noise spikes, while a higher-value electrolytic or polymer cap provides large bulk capacitance to supply transients. For a given input and output requirement, the following inequality in [公式 5](#) provides an approximation for a required absolute minimum output cap:

$$C_{\text{out}} > 1 / (f_{\text{sw}} \times \Delta V_o / I_{\text{out}} \times r) \times ((r^2 / 12 \times (1+D')) + (D \times (1+r))) \quad (5)$$

where,

- $R =$  Ripple ratio of the inductor ripple current ( $\Delta IL / I_{\text{out}}$ ),
- $\Delta V_o =$  Target output voltage undershoot,
- $D = 1 -$  duty cycle,

- $F_{SW}$  = Switching frequency,
- $I_{OUT}$  = Load current.

Using low ESR output capacitors in low-voltage applications is critical because this limits potential output voltage overshoots when the input voltage falls below the device normal operating range. To optimize the transient behavior, a feed-forward capacitor can be added in parallel with the upper feedback resistor. For this design,  $2 \times 100\text{-}\mu\text{F}, 10\text{-V}, \text{X5R}$  ceramic capacitors are used in parallel.


For further recommendations regarding component selection, refer to the LMS3655 data sheet [2].

### 2.3 Remote Port Regulation

The TPS254900-Q1 has been chosen for its optimization with automotive applications. The TPS254900 meets many of the requirements for automotive applications such as:

- Support for VBUS, D+, D– short-to-battery protection
- Cable compensation

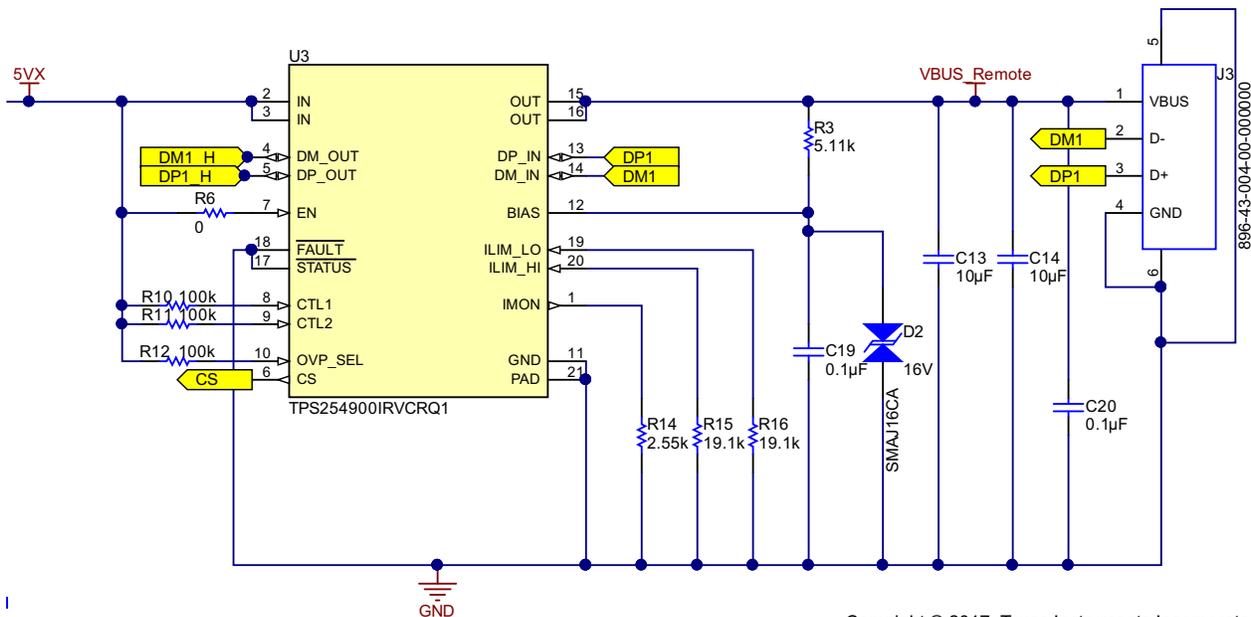The operation of the charging port circuit depends on the TPS254900 presented in 图 17 for providing the electrical signatures on D+ and D– to support BC1.2 CDP-compliant charging.



Copyright © 2017, Texas Instruments Incorporated

图 17. TPS254900-Q1 Remote CDP Port Controller

The internal switch of the TPS254900 is connected between the 5-V power source and VBUS. A CDP port is a USB port that follows USB BC1.2 requirements and supplies a minimum of 1.5 A per port. The port provides power and meets USB2.0 requirements for device enumeration. USB2.0 communication is supported and the host controller must be active to allow charging. What separates a CDP from an SDP is the host-charge handshaking logic that identifies this port as a CDP. A CDP is identifiable by a compliant BC1.2 client device and allows for additional current draw by the client device. As observable in the previous 图 17, CTL1 and CTL2 are connected through R6 and R7 for the configuration of SDP, SDP1, or CDP mode. See 表 7 for the configurations.

表 7. CTL1 and CTL2 Configurations

CTL1	CTL2	MODE	FAULT REPORT	NOTES
0	0	Client	OFF	Power Switch is disabled, only analog switch is on
0	1	SDP	ON	Standard SDP
1	0	SDP1	ON	No OUT discharge between CDP and SDP1 for port power management (PPM)
1	1	CDP	ON	No OUT discharge when changing between 10 and 11

The TPS254900-Q1 has been chosen in particular for its USB2.0 data support, integrated short-to-battery protection, and because of its cable compensation feature through the CS pin. This particular feature can be used as shown in [图 15](#).

When a load draws current through a long or thin wire, an IR drop occurs which reduces the voltage delivered to the load. In the vehicle from the voltage regulator 5-V output to the VPD\_IN (input voltage of portable device), the total resistance of power switch  $R_{DS(ON)}$  and cable resistance causes an IR drop at the PD input. So the charging current of most portable devices is less than their expected maximum charging current. The TPS254900-Q1 device detects the load currents and sets a proportional sink current that can be used to adjust output voltage of the up-stream regulator to compensate the IR drop in the charging path. The gain GCS of sink current proportional to load current is 75  $\mu\text{A/A}$ .

To design the feedback network on the regulator, the following calculations can be used:

- Choose RG according to the voltage regulator guidelines
- Calculate RFA as specified in [公式 6](#):

$$RFA = (R_{DS(ON)} + RWIRE) / GCS \quad (6)$$

Where:

- RWIRE is typically 80 m $\Omega$ /m to 120 m $\Omega$ /m and up to 3-m long
- GCS = 75  $\mu\text{A/A}$


Calculate RFB as specified in [公式 7](#):

$$RFB = VOUT / (VFB / RG) - RG - RFA \quad (7)$$

For this design, the voltage was set to 5.11 V with  $V_{FB} = 1$  V assuming a 150-m $\Omega$  cable drop and 50-m $\Omega$   $R_{DS(ON)}$  of the TPS254900 switch.

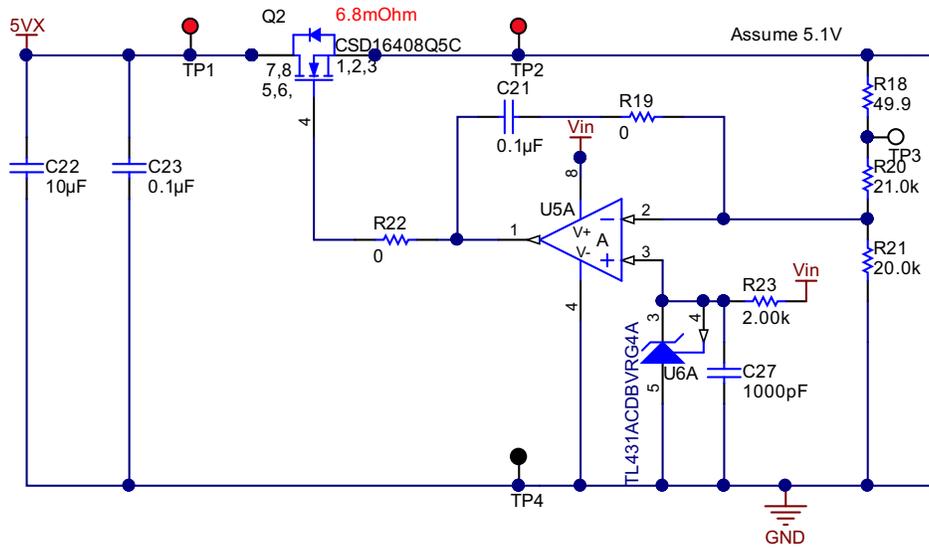
## 2.4 Local Port Controller

A unique challenge when designing for both a local port and remote port is the issue that the DC-DC regulator must be set at a higher voltage (5.11 V in this case) so that the cable compensation can compensate for the voltage droop across a long wire. The issue arises when the local port must be within a tight set of requirements, usually  $\pm 2.5\%$ . This set of restrictions becomes tricky to design without using two different regulators; so, to design for this, a very small regulation differential between input and output must be maintained. Usually this type of design restriction can be solved with a low dropout regulator (LDO); however, because this is an automotive USB port, two more challenges arise: The dropout must not only be 50 mV to 100 mV, but the LDO must also be automotive-qualified and the LDO must support up to 2.4 A. For this design, a custom LDO (see [图 18](#)) has been created using a low  $R_{DS(ON)}$  MOSFET and op amp. This discrete LDO regulates the voltage for the local port controller, which is shown in [图 19](#).



Copyright © 2017, Texas Instruments Incorporated

图 18. Custom LDO With Low Dropout

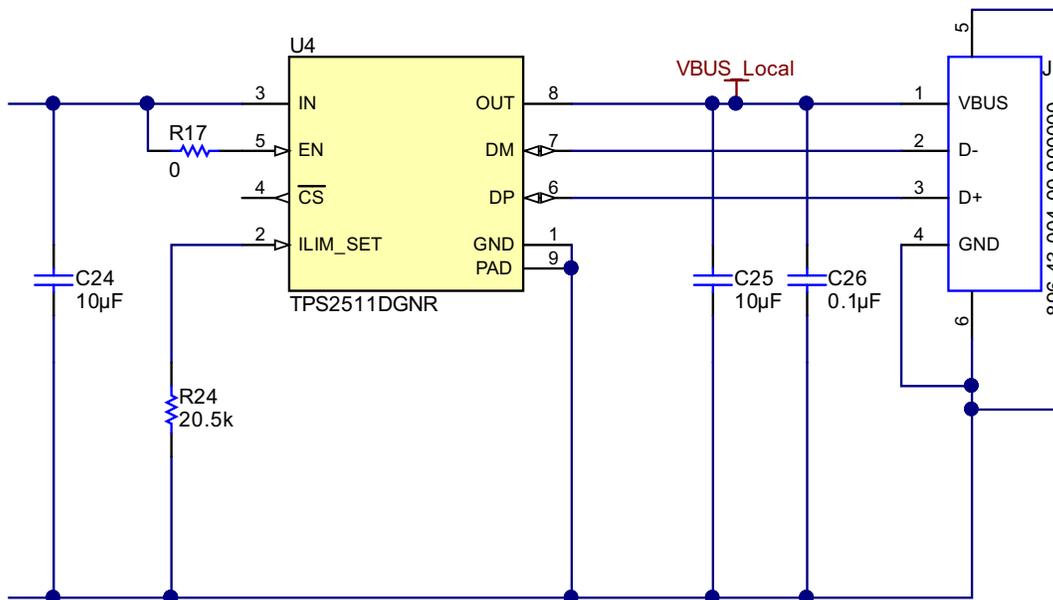

Copyright © 2017, Texas Instruments Incorporated

图 19. TPS2511 Local Port DCP Controller

The following 表 8 shows the voltages at the extremes of a no-load and full-load on either or both of the ports.

表 8. Load Current Truth Table

REMOTE LOAD	LOCAL LOAD	VBUS	V_REMOTE	V_LOCAL
0	0	5.11 V	4.98 V	5.05 V
0	1	5.11 V	4.98 V	$5.11 - (76.8 \text{ m}\Omega \times 2.4 \text{ A}) = 4.92 \text{ V}$
1	0	5.4 V	$\approx 5.28 \text{ V}$	5.4 V
1	1	5.4 V	$\approx 5.28 \text{ V}$	$5.4 \text{ V} - (76.8 \text{ m}\Omega \times 2.4 \text{ A}) = 5.22 \text{ V}$

### 3 Getting Started Hardware

This board is designed to passthrough data on the remote port in CDP mode and support dedicated charging (DCP) on the local port. Although there is not a USB output port to connect a USB host, D+ and D- can be pulled high or low to enable this detection.

To get started, simply supply 12 V to the J4 pin and plug in a USB type-A connector to either or both USB ports (see 图 20).

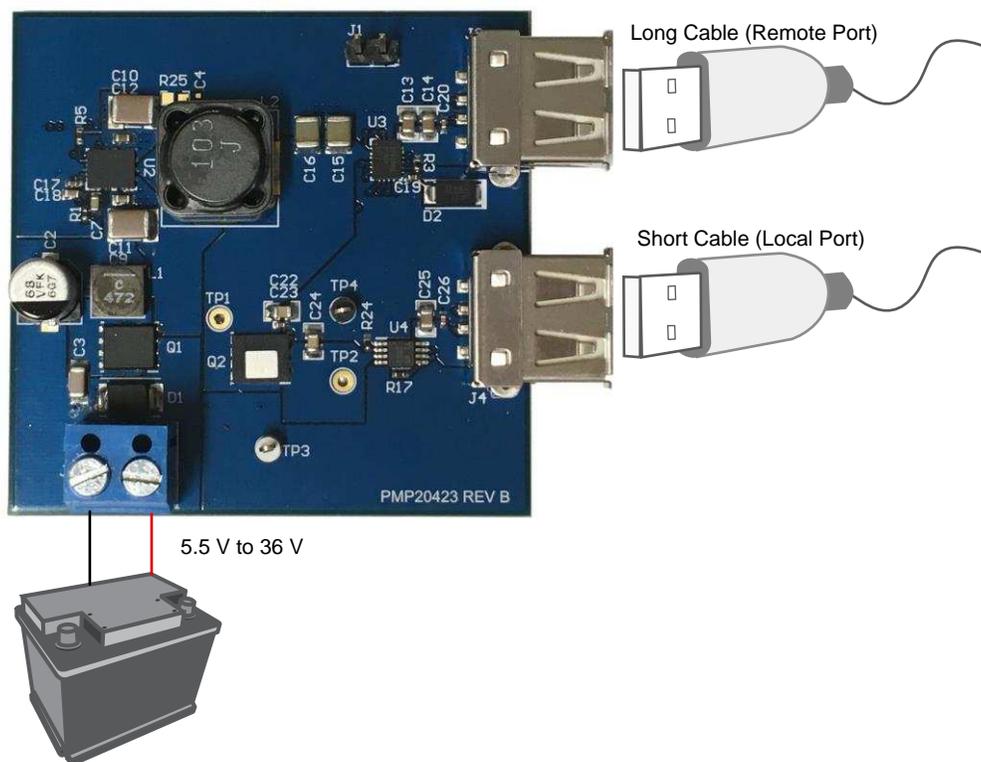



图 20. Getting Started Hardware

## 4 Testing and Results

The four-layer, 2-oz copper layer board was tested with a 1-m USB cable for the remote port. The local port was a point of load connection to an electronic load.

### 4.1 Start-Up

The following [图 21](#) shows the start-up of the LMS3655 device at the TPS254900 output (remote port, pink), the start-up of the linear regulator at the TPS2511 output (local port, green), and  $V_{IN}$  (gold) where  $V_{IN} = 12\text{ V}$  with both ports at a 0-A load.

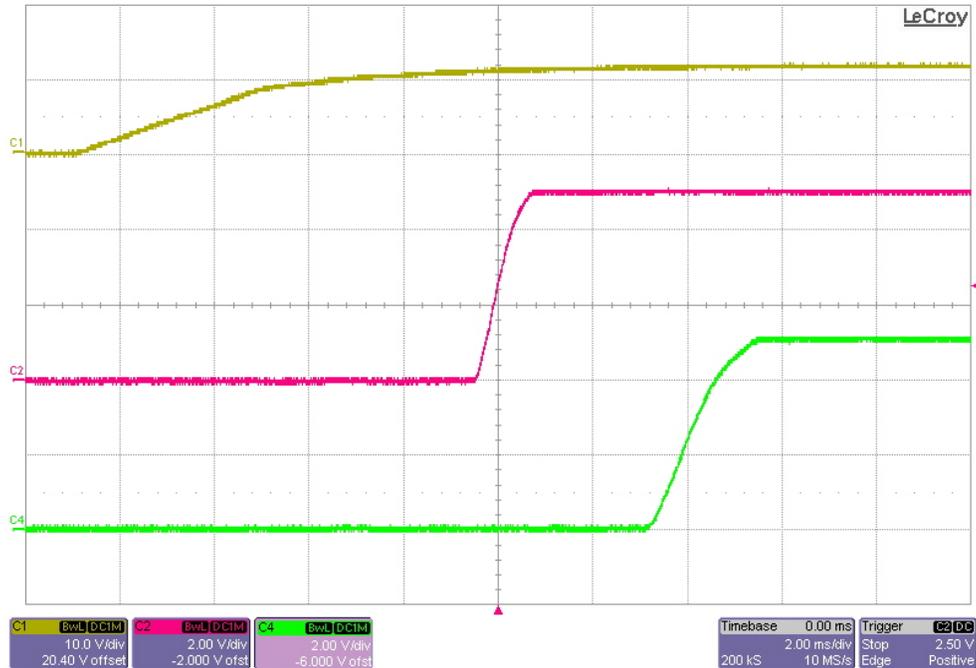

**图 21. Startup Voltage at  $V_{IN} = 12\text{ V}$ ,  $I_{OUT} = 0\text{ A}$**

### 4.2 Output Voltage

The converter voltage is one of the main concerns in this design. By measuring the output voltage based on the truth table from [表 8](#), the designer can determine if both ports can support tight requirements even using a single DC-DC. The following [表 9](#) shows the measurements. As the preceding [表 8](#) shows, 0 indicates no load and 1 indicates a full load at 2.4 A.

**表 9. Truth Table Measurements**

REMOTE LOAD	LOCAL LOAD	VBUS	REMOTE PORT VOLTAGE	LOCAL PORT VOLTAGE
0	0	5.089 V	5.089 V	5.089 V
0	1	5.086 V	5.086 V	4.876 V
1	0	5.617 V	5.081 V	5.094 V
1	1	5.610 V	5.092 V	4.890 V

### 4.2.1 Output Ripple

The waveform in the following 图 22 was captured at the remote port with  $V_{IN} = 12\text{ V}$  and the remote port loaded to 2.4 A while the local port was loaded to 0 A.

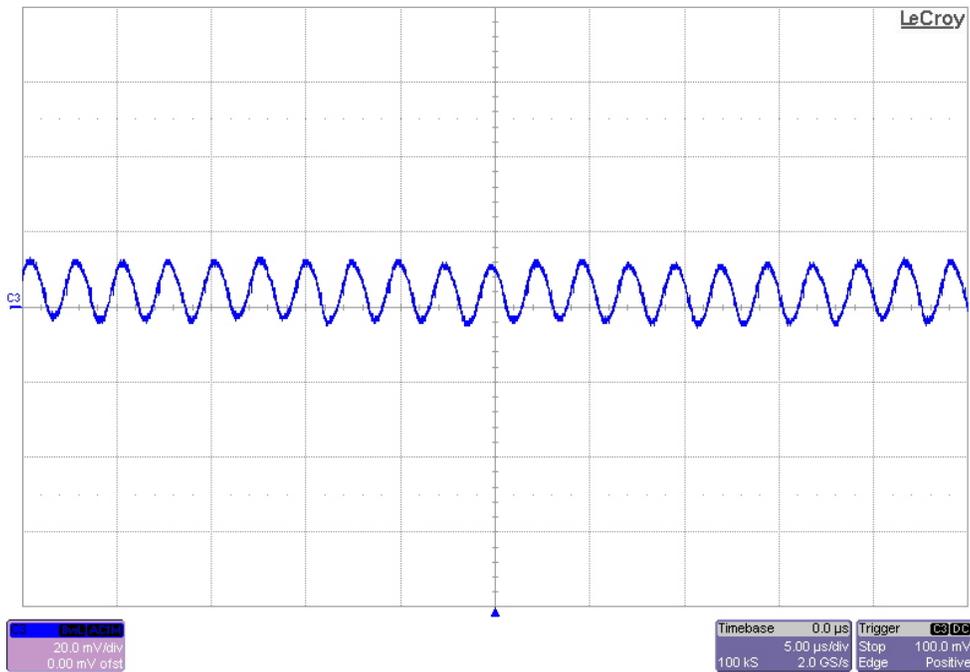


图 22. Output Ripple  $V_{IN} = 12\text{ V}$ , Remote Port = 2.4 A, Local Port = 0 A


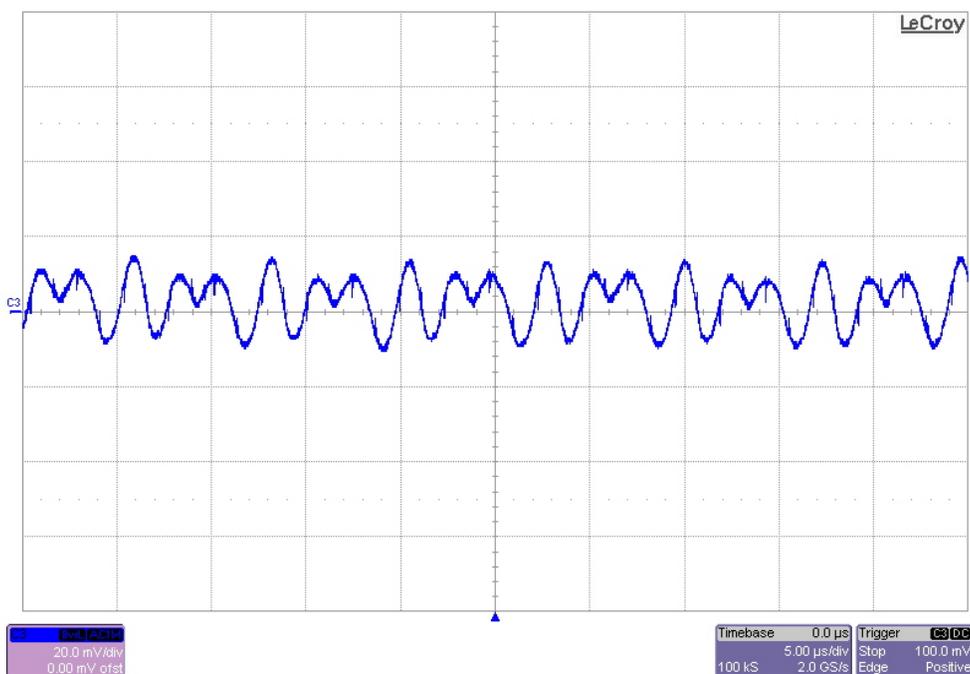


图 23. Output Ripple  $V_{IN} = 12\text{ V}$ , Remote Port = 2.4 A, Local Port = 2.4 A

## 4.2.2 Load Transients

The capture in the following [图 24](#) was taken at the remote port, with the remote load current being stepped between 0 A and 2.4 A with  $V_{IN} = 12$  V. The offset phenomena shown is due to the cable compensation offset voltage, which jumps to approximately 500 mV at 2.4 A. The local port was loaded at 2.4 A.

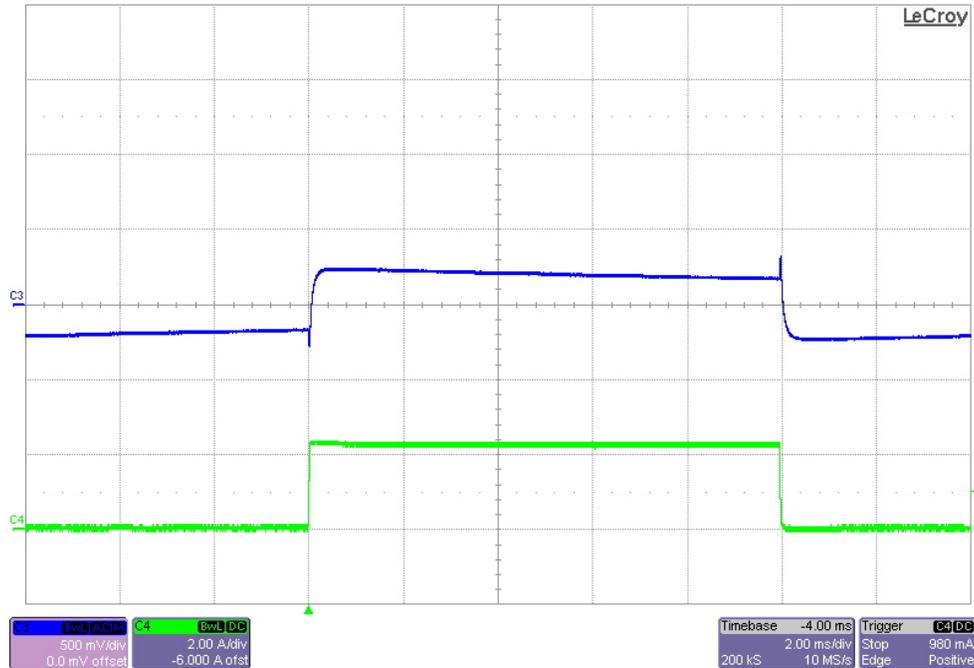

**图 24. Transient  $V_{IN} = 12$  V, Remote Load = 0 A to 2.4 A, Local Load = 2.4 A (Static)**

The following [图 25](#) was taken at the local port, with the local port stepping from 0 A to 2.4 A and remote port fully loaded to a static 2.4 A.


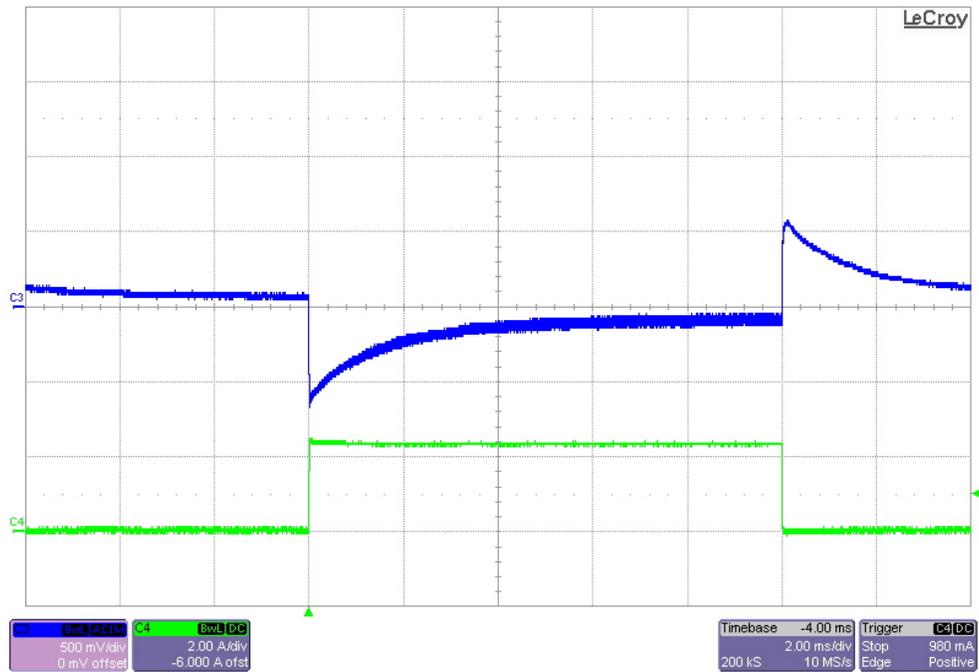


图 25. Transient  $V_{IN} = 12\text{ V}$ , Remote Load = 2.4 A (Static), Local Load = 0 A to 2.4 A

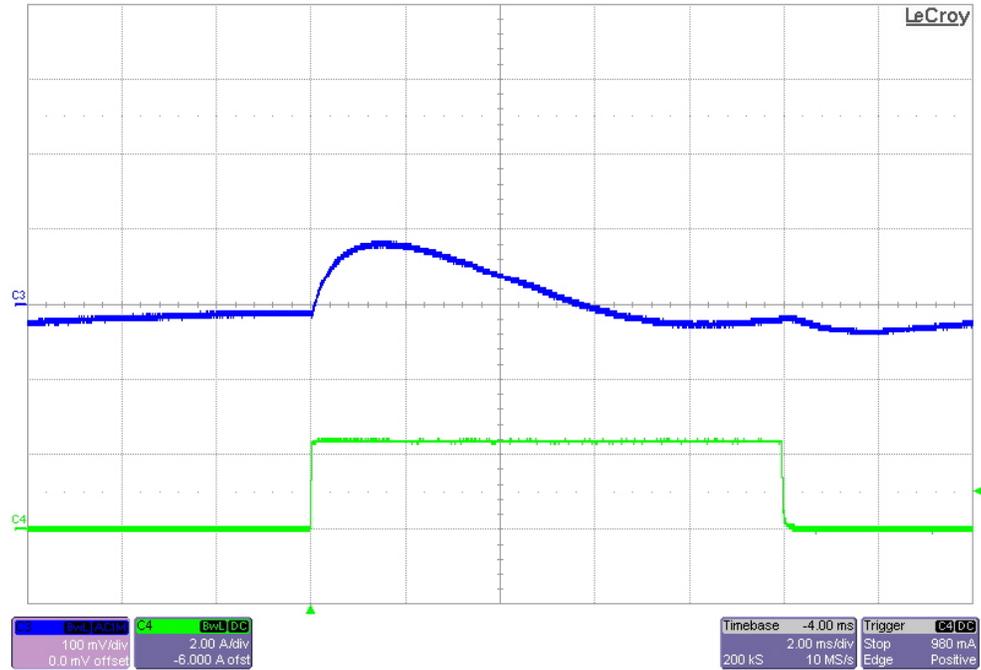
The capture in the following  was taken at the local port. The local port is unloaded during this time at 0 A, while the remote port is being stepped from 0 A to 2.4 A.



 26. Transient  $V_{IN} = 12$  V, Remote Load = 0 A to 2.4 A, Local Load = 0 (Static)
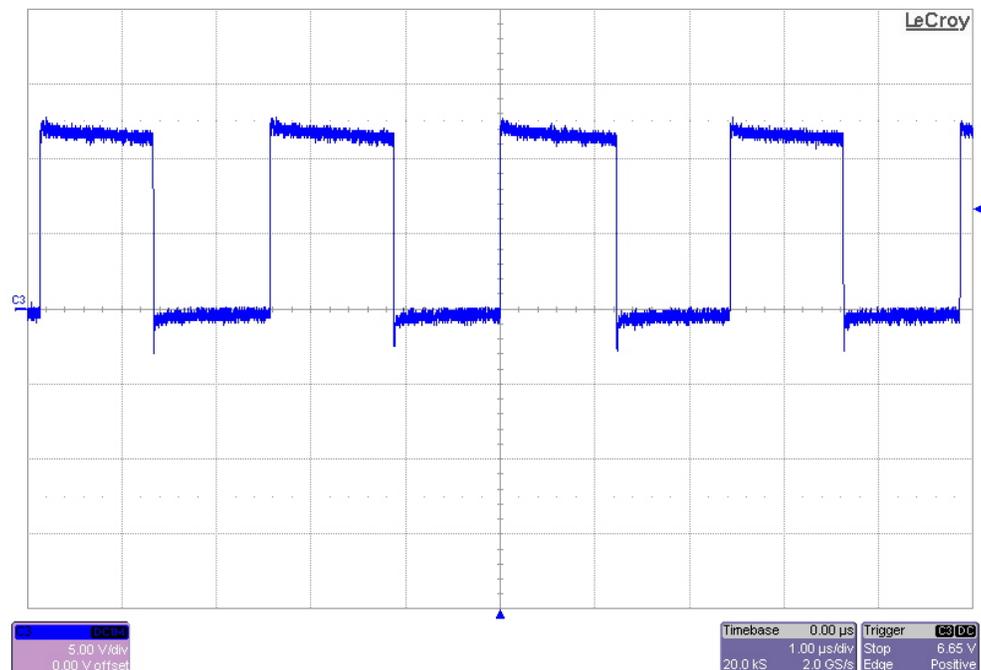
### 4.3 Switch Node

The following  shows the L1 switch node. This image was taken at  $V_{IN} = 12$  V with both ports loaded at 2.4 A, each.



 27. Switch Node  $V_{IN} = 12$  V, Remote Load = 2.4 A, Local Load = 2.4 A

### 4.4 Loop Response

The following 图 28 shows the loop response for the DC-DC LMS3655.

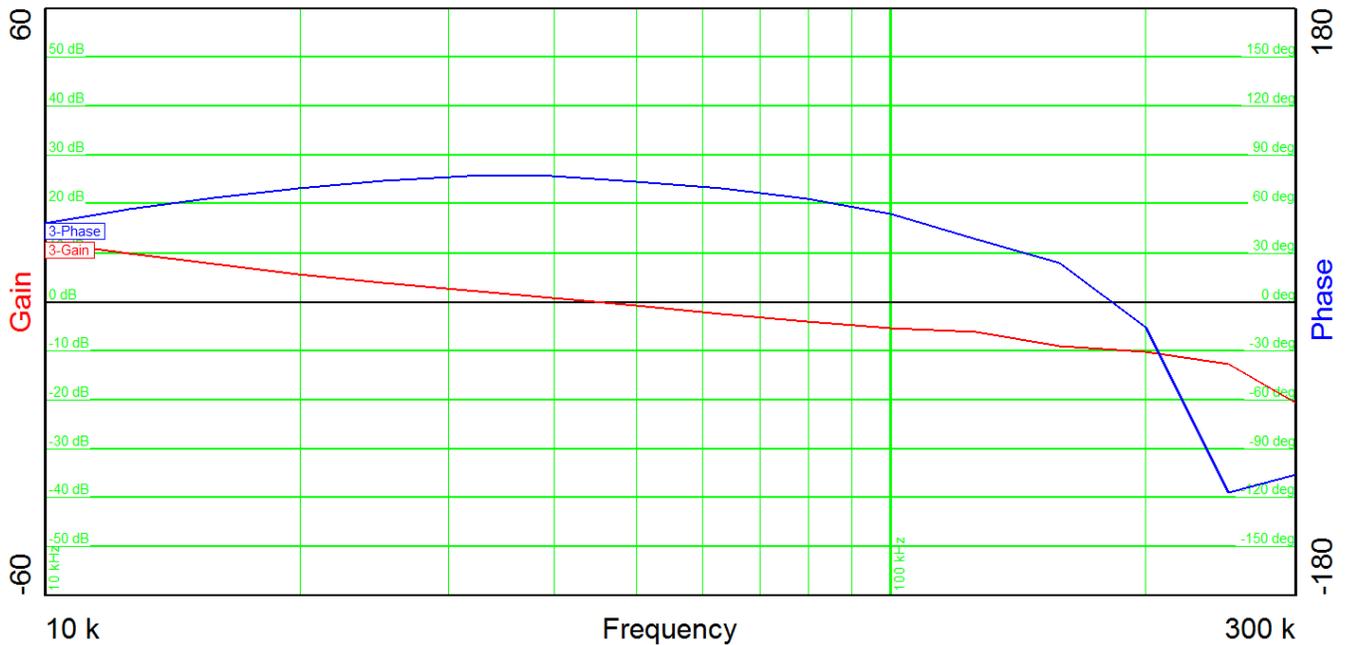


图 28. Loop Response,  $V_{IN} = 12\text{ V}$ , Full Load

### 4.5 Thermal Images

The following 图 29 and 图 30 are the thermal images of the board taken with  $V_{IN} = 12\text{ V}$ , a load of 2.4 A on each port, and no airflow. The board thermal was taken after 15 min of full loading.

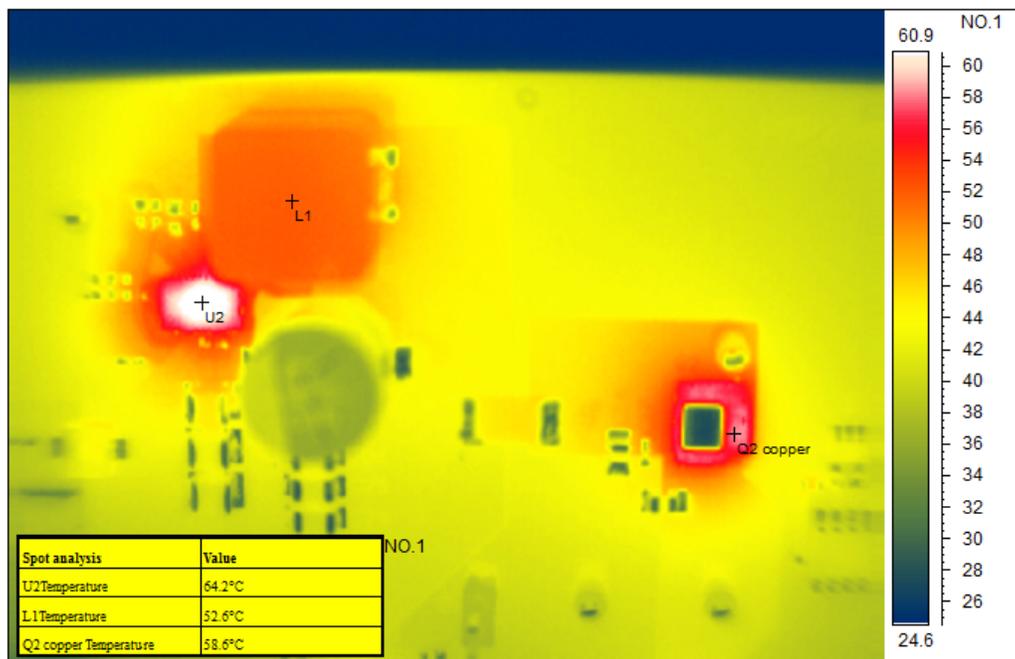


图 29. Thermal Image at Full Load—Front Side

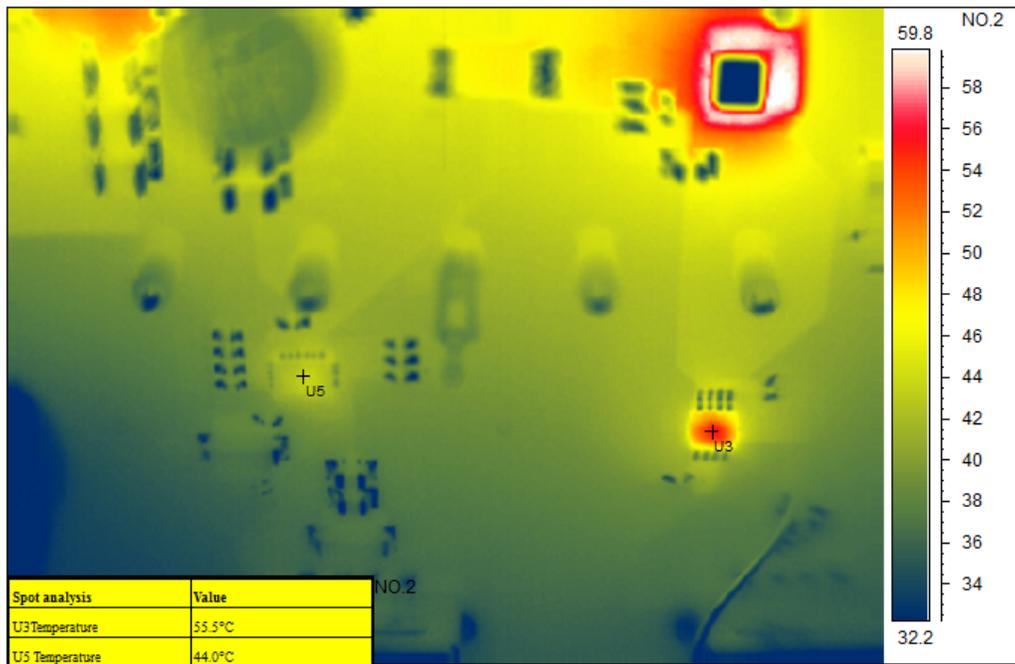


图 30. Thermal Image at Full Load—Back Side

#### 4.6 CISPR 25 Class 4 Testing

This reference design was built and tested with the goal to pass CISPR 25 standards and currently meets Class 4 of the CISPR classification standards. This CISPR EMI testing is performed using a third-party facility and follows this international standard "to protect onboard receivers from disturbances produced by conducted and radiated emissions arising in a vehicle," <sup>(1)</sup> which means that this particular design has been tested to make sure that it does not interfere with other equipment in the vehicle. As outlined in the standard, radiated disturbances do not disrupt the broadcast and mobile service or band. For this particular reference design, the broadcast standards were tested at peak, quasi-peak, and average ratings. This section outlines the individual tests for radiated and conducted emissions. For both types of tests, a car battery or a 14.5-V power supply was used in conjunction with short cables to test at the optimized performance. Additionally, resistive loads were used to emulate similar types of loads that USB devices may draw.

##### 4.6.1 Radiated Emissions

The absorber-lined shielded-enclosure (ALSE) procedure was used for testing radiated emissions. This procedure involves a chamber that has RF absorber material along the walls and ceiling of the enclosure. 表 10 和 表 11 show the broadcast lists of examples for average, quasi-peak, and peak limits for radiated disturbances for this particular ALSE method.

<sup>(1)</sup> CISPR 25 Ed. 3.0 b: 2008, pg. 7

表 10. ALSE Average Levels for CISPR 25 Radiated Emissions

SERVICE OR BAND	FREQUENCY (MHz)	LEVELS IN dB (µV/m)				
		CLASS 1	CLASS 2	CLASS 3	CLASS 4	CLASS 5
BROADCAST		AVG	AVG	AVG	AVG	AVG
LW	0, 15 - 0, 30	66	56	46	36	26


表 10. ALSE Average Levels for CISPR 25 Radiated Emissions (continued)

SERVICE OR BAND	FREQUENCY (MHz)	LEVELS IN dB (µV/m)				
		CLASS 1	CLASS 2	CLASS 3	CLASS 4	CLASS 5
BROADCAST		AVG	AVG	AVG	AVG	AVG
MW	0, 53 - 1, 8	52	44	36	28	20
SW	5, 9 - 6, 2	44	38	32	26	20
FM	76 - 108	42	36	30	24	18
TV band I	41 - 88	42	36	30	24	18
TV band II	174- 230	46	40	34	28	22
DAB III	171 - 245	50	34	28	22	16
TV band IV/V	468 - 944	55	49	43	37	31
DTTV	470 - 770	59	53	47	41	35
DAB L band	1447 - 1494	42	36	30	24	18
SDARS	2320 - 2345	48	42	36	30	24

表 11. ALSE Peak and Quasi-Peak Levels for CISPR 25 Radiated Emissions

SERVICE OR BAND	FREQUENCY (MHz)	LEVELS IN dB (µV/m)									
		CLASS 1		CLASS 2		CLASS 3		CLASS 4		CLASS 5	
		PEAK	QUASI	PEAK	QUASI	PEAK	QUASI	PEAK	QUASI	PEAK	QUASI
BROADCAST											
LW	0,15-0,30	86	73	76	63	66	53	56	43	46	33
MW	0,53-1,8	72	59	64	51	56	43	48	35	40	27
SW	5,9-6,2	64	51	58	45	52	39	46	33	40	27
FM	76-108	62	49	56	43	50	37	44	31	38	25
TV Band I	41-88	52	—	46	—	40	—	34	—	28	—
TV Band III	174-230	56	—	50	—	44	—	38	—	32	—
DAB III	171-245	50	—	44	—	38	—	32	—	26	—
TV Band IV	468-944	65	—	59	—	53	—	47	—	41	—
DTTV	470-770	69	—	63	—	57	—	51	—	45	—
DAB L Band	1447-1494	52	—	46	—	40	—	34	—	28	—
SDARS	2320-2345	58	—	52	—	46	—	40	—	34	—

For the ALSE method of radiated emissions testing, four different antennas are used to measure the full range of testing and three antennas were tested in a vertical polarization and horizontal polarization. Additionally, ambient readings were taken before each test. 图 31 shows a diagram of the first test using a rod antenna (only one polarization option). This test was conducted for the frequency range between 150 kHz to 30 MHz. This band is particularly important to test because it captures the range for the AM and FM radio frequencies.

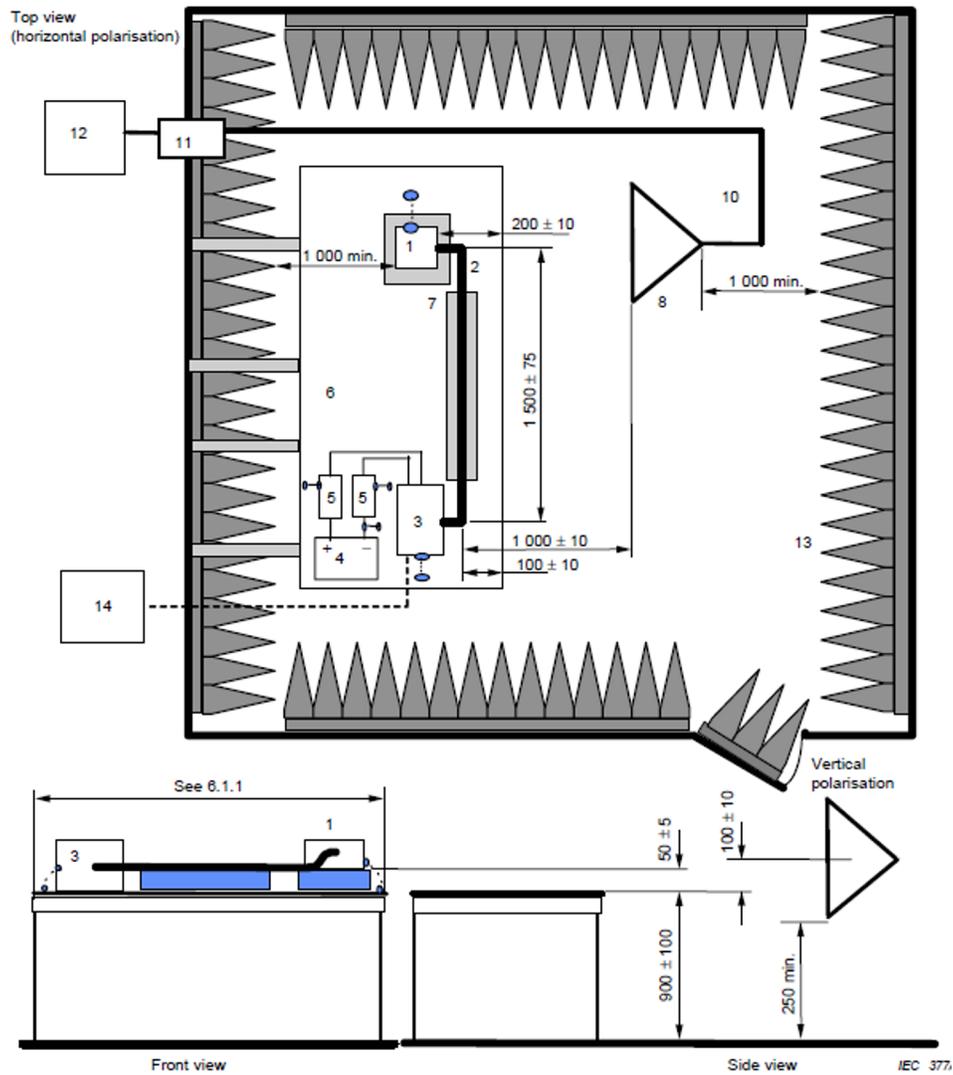

**Key**

- |   |   |
|---|---|
| 1 EUT (grounded locally if required in test plan)                       | 8 Horn antenna  |
| 2 Test harness  | 10 High-quality coaxial cable e.g. double-shielded (50 Ω) |
| 3 Load simulator (placement and ground connection according to 6.4.2.5) | 11 Bulkhead connector                                     |
| 4 Power supply (location optional)                                      | 12 Measuring instrument                                   |
| 5 Artificial network (AN)   | 13 RF absorber material                                   |
| 6 Ground plane (bonded to shielded enclosure)                           | 14 Stimulation and monitoring system                      |
| 7 Low relative permittivity support ( $\epsilon_r \leq 1.4$ )           |   |

图 31. Radiated Emissions Test Setup

The following figures show the ambient reading and the radiated emissions of the design. The first peak at 400 kHz is easy to identify and corresponds to the switching frequency of the LMS3655-Q1 device. Subsequent peaks are also observable at the fundamentals for the switching frequency at approximately 1.2 MHz, 2.0 MHz, and so on. This reference design has passed all peak and quasi-peak limits as indicated in the CISPR 25 Class 4 documentation. For the 530-kHz to 1.8-MHz CISPR 25 Class 5 specification, the quasi-peak indicates a limit at 27 dB and this design remains at 30.7 dB. For average measurements, the documentation dictates a limit of 20 dB while this design sits at 25.8 dB. For further improvements to the design (to pass the CISPR 25 Class 5 standard), see [LMS3635-Q1 3.5-A](#), [LMS3655-Q1 5.5-A](#), [36-V Synchronous, 400-kHz Step-Down Converter](#).

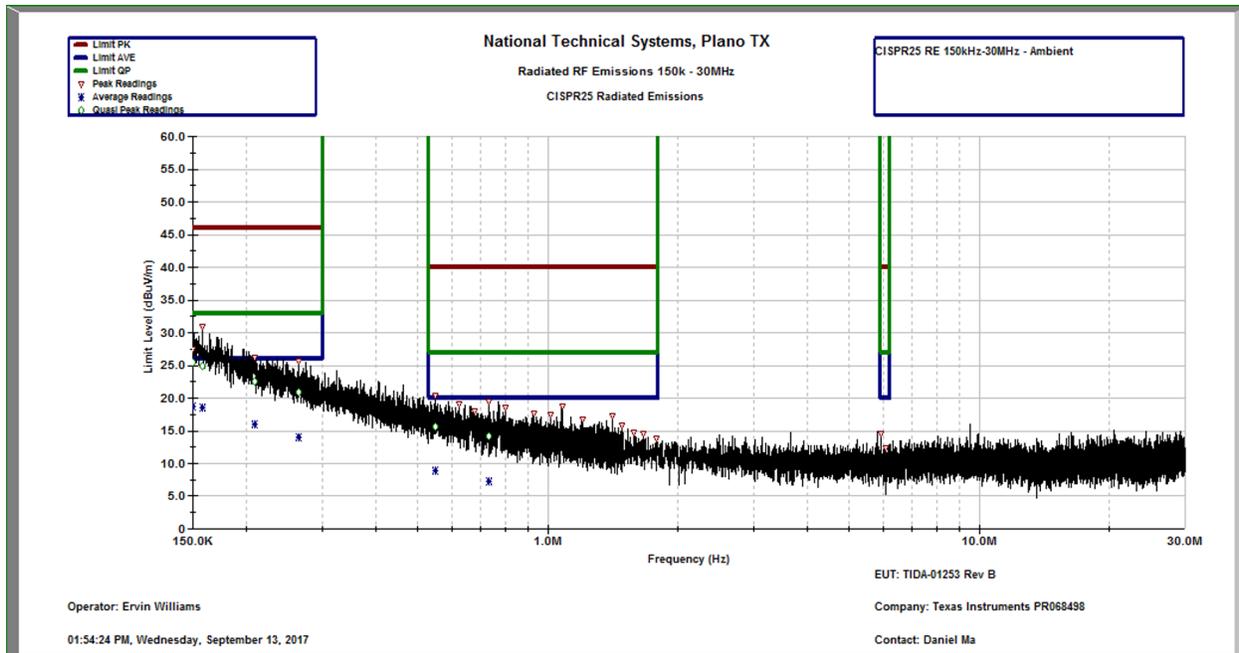


图 32. Radiated Ambient 150 kHz to 30 MHz

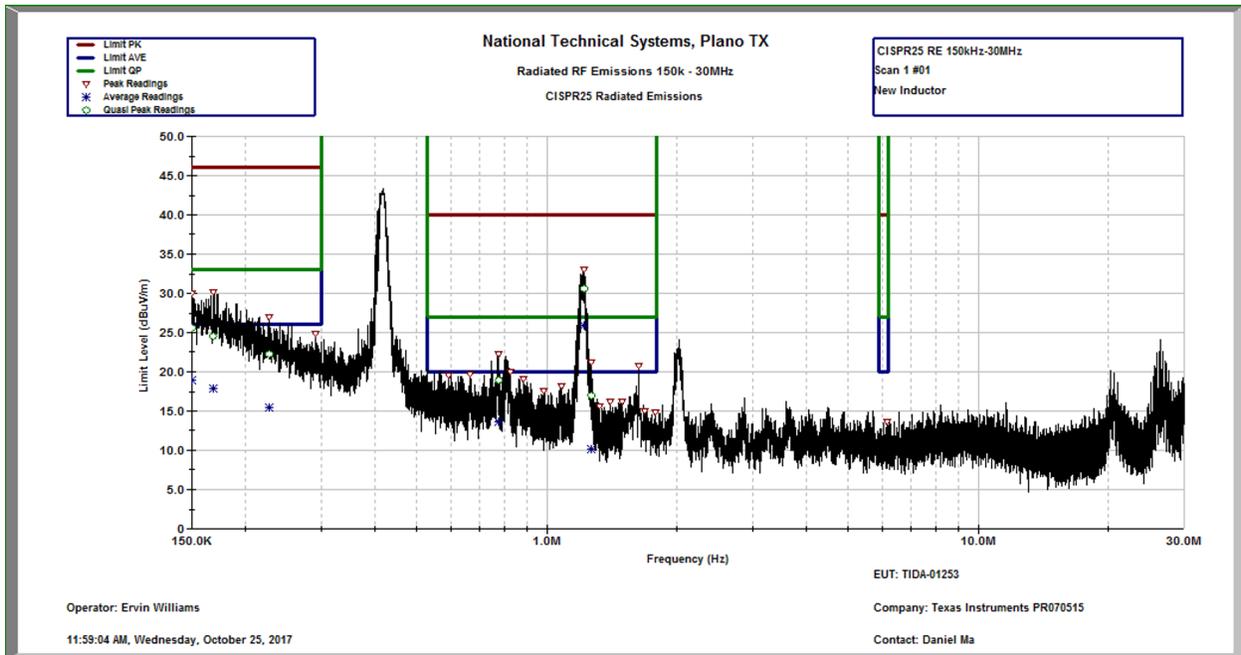


图 33. Radiated Emissions 150 kHz to 30 MHz

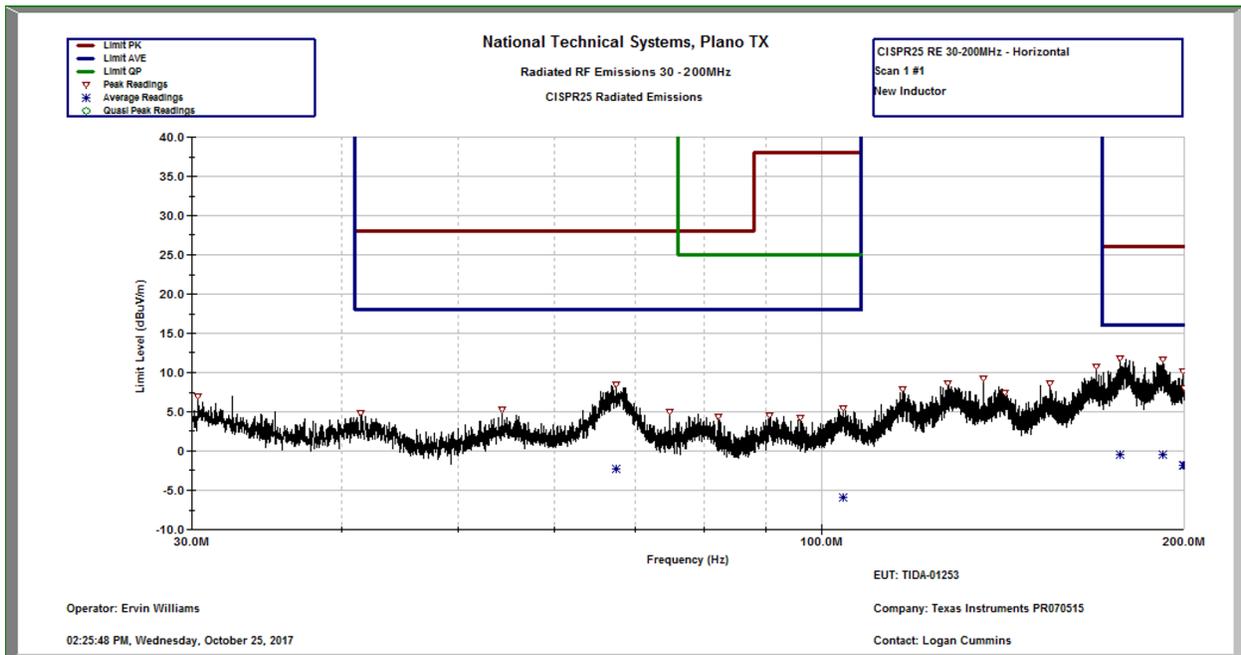


图 34. Radiated Emissions 30 MHz to 200 MHz

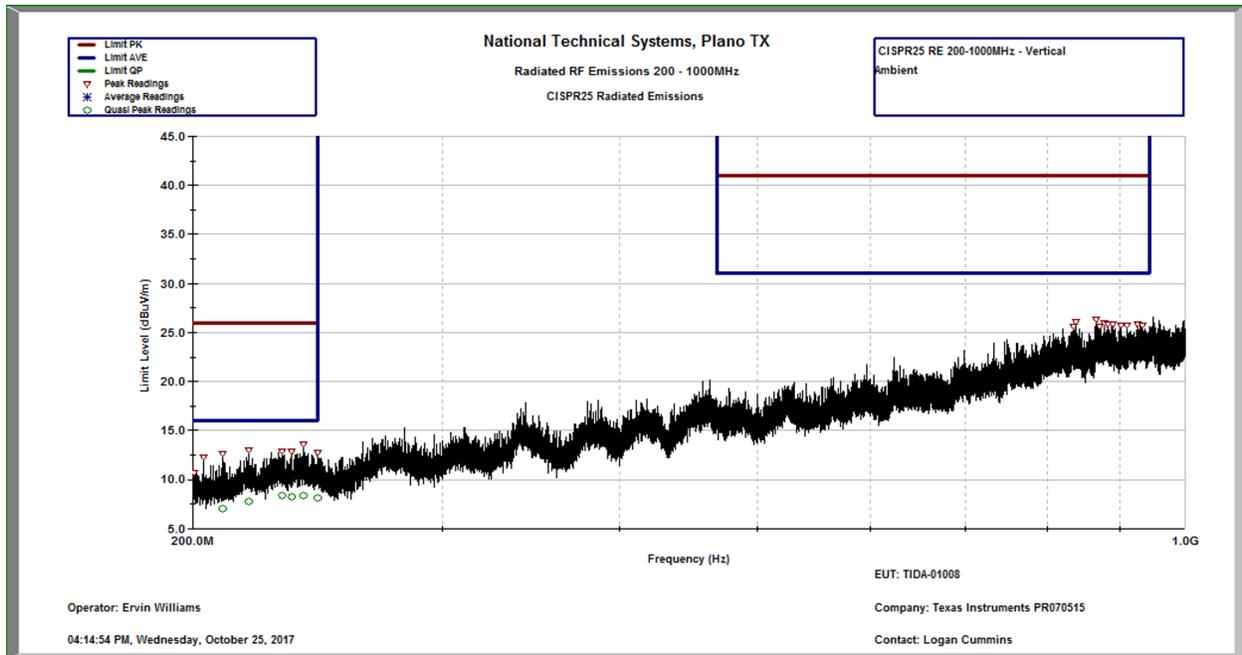


图 35. Radiated Emissions 200 MHz to 1 GHz

#### 4.6.2 Conducted Emissions

A similar test setup is required for conducted emissions testing; however, no antennas are used. There are several variations in testing that are dependent upon the system under test. For this particular reference design, the voltage method was used and the following 表 12 and 表 13 indicate the average, quasi-peak, and peak limits for these tests.


表 12. ALSE Average Levels for CISPR 25 Conducted Emissions

SERVICE OR BAND	FREQUENCY (MHz)	LEVELS IN dB ( $\mu$ V)				
		CLASS 1	CLASS 2	CLASS 3	CLASS 4	CLASS 5
<b>BROADCAST</b>		<b>AVG</b>	<b>AVG</b>	<b>AVG</b>	<b>AVG</b>	<b>AVG</b>
LW	0, 15 - 0, 30	90	80	70	60	50
MW	0, 53 - 1, 8	66	58	50	42	34
SW	5, 9 - 6, 2	57	51	45	39	33
FM	76 - 108	42	36	30	24	18
TV band I	41 - 88	48	42	36	30	24
TV band II	174- 230	Conducted emission --Voltage method Not applicable				
DAB III	171 - 245					
TV band IV/V	468 - 944					
DTTV	470 - 770					
DAB L band	1447 - 1494					
SDARS	2320 - 2345					

表 13. ALSE Peak and Quasi-Peak Levels for CISPR 25 Conducted Emissions

SERVICE OR BAND	FREQUENCY (MHz)	LEVELS IN dB ( $\mu$ V/m)									
		CLASS 1		CLASS 2		CLASS 3		CLASS 4		CLASS 5	
<b>BROADCAST</b>		<b>PEAK</b>	<b>QUASI</b>	<b>PEAK</b>	<b>QUASI</b>	<b>PEAK</b>	<b>QUASI</b>	<b>PEAK</b>	<b>QUASI</b>	<b>PEAK</b>	<b>QUASI</b>
LW	0, 15 - 0, 30	110	97	100	87	90	77	80	67	70	57
MW	0, 53 - 1, 8	86	73	78	65	70	57	62	49	54	41
SW	5, 9 - 6, 2	77	64	71	58	65	52	59	46	53	40
FM	76 - 108	62	49	56	43	50	37	44	31	38	25
TV Band I	41 - 88	58	—	52	—	46	—	40	—	34	—
TV Band III	174 - 230	Conducted Emission --Voltage Method Not Applicable									
DAB III	171 - 245										
TV Band IV	468 - 944										
DTTV	470 - 770										
DAB L Band	1447 - 1494										
SDARS	2320 - 2345										

For the voltage method of conducted emissions testing, both the positive terminal and negative terminal of the line impedance stabilization networks (LISNs) were used to measure the full range of testing. Additionally, ambient readings were taken before each test. 图 36 shows a diagram of the conducted test. This test was performed for the 150-kHz to 108-MHz frequency range. This band is particularly important to test because it captures the range for the AM and FM radio frequencies.

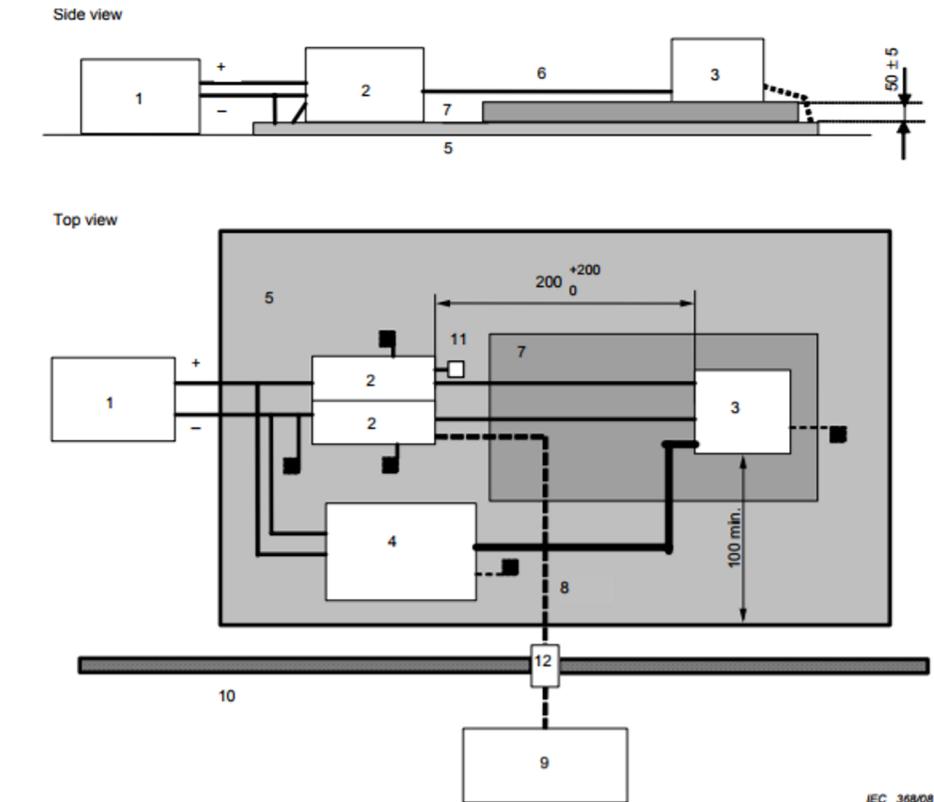

**Key**

- |  |  |
|--|--|
| 1 Power supply (may be placed on the ground plane)                   | 7 Low relative permittivity support ( $\epsilon_r \leq 1,4$ )    |
| 2 Artificial network   | 8 High-quality coaxial cable e.g. double-shielded (50 $\Omega$ ) |
| 3 EUT (housing grounded if required in test plan)                    | 9 Measuring instrument   |
| 4 Load simulator (metallic casing grounded if required in test plan) | 10 Shielded enclosure  |
| 5 Ground plane   | 11 50 $\Omega$ load  |
| 6 Power supply lines   | 12 Bulkhead connector  |

NOTE The EUT housing ground lead, when required in the test plan, should not be longer than 150 mm.

图 36. Conducted Emissions Test Setup

The following figures show the ambient reading, low-side reading, and return reading, respectively. A jump is present in the ambient reading due to the change in bandwidth to 30 MHz.

For the conducted emissions measurements, the 400 kHz is easy to identify and corresponds to the switching frequency of the LMS3655-Q1 device. On the return side, subsequent peaks are observable at the fundamentals for the switching frequency at approximately 1.2 MHz, 2 MHz, and so on. This reference design has passed all peak and quasi-peak limits as indicated in the CISPR 25 Class 5 documentation for ranges 150 kHz to 108 MHz.

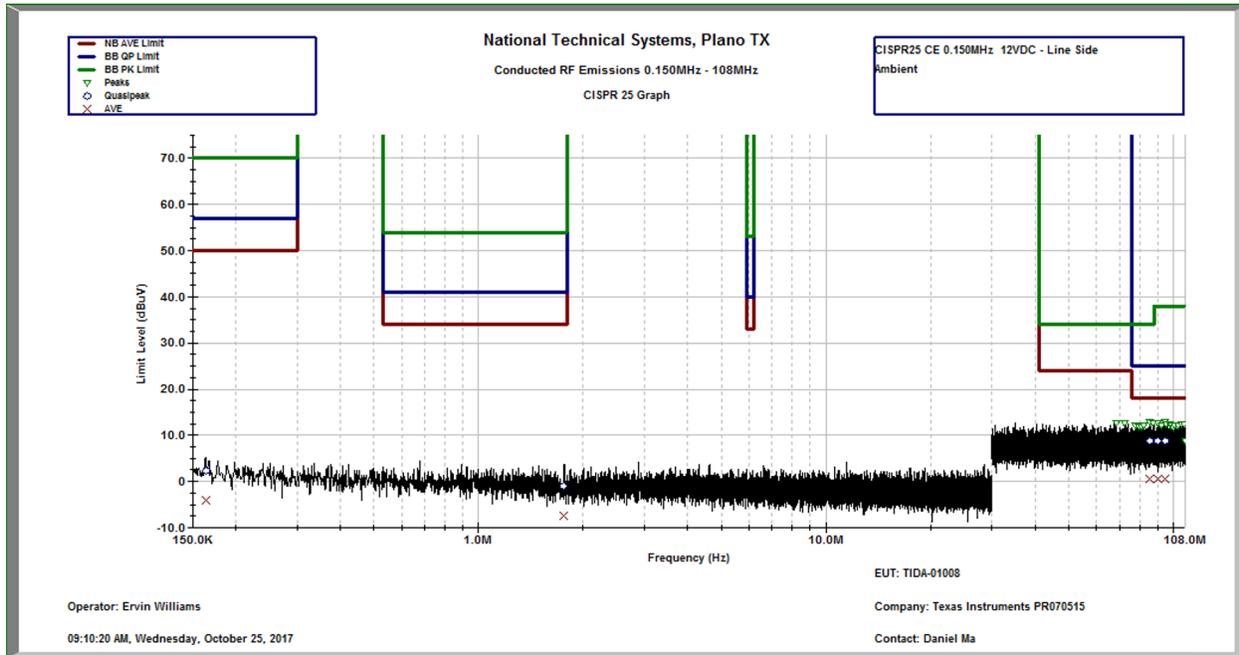


图 37. Conducted Emissions Ambient 150 kHz to 108 MHz

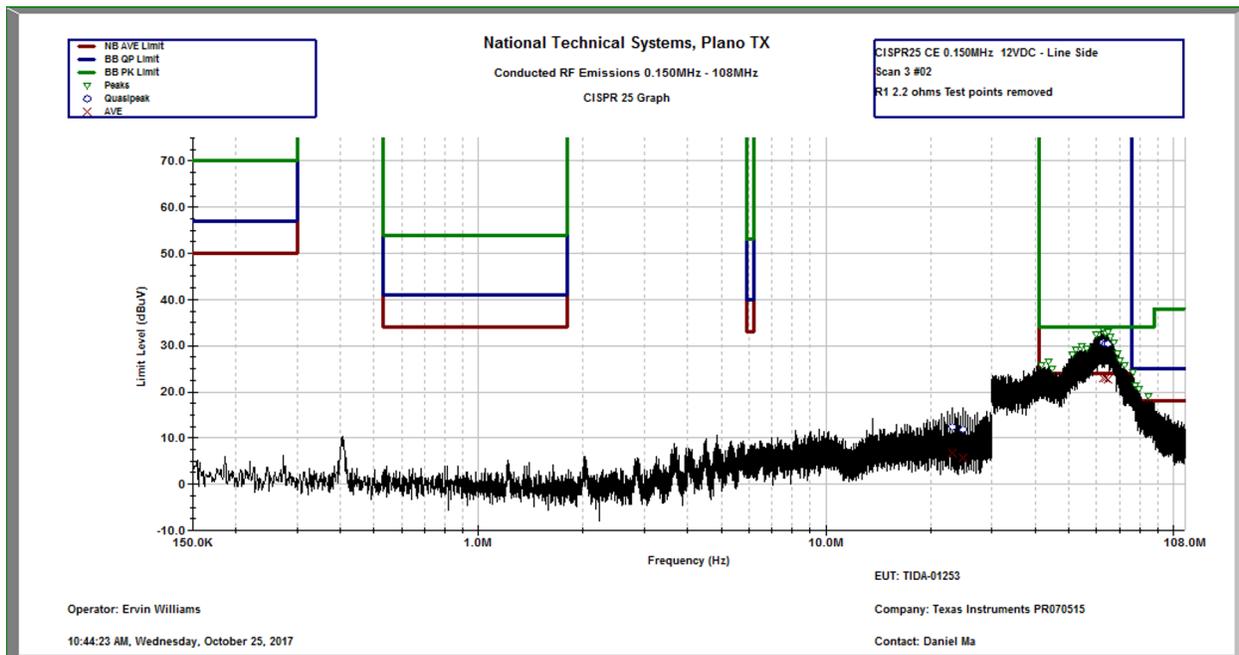


图 38. Conducted Emissions Line 150 kHz to 108 MHz

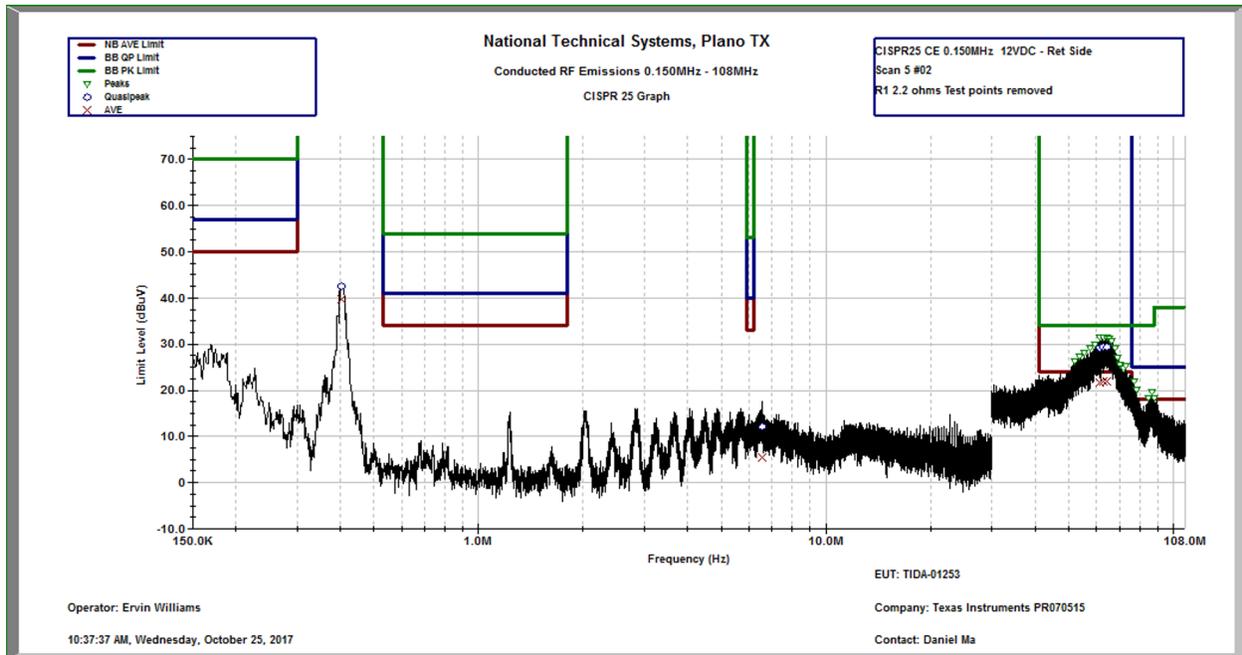


图 39. Conducted Emissions Return 150 kHz to 108 MHz

## 5 Design Files

### 5.1 Schematics

To download the schematics, see the design files at [TIDA-01253](#).

### 5.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01253](#).

### 5.3 PCB Layout Recommendations

The TIDA-01253 PCB is a four-layer board:

- The top layer has the majority of components
- The second layer is a GND plane
- The third layer is signals
- The fourth layer is also a GND plane

Follow the recommendation from the corresponding data sheet diligently for most of the components, while making a few minor deviations to optimize for EMI constraints. Fully fill the top and bottom layer with copper for the ideal thermal performance. For a layout guide, follow the recommendations for individual components in the following subsections and their respective data sheets. The following subsection walks through some recommendations for the board layout.

#### 5.3.1 DC-DC Converter

The more challenging layout of this design is the DC-DC converter. The following recommendations have been considered to maximize performance and reduce EMI:

- Compact layout and feedback resistors
- Ground plane and shape routing
- Thermal design

##### 5.3.1.1 Compact Layout and Feedback Resistors

EMI is reduced by keeping switching current loops small. Minimizing the size of high di/dt areas helps to reduce radiated EMI.

1. The switching current loops for the switch node and other switching signals are kept small.
2. The input capacitors,  $C_{in}$ , are placed close to the input and use a common ground with the output capacitors.
3. The feedback, soft-start, and enable components are routed to the AGND terminal of the device at a single point of ground, which prevents any switched currents or load currents from flowing in the analog ground traces. Poor grounding can result in degraded load regulation or erratic output-voltage ripple behavior.
4. The size of the FB node was minimized because the feedback node is a significant source of noise. Keeping feedback resistors away from the switch node helps to minimize the coupling of this noise. All of the feedback resistors R10, R14, and R5 are placed close to the FB terminal and the feedforward capacitor C7 is placed directly in parallel with R5.

##### 5.3.1.2 Ground Plane and Shape Routing

The input plane and output plane are kept as wide as possible to reduce any voltage drops on the input or output of the converter to maximize efficiency.

### 5.3.1.3 Thermal Design

An array of heat-sinking vias are connected from the exposed pad to the fourth-layer planes. For best results, use a minimum via diameter of 12 mil with thermal vias spaced 46.8-mil apart. As indicated in 4 节, 2 oz of copper per layer is used to ensure enough copper area is available for heat-sinking to maintain the junction temperature below 125°C.

### 5.3.2 TPS254900 Layout Recommendation

To follow the recommendations for this particular part, refer to the data sheet [3]. The following instructions highlight some of the slight variances from the data sheet recommendation that pertain specifically to this reference design. Many of the surrounding components are simply configuration passives and it is important to create a close, compact placement between these components and the TPS254900 device. One of the most important considerations for the layout of this component are the DP\_IN, DN\_IN, DP\_OUT, and DN\_OUT signals. USB-IF standards for the USB2.0, universal serial bus 2.0 specification, and data require that these lines must be 90-Ω differential pairs. Additionally, trace length matching is a concern, so adding trace length is beneficial to maintaining signal integrity. A free online [Impedance calculator](#) from Mantaro Product Development Services [4] can be used to calculate the differential micro strip impedance, trace width, separation, and so on. For the DP\_IN/DN\_IN signal pair coming from the USB type-A connector, the signals are differentially routed on the top layer and signal layer 2. A GND plane is situated directly below the DP\_IN/DN\_IN layer to keep the signals from coupling with other traces. The same GND layer consideration should be taken into consideration for DP\_OUT/DN\_OUT, which is routed to J1.

### 5.3.3 LM74610 Layout Recommendation

For the reverse battery protection, the input capacitors are placed on the front of the board and the ideal recommendation is to rotate them 90° from each other due to possible flexing of the board. Take care to keep these components close to the input connectors of the board. The input to the LM74610 passes through the TVS diodes to pin 4 and the anode of Q1. To make routing easier, Q1 is placed below the LM74610 with C12 so that the gate drive and gate pull down of Q1 and VCAPH/VCAPL can be routed on signal layer 2 underneath the part. The output and cathode of Q1 goes directly to the pi filter. For additional EMI protection, a common-mode choke can be used with the pi filter to reduce high-frequency EMI.

## 5.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01253](#).

## 5.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01253](#).

## 5.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01253](#).

## 6 Software Files

To download the software files, see the design files at [TIDA-01253](#).

## 7 Related Documentation

1. Texas Instruments, [LM74610-Q1 Zero IQ Reverse Polarity Protection Smart Diode Controller](#)
2. Texas Instruments, [LMS3635-Q1 3.5-A, LMS3655-Q1 5.5-A, 36-V Synchronous, 400-kHz Step-Down Converter](#)
3. Texas Instruments, [TPS254900-Q1 Automotive USB Host Charger With Short-to- \$V\_{BATT}\$  Protection](#)
4. Mantaro.com, [Impedance Calculators](#)

### 7.1 商标

DualCool, NexFET are trademarks of Texas Instruments.  
WEBENCH is a registered trademark of Texas Instruments.

## 8 About the Author

**HOPE BOVENZI** is a Systems Engineer at Texas Instruments. Hope earned her bachelor of science in electrical engineering from the University of California at Davis in 2012. As a member of the Automotive Systems Engineering team at Texas Instruments, she is responsible for developing reference design solutions for the Automotive Infotainment and Cluster segment and has a background in power design.

## 9 Special Thanks

Special thanks to **CHRIS SARLI** and **DANIEL MA** for layout and testing considerations in this design

## 有关 TI 设计信息和资源的重要通知

德州仪器 (TI) 公司提供的技术、应用或其他设计建议、服务或信息，包括但不限于与评估模块有关的参考设计和材料（总称“TI 资源”），旨在帮助设计人员开发整合了 TI 产品的应用；如果您（个人，或如果是代表贵公司，则为贵公司）以任何方式下载、访问或使用了任何特定的 TI 资源，即表示贵方同意仅为该等目标，按照本通知的条款进行使用。

TI 所提供的 TI 资源，并未扩大或以其他方式修改 TI 对 TI 产品的公开适用的质保及质保免责声明；也未导致 TI 承担任何额外的义务或责任。TI 有权对其 TI 资源进行纠正、增强、改进和其他修改。

您理解并同意，在设计应用时应自行实施独立的分析、评价和判断，且应全权负责并确保应用的安全性，以及您的应用（包括应用中使用的 TI 产品）应符合所有适用的法律法规及其他相关要求。就您的应用声明，您具备制订和实施下列保障措施所需的一切必要专业知识，能够 (1) 预见故障的危险后果，(2) 监视故障及其后果，以及 (3) 降低可能导致危险的故障几率并采取适当措施。您同意，在使用或分发包含 TI 产品的任何应用前，您将彻底测试该等应用和该等应用所用 TI 产品的功能而设计。除特定 TI 资源的公开文档中明确列出的测试外，TI 未进行任何其他测试。

您只有在为开发包含该等 TI 资源所列 TI 产品的应用时，才被授权使用、复制和修改任何相关单项 TI 资源。但并未依据禁止反言原则或其他法律授予您任何 TI 知识产权的任何其他明示或默示的许可，也未授予您 TI 或第三方的任何技术或知识产权的许可，该等许可包括但不限于任何专利权、版权、屏蔽作品权或与使用 TI 产品或服务的任何整合、机器制作、流程相关的其他知识产权。涉及或参考了第三方产品或服务的信息不构成使用此类产品或服务的许可或与其相关的保证或认可。使用 TI 资源可能需要您向第三方获得对该等第三方专利或其他知识产权的许可。

TI 资源系“按原样”提供。TI 兹免除对 TI 资源及其使用作出所有其他明确或默示的保证或陈述，包括但不限于对准确性或完整性、产权保证、无屡发故障保证，以及适销性、适合特定用途和不侵犯任何第三方知识产权的任何默认保证。

TI 不负责任何申索，包括但不限于因组合产品所致或与之有关的申索，也不为您辩护或赔偿，即使该等产品组合已列于 TI 资源或其他地方。对因 TI 资源或其使用引起或与之有关的任何实际的、直接的、特殊的、附带的、间接的、惩罚性的、偶发的、从属或惩戒性损害赔偿，不管 TI 是否获悉可能会产生上述损害赔偿，TI 概不负责。

您同意向 TI 及其代表全额赔偿因您不遵守本通知条款和条件而引起的任何损害、费用、损失和/或责任。

本通知适用于 TI 资源。另有其他条款适用于某些类型的材料、TI 产品和服务的使用和采购。这些条款包括但不限于适用于 TI 的半导体产品 (<http://www.ti.com/sc/docs/stdterms.htm>)、[评估模块](http://www.ti.com/sc/docs/sampters.htm)和样品 (<http://www.ti.com/sc/docs/sampters.htm>) 的标准条款。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122  
Copyright © 2018 德州仪器半导体技术（上海）有限公司