

TI Designs: TIDA-01581

具有电流平衡功能的汽车日间行车灯双灯串 LED 驱动器参考设计



说明

该参考设计是一款双灯串发光二极管 (LED) 驱动器，它实现了一个用于平衡两个 LED 灯串中电流的运算放大器电路。该运算放大器电路可检测参考灯串中的电流，并使用来自镜像灯串的反馈对在这些灯串之间调节电流的 MOSFET 进行偏置。该设计使用采用升压配置的 TPS92692-Q1 多拓扑 LED 驱动器来驱动 LED。

TPS92692-Q1 采用 扩频频率调制，以提高抗电磁干扰 (EMI) 性能并实现模拟电流调节和内部脉宽调制 (PWM) 调光。该设计包含可调线性热折返特性（使用 LMT87-Q1 模拟温度传感器）以及电流限制功能，以便在镜像灯串无法打开电路时提供保护。该设计还 提供 两种亮度模式：一种模式是最大亮度模式（“DRL”），另一种模式是可以降低亮度的 PWM 调光模式（“位置”）。

资源

TIDA-01581	设计文件夹
TPS92692-Q1	产品文件夹
TLV2316-Q1	产品文件夹
LMT87-Q1	产品文件夹
LM2901-Q1	产品文件夹

特性


- 使用单个 LED 驱动器的双灯串电流平衡
- 针对 CISPR25 5 类传导和辐射发射进行了测试
- 可实现两种亮度模式的 PWM 调光
- 电流限制
- 通过冷启动运行
- 无需微控制器单元 (MCU) 即可运行

应用


- [汽车日间行车灯](#)
- [汽车前灯](#)
- [汽车尾灯和制动灯](#)



咨询我们的 E2E™ 专家

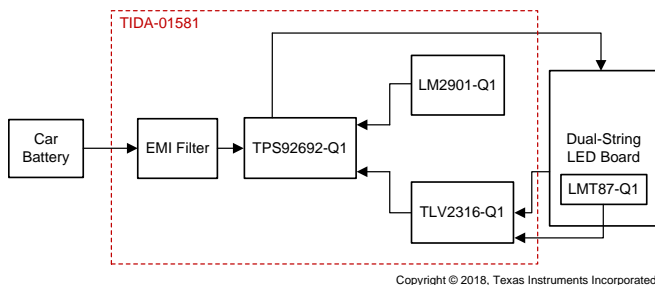

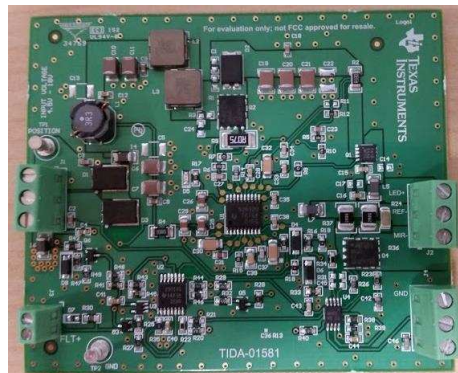Copyright © 2018, Texas Instruments Incorporated



该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

1 System Description

This reference design details a solution for driving two parallel LED strings in applications for automotive daytime-running lights or position lamps using only a single LED driver, while keeping the current in the two LED strings equal. Implementation of this dual-string current mirror design can reduce the voltage required to drive the LEDs by half as compared to driving the same number of LEDs in series. The system also includes EMI filtering, thermal foldback, and current limiting. EMI filtering reduces conducted and radiated emissions. Thermal foldback can reduce the LED current as temperature increases, which protects the LEDs from thermal failure. Current limiting protects the reference string if the mirrored string fails to open. This feature is important because it prevents the intended current from doubling and flowing through the reference string in this condition.


1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Input voltage	6 V to 18 V, 14 V (typ)
Input current	980 mA at 14 V
Output current (per string)	200 mA
Output power (both strings)	12 W
Output voltage	30 V (typ)
Number of series LEDs	10
LED forward voltage	3 V (typ)
Current balance accuracy	±2%
Boost converter switching frequency	390 kHz
Spread-spectrum frequency modulation dither frequency	600 Hz
PWM dimming frequency	240 Hz
Form factor	77 mm × 66 mm, two-layer

2 System Overview

2.1 Block Diagram

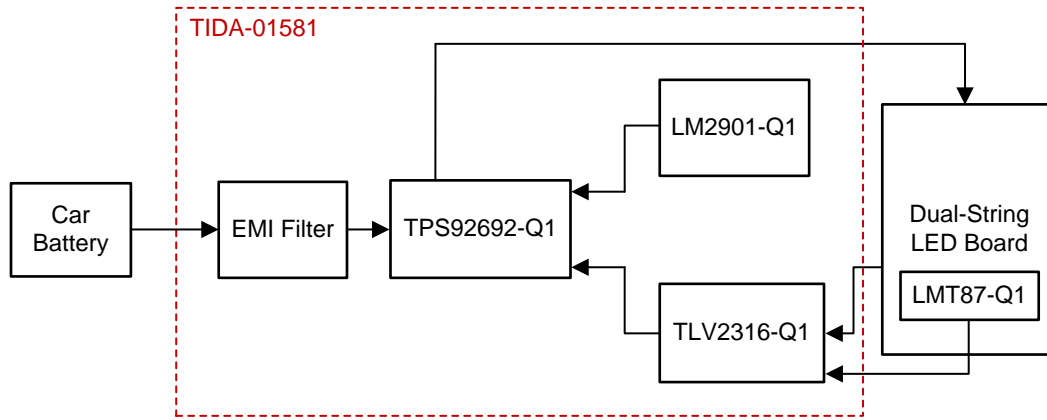

Copyright © 2018, Texas Instruments Incorporated

图 1. TIDA-01581 Block Diagram


2.2 Highlighted Products

2.2.1 TPS92692-Q1

The TPS92692-Q1 is a high-accuracy, multi-topology peak current mode controller designed for driving LEDs. The driver incorporates a rail-to-rail current amplifier to directly measure LED current. The driver can accept a wide input voltage from 4.5 V to 65 V and step-up or step-down the voltage based on the desired LED current. The user can enable spread-spectrum frequency modulation, which adds dither to the switching frequency, improving EMI performance. Additional features include analog dimming, integrated PWM generation, fault protection, current monitoring, and thermal protection. This device also has an accessible internal 5-V reference voltage which is used to power the other devices, and can source up to 30 mA.

Control the LED current with analog or PWM dimming. A linear analog dimming response can be achieved by varying the voltage of the high-impedance IADJ pin between 140 mV to 2.25 V. In this design, analog dimming is coupled with the LMT87-Q1 and an amplifier to achieve linear thermal foldback. Alternately, the average LED current can be controlled with the internal PWM generator. Accomplish this task by varying the voltage on the DIM/PWM pin between 1 V and 3 V, which sets the duty cycle of the PWM waveform.

图 2 shows the TPS92692-Q1 functional block diagram.

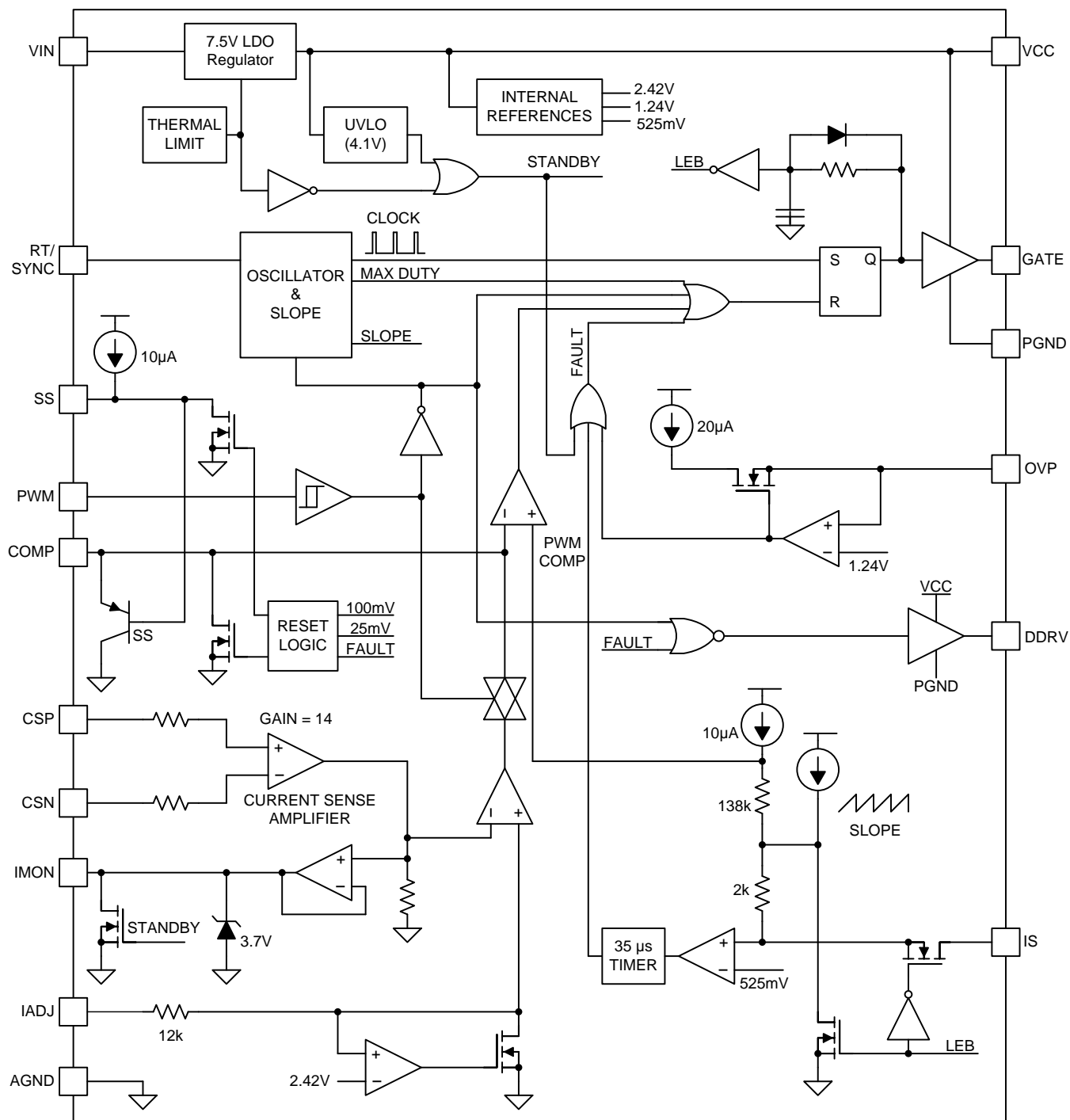

Copyright © 2017, Texas Instruments Incorporated

图 2. TPS92692-Q1 Block Diagram

2.2.2 LMT87-Q1

The LMT87-Q1 is a low-power, precision CMOS temperature sensor with a linear voltage output. The device emulates a negative temperature coefficient (NTC) thermistor by having an output voltage that is inversely proportional to temperature. Unlike a thermistor, the device has an exceptional linear response, which allows for linear thermal foldback in this design. The LMT87-Q1 resides on the printed-circuit board (PCB) containing the LED strings to sense the heat being generated by the LEDs, and reduce the current if necessary.

图 3 shows the LMT87-Q1 functional block diagram.


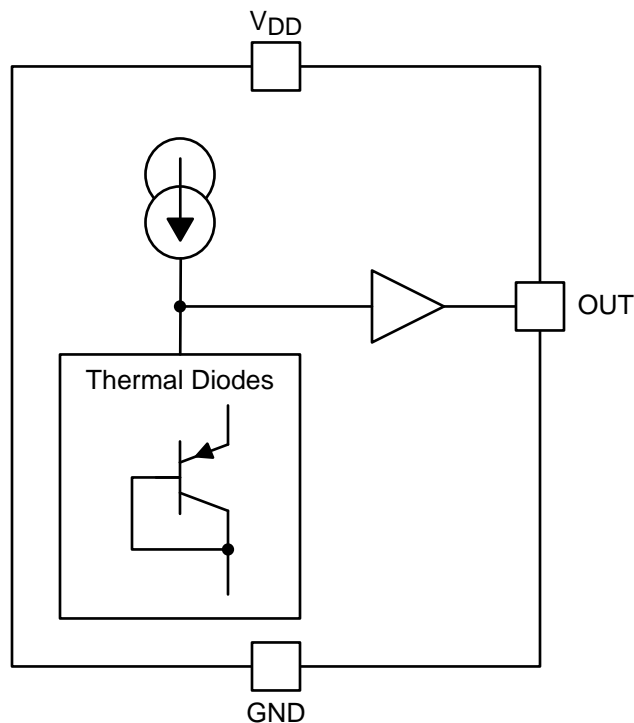


图 3. LMT87-Q1 Block Diagram

2.2.3 TLV2316-Q1

TLV2316-Q1 is a dual-channel, low-power, general-purpose op amp for cost-sensitive systems. The device features rail-to-rail input and output swings, low quiescent current, and a wide bandwidth of 10 MHz. In this design, the TLV2316-Q1 is coupled with a MOSFET to accurately balance the current between the two strings of LEDs. In addition, one channel is used for signal conditioning the temperature sensor and allows the designer to adjust the thermal foldback start point.

图 4 shows the TLV2316-Q1 functional block diagram.

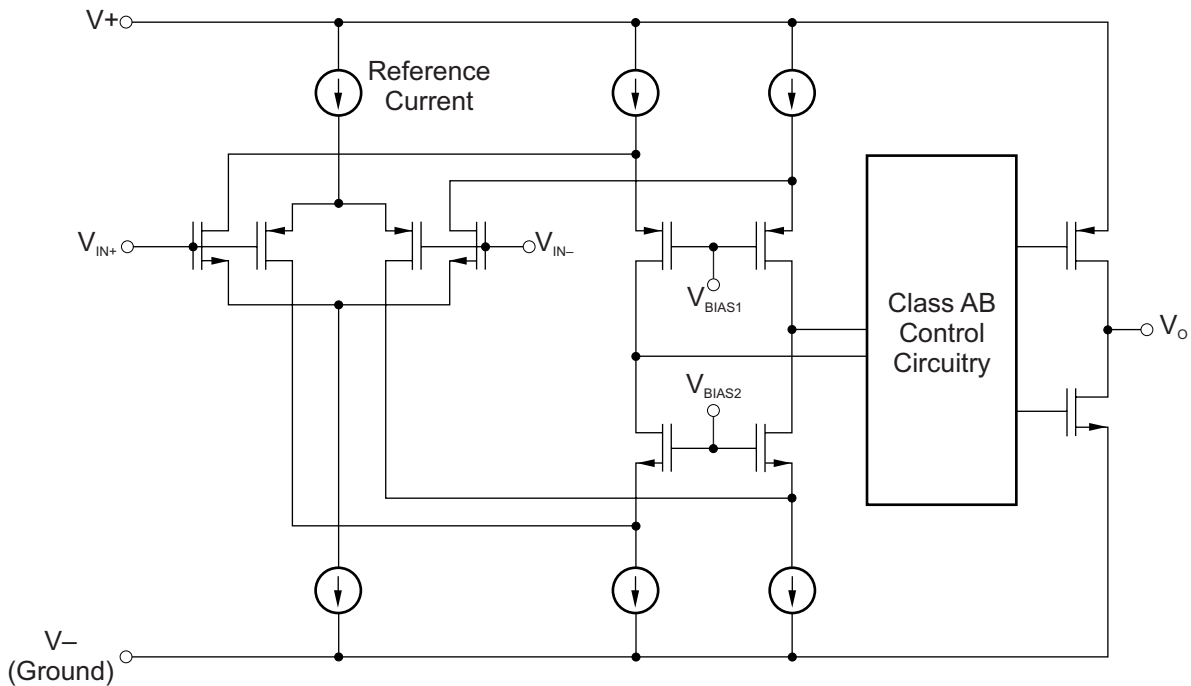


Copyright © 2016, Texas Instruments Incorporated

图 4. TLV2316-Q1 Block Diagram

2.2.4 LM2901-Q1

LM2901-Q1 is a quad-channel, high voltage comparator. In this reference design, one channel is used to current limit the reference string in the event of an open-circuit failure of the secondary string. The other channels can be used for fault detection or other functions.

图 5 shows the LM2901-Q1 functional block diagram.

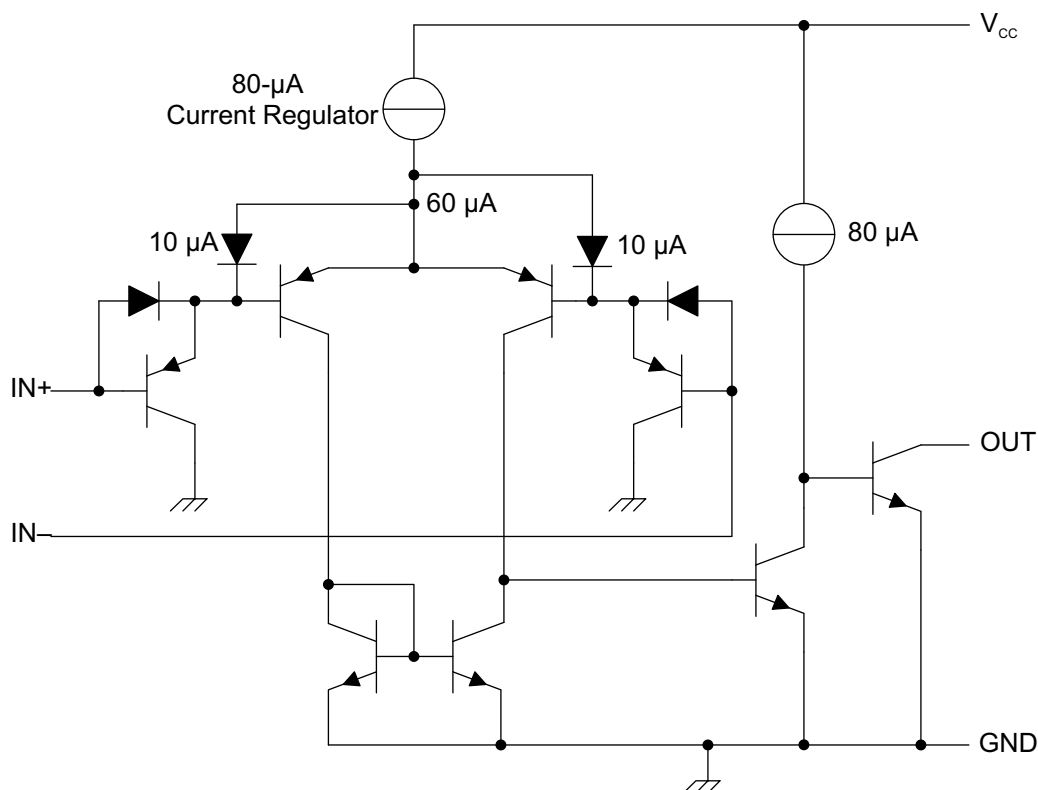

Copyright © 2016, Texas Instruments Incorporated

图 5. LM2901-Q1 Block Diagram

2.3 System Design Theory

2.3.1 Current Balancing

A requirement of this design is to use a single LED driver to drive two parallel strings of LEDs. If the LED strings are connected in parallel without a balancing circuit, the current in each string fluctuates due to variation in the LED forward voltage. The LED forward voltage can change with both temperature and manufacturing process variation. Use of an op-amp-based mirror accomplishes the current balancing in this design, as 图 6 shows. The low-side resistors measure the current in each string. The reference string is a string of LEDs with a low-side sense resistor that sets the current through the mirrored string. The mirrored string is in series with a low-side MOSFET that can control the amount of current flowing in the string. The op amp biases the MOSFET to force the voltage at the source to be equal to the voltage at the non-inverting terminal of the op amp. This biasing ensures that the current in each string is equal. A restriction on this circuit is that the forward voltage drop of the reference string must be greater than the mirrored string, which ensures that the MOSFET has sufficient headroom for correct biasing. The designer can accomplish this extra voltage drop in the reference string by implementing at least one more LED or a series resistor. This additional voltage drop is observable across the MOSFET in the mirrored string. Therefore, the MOSFET must dissipate the same amount of power dissipated by the additional LED or series resistor to ensure equal current in both strings. Although this requirement is restrictive, it allows for convenient fault detection that can detect a single LED that has been shorted or opened in either string.

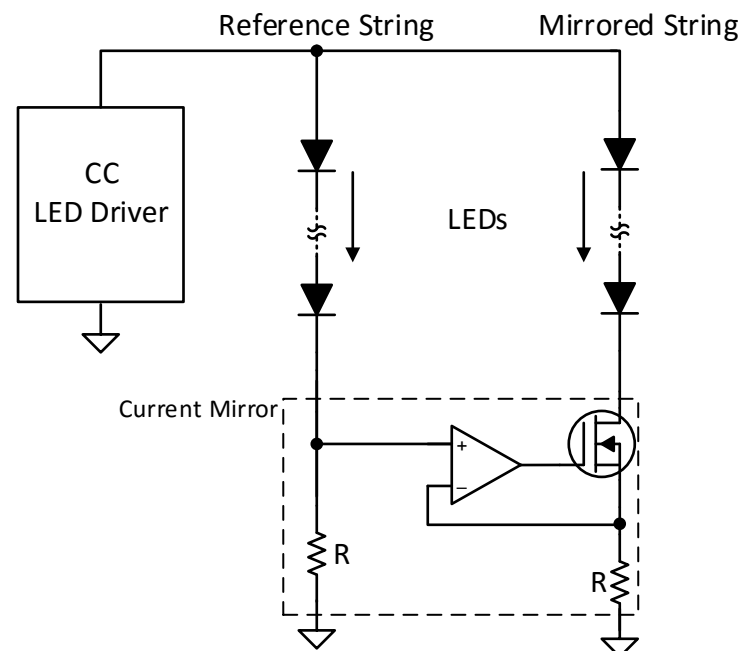


图 6. Block Diagram for Op-Amp-Based Current Mirror

2.3.2 Stability Analysis

Analyze the stability of this op-amp-based circuit and then provide any necessary compensation to achieve a stable design. Unstable designs may have unbalanced currents and undesired transient behavior. An effective way to perform this analysis is by using the TINA-TI™ SPICE simulation tool for AC loop-gain analysis.

To perform an AC loop-gain analysis, the user must first break the feedback loop and inject a small signal AC source. However, simply breaking the feedback path does not provide the correct DC operating point and causes the op amp to saturate to one rail. Instead, this reference design implements a circuit as shown in 图 7. The large capacitance of C1 allows AC to pass, while the large inductance of L1 blocks AC and allows DC to pass. This provides a correct DC bias point to the op-amp circuit while still allowing the designer to inject a small signal source. In this circuit, VF1 represents the loop gain and indicates stability. For more information on op-amp AC analysis in TINA-TI, see the section regarding Stability in the [TI Precision Labs - Op Amps](#) training resource.

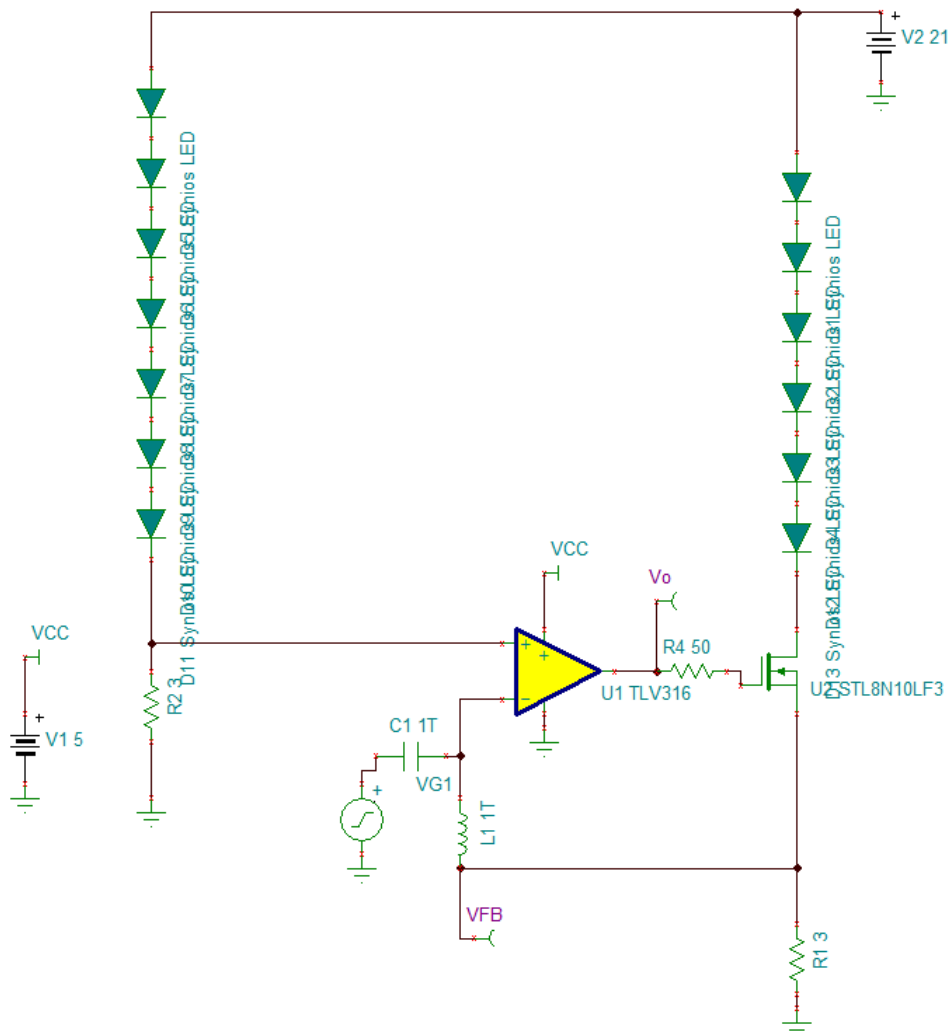


图 7. TINA-TI™ Circuit for AC Analysis

图 8 显示了 AC 扫频的结果。相位裕度约为 8° ，且闭环增益大于 20 dB，因此系统不稳定。需要额外的补偿来实现稳定的设计。

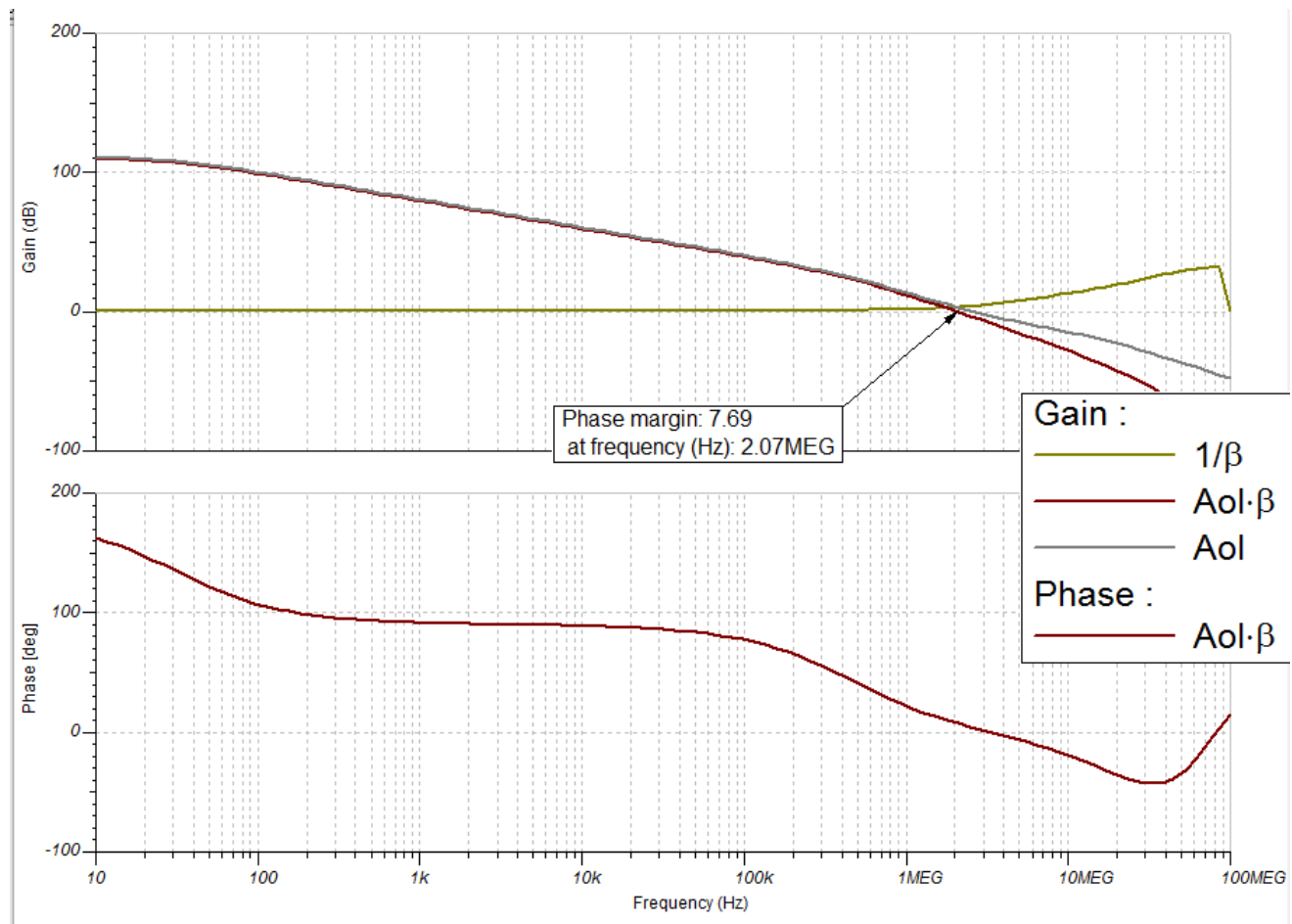


图 8. TINA-TI™ AC Sweep Showing Circuit Instability

图 9 显示了带有补偿的电路。R3、R5 和 C2 形成噪声增益补偿网络，将环路增益相位在交叉频率处推高。图 10 显示了添加补偿元件后的 AC 扫描。相位裕度约为 49°。噪声增益补偿在 1/beta 曲线上添加了一个零极点对，并增加了高频增益。这种补偿导致 Aol 和 1/beta 曲线在较低频率处相交，并以每十年 20-dB 的稳定速率收敛。

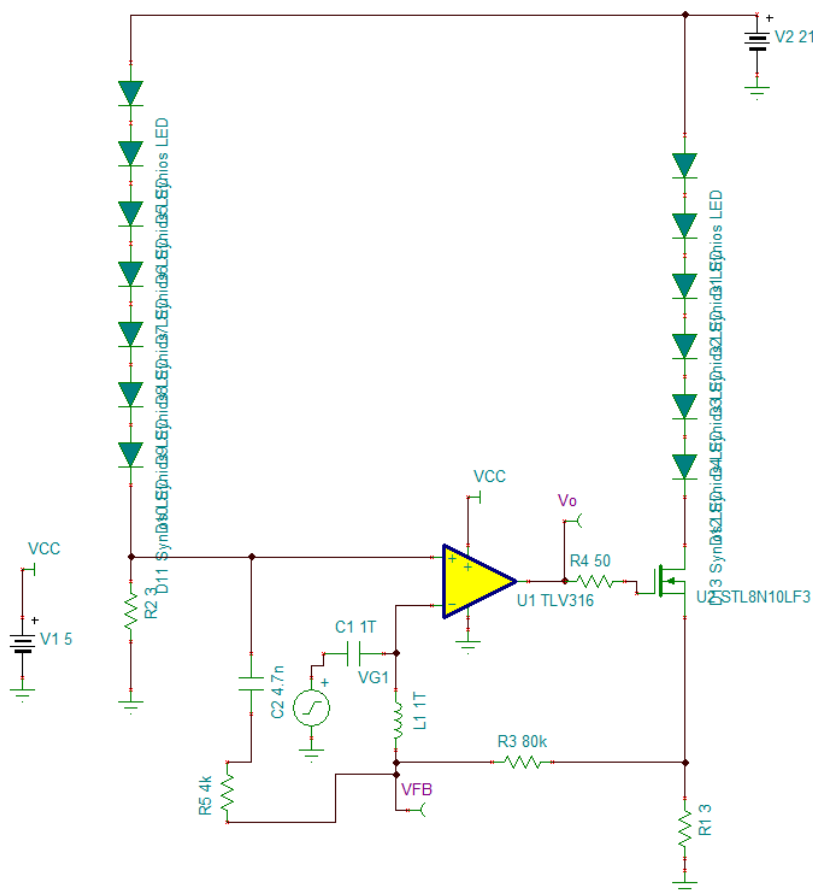


图 9. TINA-TI™ Compensated Current Mirror Circuit

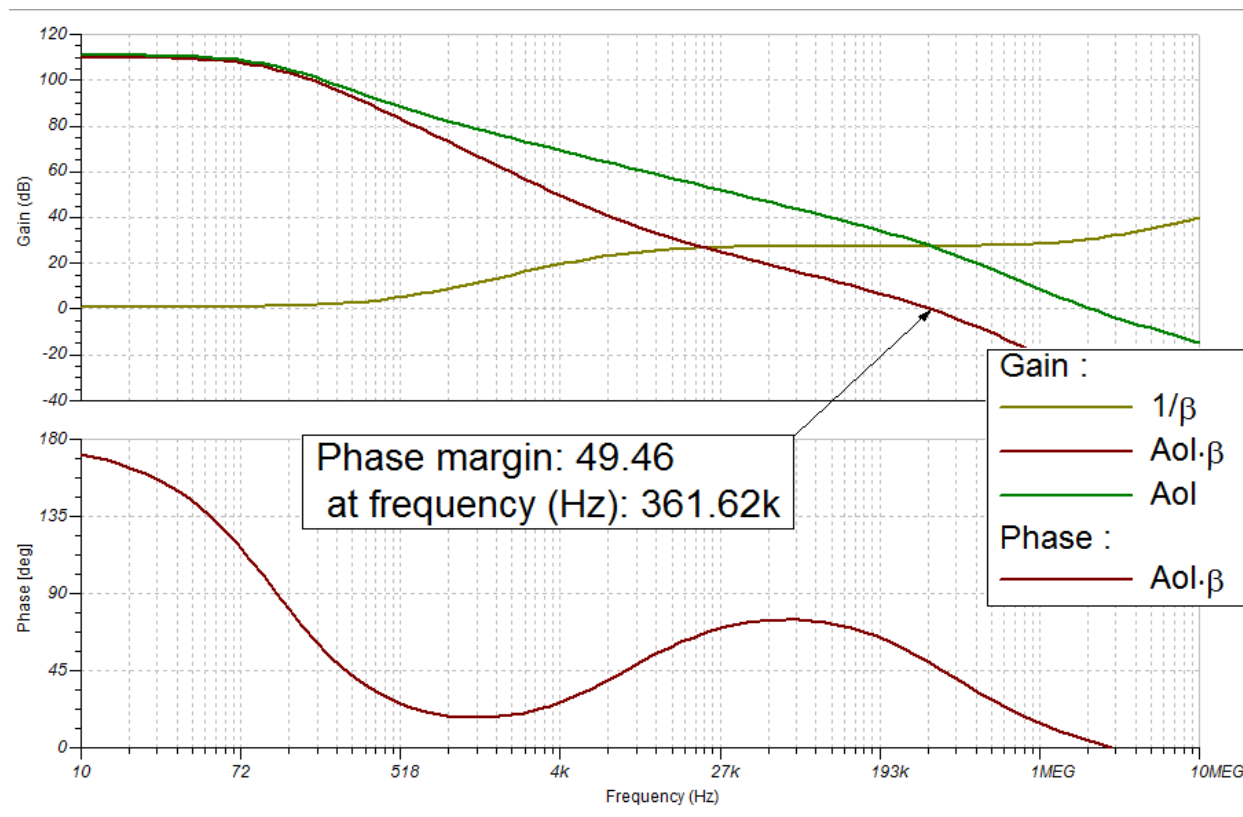


图 10. TINA-TI™ AC Sweep of Compensated Circuit

2.3.3 Position and DRL Modes

This design features two operating modes for setting the brightness of the LEDs: Position and DRL. In DRL mode, the LEDs operate at full brightness and the current is limited by the internal current sense amplifier connected to the current sense resistor R_{CS} . 公式 1 sets the LED current. A value of $0.43\ \Omega$ has been chosen to set the total current to approximately 400 mA, or 200 mA per string.

$$I_{LED} = 170.7 \frac{mV}{R_{CS}} \quad (1)$$

In Position mode, the LEDs are dimmed using the TPS92692 internal PWM generator. A voltage between 1 V and 3 V sets the PWM duty cycle between 0% and 100%, respectively. In this design, the duty cycle is set to 8% after enabling the Position mode. 图 11 shows the components used to set up the two modes. In Position mode, the resistor divider formed by R16 and R19 sets the voltage at the DIM/PWM pin. If connecting the DRL pin instead, the VBAT2 connection that sets the duty cycle to 100% overrides the voltage at this pin. R18 and R19 set the voltage.

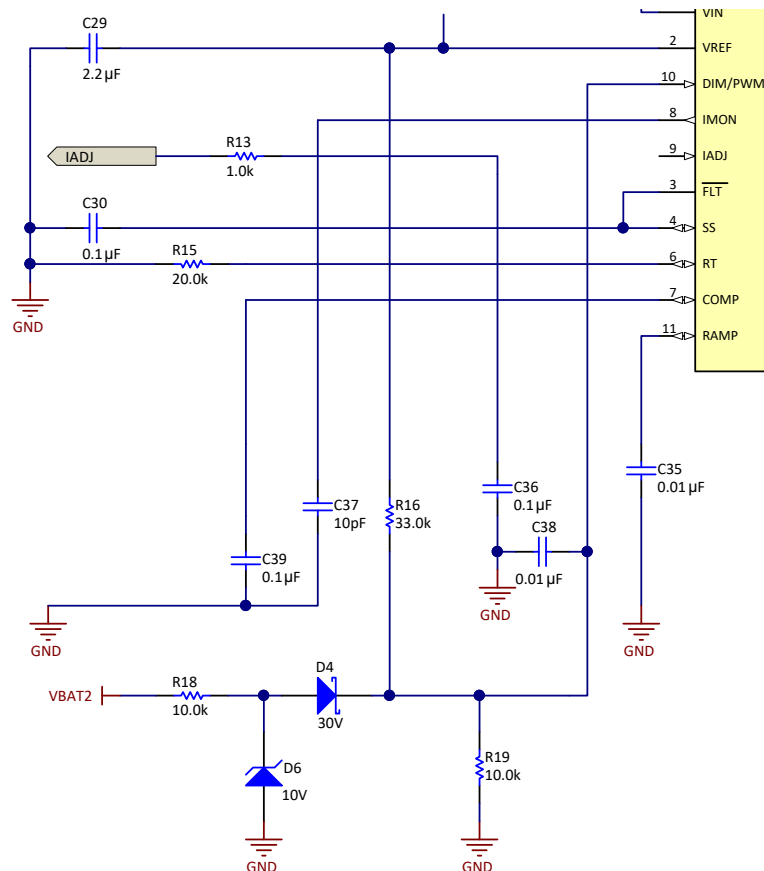


图 11. 'DRL' and 'Position' Schematic

2.3.4 Reference String Current Limit

Because the current-balancing circuit relies on the reference string, if the mirrored string fails to open, then all of the current is free to flow through the reference string. The driver monitors the current it delivers and increases the voltage to push the full current through one string, which doubles the intended current through the LEDs. This high current can generate heat and pose a hazard if the LEDs are not rated for the current.

To account for this hazard, use a simple comparator circuit to monitor the current in the reference string. If the current rises above a threshold, the comparator turns on a field-effect transistor (FET) and pulls down the IADJ pin. This process repeats when the current falls back below the threshold, which causes a flickering. The purpose is not to maintain operation of the LEDs, but to prevent an overheating condition. The fault detection circuit will indicate if the mirrored string has failed. 图 12 shows the current-limiting circuit. V_{ILM} is the voltage at which the current must be limited. Determine this voltage by using $V_{ILM} = I_{LM} \times R$ where I_{LM} is set at or below the maximum continuous LED current. In this case, the limit is set to 300 mA, which is the maximum current for these LEDs. If the LEDs used can handle double the intended current, implementing this circuit may not be necessary.

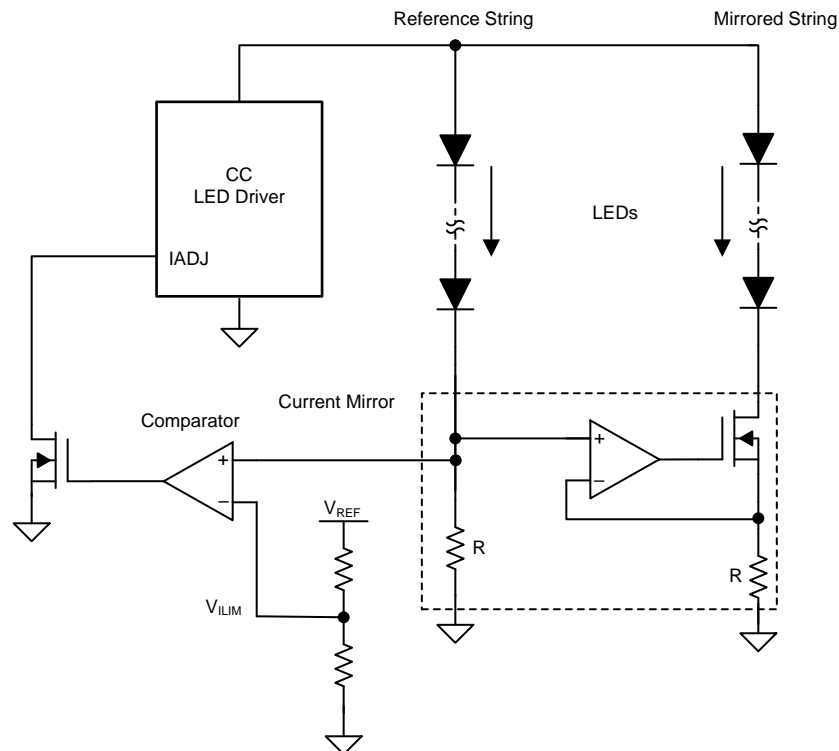


图 12. Reference String Current Limit

2.3.5 Thermal Foldback

This design includes an adjustable thermal foldback that reduces the LED current as the LED board temperature increases. This foldback prevents the LEDs from overheating. Achieve this thermal foldback by using the LMT87-Q1 temperature sensor to adjust the voltage on the analog dimming pin (IADJ). Use a non-inverting amplifier to interface the temperature sensor with the LED driver. 图 13 shows the amplifier schematic. J4 connects directly to the temperature sensor on the LED PCB.

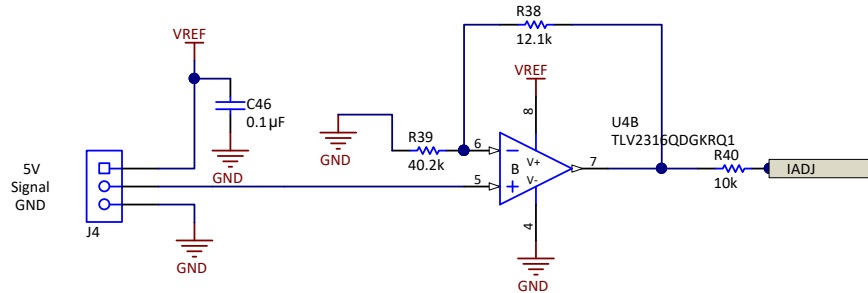


图 13. Thermal Foldback Amplifier Schematic

To set the led current between 0% and 100%, modulate the analog dimming pin (IADJ) between 140 mV to 2.25 V. The LMT87-Q1 varies the output voltage from 3.25 V to 0.5 V over a temperature range of -50°C to 150°C . Use the non-inverting amplifier to adjust the temperature at which the foldback begins, which is based on the gain value. 公式 2 shows the output voltage of the LMT87-Q1 as a function of temperature.

$$V_{\text{TEMP}} (\text{mV}) = 2230.8 \text{ mV} - \left(13.582 \frac{\text{mV}}{^{\circ}\text{C}} (T - 30^{\circ}\text{C}) \right) - \left(0.00433 \frac{\text{mV}}{^{\circ}\text{C}^2} (T - 30^{\circ}\text{C})^2 \right) \quad (2)$$

图 14 shows the voltage at the output of the LMT87-Q1 device as well as the output amplified by a gain of 1.3, which is the voltage at the IADJ pin. The black horizontal line shows where the thermal foldback begins for each voltage curve. Higher gains cause the thermal foldback to begin at a higher temperature.

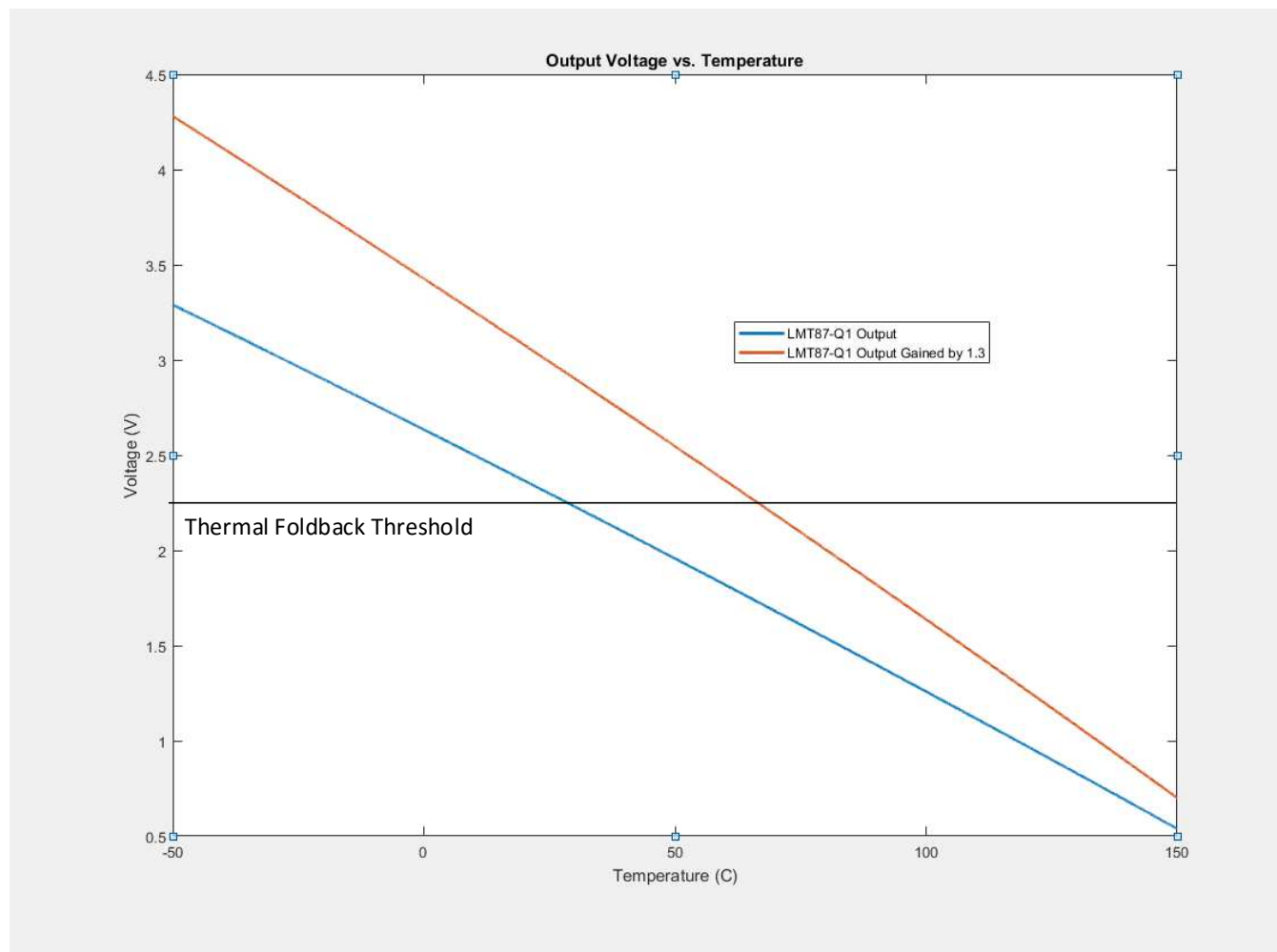


图 14. LMT87-Q1 Output Voltage and Amplified Output Voltage

The result as given by 图 15 is produced by multiplying the LMT87 output voltage by the chosen amplifier gain and calculating the LED current output . The gain in this design is set to 1.3.

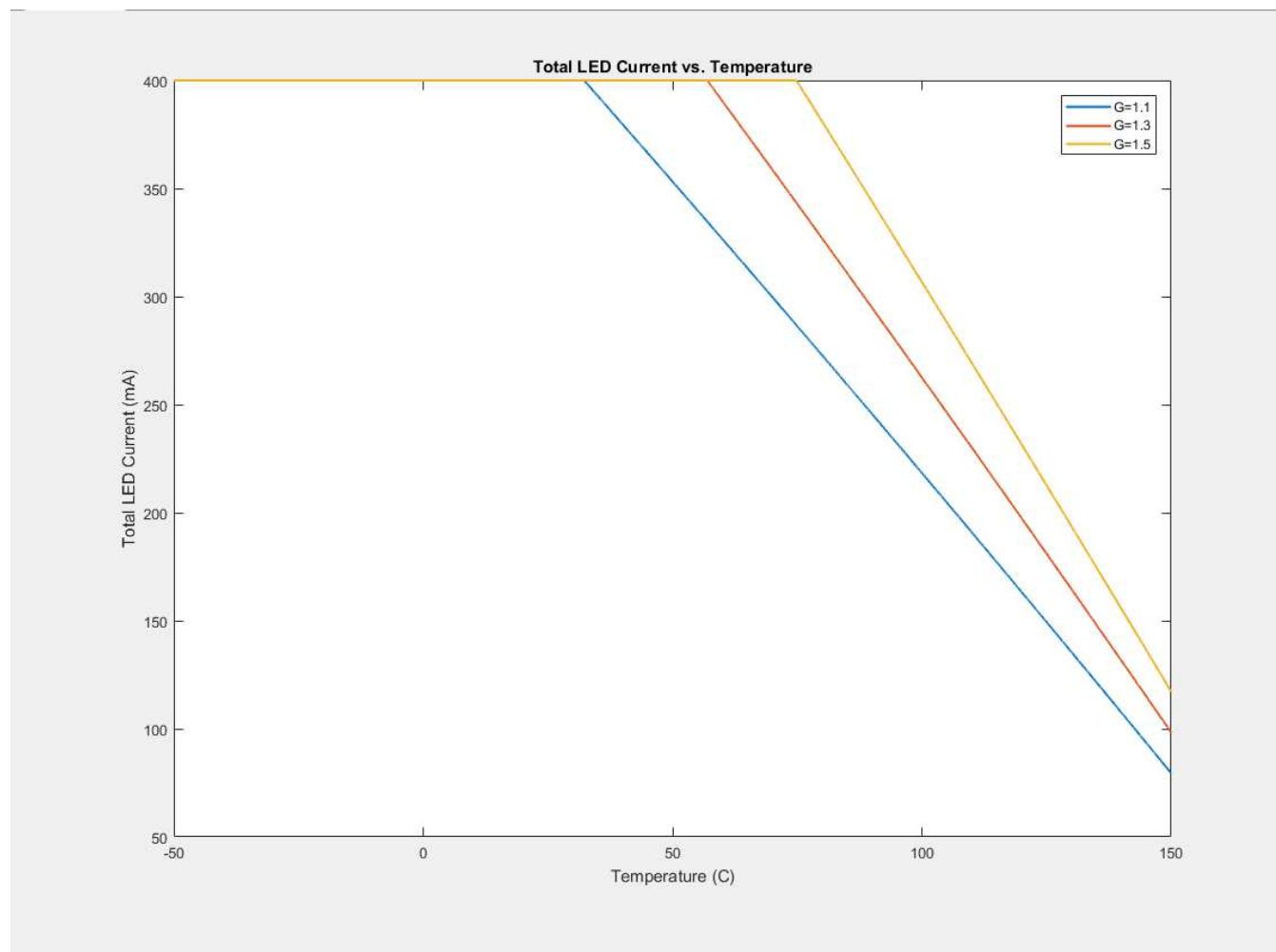


图 15. Thermal Foldback Response for Different Amplifier Gains

3 Hardware, Software, Testing Requirements, and Test Results

3.1 Required Hardware and Software

3.1.1 Hardware

The required hardware consists of the LED driver board and an LED daughterboard which contains the LEDs and temperature sensor. The LEDs used on the LED board for testing are Osram Synios P2720. The LED+ connection on the driver board must be connected to the positive of both LED strings. The negative of the strings must be connected REF– and MIR– connections on the driver board. The temperature sensor must be properly connected to the 5V, GND, and Signal connections of the driver board. 图 16 shows the proper way to connect the LED board and LED driver board.

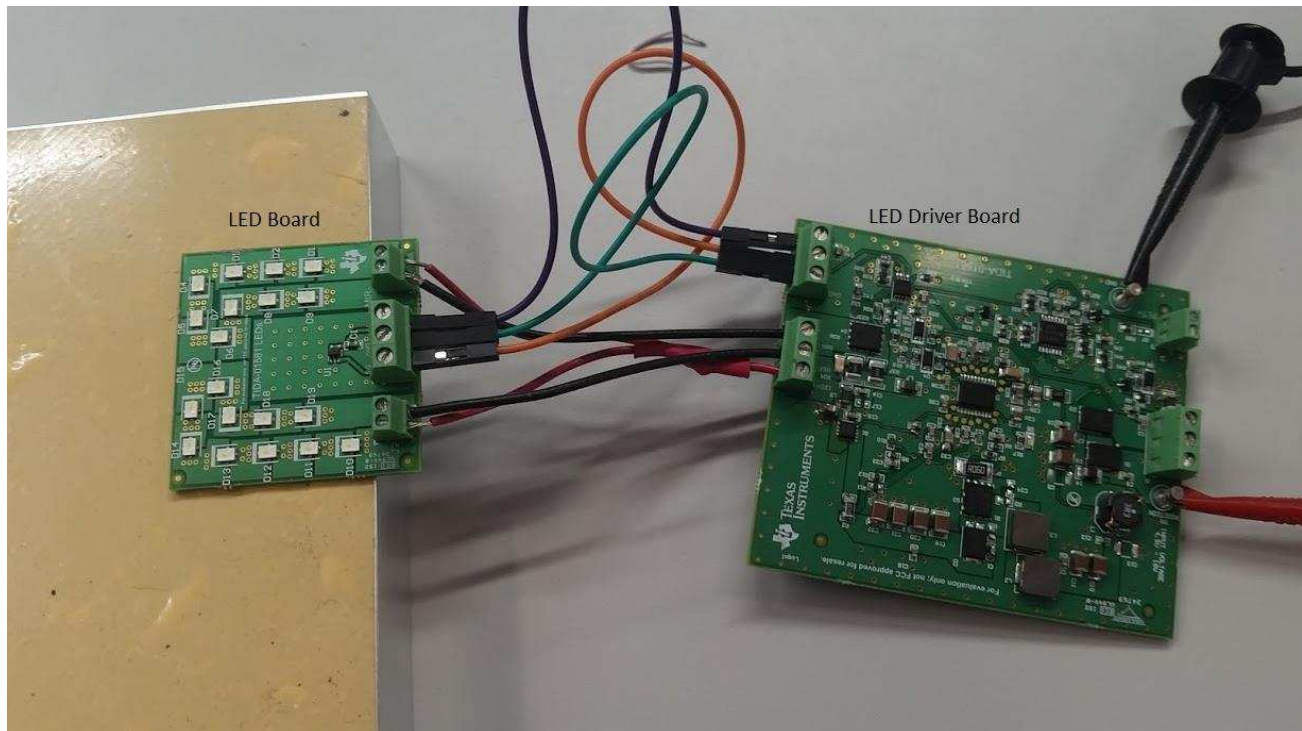


图 16. Driver Board and LED Board Connection

3.2 Testing and Results

3.2.1 Current Balance Accuracy

After connecting the LED driver board to the LED board, as specified in [Hardware](#), a 14-V DC was applied to the DRL connection. Current probes were used to measure the current in each string during start-up. [图 17](#) shows the current in each string during start-up. This result shows that the current-balancing circuit accurately controls the current through both strings. The current in each string settles smoothly to 200 mA.

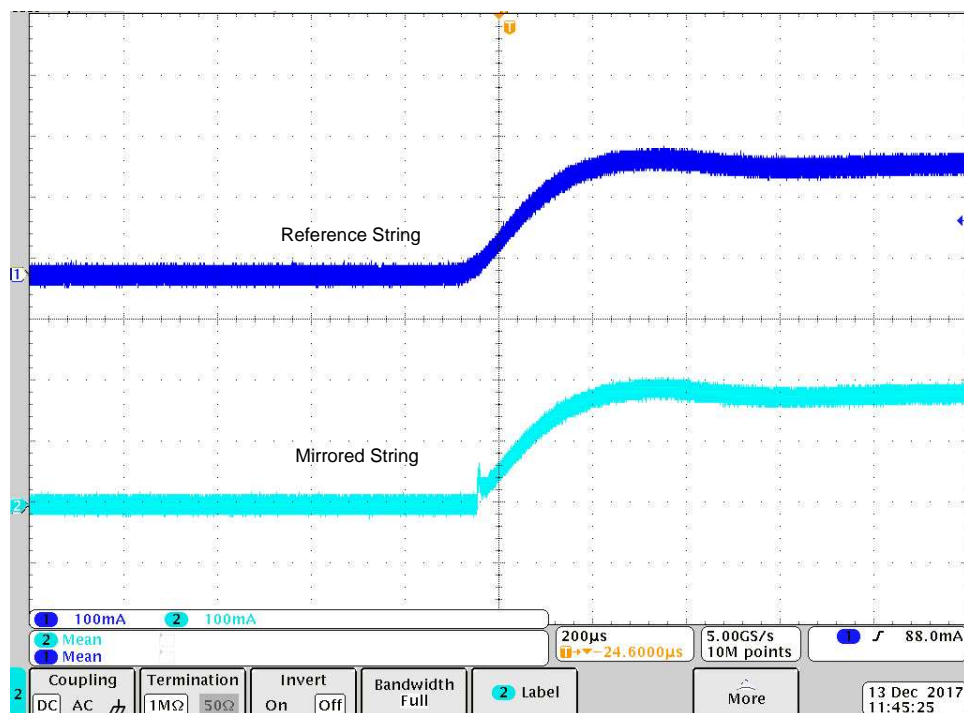


图 17. Turnon Current in Each String in 'DRL' Mode

The steady-state current in DRL mode was also measured in both strings to indicate the accuracy balance, which 图 18 shows. This result also shows a difference of 2 mA between the strings.

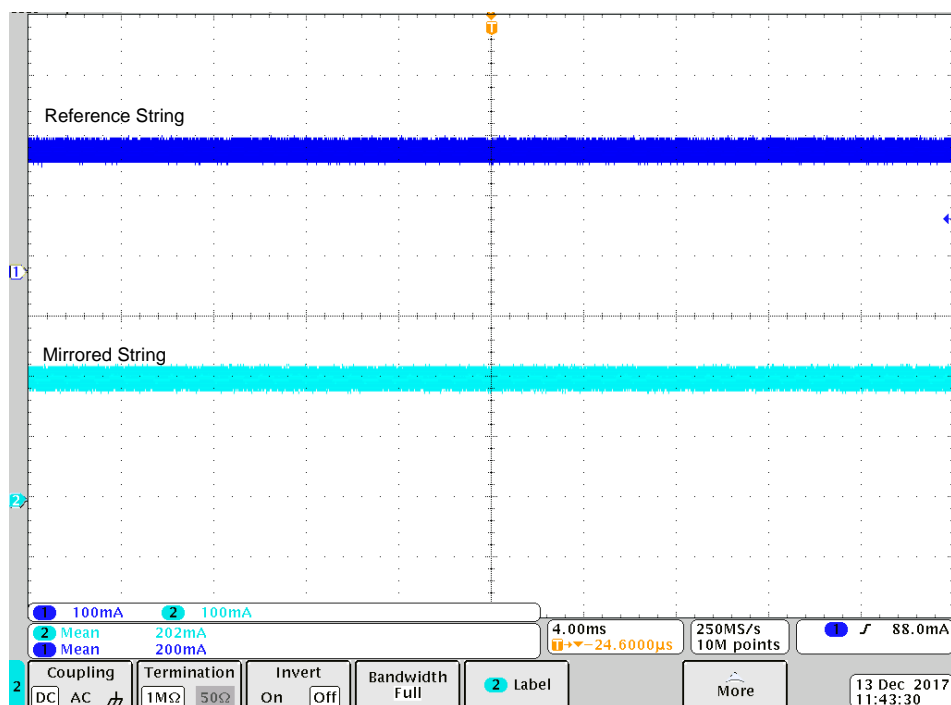


图 18. Steady-State Current Oscilloscope Capture in 'DRL' Mode

The average current in each string was also measured with two ammeters in DRL mode. This result is more accurate than the oscilloscope capture. 图 19 shows a photo of the results. The current difference between the strings is less than 1%.

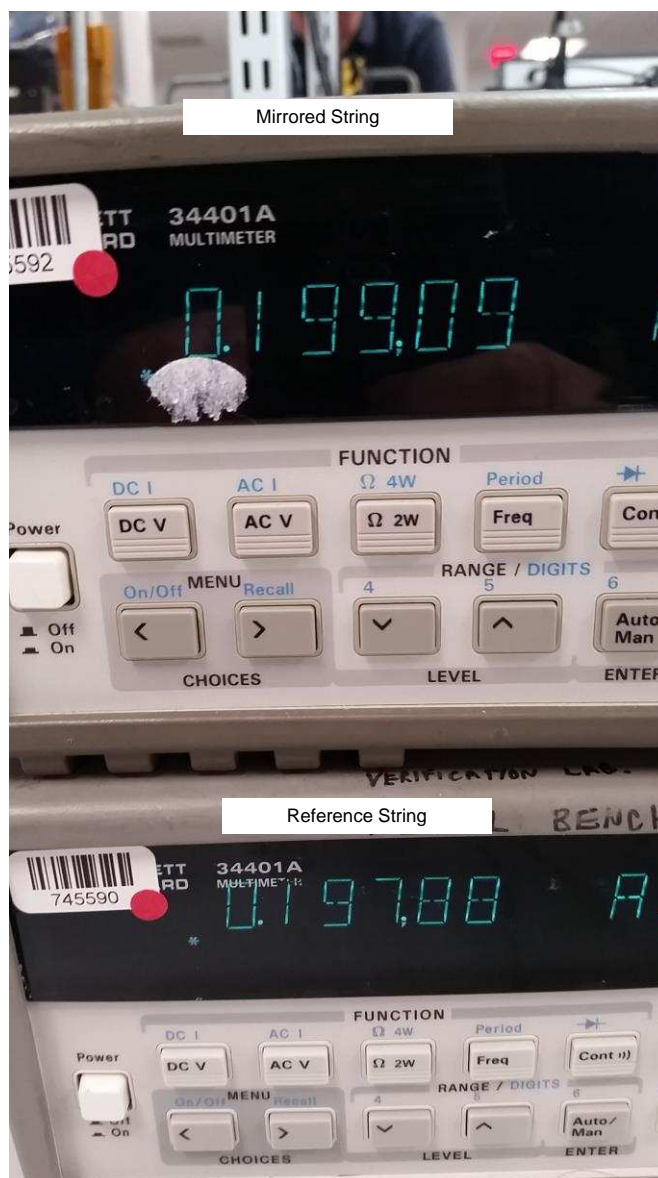


图 19. Ammeter Measurement of Average String Current in 'DRL' Mode

The ammeter measurement was repeated for the Position mode to compare the average currents between the two strings during PWM. 图 20 shows an image of this result. The current difference between the two strings is less than 1%.

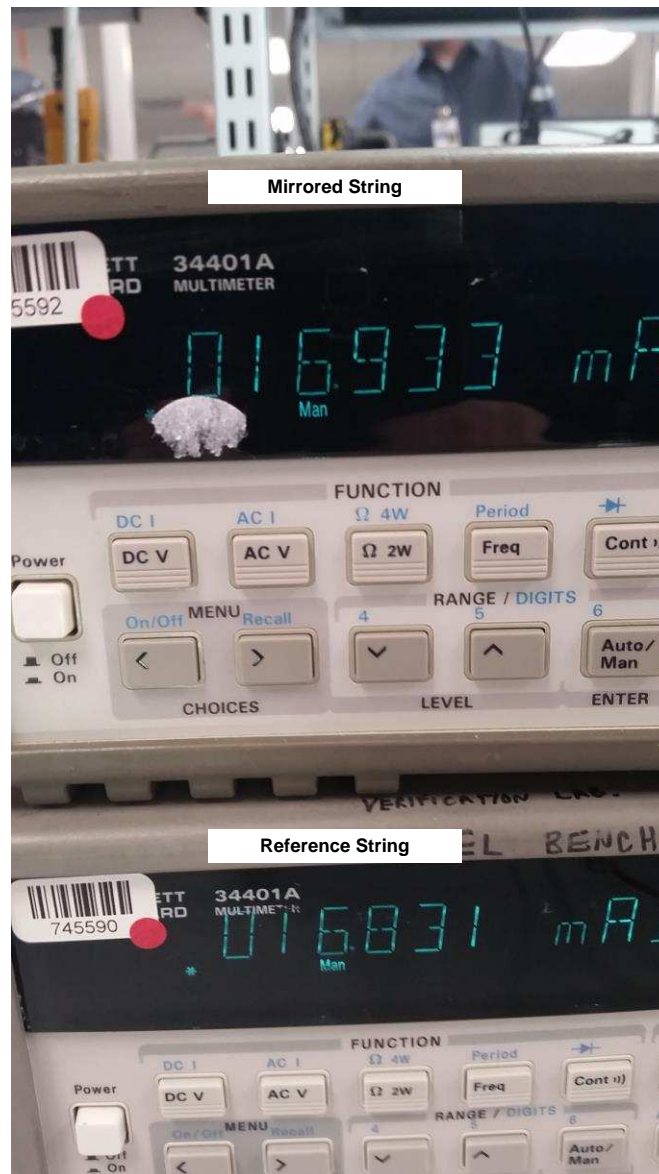


图 20. Ammeter Measurement of Average String Current in 'Position' Mode

图 21 shows the PWM transient. Channel 1 is the reference current and channel 2 is the mirrored current. This result shows that the circuit accurately balances the current during PWM dimming. This result confirms an equal brightness of the strings when using the Position mode.

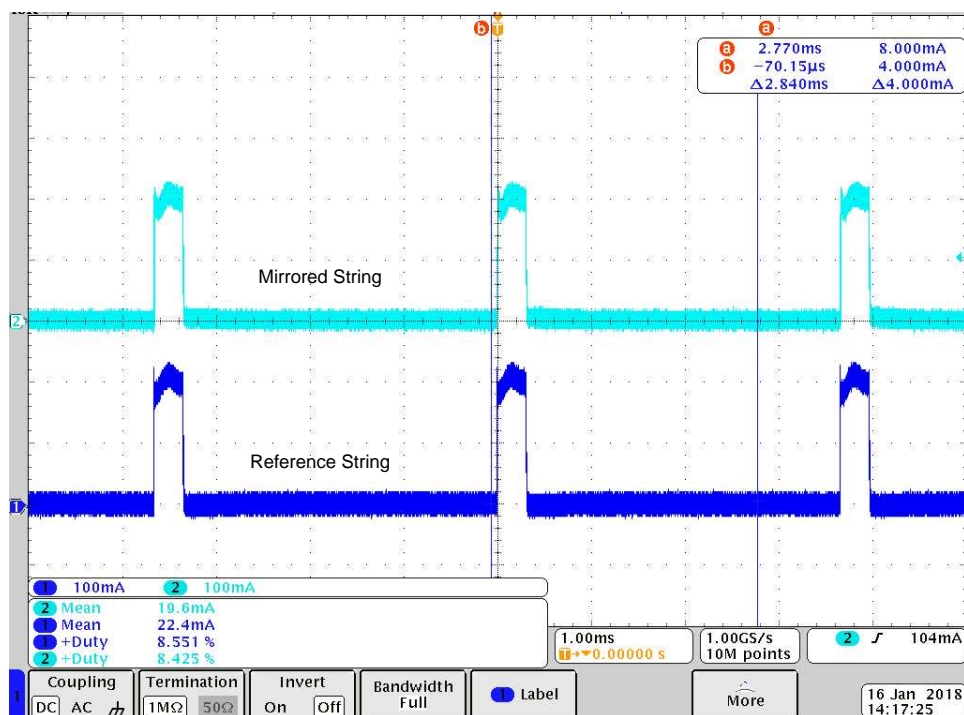


图 21. Reference and Mirrored-Current PWM Transient

3.2.2 Reference String Current Limit

The reference string current limit was tested by disconnecting the mirrored string of LEDs while the power is connected to the DRL input. 图 22 shows the current limit waveform. Channel 2 is the current flowing through the reference string of LEDs and channel 3 is the voltage of IADJ. When the current reaches 300 mA, the current limit circuit pulls IADJ to ground. This cycle repeats every 36 ms based on the LED driver fault timer because the device is in hiccup mode. The LEDs flicker in this condition.

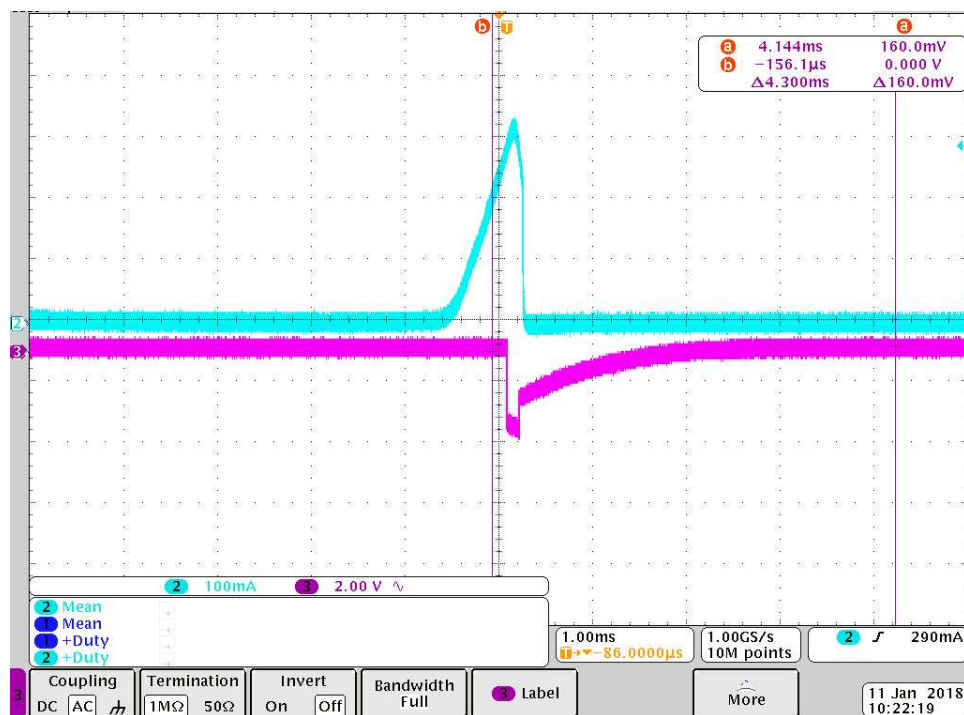


图 22. Waveform of Reference String Current Limit

3.2.3 Thermal Foldback Response

The LED board was heated from 20°C to 125°C and the current was measured. 图 23 shows both the calculated response and measured response. The measured response accurately corresponds with the calculated response described in 节 2.3.5.

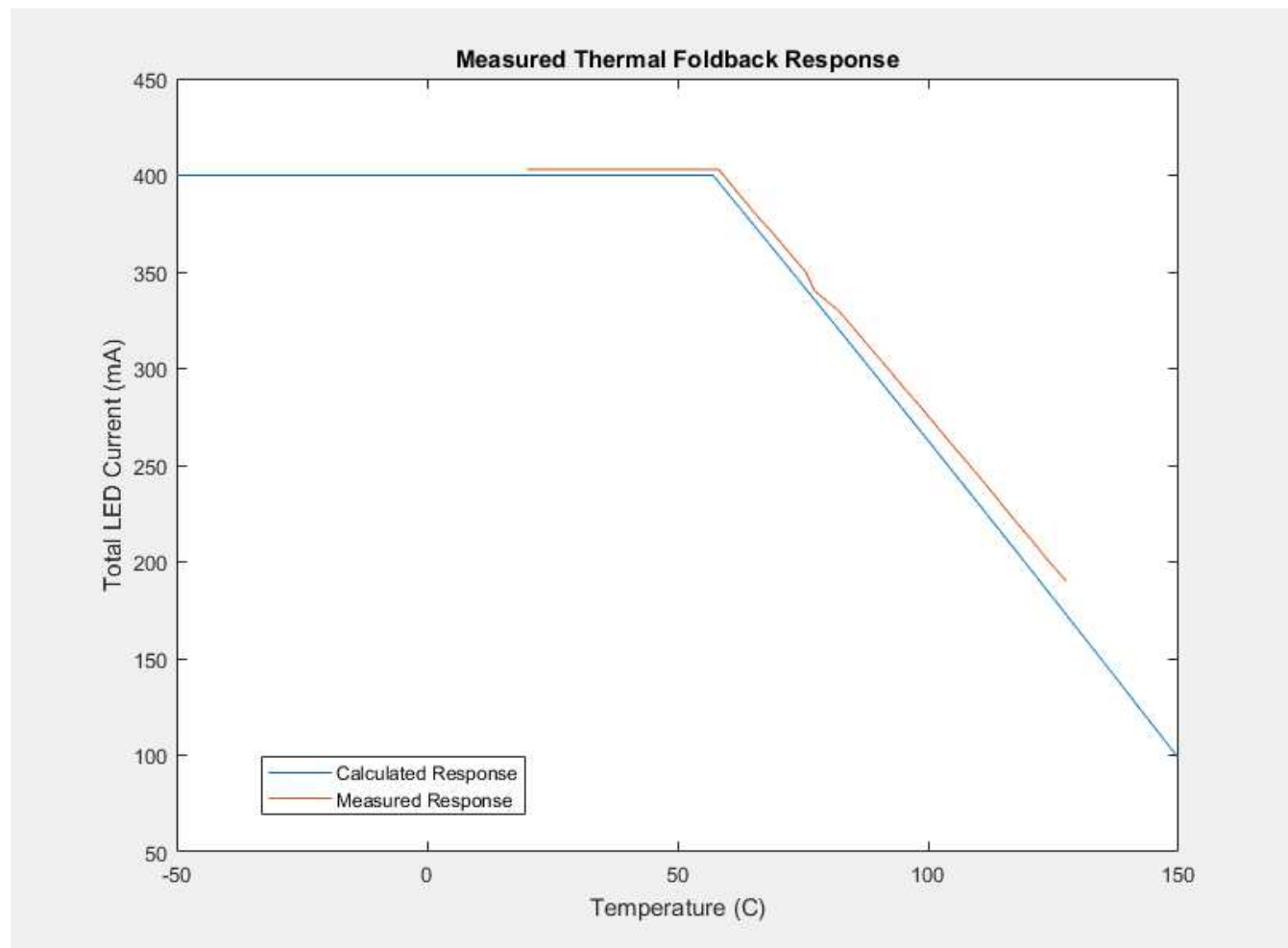


图 23. Calculated and Measured Thermal Foldback Response

3.2.4 Thermal Image

图 24 shows a thermal image of the reference design in DRL mode operation at room temperature with the board driving the LEDs at 12 W. The recorded maximum temperature is 50°C. The reverse polarity protection diode, the switched-mode power-supply (SMPS) switching MOSFET, and the current balancing MOSFET have the highest temperature regions.

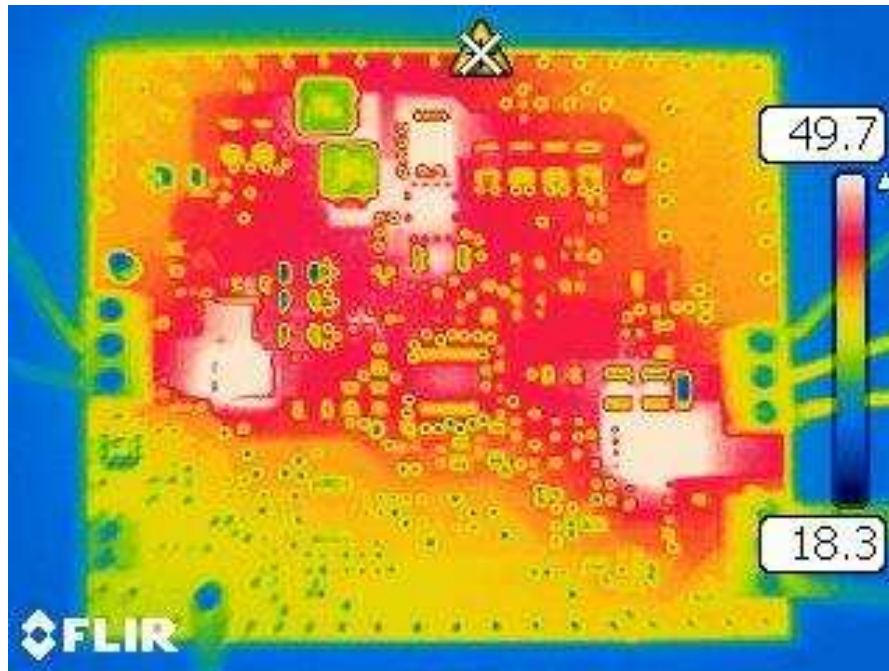


图 24. Thermal Image of TIDA-01581

3.2.5 EMI Testing Unshielded Inductors

The reference design was tested against CISPR25 Class-5 limits for both conducted and radiated emissions. The board was tested in DRL mode in which it drove 19 LEDs at a current of 200 mA and power of 12 W.

Before EMI testing, the switch node was examined for ringing. In 图 25, the switch node is the node connected to the output of the inductor (L3), the anode of the rectification diode (D2), and the switching MOSFET Q2. Switch node ringing has a significant negative impact on EMI results and must be addressed before running EMI tests. 图 26 shows the switch node waveform measured directly from the inductor output to ground using the tip and barrel method. Note the significant ringing on the rising edge of the waveform.

A snubber circuit across the rectifying diode was used to eliminate this ringing before EMI testing. 图 25 (R1,C1) shows this snubber circuit. The actual values used were $R1 = 15\ \Omega$ and $C1 = 470\ \text{pF}$. The snubber effectively dissipates high-frequency AC signals such as the ringing waveform. For additional details on using an RC snubber to minimize ringing in a boost converter design, see [Minimizing Ringing at the Switch Node of a Boost Converter](#). A gate resistor was also added to the switching FET to slow the rise time, which results in a small decrease in efficiency but improves EMI performance.

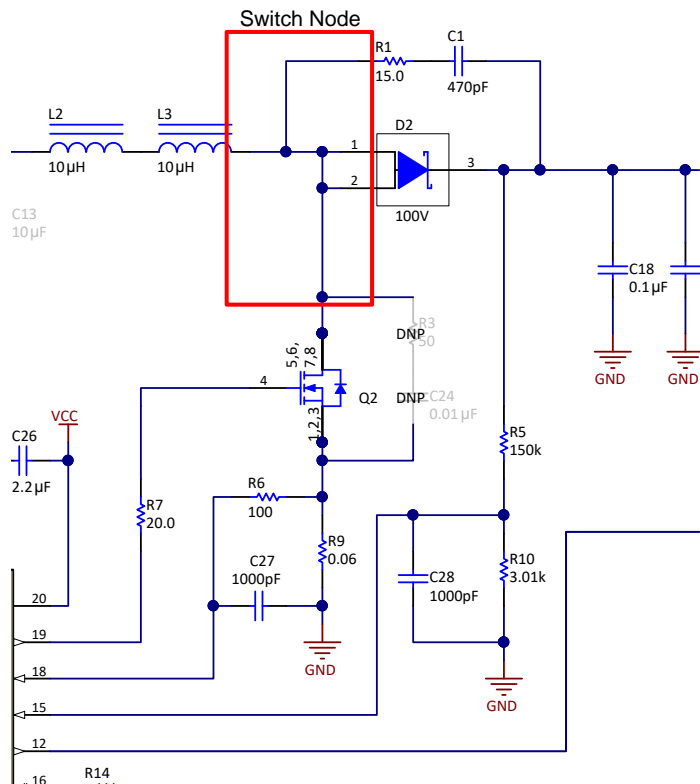


图 25. Snubber Circuit (R1,C1)

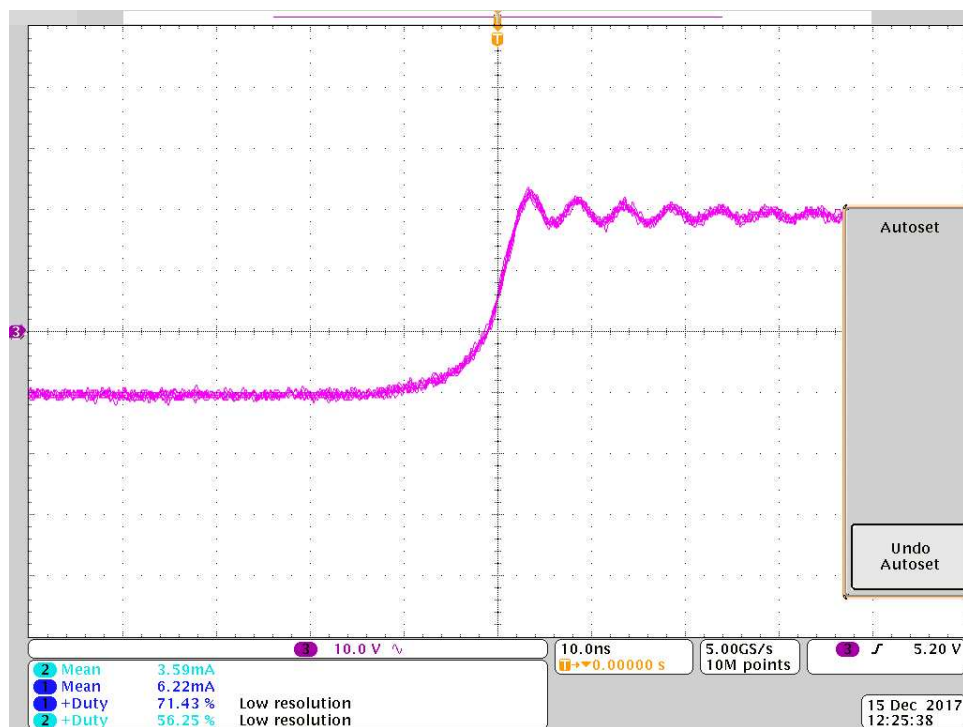


图 26. Switch Node Waveform

EMI tests were performed on the board with both unshielded and shielded inductors. 图 27 shows an image of the board with unshielded inductors (Vishay IHLP-2525BD-A1). In this design, two smaller inductors in series were used instead of one large inductor. In this case, two 10-uH were placed in series instead of a single 22 μ H. The reason for doing this is because smaller components perform better in vibration and physical stress testing. The smaller inductors are less likely to have an issue, such as breaking off the board or breaking a solder joint during stress tests.

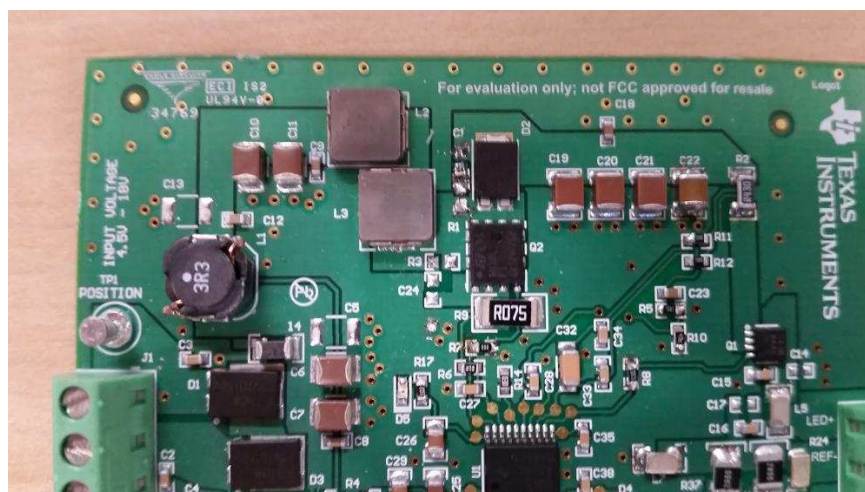


图 27. TIDA-01581 With Unshielded Inductors (Vishay IHLP-2525BD-A1)

The EMI test was set up according to the CISPR25 standard with Class 5 limits. 图 28 through 图 33 show the results of the EMI testing.

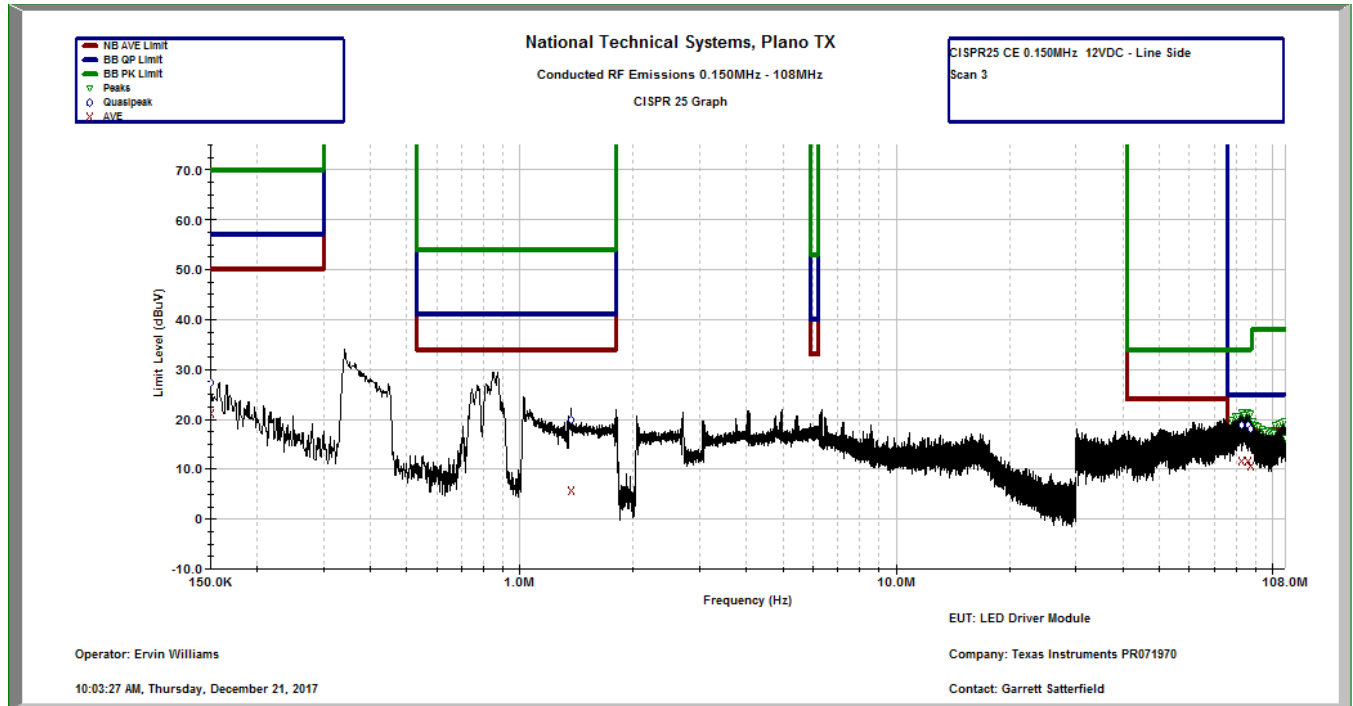


图 28. CISPR25 Class-5 Conducted Emissions (Line)

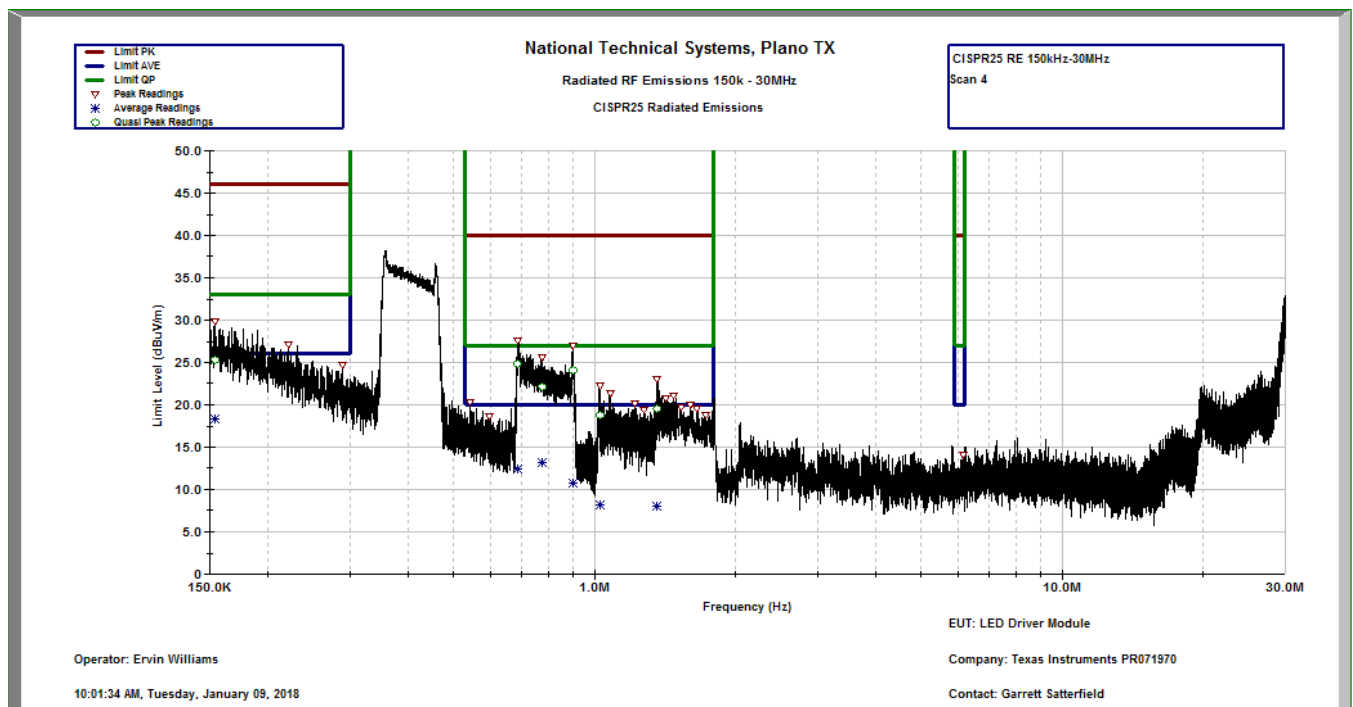


图 29. CISPR25 Class-5 Radiated Emissions: 150 KHz to 30 MHz

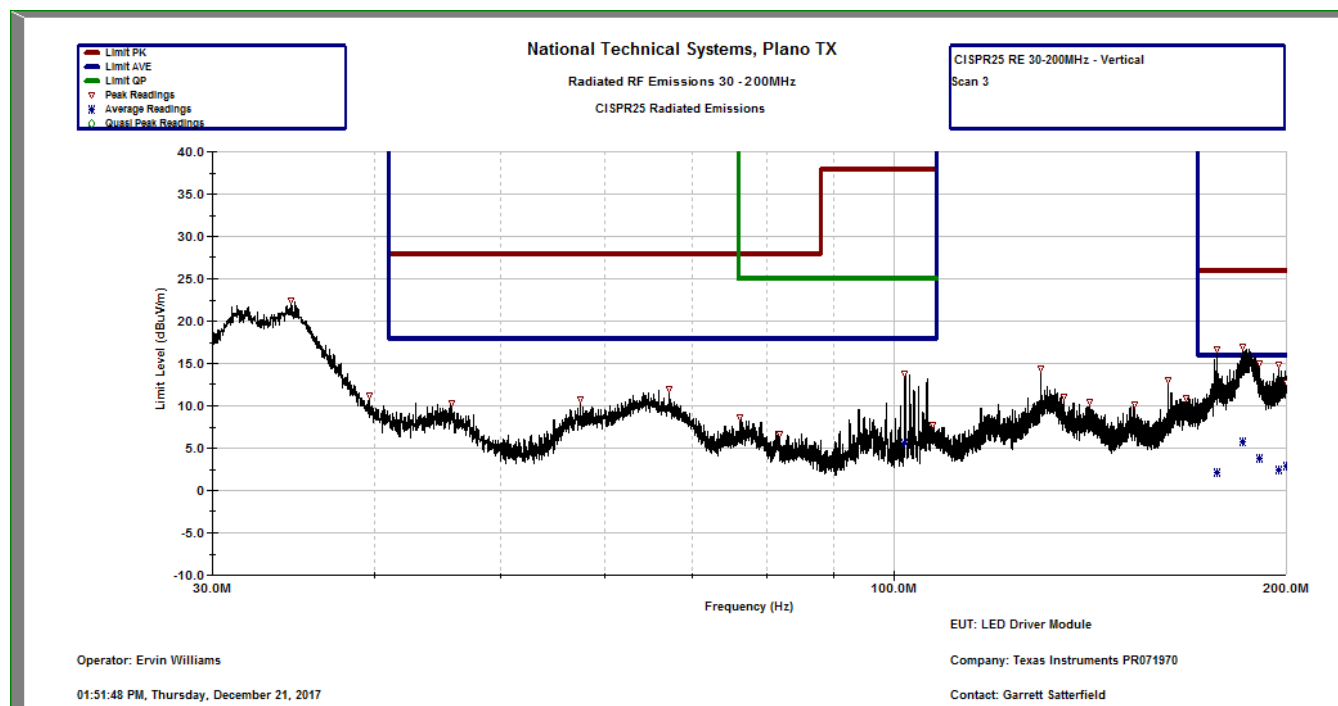


图 30. CISPR25 Class-5 Radiated Emissions: 30 MHz to 200 MHz (Vertical)

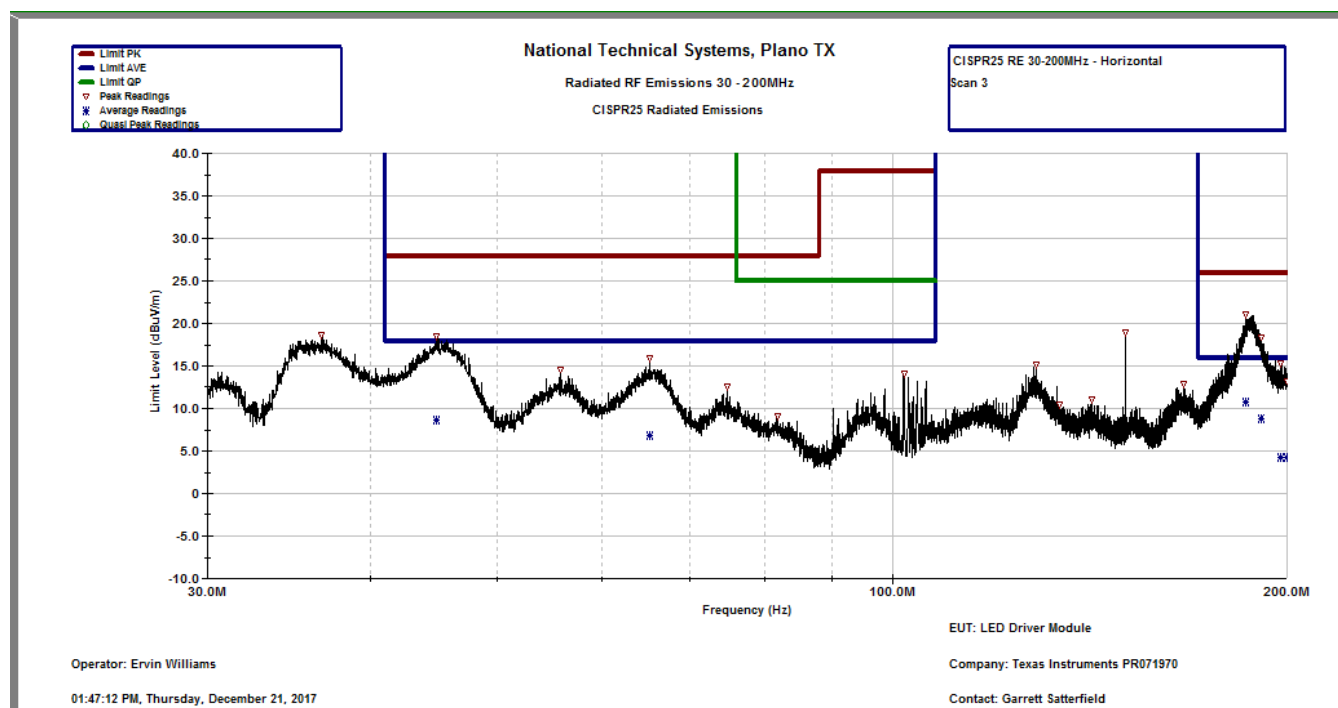


图 31. CISPR25 Class-5 Radiated Emissions: 30 MHz to 200 MHz (Horizontal)

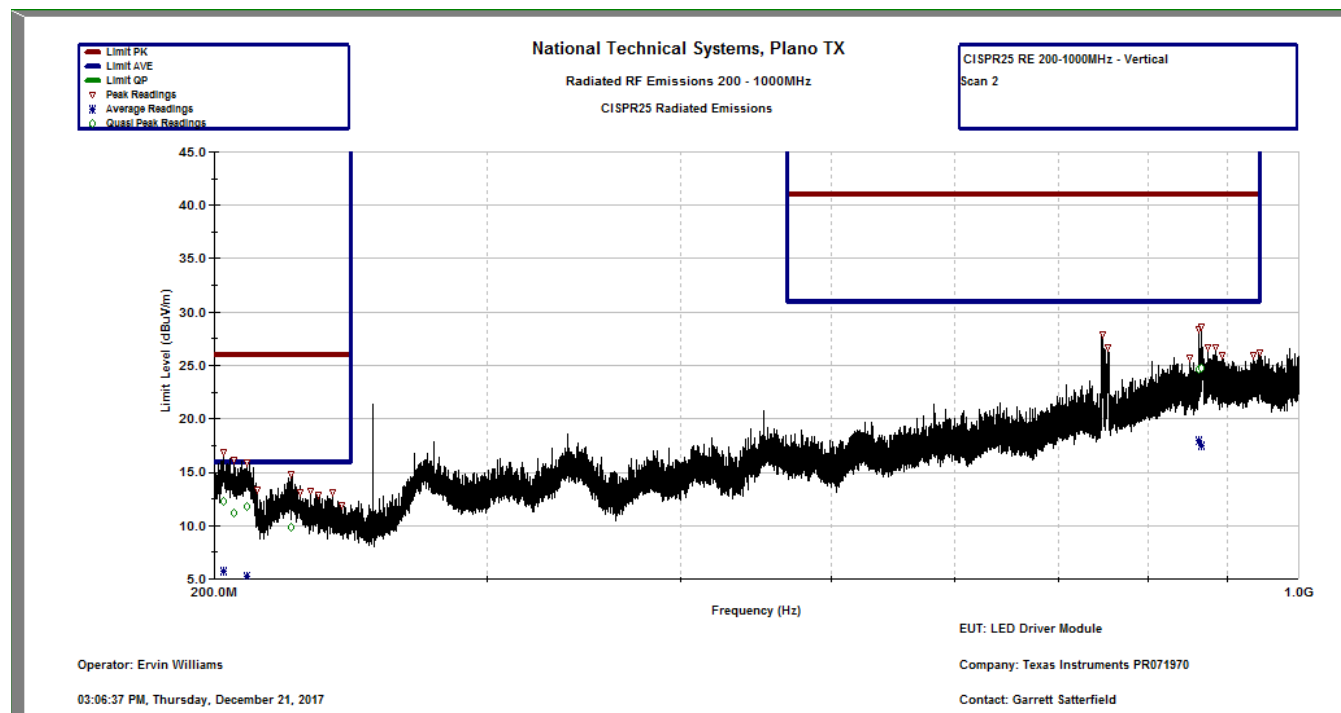


图 32. CISPR25 Class-5 Radiated Emissions: 200 MHz to 1 GHz (Vertical)

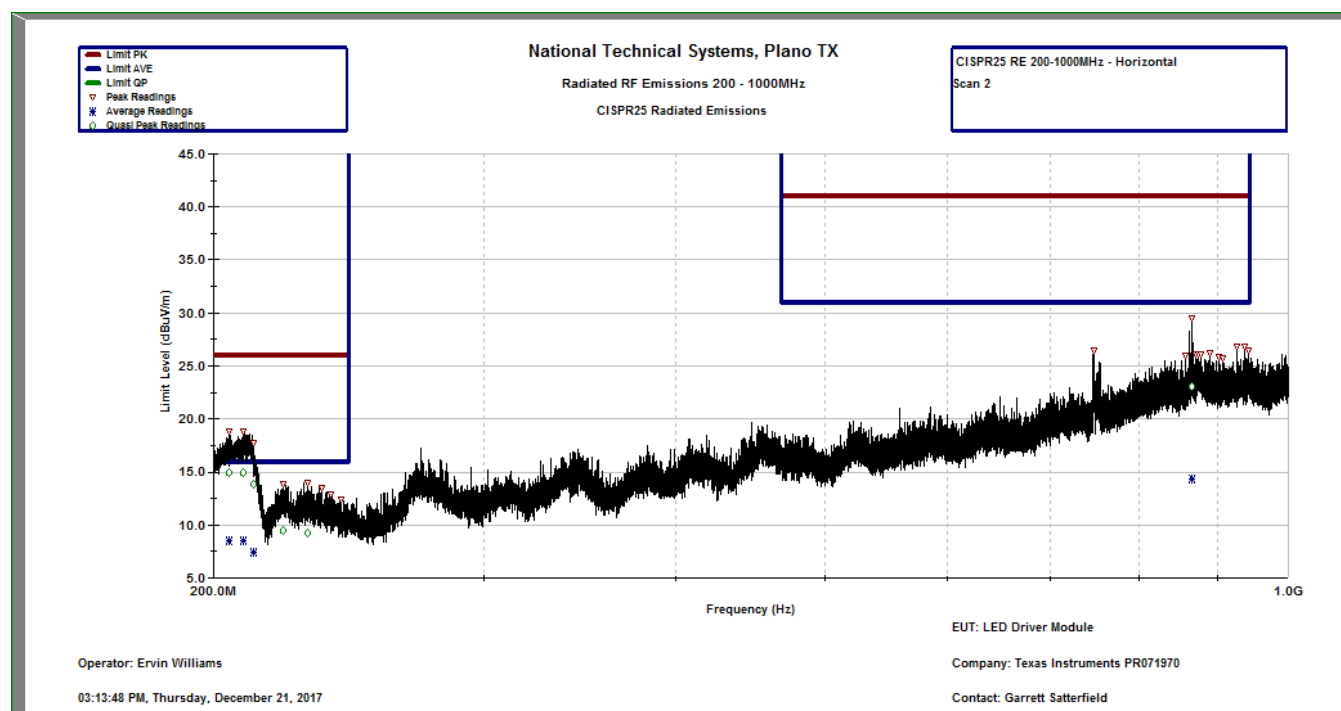


图 33. CISPR25 Class-5 Radiated Emissions: 200 MHz to 1 GHz (Horizontal)

3.2.6 EMI Testing Shielded Inductors

Additional tests were completed using shielded inductors instead of the standard inductors. 图 34 shows how the shielded inductors were mounted to the board. The inductors used were Cyntec VCMT053-T-100MN5 (shielded). These inductors included two extra PCB connections that attach to ground and connect to the metal shield that covers the inductor.

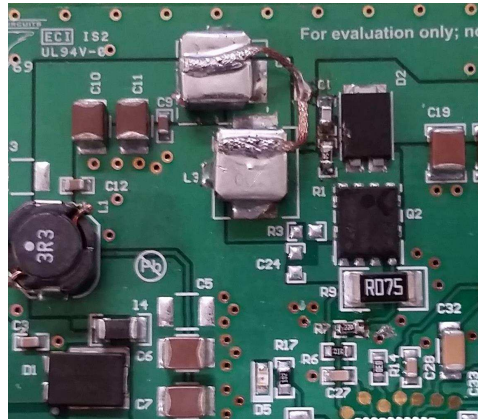


图 34. TIDA-01581 With Shielded Inductors Mounted (Cyntec VCMT053T-100MN5 Shielded)

图 35 shows an example of the results. Note the 2- to 3-dB improvement over some frequency ranges as compared to using unshielded inductors (see for comparison). Consider using shielded inductors if more margin is required between the test data and limit lines.

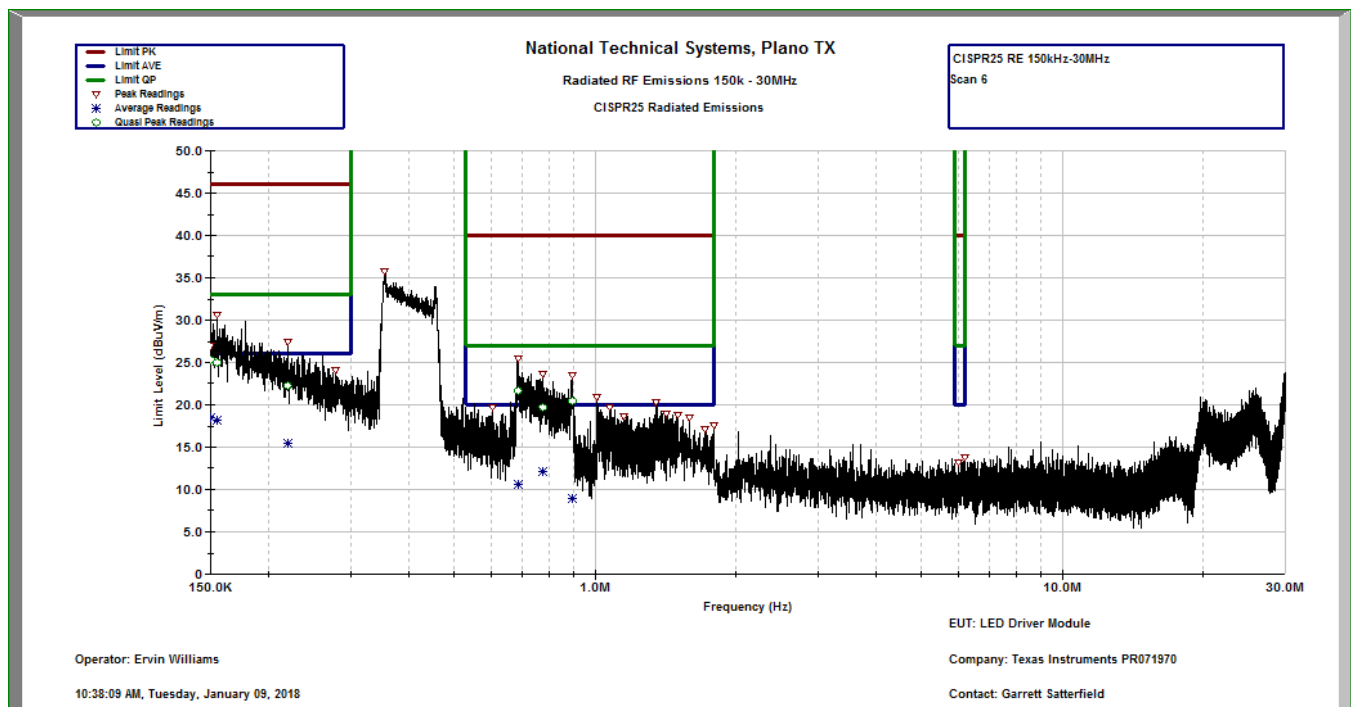


图 35. CISPR25 Class-5 Radiated Emissions: 150 kHz to 30 MHz With Shielded Inductors

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [TIDA-01581](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01581](#).

4.3 PCB Layout Recommendations

Use the following layout recommendations for optimal circuit and EMI performance:

- Use low equivalent series resistance (ESR) decoupling capacitors and place them as close to the IC pin as possible.
- Use copper pours in the boost converter component section instead of traces.
- Keep the output loop formed by the rectification diode, output capacitors, and low-side sense resistor as small as possible, as this is a discontinuous current path with high di/dt.
- Ensure that the traces cut as little as possible from the second-layer ground plane and that they do not cut in the path of the return current.
- Place the analog circuitry away from the switching power supply components.
- Keep the feedback traces that connect to CSP and CSN as short as possible.

4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01581](#).

4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01581](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01581](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01581](#).

5 Software Files

To download the software files, see the design files at [TIDA-01581](#).

6 Related Documentation

1. Texas Instruments, [Minimizing Ringing at the Switch Node of a Boost Converter Application Report](#)
2. Texas Instruments, [Driving Daytime Running Lights LEDs With Thermal Foldback Reference Design](#)
3. Texas Instruments, [0-W, Dual-Stage LED Driver Reference Design With Pre-Boost Control for Automotive Headlights](#)

6.1 商标

E2E, TINA-TI are trademarks of Texas Instruments.

All other trademarks are the property of their respective owners.

7 Terminology

CMOS— Complementary metal–oxide–semiconductor

'DRL'— Full brightness mode

EMI— Electromagnetic interference

ESR— Equivalent series resistance

FET— Field-effect transistor

LED— Light-emitting diode

MCU— Microcontroller unit

MOSFET— Metal-oxide-semiconductor field-effect transistor

NTC— Negative temperature coefficient

Op Amp—Operational amplifier

PCB— Printed-circuit board

'Position'— PWM dimming mode

PWM— Pulse-width modulation

SMPS— Switched-mode power supply

8 About the Author

GARRETT SATTERFIELD is an applications engineer at Texas Instruments where he is responsible for developing reference designs for automotive systems. Garrett received his BSEE from The Georgia Institute of Technology in 2016.

有关 TI 设计信息和资源的重要通知

德州仪器 (TI) 公司提供的技术、应用或其他设计建议、服务或信息，包括但不限于与评估模块有关的参考设计和材料（总称“TI 资源”），旨在帮助设计人员开发整合了 TI 产品的应用；如果您（个人，或如果是代表贵公司，则为贵公司）以任何方式下载、访问或使用了任何特定的 TI 资源，即表示贵方同意仅为该等目标，按照本通知的条款进行使用。

TI 所提供的 TI 资源，并未扩大或以其他方式修改 TI 对 TI 产品的公开适用的质保及质保免责声明；也未导致 TI 承担任何额外的义务或责任。TI 有权对其 TI 资源进行纠正、增强、改进和其他修改。

您理解并同意，在设计应用时应自行实施独立的分析、评价和判断，且应全权负责并确保应用的安全性，以及您的应用（包括应用中使用的 TI 产品）应符合所有适用的法律法规及其他相关要求。您就您的应用声明，您具备制订和实施下列保障措施所需的一切必要专业知识，能够 (1) 预见故障的危险后果，(2) 监视故障及其后果，以及 (3) 降低可能导致危险的故障几率并采取适当措施。您同意，在使用或分发包含 TI 产品的任何应用前，您将彻底测试该等应用和该等应用所用 TI 产品的功能而设计。除特定 TI 资源的公开文档中明确列出的测试外，TI 未进行任何其他测试。

您只有在为开发包含该等 TI 资源所列 TI 产品的应用时，才被授权使用、复制和修改任何相关单项 TI 资源。但并未依据禁止反言原则或其他法律授予您任何 TI 知识产权的任何其他明示或默示的许可，也未授予您 TI 或第三方的任何技术或知识产权的许可，该等产权包括但不限于任何专利权、版权、屏蔽作品权或与使用 TI 产品或服务的任何整合、机器制作、流程相关的其他知识产权。涉及或参考了第三方产品或服务的信息不构成使用此类产品或服务的许可或与其相关的保证或认可。使用 TI 资源可能需要您向第三方获得对该等第三方专利或其他知识产权的许可。

TI 资源系“按原样”提供。TI 兹免除对 TI 资源及其使用作出所有其他明确或默示的保证或陈述，包括但不限于对准确性或完整性、产权保证、无屡发故障保证，以及适销性、适合特定用途和不侵犯任何第三方知识产权的任何默认保证。

TI 不负责任何申索，包括但不限于因组合产品所致或与之有关的申索，也不为您辩护或赔偿，即使该等产品组合已列于 TI 资源或其他地方。对因 TI 资源或其使用引起或与之有关的任何实际的、直接的、特殊的、附带的、间接的、惩罚性的、偶发的、从属或惩戒性损害赔偿，不管 TI 是否获悉可能会产生上述损害赔偿，TI 概不负责。

您同意向 TI 及其代表全额赔偿因您不遵守本通知条款和条件而引起的任何损害、费用、损失和/或责任。

本通知适用于 TI 资源。另有其他条款适用于某些类型的材料、TI 产品和服务的使用和采购。这些条款包括但不限于适用于 TI 的半导体产品 (<http://www.ti.com/sc/docs/stdterms.htm>)、评估模块和样品 (<http://www.ti.com/sc/docs/sampters.htm>) 的标准条款。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122
Copyright © 2018 德州仪器半导体技术（上海）有限公司