

TI Designs: TIDA-00892

具有集成信号和电源的隔离式 RS-485 参考设计



说明

此 TI 设计提供了一种紧凑型解决方案，能够生成隔离式直流电源，同时支持隔离式 RS-485 通信。TIDA-00892 包含一个带有集成电源的增强型数字隔离器和一个 RS-485 收发器。该解决方案采用尽量减少占用面积的设计。

资源

| | |
|-----------------------------|-------|
| TIDA-00892 | 设计文件夹 |
| ISOW7841 | 产品文件夹 |
| SN65HVD1473 | 产品文件夹 |




咨询我们的 E2E 专家

特性

- 最小的组合解决方案：
 - 相当于 ISOW7841 器件封装尺寸
- 单电源解决方案：
 - 无需独立电源为接口侧组件供电
- 降低了 BOM 成本；解决方案消除了使用独立变压器的必要
- 简化了设计
- 可扩展至其他全双工 RS-485 收发器：
 - SN65HVD14xx、SN65HVD7x 和 SN65HVD3x
- 还可通过较小的布局更改扩展至半双工

应用

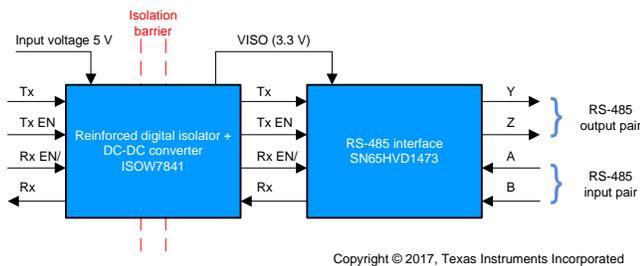- 电网通信模块
- 楼宇自动化和暖通空调 (HVAC)
- 工业自动化
- 医疗设备
- 电机驱动器



该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

1 System Overview

1.1 Design Theory

1.1.1 Isolation in Data Communication

Most industrial interface systems are areas where noise can seriously affect the integrity of data transfer. A tested method of improving noise performance for any interface circuit is galvanic isolation. Isolating the low-voltage (LV) microcontroller (MCU) side from the high-voltage (HV) interface side has proven to be an effective solution to protect from data corruption and to protect LV side components from seeing HV stresses like electrostatic discharge (ESD), electrical fast transient (EFT), and surge.

Common-mode noise effects and many forms of radiated noise can affect the communication system. Unwanted currents and voltages on a cable bus connecting multiple systems can cause severe problems. These voltages and currents come primarily from two sources: ground loops and electrical line surges. Ground loops occur when a bus or system uses multiple ground paths. Two system grounds connected to the bus and separated by hundreds or thousands of meters may not have the same potential. Because of this potential difference, current flows between these points. This unintended current flow can cause bit errors and damage or destroy components. Electrical surges can be caused by many sources, the result of currents coupled onto cable lines through induction. Long cable lines in industrial environments are especially susceptible to this phenomenon. The operation of electric motors, in particular, causes rapid changes in the ground potential. These changes can generate a current flow through any nearby lines to equalize the ground potential. Other HV stress voltage sources include ESDs, coupled transient noises (EFT) and lightning strikes (surge). These induced surges can result in thousands of volts of potential on the line and manifest themselves as transient current and voltage surges. Thus, a remote node may receive a 5-V switching signal superimposed on a HV level with respect to the local ground. These uncontrolled voltages and currents can corrupt the signal and be catastrophic to the device and system, damaging or destroying the components connected to the bus and resulting in system failure. RS-485 systems that run over long distances and connect multiple systems are especially susceptible to these events.

Isolating the RS-485 system devices from each of the systems connected to the bus prevents ground loops and electrical surges from destroying circuits. Isolation prevents ground loops as each system connected to RS-485 cable bus and each RS-485 circuit has a separate and isolated ground. By referencing each RS-485 circuit only to one ground, ground loops are eliminated. Isolation also allows the RS-485 circuit reference voltage levels to rise and fall with any surges that appear on the cable line. Allowing the circuit voltage reference to move with surges, rather than being clamped to a fixed ground, prevents devices from being damaged or destroyed. To accomplish system isolation, both the RS-485 signal lines and power supplies must be isolated.

1.1.2 RS-485 Communication

Industrial and instrumentation applications (I and I) require transmission of data between multiple systems often over very long distances. The RS-485 bus standard is one of the most widely used physical layer bus designs in I and I applications.

The key features of RS-485 that make it ideal for use in I and I communications applications are:

- Long distance links of up to 4000 feet
- Bidirectional communications possible over a single pair of twisted cables
- Differential transmission increases noise immunity and decreases noise emissions

- Multiple drivers and receivers can be connected on the same bus
- Wide common-mode range allows for differences in ground potential between the driver and receiver

In harsh and noisy environments such as multi-unit residential buildings or industrial settings, an RS-485 bus architecture can be used to implement a low-cost, yet robust communications network. The differential nature of RS-485 signaling makes it less susceptible to external interference. Moreover, the RS-485 specification supports multidrop configurations, thus allowing the connection of multiple meters to a single bus. For instance, RS-485 can be used in an apartment building to transmit data from meters in each apartment to a central unit that aggregates the data from the individual meters, which can then be read through a wireless or PLC link. A similar approach can be used in industrial systems that require multiple cost centers to be metered.

1.2 System Description

The TIDA-00892 reference design combines both data and power isolation along with RS-485 communication interface to provide a robust, low-cost, low footprint solution that customers can directly place on their designs. This TI Design combines a High-Performance Reinforced Digital Isolator with Integrated High-Efficiency, Low Emissions DC-DC Converter (ISOW7841) with a Robust 3.3V Full-Duplex RS-485 Transceiver (SN65HVD1473).

The TIDA-00892 does not require any additional components to generate the isolated power. This makes the solution less than a quarter of the size of all existing solutions using a discrete transformer to generate the required isolated power. This TI Design takes a single power supply input (3 to 5.5 V) and digital signals referred to the input supply level. The board generates an isolated power supply using an integrated DC-DC converter. This isolated supply is used to power the RS-485 transceiver. The input signals are isolated and connected to the transceiver, which converts the digital signals into its RS-485 counterpart.

An electricity grid without adequate communications is simply a power broadcaster. It is through the addition of two-way communications that the power grid is made "smart." Communications enables utilities to achieve three key objectives: intelligent monitoring, security, and load balancing. By using two-way communications, data can be collected from sensors and meters located throughout the grid and transmitted directly to the grid operator's control room. This added communications capability provides enough bandwidth for the control room operator to actively manage the grid. The communications must be reliable, secure, and cost effective. The sheer scale of the electrical grid network makes cost a critical consideration when implementing a communications technology. The communications used in grid infrastructure systems is dominated by RS-485. The TIDA-00892 design can fit in to power the RS-485 bus side and provide a cost-effective, low-footprint solution to this requirement.

PLCs and grid communication systems have been an integral part of factory automation and industrial process control. They use digital and analog I/O modules to interface to sensors, actuators, and other equipment. Analog inputs for the PLC system include temperature sensors and transmitters, current sensors, voltage sensors, and others that can convert a physical quantity to an electrical signal. Digital inputs include push-buttons, proximity switches, photo sensors, pressure switches, and more. These signals need to be either group isolated or per channel isolated. PLCs are expected to work in harsh industrial environments. Hence sensor signals are converted to digital domain and coupled through a digital isolator to control domain. For sensor signal conditioning, power is generated from the backplane side by an isolated DC-DC converter. Fitting in the TIDA-00892 can significantly reduce the required area and bring down the BOM cost by eliminating the requirement for discrete transformers.


Medical equipment need isolation for patient safety. For ECG, multiple leads are connected to the patient. The signal chain must be robust enough to capture very weak signals, digitize and process it, and pass it to the system controller over the isolation barrier. The power for signal processing units is typically generated by onboard isolated DC-DC converters. This power can be replaced directly with the TIDA-00892 to get both communication and power isolation with the RS-485 interface. Also any peripheral connected to this equipment must be isolated from the controller. This solution makes sense to digitally isolate the interface signals and also power up the transceivers.

1.3 Key System Specifications

表 1. Key System Specifications

| FEATURE | SPECIFICATION | VALUE |
|------------------------|--------------------|-------------------------------------|
| Input supply | Input voltage | 3 to 5 V |
| | Output voltage | 3.3 V |
| Isolated output supply | Output current | 75 mA (3.3 V _{IN}) |
| | | 130 mA (5 V _{IN}) |
| Communication | Max data rate | 20 Mbps (full-duplex communication) |
| Isolation | Clearance | > 3 mm |
| | Working voltage | 300 V _{RMS} |
| | CMTI | > 100 kV/μs |
| EMI or EMC | ESD | 6 kV (across barrier) |
| | | 16 kV (across RS-485 lines) |
| | Radiated emissions | CISPR22 (Class A) |

1.4 Block Diagram

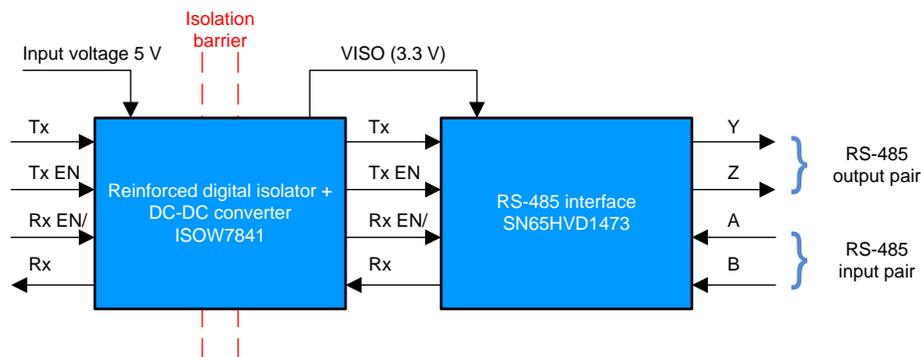

Copyright © 2017, Texas Instruments Incorporated

图 1. TIDA-00892 Block Diagram

图 1 shows the high-level block diagram of the TIDA-00892. As previously mentioned, this TI Design can be broken down into two main sections: the isolation block (ISOW7841) and the interface block (SN65HVD1473).

The TIDA-00892 works on a single input of 3 to 5.5 V. The integrated power supply can produce an isolated output voltage of 3.3 V (for any input) or 5 V (for VCC1 ≥ 5 V). This can be used to power up the RS-485 interface block. The TIDA-00892 communicates with digital signals on one side and gives the RS-485 lines on the other. The design can be interfaced to an MCU transmitting and receiving data while controlling the TX and RX enable lines. These signals are isolated from the RS-485 lines available for communication to the field side. The SN65HVD1473 RS-485 transceiver and the isolated power supply integrated four channel digital isolator. The side A of the isolator is powered from a 5-V or 3.3-V power supply, the secondary side of the isolator will be powered through the integrated isolated power supply. The integrated power supply can produce two voltage configurations on side B: 5 V or 3.3 V for the 5-V supply on side A and 3.3 V for the 3.3-V supply on side A. The two available voltage configurations enable the same design to be used with other transceivers.

The load in this TI Design is the RS-485 transceiver. The design can interface with the MCU to transmit and receive data and enable transmission and reception. The signals to and from the MCU are isolated from the transceiver. The TIDA-00892 board can be broken down to two main sections: the isolation block and the interface block.

1.5 Highlighted Products

The TIDA-00892 features the following devices from Texas Instruments.

1.5.1 ISOW7841

The ISOW784x is a family of high-performance quad-channel reinforced digital isolators with an integrated high-efficiency power convertor. The integrated DC-DC convertor provides up to 650 mW of isolated power at high efficiency and can be configured for various input and output voltage configurations. These devices eliminate the need for a separate isolated power supply in space-constrained isolated designs. ISOW784x devices provide high electromagnetic immunity and low emissions, while isolating CMOS or LVCMOS digital I/Os. The signal isolation channel has a logic input and output buffer separated by a silicon dioxide (SiO₂) insulation barrier, whereas power isolation uses on-chip transformers separated by a thin film polymer as insulation material. These devices prevent noise currents on a data bus or other circuits from entering the local ground and interfering with or damaging sensitive circuitry. Through innovative chip design and layout techniques, the electromagnetic compatibility of the ISOW784x has been significantly enhanced to ease system level ESD, EFT, surge, and emissions compliance. The high efficiency of the power convertor allows operation at a higher ambient temperature. The ISOW784x family of devices is available in a 16-pin SOIC wide-body (DWE) package.

- Integrated high efficiency DC-DC convertor with on-chip transformer
- Wide input supply range: 3 to 5.5 V
- Regulated 5- or 3.3-V output
- Up to 0.65-W output power
- 130-mA load current (5 to 5 V; 5 to 3.3 V;)
- 75-mA load current (3.3 to 3.3 V)
- Soft start to limit inrush current
- Overload and short circuit protection
- Thermal shutdown
- Signaling rate up to 100 Mbps
- Low prop-delay: 13 ns typical (5-V supply)
- High CMTI: ± 100 kV/ μ s (min)
- Robust electromagnetic compatibility (EMC)
 - System level ESD, EFT, and surge immunity
 - Low radiated emissions
- Safety-related certifications
 - 7071- V_{PK} Reinforced Isolation per DIN V VDE V 0884-10 (VDE V 0884-10): 2006-12
 - 5000- V_{RMS} Isolation for 1 Minute per UL 1577
 - CSA Component Acceptance Notice 5A, IEC 60950-1 and IEC 60601-1 End Equipment Standards
 - CQC Approval per GB4943.1-2011
 - TUV Certification according to EN 60950-1 and EN 61010-1
 - All agency certifications are planned
- Extended temperature range: -40°C to 125°C

1.5.2 SN65HVD1473

The SN65HVD1473 is a full-duplex transceiver that features the highest ESD protection in the RS-485 portfolio, supporting ± 16 -kV IEC61000-4-2 contact discharge and $> \pm 30$ -kV HBM ESD protection. This RS-485 transceiver has a robust 3.3-V driver and receiver and is offered in a standard SOIC package as well as in a small-footprint MSOP package. The large receiver hysteresis of the SN65HVD1473 device provides immunity to conducted differential noise and the wide operating temperature enables reliability in harsh operating environments. This device combines a differential driver and a differential receiver, which operate from a single 3.3-V power supply. Each driver and receiver has a separate input and output pins for full-duplex bus communications designs. These devices all feature a wide common-mode voltage range which makes the devices suitable for multi-point applications over long cable runs.

The SN65HVD1473 device has active-high driver enables and active-low receiver enables. A low, less than 5- μ A standby current can be achieved by disabling both the driver and receiver.

- 1/8 unit-load options available
 - Up to 256 nodes on the bus
- Bus I/O protection
 - $> \pm 30$ -kV HBM protection
 - $> \pm 16$ -kV IEC-61000-4-2 Contact Discharge
 - $> \pm 4$ -kV IEC61000-4-4 Fast Transient Burst
- Extended industrial temperature range:
 - -40°C to 125°C
- Large receiver hysteresis (70 mV) for noise rejection
- Low power consumption
 - < 1.1 -mA quiescent current during operation
 - Low standby supply current: 10 nA typical, < 5 μ A (max)
- Glitch-free power-up and power-down protection for hot-plugging applications
- 5-V tolerant logic inputs compatible with 3.3-V or 5-V controllers

2 Getting Started Hardware

2.1 Board Description

图 2 shows the size of the isolated RS-485 with an integrated power solution. The solution space within the board has been marked in red and is slightly bigger than the ISOW7841 IC. The full board measures 31 × 13.3 mm while the actual solution space (marked in red) is 11.9 × 11.2 mm.

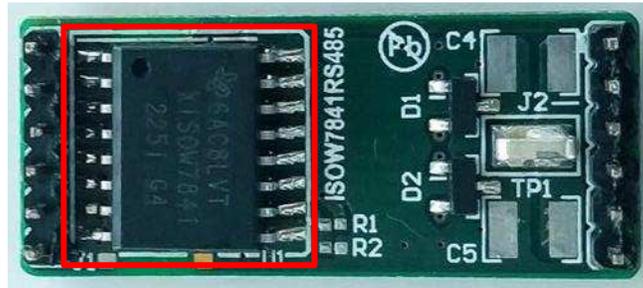


图 2. Solution Space

图 3 shows the locations of the connectors on the board for interfacing with the solution.



图 3. Connectors

2.2 Connectors Description

表 2. Connectors

| CONNECTOR | PIN POSITION | PIN NAME | I/O OR POWER | DESCRIPTION |
|-----------|--------------|----------|--------------|---------------------------|
| J1 | 1 | VIN | Power | Input supply (3 to 5.5 V) |
| | 2 | Tx | I | Digital driver input |
| | 3 | Tx EN | I | Driver enable |
| | 4 | Rx EN/ | I | Receiver enable |
| | 5 | Rx | O | Digital receiver output |
| | 6 | GND1 | Ground | Input supply ground |
| J2 | 1 | VISO | Power | Isolated power output |
| | 2,3 | Y, Z | O | RS-485 output pair |
| | 5,4 | A, B | I | RS-485 input pair |
| | 6 | GND2 | Ground | Isolated output ground |

The design comes pre-populated with two of the TI ICs (ISOW7841 and SN65HVD1473) and a 120- Ω termination resistor on the bus to match the transmission line impedance. VCC1 and GND1 are connected at Pin 1 and Pin 6 of J1, respectively. The digital input can be applied to Pin 2 of J1 and the receiver output can be observed on Pin 5 of J1. On the other side of the board, the differential bus lines A and B (RS-485 input lines) are Pin 5 and Pin 4 respectively on J2, while Y and Z (RS-485 output lines) are connected to Pin 2 and Pin 3 respectively on J2. The boards include male berg heads to allow bus cables to be securely attached.

Connect MCU Tx to Pin 2 of J1 and MCU Rx to Pin 5 of J1. Connect the driver and receiver enable lines from MCU to Pins 3 and 4, respectively. The RS-485 lines, AB and YZ, need to be connected as individual pairs of twisted pair cables. The system can be configured and used for half-duplex or full-duplex communication by providing appropriate transmit and receive enable signal from MCU side.


This TI Design can be extended to other RS-485 transceivers by replacing the existing transceiver on the board and selecting the right voltage configuration. The isolated output voltage configuration can be easily changed by changing the resistor combination of R1 and R2. See 表 3 to understand how to realize the required voltage configuration.

表 3. Voltage Configurations

| INPUT VOLTAGE (V) | OUTPUT VOLTAGE (V) | R1 (Ω) | R2 (Ω) |
|-------------------|--------------------|-----------------------|-----------------------|
| 5.0 | 5.0 | Populate | Do Not Populate |
| | 3.3 | Do Not Populate | Populate |
| 3.3 | 3.3 | Do Not Populate | Populate |
| | 5.0 | Invalid configuration | Invalid configuration |


3 Testing and Results

3.1 Test Setups

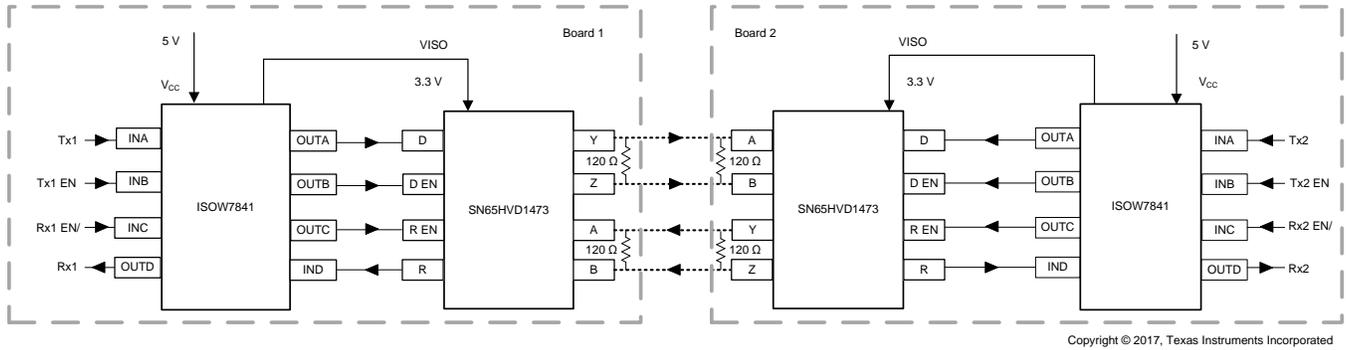

Copyright © 2017, Texas Instruments Incorporated

图 4. Full Duplex Communication Test Setup

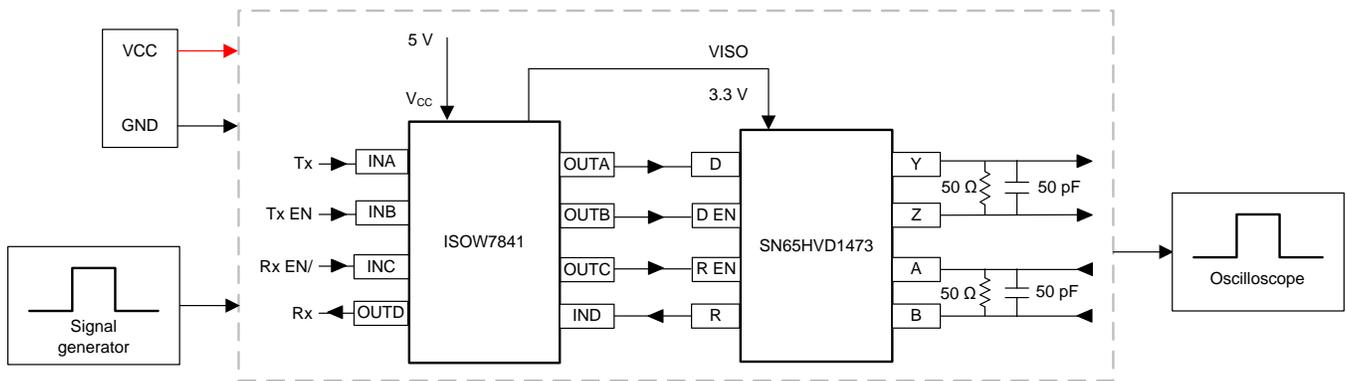

Copyright © 2017, Texas Instruments Incorporated

图 5. Typical Test Setup

3.2 Full-Duplex Communication

As shown in 图 4, two boards are connected to each other, forming a full-duplex system for the test setup. Both the boards are powered with a 5-V supply voltage and VISO is configured for 3.3 V in a full-duplex mode (Tx EN pulled high and Rx EN pulled low).

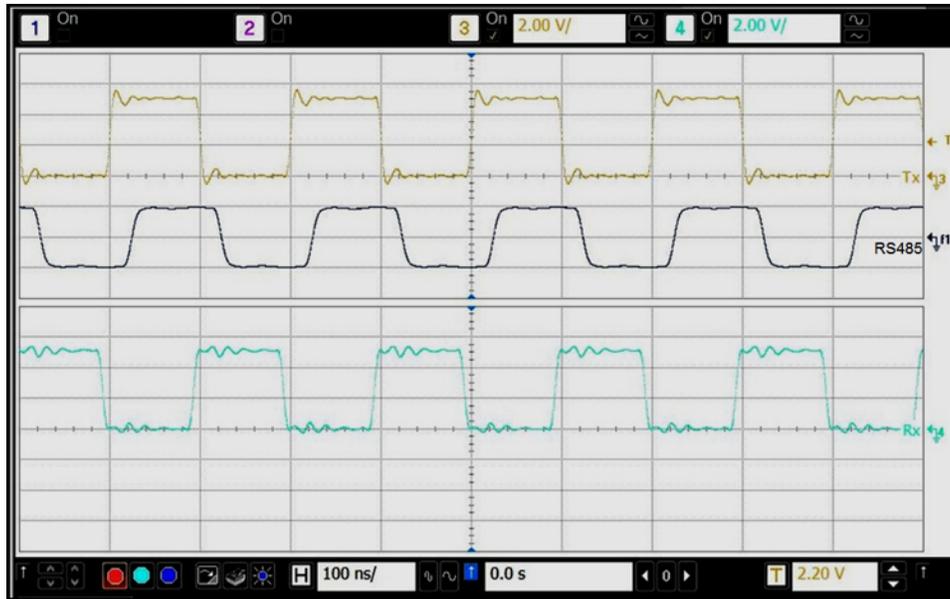


图 6. Full-Duplex Communication

3.3 Propagation Delay

As shown in 图 5, single board propagation delay from digital side to RS-485 side was measured.

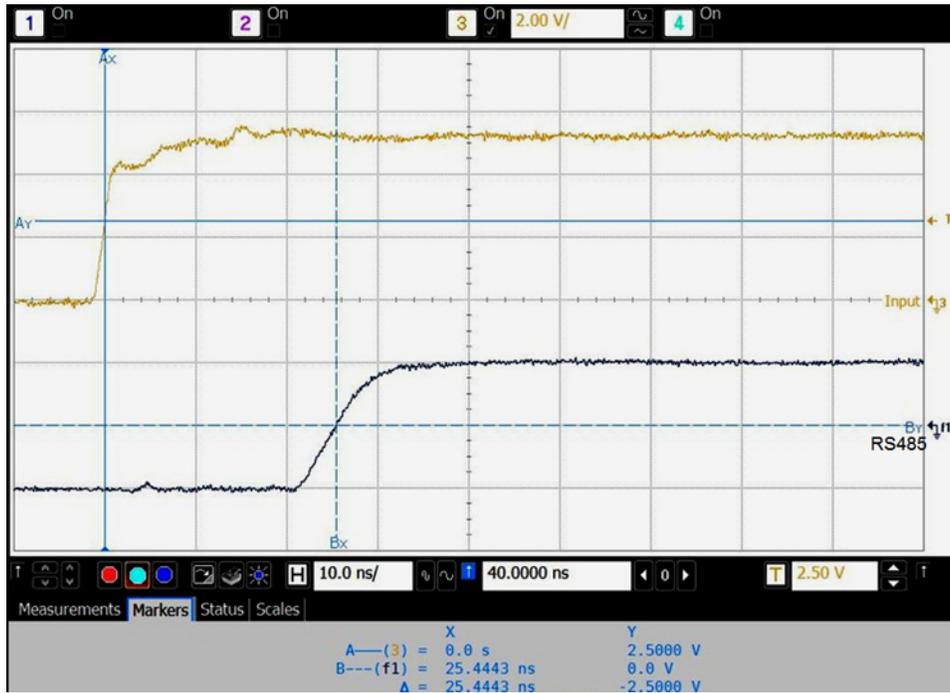


图 7. Propagation Delay (Low to High)

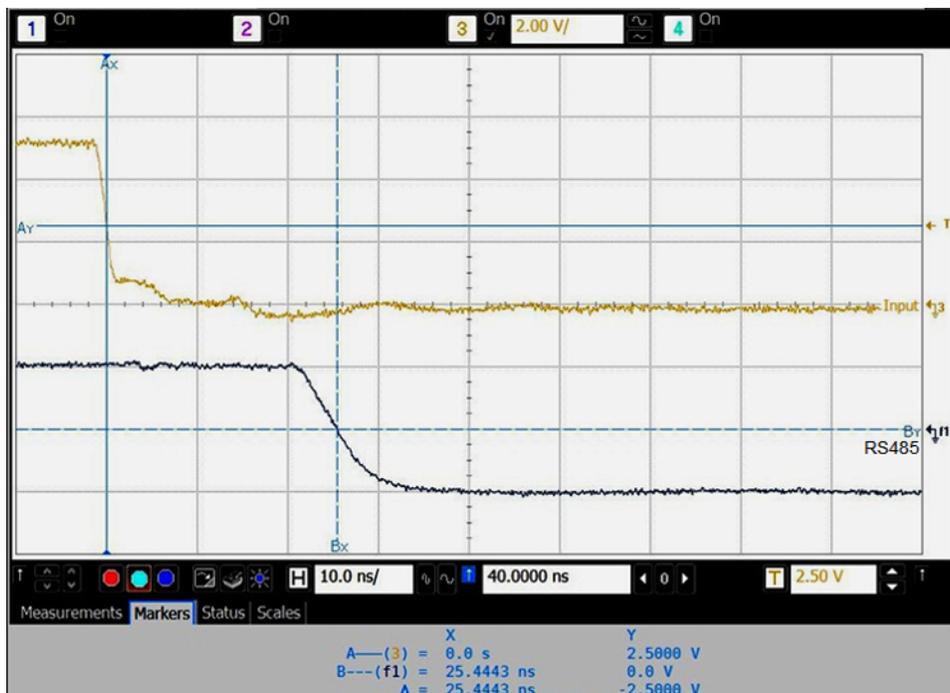


图 8. Propagation Delay (High to Low)

3.4 Jitter

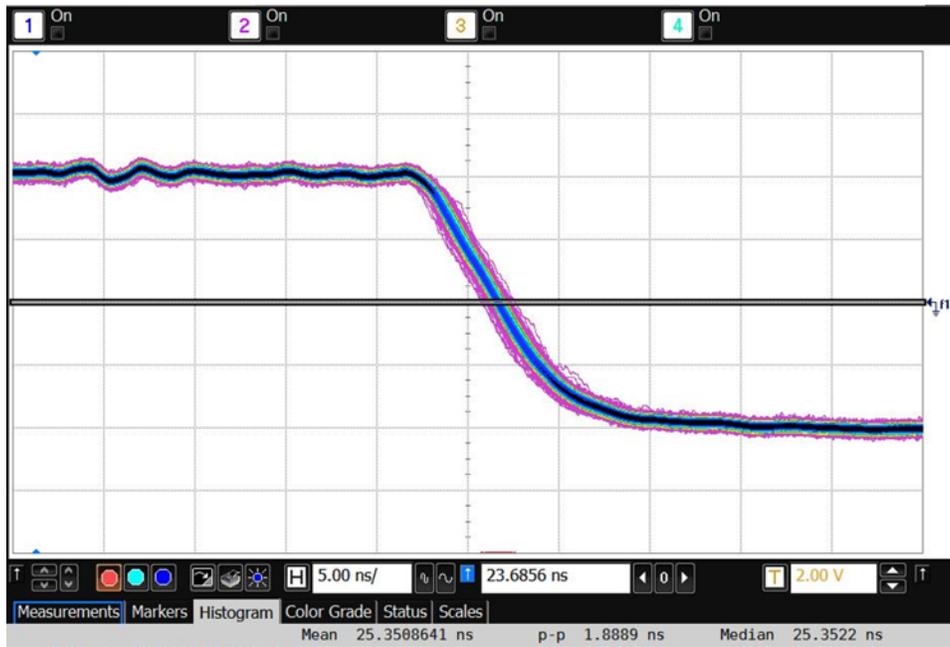


图 9. Jitter

3.5 Eye Diagram

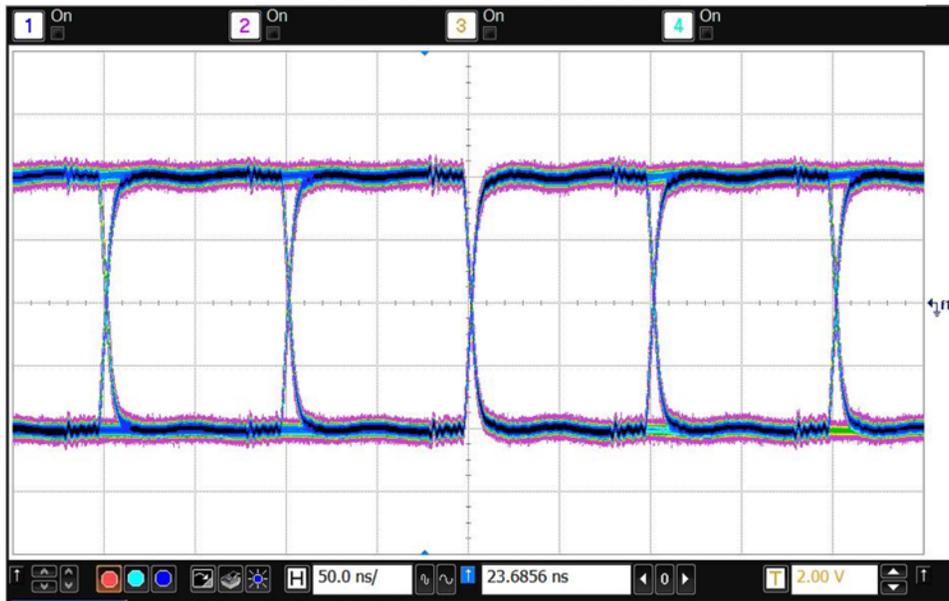


图 10. Eye Diagram

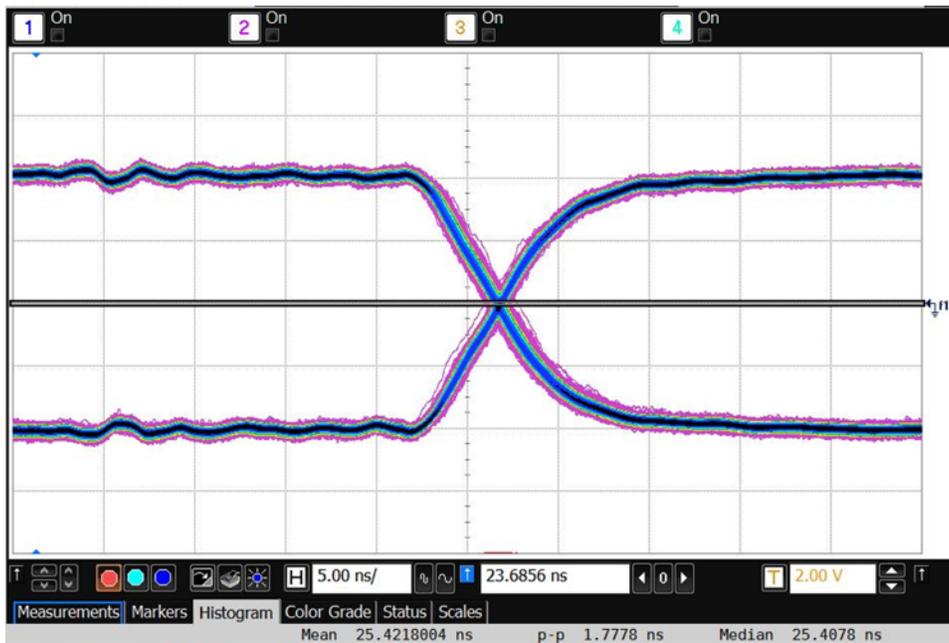


图 11. Eye Closure

3.6 Current Consumption

Current consumption of the TIDA-00892 was measured with both the RS-485 receiver and transmitter toggling at different data rates. Termination resistors were populated as per [图 5](#).

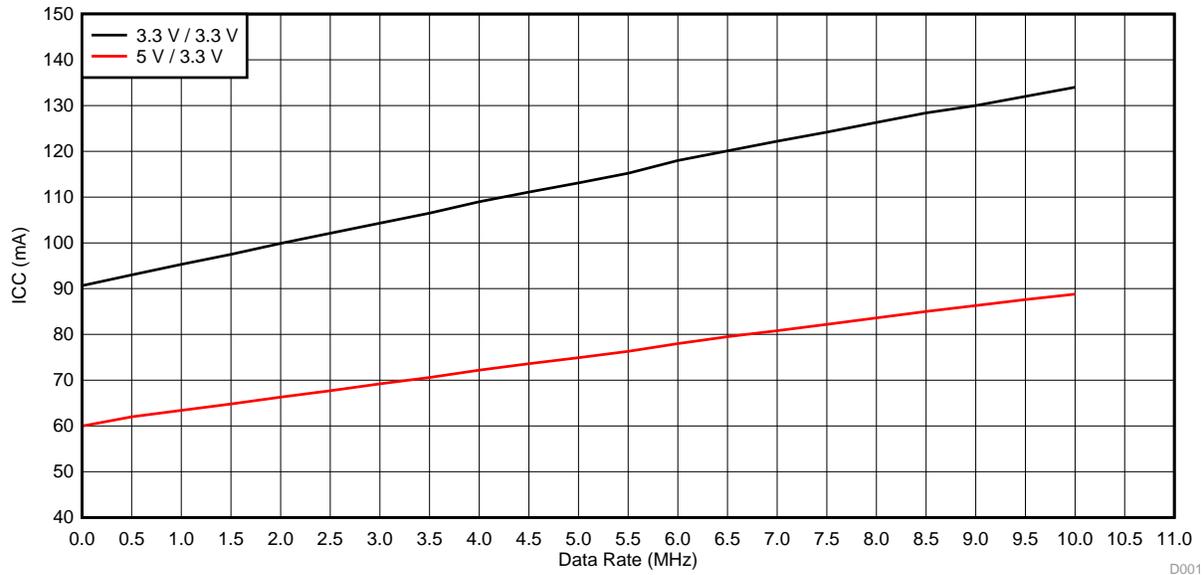


图 12. ICC versus Data Rate

3.7 IEC-ESD Performance (IEC-61000-4-2)

Contact discharge IEC-ESD testing was performed on the TIDA-00892 using a pointed contact discharge tip. The board was subjected to mainly two kinds of ESD strikes. In the "Across barrier" row, the interface side was struck with the reference ground or power earth connected at the MCU side ground (GND1). Similarly for the "Same side" row, the interface lines were struck with the reference ground or power earth connected to the interface side ground (GND2). [表 4](#) shows the IEC-ESD test results. Each of the stressed pins were subjected to 10 strikes of each polarity of the corresponding stress voltage.

表 4. IEC-ESD Results

| NATURE OF STRIKE | STRIKE POINT | STRESS VOLTAGE | RESULT |
|------------------|--------------|----------------|--------|
| Across barrier | VISO | ±6 kV | Pass |
| | Y | ±6 kV | Pass |
| | Z | ±6 kV | Pass |
| | A | ±6 kV | Pass |
| | B | ±6 kV | Pass |
| | GND2 | ±6 kV | Pass |
| Same side | Y | ±16 kV | Pass |
| | Z | ±16 kV | Pass |
| | A | ±16 kV | Pass |
| | B | ±16 kV | Pass |

3.8 Radiated Emissions (CISPR 22)

The emissions measurements were done according to CISPR 22 standard in a certified facility. 图 13 shows the emissions measurement for the TIDA-00892 design when the communication lines were being operated under a static high condition.

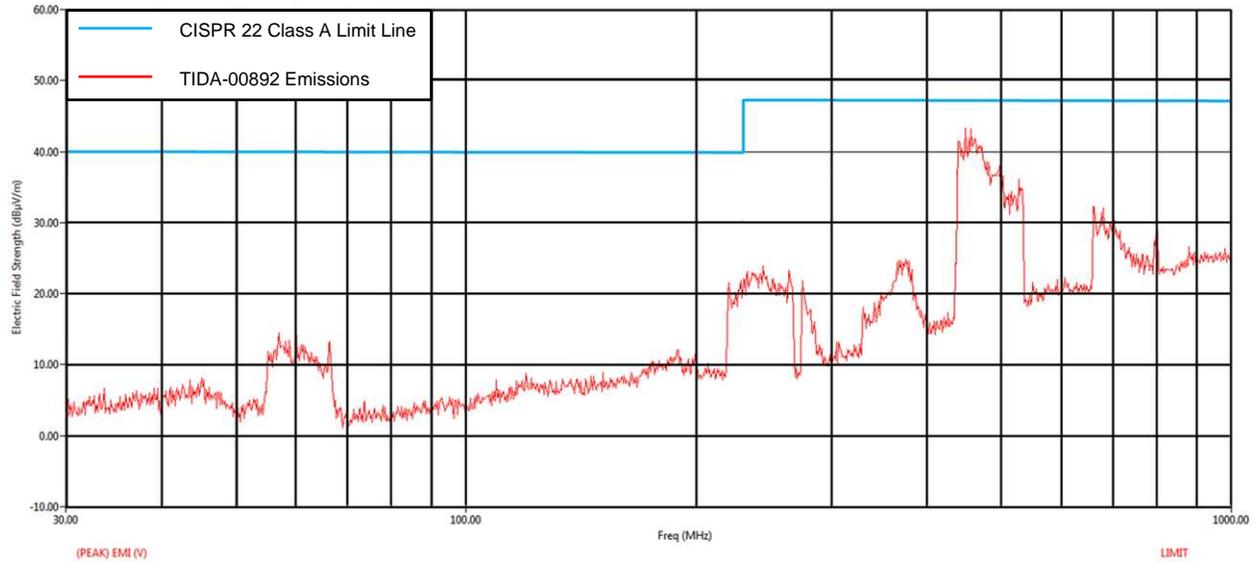


图 13. Radiated Emissions (CISPR 22)

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [TIDA-00892](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-00892](#).

4.3 PCB Layout Recommendations

4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-00892](#).

4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-00892](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-00892](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-00892](#).

5 Related Documentation

1. Texas Instruments, [ISOW784x High-Performance, 5000-VRMS Reinforced Quad-Channel Digital Isolators With Integrated High-Efficiency, Low-Emissions DC-DC Converter](#), ISOW784x Datasheet (SLLSEY2)
2. Texas Instruments, [SN65HVD147x 3.3-V Full-Duplex RS-485 Transceivers With \$\pm 16\$ -kV IEC ESD](#), SN65HVD147x Datasheet (SLLSEJ8)
3. Texas Instruments, [Isolated RS-232 With Integrated Signal and Power Reference Design](#), TIDA-01230 Design Guide (TIDUCT3)

5.1 商标

All trademarks are the property of their respective owners.

6 About the Authors

ANAND REGHUNATHAN is an applications engineer at Texas Instruments, where he is responsible for defining new high-performance products and providing application support on existing products for industrial and automotive markets, specifically for isolation products. Anand brings to the role an experience in EMC testing for both isolation and interface products. Anand earned his bachelor of technology (B.Tech) in electronics and communications engineering from College of Engineering, Trivandrum, India.

NEERAJ BHARDWAJ is an applications engineer at Texas Instruments, where he is responsible for defining new high-performance analog products and application support on existing products for industrial and automotive markets. He has a high level of experience in motor drive systems and high-voltage systems with an emphasis in safety applications, standards, test and characterization of mixed signal processors, and EMC cognizant systems design. In his previous role, he led the Systems and Applications team in the Safety and Security Microcontroller Group in TI. He mentors teams on competitive robotics. He has over 20 years of experience in the industry and has worked for TI since 2005. He has a B.E. degree in electrical engineering specialized in high voltage and power electronics from the Government Engineering College Jabalpur and a M.Tech. degree in aerospace engineering specialized in control and guidance from the Indian Institute of Technology Bombay.

修订历史记录

注：之前版本的页码可能与当前版本有所不同。

| Changes from Original (March 2017) to A Revision | Page |
|---|-------------|
| • 已更改 TIDA-00892 框图中的接口名称 | 1 |

有关 TI 设计信息和资源的重要通知

德州仪器 (TI) 公司提供的技术、应用或其他设计建议、服务或信息，包括但不限于与评估模块有关的参考设计和材料（总称“TI 资源”），旨在帮助设计人员开发整合了 TI 产品的应用；如果您（个人，或如果是代表贵公司，则为贵公司）以任何方式下载、访问或使用了任何特定的 TI 资源，即表示贵方同意仅为该等目标，按照本通知的条款进行使用。

TI 所提供的 TI 资源，并未扩大或以其他方式修改 TI 对 TI 产品的公开适用的质保及质保免责声明；也未导致 TI 承担任何额外的义务或责任。TI 有权对其 TI 资源进行纠正、增强、改进和其他修改。

您理解并同意，在设计应用时应自行实施独立的分析、评价和判断，且应全权负责并确保应用的安全性，以及您的应用（包括应用中使用的 TI 产品）应符合所有适用的法律法规及其他相关要求。就您的应用声明，您具备制订和实施下列保障措施所需的一切必要专业知识，能够 (1) 预见故障的危险后果，(2) 监视故障及其后果，以及 (3) 降低可能导致危险的故障几率并采取适当措施。您同意，在使用或分发包含 TI 产品的任何应用前，您将彻底测试该等应用和该等应用所用 TI 产品的功能而设计。除特定 TI 资源的公开文档中明确列出的测试外，TI 未进行任何其他测试。

您只有在为开发包含该等 TI 资源所列 TI 产品的应用时，才被授权使用、复制和修改任何相关单项 TI 资源。但并未依据禁止反言原则或其他法律授予您任何 TI 知识产权的任何其他明示或默示的许可，也未授予您 TI 或第三方的任何技术或知识产权的许可，该等许可包括但不限于任何专利权、版权、屏蔽作品权或与使用 TI 产品或服务的任何整合、机器制作、流程相关的其他知识产权。涉及或参考了第三方产品或服务的信息不构成使用此类产品或服务的许可或与其相关的保证或认可。使用 TI 资源可能需要您向第三方获得对该等第三方专利或其他知识产权的许可。

TI 资源系“按原样”提供。TI 兹免除对 TI 资源及其使用作出所有其他明确或默示的保证或陈述，包括但不限于对准确性或完整性、产权保证、无屡发故障保证，以及适销性、适合特定用途和不侵犯任何第三方知识产权的任何默认保证。

TI 不负责任何申索，包括但不限于因组合产品所致或与之有关的申索，也不为您辩护或赔偿，即使该等产品组合已列于 TI 资源或其他地方。对因 TI 资源或其使用引起或与之有关的任何实际的、直接的、特殊的、附带的、间接的、惩罚性的、偶发的、从属或惩戒性损害赔偿，不管 TI 是否获悉可能会产生上述损害赔偿，TI 概不负责。

您同意向 TI 及其代表全额赔偿因您不遵守本通知条款和条件而引起的任何损害、费用、损失和/或责任。

本通知适用于 TI 资源。另有其他条款适用于某些类型的材料、TI 产品和服务的使用和采购。这些条款包括但不限于适用于 TI 的半导体产品 (<http://www.ti.com/sc/docs/stdterms.htm>)、[评估模块](http://www.ti.com/sc/docs/sampters.htm)和样品 (<http://www.ti.com/sc/docs/sampters.htm>) 的标准条款。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122
Copyright © 2018 德州仪器半导体技术（上海）有限公司