

TI Designs: TIDA-01572

PC 立体声音音频参考设计



说明


该立体声音频子系统采用 TAS2770 器件，与 PC 应用中的编解码器驱动器解决方案相比能够提供更高质量的音频。该器件支持使用智能放大器算法，该算法通过实时监测扬声器的物理条件，能够在为扬声器提供保护的同时最大限度提高声压级 (SPL)。此设计提供了工作布局和设计建议，支持快速调整该解决方案。

资源

TIDA-01572	设计文件夹
TAS2770	产品文件夹
TAS2770EVM-STEREO	工具文件夹
TL760M33-Q1	产品文件夹
TPS736	产品文件夹
TPS62085	产品文件夹



咨询我们的 E2ETM 专家

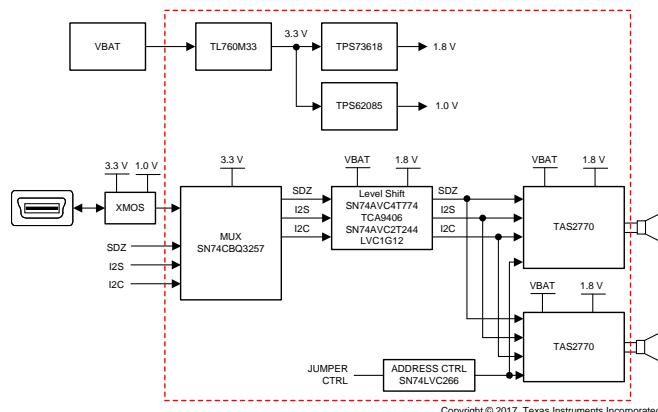


Copyright © 2017, Texas Instruments Incorporated

特性

- 高性能 D 类放大器支持 4.5V 至 16V 的宽 VBAT 电源电压范围
- 15W 连续功率，4Ω 负载，12.6V 电压 (1% THD+N)
- 用于诊断的集成电压和电流检测功能
- 32μV 空闲通道噪声和扩频低 EMI 模式
- 支持 I²S 和 SoundWireTM输入
- 小型 26 引脚 QFN (3.5mm × 4mm) 封装
- 输入多路复用功能支持多个输入源

应用

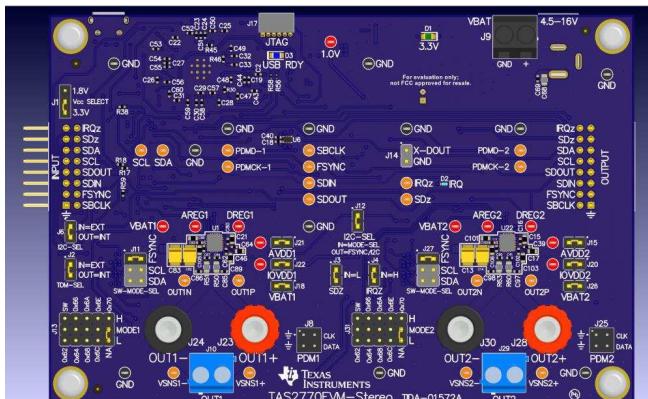- PC 和笔记本电脑
- 无线 (BT) 扬声器
- 恒温器
- 可视门铃
- 视频通信系统



该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

1 System Description

This stereo audio subsystem uses two TAS2770 devices for improved audio capabilities over CODEC solutions. The TAS2770 is highly configurable to various audio input formats and has integrated speaker voltage and current sensing, which can be used to determine the maximum audio signal while simultaneously protecting against thermal and mechanical failure mechanisms.

This design incorporates a simple power solution to provide the necessary rails to operate and interface with the TAS2770 device. The user is only required to provide VBAT with a supply ranging from 4.5 V to 16 V.

For ease of use, this design incorporates an XMOS device, which allows for testing and development using a USB interface. If desired, however, the board can be set to accept external I²C and I²S bus connections to test using another system, such as an audio analyzer.

After connecting the device to a PC running PurePath™ Console 3 with the TAS2770-specific application, the user can quickly and easily configure the device. Among the many features of the TAS2770 is a battery protection output limiter. This limiter controls the automatic gain control to help maintain a quality audio output while preventing excessive demand on the battery system. Brownout protection is also included to protect the system from failing due to potential demands generated by the audio system. In addition, the designer can configure the inter-chip limiter alignment (ICLA) to ensure that, while in a multichannel configuration, all the channels that are actively grouped together attack equally to maintain audio continuity and balance.


1.1 Key System Specifications

表 1. Key System Specifications

PARAMETERS	SPECIFICATIONS
Power supply	4.5-V to 16-V DC
Digital interfaces	I ² S, I ² C, SoundWire, pulse desnity modulation (PDM)
TAS2770EVM stereo power consumption	节 3.2.2.1
SPL	节 3.2.2.2
Idle channel noise	节 3.2.2.2
THD+N versus frequency	节 3.2.2.2
THD+N versus power	节 3.2.2.2

2 System Overview

2.1 Block Diagram

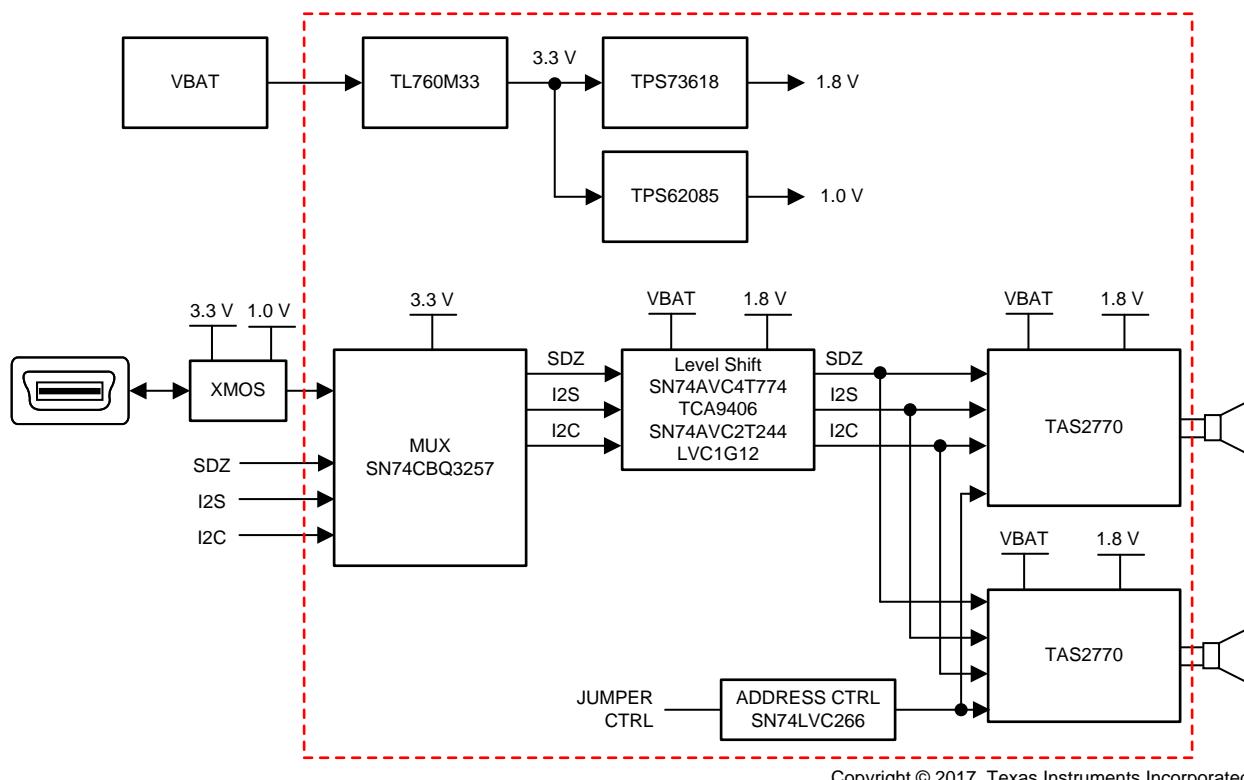

Copyright © 2017, Texas Instruments Incorporated

图 1. TIDA-01572 Block Diagram

2.2 Design Considerations

2.2.1 RJQ Layout

The quad-flatpack, no-lead (QFN) HotRod™ package allows for improved connections to the die by eliminating wire bonds by attaching the die directly to the lead frame. This configuration has better electrical and thermal characteristics than standard QFN packages, which improves the overall power delivery and audio performance. The leads in this package type are customizable to best suit the requirements of the device. However, due to the unique shape of the pads and relative pitch available in this package, some caution must be exercised to ensure proper installation. Due to the relative proximity, shape, and size of pins 1 and 26 and pins 9 and 10, pins may become shorted through a solder bridge if too much solder is used to attach the device. Leave some margin near the inner extremities of the pads where the spacing is tight to help eliminate this risk. For more details regarding the use of this package and layout best practices, see [HotRod QFN Package PCB Attachment Application Report](#). 图 2 shows an example layout. See the Gerber files in [Gerber Files](#).

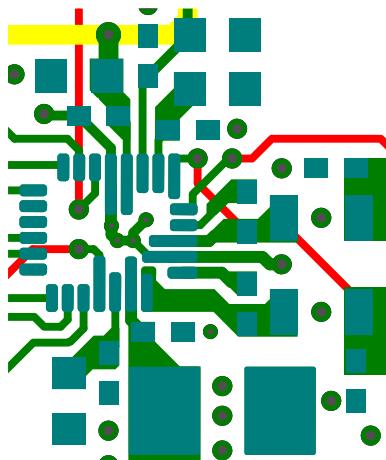


图 2. TIDA-01572 Reference Layout

Follow these guidelines during layout:

- Do not use vias for traces that carry high current. Such examples include the traces for VBAT, PGND, SPK_P, and SPK_M.
- Use epoxy-filled vias for the interior pads.
- Connect VSENSE+ and VSENSE- as close as possible to the speaker. VSENSE+ and VSENSE- must be connected between the electromagnetic interference (EMI) ferrite filter and the speaker if EMI ferrites are used on SPK_P and SPK_M.
- Use a ground plane with multiple vias for each terminal to create a low-impedance connection to GND for minimum ground noise.
- Use supply decoupling capacitors as shown in the schematics (see [Schematics](#)).
- If using EMI ferrites, place them close to the device.

2.2.2 Power

This device operates from a 4.5-V to 16-V VBAT supply where each channel is capable of driving a $4\text{-}\Omega$ load with up to 15 W. A barrel jack connection is available on this evaluation module (EVM) for convenience; however, when using this connection, note the importance of selecting a supply with an appropriate current limit for the desired power levels. This connection is ideal for use in portable demonstrations.

Screw-down terminals that can accommodate other supplies are also available. This terminal is ideal for lab testing while using a programmable bench top supply.

The onboard power supplies accept voltages within the specified operating range to generate 1-V, 1.8-V, and 3.3-V rails. These rails drive the various peripherals to the TAS2770 and drive the AVDD and IOVDD pins of the device.

2.2.3 Digital Audio Inputs

For ease of use, this design implements a USB controller to host I²S and I²C interfaces. When connected to a PC with PurePath™ Console 3 (PPC3) installed, a convenient and easy-to-use graphical user interface (GUI) is available to assist the user in configuring the device.

In addition, there is onboard multiplexing that allows the user to provide inputs for both of these buses from an external source. If desired, multiple boards may be connected together to create a four-, six-, or eight-channel configuration. The user can configure the TAS2770 device for ICLA, which allows each device that shares the same SDOUT data line to monitor the state of other channels. Devices that are programmed to monitor each other's limiter settings act together to provide consistent audio levels among all channels.

For more information, see [节 3.1.3.3.](#)

2.3 Highlighted Products

2.3.1 TAS2770

The TAS2770 is a mono, digital input Class-D audio amplifier optimized for efficiently driving high peak power into small loudspeakers. The Class-D amplifier is capable of delivering 14.2 W of peak power into a 4- Ω load while sustaining 11.6 W continuously with less than 0.03% THD+N at a battery voltage of 12.6 V.

Integrated speaker voltage and current sense allows for real-time monitoring of loudspeaker behavior. A battery-tracking, peak-voltage limiter with brownout prevention optimizes amplifier headroom over the entire charge cycle of 2S or 3S battery systems.

Up to eight devices can share a common bus using either I²S or test data management (TDM) + I²C.

The TAS2770 device is available in a 26-pin, 0.4-mm pitch QFN for a compact printed-circuit board (PCB) footprint.

2.3.2 TL760M33

The TL760 is an integrated linear-voltage regulator featuring operation from an input as high as 30 V. The TLV760 has a maximum dropout of 1.2 V at the full 100-mA load across the operating temperature. Standard packaging for the TLV760 is the three-pin, SOT-23 package.

The TL760 is available in 3.3 V, 5 V, 12 V, and 15 V. The SOT-23 packaging of the TL760 series allows the device to be used in space-constrained applications. The TL760 is a small-size alternative to the LM78Lxx series and similar devices. This application uses the 3.3-V version of this device.

The TL760 is designed to bias digital and analog circuits in applications that are subject to voltage transients and spikes up to 30 V—for example, appliances and automation applications. The device has robust internal thermal protection, which protects itself from potential damage caused by conditions like short to ground, increases in ambient temperature, high load, or high dropout events.

2.3.3 TPS73618

The TPS736xx family of LDO linear voltage regulators uses a new topology—an NMOS pass element in a voltage-follower configuration. This topology is stable using output capacitors with low equivalent series resistance (ESR) and allows operation without a capacitor. The topology also provides high reverse blockage (low reverse current) and ground-pin current that is nearly constant over all values of output current.

The TPS736xx uses an advanced BiCMOS process to yield high precision while delivering low dropout voltages and low ground-pin current. Current consumption, when not enabled, is under 1 μ A and ideal for portable applications. The low output noise (30 μ V_{RMS} with 0.1- μ F CNR) is ideal for powering voltage-controlled oscillators (VCOs). These devices are protected by a thermal shutdown and foldback current limit.

The TPS73618 generates a 1.8-V supply in this application to provide AVDD and IOVDD.

2.3.4 TPS62085

The TPS62085 device is a high-frequency synchronous step-down converter optimized for a small solution size and high efficiency. With an input voltage range of 2.5 V to 6 V, this device supports common battery technologies. The device focuses on high-efficiency step-down conversion over a wide output current range. At medium-to-heavy loads, the converter operates in pulse-width modulation (PWM) mode and automatically enters power save mode operation at light load to maintain high efficiency over the entire load current range.

To address the requirements of system power rails, the internal compensation circuit allows a large selection of external output capacitor values ranging from 10 μ F to 150 μ F. Together with DCS-Control architecture, excellent load transient performance and output voltage regulation accuracy are achieved. The device is available in a 2-mm \times 2-mm QFN package.

2.4 System Design Theory

TAS2770 is a mono, digital input Class-D amplifier. To achieve stereo or higher channel-count configurations, multiple devices can share the I²S data bus to provide ICLA. This design pairs two units to accomplish the stereo application, but the designer may pair multiple boards to create four-, six-, or eight-channel solutions.

The VBAT supply range of TAS2770 pairs well into the PC and notebook space. The built-in limiter helps with battery tracking to automatically adjust gain to keep the outputs within the user-specified limits. When ICLA is implemented, the paired devices respond to changes in each other's gain settings to provide balanced control while smoothly adjusting to stay within the operating limits of the battery supply.

This design is intended to accommodate uses for evaluating performance in a controlled environment and to easily provide access to audio streaming over USB. The design also allows the user to drive the inputs from an audio analyzer or other system with accessible I²S or I²C signals.

Suitable onboard power is also provided to simply integration and testing. The user is only required to provide a VBAT voltage in the range of 4.5 V to 16 V.

3 Hardware, Software, Testing Requirements, and Test Results

3.1 Required Hardware and Software

3.1.1 Hardware

- TAS2770EVM stereo board
- 4.5-V to 16-V wired DC bench top supply or barrel jack
- Speakers rated at or above expected output power
- USB-A to USB-B micro cord

3.1.2 Software

- PurePath Console 3 (PPC3)—available from [MySecureSoftware](#)
- TAS2770 PPC3 App—downloaded within PPC3
- Media player

3.1.3 User Configuration

3.1.3.1 Stereo Setup

1. Install PurePath Console 3 with the TAS2770EVM-STEREO plug-in.
2. Connect the first speaker to J10 on the EVM. Alternatively, J23 and J24 can be used for speaker connections.
3. Connect a second speaker to J29 on the EVM. Alternatively, J28 and J30 can be used for speaker connections (see [图 3](#)).
4. Attach a power supply to connector J9. There is also an alternate barrel jack connector (J19) adjacent to this connector.
5. Set jumper J13 to select the desired I²C address for channel 1.
6. Set jumper J31 to select the desired I²C address for channel 2.
7. Connect the EVM to a Windows® 7+ PC with a micro-USB cable (J16).

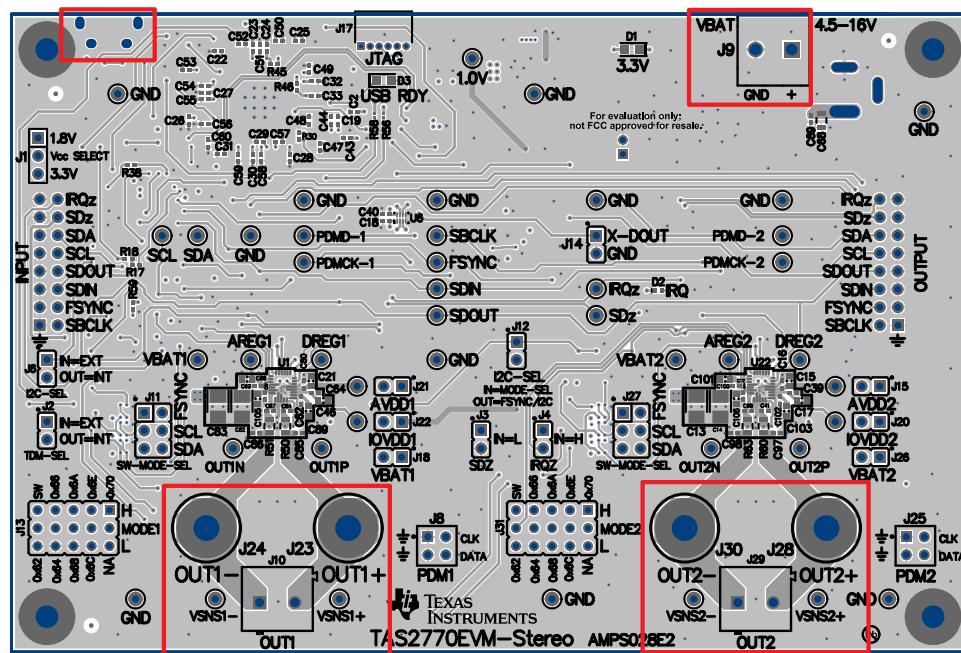


图 3. TAS2770EVM-STEREO Stereo Configuration

8. Verify that the EVM is the default playback device by opening the sound dialog from the Windows Control Panel (see [图 4](#)).

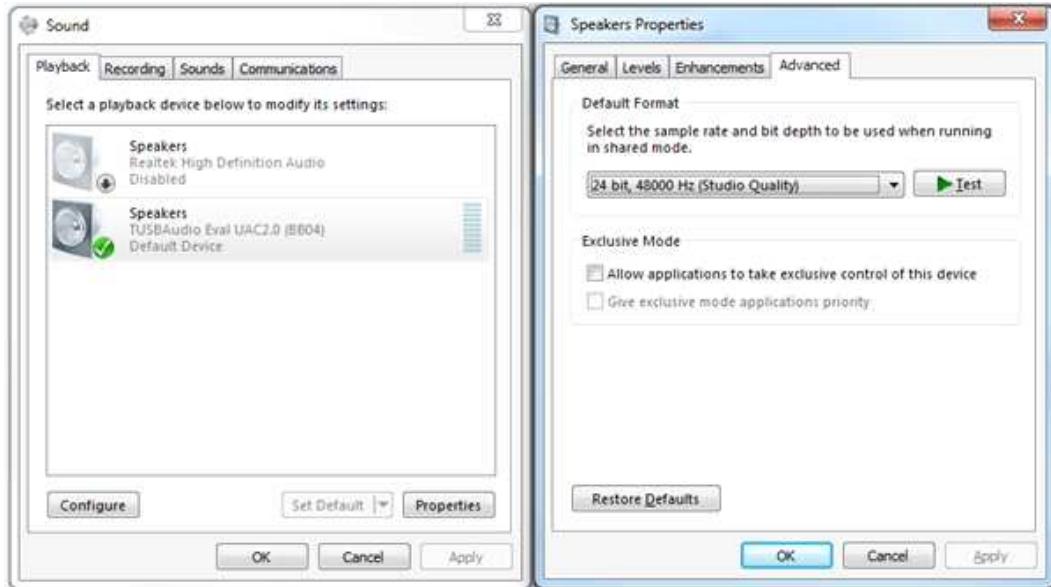


图 4. Playback Device Settings

9. Set the sampling rate using the Windows setting by opening *Properties* → *Advanced*. The TAS2770EVM-STEREO supports 44.1-KHz and 48-KHz sampling rates.
10. Set the bit depth as desired using the *Texas Instruments Audio Control Panel*, which is accessible from the system tray shown in [图 5](#).
11. Proceed to configure the device using PPC3.

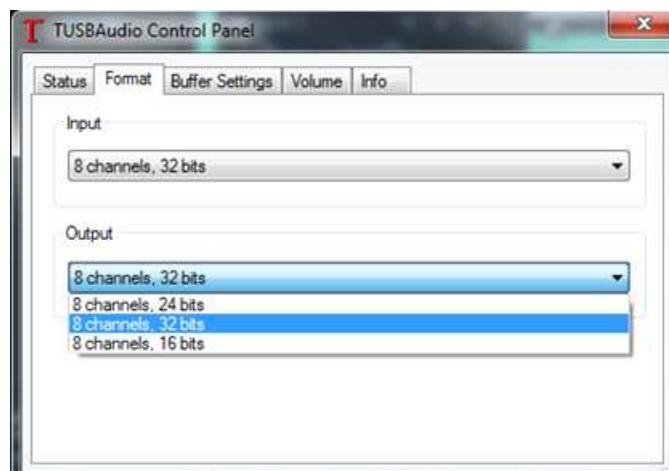


图 5. Texas Instruments Audio Control Panel

3.1.3.2 Mono Setup

1. Install PurePath Console 3 with the TAS2770EVM-STEREO plug-in.
 2. Connect the first speaker to J10 on the EVM (see [图 6](#)). Alternatively, J23 and J24 can be used for speaker connections.
 3. Attach a power supply to connector J9. There is also an alternate barrel jack connector (J19) adjacent to this connector.
 4. Set jumper J13 to select the desired I²C address for channel 1.
 5. Connect the EVM to a Windows 7+ PC with a micro-USB cable (J16).

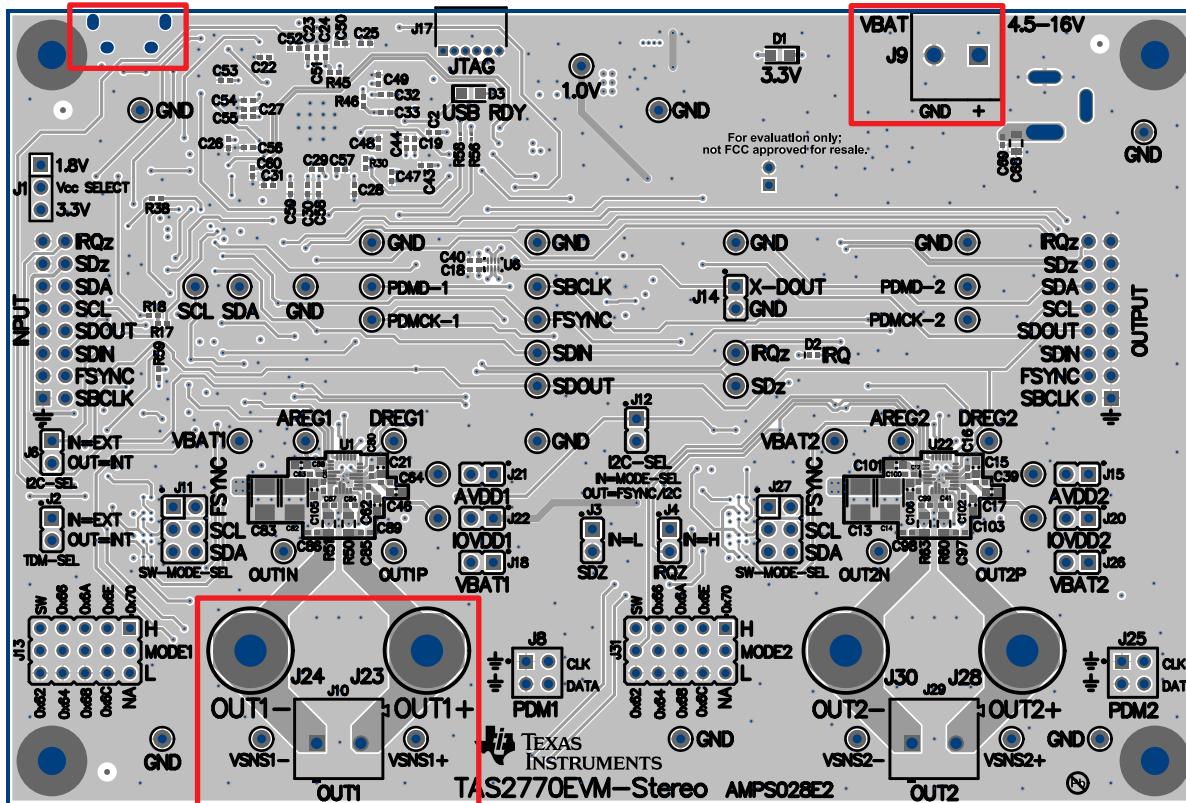


图 6. TAS2770EVM-STEREO Mono Configuration

6. Verify that the EVM is the default playback device by opening the sound dialog from the Windows Control Panel, as shown in [图 4](#).
 7. Set the sampling rate using the Windows setting by opening *Properties* → *Advanced*. The TAS2770EVM-STEREO supports 44.1-KHz and 48-KHz sampling rates.
 8. Set the bit depth as desired using the Texas Instruments Audio Control Panel accessible from the system tray shown in [图 5](#).
 9. Proceed to configure the device using PPC3.

3.1.3.3 Multichannel Setup

1. Install PurePath Console 3 with the TAS2770EVM-STEREO plug-in
2. Connect up to four TAS2770EVM-STEREOs together using connectors J5 and J7 (see 图 7).
3. Attach a power supply to each board.
4. The left-most board must have jumpers set to match the stereo configuration. On all other boards, insert a jumper on J2 and J6 (see 图 7 for details).
5. Set jumpers J13 and J31 on each board to a unique address.
6. Configure the sampling rate and bit depth as discussed in 节 3.1.3.2 steps six through eight.
7. Proceed to configure the device using PPC3.
8. Connect the left-most EVM to a Windows 7+ PC with a micro-USB cable (J16).

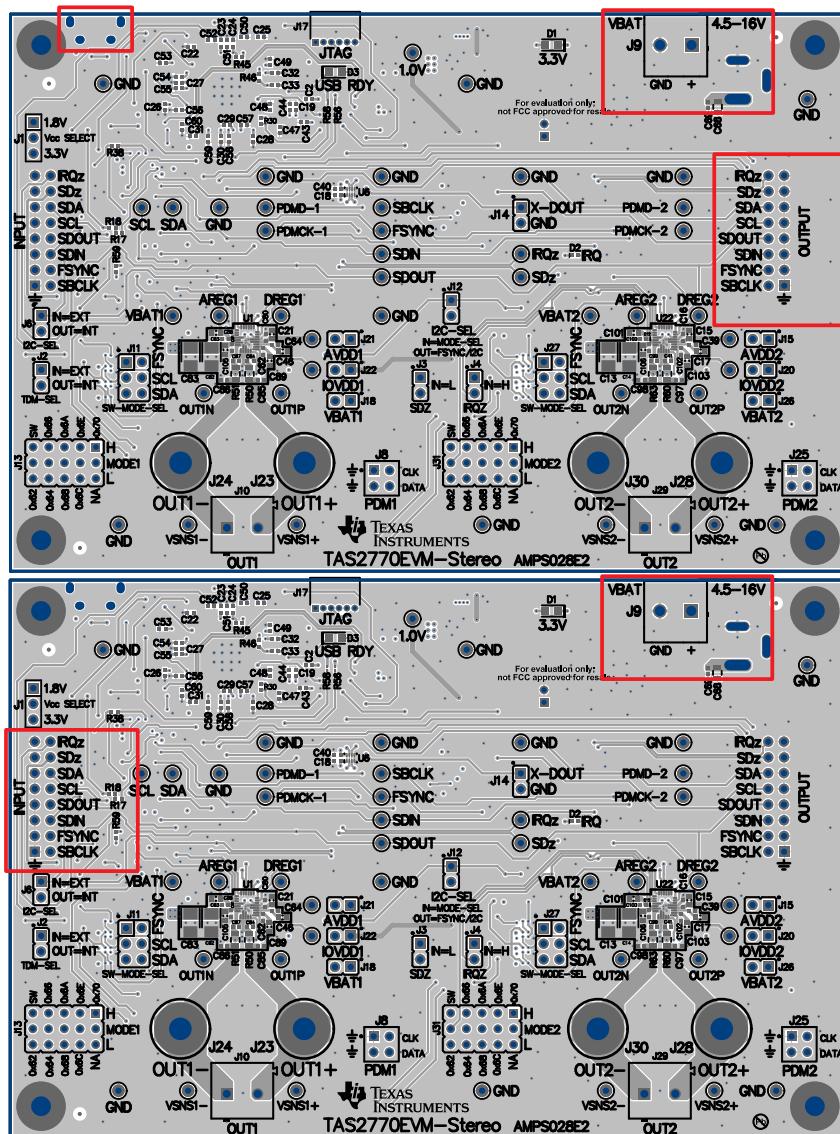


图 7. Multichannel Setup

3.1.3.4 Digital Audio Interfaces

The various digital audio interfaces on the TAS2770 reference board can be selected through hardware settings and software settings. Several headers close to the TAS2770 device allow access to the following digital audio signals:

- I²S Data Out (SDOUT) from the TAS2770 (for example, current and voltage sense data)
- I²S Data In (SDIN) to the TAS2770
- I²S Word Clock or frame sync (FSYNC)
- I²S Bit Clock (SBCLK)
- PDM Clock (PDMCLK0)—Optional input source for TAS2770
- PDM Clock (PDMCLK1)—Optional input source for TAS2770
- PDM Data (PDMD0)—Optional input source for TAS2770
- PDM Data (PDMD1)—Optional input source for TAS2770
- I²C Clock (SCLK)
- I²C Data (SDA)

TAS2770 can be configured for SoundWire mode:

- SoundwireSM clock—SBCLK
- SoundwireSM data—SDOUT
- SoundwireSM address—SDA
- SoundwireSM address—FSYNC
- SoundwireSM address—SCL

A jumper inserted in the SW slot of J13 sets the TAS2770 device to SoundWire mode. Then, the designer can set J11 as desired to configure the device address.

Jumpers J2 and J6 control the selection between the USB (internal) and external inputs. These jumpers set the TDM and I²C, respectively.

3.1.3.4.1 Digital Audio Interface Selection

3.1.3.4.1.1 USB

The TAS2770 reference board contains an XMOS microcontroller (MCU) that acts as a USB human interface device (HID) and USB-class audio interface. To select USB, remove jumpers J6 and J2. Insert a jumper in J12.

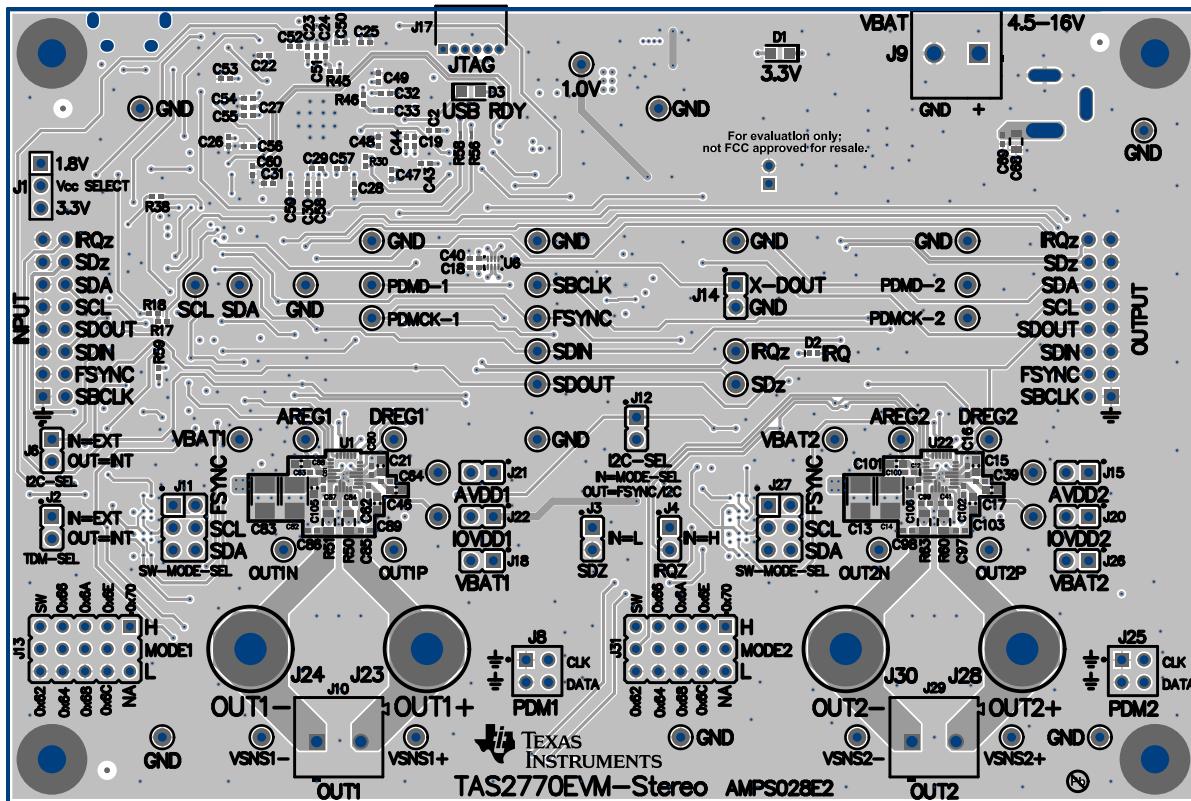


图 8. USB Audio Input Configuration

3.1.3.4.1.2 Direct (AP/PSIA)

Insert a jumper on J2 and connect the external digital audio source (for example AP or PSIA) to the external input header pin. The odd-numbered pins on this header provide a ground for each signal. 图 9 shows this configuration. Note that the jumper setting for J1 must reflect the logic level of the external source.

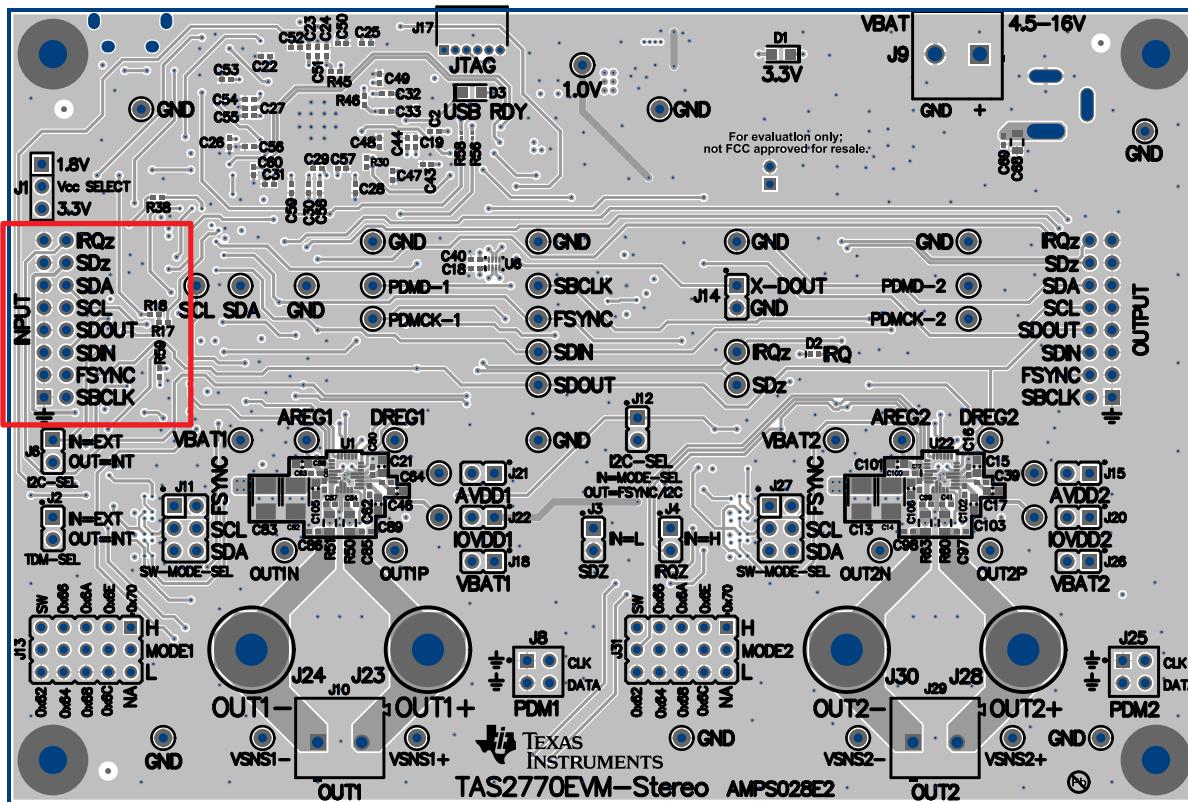


图 9. AP/PSIA Input Configuration

3.2 Testing and Results

3.2.1 Test Setup

Stereo audio for PC design testing was carried out using the TAS2770EVM-STEREO configured for external I²S inputs while using I²C inputs controlled over USB and the PPC3 audio.

Acoustic tests were performed using 8-Ω compatible speakers with a recommended operating power of 25 W at a distance of 1 m.

Electrical tests were performed using an Audio Precision® 2700 series analyzer with the accompanying AUX-0025 passive filter. The TAS2770 was loaded with an 8-Ω resistor in series with 33-μH inductance to emulate a real speaker. All typical characteristics for the devices are measured using the bench EVM and an Audio Precision SYS-2722 Audio Analyzer. A PSIA interface allows the I²S interface to be driven directly into the SYS-2722. The SPEAKER OUT terminal is connected to the Audio Precision Analyzer inputs as shown in [图 10](#). A differential to single-ended (D2S) filter with a first-order passive pole at 120 kHz is added. This addition ensures that the high-performance Class-D amplifier detects a fully-differential-matched loading at its outputs and while detecting no measurable degradation in performance due to the loading effects of the AUX filter on the Class-D outputs.

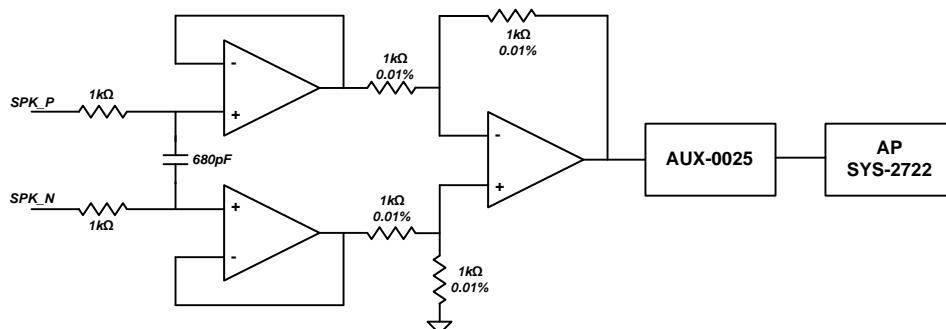


图 10. Differential to Single-Ended (D2S) Filter

The design was powered using an Agilent® bench top supply set to 16 V. Current measurements were taken using an Agilent digital multimeter.

3.2.2 Test Results

3.2.2.1 Power Consumption


表 2. TIDA-01572 Power Consumption

PARAMETER	CONDITIONS	SUPPLY	VALUE	UNITS
TAS2770 EVM-Stereo current consumption	Hardware shutdown	EVM supply	178	mA
	Software shutdown		180	
	Idle channel		208	

表 2. TIDA-01572 Power Consumption (continued)

PARAMETER	CONDITIONS	SUPPLY	VALUE	UNITS
TAS2770 current consumption	Hardware shutdown	VBAT	0.2	μA
		AVDD	0.1	
		IOVDD	0.1	
	Software shutdown	VBAT	0.5	μA
		AVDD	9.1	
		IOVDD	0.1	
	Idle channel	VBAT	5.25	mA
		AVDD	9.72	
		IOVDD	8.9	μA

3.2.2.2 Amplifier Performance

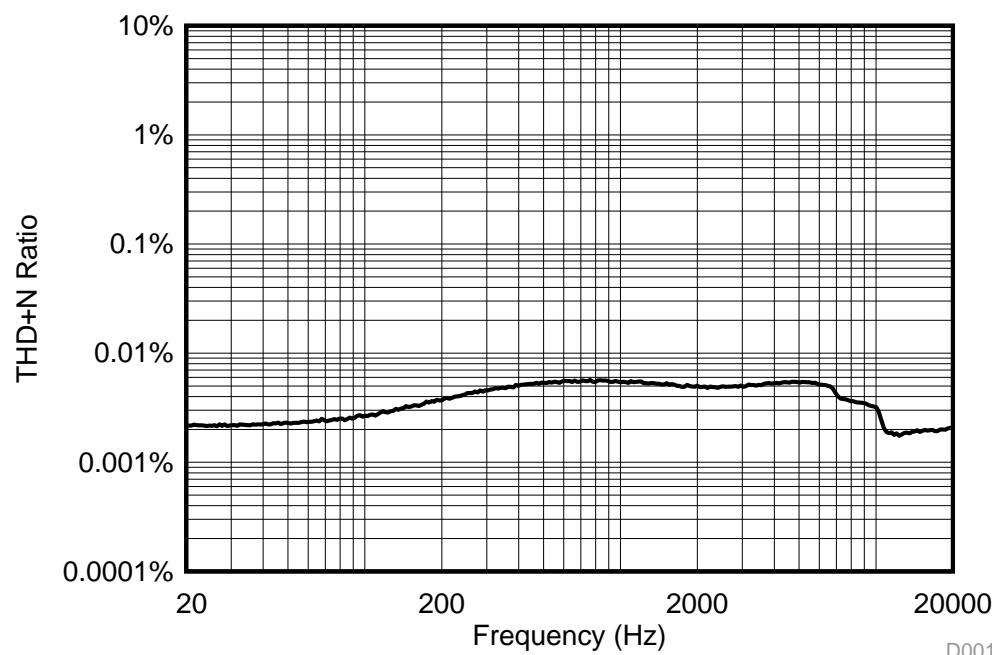
图 11. TIDA-01572 THD+N versus Frequency at 1 W, VBAT = 12 V

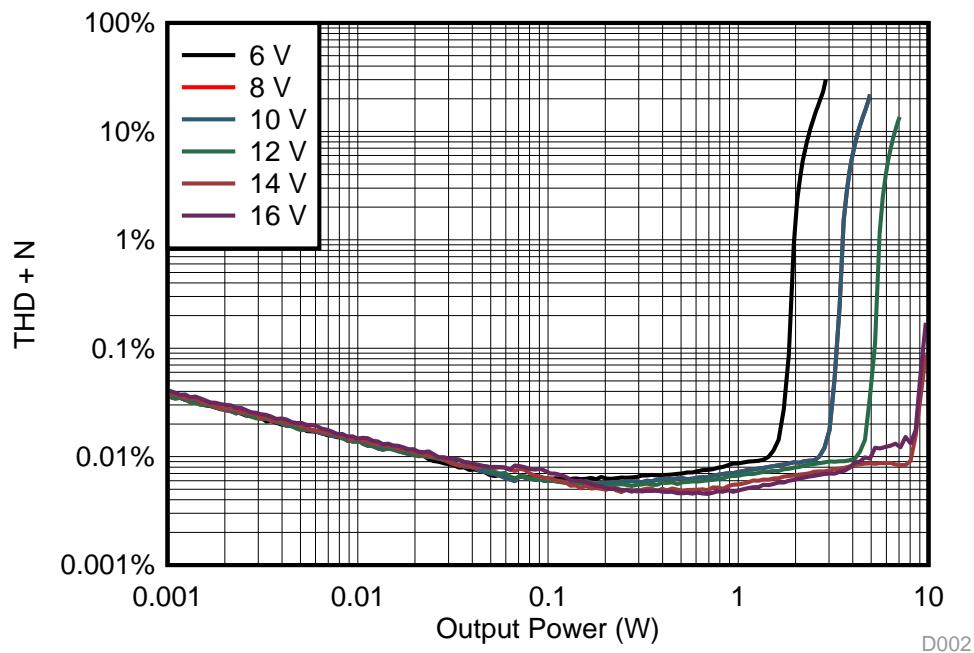


图 12. TIDA-01572 THD+N versus Output Power at 1 kHz

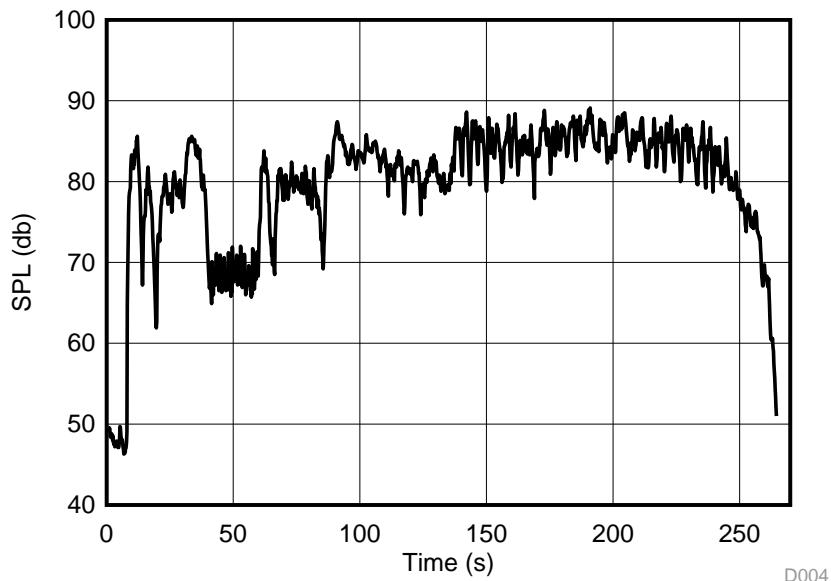


图 13. TIDA-01572 SPL at 1 m, VBAT = 12 V, While Playing Music

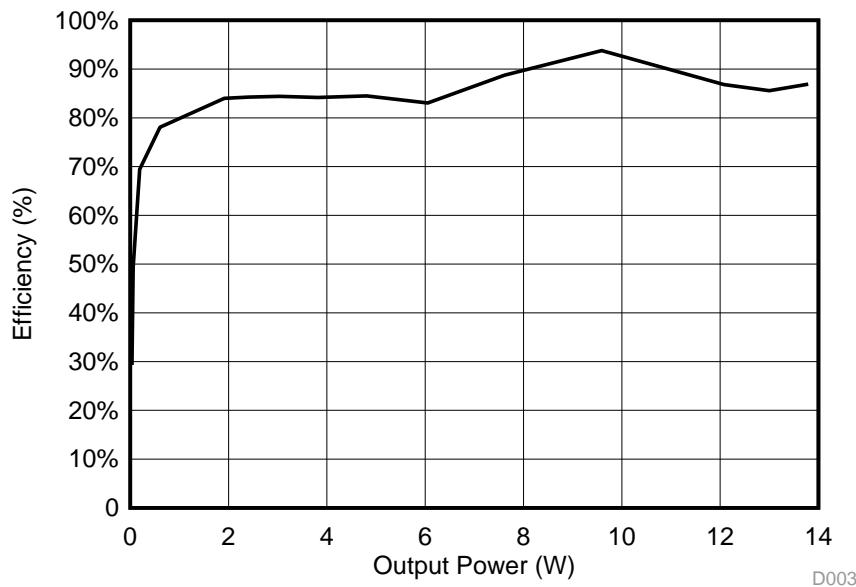


图 14. TIDA-01572 Power Efficiency, VBAT = 16 V



图 15. Idle Channel Noise, VBAT = 12 V ⁽¹⁾

⁽¹⁾ The final, correct measurement is 35.48 μ V; however the test circuit divides this value in half. Note that a value of 17.74 μ V is too low.

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [TIDA-01572](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01572](#).

4.3 PCB Layout Recommendations

4.3.1 Layout Prints

4.3.1.1 TAS2770 Reference Board PCB Layout

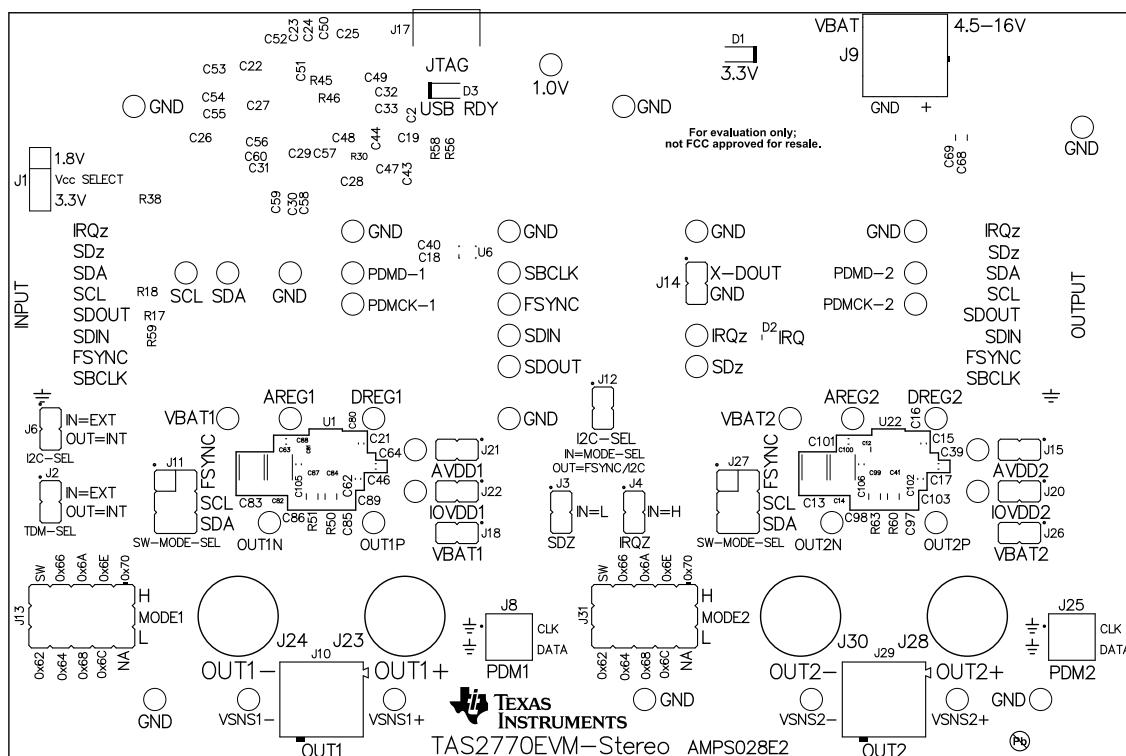


图 16. PCB: Top Silkscreen

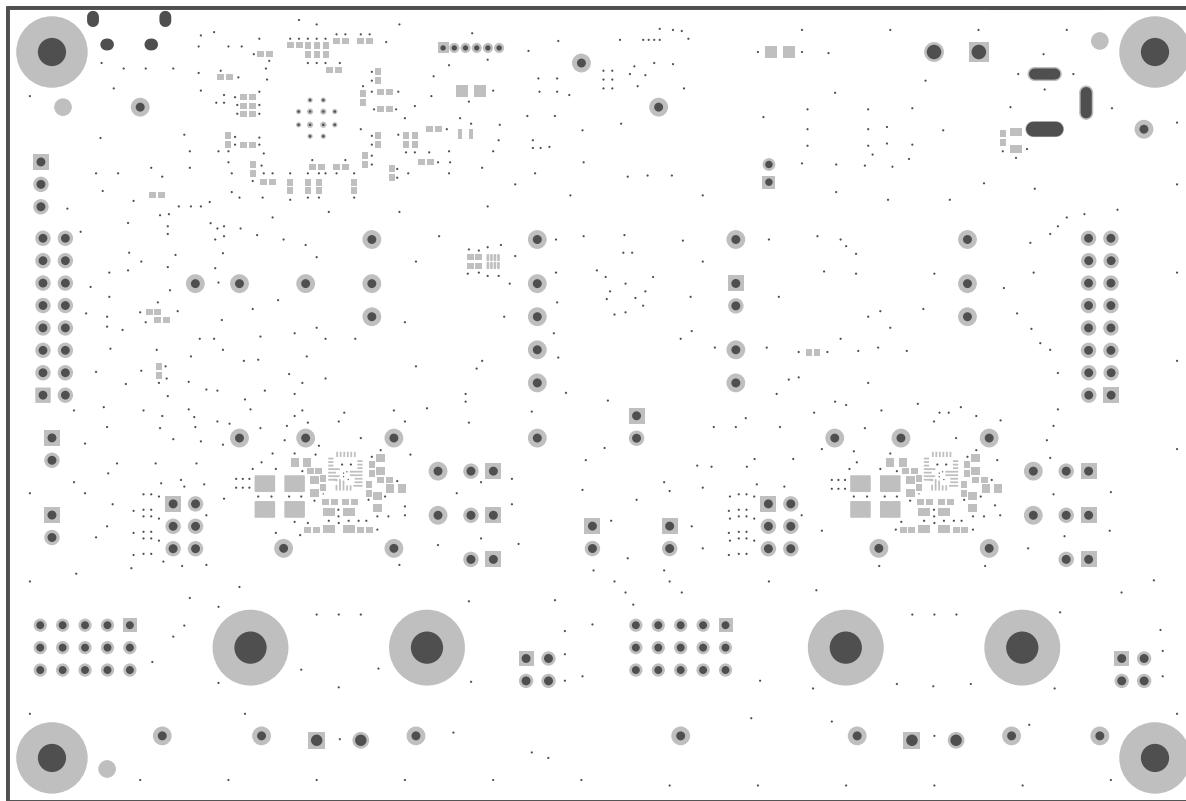


图 17. PCB: Top Solder Mask

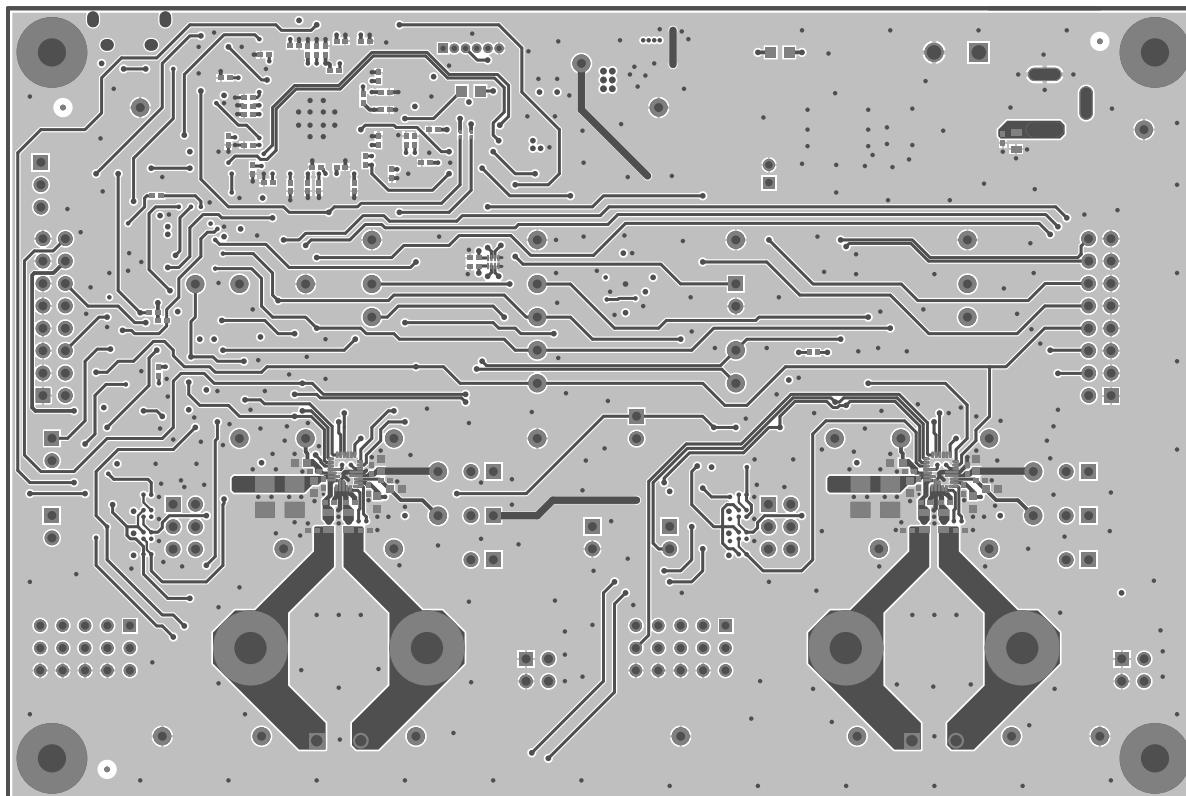


图 18. PCB: Top Copper

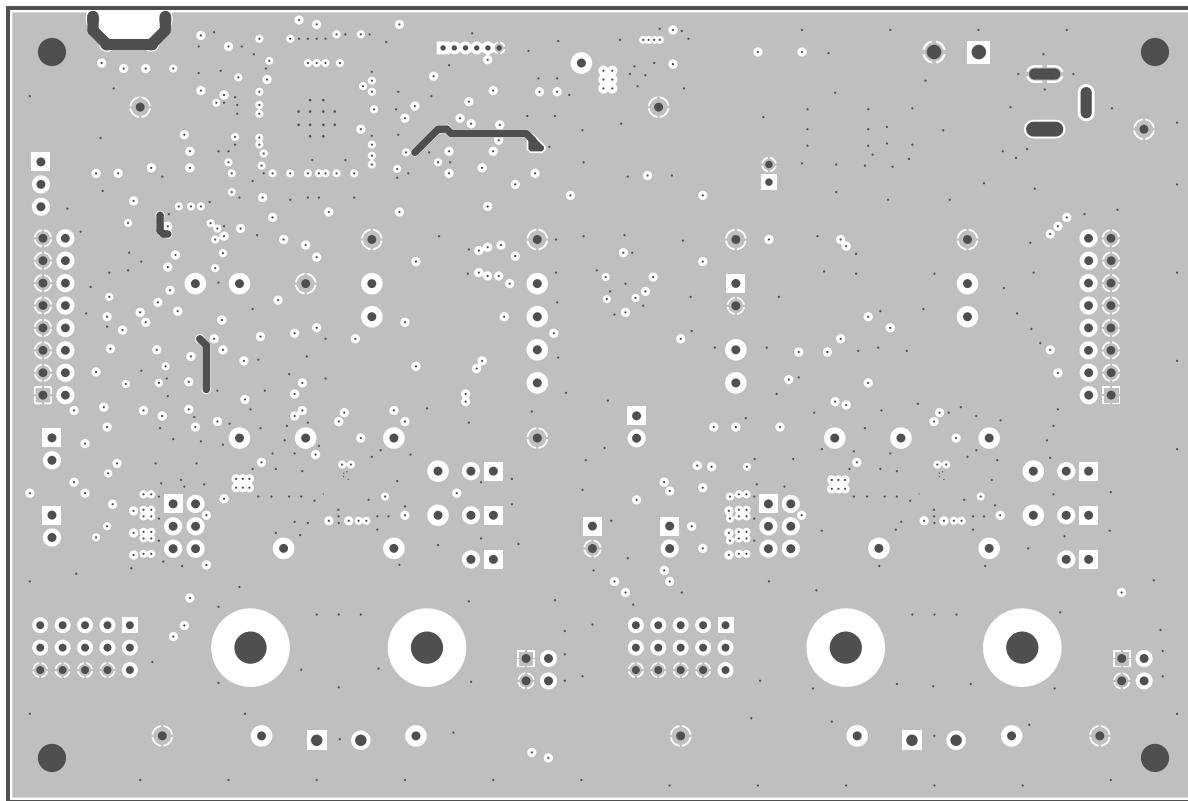


图 19. PCB: Copper Layer 2

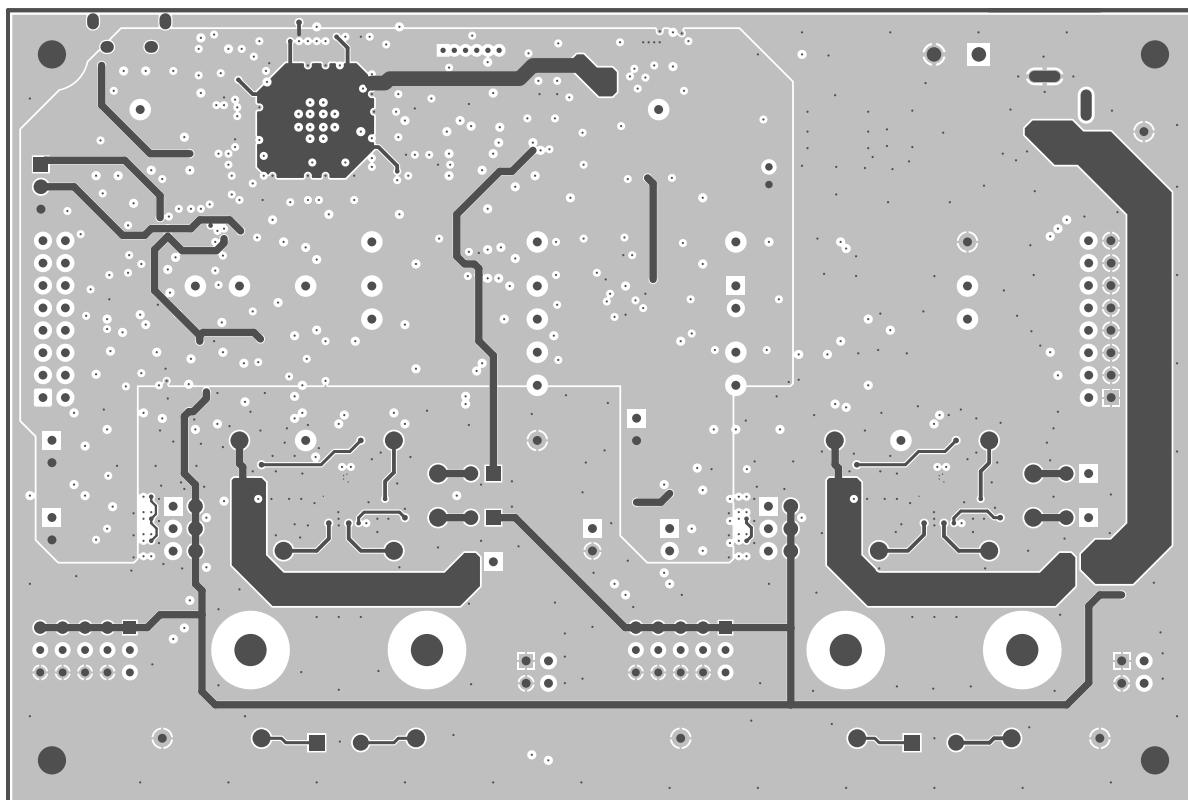


图 20. PCB: Copper Layer 3

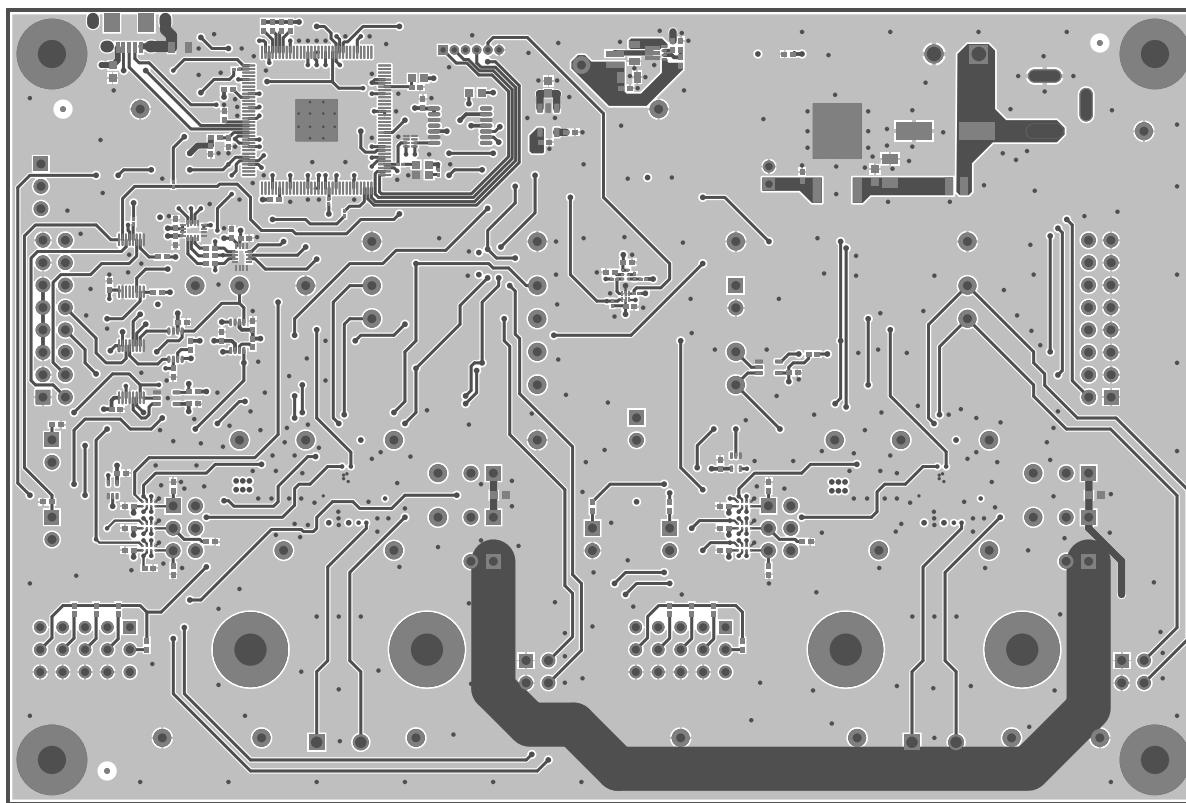


图 21. PCB: Bottom Copper

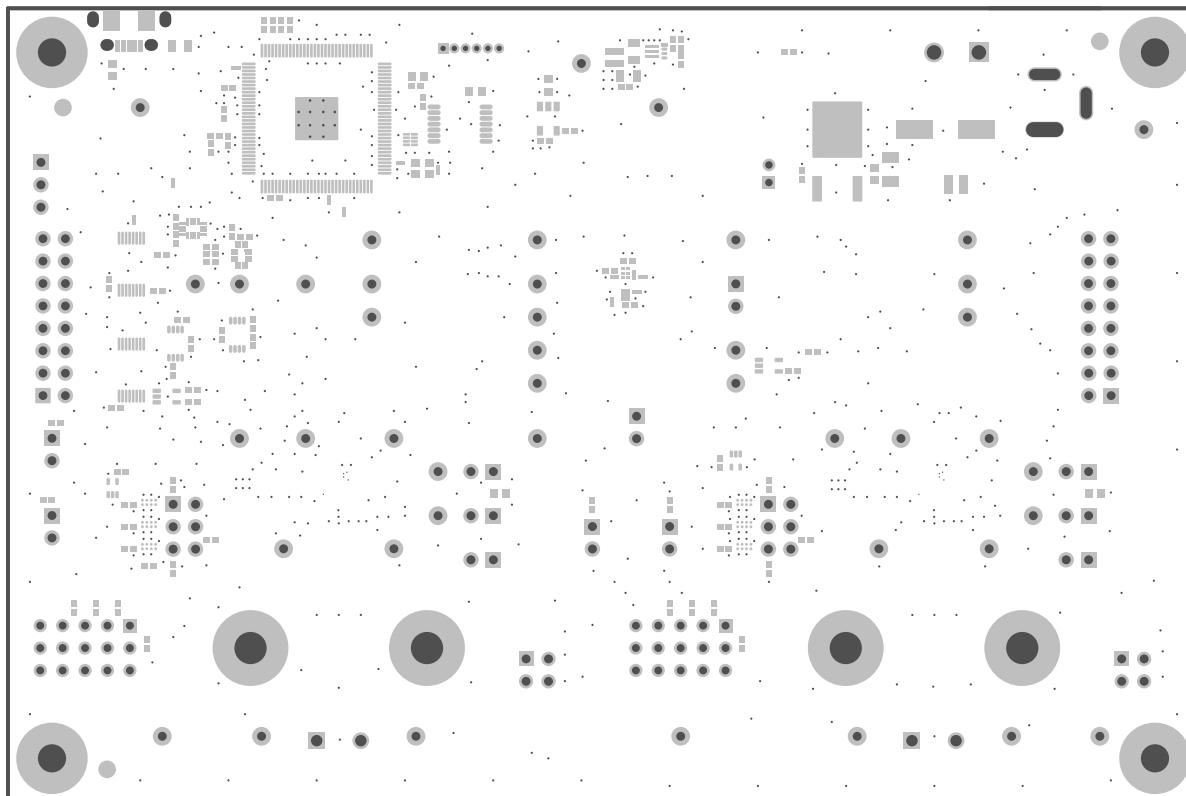


图 22. PCB: Bottom Solder Mask

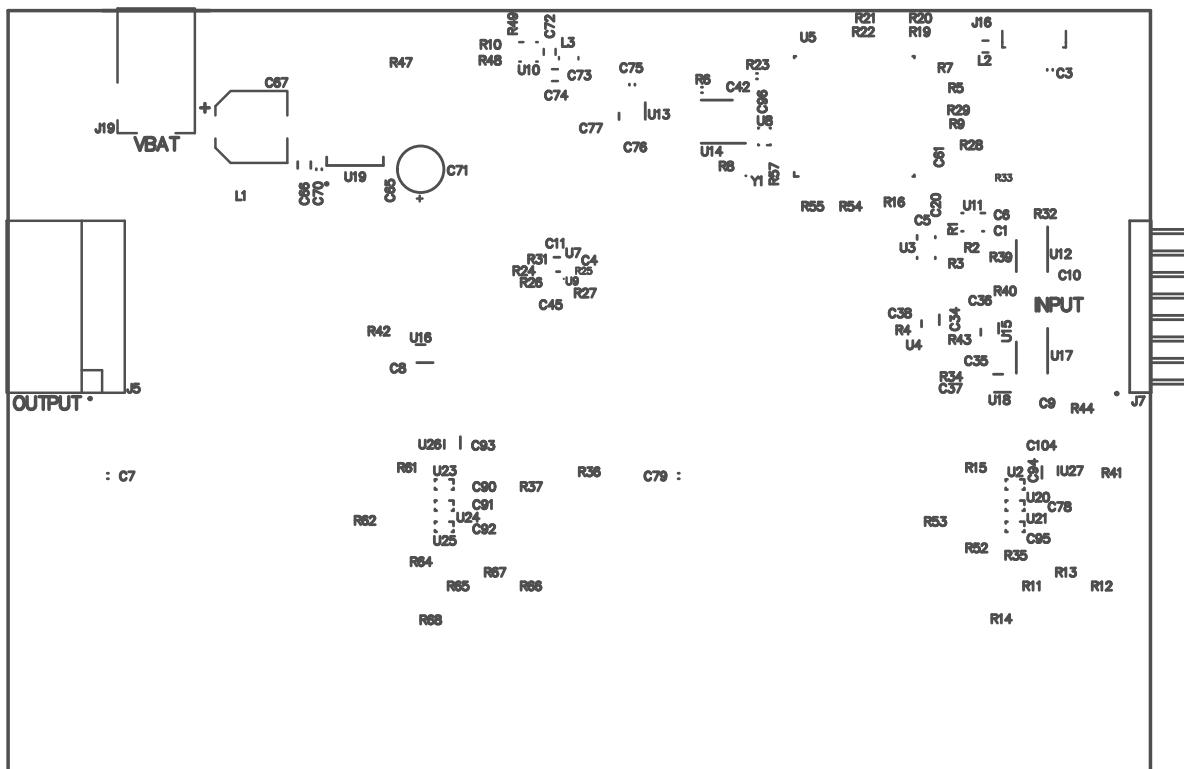


图 23. PCB: Bottom Silk Screen

To download the layer plots, see the design files at [TIDA-01572](#).

4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01572](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01572](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01572](#).

5 Software Files

To access to the TAS2770 PPC3 App, please submit a request to [MySecureSoftware](#).

6 Related Documentation

1. Texas Instruments, [HotRod QFN Package PCB Attachment Application Report](#)

6.1 商标

E2E, PurePath, HotRod are trademarks of Texas Instruments.
Agilent is a registered trademark of Agilent Technologies, Inc.
Audio Precision is a registered trademark of Audio Precision, Inc.
SoundWire is a trademark of MIPI Alliance, Inc.
Windows is a registered trademark of Microsoft Corporation.
All other trademarks are the property of their respective owners.

有关 TI 设计信息和资源的重要通知

德州仪器 (TI) 公司提供的技术、应用或其他设计建议、服务或信息，包括但不限于与评估模块有关的参考设计和材料（总称“TI 资源”），旨在帮助设计人员开发整合了 TI 产品的应用；如果您（个人，或如果是代表贵公司，则为贵公司）以任何方式下载、访问或使用了任何特定的 TI 资源，即表示贵方同意仅为该等目标，按照本通知的条款进行使用。

TI 所提供的 TI 资源，并未扩大或以其他方式修改 TI 对 TI 产品的公开适用的质保及质保免责声明；也未导致 TI 承担任何额外的义务或责任。TI 有权对其 TI 资源进行纠正、增强、改进和其他修改。

您理解并同意，在设计应用时应自行实施独立的分析、评价和判断，且应全权负责并确保应用的安全性，以及您的应用（包括应用中使用的所有 TI 产品）应符合所有适用的法律法规及其他相关要求。你就您的应用声明，您具备制订和实施下列保障措施所需的一切必要专业知识，能够（1）预见故障的危险后果，（2）监视故障及其后果，以及（3）降低可能导致危险的故障几率并采取适当措施。您同意，在使用或分发包含 TI 产品的任何应用前，您将彻底测试该等应用和该等应用所用 TI 产品的功能而设计。除特定 TI 资源的公开文档中明确列出的测试外，TI 未进行任何其他测试。

您只有在为开发包含该等 TI 资源所列 TI 产品的应用时，才被授权使用、复制和修改任何相关单项 TI 资源。但并未依据禁止反言原则或其他法理授予您任何 TI 知识产权的任何其他明示或默示的许可，也未授予您 TI 或第三方的任何技术或知识产权的许可，该等产权包括但不限于任何专利权、版权、屏蔽作品权或与使用 TI 产品或服务的任何整合、机器制作、流程相关的其他知识产权。涉及或参考了第三方产品或服务的信息不构成使用此类产品或服务的许可或与其相关的保证或认可。使用 TI 资源可能需要您向第三方获得对该等第三方专利或其他知识产权的许可。

TI 资源系“按原样”提供。TI 兹免除对 TI 资源及其使用作出所有其他明确或默认的保证或陈述，包括但不限于对准确性或完整性、产权保证、无屡发故障保证，以及适销性、适合特定用途和不侵犯任何第三方知识产权的任何默认保证。

TI 不负责任何申索，包括但不限于因组合产品所致或与之有关的申索，也不为您辩护或赔偿，即使该等产品组合已列于 TI 资源或其他地方。对因 TI 资源或其使用引起或与之有关的任何实际的、直接的、特殊的、附带的、间接的、惩罚性的、偶发的、从属或惩戒性损害赔偿，不管 TI 是否获悉可能会产生上述损害赔偿，TI 概不负责。

您同意向 TI 及其代表全额赔偿因您不遵守本通知条款和条件而引起的任何损害、费用、损失和/或责任。

本通知适用于 TI 资源。另有其他条款适用于某些类型的材料、TI 产品和服务的使用和采购。这些条款包括但不限于适用于 TI 的半导体产品 (<http://www.ti.com/sc/docs/stdterms.htm>)、**评估模块** 和样品 (<http://www.ti.com/sc/docs/samptersms.htm>) 的标准条款。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122
Copyright © 2018 德州仪器半导体技术（上海）有限公司