



## 说明

该参考设计可以为采用 LiSOCl2 电池的智能仪表应用中的 NB-IoT（窄带物联网）提供电源解决方案。该设计是一款高效的低待机电流解决方案，可将电池使用时间延长 50% 以上。

## 资源

TIDA-050010

TPS61099

LMC555

CSD18533KCS

设计文件夹

产品文件夹

产品文件夹

产品文件夹





咨询我们的 E2E™ 专家

## 特性

- 工作输入电压范围：2V 至 4V
- 3.6V 固定输出电压
- 高达 320mA 的输出电流
- 在轻负载情况下具有  $1\mu A$  的静态电流
- 在开路负载情况下且温度为 85°C 时具有约  $4\mu A$  的待机电流
- 在 10mA 至 320mA 负载下具有高达 93% 的效率
- 具有宽输入电压范围和高效率，从而延长电池寿命
- 可模拟窄带物联网负载特性，以便轻松进行测试
- 外部组件数量较少，可实现小解决方案尺寸

## 应用

- 燃气表
- 热量计
- 水表

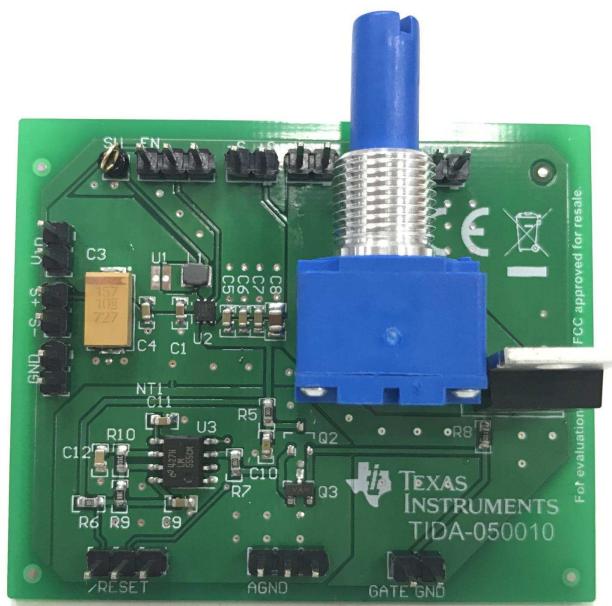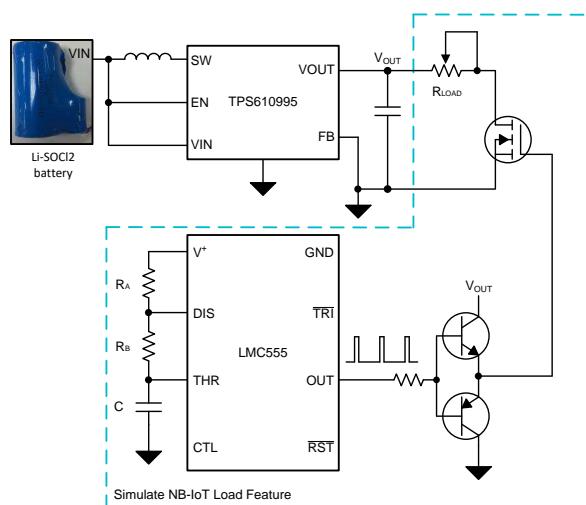

该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。


## 1 System Description

Smart meters consists of electricity meters, gas meters, heat meters and water meters. Some smart meters use NarrowBand-Internet of Things (NB-IoT) to transfer data and information. This technology supports battery life of more than 10 years for a wide range of use cases. The typical range of input voltage of NB-IoT modules (such as the ZTE ZM8300G module) is from 3 V to 4.2 V (with a typical voltage 3.6 V). The typical maximum peak current for these modules is up to 300 m A.

The Li-SOCl<sub>2</sub> battery currently has the highest energy density, the longest storage period, and the least self-discharge rate (less than 1% per year at room temperature). This battery is very useful for smart meters including e-meters, water meters, and trackers, which are long-term products. The typical voltage of a Li-SOCl<sub>2</sub> battery is approximately 3 to 3.6 V, and the maximum continuous output current is approximately 150 mA for an 8.5-Ah battery. Because the continuous output current of a Li-SOCl<sub>2</sub> battery is not enough for NB-IoT, a super capacitor is connected with Li-SOCl<sub>2</sub> battery in parallel to provide a pulse high current.

图 1 shows the voltage curves for a Li-SOCl<sub>2</sub> battery (3.67 V) in parallel with super capacitor (SPC1520) with a discharge current is 350 mA. At low ambient temperature, the output voltage of the Li-SOCl<sub>2</sub> battery is less than 3 V. The NB-IoT module connected directly to a Li-SOCl<sub>2</sub> battery stops working even though a large capacity (about 2/3 capacity at -20°C) is still available, so a boost converter is needed. The TPS610995 can boost the battery voltage to 3.6 V to give a steady power to NB-IoT module.

**图 1. Voltage Curves for Li-SOCl<sub>2</sub> Battery (3.67 V) In Parallel With Super Capacitor, 350 mA**

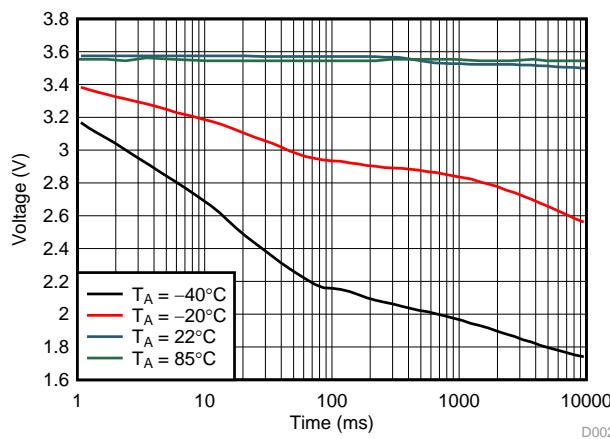

(1) See the [EVE SPC \(Super Pulse Capacitor cell\) Model SPC1520.data sheet](#), for more information.

### 1.1 Key System Specifications

**表 1. Key System Specifications**


| PARAMETER  | SPECIFICATIONS             |
|--|----------------------------|
| Input voltage range                              | 2 V to 4 V                 |
| Output voltage                                   | 3.6 V                      |
| Output current                                   | up to 320 mA               |
| No load input current ( $V_{in}$ = 3 V)          | 1 $\mu$ A                  |
| Efficiency ( $V_{in}$ = 3 V, $I_{out}$ = 300 mA) | 94 %                       |
| Monitor load range                               | 2 $\Omega$ to 1 k $\Omega$ |

## 2 System Overview

### 2.1 Block Diagram

图 2 shows the system block diagram. This system has two parts. One is the TPS610995 boost converter to boost the Li-SOCl2 battery to 3.6 V, the other part is simulate NB-IoT load feature.

**图 2. TIDA-050010 Block Diagram**

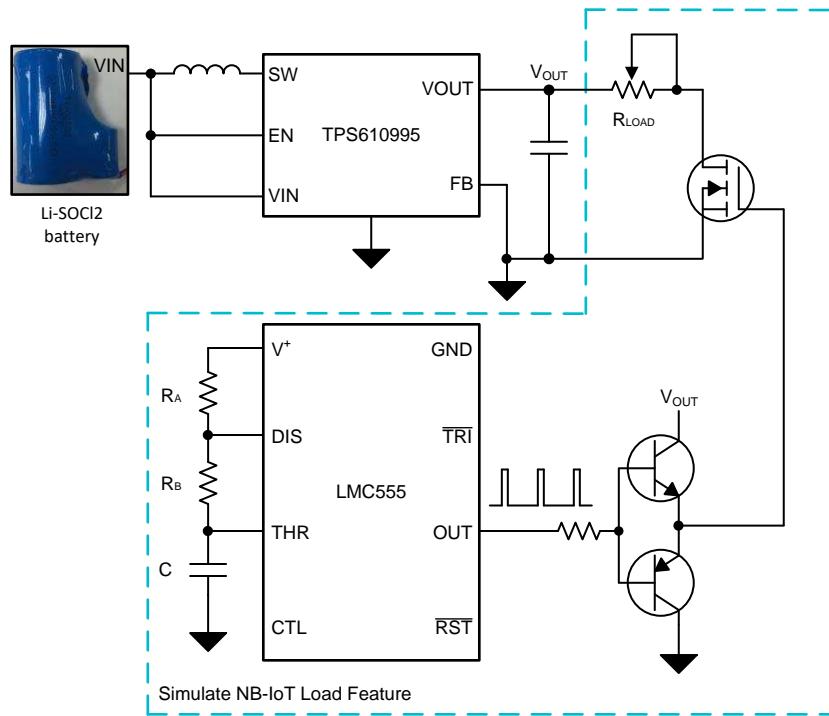

### 2.2 Design Considerations

#### 2.2.1 Load Monitor

This reference design uses the LMC555 device to generate a pulse that drives a MOSFET to monitor the NB-IoT load feature. Users can change the resistance by sliding the rheostat (R<sub>LOAD</sub>) to change the peak output current.

Use 公式 1 to calculate the pulse width of the output load current of the LMC555 device.

$$t_{on} = 0.693 \times (R_A + R_B) \times C = 0.693 \times (1\text{ k}\Omega + 23.2\text{ k}\Omega) \times 10\text{ }\mu\text{F} = 167\text{ ms} \quad (1)$$

Use 公式 2 to calculate the frequency of the output load current of the LMC555 device.

$$f = \frac{1.44}{(R_A + 2 \times R_B) \times C} = \frac{1.44}{(1\text{ k}\Omega + 2 \times 23.2\text{ k}\Omega) \times 10\text{ }\mu\text{F}} = 3\text{ Hz} \quad (2)$$

## 2.3 Highlighted Products

### 2.3.1 TPS610995

The TPS610995 is part of the TPS61099 family of devices. The TPS610995 device is a fixed output voltage ( $V_{out} = 3.6$  V) version. The TPS610995 boost converter uses a hysteretic control topology to obtain maximum efficiency at minimal quiescent current. The TPS610995 device only consumes 1- $\mu$ A quiescent current and can achieve up to 75% efficiency at a 10- $\mu$ A load. The TPS610995 device can also support up to 320-mA output current from 2 V to 3.6 V conversion and achieve up to 93% at a 320-mA load. The TPS610995 device also offers Down Mode operation. In Down Mode, the output voltage can still be regulated at a target value even when the input voltage is higher than the output voltage. The TPS610995 device supports true shutdown function when it is disabled, which disconnects the load from the input supply to reduce the current consumption. The TPS610995 device is available in a 6-pin, 2-mm × 2-mm, WSON package, the total boost converter size is about 14mm\*8mm, including a input tantalum capacitor and a output 0603 ceramic capacitor.

### 2.3.2 LMC555

The LMC555 device is a CMOS version of the industry standard 555 series general-purpose timers. The LMC555 offers the same capability of generating accurate time delays and frequencies as the LM555 but with much lower power dissipation and supply current spikes. When operated as a one-shot, the time delay is precisely controlled by a single external resistor and capacitor. In the astable mode the oscillation frequency and duty cycle are accurately set by two external resistors and one capacitor. The use of TI's LMCMOS process extends both the frequency range and the low supply capability.

### 2.3.3 CSD18533KCS

The CSD18533KCS is a 5.0 m $\Omega$ , 60 V TO-220 NexFET™ power MOSFET, which is designed to minimize losses in power conversion applications.

## 3 Hardware, Testing Requirements, and Test Results

### 3.1 Required Hardware

#### 3.1.1 Hardware

The reference design used this hardware to test the design:

- DC power source
- Digital oscilloscope
- Multimeters

### 3.2 Testing and Results

#### 3.2.1 Test Setup

See 4.1 节 and 4.2 节 for the test schematic and bill of materials.

To test the design:

1. Check that pin 1 and pin 2 of U1 are connected by a line.
2. Connect the EN pin (pin 2) to the input voltage (pin 3) through the EN jumper.
3. Connect the RESET pin (pin 2) to the input voltage (pin 3) through the RESET jumper.

4. Connect the input terminal of the reference board to the DC power source.


### 3.2.2 Test Results

#### 3.2.2.1 Comparison


图 3 和 图 4 展示了测试结果的比较。通道 2 是 Li-SOCl<sub>2</sub> 电池连接到超级电容的输出。通道 1 是 TPS610995 提升转换器的输出。通道 4 是输出电流。

一个 320-mA, 130-ms 脉冲电流用于监测 NB-IoT 负载功能。图 3 展示了在 -40°C 环境温度下，直接将 Li-SOCl<sub>2</sub> 电池连接到超级电容时的测试结果。在这种情况下，Li-SOCl<sub>2</sub> 电池的输出在 320-mA 脉冲电流下降低至 2.8 V。NB-IoT 模块在这种情况下停止工作。图 4 展示了使用 TPS610995 提升转换器时的测试结果。TPS610995 提升转换器的输出在脉冲输出电流下保持稳定。NB-IoT 模块继续进行稳定的操作。

**图 3. Simulate NB-IoT Working Without TPS610995 at  $T_A = -40^\circ\text{C}$**

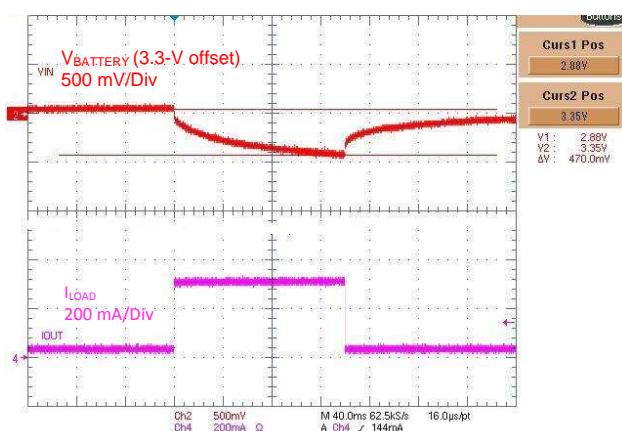


**图 4. Simulate NB-IoT Working With TPS610995 at  $T_A = -40^\circ\text{C}$**

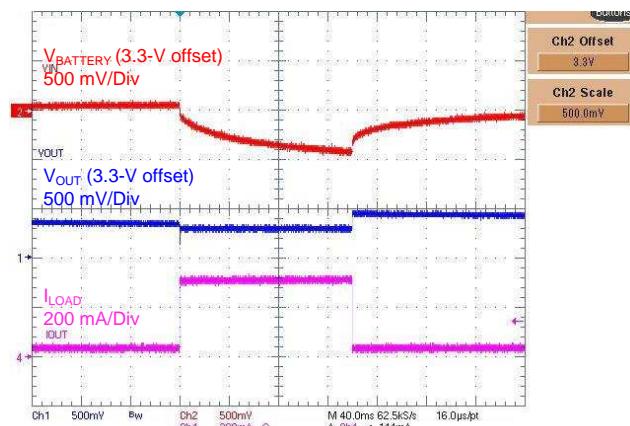

#### 3.2.2.2 Efficiency Curves

图 5 展示了不同输入电压下的负载效率曲线。


**图 5. TPS610995 Load Efficiency for Different Input Voltages**

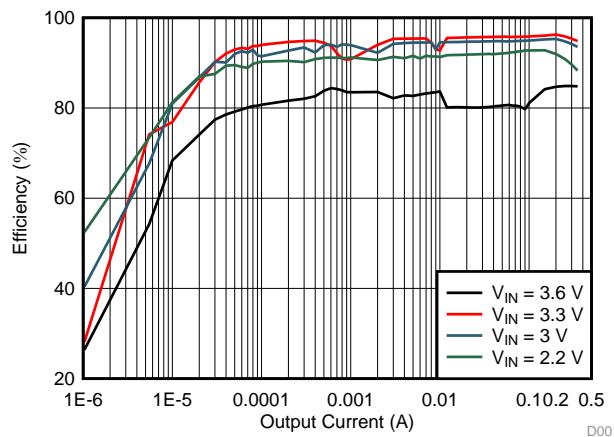

### 3.2.2.3 Output Voltage Ripple


图 6, 图 7, 和 图 8 show the waveforms for output voltage ripple. 图 6 shows burst mode operation, 图 7 shows discontinuous current operation and 图 8 shows continuous current operation.

图 6. Output Voltage Ripple

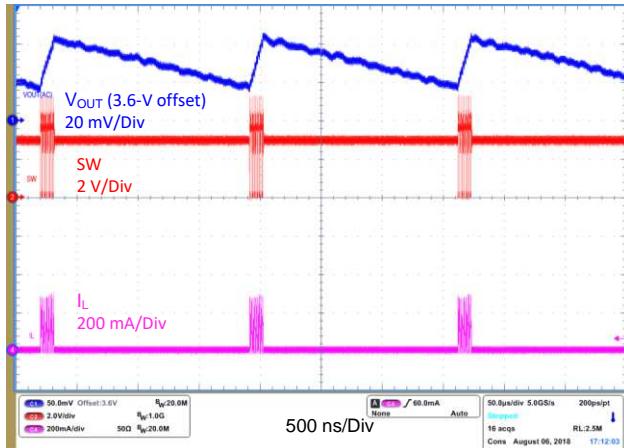


$V_{IN} = 3 \text{ V}$ ; Open Load

图 7. Output Voltage Ripple

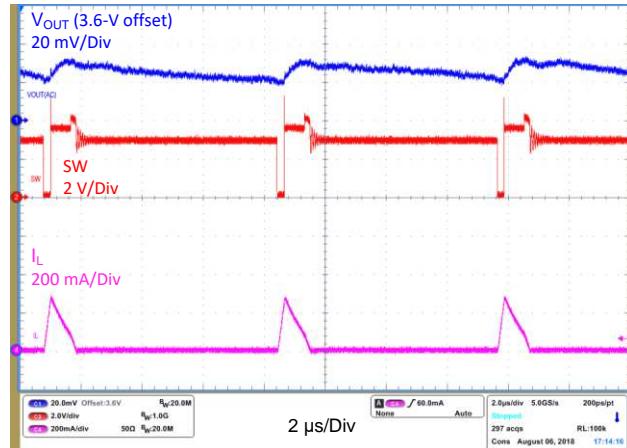

$V_{IN} = 3 \text{ V}$ ;  $I_{OUT} = 10 \text{ mA}$

图 8. Output Voltage Ripple

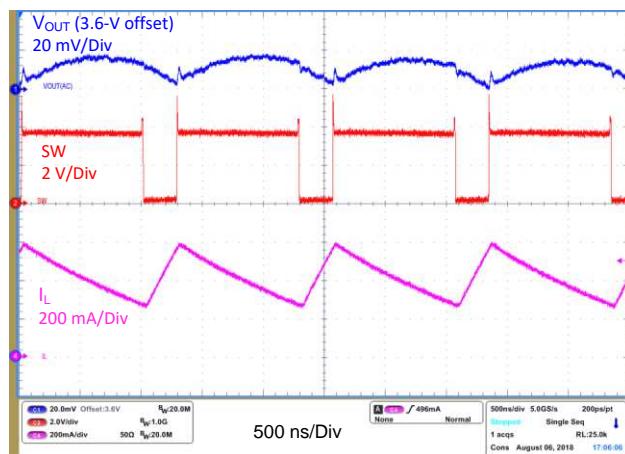


$V_{IN} = 3 \text{ V}$ ;  $I_{OUT} = 320 \text{ mA}$

### 3.2.2.4 Start Up by EN


图 9 和 图 10 展示了由 EN 引脚启动时的波形。

图 9. Startup by EN

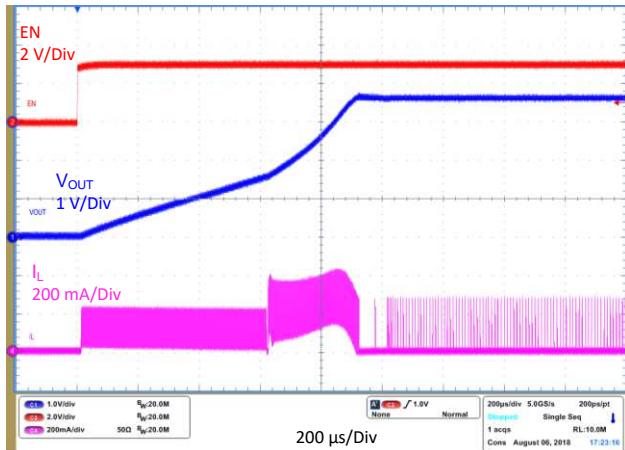

$V_{IN} = 3 \text{ V}$ ;  $I_{OUT} = 10 \text{ mA}$

图 10. Startup by EN

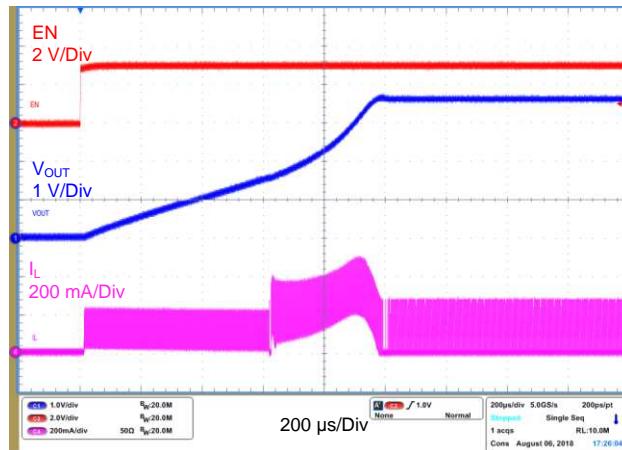


$V_{IN} = 3 \text{ V}$ ;  $I_{OUT} = 50 \text{ mA}$

### 3.2.2.5 Load Transient


图 11 和 图 12 展示了负载瞬态波形。

图 11. Load Transient

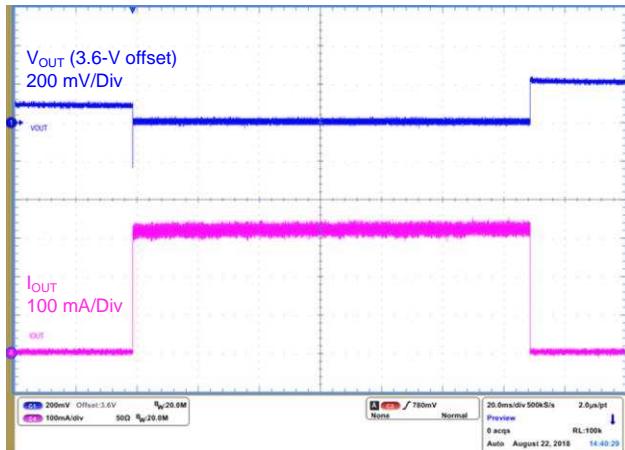

$V_{IN} = 3 \text{ V}$ ;  $I_{OUT}$  from 0 mA to 320 mA

图 12. Load Transient

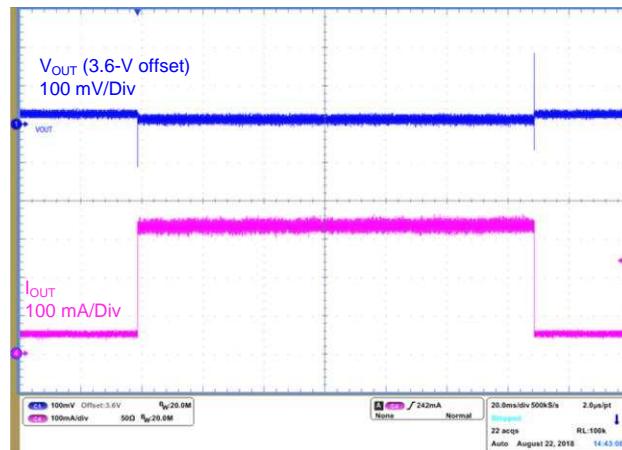


$V_{IN} = 3 \text{ V}$ ;  $I_{OUT}$  from 50 mA to 320 mA

### 3.2.2.6 Line Regulation

图 13 显示了线调节波形。

图 13. Line Regulation

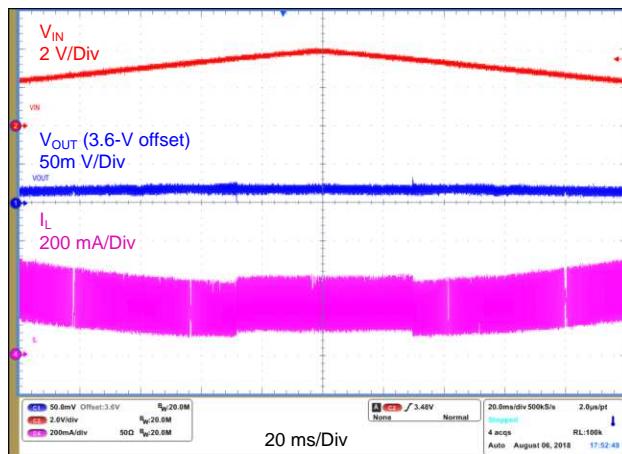

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-050010](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-050010](#).

### 4.3 Layout Prints

To download the layer plots, see the design files at [TIDA-050010](#).

### 4.4 Altium Project

To download the Altium Designer® project files, see the design files at [TIDA-050010](#).

### 4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-050010](#).

### 4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-050010](#).

## 5 Related Documentation

1. Texas Instruments, [CSD18533KCS 60 V N-Channel NexFET™ Power MOSFET data sheet](#)
2. Texas Instruments, [LMC555 CMOS Timer data sheet](#)
3. Texas Instruments, [TPS61099x Synchronous Boost Converter with Ultra-Low Quiescent Current data sheet](#)
4. Endrich, [EVE SPC \(Super Pulse Capacitor cell\) Model SPC1520.data sheet](#).

### 5.1 商标

E2E, NexFET are trademarks of Texas Instruments.

Altium Designer is a registered trademark of Altium LLC or its affiliated companies.

All other trademarks are the property of their respective owners.

## 重要声明和免责声明

TI 均以“原样”提供技术性及可靠性数据（包括数据表）、设计资源（包括参考设计）、应用或其他设计建议、网络工具、安全信息和其他资源，不保证其中不含任何瑕疵，且不做任何明示或暗示的担保，包括但不限于对适销性、适合某特定用途或不侵犯任何第三方知识产权的暗示担保。

所述资源可供专业开发人员应用TI 产品进行设计使用。您将对以下行为独自承担全部责任：(1) 针对您的应用选择合适的TI 产品；(2) 设计、验证并测试您的应用；(3) 确保您的应用满足相应标准以及任何其他安全、安保或其他要求。所述资源如有变更，恕不另行通知。TI 对您使用所述资源的授权仅限于开发资源所涉及TI 产品的相关应用。除此之外不得复制或展示所述资源，也不提供其它TI 或任何第三方的知识产权授权许可。如因使用所述资源而产生任何索赔、赔偿、成本、损失及债务等，TI 对此概不负责，并且您须赔偿由此对TI 及其代表造成的损害。

TI 所提供产品均受TI 的销售条款 (<http://www.ti.com.cn/zh-cn/legal/termsofsale.html>) 以及ti.com.cn 上或随附TI 产品提供的其他可适用条款的约束。TI 提供所述资源并不扩展或以其他方式更改TI 针对TI 产品所发布的可适用的担保范围或担保免责声明。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122  
Copyright © 2018 德州仪器半导体技术（上海）有限公司

## 重要声明和免责声明

TI 均以“原样”提供技术性及可靠性数据（包括数据表）、设计资源（包括参考设计）、应用或其他设计建议、网络工具、安全信息和其他资源，不保证其中不含任何瑕疵，且不做任何明示或暗示的担保，包括但不限于对适销性、适合某特定用途或不侵犯任何第三方知识产权的暗示担保。

所述资源可供专业开发人员应用TI 产品进行设计使用。您将对以下行为独自承担全部责任：(1) 针对您的应用选择合适的TI 产品；(2) 设计、验证并测试您的应用；(3) 确保您的应用满足相应标准以及任何其他安全、安保或其他要求。所述资源如有变更，恕不另行通知。TI 对您使用所述资源的授权仅限于开发资源所涉及TI 产品的相关应用。除此之外不得复制或展示所述资源，也不提供其它TI 或任何第三方的知识产权授权许可。如因使用所述资源而产生任何索赔、赔偿、成本、损失及债务等，TI 对此概不负责，并且您须赔偿由此对TI 及其代表造成的损害。

TI 所提供产品均受TI 的销售条款 (<http://www.ti.com.cn/zh-cn/legal/termsofsale.html>) 以及ti.com.cn 上或随附TI 产品提供的其他可适用条款的约束。TI 提供所述资源并不扩展或以其他方式更改TI 针对TI 产品所发布的可适用的担保范围或担保免责声明。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122  
Copyright © 2018 德州仪器半导体技术（上海）有限公司