

# 设计指南: TIDA-010048

## 通道至通道隔离式模拟输入模块参考设计



### 说明

此参考设计是一款四路通道至通道、隔离式 4–20mA、电流环路模拟输入模块。该设计包括用于状态监控传感器和模块的短路、过流和过压限制功能。该模拟输入模块的主要特性包括通道隔离、多通道模拟输入模块（由使用 TI LM5180 器件的单反激转换器供电）、电源（为 2 线制发送器和短路保护电路供电）。此设计还可支持四通道模拟输入模块。

### 资源

TIDA-010048	设计文件夹
LM5180	产品文件夹
ADS122U04	产品文件夹
TPS2662	产品文件夹
ISO7721	产品文件夹
TPS7A47	产品文件夹
TVS3300	产品文件夹
SN74LV4052A	产品文件夹

### 特性


- 1 至 4 路通道至通道隔离式模拟输入模块。
- 适用于具有输出功率限制（短路电流限制为 25mA）的现场发送器的电源
- 发送器电源:  $25 \pm 1\text{V}$ ,  $\text{I}_{\text{OUT}} < 25\text{mA}$  (峰值)
- 误接线输入保护
- UART 接口 24b  $\Delta\Sigma$ ADC，用于降低 BOM 尺寸和成本

### 应用

- 混合模块 (AI、AO、DI、DO)
- 模拟输入模块



咨询我们的 E2ETM 专家

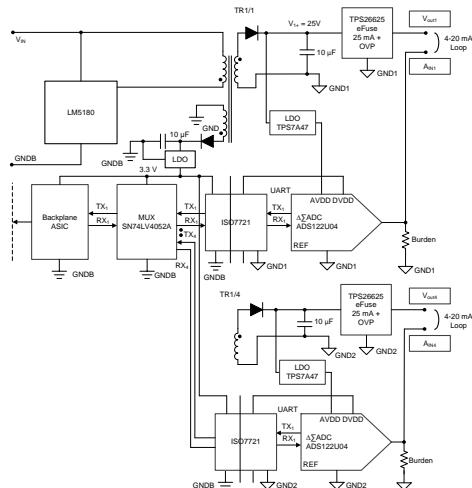


该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

## 1 System Description

The TIDA-010048 universal analog input module is four channel-to-channel isolated with short-circuit protection, over-current limit, overvoltage limit and high-performance design. Analog input modules digitalize temperature, current (4–20 mA) and voltage ( $\pm 10V$ ). Analog input modules are challenged with increasing channel density, tolerating high common mode voltages, high throughput with low power, functional or intrinsic safety, high dynamic range, EMI and miswiring protection. This design implements a two-wire 4–20 mA current-loop analog input module system. The design supports remote sensor transmitters without an additional power supply which can eliminate the external ground pin on the casing so the field engineer can avoid miswiring problems. It also can support four-channel analog input module with a single flyback converter. This means the PLC side can reduce the cost and BOM size and achieve channel-to-channel isolated analog input module system. **图 1** shows the typical two-wire current-loop system. The supply of the field transmitter is provided by the analog input module side and current output of field transmitter transfer the analog signal back to analog input module side. There is another key characteristic of this design which uses the eFuse to prevent the overcurrent and overvoltage simultaneously to limit the power flow into the field side.

**图 1. Typical Two-Wire Current-Loop System**

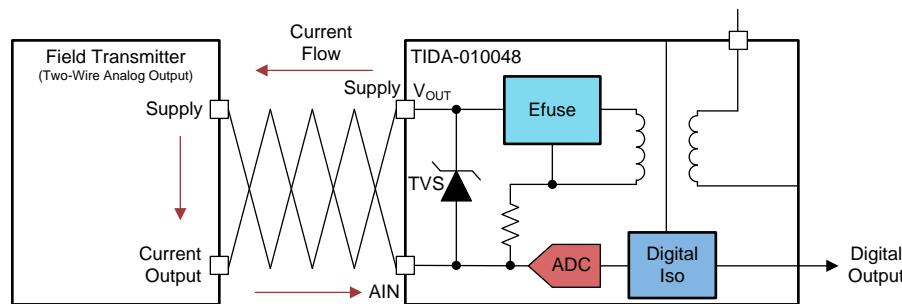

### 1.1 Key System Specifications


**表 1. Key System Specifications**

<b>PARAMETER</b>		<b>SPECIFICATIONS</b>
Number of analog input channels (2-wire transmitters)		Four Channels
Power supply part for 2-wire transmitter per channel	Supply voltage	25 VDC
	Overvoltage limit	33 VDC
	Overcurrent and short-circuit limit	25 mA
Isolation	Between backplane and analog input channels	1000 VAC, 1 minute
	Between analog input channels	1000VAC, 1 minute
Analog input module for current loop per channel	Range	4–20 mA
	Resolution	24-bit
	Internal PGA Gain	1, 2
	Sampling Cycle	20 SPS to 1000 SPS
Form factor	Each Channel	5.2 cm x 1.8 cm
	Entire board	9.5 cm x 8.4 cm
Operating temperature		-40°C to 85°C

## 2 System Overview

### 2.1 Block Diagram

图 2. System Block Diagram

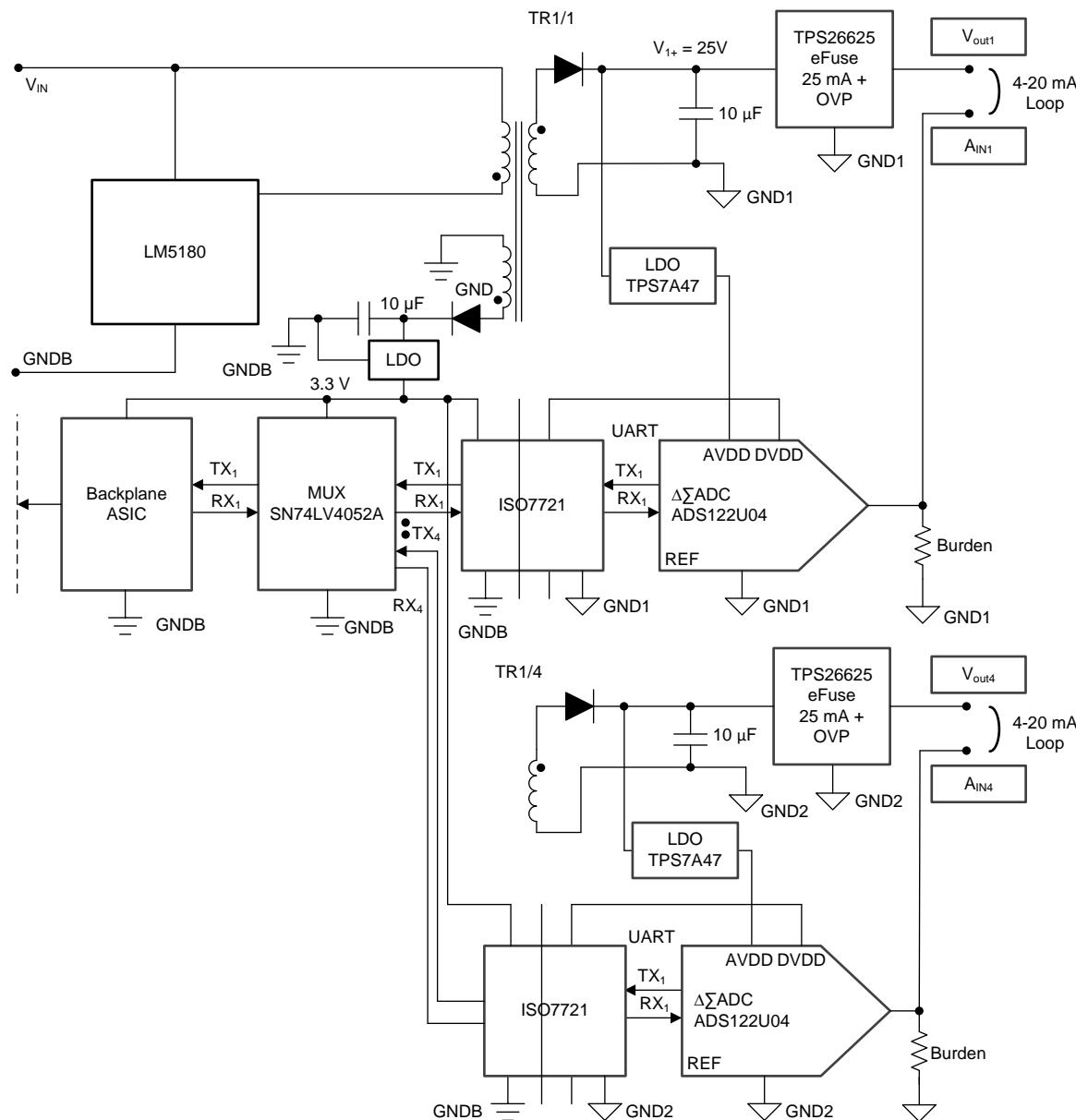

## 2.2 Design Considerations

The block diagram in [图 2](#) is separated into three parts: isolated power, analog front end, and digital isolation signal readout circuit.

The isolated power is mainly implemented with TI's flyback converter (LM5180). The transformer uses Wurth Electronics to customize the transformer which can achieve one-four channel isolated power. The current limit on every channel is set into 25 mA at 25 V DC which is enough for field transmitter applications. The isolation level is decided by the transformer which is functional insulation. The rated voltage of this transformer can be up to 1000 VAC for one minute. If a higher level of isolation is required, the transformer design can be changed to meet the specification.  $V_{IN}$  and  $V_{OUT}$  voltage are equal to 25 V. The current limit and voltage threshold of every channel which is decided by the eFuse set up at 25 mA and 33 V. Every isolated maximum channel power can provide the field side to 1.25 W.

The analog front end circuit implements a 4–20 mA current loop by the ADS122U04 device which uses the UART interface and a 24-bit  $\Delta\Sigma$ ADC. It could reduce the channel number of digital isolator and the BOM size and cost. The power of ADC is supplied by the wide  $V_{IN}$  LDO (TPS7A47). Using the wide  $V_{IN}$  LDO can reduce the additional buck converter for stepping down voltage and retains ADC performance. If there are other analog input requirements such as voltage  $\pm 10$  V, 0–5 V, 0–10 V; Current  $\pm 25$  mA, 0–20 mA; temperature input RTD, thermocouple and thermistor, see the following TI reference design.

The designers can choose a dual-channel digital isolator for signal isolation due to UART ADC. It can reduce the silicon package size and total BOM cost. A dual four-channel analog MUX in the PLC side helps the customer choose the necessary analog input module to measure the analog signal which can decrease the pins of UART interface on the microcontroller in the backplane side. This provides more flexibility in analog input module system design.

## 2.3 Highlighted Products

### 2.3.1 LM5180

The LM5180 device is a primary-side regulated (PSR) flyback converter with high efficiency over a wide input voltage range of 4.5 V to 65 V. The isolated output voltage is sampled from the primary-side flyback voltage, eliminating the need for an optocoupler, voltage reference, or third winding from the transformer for output voltage regulation.

### 2.3.2 ADS122U04

The ADS122U04 device is a high precision, 24-bit, analog-to-digital converter (ADC) that offers integrated PGA, reference, and internal fault monitors. The device features two differential or four single-ended inputs through a flexible input multiplexer (MUX). The device data rates can be up to 2000 samples-per-second (SPS) with single-cycle settling. At 20 SPS, the digital filter offers simultaneous 50-Hz and 60-Hz rejection for noisy industrial applications. The internal PGA offers gains up to 128. The ADS122U04 features a 2-wire, UART-compatible interface. With a UART interface, engineers only need a two-channel digital isolator. It could reduce the cost and BOM size.

### 2.3.3 TPS26625

The TPS2662X family have a wide supply input range of 4.5 V to 57 V. The device can withstand and protect the loads from positive and negative supply voltages to  $\pm 60$  V. TPS26625 devices support both input as well as output reverse polarity protection features. Load, source, and device protection are provided with many adjustable features including overcurrent, output slew rate and overvoltage, undervoltage thresholds. Therefore, using a single eFuse circuit can achieve power limit functions for field transmitter in hazardous region.

### 2.3.4 TPS7A47

The TPS7A470x is a family of positive voltage (+36 V), ultra-low noise ( $4 \mu\text{V}_{\text{RMS}}$ ) low-dropout linear regulators (LDO) capable of sourcing a 1-A load. The TPS7A47 device is designed with bipolar technology, high-precision instrumentation applications where clean voltage rails are critical to maximize system performance. This feature makes the device ideal for powering operational amplifiers, analog-to-digital converters (ADCs), digital-to-analog converters (DACs), and other high-performance analog circuitry in critical applications such as medical, radio frequency (RF), and test-and-measurement.

### 2.3.5 TVS3300

The TVS3300 is a protection device with a very low leakage current component. It also can robustly shunt up to 35 A of IEC 61000-4-5 fault current to protect systems from high-power transients or lightning strikes. The device offers a solution to the common industrial signal line EMC requirement to survive up to 1-kV IEC 61000-4-5 open circuit voltage coupled through a  $42\text{-}\Omega$  impedance.

### 2.3.6 ISO7721

The ISO772X devices are high-performance, dual-channel digital isolators with  $5000 \text{ V}_{\text{RMS}}$  (DW and DWV packages) and  $3000 \text{ V}_{\text{RMS}}$  (D package) isolation ratings per UL 1577. These devices are also certified by VDE, TUV, CSA, and CQC. The ISO7721 device has both channels in the opposite direction; therefore, it also could support UART interface.

### 2.3.7 SN74LV4052A


The SN74LV4052A device is a dual, 4-channel multiplexer and demultiplexer that is designed for 2-V to 5.5-V  $V_{\text{cc}}$  operation. The dual 4-channel MUX can help to choose the necessary analog input module to measure analog signal.

## 2.4 System Design Theory

### 2.4.1 Channel-to-Channel Isolated Power Supply for Field Transmitter

This reference design provides four channel-to-channel isolated power supplies for 4–20 mA current-loop circuit as 图 3 illustrates. The four-channel supply units are all powered up by the single flyback converter (LM5180). Every channel can support the current up to 30 mA and output voltage at 25 V. The isolated rated voltage is 1000 VAC in 1 minute.

**图 3. Flyback Transformer Symbol for TIDA-010048**

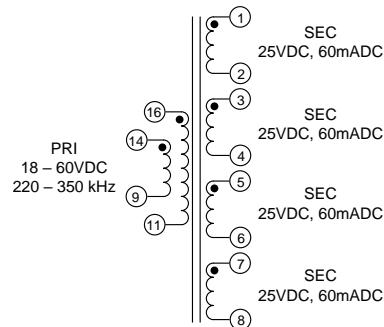


The detailed requirements of the transformer follow:

- Four 25-V isolated outputs: all of them with 30 mA
- Switching frequency range: 100 kHz–350 kHz
- Isolation voltage:
  - Primary to secondary, 1000-VAC for 1 minute
  - Secondary to secondary, 1000-VAC for 1 minute
- Functional insulation between windings

If the design architecture requires higher safety requirement more than functional isolation, the transformer can be redesigned.


**图 4. Channel-to-Channel Isolated Power Supply Using LM5180**

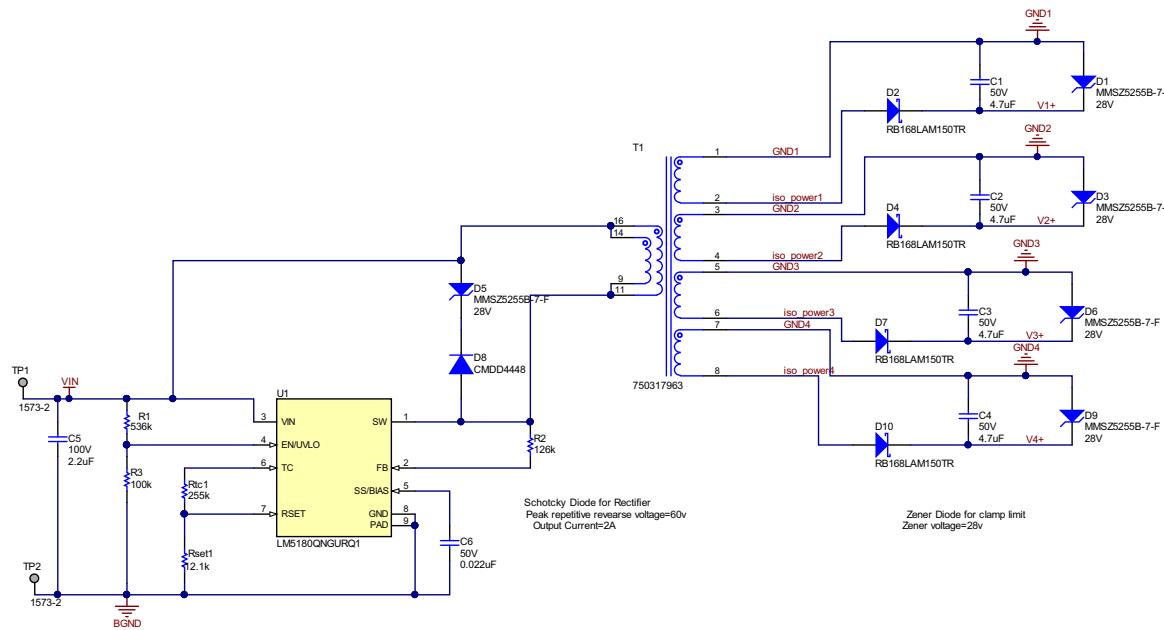

#### 2.4.2 Analog Front End

The module features a two-wire, four channel, 4–20 mA analog input module which can be used with sensor transmitters with 4–20 mA current loop. The main purpose of this circuit is to build a reliable delivery of 4–20 mA loop current analog input front end. 图 5 shows the detail of the analog front end circuit.  $R_{shunt}$  is the  $R_{shunt}$  to transfer the current signal into voltage. A first-order resistor-capacitor (RC) filter is used in the AFE. The filter corner frequency is set at 1.6 kHz. D3 is for shifting the input signal level. It can make the analog input signal remain in full-scale range of the ADC when the PGA is on. The ADC using a UART interface can reduce the number channels of digital isolator.


图 5. Analog Input Front End

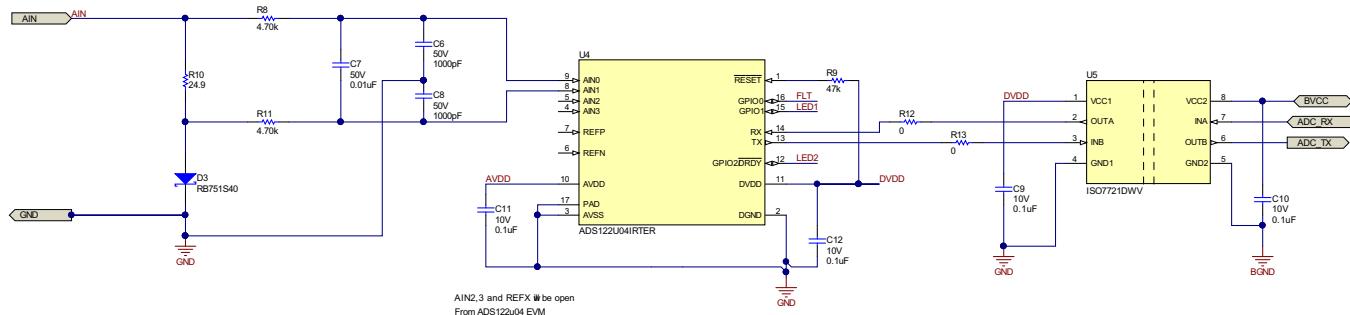

#### 2.4.3 Data Accquisition Systems Using UART Interface

In the [Reducing System Cost, Size and Power Consumption in Isolated Data Acquisition Systems Using ADS122U04 Tech Note](#), the ADS122U04 replaces the standard SPI interface with a 2-wire UART interface. Engineers only need a twochannel digital isolator with no additional uC or processor in the ADC side which is depicted in [图 6](#). Using TI's ADS122U04 device, the industry's first sensor measurement ADC with UART interface, designers can reduce their digital isolator power consumption and cost by > 30% compared to conventional implementations while still taking advantage of the high resolution and integration of a 24-bit delta-sigma ADC. To build the data acquisition systems for four sets of analog input modules, the design uses the dual four-channel MUX to capture the required data from different analog input module as [图 6](#) shows.

图 6. Data Acquisition Systems Using UART Interface Block Diagram

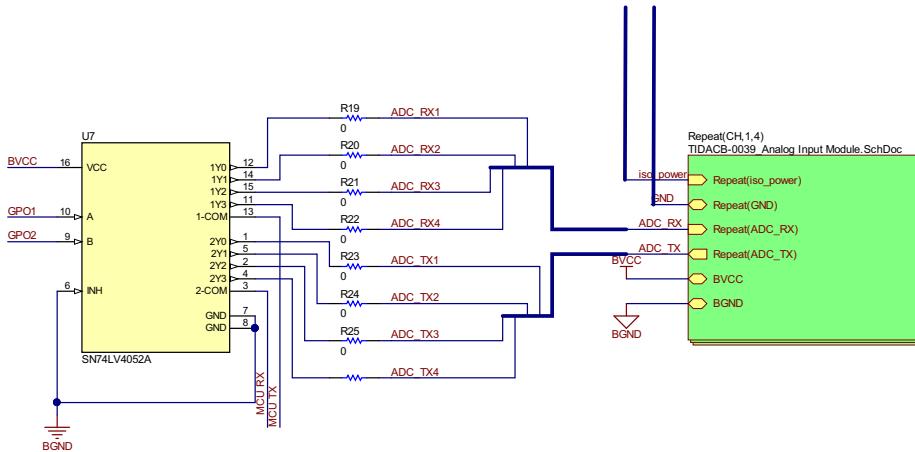

#### 2.4.4 Two-Wire 4–20 mA Current-Loop Analog Input Module


[图 1](#) shows a typical two-wire, 4–20 mA current-loop analog input module which TIDA-010048 is based on. The key advantage of the two-wire system can provide 4–20 mA power for the field transmitter. Therefore, the whole field side system does not need an extra power supply to power-up the field transmitter. Another advantage is to avoid setting the grounding pin outside the casing of analog input module, so you can use TVS to connect the power supply and the analog input pin to protect the surge as the [Typical Application](#) section in the [TVS3300 33-V Flat-Clamp Surge Protection Device Data Sheet](#) details.

### 3 Test and Measurement Results

#### 3.1 Power Tree Test Result

图 7 shows the power tree test setup. Use the source measure unit to get the flyback efficiency, cross regulation, start-up waveform, and the waveform of ripple when the load variation is in the other channel. Because the actual performance data may be affected by measurement techniques and environmental variables, these curves and waveforms are presented for reference and may differ from actual field measurements.

图 7. Power Tree Test Setup

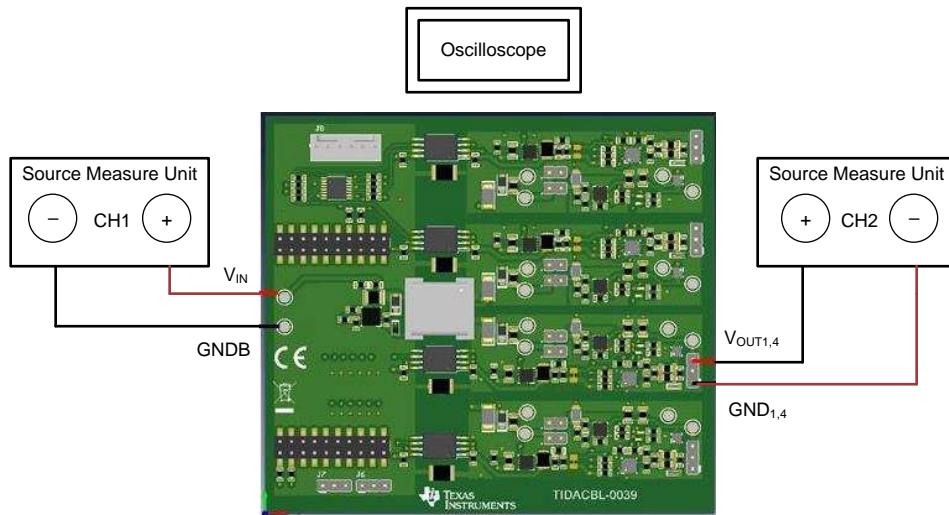

### 3.1.1 Efficiency Performance

The efficiency measurements were taken channel by channel as 图 8 shows. The efficiency performance is as expected. 表 2 shows the whole system performance. It includes the power dissipation of other channels quiescent current loss and the power loss of the signal chain circuit. Although, it is a little lower than ideal, it is still enough for the power dissipation of the field transmitter.

图 8. Efficiency Performance of Flyback

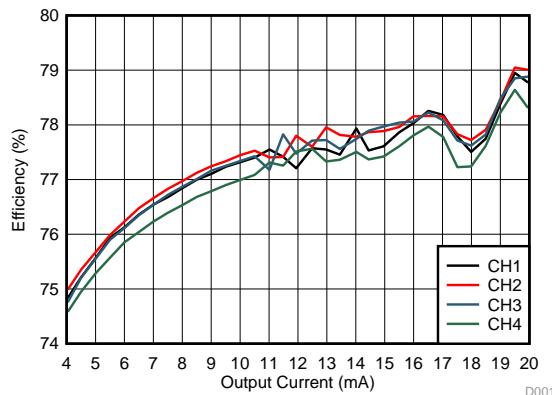



表 2. Total System Efficiency

	4 mA FOR EACH CHANNEL	12 mA FOR EACH CHANNEL	20 mA FOR EACH CHANNEL
Input power (W)	0.763	1.65	2.65
Output power (W)	0.413	1.27	2.12
Total efficiency (%)	54.1	77.3	79.9

### 3.1.2 Start-Up Waveform

图 9 shows the start-up waveform. The waveform is tested at full load at 25-V input. The four channel sets at the same output load and input situation. The default internal soft-start time of the LM5180 device is 6 ms and an externally-programmable soft start.

**图 9. Start-Up Waveform**

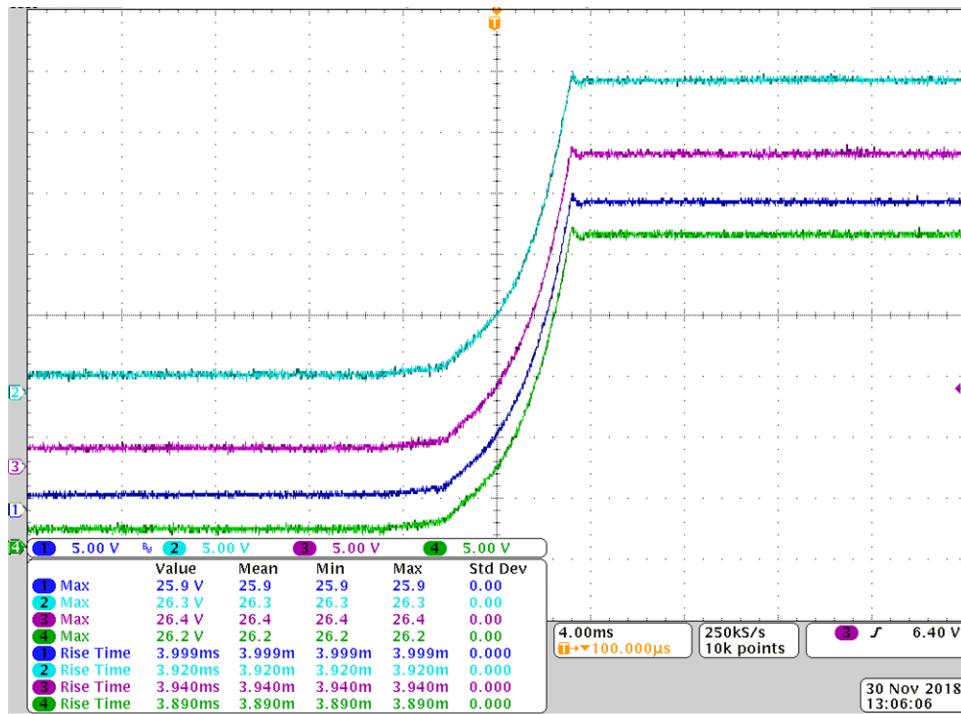

### 3.1.3 Load Regulation and Cross Regulation

图 10 shows the influence at the output of flyback with the other channel load varying from 4 mA to 20 mA. The green line and the blue line, respectively, represent the load state of the load variation channel and the constant 20-mA channel under load variation conditions. The normal channel of  $V_{OUT}$  variation is about 22.4 mV. The load variation channel of  $V_{OUT}$  variation is about 94 mV.

**图 10. Load Regulation Waveform**


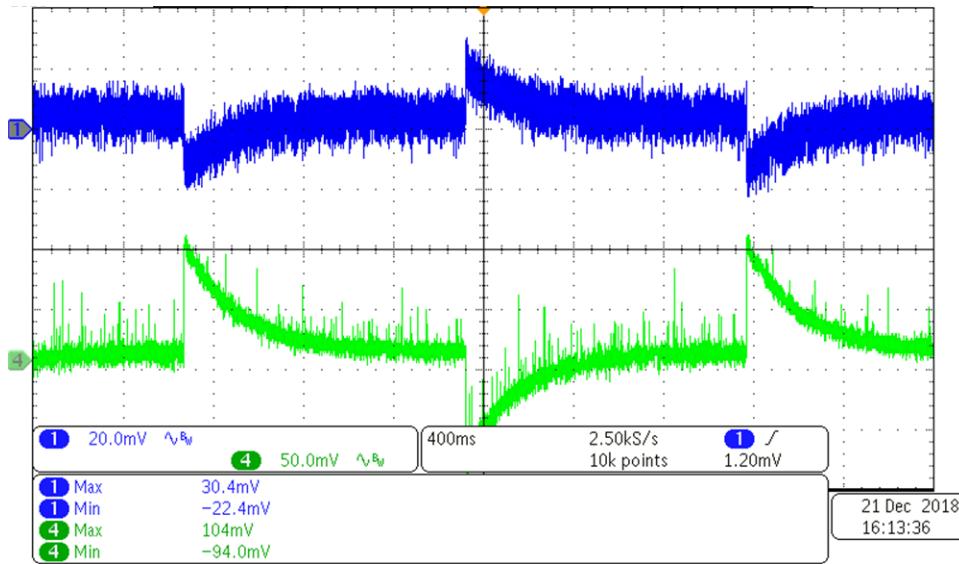


图 11 显示了参考设计的交叉调节性能。飞背输出电压受其他通道负载电流的影响。在所有条件下，4~20 mA 负载下的输出电压变化相当稳定，且 CH1,2 和 CH3,4 之间电压差的主要原因是变压器参数差异。

图 11. Cross Regulation Performance

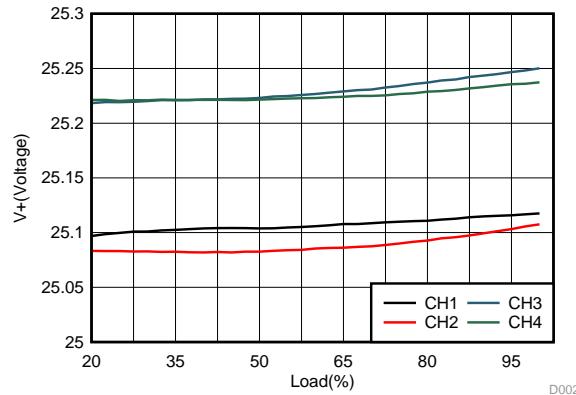

### 3.2 Test Result of Overcurrent and Short-Circuit Protection

The eFuse provides the short-circuit and overcurrent limit protection feature for two-wire current loop. 图 12 说明了系统在输出短路条件下的行为。短路行为引起约 42-mV 过电压在  $V_{OUT}$  在正常通道。图 12 也显示了自动重试功能，每周期重试时间为 512 ms。

图 12. eFuse Short-Circuit Protection Waveform

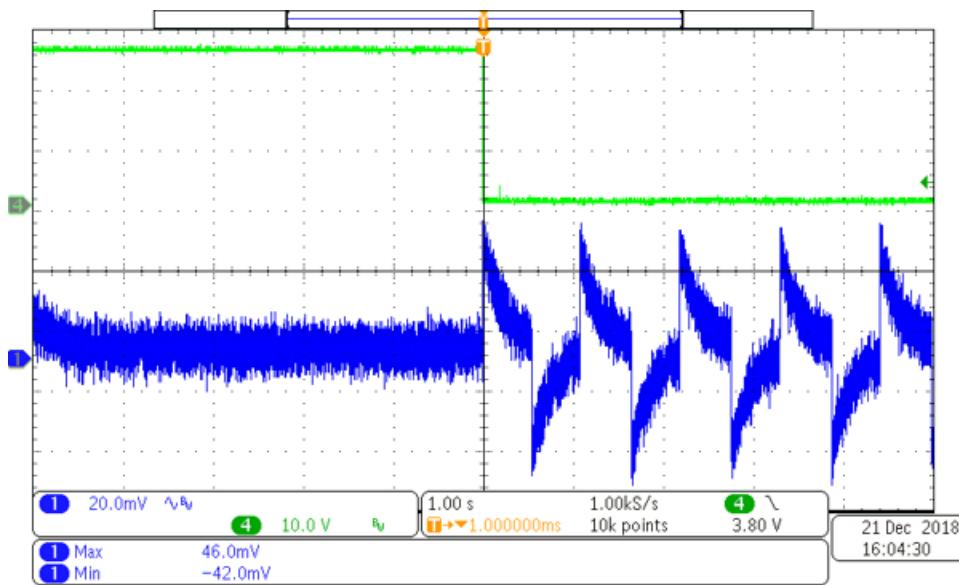


图 2 显示了正常和短通道的  $V_{OUT}$  引脚以及 FLT 引脚。FLT 引脚电压在短路发生后下降，可以向控制器侧提供警报信号，如果发生短路。

This reference design has an eFuse in the power line which can provide the overvoltage and overcurrent protection simultaneously. If the field transmitter is located in a hazardous region, any sparks or blink create the high possibility of explosion. Due to that, the eFuse can provide the power limit for the field transmitter side, it is suitable for safety applications. 表 3 shows voltage, current, and power limit of every channel.


**表 3. Power Limit by eFuse**

	<b>CH1</b>	<b>CH2</b>	<b>CH3</b>	<b>CH4</b>
Overvoltage limit	33.3 V	33.3 V	33.3 V	33.2 V
Overcurrent limit	24.944 mA	25.174 mA	25.311 mA	25.574 mA
Over power limit	830 mW	839 mW	843 mW	849 mW

### 3.3 Test Result of Analog Input Module Performance

图 13 shows the signal chain test setup. Due to the UART interface signal chain design, testing the ADC performance is easier. Using the STDI, connect the PC and the board directly to reduce the number of isolation channels and the current consumption. The 4–20 mA analog input current source used is the high precision SMU (B2912A) which is accurate up to 0.02% in the 10-mA range. It ensures the real performance of the ADC is measured. To obtain the effective and noise-free bits, the standard deviation is calculated from 750 samples taken from an externally-applied 4-mA, 12-mA, and 20-mA constant current. The loop current is not measured by an external DMM since the absolute value is not of importance. 图 14 through 图 25 show the relatively current data histogram based on 图 13 at different conditions.

**图 13. Signal Chain Test Setup**

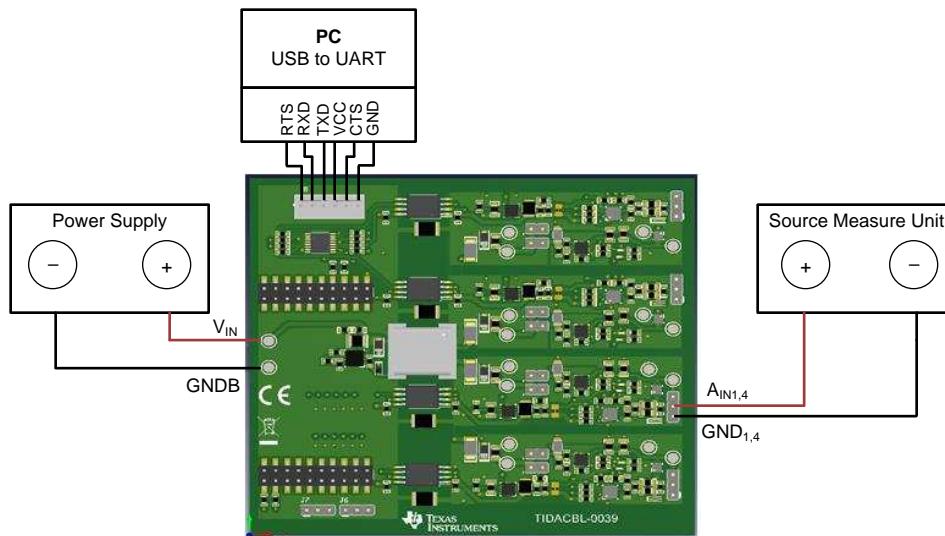

$$I_{4-20mA} = \left( \frac{2 \frac{\text{code}}{N-1} \times V_{INT,REF}}{R_{BURDEN}} \right) = \left( \frac{2^{\frac{code}{23}} \times 2.048}{24.9} \right) \quad (1)$$

The effective number of bits and noise-free bits are calculated using 公式 2 and 公式 3:

$$\text{Effective bits} = \log_2 \left( \frac{2^N}{\text{stddev[samples]}} \right)$$


where

- $N = \text{data width of converter}$


(2)

$$\text{Noise-Free bits} = \log_2 \left( \frac{2^N}{\text{stddev[samples]} \times 6.6} \right) = \text{Effective - 2.72 bits}$$
(3)


**图 14. Histogram – 4 mA, Gain = 1, SPS = 20, STD = 21.61 ENOB = 19.56**

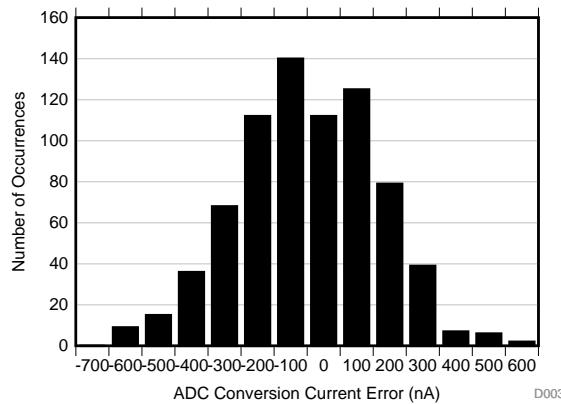


**图 15. Histogram – 4 mA, Gain = 1, SPS = 1000, STD = 183.84 ENOB = 16.47**

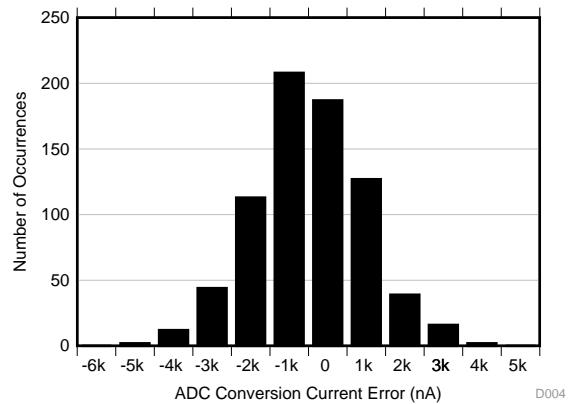


**图 16. Histogram – 4 mA, Gain = 2, SPS = 20, STD = 21.8 ENOB = 19.55**

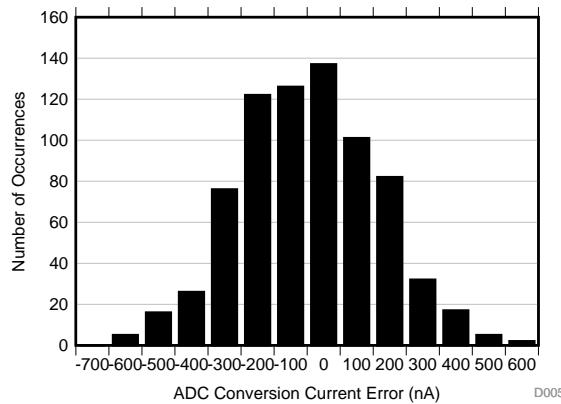

**图 17. Histogram – 4 mA, Gain = 2, SPS = 1000, STD = 149.64 ENOB = 16.77**

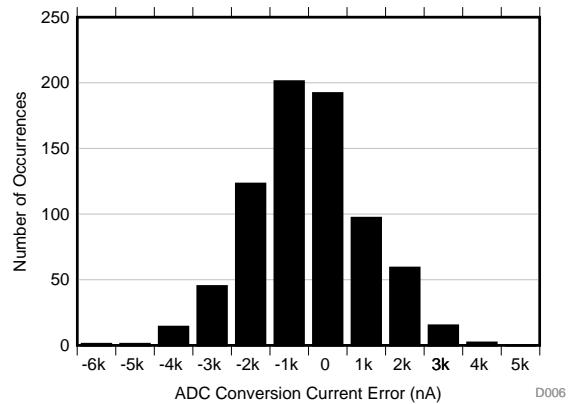

**图 18. Histogram – 12 mA, Gain = 1, SPS = 20, STD = 24.4 ENOB = 19.39**

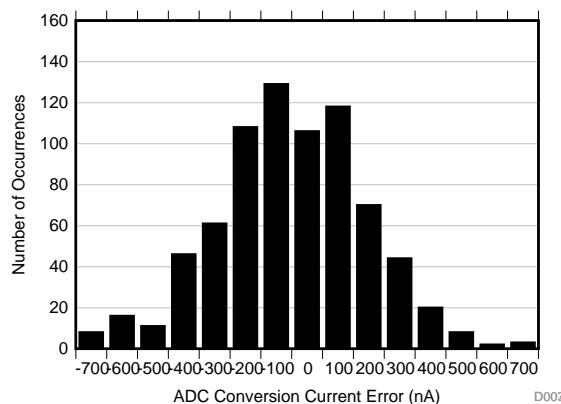

**图 19. Histogram – 12 mA, Gain = 1, SPS = 1000, STD = 152.7 ENOB = 16.75**

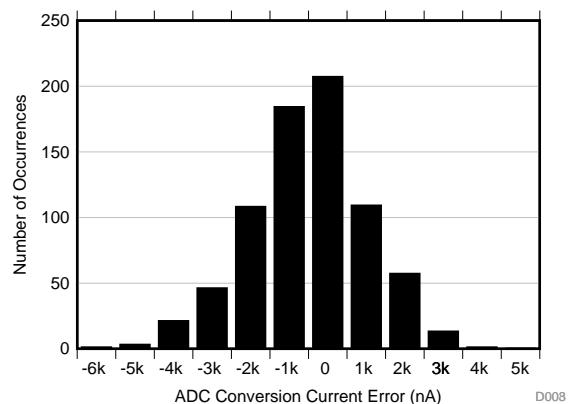


图 20. Histogram – 12 mA, Gain = 2, SPS = 20, STD = 31.25  
ENOB = 19.03

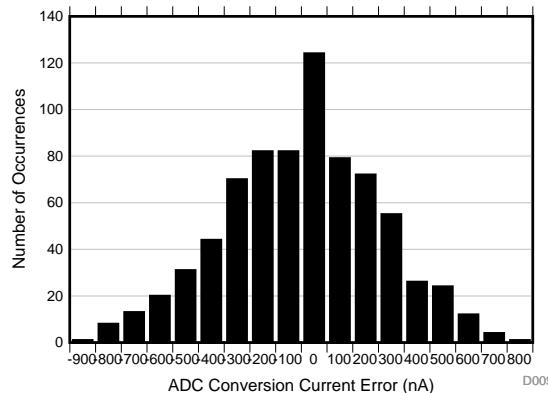


图 21. Histogram – 12 mA, Gain = 2, SPS = 1000, STD = 177.51  
ENOB = 16.53

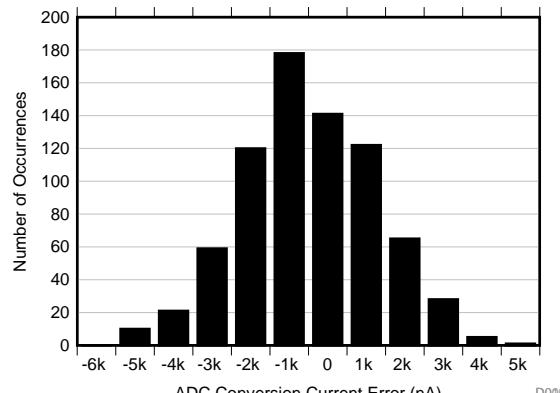


图 22. Histogram – 20 mA, Gain = 1, SPS = 20, STD = 25.43  
ENOB = 19.33

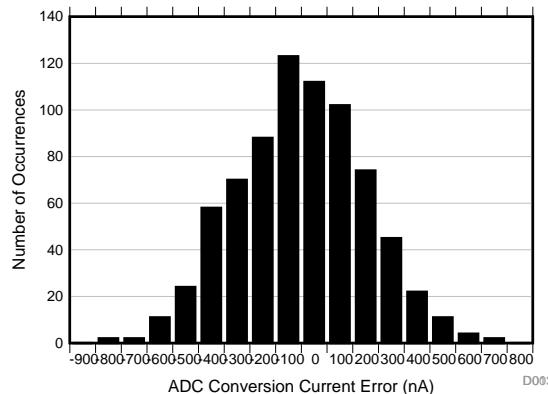


图 23. Histogram – 20 mA, Gain = 1, SPS = 1000, STD = 150.07  
ENOB = 16.77

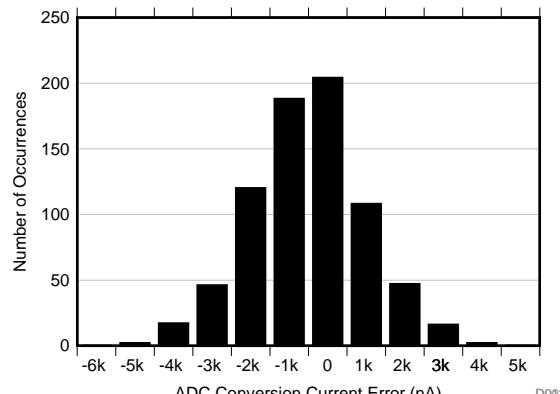


图 24. Histogram – 20 mA, Gain = 2, SPS = 20, STD = 35.07  
ENOB = 18.87


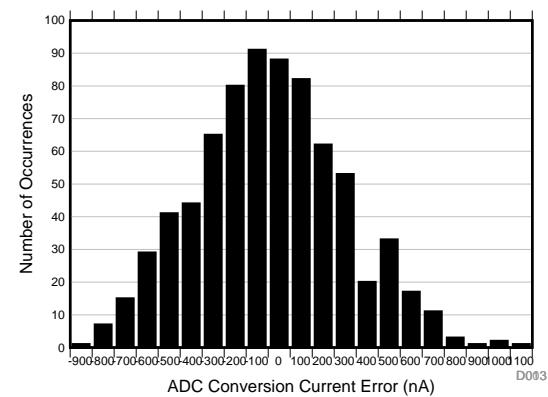


图 25. Histogram – 20 mA, Gain = 2, SPS = 1000, STD = 168.73  
ENOB = 16.60

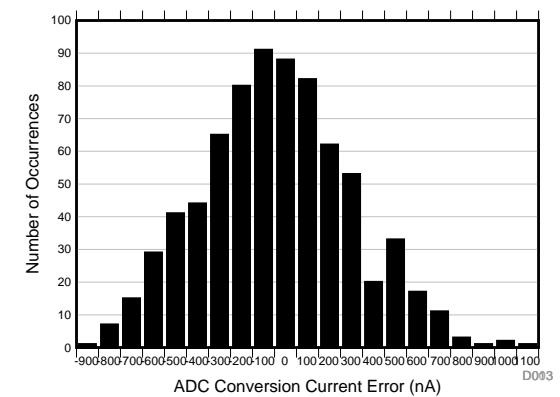

With the obtained effective bits and noise-free bits, the input referred noise can be calculated by taking the range of the input range (dependent on gain) into account (公式 4 and 公式 5). The full-scale range is  $-2.5\text{ V}$  to  $2.5\text{ V} = 5\text{ V}$ .

$$\text{RMS noise } (\mu\text{V}_{\text{RMS}}) = \frac{\left( \frac{\text{Full-scale range}}{\text{Gain}} \right)}{2^{\text{effective bits}}} \quad (4)$$

$$\text{Peak noise}(\mu\text{V}_{\text{PP}}) = \frac{\left( \frac{\text{Full-scale range}}{\text{Gain}} \right)}{2^{\text{noise-free bits}}} \quad (5)$$

表 4 和 表 5 总结了在不同采样率情况下，设备噪声性能。数据代表了典型噪声性能，采样率为  $T_A = 25^\circ\text{C}$  时使用内部 2.048-V 参考电压。由于实际性能数据可能受到测量技术及环境变量的影响，这些测量结果仅供参考，与实际现场测量可能存在差异。

**表 4. Effective Resolution From RMS Noise (Noise-Free Resolution From Peak-to-Peak Noise) at AVDD = 3.3 V, AVSS = 0 V, Normal Mode, PGA Enabled,  $I_{\text{IN}} = 4$  mA, 12 mA, 20 mA and Internal  $V_{\text{REF}} = 2.048$  V**


GAIN (PGA ENABLE)		
	1	2
4-mA Data Rate (SPS)		
20	19.56 (16.84)	19.55 (16.83)
1000	16.82 (14.10)	16.77 (14.05)
12-mA Data Rate (SPS)		
20	19.39 (16.66)	19.03 (16.31)
1000	16.74 (14.02)	16.52 (13.80)
20-mA Data Rate (SPS)		
20	19.33 (16.61)	18.86 (16.14)
1000	16.77 (14.04)	16.60 (13.87)

**表 5. Noise in  $\mu\text{V}_{\text{RMS}}$  ( $\mu\text{V}_{\text{PP}}$ ) at AVDD = 3.3 V, AVSS = 0 V, Normal Mode, PGA Enabled,  $I_{\text{IN}} = 4$  mA, 12 mA, 20 mA and Internal  $V_{\text{REF}} = 2.048$  V**


GAIN (PGA ENABLE)		
	1	2
4-mA Data Rate (SPS)		
20	5.28 (34.82)	2.66 (17.56)
1000	35 (230)	18.3 (121)
12-mA Data Rate (SPS)		
20	5.96 (39.3)	3.81 (25.18)
1000	37.3 (246)	21.7 (143)
20-mA Data Rate (SPS)		
20	6.21 (41)	4.28 (28.3)
1000	36.6 (242)	20.6 (136)

This reference design measures the noise performance in load transient (4 mA to 20 mA). 图 26 through 图 31 show the noise performance of ADC. 表 6 through 表 9 show the detailed results. As the tables show, the overvoltage does not significantly affect the overall ADC performance, due to wide  $V_{IN}$  LDO with high PSRR.


**图 26. Histogram – 4 mA, Gain = 1, SPS = 20, STD = 20.96  
ENOB = 19.61**

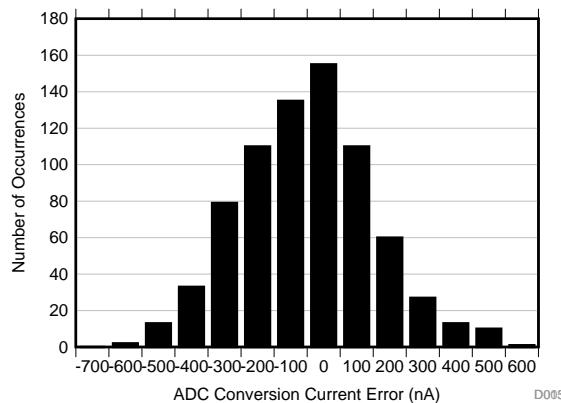


**图 27. Histogram – 4 mA, Gain = 1, SPS = 1000, STD = 141.87  
ENOB = 16.85**

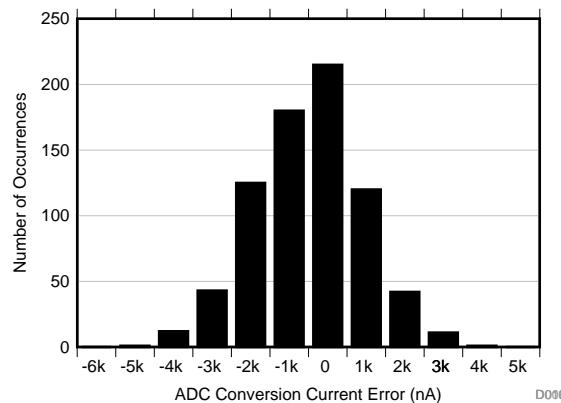


**图 28. Histogram – 12 mA, Gain = 1, SPS = 20, STD = 25.24  
ENOB = 19.34**

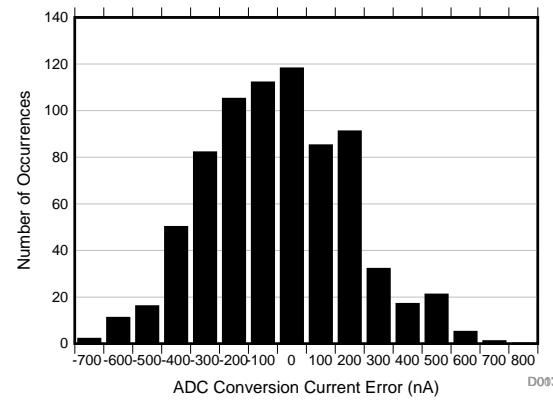


**图 29. Histogram – 12 mA, Gain = 1, SPS = 1000, STD = 163  
ENOB = 16.55**

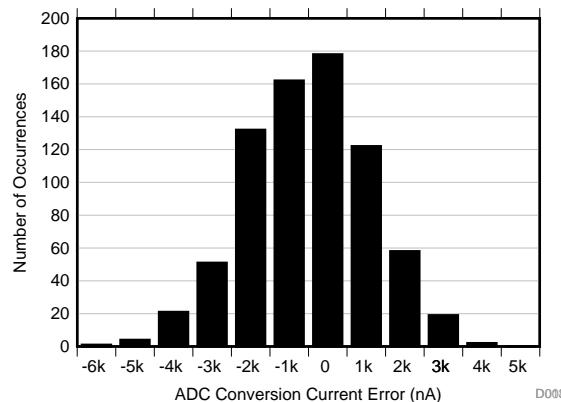

**图 30. Histogram – 20 mA, Gain = 1, SPS = 20, STD = 24.02  
ENOB = 19.41**

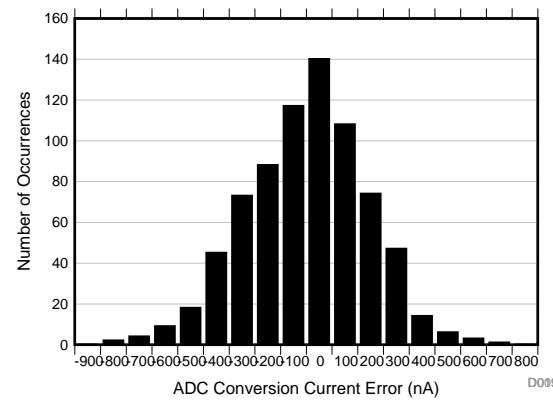

**图 31. Histogram – 20 mA, Gain = 1, SPS = 20, STD = 161.22  
ENOB = 16.67**

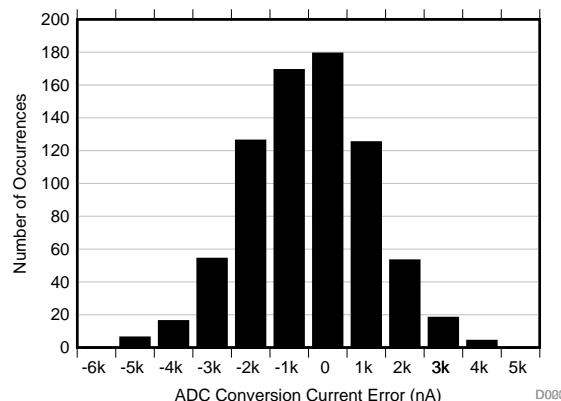

**表 6. Effective Resolution From RMS Noise (Noise-Free Resolution From Peak-to-Peak Noise) at AVDD = 3.3 V, AVSS = 0 V, Normal Mode, PGA Enabled,  $I_{IN}$  = 4 mA, 12 mA, 20 mA and Internal  $V_{REF}$  = 2.048 V, Load Variation From 4–20 mA**

		GAIN (PGA ENABLE)
4-mA Data Rate (SPS)		1
20		19.61 (16.89)
1000		16.85 (14.13)
12-mA Data Rate (SPS)		1
20		19.34 (16.62)
1000		16.65 (13.93)
20-mA Data Rate (SPS)		1
20		19.41 (16.69)
1000		16.67 (13.94)

**表 7. Noise in  $\mu V_{RMS}$  ( $\mu V_{PP}$ ) at AVDD = 3.3 V, AVSS = 0 V, Normal Mode, PGA Enabled,  $I_{IN}$  = 4 mA, 12 mA, 20 mA and Internal  $V_{REF}$  = 2.048 V, Load Variation From 4–20 mA**

		GAIN (PGA ENABLE)
4-mA Data Rate (SPS)		1
20		5.12 (33.8)
1000		34.6 (229)
12-mA Data Rate (SPS)		1
20		6.16 (40.7)
1000		39.8 (263)
20-mA Data Rate (SPS)		1
20		5.87 (38.7)
1000		39.4 (260)

**表 8. Effective Resolution From RMS Noise (Noise-Free Resolution From Peak-to-Peak Noise) at AVDD = 3.3 V, AVSS = 0 V, Normal Mode, PGA Enabled,  $I_{IN}$  = 4 mA, 12 mA, 20 mA and Internal  $V_{REF}$  = 2.048 V, Short Circuit**

4-mA Data Rate (SPS) = 20	Gain (PGA enable) = 1
	19.61 (16.89)
12-mA Data Rate (SPS) = 20	Gain (PGA enable) = 1
	19.34 (16.62)
20-mA Data Rate (SPS) = 20	Gain (PGA enable) = 1
	19.41 (16.69)

**表 9. Noise in  $\mu V_{RMS}$  ( $\mu V_{PP}$ ) at AVDD = 3.3 V, AVSS = 0 V, Normal Mode, PGA Enabled,  $I_{IN}$  = 4 mA, 12 mA, 20 mA and Internal  $V_{REF}$  = 2.048 V, Short Circuit**

4-mA Data Rate (SPS) = 20	Gain (PGA enable) = 1
	5.39 (31.47)
12-mA Data Rate (SPS) = 20	Gain (PGA enable) = 1
	5.91 (31.26)
20-mA Data Rate (SPS) = 20	Gain (PGA enable) = 1
	5.77 (31.32)

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-010048](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-010048](#).

### 4.3 Altium Project

To download the Altium Designer® project files, see the design files at [TIDA-010048](#).

### 4.4 Gerber Files

To download the Gerber files, see the design files at [TIDA-010048](#).

### 4.5 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-010048](#).

## 5 Software Files

To download the software files, see the design files at [TIDA-010048](#).

## 6 Related Documentation

1. Texas Instruments, [Reducing System Cost, Size and Power Consumption in Isolated Data Acquisition Systems Using ADS122U04 Tech Note](#)
2. Texas Instruments, [TVS3300 33-V Flat-Clamp Surge Protection Device Data Sheet](#)
3. Texas Instruments, [LM5180 65-V<sub>IN</sub> PSR Flyback DC/DC Converter With 100-V, 1.5-A Integrated Power MOSFET](#)
4. Texas Instruments, [ADS122U04 24-Bit, 4-Channel, 2-kSPS, Delta-Sigma ADC With UART Interface Data Sheet](#)
5. Texas Instruments, [TPS2662x 60-V, 800-mA Industrial eFuse With Integrated Input and Output Reverse Polarity Protection Data Sheet](#)
6. Texas Instruments, [ISO772x High-Speed, Robust EMC, Reinforced Dual-Channel Digital Isolators Data Sheet](#)
7. Texas Instruments, [TPS7A470x 36-V, 1-A, 4-µVRMS, RF LDO Voltage Regulator Data Sheet](#)
8. Texas Instruments, [TVS3300 33-V Flat-Clamp Surge Protection Device Data Sheet](#)
9. Texas Instruments, [SN74LV4052A Dual 4-Channel Analog Multiplexers and Demultiplexers Data Sheet](#)

## 6.1 商标

E2E is a trademark of Texas Instruments.

Altium Designer is a registered trademark of Altium LLC or its affiliated companies.

All other trademarks are the property of their respective owners.

## 6.2 *Third-Party Products Disclaimer*

TI'S PUBLICATION OF INFORMATION REGARDING THIRD-PARTY PRODUCTS OR SERVICES DOES NOT CONSTITUTE AN ENDORSEMENT REGARDING THE SUITABILITY OF SUCH PRODUCTS OR SERVICES OR A WARRANTY, REPRESENTATION OR ENDORSEMENT OF SUCH PRODUCTS OR SERVICES, EITHER ALONE OR IN COMBINATION WITH ANY TI PRODUCT OR SERVICE.

## 7 About the Author

**BEN SU** is a Field Application Engineer at Texas Instruments. Ben has mixed-signal IC design experience in TSMC fabrication and focused on wireless power IC and SAR ADC during his study career. Ben earned his masters degree in electrical engineering from National Chiao Tung University in Hsinchu, Taiwan.

## 重要声明和免责声明

TI 均以“原样”提供技术性及可靠性数据（包括数据表）、设计资源（包括参考设计）、应用或其他设计建议、网络工具、安全信息和其他资源，不保证其中不含任何瑕疵，且不做任何明示或暗示的担保，包括但不限于对适销性、适合某特定用途或不侵犯任何第三方知识产权的暗示担保。

所述资源可供专业开发人员应用TI 产品进行设计使用。您将对以下行为独自承担全部责任：(1) 针对您的应用选择合适的TI 产品；(2) 设计、验证并测试您的应用；(3) 确保您的应用满足相应标准以及任何其他安全、安保或其他要求。所述资源如有变更，恕不另行通知。TI 对您使用所述资源的授权仅限于开发资源所涉及TI 产品的相关应用。除此之外不得复制或展示所述资源，也不提供其它TI 或任何第三方的知识产权授权许可。如因使用所述资源而产生任何索赔、赔偿、成本、损失及债务等，TI 对此概不负责，并且您须赔偿由此对TI 及其代表造成的损害。

TI 所提供产品均受TI 的销售条款 (<http://www.ti.com.cn/zh-cn/legal/termsofsale.html>) 以及ti.com.cn 上或随附TI 产品提供的其他可适用条款的约束。TI 提供所述资源并不扩展或以其他方式更改TI 针对TI 产品所发布的可适用的担保范围或担保免责声明。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122  
Copyright © 2019 德州仪器半导体技术（上海）有限公司

## 重要声明和免责声明

TI 均以“原样”提供技术性及可靠性数据（包括数据表）、设计资源（包括参考设计）、应用或其他设计建议、网络工具、安全信息和其他资源，不保证其中不含任何瑕疵，且不做任何明示或暗示的担保，包括但不限于对适销性、适合某特定用途或不侵犯任何第三方知识产权的暗示担保。

所述资源可供专业开发人员应用TI 产品进行设计使用。您将对以下行为独自承担全部责任：(1) 针对您的应用选择合适的TI 产品；(2) 设计、验证并测试您的应用；(3) 确保您的应用满足相应标准以及任何其他安全、安保或其他要求。所述资源如有变更，恕不另行通知。TI 对您使用所述资源的授权仅限于开发资源所涉及TI 产品的相关应用。除此之外不得复制或展示所述资源，也不提供其它TI 或任何第三方的知识产权授权许可。如因使用所述资源而产生任何索赔、赔偿、成本、损失及债务等，TI 对此概不负责，并且您须赔偿由此对TI 及其代表造成的损害。

TI 所提供产品均受TI 的销售条款 (<http://www.ti.com.cn/zh-cn/legal/termsofsale.html>) 以及ti.com.cn 上或随附TI 产品提供的其他可适用条款的约束。TI 提供所述资源并不扩展或以其他方式更改TI 针对TI 产品所发布的可适用的担保范围或担保免责声明。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122  
Copyright © 2019 德州仪器半导体技术（上海）有限公司