

设计指南: TIDA-050027

具有灵活分区以最大限度实现节能的多轨电视电源参考设计



说明

TIDA-050027 参考设计是适用于电视 (TV) 平台的配电解决方案。通过提供模拟常用电压轨和外设的配置, 该设计可以用作包含 LCD 和 OLED 电视在内的多种电视电源架构的参考设计。在输入方面, 电子保险丝用于短路保护, 而高效的降压转换器为内核轨、常开电源轨和外设轨提供所需的电源。降压转换器和 LDO 的 5V 电压轨上配备两个电压监控器, 用于监控电压轨并在欠压条件下复位。此外, 低 I_Q 低压降稳压器 (LDO) 为某些外设轨提供低噪声数字电源。除了这些电源组件, 负载开关通过受控压摆率控制电压, 实现电源定序和节省功耗。此外, 集成负载开关提供自我保护, 同时减少物料清单 (BOM) 数量并缩小解决方案尺寸。

资源

- TIDA-050027 设计文件夹
- TPS22919、TPS22975 产品文件夹
- TPS2595、TPS22810 产品文件夹
- TLV755、TLV62568 产品文件夹
- TLV62569A、TLV809E 产品文件夹
- TPS564201、TPS566250 产品文件夹

特性



- 通过常用电视轨的全功能电源树, 可以在系统设计中选择适当的负载开关、降压转换器和 LDO
- 高效降压转换器具有快速瞬态响应和更少的物料清单 (BOM) 数量, 适用于更小的解决方案尺寸
- 集成式保护特性提高系统可靠性并减少客户退货
- 关闭未使用的负载可提高系统效率并降低待机电流
- 与分立式 FET 解决方案相比, 负载开关可提供更小的解决方案尺寸和更少的组件数量
- 高精度电压监控器可确保电压轨的正常运行, 并维护电压监控器上的

应用

- 高清电视
- 超高清 4K OLED 电视
- 超高清 LCD 电视



Search Our E2E™ support forums

  

该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

1 System Description

This reference design showcases a power distribution solution for televisions (TVs). Since many TV architectures require similar core voltage and peripheral rails, this design can be used across multiple TV architectures including OLED and LCD TVs.

This design incorporates four buck converters as well as two LDOs to power the core rails, always-on rails, memory, and peripherals such as USB ports and TV tuner. Each buck converter is chosen to handle specific requirements for each of the rails. For the core rail, the requirements include steady output voltage with very good transient response to avoid affecting performance. The remainder of the rails require high efficiency with good transient response. The LDOs for the peripherals provide a I_Q power supply that also require a clean-power supply such as the TV Tuner.

This design also incorporates nine load switches for peripheral loads commonly found on most TVs including: Panel Power (TCON), Stand-by (STBY) rails, WIFI, NAND, USB, and TV Tuner blocks. All of the load switches have their ON pins connected to external jumpers for quick access to each peripheral rail. An eFuse at the input manages short-circuit and overvoltage events that could potentially damage downstream DC/DC converters and load switches. The reference design also includes common voltage rails found in most TV solutions, including 5 V Peripheral, 3.3 V Standby, 1.5 V DRAM, 3.3 V I/O, and 1.1 V Core rail. Finally, a USB-A header is included at the output of the 5 V USB switch to support USB loads. By using integrated devices, this reference design reduces BOM count, improves system reliability, and enables faster design cycles.

Each main voltage rail (5 V, 3.3 V, and 1.8 V) is accompanied by a discrete FET solution. This allows a direct performance comparison between the integrated load switch and a discrete FET solution. Test points are included at the output of each peripheral and voltage rail, and silkscreen traces outline the size of each solution.

1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	SPECIFICATIONS	DETAILS
Input voltage range	V_{IN}	12 V to 16 V


DEVICES	DEVICES	VIN	VOUT	IOUT
DC/DCS	TPS564201	12 V to 16 V	5 V	4 A
	TPS566250	12 V to 16 V	1 V	6 A
	TLV62569A	5 V	1.5 V	2 A
	TLV62568	5 V	3.3 V	1 A
LDOs	TLV759P	5 V	1.8 V	1 A
	TLV75518	3.3 V	1.8 V	400 mA

PARAMETER	DEVICES	VIN	RON	IOUT
eFuse	TPS2595	12 V to 16 V	34 mΩ	4 A
Load Switch	TPS22810	12 V to 16 V	79 mΩ	2 A
	TPS22975	5 V	16 mΩ	6 A
	TPS22919	5 V, 3.3 V, 1.8 V	89 mΩ at 5 V	1.5 A
USB Switch	TPS25221	5 V	70 mΩ	2 A

2 System Overview

2.1 Block Diagram

图 1. TIDA-050027 Block Diagram

 


2.2 Design Considerations

2.2.1 Total Solution Size

Referring to 图 2, the design is laid out in three main stages: Front-end stage, Power Stage, and Peripherals. Using integrated devices simplifies the solution complexity while keeping the PCB space as compact and space-efficient as possible.

图 2. TIDA-050027 Reference Board

 

The front-end stage includes an eFuse at the input alongside two DC/DCs. The TPS2595 eFuse provides short-circuit and overvoltage protection, while the two DC/DCs emulate voltage rails commonly found on televisions: a 1.1 V core (1V1_CORE) and a 5 V rail for downstream components. The core rail is an always-on, high current rail for the TV SoC, while the 5 V rail leads to downstream power components. The total solution size of the front end components is 111mm², with 7mm² for the eFuse and 104mm² for the DC/DC components.

The power stage components consist of additional DC/DCs to power a 3.3 V standby rail (3V3_STBY), as well as a 1.5 V rail for DRAM or SoC Memory modules. The standby rail is useful when the TV enters a low-power mode, such as a sleep or rest state. The 1.5 V rail is another high current rail used for additional SoC modules, such as a memory or DRAM. The total solution size of the DC/DC components is 56mm². There are also 5 V peripherals connected to the 5 V rail with integrated load switches, including WiFi (5V_WIFI) and USB (5V_USB). A discrete FET implementation is also included to compare performance and size against an integrated solution.

The Peripherals included on this TV reference design emulate common rails and outputs found on TV power designs. A TPS22975 load switch is included at the input of the 5 V peripheral rail, allowing easy access to power down all of the peripherals, for example during standby mode. An LDO converts the 5 V rail into a 3.3 V rail for peripherals including Ethernet, NAND, eMMC, and I/O. Another LDO branches off the 3.3 V down to 1.8 V, providing access to 1.8 V loads such as TV tuners and digital voltage rails required by the SoC. Finally, load switches are included on the front end 12 V line for 12 V rails such as audio and TCON.

表 2. Solution Area Size

Name of Box	Included Components	Total Solution Size
Input Protection	TPS2595	7mm ²
Core / SoC Rail	TPS566250	57mm ²
5 V Main	TPS564201	47mm ²


表 2. Solution Area Size (continued)

Name of Box	Included Components	Total Solution Size
DC/DCs	TLV62568, TLV62569A	56mm ²
Peripherals	TPS22975, TLV757	14.18mm ²

 2.2.2 Power Switching Complexity and Size

As televisions push for higher resolution and greater complexity, their power designs are also getting larger and more complex. As the number of power rails and peripherals increases, additional devices and passive components need to be selected and integrated into the system. As the BOM complexity increases, the number of design considerations increase: including design and layout cycles, PCB space, and points of failure/visual inspection.

A discrete switching circuit contains several components to control the turnon and turnoff behavior of a discrete power MOSFET. 图 3 shows a common discrete FET implementation, which is used on the reference design. In comparison, 图 4 shows a TPS22919 integrated load switch that can also be used to turn on and or off the corresponding load. Compared to a discrete solution, integrated load switches reduce the BOM count, which helps to reduce the total solution complexity and size.



The TPS22919 also contains additional features that are difficult or not possible to implement discretely. Features such as self-protection and recovery from short circuits, controlled slew rate, thermal shutdown, and quick output discharge (QOD), would require additional components or oversized FETs to be done discretely. With an integrated load switch, this can be accomplished using a single device. 节 3.2.2 will demonstrate and compare the discrete circuit and the TPS22919 in-depth, providing power on and or off waveforms, thermal images, and transient event waveforms. For more information regarding the drawbacks and limitations of a discrete switching solution, please refer to [Integrated Load Switches versus Discrete MOSFETs](#) app note.

表 3. Discrete FET vs. TPS22919 Load Switch Comparison

	Discrete Solution	TPS22919
BOM Count	6 components	1 component
Solution Size	17.08mm ²	4.1mm ²
Rise Time	RC Based	Linear, ~1 ms
Thermal Shutdown		✓
Short Circuit Protection		✓

表 3. Discrete FET vs. TPS22919 Load Switch Comparison (continued)


	Discrete Solution	TPS22919
Quick Output Discharge (QOD)	Implemented using External Components	✓

图 5 compares the solution size of both switching solutions. The three discrete FETs, (1V8_DIS, 3V3_DIS, 5V_DIS), consists of 18 components with a total solution size of 275mm². In comparison, the three integrated rails consists of three TPS22919 load switches, with a 76 percent reduction in solution size.

表 4. Discrete vs. Integrated Solution Size

Solution	Included Components	Number of Components	Total Solution Size
3 Load Switches	3* TPS22919 (1V8_TV, 3V3_ETH, 5V_WIFI)	3	12.3mm ²
3 Discrete FETs	3* PMOS FET 3* BJT 9*Resistors 3*Gate Capacitor	18	51.24mm ²

图 5. Discrete vs. Integrated Solution Size

 

2.2.3 Protection Features

Protection features allows for safer and more reliable systems, reducing system failures and customer returns. In television power architectures, features such as inrush current protection, short circuit protection, thermal shutdown, and power sequencing ensure that the system remains robust, while preventing damage to sensitive components.

During startup, inrush current is controlled to protect the MOSFET, PCB traces, and prevent voltage dip that could leave the system in an undesired state. When power is initially applied to the system, capacitor charging can result in a spike of inrush current, which can exceed the nominal load current. The TPS2595 eFuse at the input manages inrush current to the downstream voltage rails, while the TPS22919 manages inrush current to the various peripheral loads. By increasing the rise time of each voltage rail using slew rate control, this minimizes the inrush current while protecting the downstream load. To implement this configuration using discrete components, additional passive components such as a gate resistor and capacitors need to be included, which increases BOM count, solution size, and timing complexity.

The eFuse and integrated load switches also provide short circuit protection and thermal shutdown. The eFuse at the input prevents damage to downstream components in case of an overvoltage/overcurrent or fault condition, while the TPS22919 offers self protection, meaning that it will protect itself from short circuit events on the peripheral rails. The TPS22919 also has thermal shutdown to prevent damage to the device from overheating, which could occur during startup into a capacitive load or a high-current fault condition.

The voltage supervisor allows for monitoring of the buck converter and LDO for undervoltage conditions and turn off appropriately when they reach below the voltage thresholds for each device. When the voltage at the output of these devices falls below the set voltage thresholds for the voltage supervisors, they will output an active-low signal from the $\overline{\text{RESET}}$ pin to disable the devices.


2.2.4 Power Consumption

To reduce standby power for the system, this reference design reduces power consumption by choosing high efficiency and low I_Q power components and by disconnecting loads and peripherals from DC/DC converters when not in use, which is common practice in standby mode.

In this design, load switches are used to emulate various peripheral rails, which can be turned on or off when not in use. If the TV requires all the peripherals to be off in a certain mode, such as standby mode, the TPS22975 can also be used to turn off all the various peripheral rails. The switches can also be used for power sequencing. Power Sequencing is critical for voltage rails that must turn on in a specific order to ensure operation safety and reliability. Sequencing the rails also staggers the inrush current during startup, which reduces system stress and prevents unexpected reverse bias conditions. On this TV power design, the load switches can be sequenced to ensure that the core rails (1V1_CORE, DRAM, Panel), are up before the peripheral rails are operational.

Televisions also contain always-on rails to power critical system components such as core SoC rails, standby rails, and DRAM power. These rails must remain on throughout all operation modes. Therefore, all of the four DC/DC converters remain enabled to emulate powering always-on loads.

图 6. Power Tree

 

2.3 Highlighted Products

2.3.1 TPS22919

The TPS22919 device is a small, single channel load switch with controlled slew rate. When power is first applied, a Smart Pull Down is used to keep the ON pin from floating until system sequencing is complete. When the pin is deliberately driven High ($>V_{IH}$), the Smart Pull Down is disconnected to prevent unnecessary power loss. The TPS22919 load switch is also self-protected, meaning that it will protect itself from short circuit events on the output of the device. It also has thermal shutdown to prevent any damage from overheating.

2.3.2 TPS22810

The TPS22810 is a single channel load switch with configurable rise time and with an integrated quick output discharge (QOD). In addition, the device features thermal shutdown to protect the device against high junction temperature. Because of this, safe operating area of the device is inherently ensured. The device contains an N-channel MOSFET that can operate over an input voltage range of 2.7 V to 18 V.

2.3.3 TPS22975

The TPS22975 is a single-channel load switch that provides a configurable rise time to minimize inrush current. TPS22975 has an optional 230- Ω on-chip load resistor for quick output discharge when switch is turned off. The TPS22975 is available in a small, space-saving 2-mm \times 2-mm 8-pin SON package (DSG) with integrated thermal pad allowing for high power dissipation.

2.3.4 TPS2595

The TPS2595 eFuse (integrated FET hot swap devices) is a highly integrated circuit protection and power management solution in a small package. The device provides multiple protection modes using very few external components and are a robust defense against overloads, short circuits, voltage surges, and excessive inrush current.

2.3.5 TPS566260

The TPS566250 is a 18 V, 6A synchronous step-down (buck) converter with dynamic voltage scaling (DVS) capability through I²c . It operates using D-CAP2™ control mode which provides very fast transient response, and reduces the required output capacitance required to meet a specific level of performance. This device also would not require external compensation which reduces the total size and cost of implementation. The output voltage of the device can be set by either FB with resistor divider or it can be dynamically set from 0.6 V ~ 1.87 V through I²C compatible interface.

2.3.6 TPS564201A

The TPS564201 is a simple, easy-to-use, 4-A synchronous step-down converter in SOT-23 package. The device is optimized to operate with minimum external component count and also optimized to achieve high efficiency at both normal and light load conditions. This solution is a part of a pin-to-pin compatible family of devices (TPS56x201) which would support from 1A ~5A current loads.

2.3.7 TLV65268

The TLV62568 device is a synchronous step-down buck DC-DC converter optimized for high efficiency and compact solution size. The device integrates switches capable of delivering an output current up to 1A. In order to provide the lowest power consumption for an always on rail, the device enters power save mode at light loads. If lower ripple is required, the TLV62568A can be used instead. In shutdown, the current consumption is reduced to less than 2 μ A.

2.3.8 TLV65269A

The TLV62569A device is a synchronous step-down buck DC-DC converter optimized for high efficiency and compact solution size. The device integrates switches capable of delivering an output current up to 2 A. In order to provide the lowest ripple and best transient response for powering the DRAM rail, the device operates only in pulse width modulation (PWM) mode without a power saving mode. If light load efficiency is important, the TLV62569 can be used instead. In shutdown, the current consumption is reduced to less than 2 μ A.

2.3.9 TLV755/7P

The TLV755P is an ultra-small, low quiescent current, low-dropout regulator (LDO) that sources 500mA and 1 A for the TLV757P, with good line and load transient performance. The TLV755P is optimized for a wider variety of applications by supporting an input voltage range from 1.45 V to 5.5 V. To minimize cost and solution size, the device is offered in fixed output voltages ranging from 0.6 V to 5 V to support the lower core voltages of modern microcontrollers (MCUs). Additionally, the TLV755P has a low I_Q with enable functionality to minimize stand-by power. When shutdown, the device actively pulls down the output to quickly discharge the outputs and ensure a known start-up state.

2.3.10 TLV758/9P

The TLV759P low-dropout regulator (LDO) is an adjustable output, ultra-small, low quiescent current LDO that sources 1 A and 500mA for the TLV758P, with good line and load transient performance. The TLV759P is optimized for a wide variety of applications by supporting an input voltage range from 1.45 V to 5.5 V. Additionally, the TLV759P has a low I_Q with enable functionality to minimize standby power. When shutdown, the device actively pulls down the output to quickly discharge the outputs and ensure a known start-up state. Furthermore, the TLV759P supports adjustable output via resistor divider for voltage options not supported by the TLV755/7.

2.3.11 TLV809E

The TLV809E voltage supervisor is a low current (250 nA typical, 2 μ A max) circuit (reset IC) that monitors a V_{DD} voltage level. This device initiates a reset signal whenever supply voltage drops below the factory programmed threshold voltage, V_{IT} . The reset output remains low for a fixed reset time delay t_D after the V_{DD} voltage rises above the threshold voltage and hysteresis.

3 Hardware, Software, Testing Requirements, and Test Results

3.1 Required Hardware

3.1.1 System Overview

The TIDA-050027 TV Reference Design power rails can be sequenced depending on the downstream loads and peripherals. 表 5 provides an overview of the jumpers and test points on the TI Design.

表 5. Jumper/Connector Summary

Stage	Connector	Label	Description
Input	J2	-	Input Power, connector for 12 - 16 V
	JP9	-	Enable for TPS2595 (U12)
	TP21	12V_UP	Test Point for eFuse output
CORE / SoC Rail	JP11, TP23, TP24	SDA / SCL	Test Points for TPS566250 communication
	TP22	1V1_Core	Test Point for DC/DC output
5 V Main	TP25	5V_Down	Test Point for DC/DC output
DC/DCs	TP19	1V5_DRAM	Test Point for DC/DC output
	TP20	3V3_STBY	Test Point for DC/DC output
Peripherals	JP5	Peripheral_EN	Enable for TPS22975
	TP14	5V_Periph	Output of 5 V Peripheral Rail
Load Switches	JP10	12V_EN	Enable for TPS22810
	JP2	3V3_EN	Enable for TPS22919
	JP1	1V8_EN	Enable for TPS22919
	JP7	5V_EN	Enable for TPS22919
	TP8	TV	Output of 1.8 V Peripheral Rail
	TP1	TCON	Output 12 V Rail
	TP4	Audio	Output 12 V Rail
	TP9	Ethernet	Output of 3.3 V Peripheral Rail
	TP10	NAND	Output of 3.3 V Peripheral Rail
	TP11	3V3_Panel	Output of 3.3 V Standby Rail
	TP12	WIFI	Output of 5 V Peripheral Rail
	Discrete FETs	JP3	1V8_D_EN
JP4		3V3_D_EN	Enable for Discrete FET
JP8		5V_D_EN	Enable for Discrete FET
TP5		1V8_Dis	Output of 1.8 V Discrete Rail
TP6		3V3_Dis	Output of 3.3 V Discrete Rail
TP7		5V_Dis	Output of 5 V Discrete Rail

3.2 Testing and Results

3.2.1 Test Setup

To configure the reference design for operation, connect the jumpers as shown in 图 7.

图 7. TIDA-050027 Test Configuration

 


表 6. TV Configuration Setup


Description	Jumper / Connector	Value
Input Power, connector for 12 - 16 V	J2	Connect pins 1 and 2
12 V Load Switch enable	JP5, JP10	Connect pins 1 and 2
5 V, 3.3 V, 1.8 V Load Switch enable	JP1, JP2, JP6, JP7	Connect pins 1 and 2
Discrete FET Enable	JP3, JP4, JP8	Connect pins 1 and 2

3.2.2 Test Results

 3.2.2.1 Power Sequencing Demonstration

Power Sequencing is critical on voltage rails that must turn on in a specific order to ensure operational safety and reliability. For example, core rails for downstream SoCs and microcontrollers need to be powered before WIFI and other peripherals are turned on. Sequencing the rails also helps stagger the inrush current during power-up, which reduces system stress and prevents unexpected reverse bias conditions.

The TV Reference Design’s voltage rails are sequenced to emulate the power-on of a television system. After the system is initially turned on, the 12 -16 V input passes downstream and turns on the two critical rails, 1V1_Core and 5 V Main. Once both of these rails are high, the 5 V Peripherals are turned on followed by the 3.3 V and 1.8 V Peripherals. 图 8 和 图 9 demonstrate the power-on sequence.



3.2.2.2 Standby Power Demonstration

The system standby current measurements were taken in various on/off modes. In standby mode, the measured input current was 1.256mA. This includes all of the necessary “always-on” core rails, including 1V1_Core and 3V3_STBY. With all of the peripherals and load switches enabled, the design was drawing roughly 1.5mA of quiescent current. This accounts for all of the LDOs and peripheral load switches, which drew an additional 220 μA current when enabled. In comparison, three discrete FETs drew roughly 500μA when enabled.

表 7. Measured Input Current

Mode of Operation	Devices Enabled	Measured Input Current
Standby Mode	TPS2595, TPS566250, TPS564201, TLV62569A, TLV62568	1.256mA
Everything on except Discrete FETs	TPS2595, TPS566250, TPS564201, TLV62569A, TLV62568, TPS22975, TLV757, TPS22919	1.478mA
All Devices Enabled	TPS2595, TPS566250, TPS564201, TLV62569A, TLV62568, TPS22975, TLV757, TPS22919, 1V8_Dis, 3V3_Dis, 5V_Dis	1.923mA


3.2.2.3 Discrete FET vs. Integrated Load Switch Comparison

表 8. Turn On/Off Summary Table

Voltage	Parameter	Description	Section
1.8 V	1.8 V Capacitive Load	100uF	图 10
	1.8 V Load	100uF, 3.6Ω (500mA)	图 11
3.3 V	3.3 V Capacitive Load	100uF	图 12
	3.3 V Load	100uF, 5.5Ω (600mA)	图 13
5 V	5 V Capacitive Load	100uF	图 14
	5 V Load	100uF, 1Ω (1A)	图 15

 
3.2.2.3.1 1.8V Load Demonstration

As shown in 图 4 the discrete solution contains an NPN BJT is connected to the gate of the PMOS "pass FET." When the NPN BJT is enabled, it pulls down the gate of the PMOS and allows for power to flow from VIN to VOUT. However, compared to a TPS22919 solution, the discrete solution comes with a set of limitations. During power on and or off sequences, the discrete solution will have a nonlinear (RC) turn-on behavior, which can lead to a large spike of inrush current. The following waveforms will compare/contrast the turnon behaviors overlaid on one another. In the first waveform, 图 10, both switching solutions are starting into a 100uF capacitive load. The TPS22919 exhibits a linear turn on behavior, limiting the inrush current to roughly 200mA. In comparison, the discrete solution experiences a peak of over 400mA of inrush current. In 图 11, both solutions are starting into a 500mA / 100uF load. The TPS22919 helps to manage the inrush current with the controlled slew rate, while the discrete solution peaks at 700mA of inrush current.




3.2.2.3.2 3.3V Load Demonstration

图 12 和 图 13 provide a comparison between the discrete solution and the TPS22919 at 3.3 V. When starting into a capacitive load, the TPS22919 limits the inrush current to 250mA while the inrush current on the discrete solution jumps to 700mA. When starting into a 1A load with 100uF of capacitance, the TPS22919 limits the inrush current while the discrete FET peaks to 1A.

 

3.2.2.3.3 5 V Load Demonstration


图 14 和 图 15 提供在 5 V 下离散方案与 TPS22919 的比较。当启动进入容性负载时，TPS22919 将浪涌电流限制为 250mA，而离散方案的浪涌电流跃升至 1.3A。当启动进入带有 100uF 电容的 1A 负载时，TPS22919 限制浪涌电流，而离散 FET 峰值超过 1.75A。

 

3.2.2.3.4 Thermal Protection


热关断保护设备在设备结温超过其安全限值时防止设备故障。在操作期间，结温可能因许多因素而升高，包括高电流负载、启动期间的大浪涌电流或故障条件。热保护通过减少功耗来保护自身，也可能避免上游和下游组件损坏。相比之下，离散 FET 如果超过其热结温，则无法保护自己。在这种情况下，FET 可能会损坏，导致短路并损坏下游负载或外围设备。

图 16 和 图 17 提供 TPS22919 在 25°C 下高电流负载下的热成像图。在此场景中，3A 负载连接到 3V3_Eth，导致结温升高。随着温度超过 144°C，TPS22919 关闭并进行热循环，将板温降低到约 85°C。

 

In comparison, 图 18 shows the package temperature of the discrete FET at 25C under the same 3A load. The 3.3 V discrete FET will continue to power the downstream load until it fails. Unlike the TPS22919, the discrete FET does not have thermal shutdown, and will continue to be thermally stressed until the load is removed. If the FET is stressed beyond its absolute maximum rating, the device could also potentially be damaged. At higher ambient temperatures, the discrete FET will continue to be stressed beyond 143C, whereas the TPS22919 will continue to protect itself and thermally cycle.

图 18. Discrete FET Thermal Image

 


3.2.2.3.5 Transient Protection Features

TV Power Architectures can be stressed during startup and fault conditions. During these conditions, discrete FETs can dissipate more power that exceeds the physical and thermal limits of the MOSFET. If proper tests aren't taken into consideration, the system can fail due to overstressing these components. Additionally, some of these fault conditions, such as short circuit protection and hot plug protection, are often difficult to implement discretely and require additional components and design complexity. By using integrated devices on the TIDA-050027, these additional protection features can make the design more robust while simplifying the design.


The first major transient event that could severely damage the system is *Power Into Short*. In this condition, the output of the FET / IC is shorted to ground before the switch is turned on. As the FET is turned on, VOUT remains grounded at 0V. Therefore, the stress across the FET is equal to VIN. The power dissipated into the FET is equal to VIN * IOUT. Done discretely, as shown in 图 19, the FET doesn't limit the current in the transient event and passes 10A of current downstream. Since the junction temperature of the FET exceeds its thermal limit during this event, the FET is damaged and sends 10A of continuous current to the downstream component.

In comparison, the TPS22919 integrated load switch is self-protecting and prevents damaging itself during the power into short event. When the short occurs, the large VIN to VOUT voltage drop causes the switch to limit the output current (Isc). Since the output voltage starts at 0 V, a lower limit is used to minimize the power dissipation until the fault is removed. In this case, as shown in 图 20, the TPS22919 limits the output current to 0.5A while protecting itself from damage.

 

The other major transient event that could severely damage the system is *Hot Short*. In this condition, the output of the FET / IC is shorted to ground when the device is already turned on. This event is considered the more stressful event since the switch usually starts out hotter due to the pre-existing load current. The power dissipated into the switch is equal to VIN * IOUT. 图 21 demonstrates a discrete implementation. Since the discrete FET doesn't limit the current in the transient, more than 10A passes downstream and the FET fails.

In comparison, the TPS22919 integrated load switch measures the voltage drop across the device and limits the output current within t_{sc} . The device continues to limit the current until it reaches the thermal shutdown temperature. At this point, the device turns off until the junction temperature has lowered. As shown in 图 22 the TPS22919 limits the output current and turns off, dropping the output voltage to 0 V and protecting itself from damage.

 

3.2.2.4 DC/DC Efficiency and Transient Testing Results

图 23, 图 24, 图 25, 和 图 26 提供了 TIDA-050027 DC/DC 效率结果。图 27, 图 28, 图 29, 图 30, 图 31, 和 图 32 提供了 TIDA-050027 DC/DC 瞬态响应。

 


图 27. TLV62568 Transient Response

 


图 28. TLV62569A Transient Response

 


图 29. TPS564201 12V Transient Response

 


图 30. TPS564201 16V Transient Response

 


图 31. TPS566250 12V Transient Response


 


图 32. TPS566250 16V Transient Response

 

4 Design Files

4.1 Altium Project

To download the Altium Designer® project files, see the design files at [TIDA-050027](#).

4.2 Schematics

To download the schematics, see the design files at [TIDA-050027](#).

4.3 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-050027](#).

4.4 PCB Layout Recommendations

4.4.1 Layout Prints

To download the layer plots, see the design files at [TIDA-050027](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-050027](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-050027](#).

5 Software Files

To download the software files, see the design files at [TIDA-050027](#).

6 Related Documentation

1. [Integrated Load Switches versus Discrete MOSFETs](#) app report
2. [Basics of Power Switches](#) app report

6.1 商标

E2E is a trademark of Texas Instruments.

Altium Designer is a registered trademark of Altium LLC or its affiliated companies.

All other trademarks are the property of their respective owners.

6.2 Third-Party Products Disclaimer

TI'S PUBLICATION OF INFORMATION REGARDING THIRD-PARTY PRODUCTS OR SERVICES DOES NOT CONSTITUTE AN ENDORSEMENT REGARDING THE SUITABILITY OF SUCH PRODUCTS OR SERVICES OR A WARRANTY, REPRESENTATION OR ENDORSEMENT OF SUCH PRODUCTS OR SERVICES, EITHER ALONE OR IN COMBINATION WITH ANY TI PRODUCT OR SERVICE.

修订历史记录

注：之前版本的页码可能与当前版本有所不同。

Changes from A Revision (May 2019) to B Revision	Page
• 已添加 降压转换器和 LDO 的 5V 电压轨上配备两个电压监控器，用于监控电压轨并在欠压条件下复位。	1
• 已添加 产品文件夹	1
• 已添加 电压水平信息。	1
• 已更改 更改了方框图以包含 TLV809E.....	1
• 已添加 TLV809E to block diagram.	4
• 已添加 section on voltage supervisors.....	9
• 已添加 new section on TLV809E.	11

Changes from Original (May 2019) to A Revision	Page
• 已更改 将标题从适用于电视的电源开关参考设计 更改为具有灵活分区以最大限度实现节能的多轨电视电源参考设计	1

重要声明和免责声明

TI“按原样”提供技术和可靠性数据（包括数据表）、设计资源（包括参考设计）、应用或其他设计建议、网络工具、安全信息和其他资源，不保证没有瑕疵且不做任何明示或暗示的担保，包括但不限于对适销性、某特定用途方面的适用性或不侵犯任何第三方知识产权的暗示担保。

这些资源可供使用 TI 产品进行设计的熟练开发人员使用。您将自行承担以下全部责任：(1) 针对您的应用选择合适的 TI 产品，(2) 设计、验证并测试您的应用，(3) 确保您的应用满足相应标准以及任何其他功能安全、信息安全、监管或其他要求。

这些资源如有变更，恕不另行通知。TI 授权您仅可将这些资源用于研发本资源所述的 TI 产品的应用。严禁对这些资源进行其他复制或展示。您无权使用任何其他 TI 知识产权或任何第三方知识产权。您应全额赔偿因在这些资源的使用中对 TI 及其代表造成的任何索赔、损害、成本、损失和债务，TI 对此概不负责。

TI 提供的产品受 [TI 的销售条款](#) 或 [ti.com](#) 上其他适用条款/TI 产品随附的其他适用条款的约束。TI 提供这些资源并不会扩展或以其他方式更改 TI 针对 TI 产品发布的适用的担保或担保免责声明。

TI 反对并拒绝您可能提出的任何其他或不同的条款。

邮寄地址：Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2022，德州仪器 (TI) 公司