

设计指南: TIDA-050032

5V 输出、4000V 隔离电源参考设计



说明

此参考设计针对 RS485 在数据集中器中的应用，介绍了具有 5V、200mA 输出的反激式直流/直流电源转换器。4000VAC 隔离电源电路使用完全集成的转换器 TLV61046A 和现成的变压器，这是一种既简单又具有成本效益的解决方案。整个电路易于复制到系统板上，从而为 RS485 器件供电，这大大缩短了电路原理图和布局的设计时间。用户指南提供了详细的基准测试结果（如效率、负载调节和工作波形），供您参考。

资源

TIDA-050032
TLV61046A

设计文件夹
产品文件夹

特性



- 4.5V 至 5.5V 输入电压范围
- 具有 200mA 最大输入电流的 5V 输出电压
- 4000VAC 隔离变压器
- 初级侧调节，可大大降低系统成本
- 已使用评估板对电路进行测试

应用

- 电表
- 数据集中器



Search Our E2E™ support forums

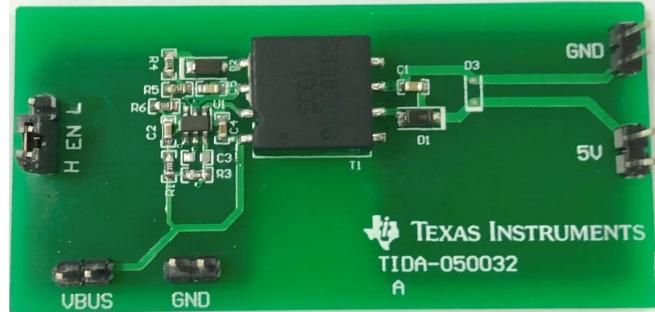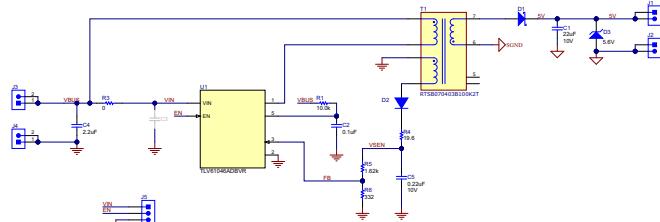

该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

1 System Description

The reference design introduces a 5-V, 200-mA output Flyback converter based on the TLV61046A used for the power supply of the RS485 in the electricity meter and data concentrator. The input voltage ranges from 4.5 V to 5.5 V and the switching frequency is typical 1MHz. By utilizing a third winding to regulate the output voltage, high cost and complex secondary control circuit can be removed. However, the output voltage would change 5.3 V to 4.75 V with output current from 20 mA to 200 mA. The isolation voltage of the transformer used in the reference design is 4000-V AC.

1.1 Key System Specifications

表 1 provides the electrical specification of the reference design. Operating conditions outside the range of the table are also possible if the electrical specification is within the value specified in the TLV61046A data sheet ([SLVSD82A](#)).

表 1. Key System Specifications

PARAMETER	MINIMUM	TYPICAL	MAXIMUM	UNIT
V_{BUS} , Input voltage	4.5	5	5.5	V
V_{OUT} , Output voltage	4.5	5	5.5	V
I_{OUT} , Output current	20	—	200	mA
Isolation voltage	4000	—	—	Vac

2 System Overview

2.1 Design Considerations

The two important technical problems to design a flyback DC-DC converter are the control IC and the transformer design. Considering the voltage rating of the switching MOSFET and output current of the reference design, TLV61046A is selected. The primary side control method is adopted to reduce the solution cost. Because the target loading is RS485 IC, which can accept wide voltage range. The transformer is built by Sunlord Electronics. This helps to provide consistent behavior in reference design board and customer's system board.


2.2 System Design Theory

图 1 shows the schematic of the reference design based on a flyback topology DC-DC. The main components in the circuit are the boost converter IC TLV61046A, transformer T1, Schottky diode D1, output capacitor and voltage sensing resistors.

The TLV61046A is boost converter integrated both the low side MOSFET and high side rectifier. The TLV61046A use a peak current, adaptive off-time control topology to regulate its FB pin voltage at 0.8 V. The winding ratio of the transformer is 1:1:1. The auxiliary winding between pin 3 and pin 4 is used to generate a voltage VSEN which is controlled by TLV61046A. By regulating the voltage at VSEN to approximately 5 V, the V_{OUT} will be 5 V. The transformer has 10- μ H inductance if the current is lower than 1 A.

The DC voltage stress of D1 is ($V_{BUS}+V_{OUT}$), which is typical 10 V. Considering voltage spike during converter switching, the Schottky voltage rating should be not lower than 20 V, and its current rating should be higher than 200 mA.

图 1. TIDA-050032 Schematic

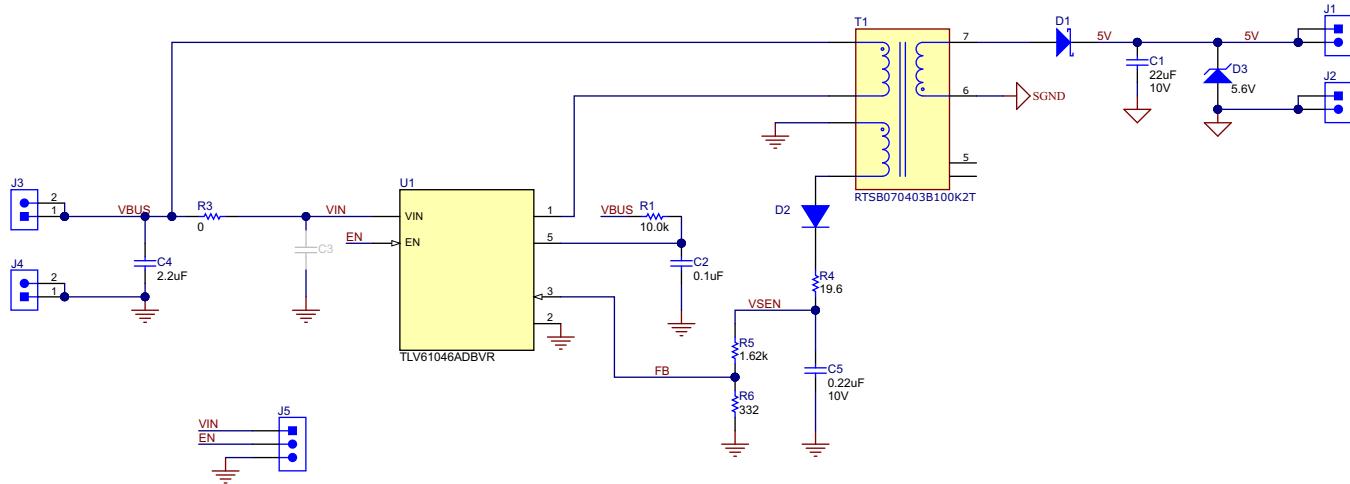

The output capacitor is selected by the output ripple requirement, defined by 公式 1. Setting 25-mV output voltage ripple at 200-mA loading condition, the effective output capacitance will be 4 μ F. Considering DC bias effect of the ceramic capacitor, at least a 10- μ F capacitor should be selected.

$$\Delta V_{OUT} = \frac{I_{OUT} \times D}{C_{OUT} \times f_{SW}} \quad (1)$$

where

- $f_{sw} = 1$ MHz, the switching frequency of the TLV61046A in CCM
- $D = 0.5$, typical duty cycle at CCM

The ratio of R5 and R6 and internal reference voltage defines the voltage level at VSEN node, as shown in [公式 2](#). Considering the forward voltage gap between the diode D2 and the Schottky D1, the VSEN voltage is set to typical 4.7 V. The sum of the R5 and R6 is approximately 2 K Ω , which adds 2.4 mA dummy load to VSEN. The dummy load is to improve the load regulation performance resulted from the non-ideal transformer and diodes. The R1 also acts as the same purpose.

$$V_{SEN} = \frac{R5 + R6}{R6} \times V_{REF} \quad (2)$$

where

- $V_{REF} = 0.798$ V
- R5 and R6 can be found in [图 1](#)

The C2 connected to the V_{OUT} pin of the TLV61046A is to provide stable voltage for the IC's internal circuit. The capacitor also acts as snubber capacitor to reduce the voltage spike in the SW pin.

3 Hardware, Testing Requirements and Test Results

3.1 Required Hardware

3.1.1 Hardware

One DC power supply, one electronic load, and an oscilloscope are required in the test. the DC power supply is used to power the board with voltage from 4.5 V to 5.5 V, while the e-load can easily add 20 mA to 200 mA loading to the board. The oscilloscope is to observe the operating waveform of input, output, and other pins in the board.

3.2 Testing and Results

3.2.1 Test Setup

The test is set up with TIDA-050032 board. A 5-V power supply is connected to the VBUS and GND connection. An e-load is connected to 5-V output connection. The EN pin is connected to H to enable the board. The waveform can be captured in the connection or the pins of each of the components.

3.2.2 Test Results

The efficiency and load regulation at different input voltage and ambient temperature can be found in [图 2](#) to [图 7](#).

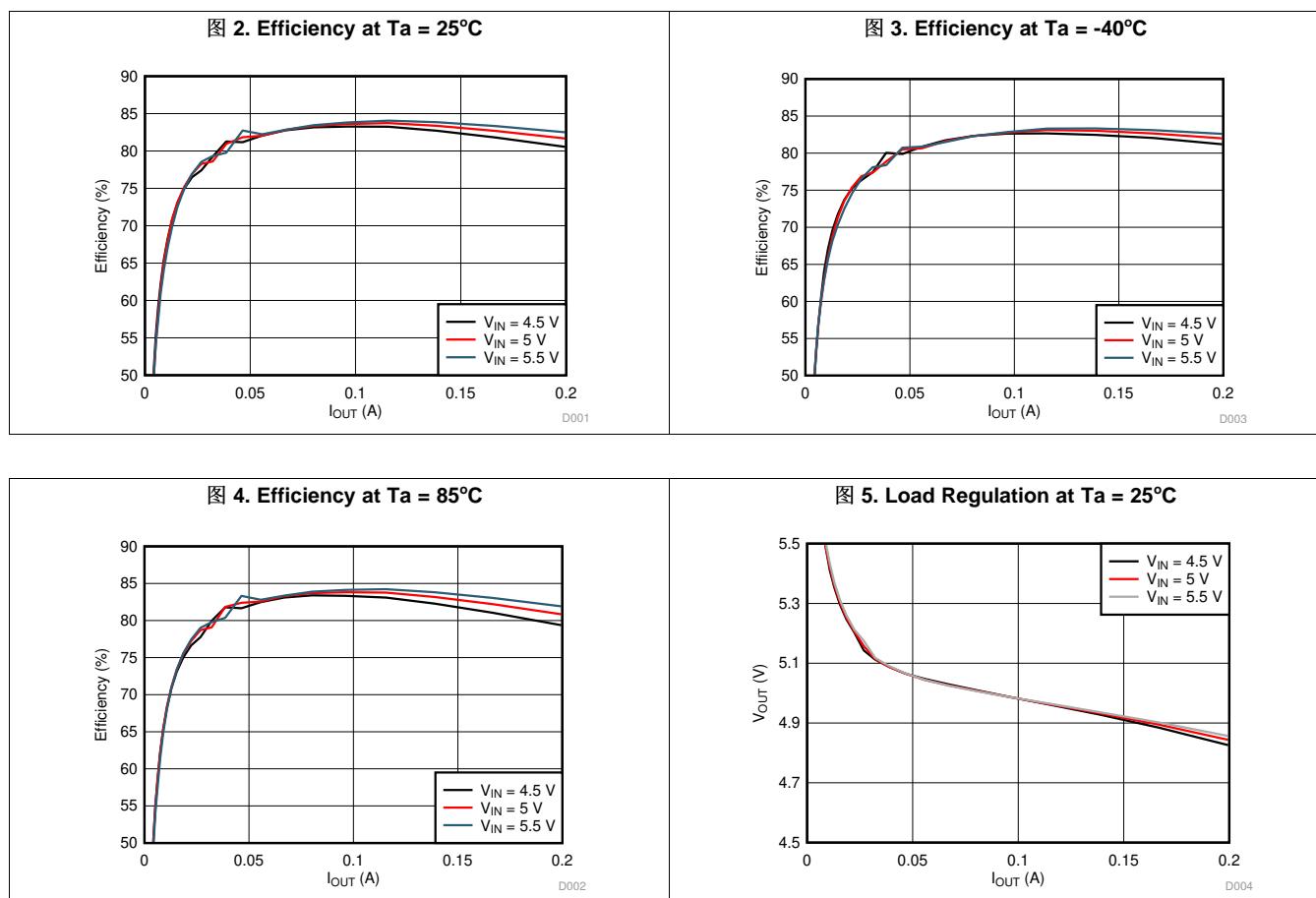
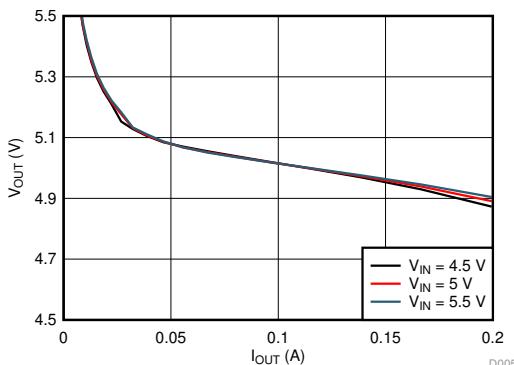
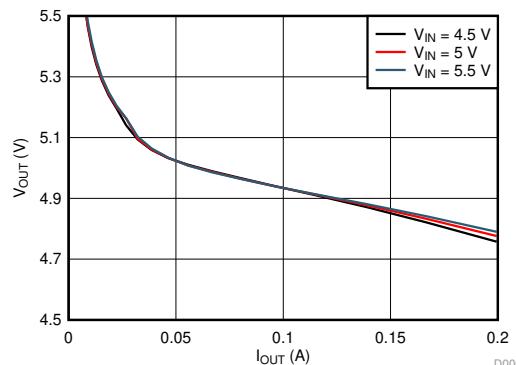
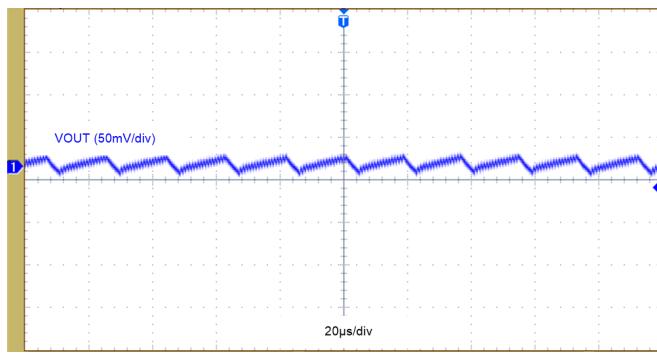
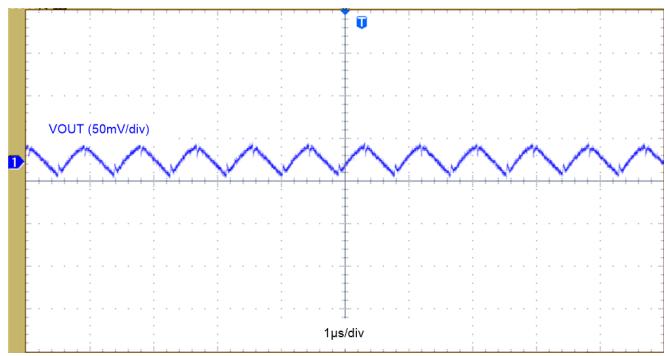


图 6. Load Regulation at $T_a = -40^\circ\text{C}$ 图 7. Load Regulation at $T_a = 85^\circ\text{C}$ 

The stable output ripple at 20mA and 200mA output current condition is shown in 图 8 and 图 9 respectively. The TLV61046A operates at power save mode at 20-mA loading condition. The ripple is less than 50 mV. At 200-mA loading condition, the ripple frequency is 1 MHz, and its peak-to-peak value is approximately 30 mV.

图 8. Output Voltage Ripple at $I_{\text{OUT}} = 20\text{ mA}$ 图 9. Output Voltage Ripple at $I_{\text{OUT}} = 200\text{ mA}$ 

The load transient between 20mA and 200mA is shown in 图 10. The waveform clearly shows that the DC output voltage drops 400 mV at full loading condition, but there is not oscillation during the load transient.

The startup waveform at 20mA loading condition is shown in 图 11.

图 10. Load Transient from 20 mA to 200mA


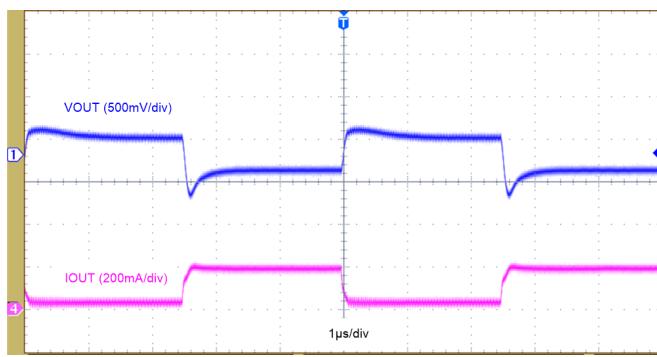


图 11. Startup Waveform at 20-mA Loading

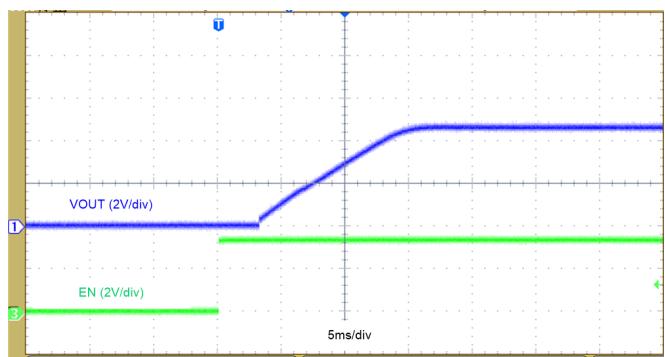

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [TIDA-050032](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-050032](#).

4.3 PCB Layout Recommendations

4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-050032](#).

4.4 Altium Project

To download the Altium Designer® project files, see the design files at [TIDA-050032](#).

5 Related Documentation

1. [TLV61046A 28-V Output Voltage Boost Converter with Power Diode and Isolation Switch data sheet \(SLVSD82A\)](#)

5.1 商标

E2E is a trademark of Texas Instruments.

Altium Designer is a registered trademark of Altium LLC or its affiliated companies.

All other trademarks are the property of their respective owners.

重要声明和免责声明

TI“按原样”提供技术和可靠性数据（包括数据表）、设计资源（包括参考设计）、应用或其他设计建议、网络工具、安全信息和其他资源，不保证没有瑕疵且不做出任何明示或暗示的担保，包括但不限于对适销性、某特定用途方面的适用性或不侵犯任何第三方知识产权的暗示担保。

这些资源可供使用 TI 产品进行设计的熟练开发人员使用。您将自行承担以下全部责任：(1) 针对您的应用选择合适的 TI 产品，(2) 设计、验证并测试您的应用，(3) 确保您的应用满足相应标准以及任何其他功能安全、信息安全、监管或其他要求。

这些资源如有变更，恕不另行通知。TI 授权您仅可将这些资源用于研发本资源所述的 TI 产品的应用。严禁对这些资源进行其他复制或展示。您无权使用任何其他 TI 知识产权或任何第三方知识产权。您应全额赔偿因在这些资源的使用中对 TI 及其代表造成任何索赔、损害、成本、损失和债务，TI 对此概不负责。

TI 提供的产品受 [TI 的销售条款](#) 或 [ti.com](#) 上其他适用条款/TI 产品随附的其他适用条款的约束。TI 提供这些资源并不会扩展或以其他方式更改 TI 针对 TI 产品发布的适用的担保或担保免责声明。

TI 反对并拒绝您可能提出的任何其他或不同的条款。

邮寄地址 : Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, 德州仪器 (TI) 公司