

TI Designs

高精度アナログ・フロントエンド・アンプおよびペリフェラル、MCCB - 電子トリップ・ユニット用



TI Designs

TI Designsは、システムをすばやく評価してカスタマイズするために必要な、手法、テスト、デザイン・ファイルなどの基盤を提供し、開発期間の短縮に役立ちます。

デザイン・リソース

TIDA-00128	デザイン・フォルダ
TINA Spice	製品フォルダ
LM5017	製品フォルダ
LM62BIM3	製品フォルダ
CSD18537NKCS	製品フォルダ
LM4041B	製品フォルダ
TPS71533	製品フォルダ
TPS55010	製品フォルダ
ISO1176	製品フォルダ
LM293	製品フォルダ

デザインの特長



- $-10^{\circ}\text{C} \sim +70^{\circ}\text{C}$ の範囲で周囲環境の影響を受けず、世界各国に対応したグローバルな設計が可能
- トリップ時間の再現性の向上
- 低電圧保護と過電流保護を備えた広入力DC-DCコンバータ
- CTの負荷および電力損失を低減したセルフパワー(CT給電)電源
- 過駆動状態での位相反転を防ぐ堅牢な設計と、高い静電気放電(ESD)保護(4kV HBM)
- MCCB/ACBの要件に対応した $-40^{\circ}\text{C} \sim 125^{\circ}\text{C}$ のデバイス動作温度

主なアプリケーション

- MCCB - 電子トリップ・ユニット(電子リリース)
- ACB - 電子トリップ・ユニット(電子リリース)
- セルフパワー型の過電流/地絡リレー、数値リレー



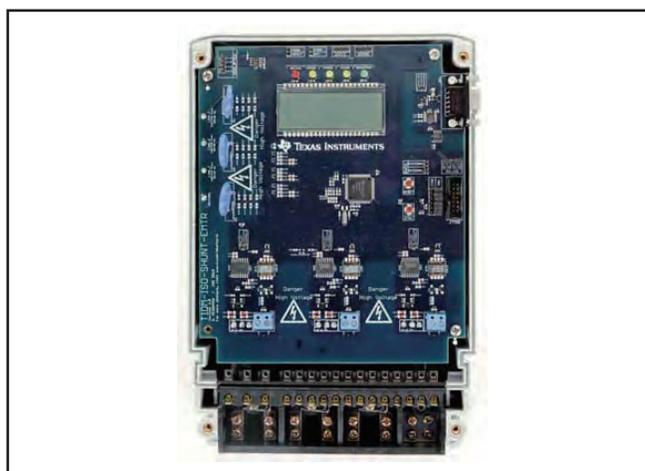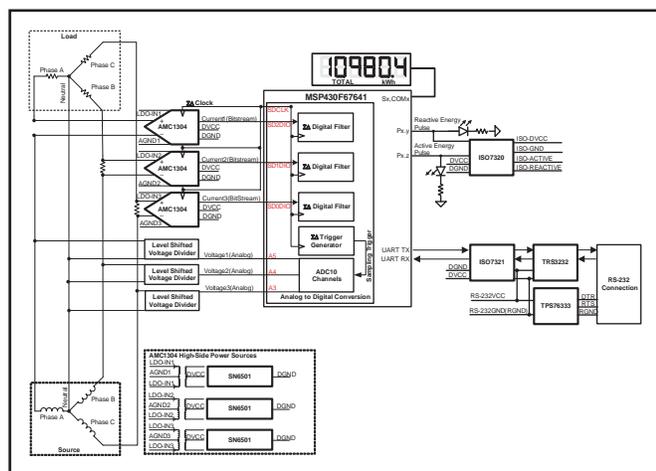[ASK Our Analog Experts](#)
[WebBench™ Calculator Tools](#)



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

WebBench, NexFET, Tiva, Cortexは、テキサス・インスツルメンツの商標です。ARMは、テキサス・インスツルメンツの登録商標です。

この資料は、Texas Instruments Incorporated(TI)が英文で記述した資料を、皆様のご理解の一助として頂くために日本テキサス・インスツルメンツ(日本TI)が英文から和文へ翻訳して作成したものです。資料によっては正規英語版資料の更新に対応していないものがあります。日本TIによる和文資料は、あくまでもTI正規英語版をご理解頂くための補助的参考資料としてご使用下さい。製品のご検討およびご採用にあたりましては必ず正規英語版の最新資料をご確認下さい。TIおよび日本TIは、正規英語版にて更新の情報を提供しているにもかかわらず、更新以前の情報に基づいて発生した問題や障害等につきましては何なる責任も負いません。

TIDU224 翻訳版

最新の英語版資料
<http://www.ti.com/lit/tidu224>

1 システム説明

この配線用遮断器 (MCCB) - TIでは、回路ブレーカに流れる電流の大きさに応じて動作する電子トリップ・ユニット(MCCB-ETU)を設計しています。これらのトリップ・ユニットは、電流センサから電力が供給され、わずかな最小電流だけで動作できます。電子トリップ・ユニットでは、デジタル・サンプリングを使用して、正弦波電流および非正弦波電流のRMS値を求めます。

ETUには、次のような利点があります。

- 正確なセンシング - ピックアップおよびトリップのタイミング
- -10°C ~ 70°C で周囲環境からの影響なし
- 調整可能な I_r (定格電流) による連続電流設定
- ピックアップ (A) 精度: $\pm 10\%$ 、遅延時間精度: $0 \sim -20\%$
- トリップに対するフォールト・ピックアップ電流入力範囲を $0.2 \sim 10 \times I_r$ の範囲で調整可能

電流入力をセンサするためには、低コストのオペアンプを使用して信号調整を行います。

低コストのオペアンプには、いくつかの制限があります。

1. DC出力オフセットが高く、レール・ツー・レール出力が低いため、ADCの範囲が制限される。
2. ピックアップおよびトリップのタイミング特性が $-10^{\circ}\text{C} \sim +70^{\circ}\text{C}$ の範囲内で変動
3. 短絡保護時の位相反転の問題により、ピックアップおよびトリップのタイミングの再現性が低下する
4. 高い入力バイアス電流によって、入力CTに負荷がかかり、測定に非直線性が生じる
5. TIではトリップ・ユニットをブレーカ・ユニットの内部に配置しているため、トリップ・ユニットが高い電磁干渉にさらされ、外部フィルタが必要となる
6. 製造時に、より多くのテストが必要

このリファレンス・デザインでは、以下の長所を備えたアナログ・フロントエンド・アンプを提供します。

1. DCオフセットが低く、レール・ツー・レール出力電圧が高いため、精度が向上
2. $-10^{\circ}\text{C} \sim +70^{\circ}\text{C}$ の範囲内で高精度および高い再現性 (ピックアップおよびトリップ時間の変動が低減)
3. 入力バイアス電流が低いため、電流トランスへの負荷が軽減
4. 飽和状態での位相反転効果が生じないため、再現性が向上
5. 電磁耐性 (EMI) が向上
6. 1~5の改善点により、製造およびテストにかかる時間が短縮され、歩留まりも向上

MCCBアナログ・フロントエンド・アンプ・リファレンス・デザインは、MCCBの電子トリップ特性を簡単に評価できる評価用プラットフォームとして開発されています。このリファレンス・デザインには、以下の機能が用意されています。

- OPA4314高精度アンプに基づく、2つのゲイン段による電流入力測定
- TI MOSFETベースのセルフパワー電源
- FSD/リレー電源生成用のDC-DCコンバータ
- 絶縁型RS-485通信
- ネジ式端子による簡単な接続
- MCUインターフェイスによる迅速で容易な評価

このデザインの全体または一部を、過電流や地絡保護、その他の保護リレーなど、他のセルフパワーまたはデュアルパワー (セルフパワーまたは24V補助入力による給電) アプリケーションで使用することもできます。

デザイン・ファイルには、PDF回路図、部品表 (BOM)、PDFレイヤ・プロット、Altiumファイル、およびGerberファイルが含まれています。

2 設計仕様

2.1 低電源電圧 (3.3VDC) の高精度オペアンプ

相入力:

R、Y、およびB入力に対する2つのゲイン。ADCへの出力はジャンパで選択可能。
レール・ツー・レール動作
低い出力DCオフセット電圧 (10mV未満)、高ゲイン

中性入力:

ADC入力に直接接続された中性入力に対して1つのゲイン。

注: 評価のために必要なゲインをユーザーが設定できます。
MCCB-ETUは、CT入力用に負荷抵抗を提供します。

2.2 電源

生成される電源:	> 12VDC: FSD/リレー駆動用 約16VDC: コンパレータ電源用 3.3VDC: オペアンプ、リファレンス、および温度センサ用
セルフパワー電源のレギュレーション:	39VDC \pm 5%
補助入力の入力電源範囲:	20~35VDC

2.3 測定用リファレンス(1.65VDC、 \pm 0.25%)

エンジニアはジャンパを使用し、入力電流用のリファレンスとして0VまたはVCC/2を選択できます。VCC/2は高精度リファレンスを使用して生成され、オペアンプを使用してバッファリングされます。選択されているリファレンスは、1.65V(公差0.1%)です。想定される最大出力誤差は \pm 0.25%未満です。

2.4 温度センサ

温度センサは0°C ~ +90°Cの温度範囲に対応し、単一の+3.3V電源 (25°Cで \pm 3.0°Cの精度)で動作します。

2.5 MOSFETスイッチ

MOSFETスイッチは、FSD/リレー出力の制御を行います。また、ゾーン選択出力 (ZSO)、サーマル・メモリ、およびLED表示にも使用できます。

2.6 通信

Modbusプロトコルを実装するための絶縁型RS-485通信インターフェイスが搭載されています。フェールセーフ用抵抗および終端抵抗を実装するオプションもあります。

2.7 EMIフィルタ

内蔵のRF/EMI除去フィルタによってパフォーマンスが向上しています。

2.8 MCUインターフェイス

電流入力および温度入力は、Tiva Cシリーズの32ビットMCUに送信されます。このMCUは、多重化入力の12ビットSAR ADCを備えています。

3 ブロック図

MCCB-ETUアナログ・フロントエンド・リファレンス・デザインには、以下のブロックが含まれています。

1. オペアンプ、EMIフィルタ、リファレンス、温度センサ、電流入力
2. セルフパワー電源
3. 絶縁型RS-485インターフェイス
4. リレー/FSD制御
5. Tiva CシリーズLaunchPadインターフェイス

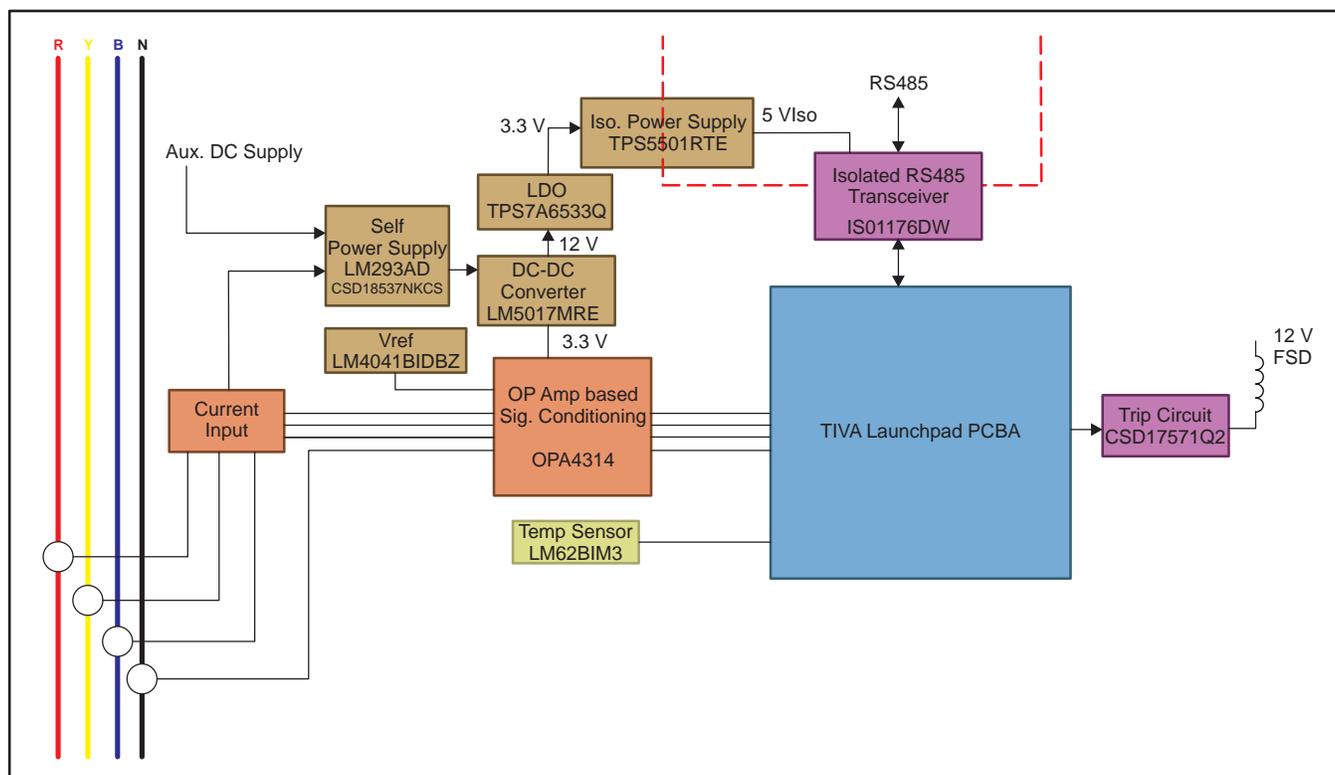


図 1. ブロック・レベル図

3.1 オペアンプ

高精度オペアンプにより、負荷抵抗に接続された電流入力を増幅します。3つの相入力オペアンプ・セクションが3相電流入力に対して2つのゲインを提供し、単一ゲインの1つのセクションが中性電流入力を提供します。広い温度範囲にわたって正確な測定を行うために、高精度の安定したリファレンスが実装されています。CT入力の接続用にはネジ式端子が用意されています。高精度の温度センサも搭載されています。

3.2 セルフパワー電源

セルフパワー電源は、入力電流から出力電圧を生成します。3相入力電流によって、電子回路が機能するために必要な電力が生成されます。オプションで、ETUを補助24VDC入力で駆動することもできます。セルフパワー出力は、FSD/リレー動作用に12Vおよび3.3Vに変換されます。MCUはDC-DCコンバータを使用して動作し、レギュレータ回路はDC-DCコンバータとレギュレータを使用して動作します。

3.3 絶縁型RS-485インターフェイス

このMCCBアナログ・フロントエンド・アンプ・デザインは、測定したデータをRS-485経由で監視システムに送信できます。

3.4 リレー/FSD制御

MOSFETベースのスイッチによって、リレー/FSD制御を行います。リレーは12V電源によって制御されます。DC-DCコンバータの出力は、プログラミング可能な抵抗によって15Vまたは18Vに調整できます。また、同じMOSFETスイッチを、ZSO、サーマル・メモリ、MCCBのLED表示など、他のアプリケーションにも使用できます。

3.5 Tiva CシリーズLaunchPadインターフェイス

このリファレンス・デザインでは、データの測定と転送にTiva Cシリーズの32ビットCPU LaunchPadを使用しています。データはUSBインターフェイスによって、PCベースのGUIに転送されます。オペアンプの出力は、TM4C123Gの12ビットADCに接続されています。

4 回路設計と部品選択

表1に、各種オペアンプの重要な特性の比較を示します。

表 1. 各種オペアンプの重要な特性の比較

Characteristics	Application's Requirement	OPA4314	LMV324	LMV824-N
Iq Total (Max) (mA)	Low	0.720	0.680	1.2 mA
Number of Channels	4	4	4	4
Rail-to-Rail	VCC	In/Out	Out	Out
Operating Temperature Range (C) (Package dependent exception exist)	-40°C to 125°C	-40°C to 125°C	-40°C to 125°C	-40°C to 125°C
Vos (Offset Voltage at 25°C) (Max) (mV)	Min offset	2.5	7	3.5
Offset Drift (Typ) (μ V/C)	Min offset drift	1	5	1
Vn at 1 kHz (Typ) (nV/rtHz)	Min noise	14	39	28
CMRR (Min) (dB)/PSRR	Max	94/92	50/50	90/85
IBias (Max) (pA)	Min	10	250000	150
Total Supply Voltage (Max) (+5 V = 5, \pm 5 V = 10)	3.3	5.5	5.5	5.5
Total Supply Voltage (Min) (+5 V = 5, \pm 5 V = 10)	2.7	1.8	2.7	2.5
Slew Rate (Typ) (V/ μ s)	> 1	1.5	1	1.4
GBW (Typ) (MHz)	>1	3	1	5
Pin/Package	14 TSSOP or SOIC	14TSSOP	14SOIC,14TSSOP	14SOIC,14TSSOP
ESD-Human model- kV	High	4	2	2
EMI filter	Integrated	Internal	No	No
Vo (Swing)	Rail-to-Rail	Vcc - 60 mV	Vcc - 400 mV	Vcc - 100 mV
Vcm (Input)	Rail-to-Rail	V(-0.2 V), V+ (+0.2 V)	V(-0.2 V), 1.9 V	V(-0.2 V), 1.9 V
Phase reversal during input overdrive	No reversal	No	TBD	TBD

表1に示す比較結果から、OPA4314は、MCCB-ETUに対して最適なコストパフォーマンスを提供することがわかります。

4.1 Op Amp with Internal EMI Filter and Reference

This reference design uses OPA4314. The quad channel OPA4314 is offered in a TSSOP-14 package. The robust design of the OPA314 devices provides unity-gain stability with capacitive loads of up to 300 pF, an integrated RF/EMI rejection filter, no phase reversal in overdrive conditions, and high electrostatic discharge (ESD) protection (4-kV HBM).

Some of the critical features are:

- Wide supply range: 1.8 V to 5.5 V
- Low noise: 14 nV/MHz at 1 kHz
- Gain bandwidth: 3 MHz
- Low input bias current: 0.2 pA
- Low offset voltage: 0.5 mV
- Unity-gain stable
- Internal RF/EMI filter
- Extended temperature range: -40°C to $+125^{\circ}\text{C}$

TI configures the op amp as a noninverting amplifier with two gains. The engineer configures the gains with gain resistors. The op amp can take AC input and rectified half wave input. The input is configured with the jumper setting shown in Figure 2 and is explained in Table 2.

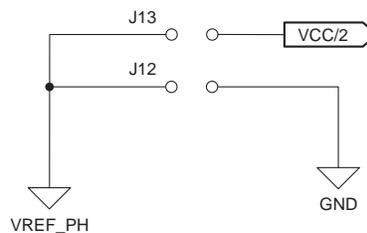


Figure 2. OPA4314 Input Jumper Configuration

Table 2. Input Jumper Configuration for OPA4314

Jumper J13 is mounted	Op amp accepts AC input
Jumper J12 is mounted	Op amp accepts rectified input

1. The neutral input is always configured for AC input.
2. Do not mount both the jumpers together.
3. During DC offset measurement ensure that the Phase inputs and neutral inputs are looped separately when the J12 is mounted.

The OPA4314 operational amplifier family incorporates an internal input low-pass filter that reduces the amplifier response to EMI. This filter provides both common-mode and differential mode filtering. The filter design has a cutoff frequency of approximately 80 MHz (-3 dB), with a roll-off of 20 dB per decade.

The reference design has LM4041-N/LM4041-N-Q1 precision micro power shunt voltage reference for providing the level shifting when the PGA is configured for AC input.

Key Specifications (LM4041-N/LM4041-N-Q1 1.2) include:

- 0.1% output voltage tolerance
- 20- μV RMS output noise
- Low temperature coefficient of < 100 PPM/ $^{\circ}\text{C}$

Using the reference design parameters from the previous list along with the op amp guarantees the trip accuracy over a wide temperature range.

A temperature sensor is provided for thermal overload trip and gain compensation functions, as required. The temperature sensor is rated for 0°C to $+90^{\circ}\text{C}$ range.

4.2 Self-Power Supply

4.2.1 Current Inputs

Figure 3 shows the current input schematics.

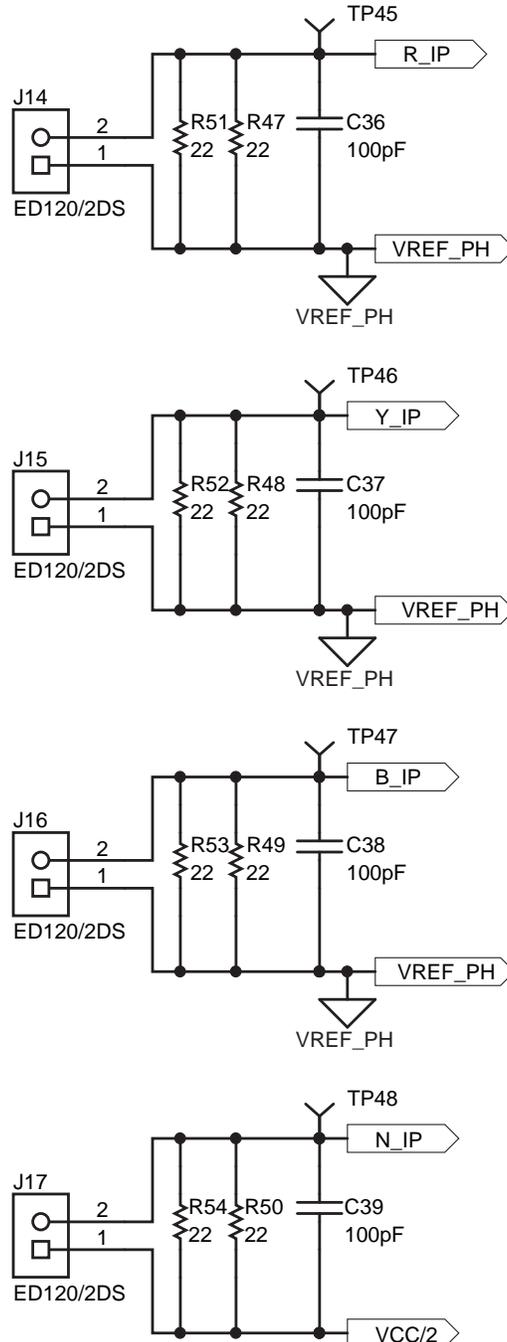


Figure 3. Current Inputs

The board provides the ability to connect up to 4 current inputs. The current input can be AC or half-wave rectified input. The design includes the ability to mount two 22R burdens. The reference design includes a screw type terminal to connect the current input. Based on the secondary current and transformer performance, the design engineer can change the burden resistor. A Rogowski coil cannot be connected directly and the output from the integrator has to be applied at the current inputs. When the integrator output is applied, burden resistors must be made as do not populate.

CAUTION

Do not leave the current terminal open and apply current during testing.

Ensure the current inputs are connected and the terminal screws are tightened before applying current for testing.

Figure 4 illustrates the self-power supply schematic.

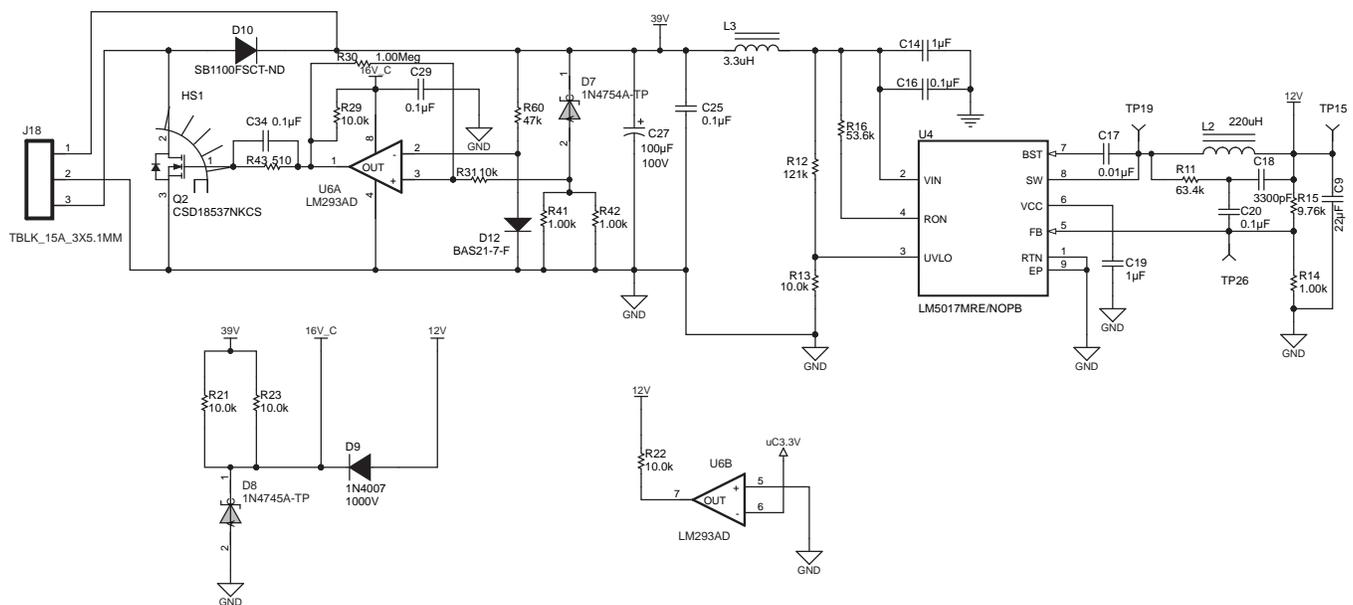


Figure 4. Self-Power Supply

The Self-Power section has provision for two inputs:

1. Half-wave rectified current inputs
2. Auxiliary DC voltage inputs

TI configures the Self-Power regulator to regulate the voltage at 39 V. The MCCB-ETU uses TI MOSFETs to shunt the current above 39 V. Increased regulation voltage reduces power dissipation and facilitates usage of lower VA current transformer. TI has a wide range of MOSFETs that can be selected for current shunting based on the application and the configured regulation voltage.

The Self-Power supply generates output voltage from the input currents. The input to the self-power generation circuit is half-wave rectified output from current transformers. The design engineer must connect the rectifier diodes externally. Optionally, power the ETU by auxiliary 24-V input. The Zener diode reference regulates the self-power to 39 V. If the output voltage exceeds 39 V, the comparator switches the MOSFET on and the MOSFET shunts the input current. When the output voltage reduces, the comparator switches the MOSFET off and the input current charges the output capacitor. The 39-V Self-Power output is converted to 12 V and 3.3 V for FSD/relay operation and electronic circuit functioning using DC-DC convertors and LDO. **The advantage of the self-power circuit is to reduce CT loading.** The critical component in the Self-Power circuit is the shunt regulation MOSFET. A wide range of MOSFETs are available and are listed in [Table 3](#).

Table 3. TI MOSFETs with Current Shunting

Product Description	Product Link
60-V, N-Channel NexFET™ Power MOSFET	CSD18537NKCS
60-V, N-Channel NexFET Power MOSFET	CSD18534KCS
80-V, N-Channel NexFET Power MOSFET	CSD19506KCS
80-V, 7.6-mΩ, N-Channel TO-220 NexFET Power MOSFET	CSD19503KCS
100-V, N-Channel NexFET Power MOSFET	CSD19535KCS
100-V, 6.4-mΩ, TO-220 NexFET Power MOSFET	CSD19531KCS

The graph in [Figure 5](#) indicates the power loss in a typical Self-Power supply.

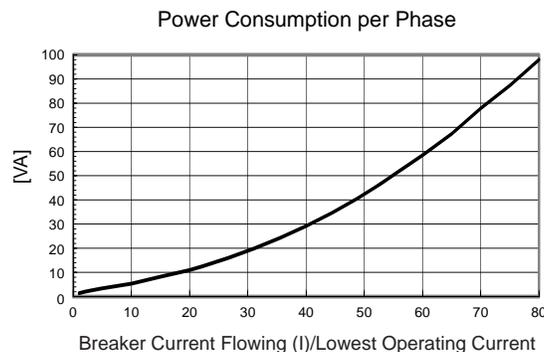


Figure 5. Typical Power Consumption for Current/Lowest Operating Current

CAUTION

Do not leave the current terminal open and apply current for testing.

Ensure the current inputs are connected and the terminal screws are tightened before applying current for testing.

By using LM5017, the clamping voltage can be increased as the device input is rated up to 100 V. The MCCB-ETU analog front end reference design details shunt clamping, with LM5017 configured in nonisolated output configuration.

4.3 Isolated RS-485 Communication Interface

The reference design provides an EMC-compliant isolated 1-Mbps, 3.3 V to 5 V RS-485 interface using an ISO1176 transceiver and the TPS55010. This board provides signal and power isolation with reduced board space and power consumption. The TPS55010 has a higher efficiency and better regulation accuracy since its Fly-Buck™ topology uses primary side feedback that provides excellent regulation over line and load. The TPS55010 provides 3.3 V to 5 V and isolation levels using off-the-shelf Fly-Buck transformers. The transformer chosen here for the design has a 475-μH primary inductance and a dielectric strength of 2500 VAC. The ISO1176 transceiver is an ideal device for long transmission lines since the ground loop is broken to provide for operation with a much larger common mode voltage range. The symmetrical isolation barrier provides 2500 VRMS of isolation between the line transceiver and the logic level interface. The RS-485 bus is available on screw type terminals and connectors.

The RS-485 bus provides an external failsafe biasing that uses external resistor biasing to ensure failsafe operation during an idle bus. If none of the drivers connected to the bus are active, the differential voltage (VAB) approaches zero or in between ±250 mV, allowing the receivers to assume random output states. To force the receiver outputs into a defined state, the design introduces failsafe biasing resistors with terminating resistors of 120 Ω. The RS-485 bus is also protected against EFT, ESD, and surges with the help of transient voltage suppressor diodes (SMCJ15CA, 1500-W series).

4.4 FSD/Relay Control

TI has a wide range of MOSFETs that can be used for driving Relay, FSD, ZS0, or LEDs. TI provides a wide range of MOSFETs with a tiny SON2x2 package. [CSD17571Q2](#) is installed in the reference design.

Table 4. TI MOSFETs for Driving Relay, FSD, ZS0, or LEDs

Product Description	Product Link
30-V, N-Channel NexFET Power MOSFETs	CSD17571Q2
N-Channel Power MOSFET, CSD13202Q2, 12-V VDS, 9.3 mΩ, R _{DS(on)} 4.5 (max)	CSD13202Q2
20-V, N-Channel NexFET Power MOSFET	CSD15571Q2
Automotive 30-V, N-Channel NexFET Power MOSFET	CSD17313Q2Q1
30-V, N-Channel NexFET Power MOSFET	CSD17313Q2
N-Channel, NexFET Power MOSFET	CSD16301Q2

4.5 Tiva C Series LaunchPad Interface

The Tiva™ C Series LaunchPad ([EK-TM4C123GXL](#)) is a low-cost evaluation platform for ARM® Cortex™ M4F-based microcontrollers. The Tiva C Series LaunchPad design highlights the [TM4C123GH6PMI](#) microcontroller USB 2.0 device interface, hibernation module, and motion control pulse-width modulator (MC PWM) module. The Tiva C Series LaunchPad also features programmable user buttons and an RGB LED for custom applications. The stackable headers of the Tiva C Series LaunchPad BoosterPack XL interface demonstrate how easy it is to expand the functionality of the Tiva C Series LaunchPad when interfacing to other peripherals on many existing BoosterPack add-on boards as well as future products. [Figure 6](#) shows a photo of the Tiva C Series LaunchPad.

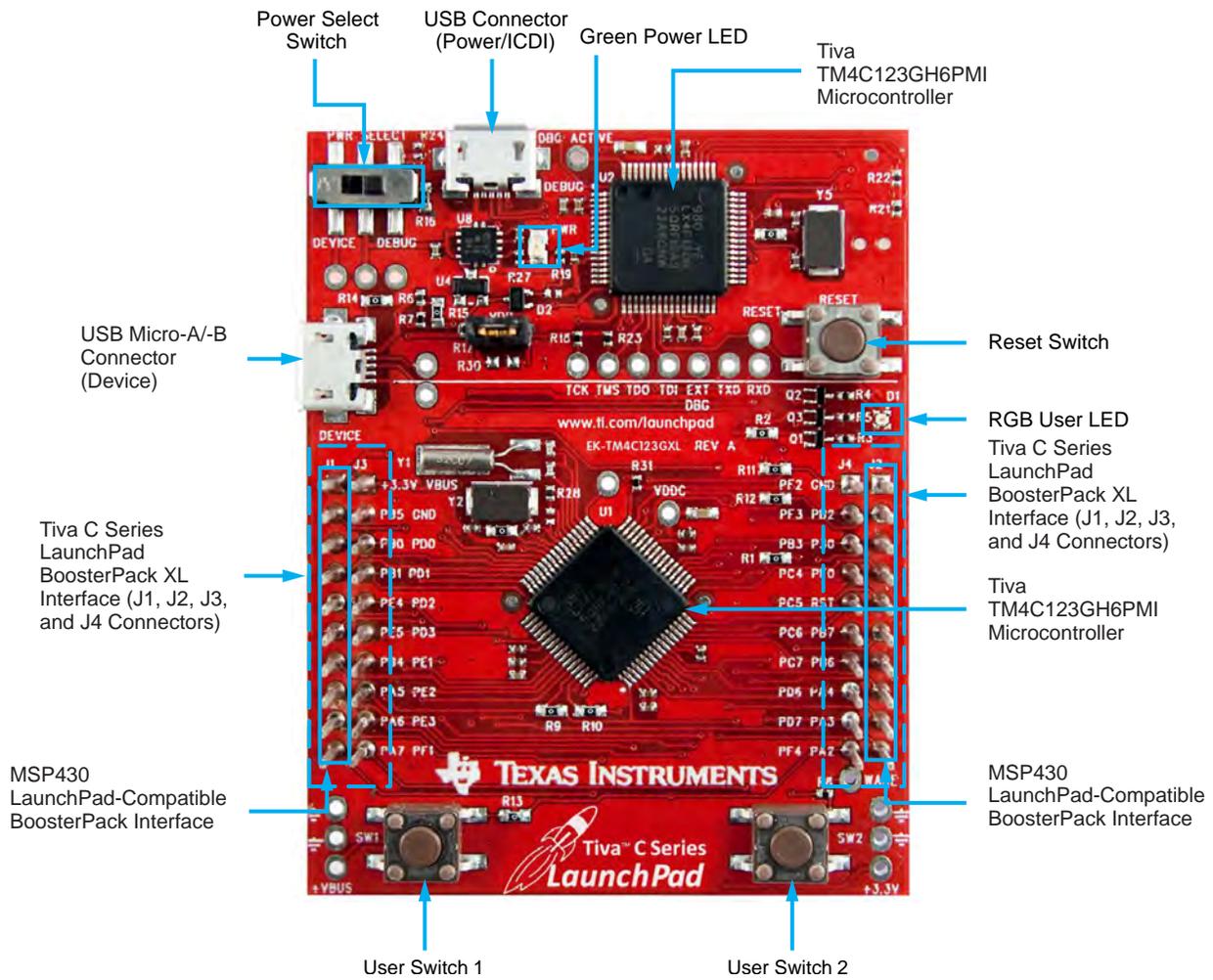


Figure 6. Tiva C Series LaunchPad

For details, refer to [EK-TM4C123GXL](#).

Care must be taken while aligning the Tiva C Series LaunchPad with the reference design board.

Table 5. Mapping Tiva C Series LaunchPad and Reference Design Connectors

Tiva C Series LaunchPad connector	Reference design connector
J1,J3	J1
J4,J2	J4

5 Test Results

This section contains descriptions of Self-Power supply rail, offset variation over temperature, accuracy testing results, and a summary of the test results.

5.1 Self-Power Supply Rail

Table 6 includes the self-power supply rail measured results.

Table 6. Self-Power Supply Rail Measured Results

Rails	Measured
39 V	39.8 V
16 V	16.12 V
12 V	12.2 V
3.3 V	3.301 V
Vref (VCC/2)	1.6554 V

5.2 Offset Variation Over Temperature

The offset voltage of an op amp increases with an increase in temperature. The offset voltage is measured by keeping the PCB in an oven and the temperature is varied, over time. The results are shown in Table 7.

Table 7. Offset Variation Over Temperature Op-Amp DC Offset Drift⁽¹⁾⁽²⁾

Amplifier	Offset Drift at -10°C (μV)	Expected Op-Amp Drift -μV (Without Resistor Drift)	Offset Drift at +55 °C (μV)	Expected Op-Amp Drift -μV (Without Resistor Drift)
OPA4314-1	300	270	-300	231
OPA4314-1	200	270	-100	231
LMV324-1	1600	1350	-1200	1155
LMV324-1	1500	1350	-1600	1155

⁽¹⁾ Reference to 25°C with 7.7 Gain

⁽²⁾ The measured value is the total drift of the amplifier including op amp and the gain resistors.

5.3 Accuracy Testing

This section contains test results including the test setup, measurement for high and low gain, and a summary of the test results.

5.3.1 Test Setup

Figure 7 illustrates the TIDA-00128 test setup.

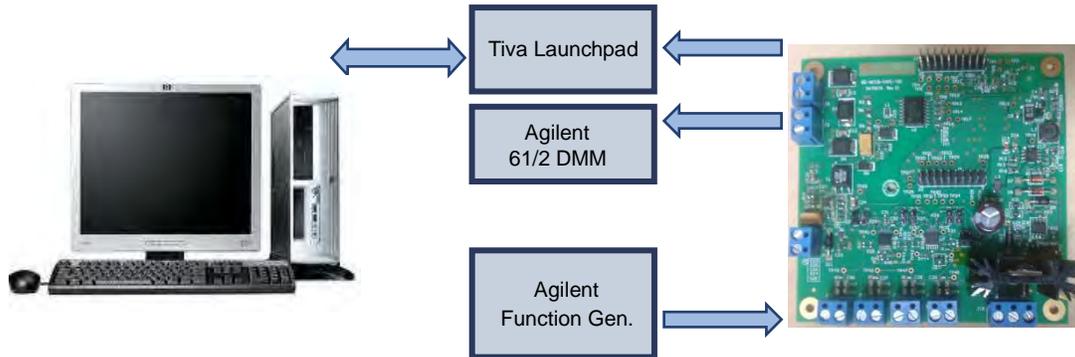


Figure 7. TIDA-00128 Test Setup

These test results are documented using the following parameters:

- The tests were performed with two different gains:
 - High Gain — for low level signals, gain is set at 7.7.
 - Low Gain — gain is reduced for higher current inputs so the op-amp output does not saturate, gain is set to 2.
- Input Signal Frequency: 50 Hz.

NOTE: All the voltages mentioned in Figure 8 through Figure 12 are Root Mean Square Values (RMS).

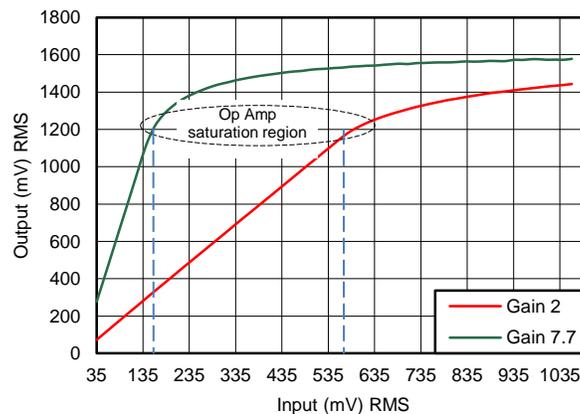


Figure 8. Saturation Level of Op-Amp Outputs for Gain 2 and Gain 7.7

5.3.2 Measurement for High Gain

The graphs in Figure 9 through Figure 10 show the results for the OPA4314 op amp designated as Op Amp1 and Op Amp2.

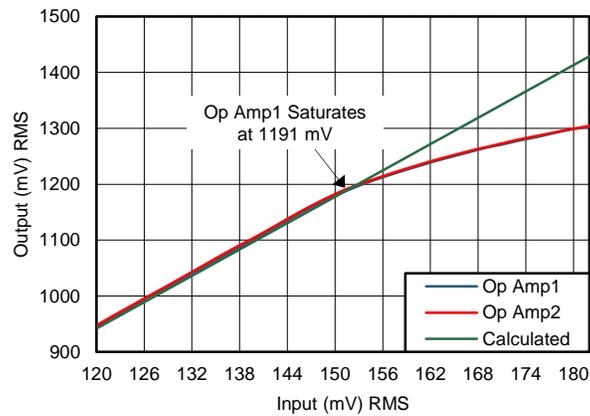


Figure 9. Saturation Level of Op-Amp Outputs (RMS)

Total error (RMS) due to ADC and op amp together is as plotted in Figure 10.

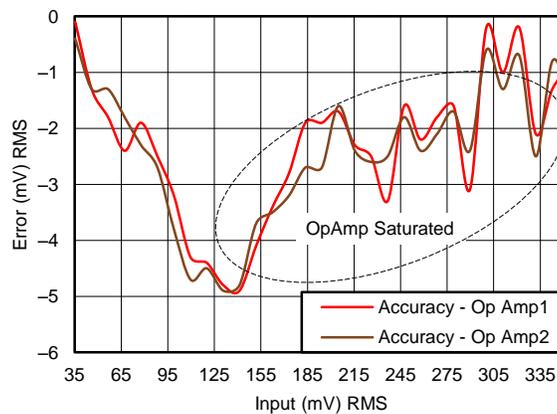


Figure 10. Total Error due to 12-bit Internal ADC and Op Amp

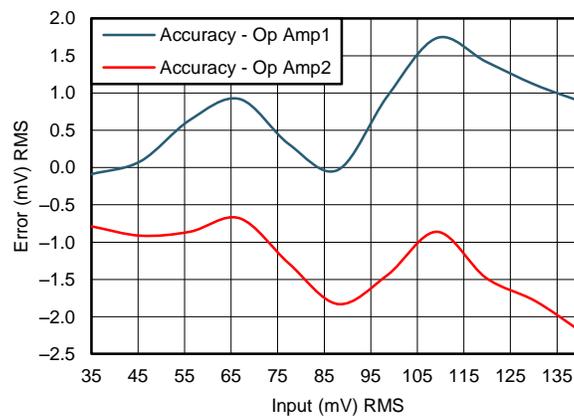


Figure 11. Error in mV RMS-Measured versus Theoretical Value

5.3.3 Measurement for Low Gain

Figure 12 through Figure 14 show the results for the op amps within OPA4314 designated as Op Amp1 and Op Amp2. These results are all obtained at a low gain: 2.

Graph over entire range (RMS) with respect to input as compared to the calculated (ideal) curve.

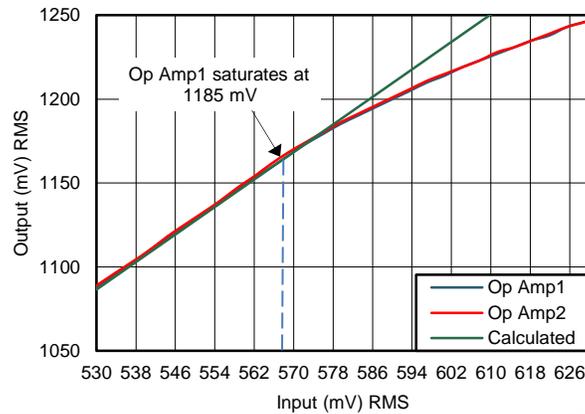


Figure 12. Saturation Level of Op Amp Output (RMS)

Total error (RMS) due to ADC and op amp together is as plotted in Figure 13.

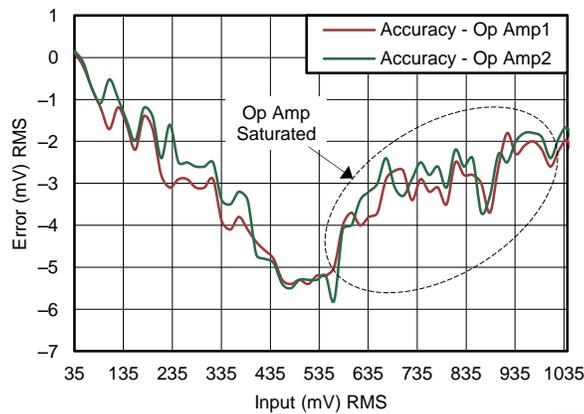


Figure 13. Total Error due to 12-bit Internal ADC and Op Amp

Figure 14 illustrates the accuracy (error in mV RMS) measured versus calculated value: for the input range before op amp saturates:

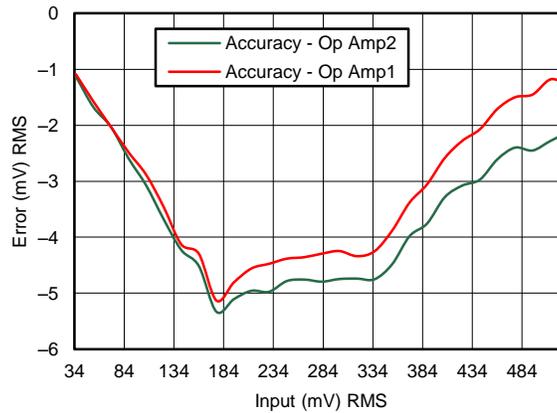


Figure 14. Error in mV RMS-Measured versus Theoretical Value

5.4 Results Summary

Table 8 presents a summary of accuracy and saturation level for the two op amps for different gain.

Table 8. Accuracy and Saturation Measurement Results Summary

	Accuracy (Error Before Op-Amp Saturation)		Saturation level	
	Gain 2	Gain 7.7	Gain 2	Gain7.7
Op Amp1	~5 mV RMS	~ +1.8 mV RMS	1184 mV RMS	1191 mV RMS
Op Amp2	~5 mV RMS	~ -2.0 mV RMS	1185 mV RMS	1194 mV RMS

6 Schematics

Figure 15 through Figure 21 represent the schematics for the high precision analog front end amplifier and peripherals for MCCB.

Page 2	BLOCK DIAGRAM
Page 3	SELF POWER + REGULATOR +FSD +LDO
Page 4	ANALOG FRONT END OPAMP +TEMP SENSOR
Page 5	ISOLATED RS485 INTERFACE
Page 6	LAUNCH PAD INTERFACE
Page 7	HARDWARE - MISCELLANEOUS

Revision History	
Revision	Notes

Figure 15. Schematics (1 of 7)

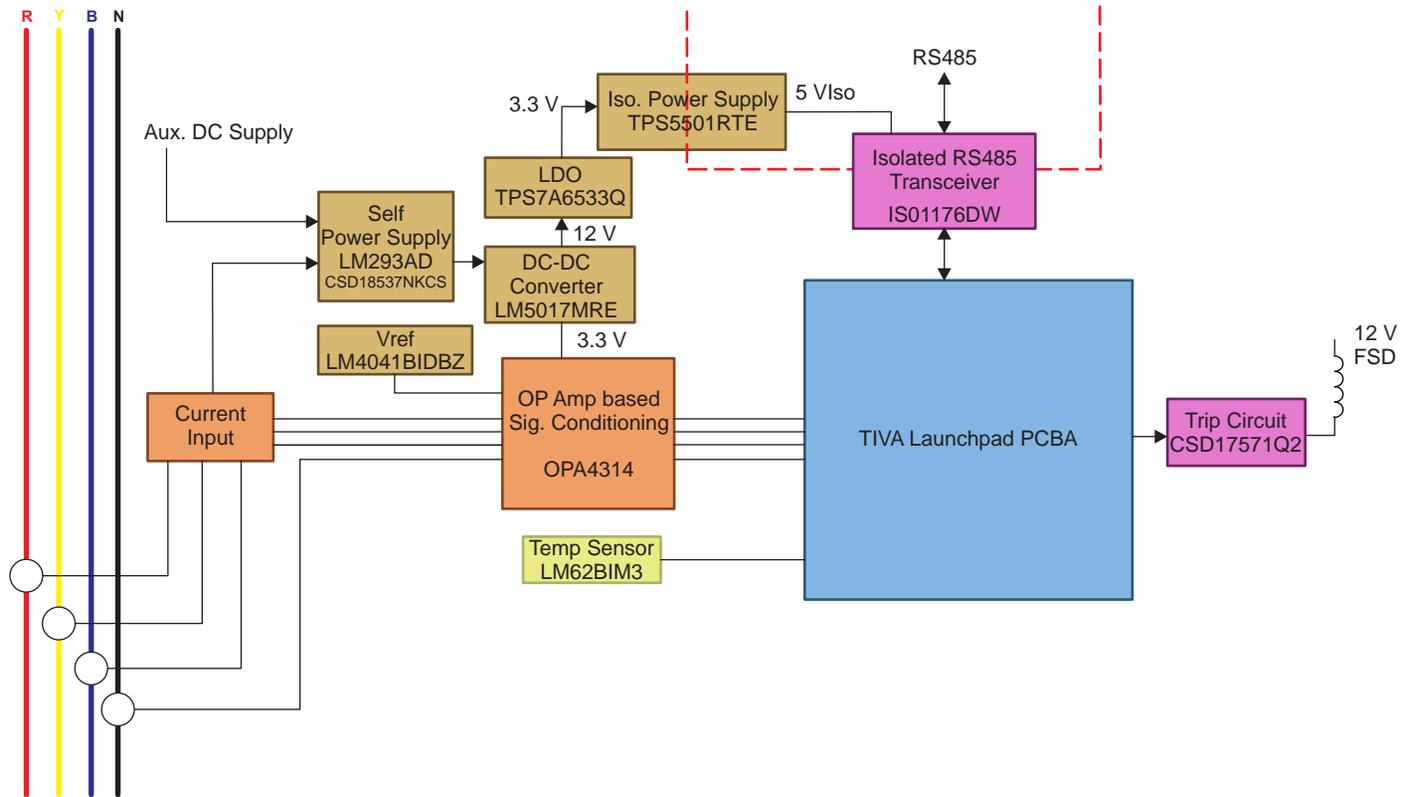


Figure 16. Schematics (2 of 7)

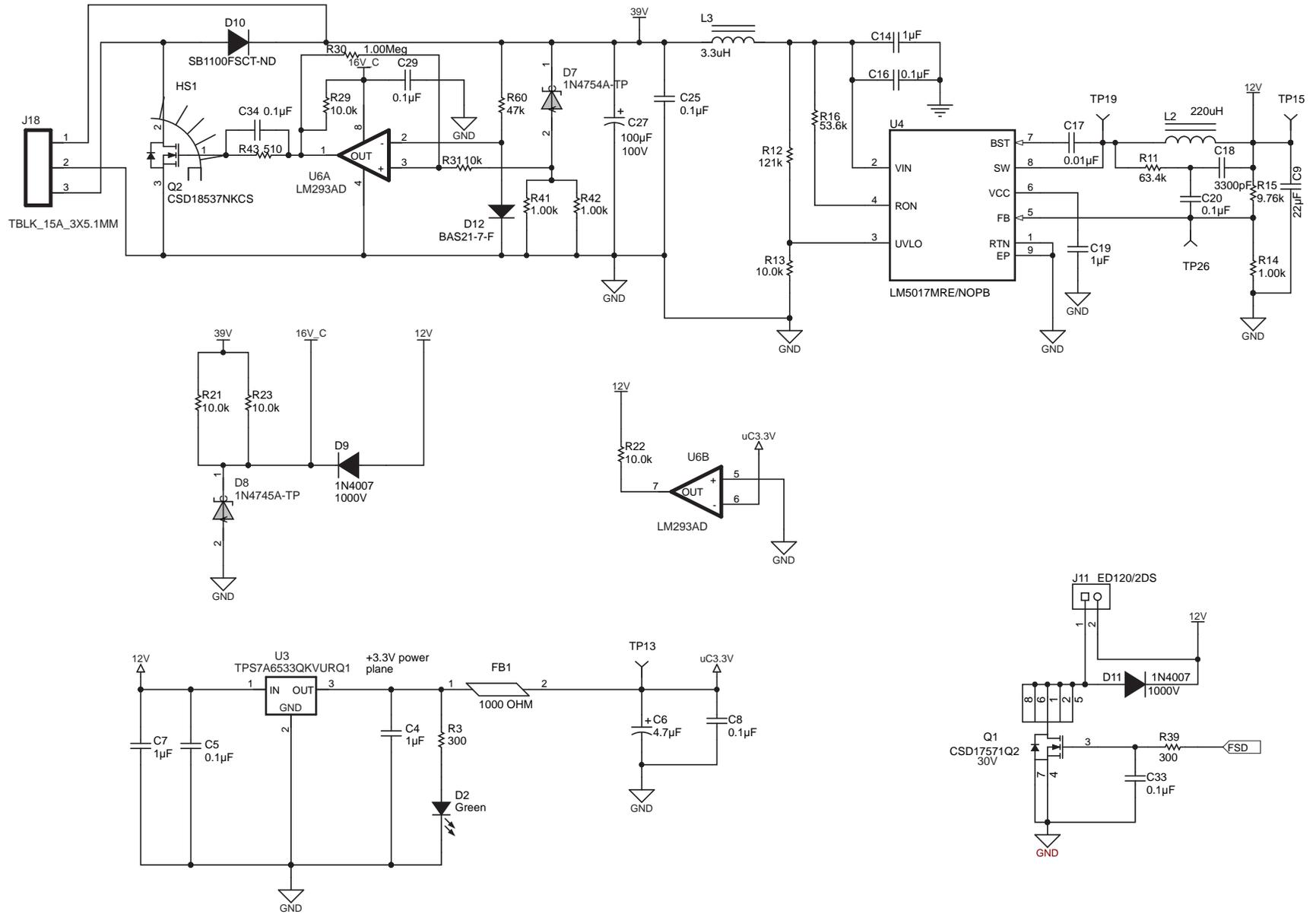


Figure 17. Schematics (3 of 7)

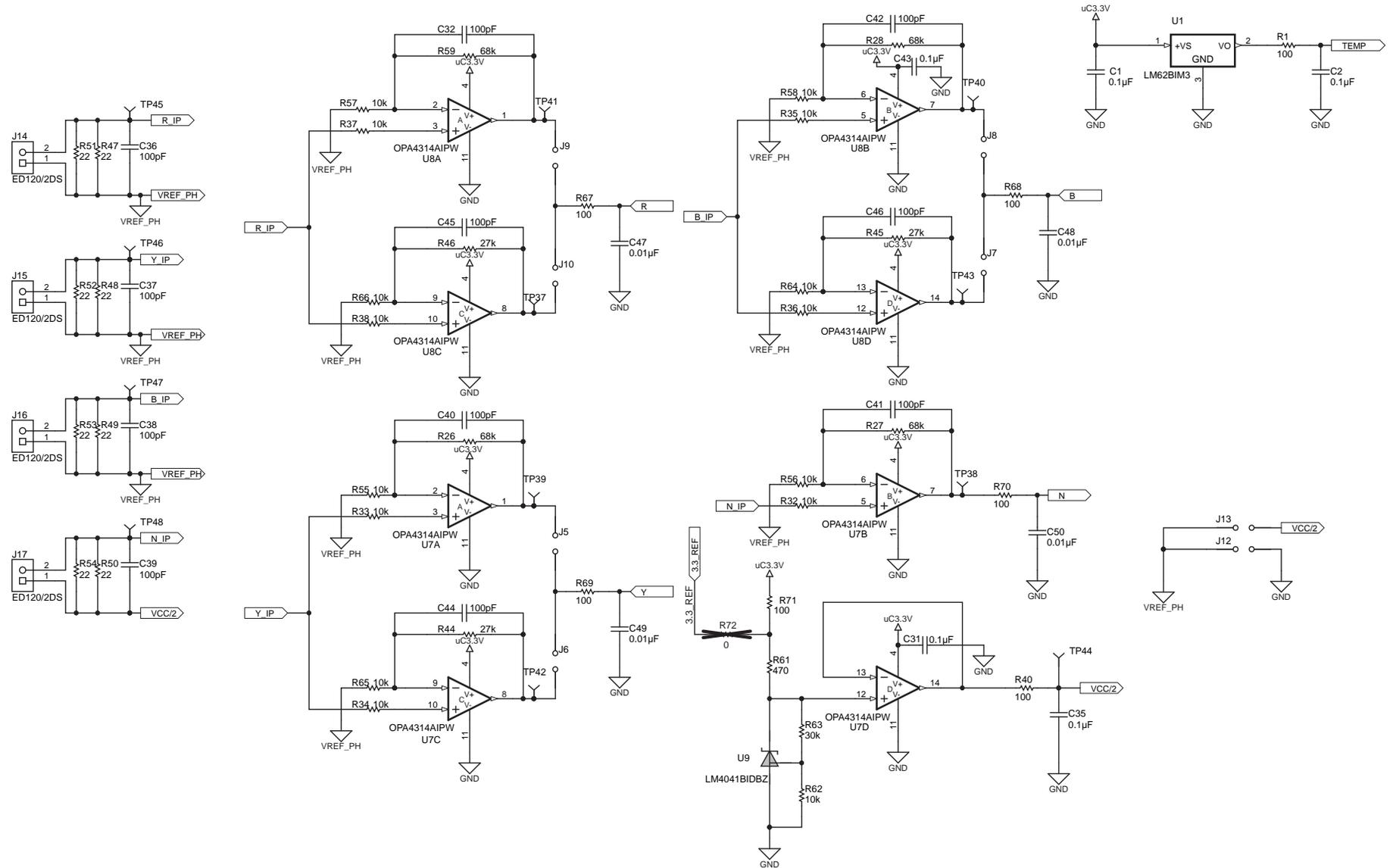


Figure 18. Schematics (4 of 7)

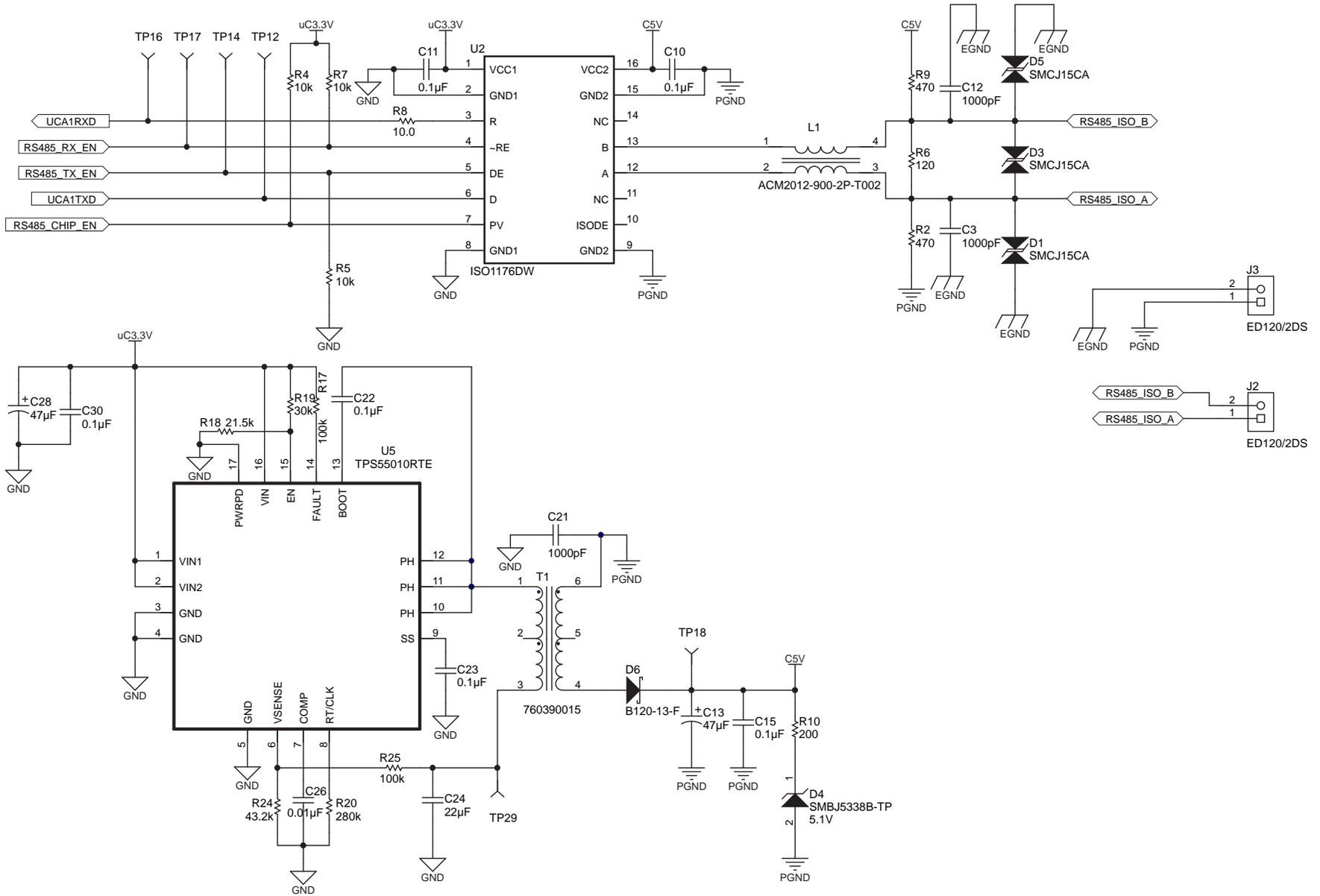


Figure 19. Schematics (5 of 7)

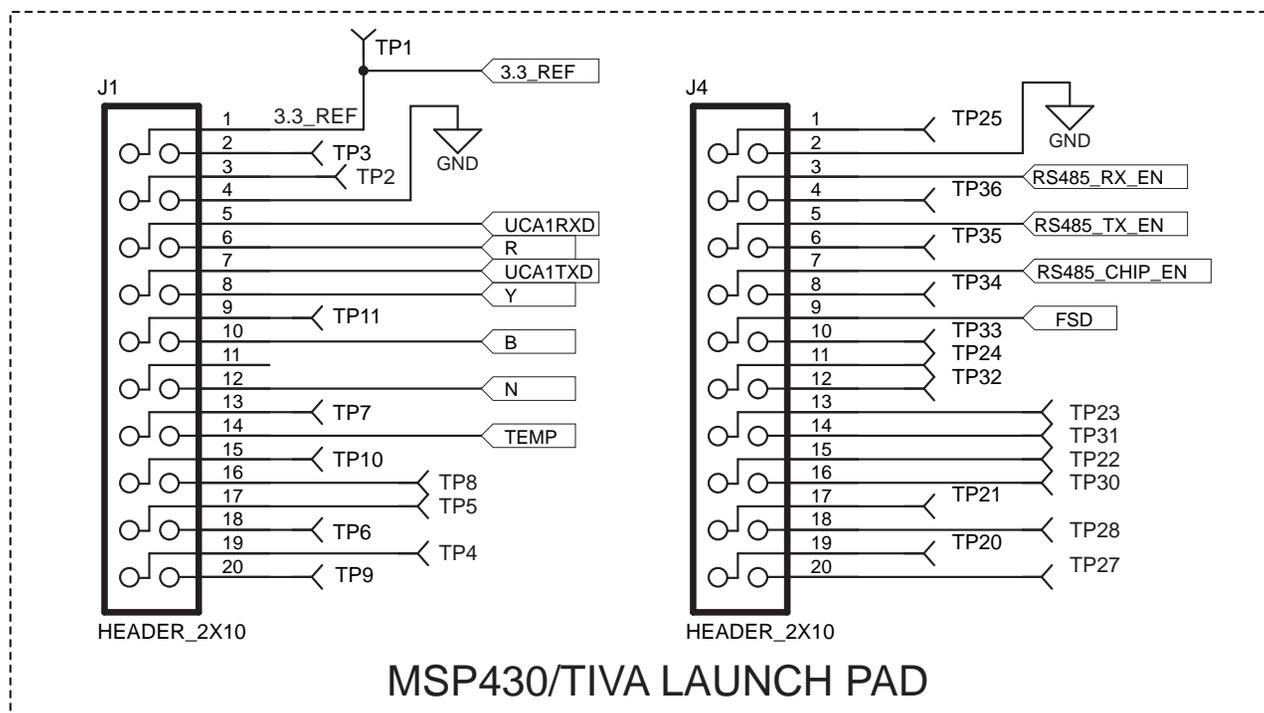


Figure 20. Schematics (6 of 7)

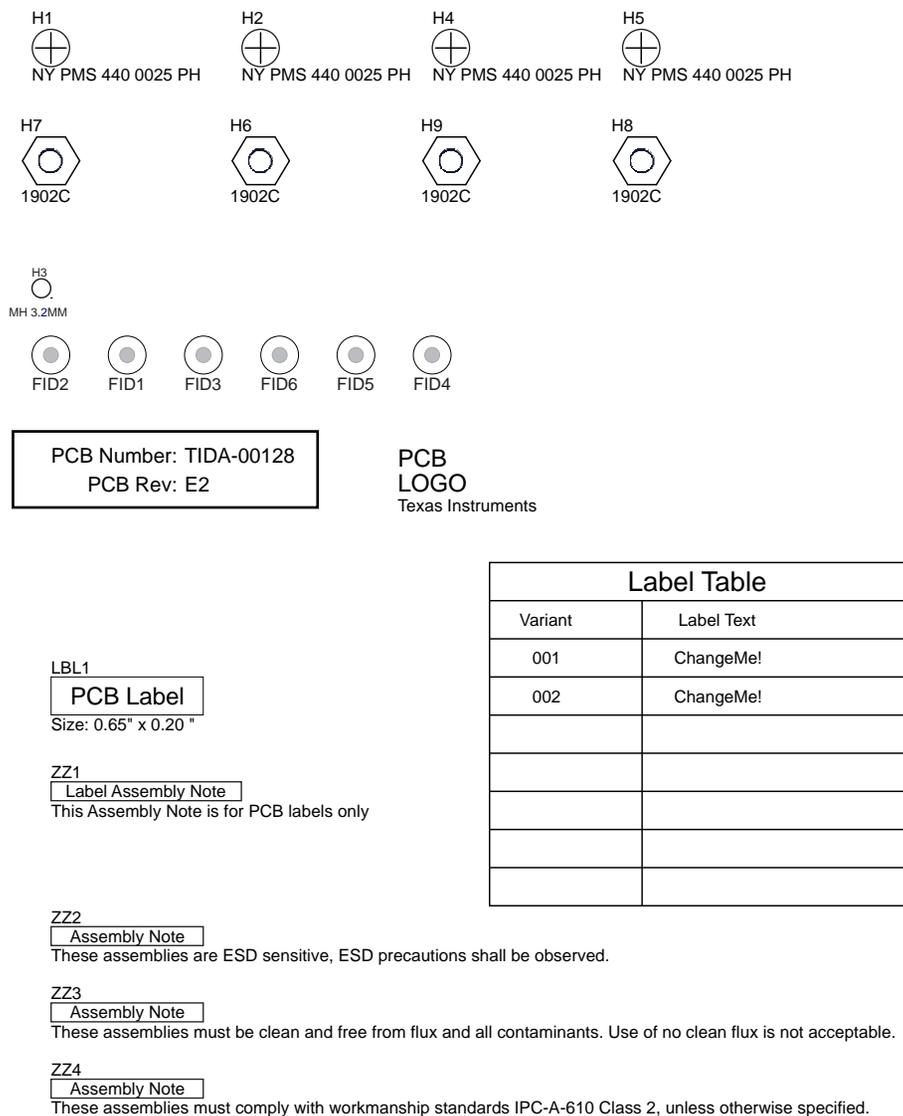


Figure 21. Schematics (7 of 7)

7 Bill of Materials

The BOM for the high precision analog front end amplifier and peripherals for MCCB is listed in [Table 9](#).

Table 9. Bill of Materials

Fitted	Description	Designator	Manufacturer	Part Number	Quantity	RoHS	Package Reference
Fitted	Printed Circuit Board	!PCB1	Any	TIDA-00128	1	O	
Fitted	CAP, CERM, 0.1 μ F, 25 V, \pm 5%, X7R, 0603	C1, C2, C10, C11, C15, C20, C22, C23, C30, C31, C33, C34, C35, C43	AVX	0603C104JAT2A	14	Y	0603
Fitted	CAP, CERM, 1000 pF, 1000 V, \pm 10%, X7R, 1206	C3, C12, C21	Yageo America	CC1206KKX7RCBB102	3	Y	1206
Fitted	CAP, CERM, 1 μ F, 16 V, \pm 10%, X7R, 0603	C4, C7	TDK	C1608X7R1C105K	2	Y	0603
Fitted	CAP, CERM, 0.1 μ F, 50 V, \pm 10%, X7R, 0603	C5, C8, C29	Kemet	C0603C104K5RACTU	3	Y	0603
Fitted	CAP, TA, 4.7 μ F, 35 V, \pm 10%, 1.9 Ω , SMD	C6	Vishay-Sprague	293D475X9035C2TE3	1	Y	6032-28
Fitted	CAP, CERM, 22 μ F, 16 V, \pm 10%, X5R, 1206	C9	MuRata	GRM31CR61C226KE15L	1	Y	1206
Fitted	CAP, TA, 47 μ F, 35 V, \pm 10%, 0.3 Ω , SMD	C13, C28	Kemet	T495X476K035ATE300	2	Y	7343-43
Fitted	CAP, CERM, 1 μ F, 100 V, \pm 10%, X7R, 1206	C14	MuRata	GRM31CR72A105KA01L	1	Y	1206
Fitted	CAP, CERM, 0.1 μ F, 100 V, \pm 10%, X7R, 0805	C16, C25	Kemet	C0805C104K1RACTU	2	Y	0805
Fitted	CAP, CERM, 0.01 μ F, 25 V, \pm 5%, C0G/NP0, 0603	C17, C26, C47, C48, C49, C50	TDK	C1608C0G1E103J	6	Y	0603
Fitted	CAP, CERM, 3300 pF, 50 V, \pm 10%, X7R, 0603	C18	Kemet	C0603C332K5RACTU	1	Y	0603
Fitted	CAP, CERM, 1 μ F, 25 V, \pm 10%, X5R, 0603	C19	TDK	C1608X5R1E105K080AC	1	Y	0603
Fitted	CAP, CERM, 22 μ F, 16 V, \pm 20%, X5R, 1206	C24	AVX	1206YD226MAT2A	1	Y	1206
Fitted	CAP, AL, 100 μ F, 100 V, \pm 20%, 0.12 Ω , TH	C27	Rubycon	100YXJ100M10X20	1	Y	10 mm x 20 mm
Fitted	CAP, CERM, 100 pF, 25 V, \pm 10%, X7R, 0603	C32, C36, C37, C38, C39, C40, C41, C42, C44, C45, C46	AVX	0603C101KAT2A	11	Y	0603
Fitted	Diode, TVS 15 V 1500 W BIDIR 5% SMC	D1, D3, D5	Littelfuse Inc	SMCJ15CA	3	Y	SMC
Fitted	LED SmartLED Green 570NM	D2	OSRAM	LG L29K-G2J1-24-Z	1		0603
Fitted	Diode, Zener, 5.1 V, 5 W, SMB	D4	Micro Commercial Components	SMBJ5338B-TP	1	Y	SMB
Fitted	Diode, Schottky, 20 V, 1A, SMA	D6	Diodes Inc.	B120-13-F	1	Y	SMA
Fitted	Diode, Zener, 39 V, 1 W, DO41	D7	Micro Commercial Co	1N4754A-TP	1		DO-41
Fitted	Diode, Zener, 16 V, 1 W, DO41	D8	Micro Commercial Co	1N4745A-TP	1		DO-41
Fitted	Diode, P-N, 1000 V, 1A, TH	D9, D11	Fairchild Semiconductor	1N4007	2	Y	DO-41
Fitted	Diode, P-N, 1100 V, 1A, TH	D10	Fairchild Semiconductor	SB1100FSCT-ND	1	Y	DO-41
Fitted	Diode, Switching, 200 V, 0.2A, SOT-23	D12	Diodes Inc.	BAS21-7-F	1	Y	SOT-23
Fitted	FERRITE CHIP 1000 OHM 300MA 0603	FB1	TDK Corporation	MMZ1608B102C	1	Y	0603
Fitted	Fiducial mark. There is nothing to buy or mount.	FID1, FID2, FID3, FID4, FID5, FID6	N/A	N/A	6		Fiducial
Fitted	Machine Screw, Round, #4-40 x 1/4, Nylon, Philips panhead	H1, H2, H4, H5	B&F Fastener Supply	NY PMS 440 0025 PH	4	Y	Screw
Fitted	Mountin hole, NPTH Drill 3.2 mm	H3			1		
Fitted	Standoff, Hex, 0.5"L #4-40 Nylon	H6, H7, H8, H9	Keystone	1902C	4	Y	Standoff
Fitted	HEATSINK TO-220 W/PINS 1.5"TALL	HS1	Aavid Thermalloy	513102B02500G	1		1.500 x 1.375in.
Fitted	Header, Male 2 x 10-pin, 100mil spacing	J1, J4	Sullins	PEC10DAAN	2		0.100 inch x 10 x 2

Table 9. Bill of Materials (continued)

Fitted	Description	Designator	Manufacturer	Part Number	Quantity	RoHS	Package Reference
Fitted	TERMINAL BLOCK 5.08MM VERT 2POS, TH	J2, J3, J11, J14, J15, J16, J17	On-Shore Technology	ED120/2DS	7	Y	TERM_BLK, 2pos, 5.08 mm
Fitted	Header, Male 2-pin, 100mil spacing,	J5, J6, J7, J8, J9, J10, J12, J13	Sullins	PEC02SAAN	8		0.100 inch x 2
Fitted	Terminal Block, 3-pin, 15-A, 5.1 mm	J18	OST	ED120/3DS	1		0.60 x 0.35 inch
Fitted	Inductor, Common Mode Filter SMD	L1	TDK	ACM2012-900-2P-T002	1		2.00 mm x 1.20 mm
Fitted	Inductor, 220 μ H .30A SMD	L2	Bourns	SRR7032-221M	1	Y	7x7 mm
Fitted	Inductor, Chip, 3.3 μ H 770MA 1210 10%	L3	EPCOS Inc	B82422H1332K	1		1210
Fitted	Thermal Transfer Printable Labels, 0.650" W x 0.200" H - 10,000 per roll	LBL1	Brady	THT-14-423-10	1	Y	PCB Label 0.650"H x 0.200"W
Fitted	MOSFET, N-CH, 30 V, 22 A, SON 2x2 MM	Q1	Texas Instruments	CSD17571Q2	1	Y	DQK
Fitted	MOSFET, N-CH, 60 V, 50 A, TO-220AB	Q2	Texas Instruments	CSD18537NKCS	1	Y	TO-220AB
Fitted	RES, 100 Ω , 1%, 0.1 W, 0603	R1, R40, R67, R68, R69, R70, R71	Vishay-Dale	CRCW0603100RFKEA	7	Y	0603
Fitted	RES, 470 Ω , 1%, 0.125 W, 0805	R2, R9	Vishay-Dale	CRCW0805470RFKEA	2	Y	0805
Fitted	RES, 300 Ω , 5%, 0.1 W, 0603	R3, R39	Vishay-Dale	CRCW0603300RJNEA	2	Y	0603
Fitted	RES, 10 k Ω , 5%, 0.1 W, 0603	R4, R5, R7	Vishay-Dale	CRCW060310K0JNEA	3	Y	0603
Fitted	RES, 120 Ω , 5%, 0.125 W, 0805	R6	Vishay-Dale	CRCW0805120RJNEA	1	Y	0805
Fitted	RES, 10.0 Ω , 1%, 0.1 W, 0603	R8	Vishay-Dale	CRCW060310R0FKEA	1	Y	0603
Fitted	RES, 200 Ω , 1%, 0.1 W, 0603	R10	Vishay-Dale	CRCW0603200RFKEA	1	Y	0603
Fitted	RES, 63.4 k Ω , 1%, 0.1 W, 0603	R11	Vishay-Dale	CRCW060363K4FKEA	1	Y	0603
Fitted	RES, 121 k Ω , 0.1%, 0.125 W, 0805	R12	Yageo America	RT0805BRD07121KL	1	Y	0805
Fitted	RES, 10.0 k Ω , 1%, 0.1 W, 0603	R13, R22	Vishay-Dale	CRCW060310K0FKEA	2	Y	0603
Fitted	RES, 1.00 k Ω , 1%, 0.1 W, 0603	R14	Yageo America	RC0603FR-071KL	1	Y	0603
Fitted	RES, 9.76 k Ω , 1%, 0.1 W, 0603	R15	Vishay-Dale	CRCW06039K76FKEA	1	Y	0603
Fitted	RES, 53.6 k Ω , 0.1%, 0.125 W, 0805	R16	Susumu Co Ltd	RG2012P-5362-B-T5	1	Y	0805
Fitted	RES, 100 k Ω , 1%, 0.1 W, 0603	R17, R25	Vishay-Dale	CRCW0603100KFKEA	2	Y	0603
Fitted	RES, 21.5 k Ω , 1%, 0.1 W, 0603	R18	Vishay-Dale	CRCW060321K5FKEA	1	Y	0603
Fitted	RES, 30 k Ω , 5%, 0.1 W, 0603	R19, R63	Vishay-Dale	CRCW060330K0JNEA	2	Y	0603
Fitted	RES, 280 k Ω , 1%, 0.1 W, 0603	R20	Vishay-Dale	CRCW0603280KFKEA	1	Y	0603
Fitted	RES, 10.0 k Ω , 1%, 0.25 W, 1206	R21, R23, R29	Vishay-Dale	CRCW120610K0FKEA	3	Y	1206
Fitted	RES, 43.2 k Ω , 1%, 0.1 W, 0603	R24	Vishay-Dale	CRCW060343K2FKEA	1	Y	0603
Fitted	RES, 68 k Ω , 5%, 0.1 W, 0603	R26, R27, R28, R59	Vishay-Dale	CRCW060368K0JNEA	4	Y	0603
Fitted	RES, 1.00 M Ω , 1%, 0.1 W, 0603	R30	Vishay-Dale	CRCW06031M00FKEA	1	Y	0603
Fitted	RES, 10 k Ω , 0.01%, 0.063 W, 0603	R31, R32, R33, R34, R35, R36, R37, R38, R55, R56, R57, R58, R62, R64, R65, R66	Stackpole Electronics Inc	RNCF0603TKY10K0	16	Y	0603
Fitted	RES, 1.00 k Ω , 1%, 0.25 W, 1206	R41, R42	Vishay-Dale	CRCW12061K00FKEA	2	Y	1206
Fitted	RES, 510 Ω , 0.1%, 0.1 W, 0603	R43	Susumu Co Ltd	RG1608P-511-B-T5	1	Y	0603
Fitted	RES, 27 k Ω , 5%, 0.1 W, 0603	R44, R45, R46	Yageo America	RC0603JR-0727KL	3	Y	0603
Fitted	RES, 22 Ω , 5%, 0.25 W, 1206	R47, R48, R49, R50, R51, R52, R53, R54	Vishay-Dale	CRCW120622R0JNEA	8	Y	1206
Fitted	RES, 47 k Ω , 5%, 0.125 W, 0805	R60	Panasonic	ERJ-6GEYJ473V	1	Y	0805
Fitted	RES, 470 Ω , 5%, 0.1 W, 0603	R61	Vishay-Dale	CRCW0603470RJNEA	1	Y	0603

Table 9. Bill of Materials (continued)

Fitted	Description	Designator	Manufacturer	Part Number	Quantity	RoHS	Package Reference
Fitted	Transformer 475 μ H SMD	T1	Würth Electronics Midcom	760390015	1	Y	10.05 mm L x 6.73 mm W
Fitted	Test Point, 0.040 Hole	TP1, TP2, TP3, TP4, TP5, TP6, TP7, TP8, TP9, TP10, TP11, TP12, TP13, TP14, TP15, TP16, TP17, TP18, TP19, TP20, TP21, TP22, TP23, TP24, TP25, TP26, TP27, TP28, TP29, TP30, TP31, TP32, TP33, TP34, TP35, TP36, TP37, TP38, TP39, TP40, TP41, TP42, TP43, TP44, TP45, TP46, TP47, TP48	STD	STD	48		
Fitted	2.7 V, 15.6 mV/ $^{\circ}$ C, Temperature Sensor, 3-pin SOT-23	U1	National Semiconductor	LM62BIM3	1	N	MF03A
Fitted	IC, ISOLATED RS-485 PROFIBUS TRANSCEIVER	U2	TI	ISO1176DW	1		SO-16
Fitted	IC, 300-mA 40-V LOW-DROPOUT REGULATOR WITH 25- μ A QUIESCENT CURRENT	U3	TI	TPS7A6533QKVURQ1	1		PFM
Fitted	100 V, 600mA Constant On-Time Synchronous Buck Regulator, DDA0008B	U4	Texas Instruments	LM5017MRE/NOPB	1	Y	DDA0008B
Fitted	IC, DC-DC Converter	U5	TI	TPS55010RTE	1		QFN-16
Fitted	IC, Dual Differential Comparators, 2-36 Vin	U6	TI	LM293AD	1		SO-8
Fitted	LOW-VOLTAGE RAIL-TO-RAIL OUTPUT OPERATIONAL AMPLIFIERS, PW0014A	U7, U8	Texas Instruments	OPA4314AIPW	2	Y	PW0014A
Fitted	IC, Micropower Shunt Voltage Reference 100 ppm/ $^{\circ}$ C, 45 μ A–12 mA, Adjustable	U9	TI	LM4041BIDBZ	1		SOT23
Not Fitted	RES, 0 Ω , 5%, 0.1W, 0603	R72	Vishay-Dale	CRCW06030000Z0EA	0	Y	0603

8 PCB Layout

This design is implemented in 2 layers PCB. For optimal performance of this design follow standard PCB layout guidelines: including providing decoupling capacitors close to all ICs and adequate power and ground connections with large copper pours. Additional considerations must be made for providing robust EMC and EMI immunity. All protection components should be placed as close to the output connectors as possible to provide a controlled return path for transient currents that does not cross sensitive components. For best performance, low impedance thick traces should be used along the protection circuits. Pour copper where ever possible.

8.1 Layout Recommendations

In order to achieve a high performance, the following layout guidelines are recommended:

1. Ensure that protection elements such as TVS diodes and capacitors are placed as close to connectors as possible.
2. Use large and wide traces to ensure a low-impedance path for high-energy transients.
3. Place the decoupling capacitors close to the supply pin of the IC.
4. Use multiple vias for power and ground for decoupling caps.
5. Place the reference capacitor close to the voltage reference.

9 Layout Prints

Figure 22 through Figure 29 illustrate the layout prints and some mechanical layout information for the high precision analog front end amplifier and peripherals for MCCB.

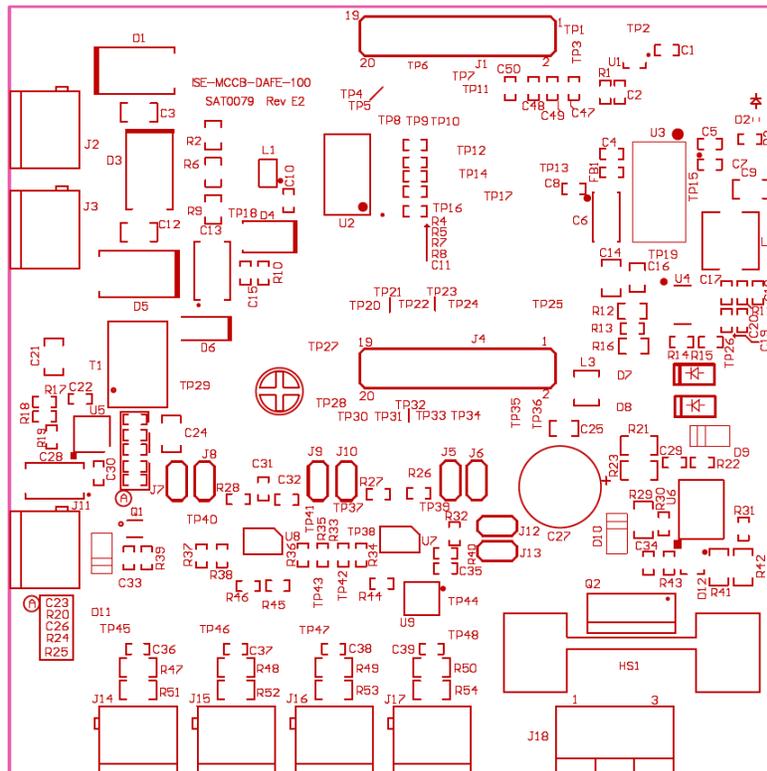


Figure 22. Top Silk Screen

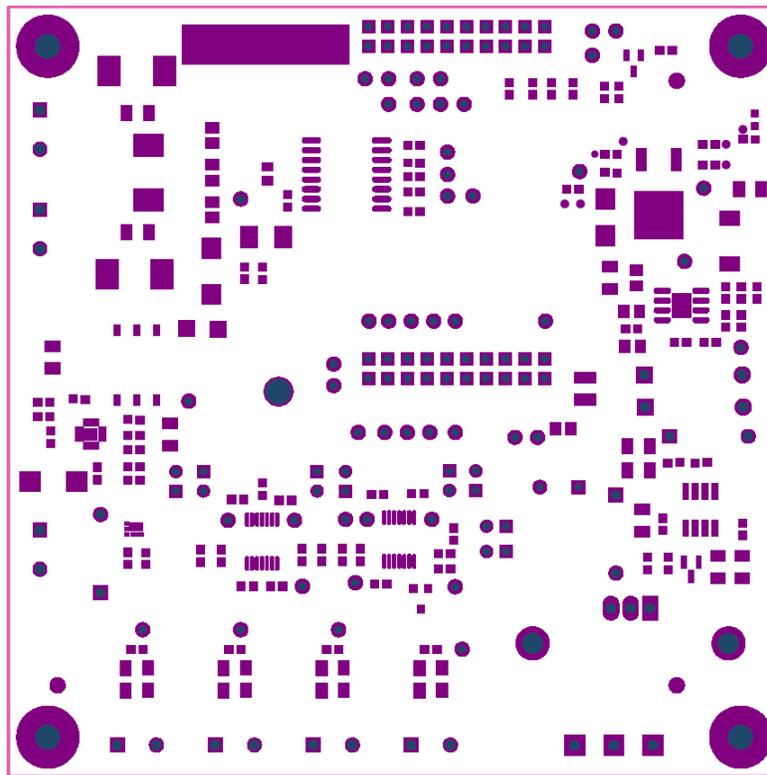


Figure 23. Top Solder Mask

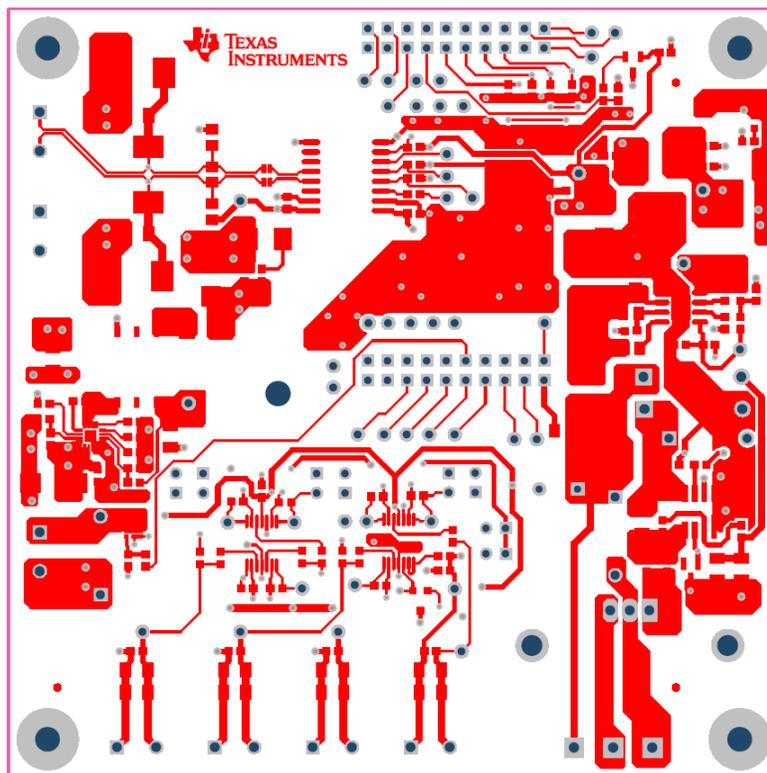


Figure 24. Top Layer

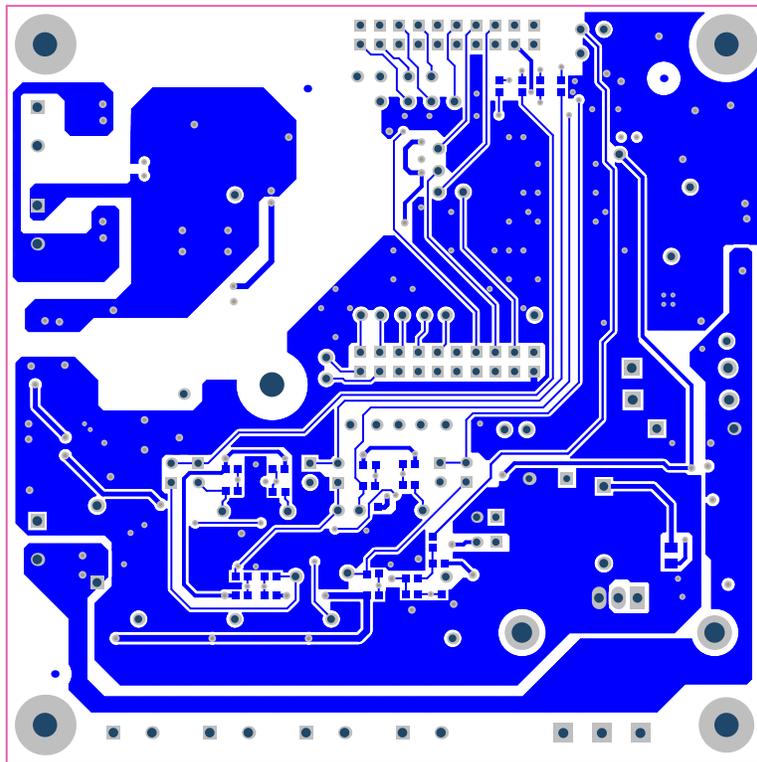


Figure 25. Bottom Layer

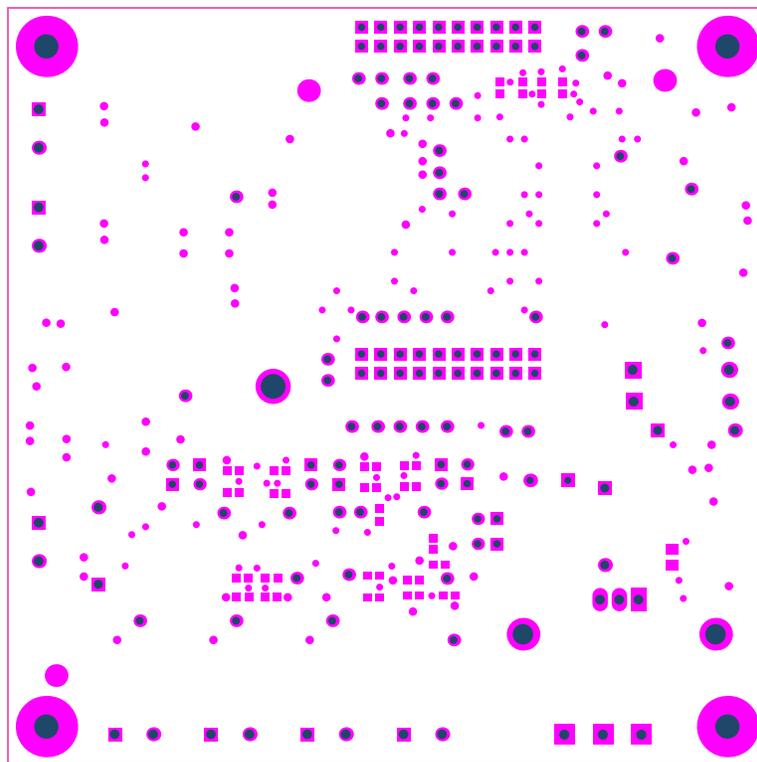


Figure 26. Bottom Solder Mask


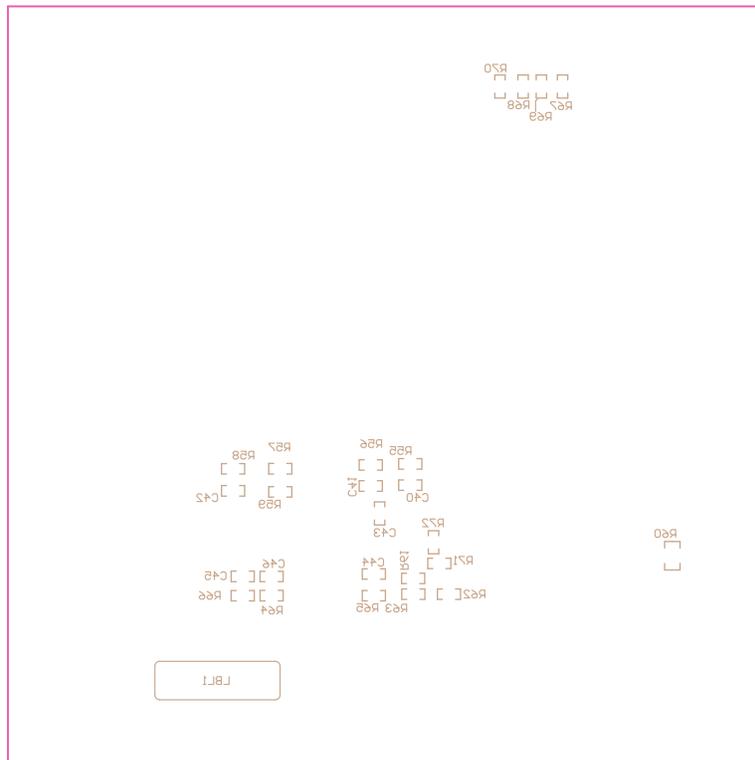


Figure 27. Bottom Silk Screen

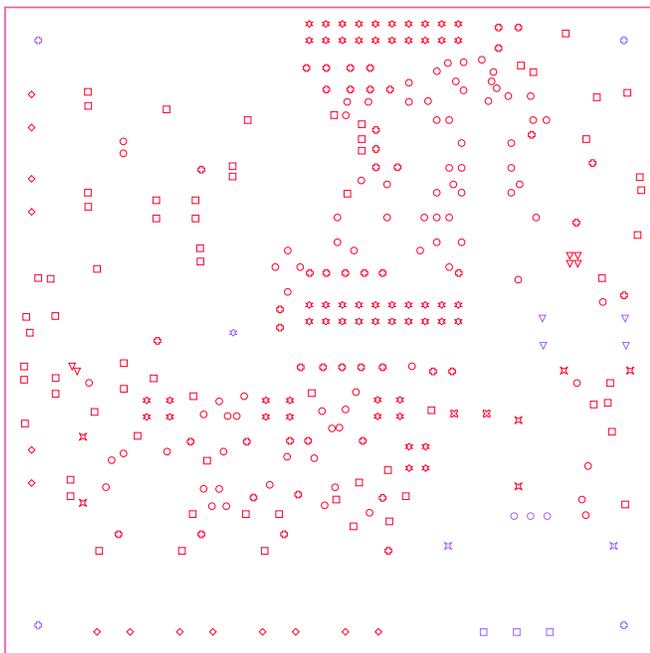

Symbol	Hit Count	Tool Size	Plated	Hole Type
▽	6	12mil (0.305mm)	PTH	Round
○	85	16mil (0.406mm)	PTH	Round
□	68	20mil (0.508mm)	PTH	Round
⊗	2	36mil (0.914mm)	PTH	Round
*	56	38mil (0.965mm)	PTH	Round
⊙	48	40mil (1.016mm)	PTH	Round
×	6	45.276mil (1.15mm)	PTH	Round
◇	14	49.213mil (1.25mm)	PTH	Round
○	3	50mil (1.27mm)	PTH	Round
▽	4	51mil (1.295mm)	PTH	Round
□	3	52mil (1.321mm)	PTH	Round
×	2	106.5mil (2.705mm)	PTH	Round
⊙	4	125.984mil (3.2mm)	PTH	Round
*	1	128mil (3.251mm)	NPTH	Round
302 Total				

Drill Table

DRILL TOLERANCES: FOR PTH +/-3MILS
FOR NPTH +/-2MILS

Figure 28. Drill Drawing

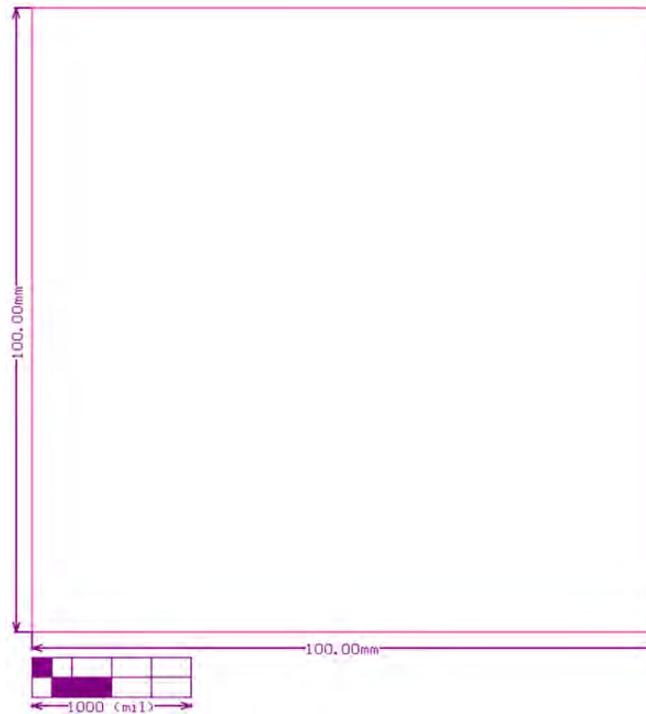


Figure 29. Mechanical Dimensions

10 Altium Project

To download the Altium Project files for the board, see the design files at: www.ti.com/tool/TIDA-00128.

11 Gerber files

To download the Gerber files for the board, see the design files at: www.ti.com/tool/TIDA-00128.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.