

TI Designs: PMP15040

サイズの制限が厳しい産業用センサ向けの、 V_{in} 範囲の広い電源のリファレンス・デザイン



概要

このリファレンス・デザインでは、スペースの制限が最も重要な問題であるようなセンサ・アプリケーションで、FPGA、ASIC、MCUに給電する方法の例を紹介します。この設計は入力電圧範囲が6V～60Vと広く、超小型で効率の高いDC/DCコンバータを使用しているため、産業用センサ、フィールド・トランスマッタ、モータ・ドライブ、PLCモジュールなどのアプリケーションに適しています。出力電圧は可変で、ユーザーの特定の要求に適応可能です。

リソース

PMP15040

デザイン・フォルダ

LMR36006

プロダクト・フォルダ

LMR36015



プロダクト・フォルダ

特長

- ソリューション・サイズの最適化 - 8.3mm×10mm
 - 少ない部品点数
 - 両面実装基板
 - スイッチング周波数: 1MHz
 - 厳密な電流制限
- 広い入力電圧範囲(6V～60V)により、ラインの差異に適合
- 低いノイズ・シグネチャと、静かなスイッチ・ノード
- 出力レール
 - 600mAで5V ($\pm 1.5\%$ 精度)
 - ユーザー固有の要件に適応するため電圧を調整可能

アプリケーション

  - ファクトリ・オートメーション - 変位トランスマッタ
- ファクトリ・オートメーション - 流量トランスマッタ
- ファクトリ・オートメーション - マシン・ビジョン
- モータ・ドライブ - ACドライブ - AC位置フィードバック



使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE (重要な注意事項)をご参照くださいますようお願いいたします。

1 System Description

The PMP15040 is optimized for size-sensitive sensor applications, specifically Field Transmitters and AC Drive Feedback systems. The standard power stage uses a Wide Vin DC/DC converter that enables peak efficiency > 90% as shown in 図 18.

A displacement transmitter uses an analog front-end to convert a signal of a sensor to an electrical representation and digital processor to convert this signal to a digital representation. A standard displacement transmitter uses a non-isolated Wide Vin DC/DC converter as the primary power stage. 図 1 highlights the PMP15040 standard placement within the field transmitter system.

 


図 1. PMP15040 Field Transmitter Block Diagram

An AC Drive Feedback system converts SIN/COS differential inputs from the resolver or encoder to digital outputs, which enables accurate rotor position feedback of AC drives. AC Drive Position Feedback uses a non-isolated Wide Vin DC/DC converter as the primary power stage paired with a Point-of-Load DC/DC converter. These two power rails are necessary to power the Digital Processing component of the system.

図 2 highlights PMP15040 standard placement within the AC Drive Position Feedback system.

 


図 2. PMP15040 Rotary Encoder Block Diagram

1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	SPECIFICATIONS
V_{IN} minimum	6-V
V_{IN} maximum	60-V
V_{IN} nominal	24-V
V_{OUT}	5-V
I_{OUT}	600-mA
F_{SW}	1-MHz
X - Dimension	8.3-mm
Y - Dimension	10-mm

2 System Overview

2.1 Block Diagrams

図 3 shows the PMP15040 block diagram.

 


図 3. PMP15040 General Block Diagram

2.2 Highlighted Products

2.2.1 LMR36006

Features:

- Synchronous buck converter
- Wide operation input voltage: 4.2 V to 60 V (with transient protection up to 66 V)
- 1-MHz switching frequency
- Low quiescent current: 25 μ A
- -40°C to $+150^{\circ}\text{C}$ junction temperature range
- Adjustable 1-V to 28-V output
- Maximum current load: 600 mA for LMR36006 and 1.5 A for LMR36015
- QFN package: 3 mm \times 2 mm

2.3 System Design Theory

The PMP15040 highlights the 8.3 mm \times 10 mm optimized solution size of the LMR36006. The synchronous buck converter, LMR36006, is a wide-input voltage range, low-quiescent current, high performance regulator with internal compensation. The LMR36006 is optimal for size-constraint applications because the LMR36006 has a 3-mm \times 2-mm QFN package size, 1-MHz switching frequency, and a tight current limit. 図 6 shows the schematic of the front-end DC/DC converter. 図 4 and 図 5 show the images of the front and back side of PMP15040 board.

 


図 4. Front of the PMP15040 Board



図 5. Back of the PMP15040 Board

The operating frequency for the LMR36006 regulator is 1 MHz, and the device implements a precise current limit. Consequently, the output filter size and component values are minimized. The LMR36006 offers three operating switching frequency variants: 400 kHz, 1 MHz, and 2.1 MHz. The 1-MHz switching frequency provides peak efficiency greater than 90% at 12 V_{IN} , and peak efficiency greater than 80% at 24 V_{IN} . When the user selects the 1-MHz variant, the inductance range can be decreased from 40 μ H – 50 μ H to 10 μ H – 25 μ H. When the user selects an inductor with an inductance of 18 μ H, the inductor should be capable of handling a maximum current of 1.2 A. Ultimately, inductor manufacturers have a wide selection of 18- μ H inductors in a 4-mm × 4-mm package size. The PMP15040 uses a 18- μ H inductor with a C_{OUT} of 22 μ F.

For the PMP15040, the LMR36006 output voltage is set to 5 V with a resistor divider from FB to V_{OUT} . The top feedback resistor (R_{FBT}) is set to 100 k Ω , and the bottom resistor (R_{FBB}) is calculated using 式 1. V_{REF} is nominally 1 V.

$$R_{FBB} = \frac{R_{FBT}}{\left[\frac{V_{OUT}}{V_{REF}} - 1 \right]} \quad (1)$$

For this 5-V example, values are $R_{FBT} = 100$ k Ω and $R_{FBB} = 24.9$ k Ω . Depending on the power requirement of the downstream digital component, the output voltage can be adjusted. For example, for a MCU which require a typical power rail of 3.3 V, the output voltage can be adjusted.

To scale the output voltage for specific system requirements, the output feedback resistors can be resized. For example, if a MCU requires a typical power rail of 3.3-V, the output voltage can be adapted by recalculating R_{FBB} . For this 3.3-V example values would be $R_{FBT} = 100$ k Ω and $R_{FBB} = 43.5$ k Ω . Furthermore, the PMP15040 output filter (L1 and C_{OUT}) will support the output voltage adjustment.

When scaling the output voltage from 5 V to 3.3 V, the corresponding output power capability of the LMR36006 will decrease from 3 W to 2 W. To increase the power capability of the PMP15040 to 7.5 W at 5 V_{OUT} and 5 W at 3.3 V_{OUT} , the pin-compatible LMR36015 offers a 1.5-A maximum output load current. To adapt the design to the LMR36015, the output filter (L1 and C_{OUT}) must be modified appropriately. TI recommends to modify the L1 to 4.7 μ H and modify the C_{OUT} to 33 μ F. Also, the saturation current of the inductor must support the increased current capability and peak current limit of 3 A. Powered iron cores exhibit a soft saturation current, allowing some relaxation in the current rating of the inductor.

 


図 6. LMR36006 Schematic

The LMR36006 and LMR36015 devices are designed with a flip-chip or HotRod technology, which greatly reduces the parasitic inductance of the pins. Package lead inductance substantially increases the switch node ringing and the corresponding EMI performance. A wire-bond package, 図 7, has significant lead inductance compared to a flipped-chip, on-lead (FCOL) package, 図 8. HotRod technology eliminates wire bonds by attaching the silicon die directly to the lead frame. Consequently HotRod technology lowers R_{DS_ON} , parasitic lead inductance, and dramatically reduces switch node ringing. The switch node waveforms of a wire bond package and a HotRod package can be seen in 図 9 and 図 10.

 


図 7. Standard QFN Package

 


図 8. FCOL QFN Package

 


図 9. Wirebond Device Switch Node Signal

 


図 10. FCOL QFN Device Switch Node Signal

The LMR36006 HotRod package enables the smallest die to package ratio and ultimately enables an optimized layout and total solution size of 8.3 mm × 10 mm shown in 図 11. The optimized layout is highlighted in 図 12 and 図 13.

 


図 11. PMP15040 Board Dimensions

 


図 12. PMP15040 PCB Layout: Top Layer

 


図 13. PMP15040 PCB Layout: Bottom Layer

For design calculations and layout examples, see the relevant data sheet for the devices:

- [LMR36006 4.2-V to 60-V, 0.6-A Synchronous Step-Down Converter in HotRod™ Package \(SNVS848\)](#)
- [LMR36015 4.2-V to 60-V, 1.5-A Synchronous Step-Down Converter in HotRod™ Package \(SNVS849\)](#)

3 Hardware, Testing Requirements, and Test Results

3.1 Required Hardware

3.1.1 Hardware

These steps outline the hardware setup:

1. Connect a DC power supply to the board input as shown in [図 14](#).
2. Connect an electronic or resistive load to the LMR36006 output (V_{OUT}), as shown in [図 14](#), to imitate the typical load.

 


図 14. PMP15040 Board Setup

3.2 Testing and Results

The following diagrams show the design performance.

3.2.1 Thermal Data

The infrared (IR) thermal image in 図 15 was taken at steady state with 24 V_{IN} and the LMR36006 output at a load of 10 mA (no airflow). The ambient temperature is approximately 22°C . The maximum IC temperature is 28.4°C .

 


図 15. Thermal Image at 24 V_{IN} , 5 V_{OUT} , $10\text{ mA I}_{\text{OUT}}$

The infrared (IR) thermal image in 図 16 was taken at the steady state with 24 V_{IN} and the LMR36006 output at a load of 300 mA (no airflow). The ambient temperature is approximately 22°C . The maximum IC temperature is 68°C .

 


図 16. Thermal Image at 24 V_{IN} , 5 V_{OUT} , $300\text{ mA I}_{\text{OUT}}$

The infrared (IR) thermal image in [図 17](#) was taken at the steady state with 24 V_{IN} and the LMR36006 output at a load of 600 mA (no airflow). The ambient temperature is approximately 22°C. The maximum IC temperature is 85°C.

 


図 17. Thermal Image at 24 V_{IN} , 5V_{OUT} , 600 mA I_{OUT}

3.2.2 Efficiency Data

[図 18](#) shows the PMP15040 efficiency data versus a load current.

 


図 18. Efficiency vs. Output Current

3.2.3 Start-Up Waveforms

図 19 shows the start-up waveform at 24-V input and no load. 図 20 shows the start-up waveform at 24-V input and 600-mA load.

 


図 19. Start-Up Waveform: $V_{IN} = 24$ V, $I_{OUT} = 0$ A

 


図 20. Start-Up Waveform: $V_{IN} = 24$ V, $I_{OUT} = 600$ mA

3.2.4 Switch Node and Output Voltage Ripple

図 21 shows the steady-state switch-node voltage and output voltage ripple at 24 V_{IN} and 0-A load. 図 22 shows the steady-state, switch-node voltage and output voltage ripple at 24 V_{IN} and 600-mA load. 図 23 shows the steady-state switch-node voltage and output voltage ripple at 60 V_{IN} and 0-A load. 図 24 shows the steady-state, switch-node voltage and output voltage ripple at 60 V_{IN} and 600-mA load.

 


図 21. Steady-State Waveform: $V_{IN} = 24$ V, $I_{OUT} = 0$ A

 


図 22. Steady-State Waveform: $V_{\text{IN}} = 24 \text{ V}$, $I_{\text{OUT}} = 600 \text{ mA}$

 


図 23. $V_{\text{IN}} = 60 \text{ V}$, $I_{\text{OUT}} = 0 \text{ A}$


 



図 24. $V_{\text{IN}} = 60 \text{ V}$, $I_{\text{OUT}} = 600 \text{ mA}$

3.2.5 Load Transient

The load transient waveforms monitor the output voltage and the load current. Channel 1 (blue) shows the output current of the LMR36006 (I_{OUT}). Channel 2 (purple) shows the output voltage of the LMR36006 (V_{OUT}). [図 25](#) and [図 26](#) show the load transient results.

 

**図 25. Load Transient: $I_{OUT} = 0 \text{ A}$ to 600 mA , $V_{IN} = 24 \text{ V}$,
 $t_R=1 \text{ A}/\mu\text{s}$**

 

**図 26. Load Transient: $I_{OUT} = 600 \text{ mA}$ to 0 A , $V_{IN} = 24 \text{ V}$,
 $t_F=1 \text{ A}/\mu\text{s}$**

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [PMP15040](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [PMP15040](#).

4.3 PCB Layout Recommendations

4.3.1 Layout Prints

To download the layer plots, see the design files at [PMP15040](#).

4.4 Altium Project

To download the Altium project files, see the design files at [PMP15040](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [PMP15040](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [PMP15040](#).

5 Related Documentation

1. [LMR36006 4.2-V to 60-V, 0.6-A Synchronous Step-Down Converter in HotRod™ Package](#) (SNVSB48)
2. [LMR36015 4.2-V to 60-V, 1.5-A Synchronous Step-Down Converter in HotRod™ Package](#) (SNVSB49)
3. [Powering up the Performance of Sensitive Test and Measurement Systems](#), blog

5.1 商標

All trademarks are the property of their respective owners.

改訂履歴

資料番号末尾の英字は改訂を表しています。その改訂履歴は英語版に準じています。

2018年6月発行のものから更新

Page

- Changed *Efficiency vs. Output Current graph* 10

重要なお知らせと免責事項

TIは、技術データと信頼性データ(データシートを含みます)、設計リソース(リファレンス・デザインを含みます)、アプリケーションや設計に関する各種アドバイス、Webツール、安全性情報、その他のリソースを、欠陥が存在する可能性のある「現状のまま」提供しており、商品性および特定目的に対する適合性の默示保証、第三者の知的財産権の非侵害保証を含むいかなる保証も、明示的または默示的にかわらず拒否します。

これらのリソースは、TI製品を使用する設計の経験を積んだ開発者への提供を意図したものです。(1)お客様のアプリケーションに適したTI製品の選定、(2)お客様のアプリケーションの設計、検証、試験、(3)お客様のアプリケーションが適用される各種規格や、その他のあらゆる安全性、セキュリティ、またはその他の要件を満たしていることを確実にする責任を、お客様のみが単独で負うものとします。上記の各種リソースは、予告なく変更される可能性があります。これらのリソースは、リソースで説明されているTI製品を使用するアプリケーションの開発の目的でのみ、TIはその使用をお客様に許諾します。これらのリソースに関して、他の目的で複製することや掲載することは禁止されています。TIや第三者の知的財産権のライセンスが付与されている訳ではありません。お客様は、これらのリソースを自身で使用した結果発生するあらゆる申し立て、損害、費用、損失、責任について、TIおよびその代理人を完全に補償するものとし、TIは一切の責任を拒否します。

TIの製品は、TIの販売約款(<https://www.tij.co.jp/ja-jp/legal/terms-of-sale.html>)、またはti.comやかかるTI製品の関連資料などのいずれかを通じて提供する適用可能な条項の下で提供されています。TIがこれらのリソースを提供することは、適用されるTIの保証または他の保証の放棄の拡大や変更を意味するものではありません。

日本語版 日本テキサス・インスツルメンツ合同会社
Copyright © 2021, Texas Instruments Incorporated