

**TI Designs: TIDA-050014****パワーDUOシンク、200W USB-C PDのリファレンス・デザイン****概要**

このUSB電力供給(PD)のリファレンス・デザインは、動作に100W以上を必要とするシステムをユーザーが実装するためのもので、同時に業界で最も低いRDS<sub>on</sub>のソリューションも示しています。このデザインは、4つの標準ソース電圧(5V、9V、15V、20V)をすべてシンクできます。標準のType-C PD動作で、最大20V/5Aまでシンク可能です。テキサス・インスツルメンツのパワーPower DUO代替モードで動作しているとき、このデザインは最大20V/10Aを出力でき、同時にRDS<sub>on</sub>を1/2に減らすことができます。

**リソース**

TIDA-050012

デザイン・フォルダ

TIDA-050014

デザイン・フォルダ

TPS65987D

プロダクト・フォルダ

TPS768

プロダクト・フォルダ

TPD2E009

プロダクト・フォルダ

**特長**



- 10Aで20Vのシンク能力
- 大電力のUSB Type-C PDシンク
- 低いRDS<sub>on</sub>
- シンク電圧をユーザーが選択可能
- システム負荷をシミュレートするためのテスト・ポイント
- プログラミングおよび構成用のFTDI

**アプリケーション**

- ノートブックおよびラップトップ
- パーソナル・エレクトロニクス
- 高電圧のパワー・バンク
- PDコントローラの統合電源パス



E2ETM エキスパートに質問

  

使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE (重要な注意事項)をご参照くださいますようお願いいたします。

## 1 System Description

This design highlights how to implement a high power USB Type-C PD sink device. This design can be referenced for various different end equipments, from Notebooks, TV's and monitors, power banks, and any other system that sinks power from a source charger. Through the use of a Texas Instruments USB PD Alternate Mode, the TPS65987D PD adapter will close both of it's load switches in parallel to double the current carrying capability and reduce the effective  $RDS_{on}$  by a factor of two. The design also highlights a feature of the TPS65987D called App Config by allowing users to select their Type-C PD input voltage through push button switches.

### 1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Input Power Source	20 V USB Type-C PD (200 W recommended for full feature use)
System Quiescent Current	3.4 mA
Typical Load Switch $RDS_{on}$	29 mOhm
Power DUO Alternate Mode $RDS_{on}$	14.5 mOhm

## 2 System Overview

### 2.1 Block Diagram

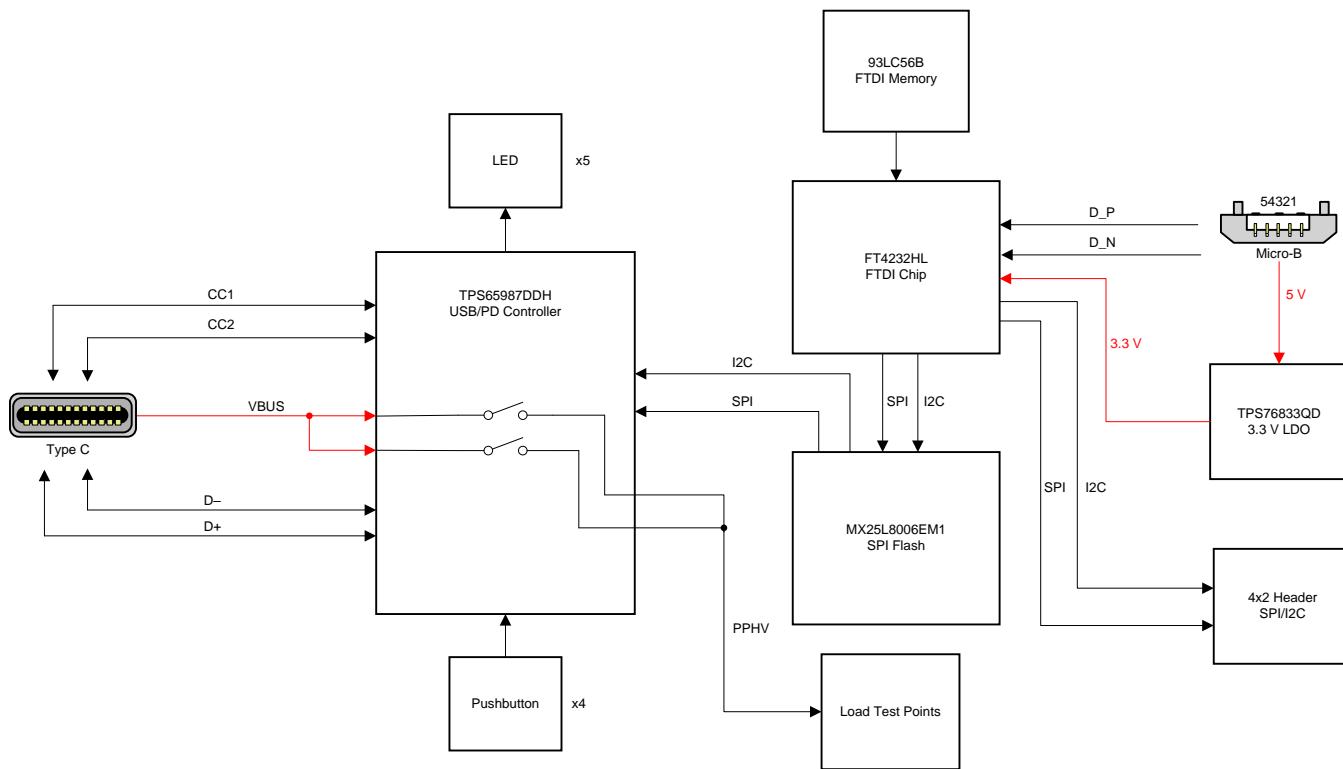


図 1. TIDA-050014 Block Diagram

### 2.2 Design Considerations

TIDA-050014 gives an example of how to implement a USB Type-C PD system that is capable of handling high current. This design can be used in monitors, dongles, power banks, and any other system that would benefit from having more than 100 W of power sourced to it. If the end user will exceed 5 A of current, it is recommended to use a tethered cable instead of a Type-C receptacle. This would allow the user to develop their own high current cable and not be limited by the cables and connectors in the design.

### 2.3 Highlighted Products

#### 2.3.1 TPS65987D

The TPS65987D is a stand-alone USB Type-C and Power Delivery (PD) controller providing cable plug and orientation detection for a single USB Type-C connector. Upon cable detection, the TPS65987D communicates on the CC wire using the USB PD protocol. When cable detection and USB PD negotiation are complete, the TPS65987D enables the appropriate power path and configures alternate mode settings for external multiplexers.

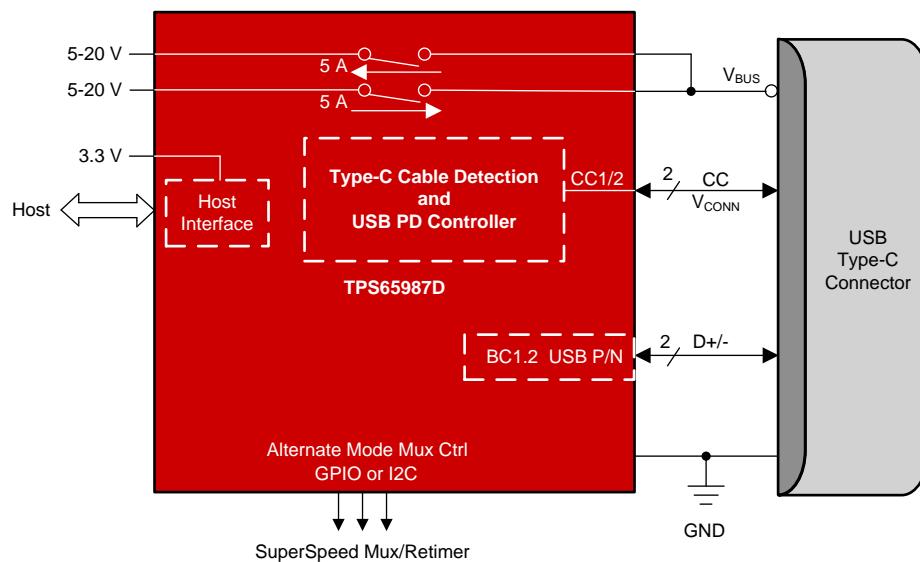


図 2. TPS65987D Simplified Schematic

### 2.3.2 TPS768xx

This device is designed to have a fast transient response and be stable with 10 mF capacitors. This combination provides high performance at a reasonable cost.

Since the PMOS device behaves as a low-value resistor, the dropout voltage is very low (typically 230 mV at an output current of 1 A for the TPS76850) and is directly proportional to the output current.

Additionally, because the PMOS pass element is a voltage-driven device, the quiescent current is very low and independent of output loading (typically 85 mA over the full range of output current, 0 mA to 1 A).

These two key specifications yield a significant improvement in operating life for battery-powered systems. This LDO family also features a shutdown mode; applying a TTL high signal to EN (enable) shuts down the regulator, reducing the quiescent current to less than 1 mA at  $T_J = 25^\circ\text{C}$ .

Power good (PG) is an active high output, which can be used to implement a power-on reset or a low-battery indicator.

 



図 3. TPS768xx Simplified Schematic

### 2.3.3 TPD2E009

The TPD2E009 device provides two ESD protection diodes with flow-through pin mapping for ease of board layout. This device has been designed to protect sensitive components which are connected to ultra high-speed data and transmission lines. The TPD2E009 offers transient voltage suppression for Level 4 of IEC 61000-4-2 Contact ESD protection. TVS protection up to a 5-A (8/20  $\mu$ s) peak pulse-current rating per the IEC 61000-4-5 (lightning) specification is also provided.

The monolithic silicon technology allows matching between the differential signal pairs. The less than 0.05-pF differential capacitance ensures that the differential signal distortion due to added ESD circuit protection remains minimal. The low capacitance (0.7-pF) is suitable for high-speed data rates up to 6 Gbps.

Typical applications for the TPD2E009 line of ESD protection products are: HDMI, USB, eSATA, and ethernet interfaces in notebooks, DVD and media players, set-top boxes, and portable computers.

 


**図 4. TPD2E009 Simplified Schematic**

## 2.4 System Design Theory

### 2.4.1 TPS65987D PD Controller

The TPS65987D has two internal power paths that are capable of handling 5 A each. This design is intended to allow for loads larger than 5 A to be applied, which is why the two power paths are connected to one another. VBUS\_SINK is connected to the Type-C connector, while PP\_HV\_Sink is connected to what would be the system load.

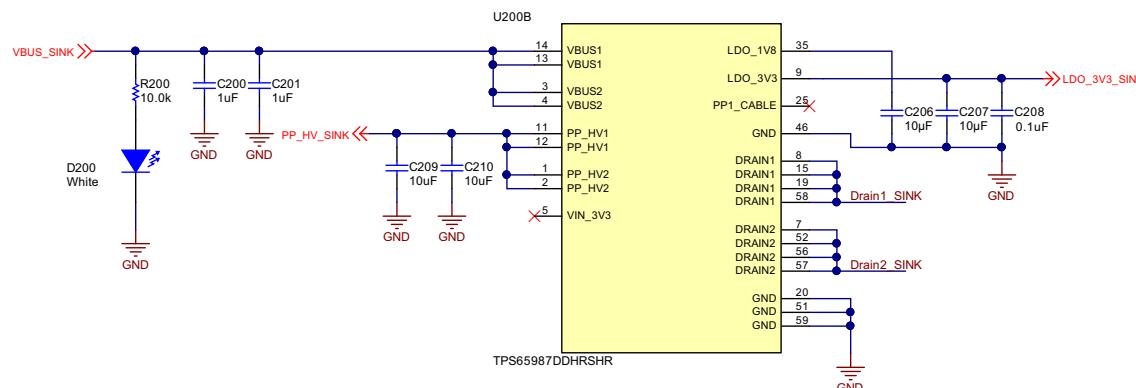

**図 5. TPS65987D Power Path**

A total of eight GPIO's are used from the TPS65987D. Four are connected to an external FET, and the other three are connected to pushbuttons. Their intended use case and functionality are explained within [2.4.3](#). The TPS65987D has the ability to change its corresponding I2C address and start function via an external resistor divider network connected to ADCIN1 and ADCIN2. In this resistor divider configuration, the TPS65987D will have an I2C address of 1 with a BP\_NoWait boot mode.

 


図 6. TPS65987D USB PD Controller Schematic

An external SPI-Flash is used for holding the application that is written onto the board from the app configuration tool. Upon booting, the TPS65987D will read back the application code from the SPI-Flash. The SPI-Flash is only accessed upon initial boot up and power on reset events.

 
 
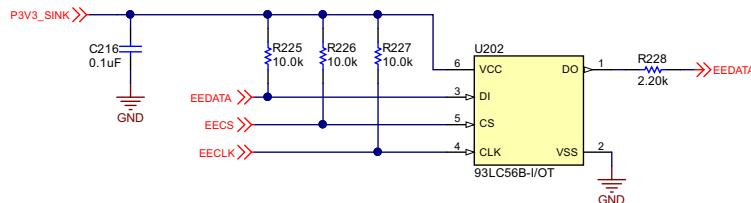



図 7. SPI Flash Schematic

## 2.4.2 FTDI

Located on the TIDA-050014 is the FT4232HL, which is an FTDI chip. This allows for the board to be programmed by a Type-B cable connected to a laptop, as the FT4232HL is able to convert the DP/DM data lines from a USB cable to SPI and I2C. The I2C lines from the FT4232HL go straight to the TPS65987D, while the SPI connections go to both the TPS65987D as well as the SPI flash. The FT4232HL needs an external source of memory, which is what the 93LC56B is used for.


**図 8. FTDI Chip Schematic FT4232HL**

**図 9. FTDI Memory Schematic 93LC56B**

 The USB Type-B cable will supply 5 V to the TIDA-050014 via VBUS. The TPS76833QD is used to regulate the 5 V from VBUS to 3.3 V, which is then used to power the FTDI.


**図 10. LDO Schematic TPS76833QD**

## 2.4.3 Buttons and LEDs

TIDA-050014 is designed to request four different PDO's depending on what the customer is wanting to test. 9V\_PB\_SINK, 15V\_PB\_SINK, and 20V\_PB\_SINK are connected to three individual GPIO pins on the TPS65987D. 5V\_PB\_SINK will be connected to HRESET. When the push buttons are not pressed, each of the GPIO's will be pulled low. Upon initial startup, each GPIO will be pulled low and the TPS65987D will go in its default state of requesting 5 V. When a push button is pressed, its corresponding GPIO will be pulled high, and then that sink voltage will be requested by the TPS65987D.

For example, a USB Type-C PD source controller, capable of supplying up to 20 V, is connected to the TIDA-050014. The TIDA-050014 will go into its default state, and request 5 V from the source controller. If the user wants the sink voltage to change to 20 V, they would then press the pushbutton labeled "20 V". This will pull 20V\_PB\_SINK and it's corresponding GPIO high. The TPS65987D would then request a 20 V PDO from the source controller, and the voltage on VBUS would then rise to 20 V. If they wish to return back to 5 V, press the button labeled "5 V". This will pull 5V\_PB\_SINK and HRESET high, and the TPD65987D will reset. When the TPS65987D comes back on, it will then request it's default voltage of 5 V.


 



図 11. Push Buttons

5V\_LED, 9V\_LED, 15V\_LED, and 20V\_LED are all connected to their own individual GPIO from the TPS65987D. These LED's signify what the TPS65987D is currently sinking from the source PD controller. For example, if 20 V is negotiated between the sink and the source PD controllers and applied on VBUS, the GPIO connected to the 20 V LED will drive the gate on the BSS138W high, allowing for current to flow turning on the LED.

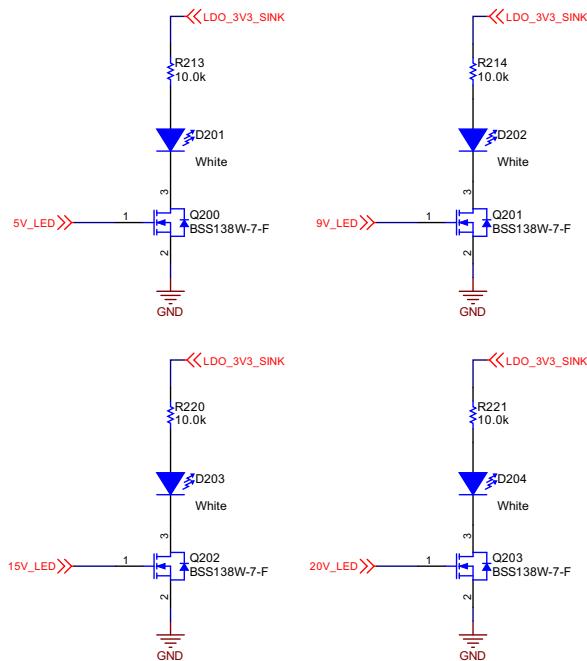

**図 12. Voltage LEDs**

#### 2.4.4 Hardware

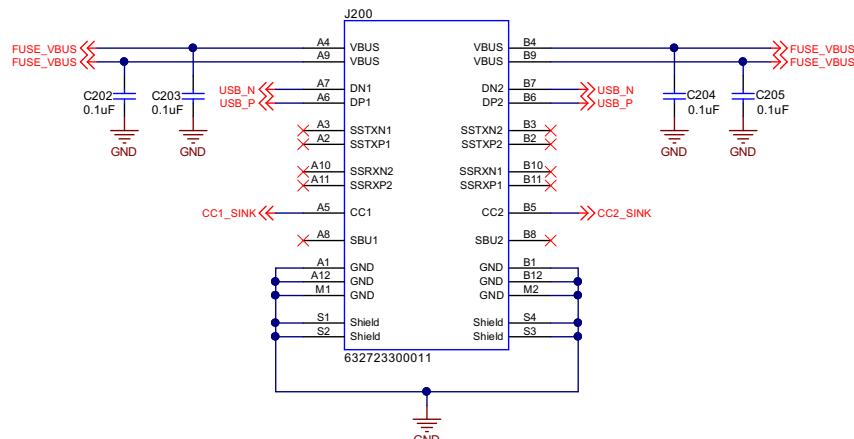

**図 13. Type-C Connector and Fuse**

 


図 14. USB Type-B Connector

 


図 15. SPI and I2C Resistors



図 16. SPI CS Header

 


図 17. Programming Header

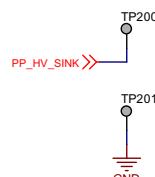


図 18. PPHV Test Points

### 3 Hardware, Software, Testing Requirements, and Test Results

#### 3.1 Required Hardware and Software

To fully test the TIDA-050014 board, the following items are required:

1. Windows PC with TPS6598x Application Customization Tool installed
2. TIDA-050012 Companion TI-Design board
3. High Current Type-C Cable
4. 230 W Barrel Jack Connector or High Powered Bench Supply capable of sourcing 20 V at 10 A
5. E-load or resistive load

##### 3.1.1 Hardware

For use of this design, a high powered power source is required. The power source must be able to source at least 20 V at 10 A.

##### 3.1.2 Software

The TPS6598x Application Customization Tool must be installed on the Windows PC used to interface with this design.

### 3.2 Testing and Results

#### 3.2.1 Test Setup

The effective  $RDS_{on}$  was measured using Power Duo mode and in normal operation. The results are highlighted in 表 2 and 表 3. Each measurement was taken with various currents going through VBUS. The boards were left for 5 minutes before the voltage drop across the power path was measured to allow for the drop to reach a steady state.

#### 3.2.2 Test Results

表 2.  $RDS_{on}$  Power Duo Mode Measurements

VBUS Voltage (V)	VBYs Current (A)	Voltage Drop across Power Path (mV)	Effective $RDS_{on}$ (mOhm)
20	1.5	21.48	14.32
20	2	28.16	14.08
20	3	44.42	14.81
20	4	58.12	14.53
20	5	76.32	15.26
20	6	97.32	16.24
20	7	120.36	17.19
20	8	145.32	18.17
20	9	175.76	19.53
20	10	216.78	21.68

表 3.  $RDS_{on}$  Single Power Path Measurements

VBUS Voltage (V)	VBYs Current (A)	Voltage Drop Across Power Path (mV)	Effective $RDS_{on}$ (mOhm)
20	1.5	44.2	29.48
20	2	56.89	28.45
20	3	86.12	28.71
20	4	119.78	29.95
20	5	158.74	31.75

From the results above, it can be seen that the Power DUO Mode  $RDS_{on}$  is about half of the single power path  $RDS_{on}$ . This can be modeled as two FETs in parallel. The effective  $RDS_{on}$  when two of the same FETs are in parallel will be roughly half  $RDS_{on}$  of a single one.

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-050014](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-050014](#).

### 4.3 PCB Layout Recommendations

#### 4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-050014](#).

### 4.4 Altium Project

To download the Altium Designer® project files, see the design files at [TIDA050014](#).

### 4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-050014](#).

### 4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-050014](#).

## 5 Software Files

To download the software files, see the design files at [TIDA-050014](#).

## 6 Related Documentation

1. [TPS65987DDH Power Path Performance and Documentation](#)

### 6.1 商標

E2E is a trademark of Texas Instruments.

Altium Designer is a registered trademark of Altium LLC or its affiliated companies.

すべての商標および登録商標はそれぞれの所有者に帰属します。

## 7 Terminology

The terminology used in this design guide is all related to the USB Type-C and PD specifications. These specifications can be downloaded from the USB-IF website.

## 重要なお知らせと免責事項

TI は、技術データと信頼性データ(データシートを含みます)、設計リソース(リファレンス・デザインを含みます)、アプリケーションや設計に関する各種アドバイス、Web ツール、安全性情報、その他のリソースを、欠陥が存在する可能性のある「現状のまま」提供しており、商品性および特定目的に対する適合性の默示保証、第三者の知的財産権の非侵害保証を含むいかなる保証も、明示的または默示的にかかわらず拒否します。

これらのリソースは、TI 製品を使用する設計の経験を積んだ開発者への提供を意図したものです。(1) お客様のアプリケーションに適した TI 製品の選定、(2) お客様のアプリケーションの設計、検証、試験、(3) お客様のアプリケーションが適用される各種規格や、その他のあらゆる安全性、セキュリティ、またはその他の要件を満たしていることを確実にする責任を、お客様のみが単独で負うものとします。上記の各種リソースは、予告なく変更される可能性があります。これらのリソースは、リソースで説明されている TI 製品を使用するアプリケーションの開発の目的でのみ、TI はその使用をお客様に許諾します。これらのリソースに関して、他の目的で複製することや掲載することは禁止されています。TI や第三者の知的財産権のライセンスが付与されている訳ではありません。お客様は、これらのリソースを自身で使用した結果発生するあらゆる申し立て、損害、費用、損失、責任について、TI およびその代理人を完全に補償するものとし、TI は一切の責任を拒否します。

TI の製品は、TI の販売条件 ([www.tij.co.jp/ja-jp/legal/termsofsale.html](http://www.tij.co.jp/ja-jp/legal/termsofsale.html))、または [ti.com](http://ti.com) やかかる TI 製品の関連資料などのいずれかを通じて提供する適用可能な条項の下で提供されています。TI がこれらのリソースを提供することは、適用される TI の保証または他の保証の放棄の拡大や変更を意味するものではありません。

Copyright © 2018, Texas Instruments Incorporated  
日本語版 日本テキサス・インスツルメンツ株式会社

## 重要なお知らせと免責事項

TI は、技術データと信頼性データ(データシートを含みます)、設計リソース(リファレンス・デザインを含みます)、アプリケーションや設計に関する各種アドバイス、Web ツール、安全性情報、その他のリソースを、欠陥が存在する可能性のある「現状のまま」提供しており、商品性および特定目的に対する適合性の默示保証、第三者の知的財産権の非侵害保証を含むいかなる保証も、明示的または默示的にかかわらず拒否します。

これらのリソースは、TI 製品を使用する設計の経験を積んだ開発者への提供を意図したものです。(1) お客様のアプリケーションに適した TI 製品の選定、(2) お客様のアプリケーションの設計、検証、試験、(3) お客様のアプリケーションが適用される各種規格や、その他のあらゆる安全性、セキュリティ、またはその他の要件を満たしていることを確実にする責任を、お客様のみが単独で負うものとします。上記の各種リソースは、予告なく変更される可能性があります。これらのリソースは、リソースで説明されている TI 製品を使用するアプリケーションの開発の目的でのみ、TI はその使用をお客様に許諾します。これらのリソースに関して、他の目的で複製することや掲載することは禁止されています。TI や第三者の知的財産権のライセンスが付与されている訳ではありません。お客様は、これらのリソースを自身で使用した結果発生するあらゆる申し立て、損害、費用、損失、責任について、TI およびその代理人を完全に補償するものとし、TI は一切の責任を拒否します。

TI の製品は、TI の販売条件 ([www.tij.co.jp/ja-jp/legal/termsofsale.html](http://www.tij.co.jp/ja-jp/legal/termsofsale.html))、または [ti.com](http://ti.com) やかかる TI 製品の関連資料などのいずれかを通じて提供する適用可能な条項の下で提供されています。TI がこれらのリソースを提供することは、適用される TI の保証または他の保証の放棄の拡大や変更を意味するものではありません。

Copyright © 2018, Texas Instruments Incorporated  
日本語版 日本テキサス・インスツルメンツ株式会社