

## デザイン・ガイド: TIDA-010075

1.0A の電流と、 $\pm 1.5\%$  の電圧精度を持つ、コスト最適化されたバッテリ充電器のリファレンス・デザイン

## 概要

このリファレンス・デザインでは、ミッドエンドまたはローエンドのロボット掃除機用の、コスト最適化されたオンボード・バッテリ充電器ソリューションを紹介します。このソリューションはレイアウト面積が  $4.8\text{cm}^2$  で、1.0A の充電電流を供給でき、 $\pm 1.5\%$  の充電電圧精度と、 $\pm 3\%$  の充電電流精度を実現します。このデザインは、安定した円滑な CC-CV 充電プロファイルを持ち、4S2P のリチウムイオン・バッテリ・パックで評価済みです。

## リソース

TIDA-010075

デザイン・フォルダ

TPS54202

プロダクト・フォルダ

TLV9001

プロダクト・フォルダ

TVS3300

プロダクト・フォルダ

## 特長


- アダプタの入力電圧範囲: 18.7V~28V
- 一定の充電電流: 1.0A
- 同期整流降圧トポロジにハイサイド FET およびローサイド FET を統合
- $\pm 1.5\%$  の充電電圧精度
- $\pm 3\%$  の充電電流精度
- レイアウトの小さな占有面積:  $4.8\text{cm}^2$
- 動作時周囲温度: 0°C~40°C

## アプリケーション

- ロボット掃除機
- コードレス掃除機
- ヒューマノイド



Search Our E2E™ support forums

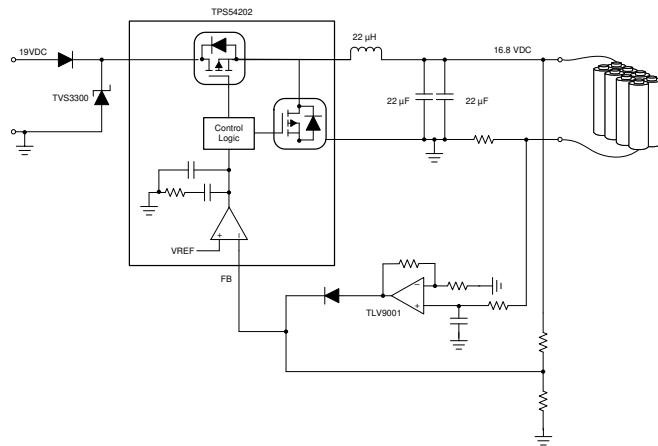

使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE (重要な注意事項)をご参照くださいますようお願いいたします。

## 1 System Description


A vacuum robot, also called a robotic vacuum cleaner, which has been around for about 23 years, is getting more intelligent and automatic. There is an expectation that robots should be able to do a full cleaning cycle before needing to charge again. With more features added in a vacuum robot, such as mopping, audio interaction, navigating thick carpet, and climbing higher thresholds, the power requirement for a full cleaning cycle is increasing, so the battery capacity is becoming bigger, typically from 2600 mAh to 5200 mAh.

Meanwhile, this also increase the requirements for the battery charger. The following items list the general requirements for an onboard charger, which means the charger circuit is implemented on the main board of the robot, which is widely used for almost all brands of vacuum robots around the world:

- High charging current
- Cost effective
- Small size
- High charging voltage accuracy
- High charging current accuracy
- Easy to design

Two different solutions are implemented to achieve an onboard charger. One is an asynchronous buck topology charger which uses the system micro controller (MCU) as the digital controller. 図 1 shows the block diagram of this solution.

図 1. Asynchronous Buck Topology Charger Controlled by System MCU

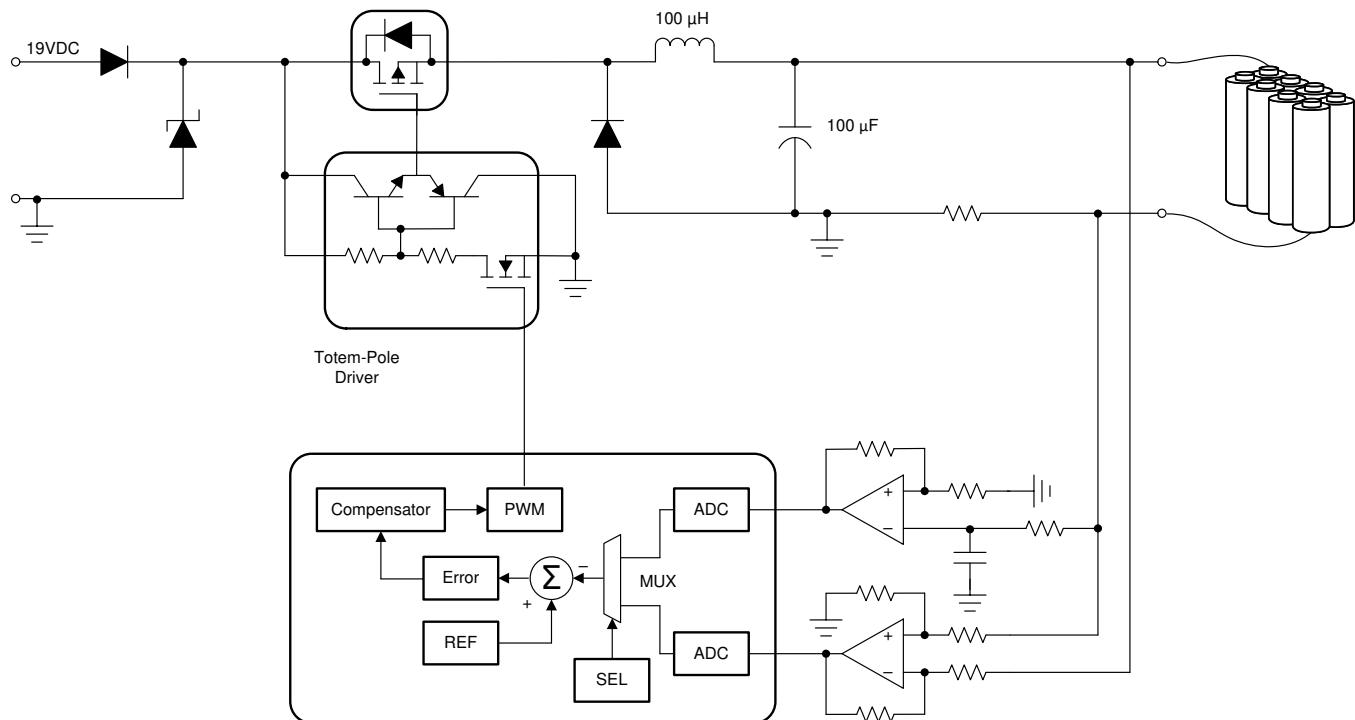


This solution is a digital-controlled, switch-mode power supply (SMPS); 'digital control' means sampling feedback information and closing the loop numerically, the error amplifier is replaced with an analog-to-digital converter (ADC) and a digital filter, the compensator uses digital-signal processing techniques to construct the control effort for the PWM.

The following items list several pros and cons of this solution:

- Limited switching frequency due to limited ADC sampling rate and Nyquist-Shannon sampling theorem, typically from 50 kHz to 100 kHz
- Large value of inductor and output capacitor needed to meet the strict output voltage regulation requirement, and large size to occupy board area
- Low efficiency due to the asynchronous buck topology and low thermal performance especially affected by the power dissipation of the free-wheeling diode
- Complex digital-signal processing techniques to achieve a stable closed loop and keep multiple MCU resources occupied, such as memory, PWM, ALU, ADC, the charging voltage accuracy depends on the accuracy of the reference voltage for ADC, and the charging voltage accuracy is around  $\pm 3\%$ .

The other mainstream solution is using a highly-integrated battery charger IC to achieve the full charging profile with  $\pm 0.5\%$  charging voltage accuracy. [图 2](#) shows the block diagram of this solution.

**图 2. Integrated Onboard Charger Based on BQ24xxx**

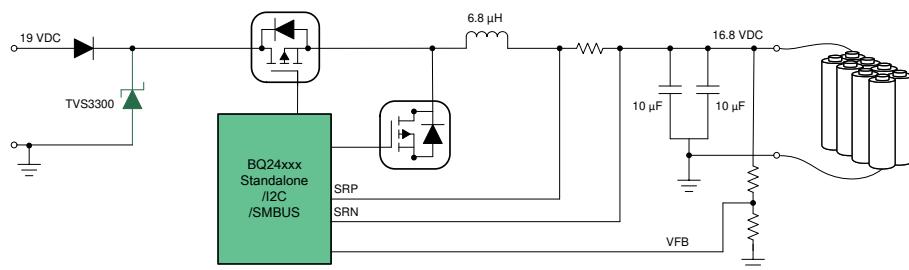

The following items list several pros and cons of this solution:

- High switching frequency from 600 kHz to 1.2 MHz, this minimizes the value of the inductor and capacitor and the layout area
- High charge current, commonly from 1.5 A to 3 A, up to 10 A, to support fast charging
- High charge voltage accuracy at  $\pm 0.5\%$ , maximized capacity extends runtime and longer battery lifetime
- Accurate termination current, typically 10% of the charge current, maximizes capacity and extends runtime
- Built-in overcurrent, overvoltage, thermal shutdown, and FET short protections to meet strict safety criterion
- Standalone topology for easy-to-implement, and host-controlled topologies for more design flexibility

TI's BQ24xxx family is well suited for this solution, the notable products are the [BQ24610](#), [BQ24725A](#), and [BQ24773](#) devices.

Meanwhile, this design provides another solution which makes trade offs between the above two solutions.

## 1.1 Key System Specifications

**表 1. Key System Specifications**

| PARAMETER           | SPECIFICATIONS | DETAILS |
|---------------------|----------------|---------|
| Input voltage range | 17 V to 28 V   | ----    |


表 1. Key System Specifications (continued)

| PARAMETER                     | SPECIFICATIONS     | DETAILS                 |
|-------------------------------|--------------------|-------------------------|
| Number of cells in series     | 4S                 | ----                    |
| Charge current                | 1.0A               | ----                    |
| Charge voltage accuracy       | $\pm 1.5\%$        | ----                    |
| Charge current accuracy       | $\pm 1\%$          | ----                    |
| Charge voltage ripple         | $\pm 0.023\%$      | <a href="#">3.2.2.2</a> |
| Efficiency                    | > 90%, up to 93.5% | <a href="#">3.2.2.3</a> |
| PCB size                      | 3.0 cm x 1.8 cm    | ----                    |
| Operating ambient temperature | 0°C to 40°C        | ----                    |

## 2 System Overview

### 2.1 Block Diagram

図 3. TIDA-010075 Block Diagram

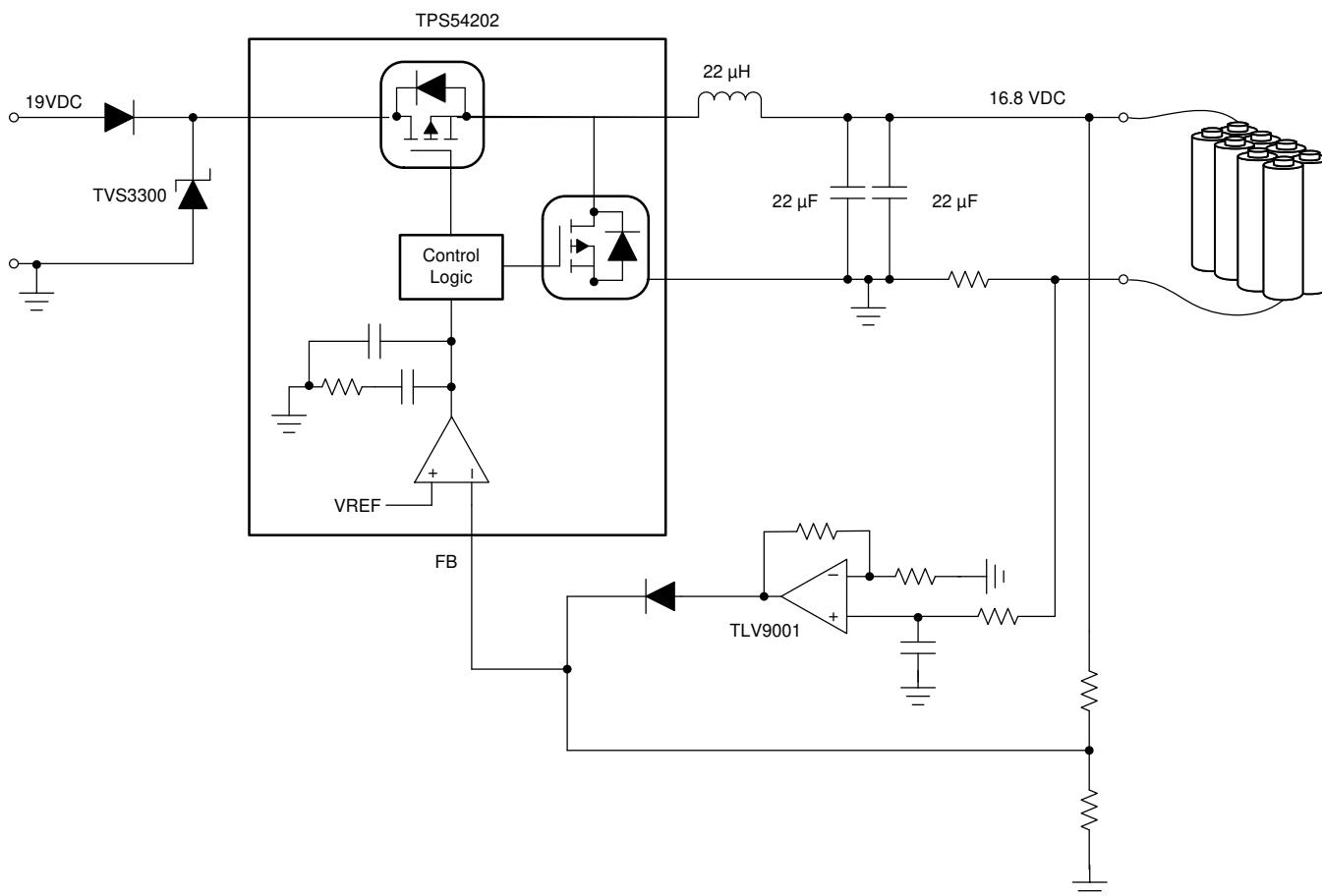

### 2.2 Design Considerations

This reference design attempts to optimize the system BOM cost and charge current capacity by trading-off the charge voltage accuracy, which affects the utilizable of the battery. This solution achieves a battery charger based on a synchronous buck converter - the TPS54202 device integrates two switching FETs, internal loop compensation, and employs the SOT-23 package achieving high power density and offering a small footprint on the PCB. The analog control eliminates the MCU resources and software workload, which is easier to implement and decreases the design cycle. This solution achieves a simple charging profile - constant voltage stage and constant current stage using the TLV9001 device which contributes high current-sensing accuracy.

## 2.3 Highlighted Products


The following subsections detail the highlighted products used in this reference design, including the key features for their selection. See their respective product data sheets for complete details on any highlighted device.

### 2.3.1 TPS54202

The TPS54202 is a 4.5-V to 28-V input voltage range, 2-A synchronous buck converter. The device includes two integrated switching FETs, internal loop compensation and 5-ms internal soft start to reduce component count. By integrating the MOSFETs and employing the SOT23 package, the TPS54202 device achieves the high power density and offers a small footprint on the PCB.

The device uses a fixed-frequency, peak current-mode control. The output voltage is compared through external resistors on the FB pin to an internal voltage reference by an error amplifier. An internal oscillator initiates the turn on of the high-side power switch. The error amplifier output is compared to the current of the high-side power switch. When the power-switch current reaches the error amplifier output voltage level, the high side power switch is turned off and the low-side power switch is turned on. The error amplifier output voltage increases and decreases as the output current increases and decreases. The device implements a current-limit by clamping the error amplifier voltage to a maximum level and also implements a minimum clamp for improved transient-response performance.

To reduce EMI, the TPS54202 device introduces frequency spread spectrum. The jittering span is  $\pm 6\%$  of the switching frequency with 1/512 swing frequency. The TPS54202H device is the verison without this EMI-friendly function.

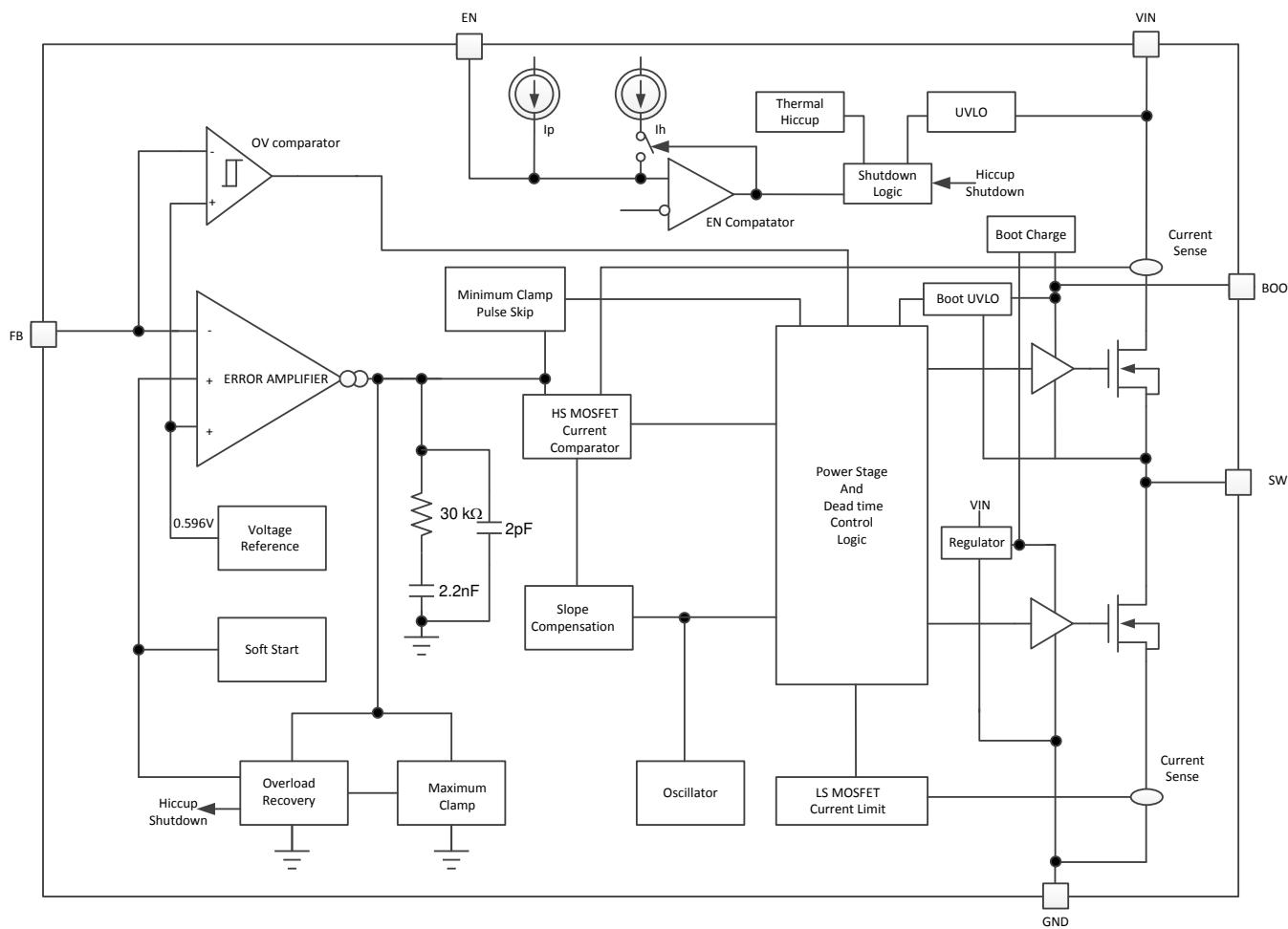**図 4. TPS54202 Functional Block Diagram**


Copyright © 2016, Texas Instruments Incorporated

### 2.3.2 TLV9001


The TLV9001 device is a single channel low-voltage operational amplifier (op amps) with rail-to-rail input and output swing capabilities. This op amp provides a cost-effective solution for space-constrained applications and high capacitive-load drive is required. The capacitive-load drive of the TLV900x family is 500 pF, and the resistive open loop output impedance makes stabilization easier with much higher capacitive loads.

The robust design of the TLV900x family simplifies circuit design. The op amps feature unity-gain stability, an integrated RFI and EMI rejection filter, and no-phase reversal in overdrive conditions.

### 2.3.3 TVS3300

The TVS3300 device robustly shunts up to 35 A of IEC 61000-4-5 fault current to protect systems from high power transients or lightning strikes. The device offers a solution to the common industrial signal line EMC requirement to survive up to 1 kV IEC 61000-4- 5 open circuit voltage coupled through a  $42\Omega$  impedance. The TVS3300 device uses a unique feedback mechanism to ensure precise flat clamping during a fault, assuring system exposure below 40 V. The tight voltage regulation allows designers to confidently select system components with a lower voltage tolerance, lowering system costs, and complexity without sacrificing robustness.

In addition, the TVS3300 device is available in small 1 mm × 1.1 mm WCSP and 2 mm × 2 mm SON footprints which are ideal for space-constrained applications, offering up to a 90 percent reduction in size compared to industry standard SMA and SMB packages. The extremely low device leakage and capacitance ensure a minimal effect on the protected line. To ensure robust protection over the lifetime of the product, TI tests the TVS3300 against 4000 repetitive surge strikes at high temperature with no shift in device performance.

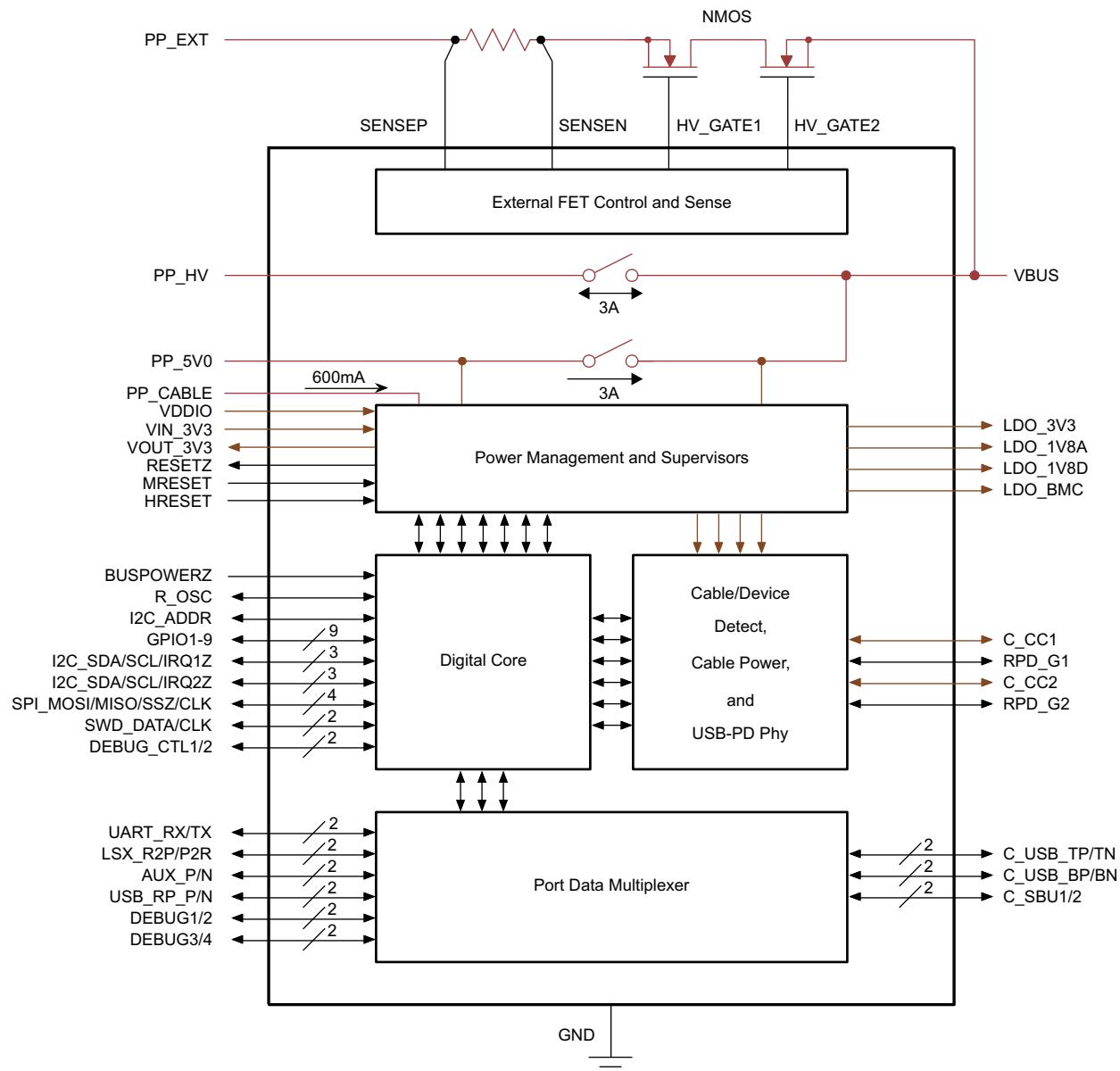**図 5. TVS3300 Functional Block Diagram**


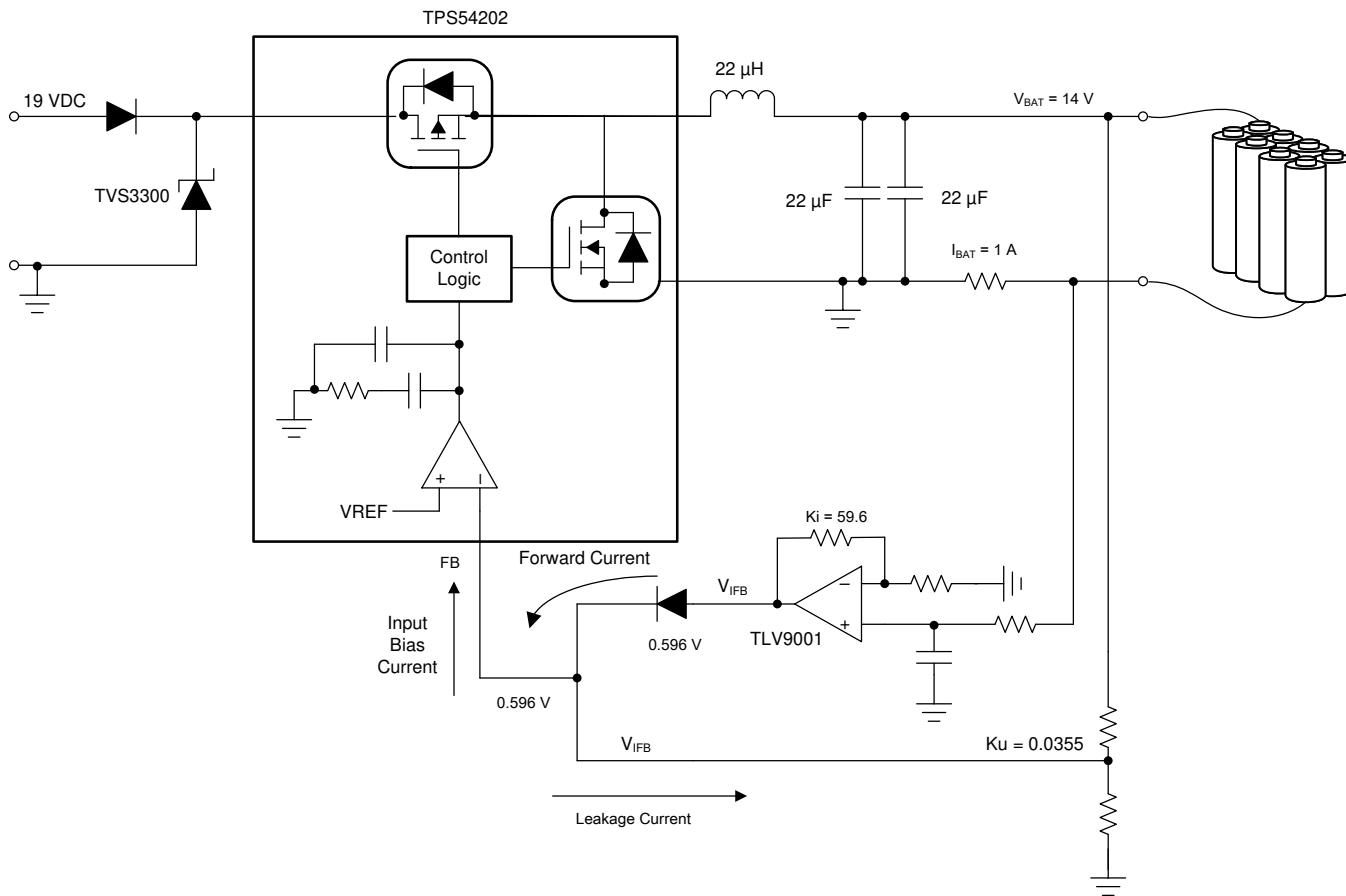
## 2.4 System Design Theory

To achieve the simplified charging profile, the battery charger should have both constant current (CC) control and constant voltage (CV) control. The TPS54202 device implements a constant-frequency, peak current mode control to improve line and load transients. The optimized internal compensation network minimizes the external component counts and simplified the constant voltage loop design.

### 2.4.1 Constant Current and Constant Voltage Control

A cost effective and simplified way to switching CV control and CC control is using one diode to achieve the OR logic function. 図 6 shows the block diagram of this implementation.

**図 6. Constant Current Control Design**



The symbols in 図 6 mean:

- $V_{IFB}$ : the output voltage of current-sensing circuit
- $V_{VFB}$ : the output voltage of voltage sensing circuit
- $K_i$  : the ratio or gain between  $V_{IFB}$  and charge current, the set point is 59.6
- $K_u$ : the ratio or gain between  $V_{VFB}$  and charge voltage, the set point is 0.0355

To better understanding the work theory of this circuit, one steady state is selected at a charge voltage of 14 V and charge current of 1 A. Thus, the related  $V_{IFB}$  is 0.596 V, and the related  $V_{VFB}$  should be 0.497 V, so the upper diode is ON, and the lower diode is OFF. According to Kirchhoff's current law (KCL), the forward current of the upper diode equals the input bias current plus leakage current of lower diode. As the input bias current is ultra low because of the high-impedance of the internal error amplifier, the dominate forward current is equal to the leakage current of the lower diode. Because the diodes should have stable forward voltage and ultra reverse current with low temperature drift, the signal Schottky barrier diode - BAT54 is selected in this design.

## 2.4.2 Current-Sensing Circuit

For the current-sensing circuit, a high-precision current sensor with low inductance and temperature coefficient is necessary. The CRM0805/1206-FX-R100ELF current-sense chip resistor is selected in this design, which has  $\pm 1\%$  tolerance,  $\pm 100 \text{ ppm}/^\circ\text{C}$  temperature coefficient, and  $> 1000\text{-M}\Omega$  insulation resistance.


This solution uses the single-supply, low-side, current-sensing solution and accurately detects load current up to 1 A, the gain required for the maximum linear output voltage depends on the required constant current value. 式 1 shows the association between gain and the target current value.

$$V_{\text{OUT}} = \frac{V_{\text{ref}} + V_{\text{fw}}}{\text{Gain}} + I_{\text{out}} \times R_{\text{shunt}} \quad (1)$$

In this solution, the target current is 0.95 A, the internal reference voltage is 0.596 V, and the forward voltage of the diodes is 0.02 V, thus the gain of this current-sensing circuit is set at 6.482.

図 7 shows the schematic of this current-sensing circuit. For more details on how to design a single-supply, low-side, unidirectional current-sensing circuit, see the [Single-supply, low-side, unidirectional current-sensing circuit](#) application report.

**図 7. Current-Sensing Circuit**

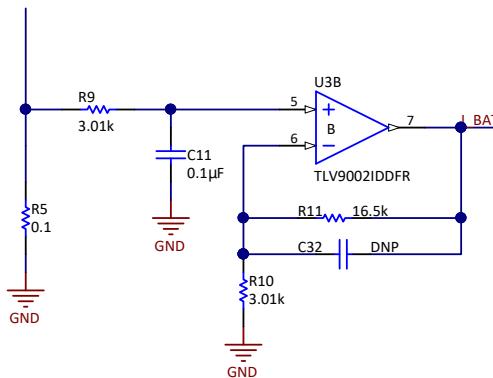


### 3 Hardware, Software, Testing Requirements, and Test Results

#### 3.1 Required Hardware

図 8 shows the overview of the PCB for the TIDA-010075 design, which features:

- Two-terminal input for power supply (J1): This pin is used to connect the DC supply from the pre-stage AC/DC output voltage.
- Two-terminal output for output voltage (J2): This pin is used as the output of this charger and to connect to the battery.
- Six-terminal connector (J3): The connector is used for the external communication interface, the pin definition from left to right is: EN, M<sub>DAC</sub>, I<sub>BAT</sub>, GND, V<sub>BAT</sub>, and V<sub>bBIAS</sub>. The EN pin is used for turning the TPS54202 device on and off, the M<sub>DAC</sub> pin is optional and is used to adjust the output voltage, the I<sub>BAT</sub> pin is the output of the current-sensing circuit, the V<sub>BAT</sub> is the output of voltage sensing circuit, and the V<sub>bBIAS</sub> is the power supply for the op amp.

図 8. TIDA-010075 Printed-Circuit Board

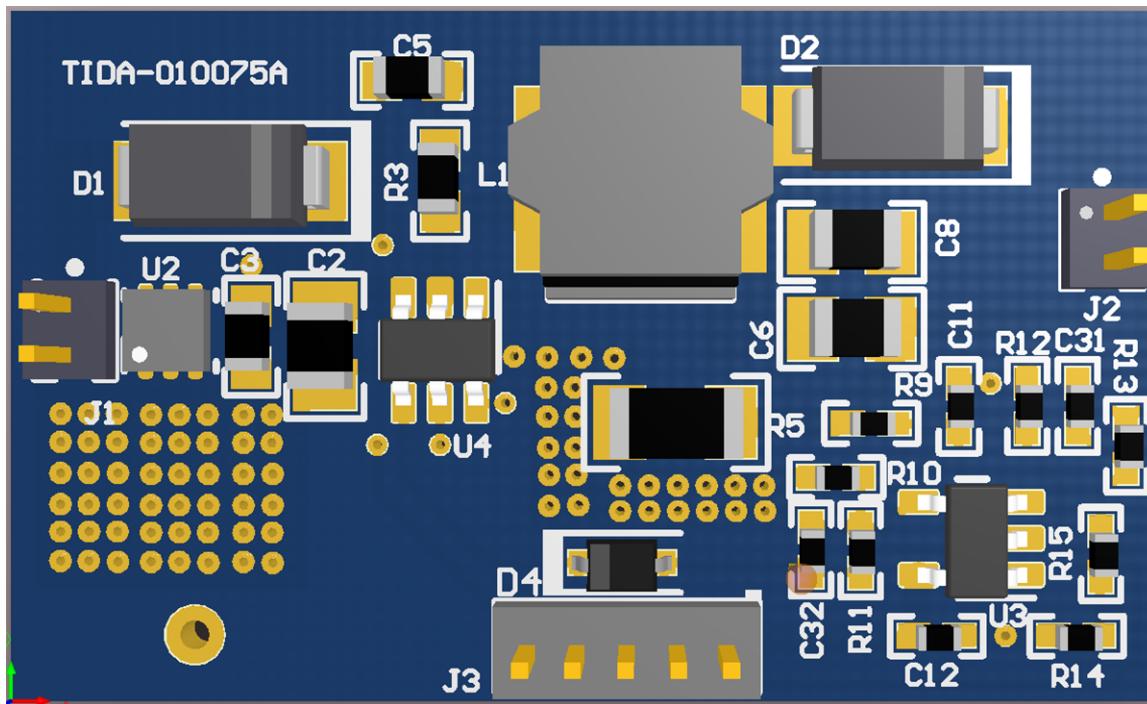

### **3.2 Testing and Results**

#### **3.2.1 Test Setup**

**表 2. Test Environment List**

| MATERIALS                     | USAGE                     | COMMENTS                |
|-------------------------------|---------------------------|-------------------------|
| DC Source                     | Power Supply              | 30-V, 2-A Power source  |
| DC Source                     | Power Supply              | 6-V, 1-A Power Source   |
| TIDA-010075 Board             | Battery charger board     | ----                    |
| Electronic Load               | Battery pack simulation   | CC, CV, CR mode         |
| Computer with PowerZ software | Collect the charging data | ----                    |
| 4S2P Li-Ion battery pack      | Load                      | With protection circuit |

The following steps show how to set up the test platform in the lab during the test:

1. Ensure the TIDA-010075 board has the right output voltage at no load
2. Connect the electronic load and choose the CV mode to test the constant output current
3. Connect the electronic load and choose the CC mode to test the constant output voltage

### 3.2.2 Test Results

#### 3.2.2.1 CV and CC Mode Steady State

図 9 shows the steady state of constant voltage (CV) mode and 図 10 shows the steady state of constant current (CC) mode. The blue curve (CH2) is the output voltage and the purple curve (CH3) is the switching frequency. The CV mode is tested at the following conditions: output voltage at 16.5 V and the output current at 0.5 A; the CC mode is tested at the following conditions: output voltage at 15 V and output current at 0.95 A.

図 9. CV Mode Steady State


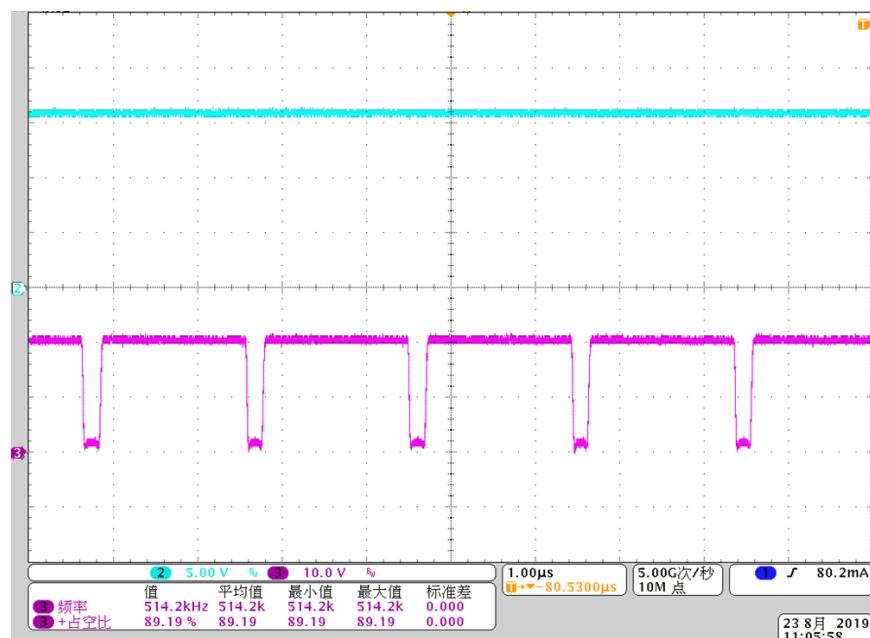



図 10. CC Mode Steady State

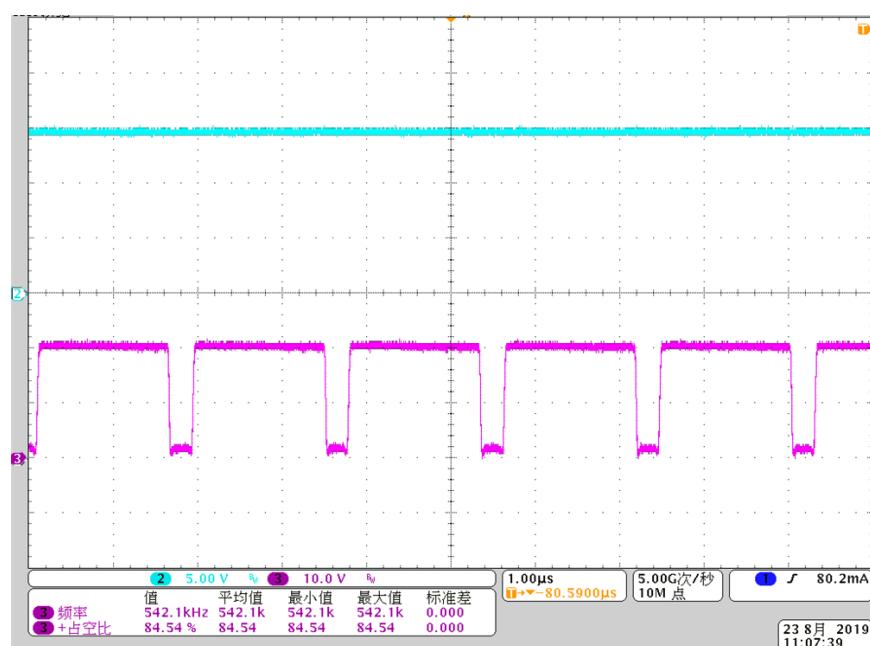


### 3.2.2.2 CV Voltage Ripple and CC Current Ripple

図 11 shows the voltage ripple of CV mode, and 図 12 shows the current ripple of CC mode. The output voltage ripple is less than  $\pm 3.8$  mV, which also means the voltage accuracy is less than  $\pm 0.0023\%$ . The output current ripple is tested by measuring the output voltage of the current-sensing circuit, the current ripple is less than  $\pm 12$  mA, which also means the current accuracy is less than  $\pm 1.2\%$ .

**図 11. CV Mode Voltage Ripple**

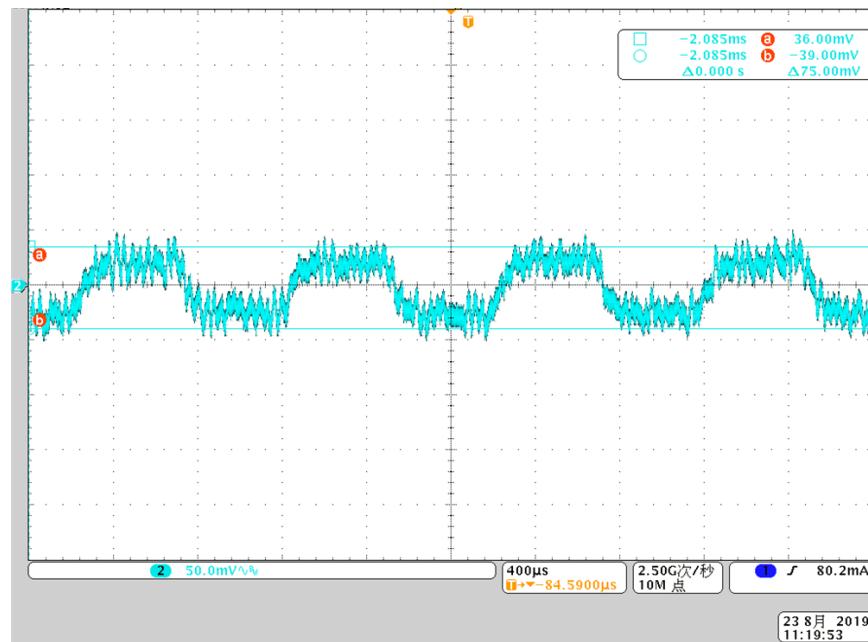

**図 12. CC Mode Current Ripple**

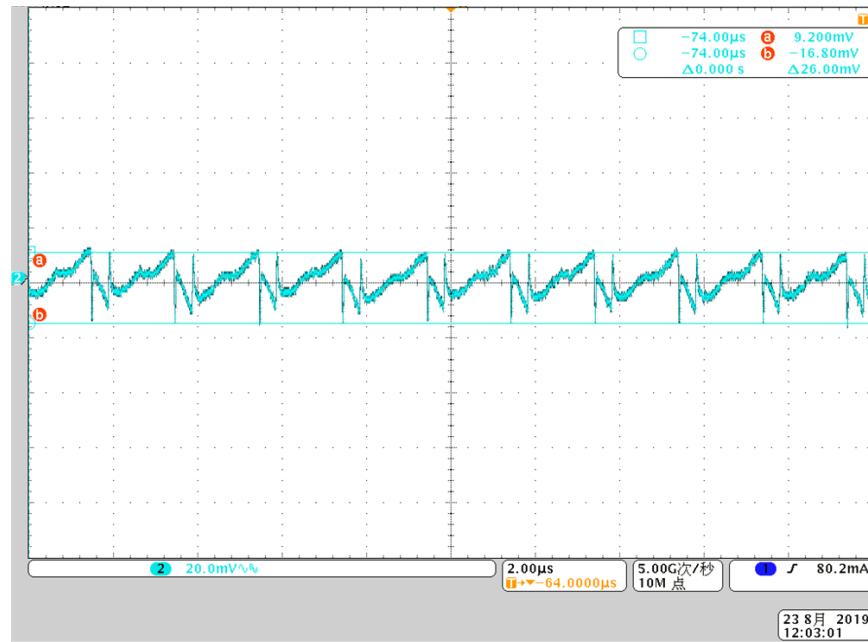

### 3.2.2.3 Efficiency Test


表 3 lists the test results of the efficiency of the battery charger across 0.1 A to 0.95 A.

**表 3. Efficiency Test Results**

| INPUT VOLTAGE (V) | INPUT DC CURRENT (A) | OUTPUT VOLTAGE (V) | OUTPUT DC CURRENT (A) | EFFICIENCY (%) |
|-------------------|----------------------|--------------------|-----------------------|----------------|
| 18.923            | 0.848                | 15.6               | 0.95                  | 92.36          |
| 18.933            | 0.834                | 16.225             | 0.9                   | 92.48          |
| 18.933            | 0.793                | 16.356             | 0.85                  | 92.60          |
| 18.929            | 0.747                | 16.389             | 0.8                   | 92.72          |
| 18.946            | 0.699                | 16.412             | 0.75                  | 92.95          |
| 18.938            | 0.652                | 16.418             | 0.7                   | 93.08          |
| 18.957            | 0.605                | 16.43              | 0.65                  | 93.12          |
| 18.948            | 0.558                | 16.442             | 0.6                   | 93.31          |
| 18.964            | 0.511                | 16.446             | 0.55                  | 93.34          |
| 18.959            | 0.465                | 16.462             | 0.5                   | 97.37          |
| 18.973            | 0.418                | 16.466             | 0.45                  | 93.43          |
| 18.969            | 0.372                | 16.478             | 0.4                   | 93.41          |
| 18.982            | 0.325                | 16.483             | 0.35                  | 93.51          |
| 18.982            | 0.279                | 16.496             | 0.3                   | 93.44          |
| 18.992            | 0.233                | 16.505             | 0.25                  | 93.25          |
| 18.992            | 0.188                | 16.515             | 0.2                   | 92.51          |
| 19.001            | 0.142                | 16.522             | 0.15                  | 91.85          |
| 19.003            | 0.097                | 16.534             | 0.1                   | 89.70          |

図 13 shows the efficiency curve of these test conditions.


**図 13. Efficiency Versus Output Current**

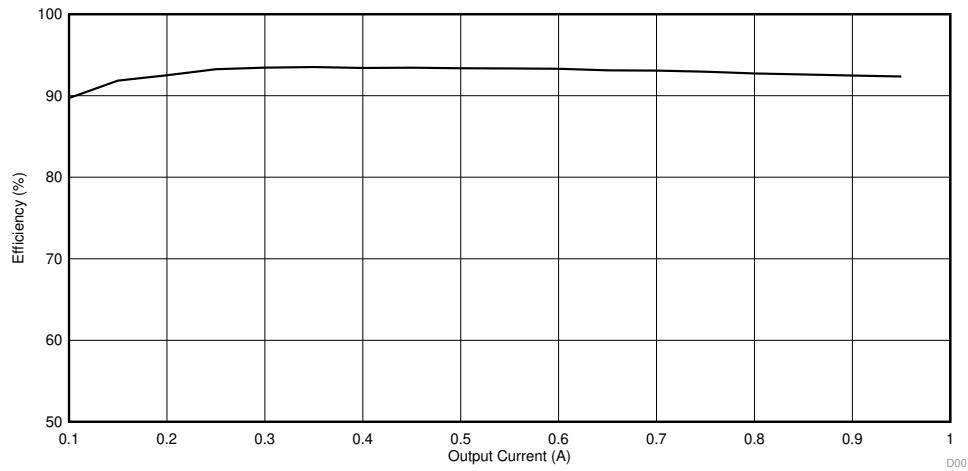

### 3.2.2.4 Thermal Test

図 14 shows the thermal image of the board after 10 minutes of continuous running. The maximum temperature observed on the TPS54202 device is 75.7°C, and the maximum temperature on the input reverse current protection diode is 80.6°C.

図 14. Thermal Test

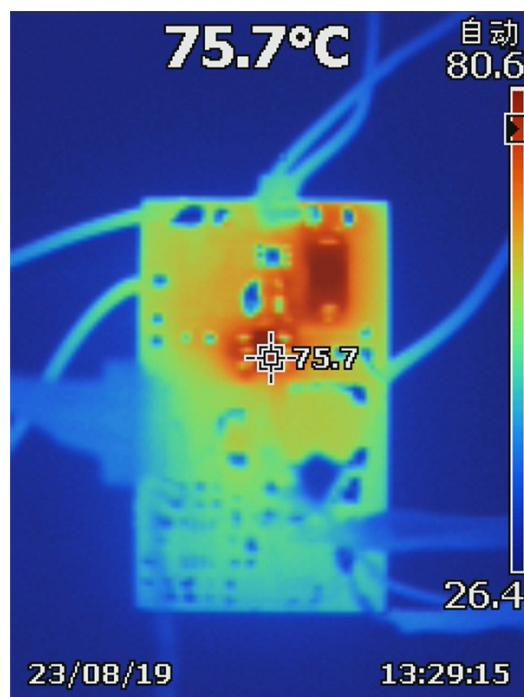

### 3.2.2.5 Voltage and Current Close Loop Stability

図 15 shows the voltage close loop stability performance of TIDA-010075 reference design, the gain crossover frequency is 19.68 kHz, and the phase margin is 65.045°, which means this control circuit is stable and can provide enough bandwidth.

図 15. Voltage Close Loop Stability


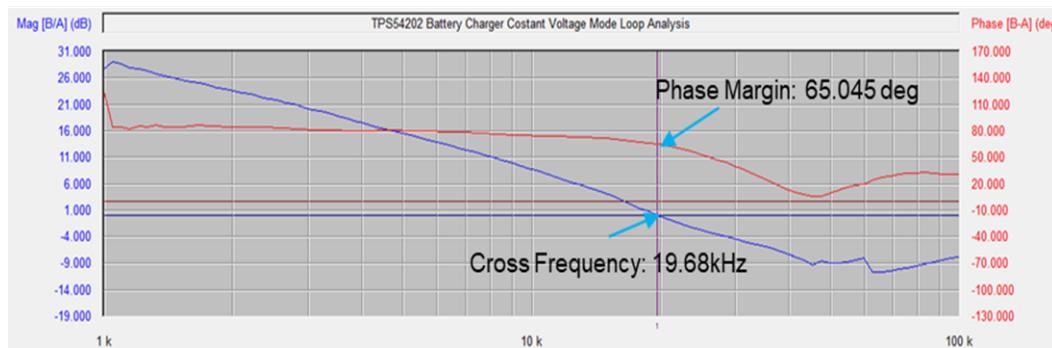


図 16 shows the current close loop stability performance of TIDA-010075 reference design, the gain crossover frequency is 15.28 kHz, and the phase margin is 51.886°, which means this control circuit is stable and can provide enough bandwidth.


図 16. Current Close Loop Stability

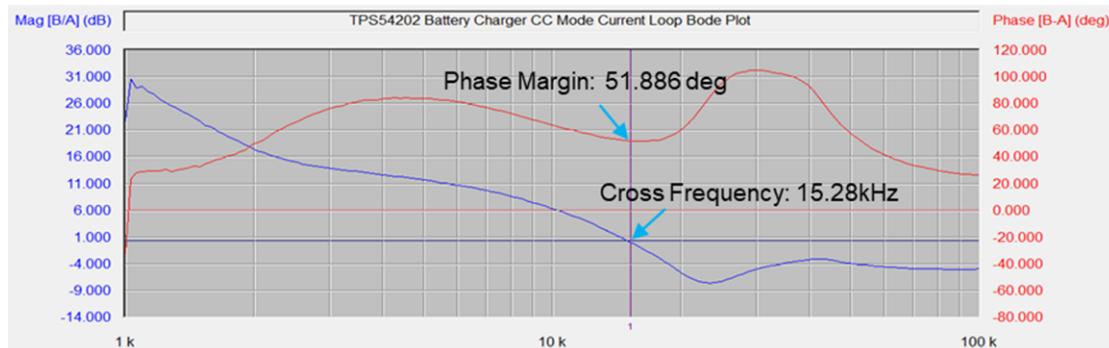

### 3.2.2.6 Charging Profile

図 17 shows the charging profile of this solution, the load is using a 4S2P battery pack with protection circuit.

図 17. Charging Profile

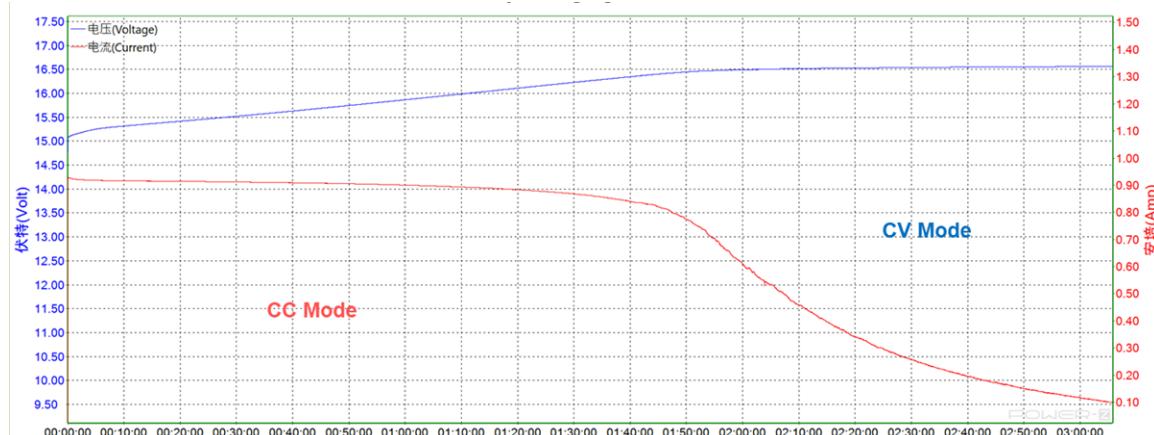

The charging profile consists of CV mode and CC mode, the transformation between CC to CV is smooth and stable.

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-010075](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-010075](#).

### 4.3 PCB Layout Recommendations

#### 4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-010075](#).

### 4.4 Altium Project

To download the Altium Designer® project files, see the design files at [TIDA-010075](#).

### 4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-010075](#).

### 4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-010075](#).

## 5 Software Files

To download the software files, see the design files at [TIDA-010075](#).

## 6 Related Documentation

1. Texas Instruments, [TPS54202 4.5-V to 28-V Input, 2-A Output, EMI Friendly Synchronous Step Down Converter Data Sheet](#)
2. Texas Instruments, [TLV900x Low-Power, RRIO, 1-MHz Operational Amplifier for Cost-Sensitive Systems Data Sheet](#)
3. Texas Instruments, [TVS3300 33-V Flat-Clamp Surge Protection Device Data Sheet](#)
4. Texas Instruments, [Single-supply, low-side, unidirectional current-sensing circuit application report](#)
5. Texas Instruments, [Difference amplifier \(subtractor\) circuit application report](#)

### 6.1 商標

E2E is a trademark of Texas Instruments.

Altium Designer is a registered trademark of Altium LLC or its affiliated companies.

すべての商標および登録商標はそれぞれの所有者に帰属します。

### 6.2 Third-Party Products Disclaimer

TI'S PUBLICATION OF INFORMATION REGARDING THIRD-PARTY PRODUCTS OR SERVICES DOES NOT CONSTITUTE AN ENDORSEMENT REGARDING THE SUITABILITY OF SUCH PRODUCTS OR SERVICES OR A WARRANTY, REPRESENTATION OR ENDORSEMENT OF SUCH PRODUCTS OR SERVICES, EITHER ALONE OR IN COMBINATION WITH ANY TI PRODUCT OR SERVICE.

## 7 About the Author

**ZHILONG (BRYAN) LIU** is a system engineer at Texas Instruments, responsible for developing subsystem design solutions for the industrial appliances systems. He has system-level product experience in analog and mixed-signal designs. Bryan earned his Bachelor of Technology in electrical and information engineering from Xidian University, and his Master of Technology in circuit and system from Xidian University.

## 重要なお知らせと免責事項

TIは、技術データと信頼性データ(データシートを含みます)、設計リソース(リファレンス・デザインを含みます)、アプリケーションや設計に関する各種アドバイス、Webツール、安全性情報、その他のリソースを、欠陥が存在する可能性のある「現状のまま」提供しており、商品性および特定目的に対する適合性の默示保証、第三者の知的財産権の非侵害保証を含むいかなる保証も、明示的または默示的にかかわらず拒否します。

これらのリソースは、TI製品を使用する設計の経験を積んだ開発者への提供を意図したもので、(1)お客様のアプリケーションに適したTI製品の選定、(2)お客様のアプリケーションの設計、検証、試験、(3)お客様のアプリケーションに該当する各種規格や、その他のあらゆる安全性、セキュリティ、規制、または他の要件への確実な適合に関する責任を、お客様のみが単独で負うものとします。

上記の各種リソースは、予告なく変更される可能性があります。これらのリソースは、リソースで説明されているTI製品を使用するアプリケーションの開発の目的でのみ、TIはその使用をお客様に許諾します。これらのリソースに関して、他の目的で複製することや掲載することは禁止されています。TIや第三者の知的財産権のライセンスが付与されている訳ではありません。お客様は、これらのリソースを自身で使用した結果発生するあらゆる申し立て、損害、費用、損失、責任について、TIおよびその代理人を完全に補償するものとし、TIは一切の責任を拒否します。

TIの製品は、[TIの販売条件](#)、または[ti.com](http://ti.com) やかかる TI 製品の関連資料などのいずれかを通じて提供する適用可能な条項の下で提供されています。TIがこれらのリソースを提供することは、適用される TI の保証または他の保証の放棄の拡大や変更を意味するものではありません。

お客様がいかなる追加条項または代替条項を提案した場合でも、TIはそれらに異議を唱え、拒否します。

郵送先住所 : Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2022, Texas Instruments Incorporated