

Design Guide: TIDA-050056

12Vin、3.3Vout、1A の高出力密度降圧コンバータのリファレンス・デザイン



概要

TIDA-050056 は、5V~17V の入力電圧を受け入れる降圧コンバータのリファレンス・デザインであり、設計スペースが非常に限られているアプリケーションを想定しています。TPS629210-Q1 降圧コンバータを採用したこのリファレンス・デザインは、入力電圧を 3.3V 出力に降圧し、高効率かつ低静止電流で最大 1A の負荷に電力供給できます。このデザインに使用されているインダクタは、DCR (直流抵抗) が約 138mΩ の 1.5μH インダクタです。すべての外部部品を含むソリューション全体のサイズは 20mm² です。このデザインは、業界最小の動作時静止電流 (I_Q) で高効率の DC/DC 変換と小型のソリューション・サイズを実現します。同じデザインを、TPS629210-Q1 とピン互換である TPS629210 デバイスにも適用できます。

Resources

[TIDA-050056](#)

Design Folder

[TPS629210-Q1](#)

Product Folder


[TPS629210](#)

Product Folder



Ask our TI E2E™ support experts

Design Images

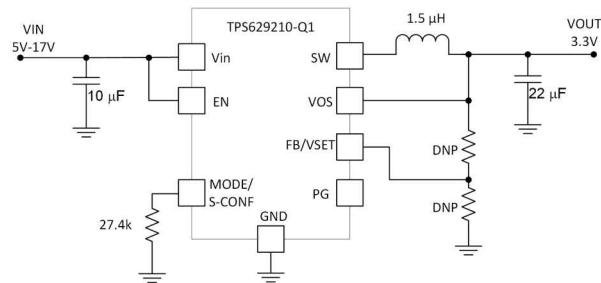

1 System Description

The TIDA-050056 is designed by using the TPS629210-Q1 high efficiency and low I_Q DC/DC Buck converter. The design is optimized for small total solution size, low BOM count, high efficiency, best thermal performance and lowest quiescent current possible. TPS629210-Q1 allows high switching frequency that enables small component selection without compromising on efficiency. The internal feedback (VSET) feature eliminates need of external feedback resistors. Small size and less pin count reduces external component counts. This design is ideal for applications where space is limited such as smart lock, wearable devices and so on. The efficiency and low I_Q are ideal for battery operating systems. The design allows to efficiently use the battery power and extend its life time.

表 1-1. Key System Specifications

Parameter	Min	Typ	Max	Unit
Input Voltage	5	12	17	V
Output Voltage	3.267	3.3	3.333	V
Output Current	0		1	A
Switching Frequency		2.5		MHz
Operating Quiescent Current		4		μ A
Junction Temperature	-40		150	°C
Output Discharge		Enabled		

2 System Overview

2.1 Block Diagram

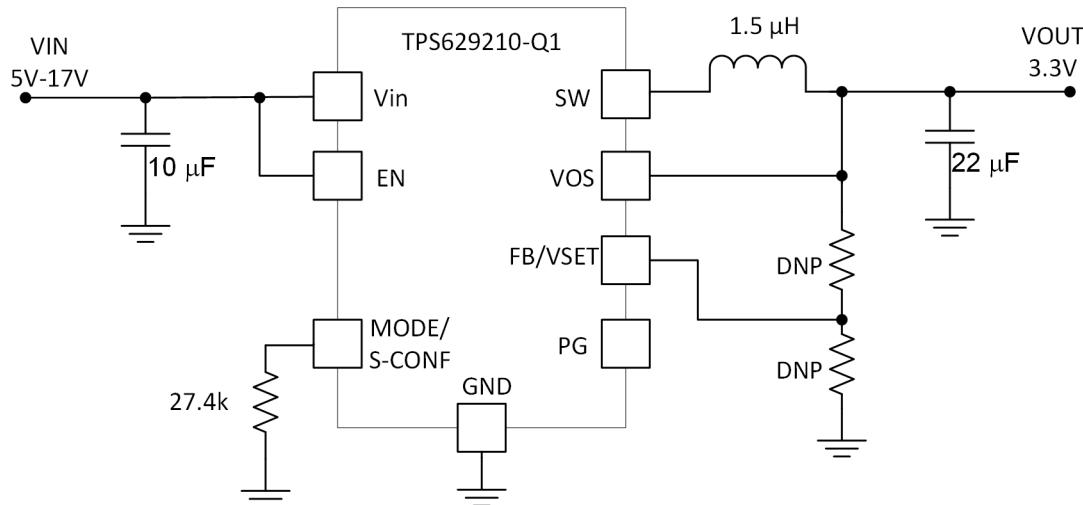


図 2-1. TIDA-050056 Block Diagram

2.2 Design Considerations

By connecting 27.4-k Ω resistor on MODE/S-CONF pin, the device is configured to:

- **VSET operation:** VOUT is sensed only through the VOS pin by an internal resistor divider. The target output voltage is programmed by an external resistor connected between the FB/VSET pin and GND. In this design, FB/VSET pin is floating and thus the VOUT is programmed to 3.3-V
- **2.5-MHz Switching Frequency with AEE (Automatic Efficiency Enhancement):** The MODE/S-CONF pin is configured to AEE mode which provides efficiency enhancement over the entire input voltage and output voltage range by automatically adjusting the switching frequency of the converter. The efficiency decreases if VOUT decreases, VIN increases, or both. To keep the efficiency high over the entire duty cycle range (VOUT/VIN ratio), the switching frequency is adjusted while maintaining the ripple current. The AEE feature provides an efficiency enhancement for various duty cycle, especially for lower VOUT values where fixed frequency converters suffer from a significant efficiency drop. Furthermore, this feature compensates for the very small duty cycle of high VIN to low VOUT conversion, which limits the control range in other topology.
- **Power Save Mode Operation(Auto PFM/PWM):** The MODE/S-CONF pin is configured for power save mode(Auto PFM/PWM). The device operates in PWM mode as long as the output current is higher than half of the ripple current of the inductor. To maintain high efficiency at light loads, the device enters power save mode at the boundary to discontinuous conduction mode (DCM). This happens if the output current becomes smaller than half of the ripple current of the inductor. The power save mode is entered seamlessly when the load current decreases. This ensures a high efficiency in light load operation. The device remains in power save mode as long as the inductor current is discontinuous. In power save mode, the switching frequency decreases linearly with the load current maintaining high efficiency. The transition in and out of power save mode is seamless in both directions.
- **Output Discharge Function Enabled:** The output discharge function is enabled to ensure a defined down-ramp of the output voltage when the device is being disabled but also to keep the output voltage close to 0-V when the device is off. The output discharge feature is only active once TPS629210-Q1 have been enabled at least once since the supply voltage is applied.

2.3 Highlighted Features

The TPS629210-Q1 is a high efficiency, small and flexible synchronous step-down DC/DC converter that is easy to use. A selectable switching frequency of 2.5-MHz or 1.0-MHz allows the use of small inductors and provides fast transient response. The device supports high output voltage accuracy of -1.5% and +1.1% across temperature range (-40°C to 150°C) using VSET feature. The wide input voltage of 3-V to 17-V supports a variety of nominal inputs, like 12-V supply rails, single-cell or multi-cell Li-Ion, and 5-V or 3.3-V rails.

The TPS629210-Q1 provides a MODE/S-CONF input to set the internal/external feedback, switching frequency, output voltage discharge and auto PFM/PWM or forced PWM operation. To maintain high efficiency at light load, auto PFM/PWM should be selected. Additionally, to provide high efficiency at very small load, the device has a low typical quiescent current of 4- μ A. If enabled AEE mode, the device provides automatic efficiency enhancement across VIN, VOUT and load current. The device is available in small 8-pin SOT583 package.

2.4 System Design Theory

The TPS629210-Q1 is optimized to work within a range of external components. The LC output filters inductance and capacitance have to be considered together, creating a double pole, responsible for the corner frequency of the converter. See the [TPS629210-Q1](#) data sheet for more details.

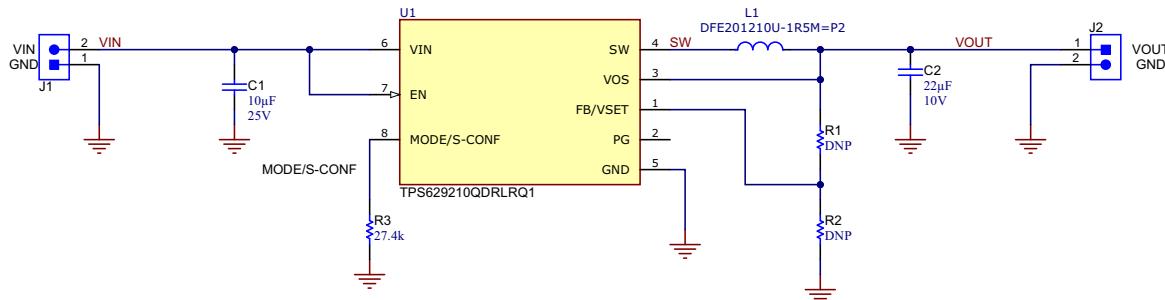


图 2-2. Buck Converter Circuit Design Using TPS629210-Q1

The TIDA-050056 is designed with a nominal 1.5- μ H inductor to support 3.3-V output voltage. A shielded wire-wound inductor from Murata (DFE201210U-1R5=P2) is used in this design. It has 2.5-A saturation current and 138-m Ω maximum DCR. 1.5- μ H inductance is ideal for size and ripple given the VOUT of this 3.3-V design. The larger values can be used to achieve a lower inductor ripple current but they can have a negative impact on efficiency and transient response. Small values that 1.5- μ H will cause a larger inductor ripple current which causes a larger negative inductor current in forced PWM mode at low or no output current.

A small low equivalent series resistance(ESR) multilayer ceramic capacitor(MLCC) is recommended to obtain the best filtering. For this design, a 10- μ F /25-V multilayer ceramic chip capacitor from Murata (GRM188R61E106MA73L) is used as an input capacitor. It is designed to withstand up to 25-V which is enough for input voltage range that we want to cover in this design.

For the output capacitor, the voltage rating is much smaller than the input, only 6-V to 10-V capacitor rating is needed. A 22- μ F/10-V multilayer ceramic chip capacitor from Murata(GRM188R61A226ME15D) is chosen.

The MODE/S-CONF requires an E96 resistor series, 1% accuracy, temperature coefficient better or equal than ± 200 -ppm/ $^{\circ}$ C. A small size 0402 package (CRCW040227K4FKED) from Vishay is used in this design.

3 Hardware Requirements, Test Setup, and Test Results

3.1 Hardware Requirements

For testing purposes, this reference design requires the following equipment:

- A power supply that is capable of supplying at least 1-A of current and up to 20-V.
- Current and voltage multimeters to measure the currents and voltages during the related tests.
- The TIDA-050056 board is a printed circuit board(PCB) with all the components in this design.
- Resistive load and electronic load that are capable at least 1-A.
- Thermal camera used to measure the thermal rise of the board during operation.
- Oscilloscope to capture voltage and current waveforms.

3.2 Test Setup

図 3-1 shows test setup for TIDA-050056.

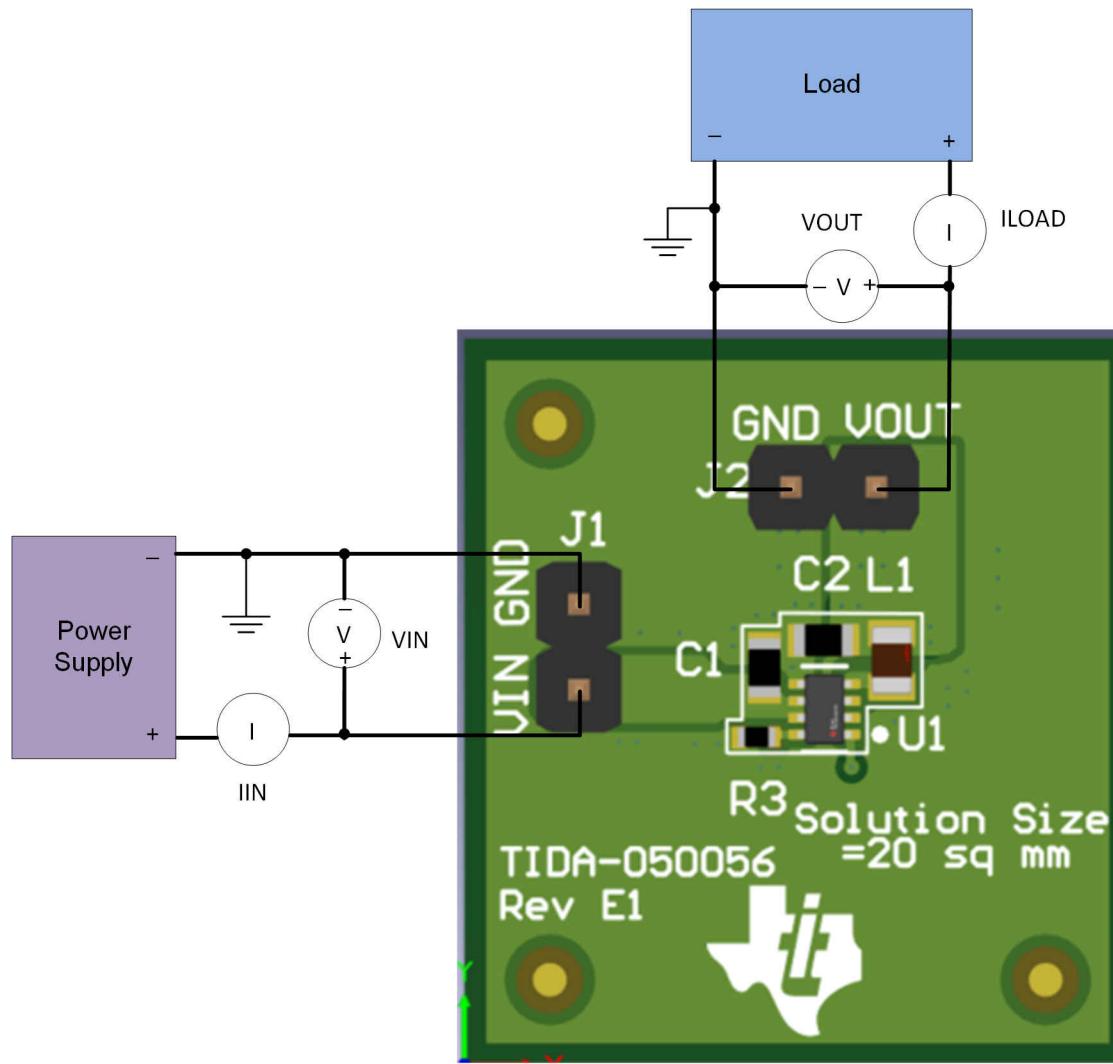


図 3-1. Test Setup

3.3 Test Results

This section provides the test results of TIDA-050056.

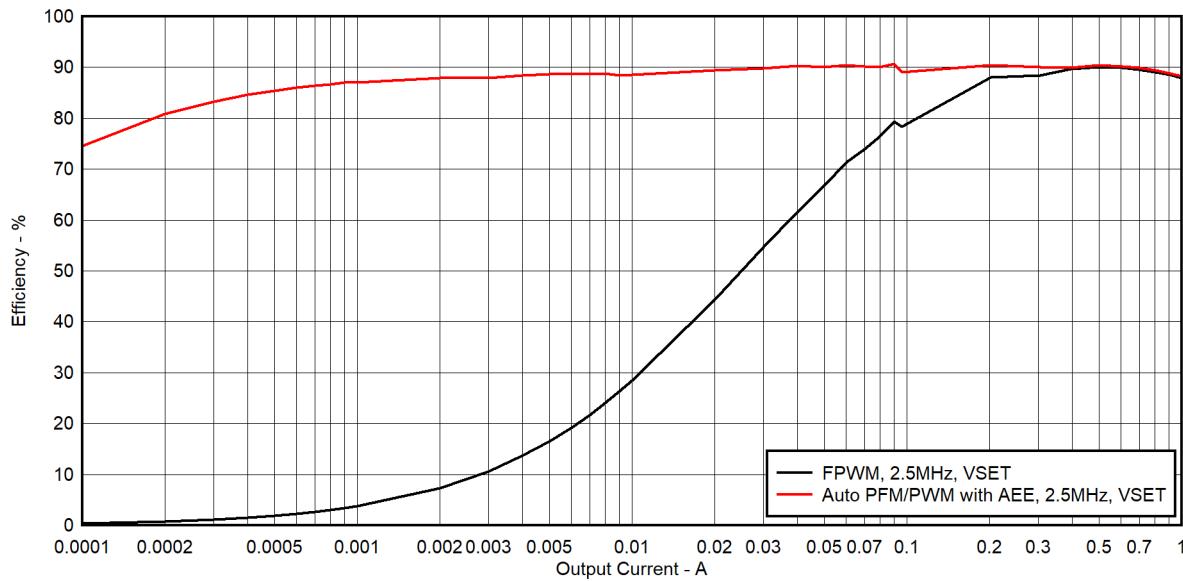


図 3-2. Efficiency $V_{IN}=12\text{-V}$, $V_{OUT}=3.3\text{-V}$, $F_{SW}=2.5\text{-MHz}$, VSET

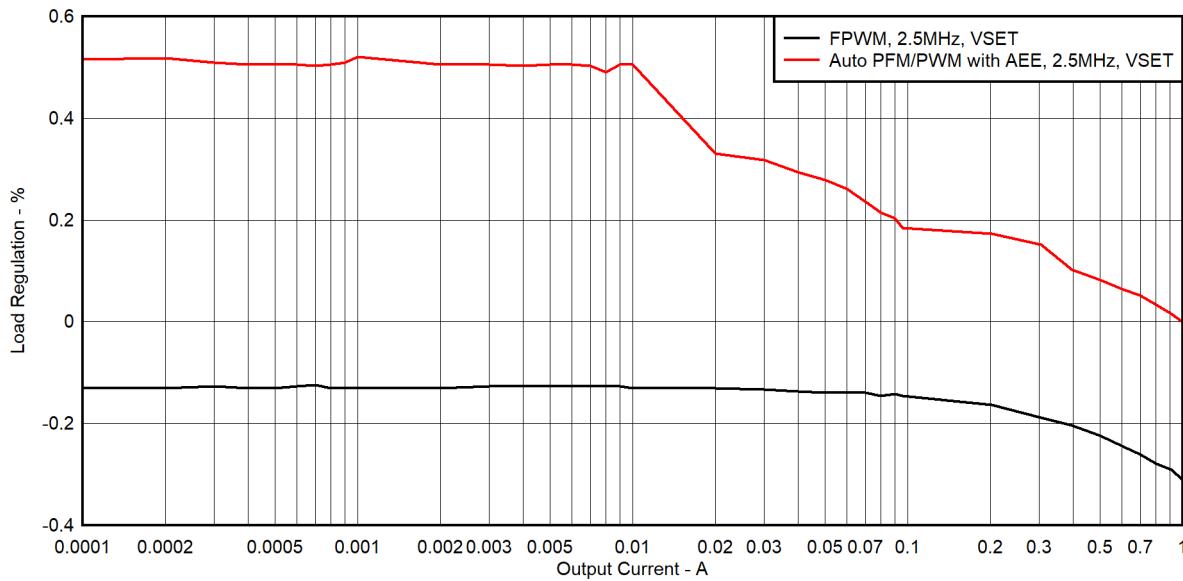


図 3-3. Load Regulation $V_{IN}=12\text{-V}$, $V_{OUT}=3.3\text{-V}$, $F_{SW}=2.5\text{-MHz}$, VSET

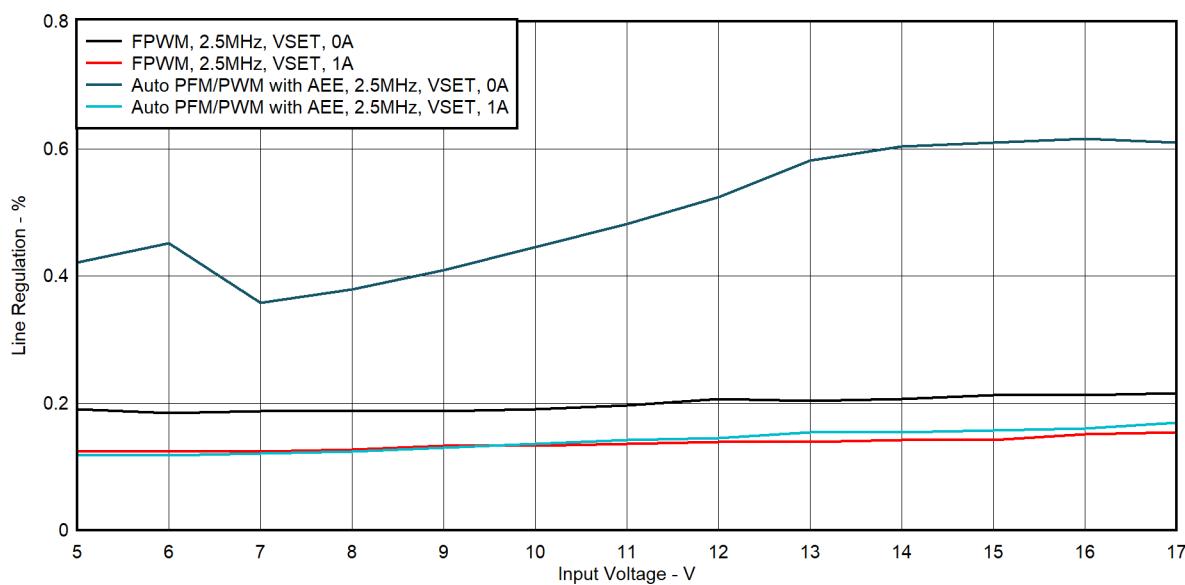


図 3-4. Line Regulation $V_{IN}=5\text{-V}$ to 17-V , $I_{OUT}=0\text{-A}$ and 1-A , $F_{SW}=2.5\text{-MHz}$, $VSET$

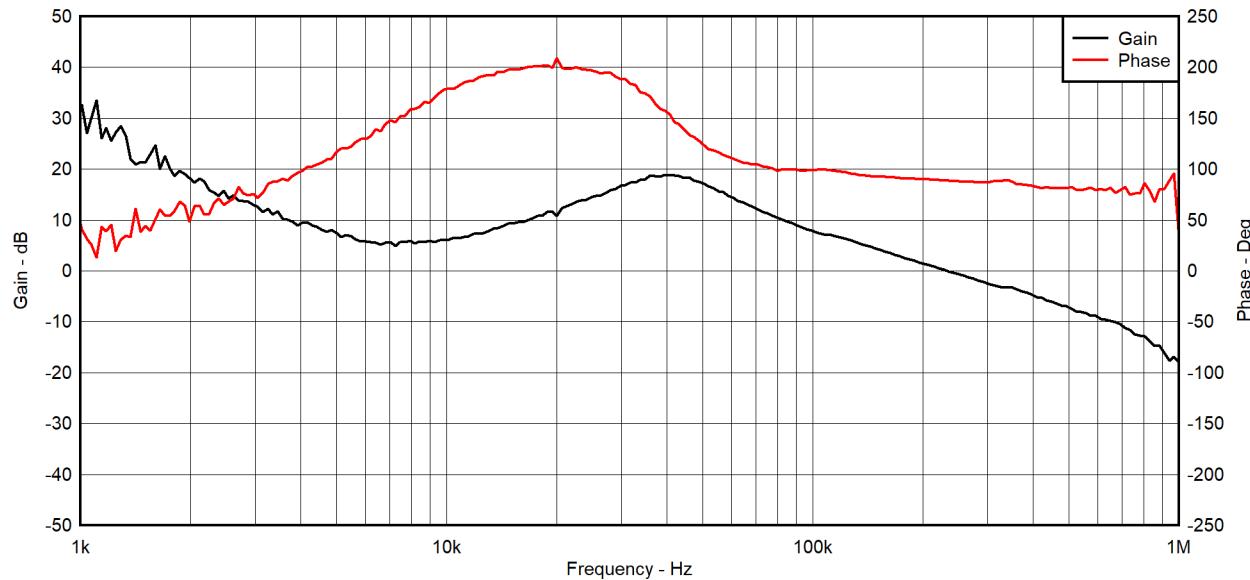


図 3-5. Loop Response Auto PFM/PWM with AEE, $VSET$, $V_{IN}=12\text{-V}$, $V_{OUT}=3.3\text{-V}$, $I_{OUT}=1\text{-A}$

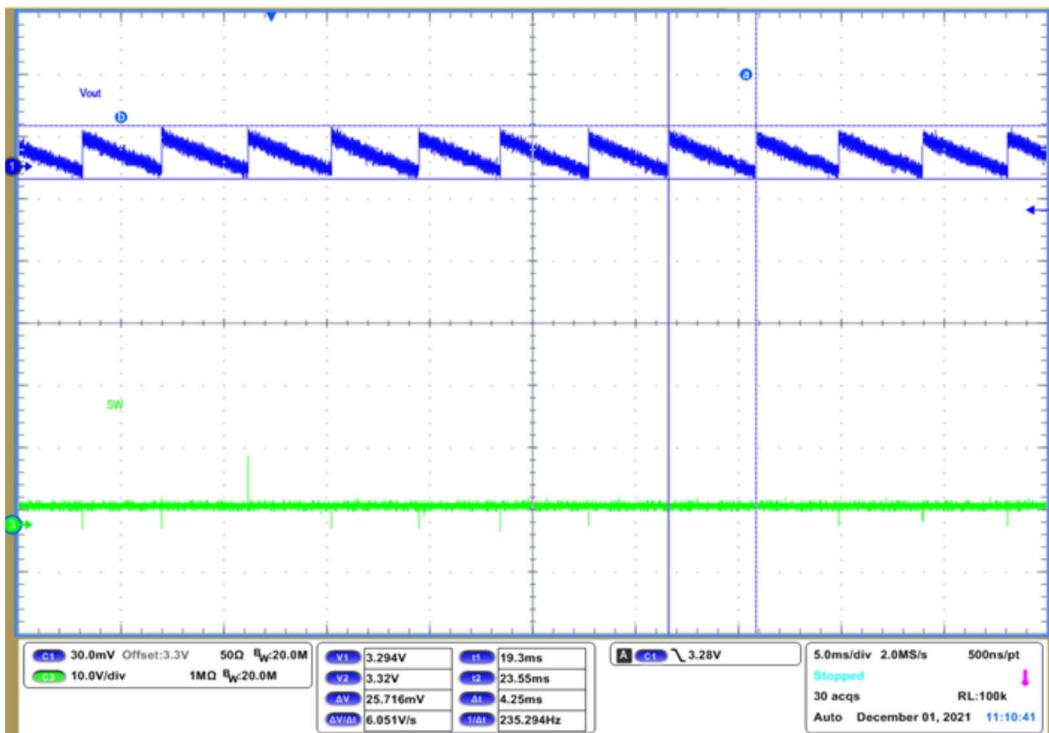


図 3-6. Output Voltage Ripple Auto PFM/PWM, $V_{IN}=12\text{-V}$, $V_{OUT}=3.3\text{-V}$, $I_{OUT}=0\text{-A}$

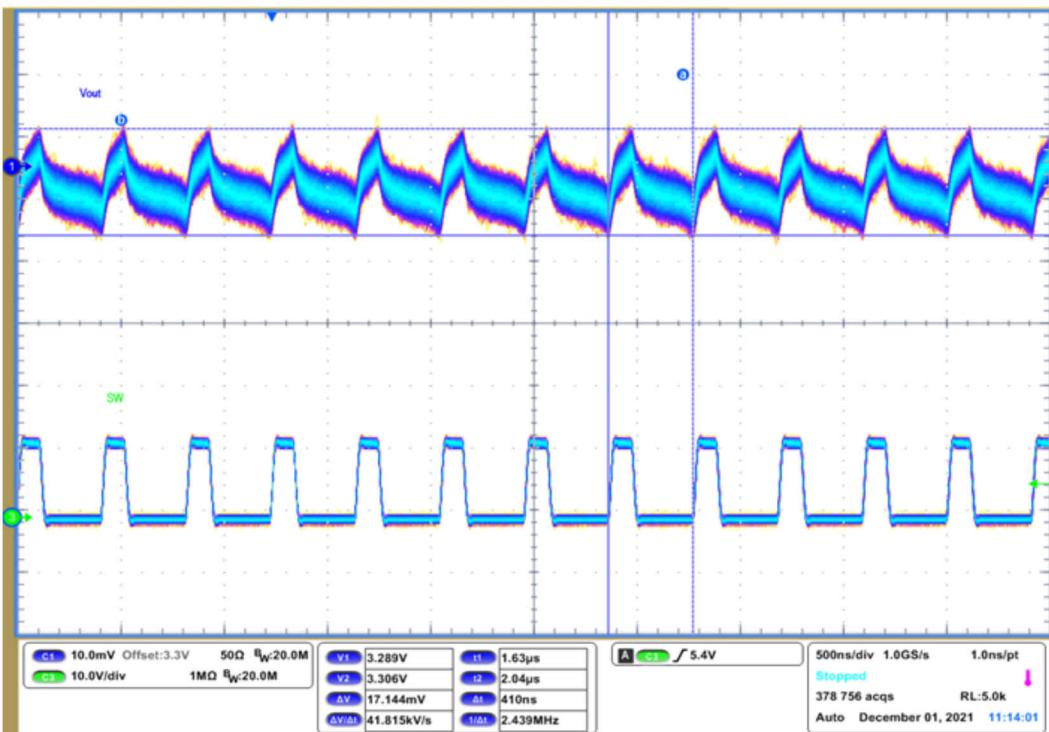


図 3-7. Output Voltage Ripple Auto PFM/PWM, $V_{IN}=12\text{-V}$, $V_{OUT}=3.3\text{-V}$, $I_{OUT}=1\text{-A}$

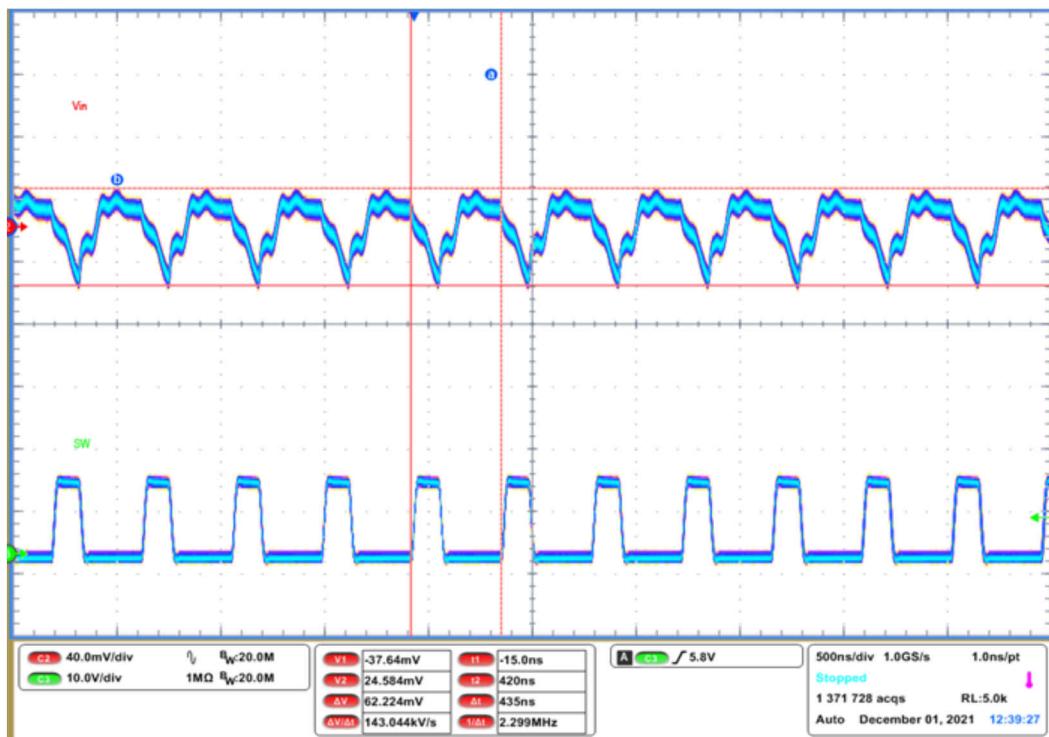


図 3-8. Input Voltage Ripple Auto PFM/PWM, $V_{IN}=12\text{-V}$, $V_{OUT}=3.3\text{-V}$, $I_{OUT}=1\text{-A}$

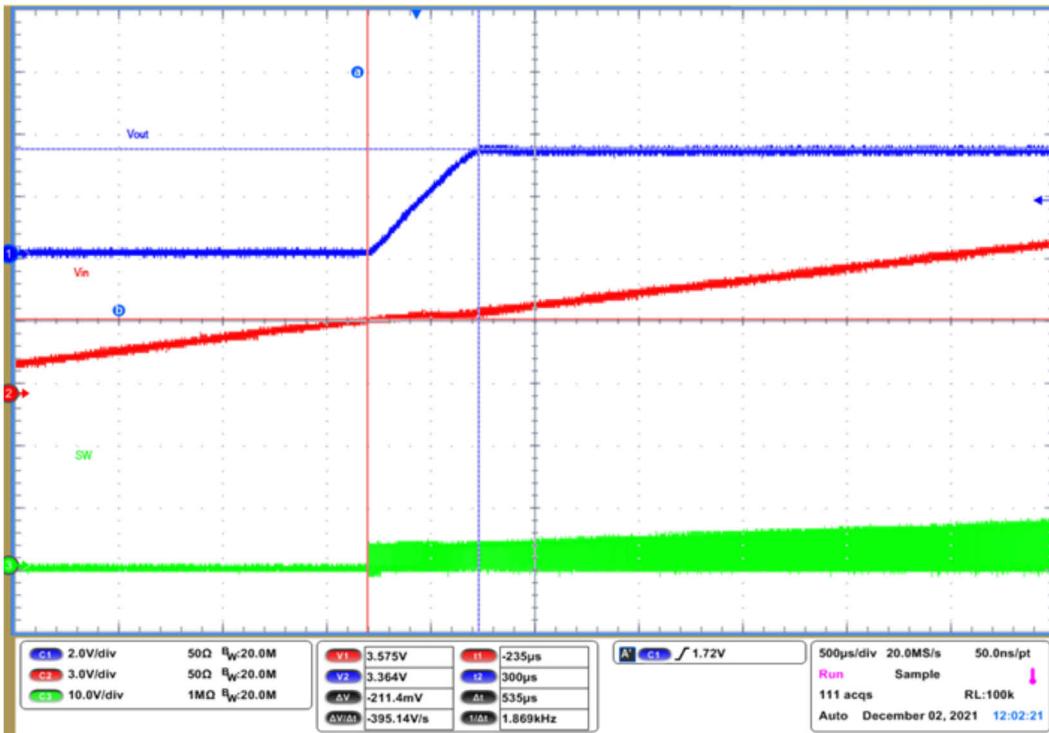


図 3-9. Start up Auto PFM/PWM with AEE, $V_{IN}=12\text{-V}$, $V_{OUT}=3.3\text{-V}$, $I_{OUT}=1\text{-A}$

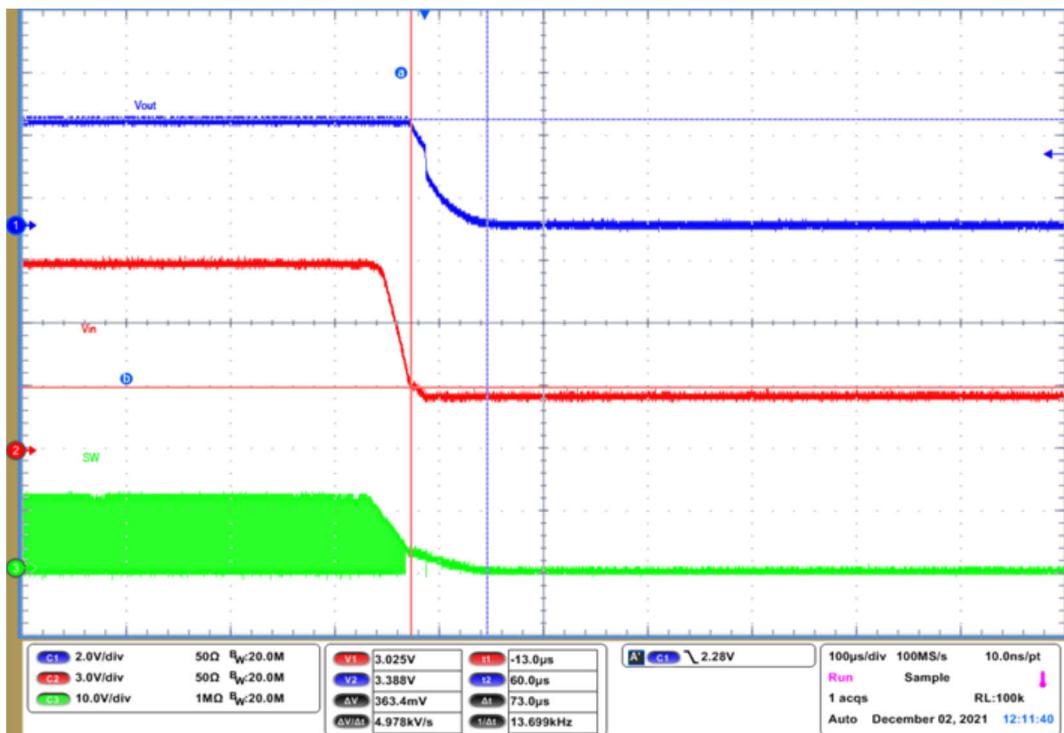


図 3-10. Shut down Auto PFM/PWM with AEE, $V_{IN}=12\text{-V}$, $V_{OUT}=3.3\text{-V}$, $I_{OUT}=1\text{-A}$

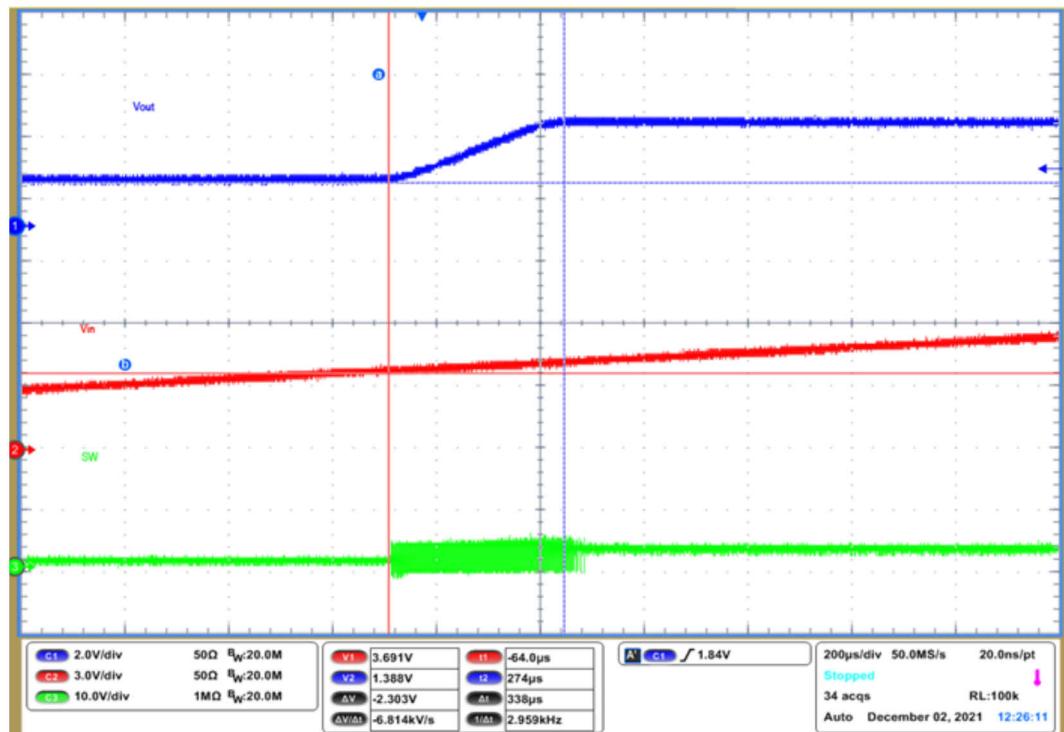


図 3-11. Pre-bias start up Auto PFM/PWM, $V_{IN}=12\text{-V}$, $V_{OUT}=3.3\text{-V}$, $I_{OUT}=0\text{-A}$

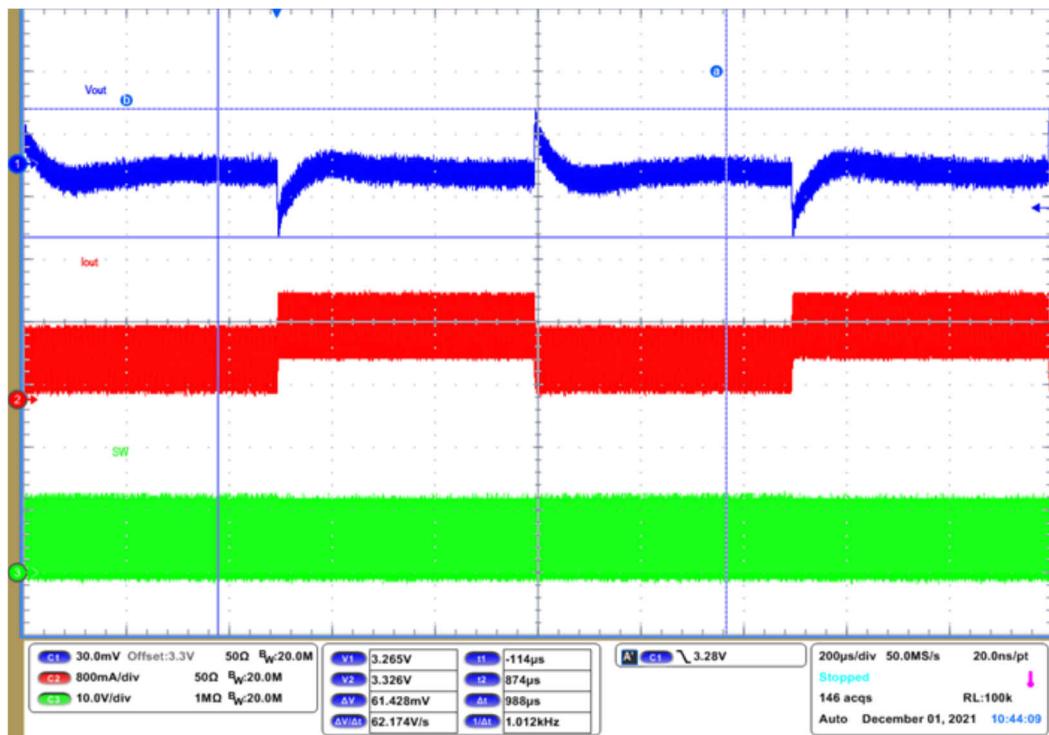


図 3-12. Load Transient Auto PFM/PWM, $V_{IN}=12\text{-V}$, $V_{OUT}=3.3\text{-V}$, $I_{OUT}=0.5\text{-A}$ to 1-A , Slew rate= $1\text{-A}/\mu\text{s}$

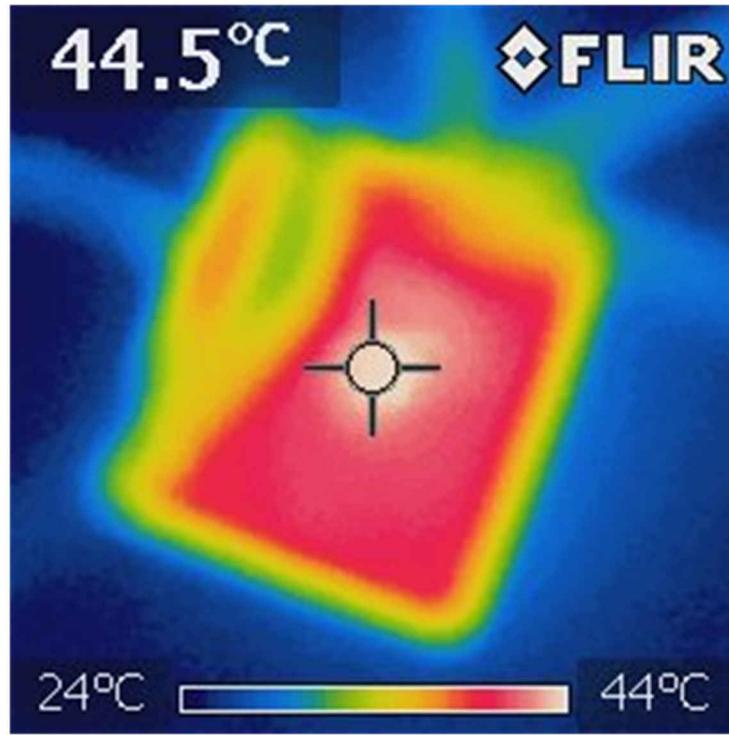


図 3-13. Thermal Image Auto PFM/PWM, $V_{IN}=12\text{-V}$, $V_{OUT}=3.3\text{-V}$, $I_{OUT}=1\text{-A}$

4 Design and Documentation Support

4.1 Design Files

4.1.1 Schematics

To download the schematics, see the design files at [TIDA-050056](#).

4.1.2 BOM

To download the bill of materials (BOM), see the design files at [TIDA-050056](#).

4.1.3 PCB Layout Recommendations

4.1.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-050056](#).

4.1.4 Altium Projects

To download the Altium Designer project files, see the design files at [TIDA-050056](#).

4.1.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-50056](#).

4.1.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-050056](#).

4.2 Documentation Support

1. Texas Instruments, [TPS629210-Q1 3-V to 17-V, 1-A Low \$I_Q\$ Converter in a SOT583 Package](#) data sheet.
2. Texas Instruments, [TPS629210 3-V to 17-V1-A, Low \$I_Q\$ Buck Converter in SOT583 Package](#) data sheet.

4.3 サポート・リソース

[TI E2E™ サポート・フォーラム](#)は、エンジニアが検証済みの回答と設計に関するヒントをエキスパートから迅速かつ直接得ることができる場所です。既存の回答を検索したり、独自の質問をしたりすることで、設計で必要な支援を迅速に得ることができます。

リンクされているコンテンツは、該当する貢献者により、現状のまま提供されるものです。これらは TI の仕様を構成するものではなく、必ずしも TI の見解を反映したものではありません。TI の使用条件を参照してください。

4.4 Trademarks

TI E2E™ and DCS-Control™, and are trademarks of Texas Instruments.

すべての商標は、それぞれの所有者に帰属します。

5 About the Author

Matthew Murdock is System Engineer at Texas Instruments for over a decade responsible for defining new products and technology platforms based on our marketing strategy and business opportunities.

Nancy Zhang is Application Engineer at Texas Instruments for over a decade responsible for Intel server platform, mid-voltage low current buck converter, and modules support.

Matthew Murdock and Nancy Zhang also provides application support and system design for customers to understand their overall product ecosystem and how best to use mid-voltage buck converters.

重要なお知らせと免責事項

TIは、技術データと信頼性データ(データシートを含みます)、設計リソース(リファレンス・デザインを含みます)、アプリケーションや設計に関する各種アドバイス、Webツール、安全性情報、その他のリソースを、欠陥が存在する可能性のある「現状のまま」提供しており、商品性および特定目的に対する適合性の默示保証、第三者の知的財産権の非侵害保証を含むいかなる保証も、明示的または默示的にかかわらず拒否します。

これらのリソースは、TI製品を使用する設計の経験を積んだ開発者への提供を意図したもので、(1)お客様のアプリケーションに適したTI製品の選定、(2)お客様のアプリケーションの設計、検証、試験、(3)お客様のアプリケーションに該当する各種規格や、その他のあらゆる安全性、セキュリティ、規制、または他の要件への確実な適合に関する責任を、お客様のみが単独で負うものとします。

上記の各種リソースは、予告なく変更される可能性があります。これらのリソースは、リソースで説明されているTI製品を使用するアプリケーションの開発の目的でのみ、TIはその使用をお客様に許諾します。これらのリソースに関して、他の目的で複製することや掲載することは禁止されています。TIや第三者の知的財産権のライセンスが付与されている訳ではありません。お客様は、これらのリソースを自身で使用した結果発生するあらゆる申し立て、損害、費用、損失、責任について、TIおよびその代理人を完全に補償するものとし、TIは一切の責任を拒否します。

TIの製品は、[TIの販売条件](#)、またはti.com やかかる TI 製品の関連資料などのいずれかを通じて提供する適用可能な条項の下で提供されています。TIがこれらのリソースを提供することは、適用される TI の保証または他の保証の放棄の拡大や変更を意味するものではありません。

お客様がいかなる追加条項または代替条項を提案した場合でも、TIはそれらに異議を唱え、拒否します。

郵送先住所 : Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2022, Texas Instruments Incorporated