

# Decompensated Amplifier Stabilization Circuit



## Design Goals


Input	Output	Supply		
		V <sub>cc</sub>	V <sub>ee</sub>	V <sub>ref</sub>
2 V <sub>pp</sub> , 500 kHz Square wave	Gain = 1 V/V	5 V	0 V	2.5 V

## Design Description


A [decompensated amplifier](#) is defined as an amplifier that is not inherently stable below a minimum specified gain, but offers a higher gain bandwidth product (GBWP) and sometimes lower noise versus its unity-gain stable counterpart (see [OPA858](#) versus [OPA859](#)). This circuit document presents three different external compensation methods for making these amplifiers unity-gain stable. Each circuit increases low gain stability at the expense of bandwidth. The first two circuits modify the amount-of-feedback ( $\beta$ ) to increase the noise-gain ( $1/\beta$ ). The third circuit uses the output impedance of the amplifier in conjunction with an output load to attenuate the effective open-loop gain ( $A_{OL}$ ).

These examples stabilize the [OPA607](#), a  $\geq 6$  V/V decompensated amplifier, in a unity-gain difference amplifier circuit.

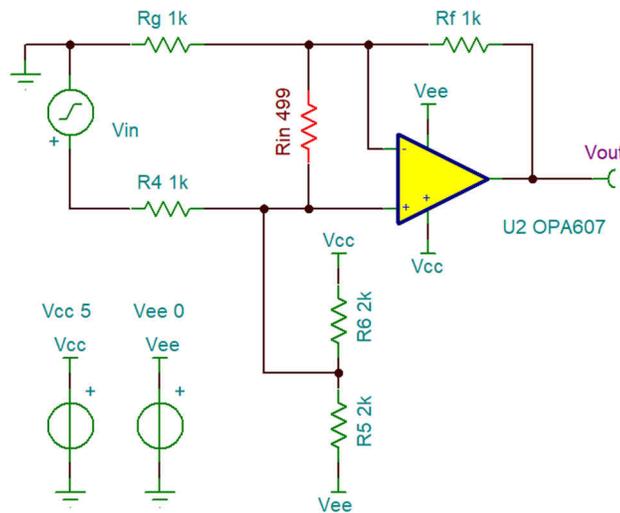
### Compensation Circuit 1: Differential Input Resistor ( $R_{IN}$ )



Circuit 1 Schematic

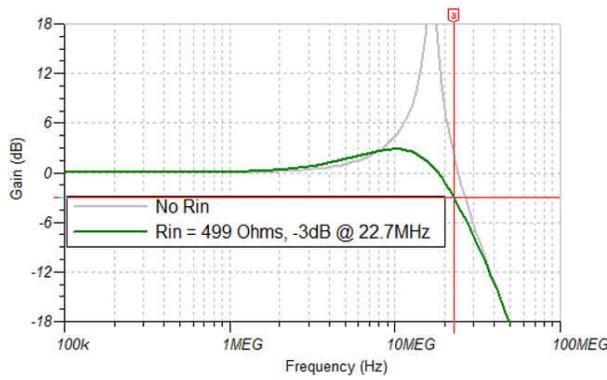

Frequency Response

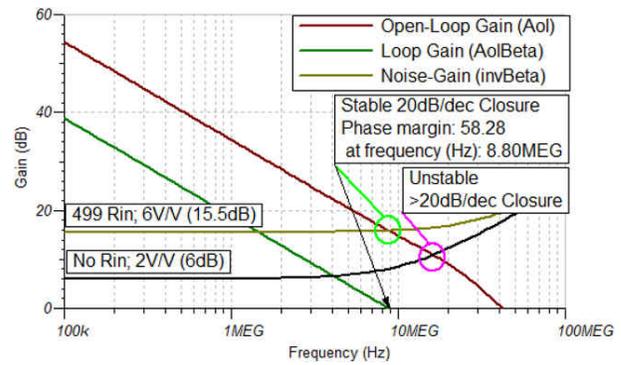

Noise-Gain (Amount of Feedback) Stability Analysis

## Design Notes

Add a resistor ( $R_{IN}$ ) between the two inputs that is small enough to decrease the amount-of-feedback ( $\beta$ ) to  $\leq 1/6$ , and increase the noise-gain ( $1/\beta$ ) to  $\geq 6$ .  $R_{IN}$  does not affect the signal gain because of the virtual short between the two inputs. This method increases the noise gain of the amplifier uniformly across all frequencies, but sacrifices the least bandwidth.

## Design Steps

In this difference amplifier circuit example,  $\Delta V(R_{IN})$  is the voltage across resistor  $R_{IN}$  in the [circuit 1 schematic](#), and  $\Delta V(OUT)$  is the voltage at  $V_{out}$ .  $\beta$  is the ratio  $\Delta V(R_{IN}) / \Delta V(OUT)$  that is divided across the feedback. This ratio can be factored into:

$$\beta = \frac{\Delta V(R_{IN})}{\Delta V(OUT)} = \frac{\Delta V(IN-)}{\Delta V(OUT)} \times \frac{\Delta V(R_{IN})}{\Delta V(IN-)}$$

First, the amount of  $\Delta V(OUT)$  fed back to  $\Delta V(IN-)$  across the feedback resistor  $R_F$  is:

$$\frac{\Delta V(IN-)}{\Delta V(OUT)} = \frac{Z_G}{Z_G + R_F}$$

$Z_G$  represents the resistance out of  $IN-$ . To calculate  $Z_G$ , add  $R_{IN}$  to the resistance out of  $IN+$ , which is the parallel combination of  $R_4 \parallel R_5 \parallel R_6$ . The result adds in parallel with the gain resistor  $R_G$  at  $IN-$  to form  $Z_G$ .

$$Z_G = (R_{IN} + R_4 \parallel R_5 \parallel R_6) \parallel R_G$$

Second, because of the series resistance out of  $IN+$ , the voltage  $\Delta V(R_{IN})$  is only a fraction of  $\Delta V(IN-)$ .

$$\frac{\Delta V(R_{IN})}{\Delta V(IN-)} = \frac{R_{IN}}{R_{IN} + R_4 \parallel R_5 \parallel R_6}$$

When  $R_{IN} = \infty$ ,  $\beta = 1/2$  in this example circuit, where  $R_4 \parallel R_5 \parallel R_6 = 500 \Omega$ ,  $R_G = 1 \text{ k}\Omega$ , and  $R_F = 1 \text{ k}\Omega$ . To stabilize the OPA607, set  $\beta = 1/6$  and solve for  $R_{IN}$ . This can also be solved with simulation, as shown in the [noise-gain stability analysis](#) image.  $R_{IN} = 500 \Omega$  raises the noise-gain up from 2 V/V to 6 V/V. A smaller  $R_{IN}$  further increases  $1/\beta$ .


$$\frac{\Delta V(IN-)}{\Delta V(OUT)} = \frac{(R_{IN} + 500 \Omega) \parallel 1 \text{ k}\Omega}{(R_{IN} + 500 \Omega) \parallel 1 \text{ k}\Omega + 1 \text{ k}\Omega} = \frac{1}{3}$$

$$\frac{\Delta V(R_{IN})}{\Delta V(IN-)} = \frac{R_{IN}}{R_{IN} + 500} = \frac{1}{2}$$


$$\beta = \frac{\Delta V(IN-)}{\Delta V(OUT)} \times \frac{\Delta V(R_{IN})}{\Delta V(IN-)} = \frac{1}{3} \times \frac{1}{2} = \frac{1}{6}$$
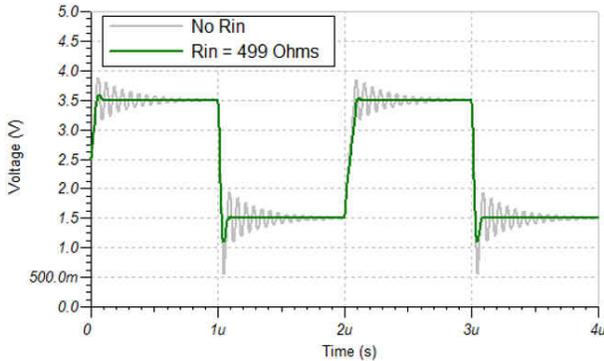
## Design Results

The silver peaking in the [Frequency Response](#) and ringing in the [Square-Wave Response](#) are signs of  $< 45^\circ$  of phase margin and instability. Simulation and measurement of this circuit (see the following images) show that  $R_{IN} = 499 \Omega$  is sufficient for external compensation and stability. The higher undershoot shown is due to the faster falling edge slew rate of the OPA607.




500 kHz, 2 Vpp Square-Wave Response

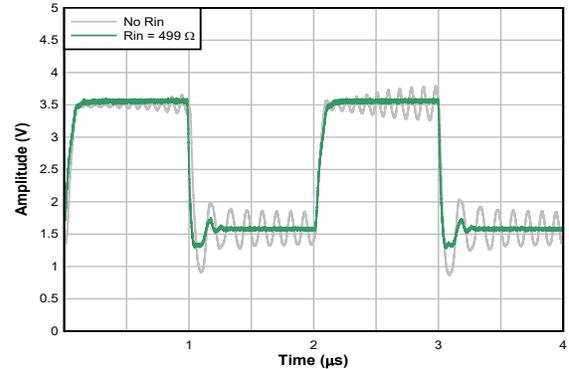


Circuit 1 Measurement

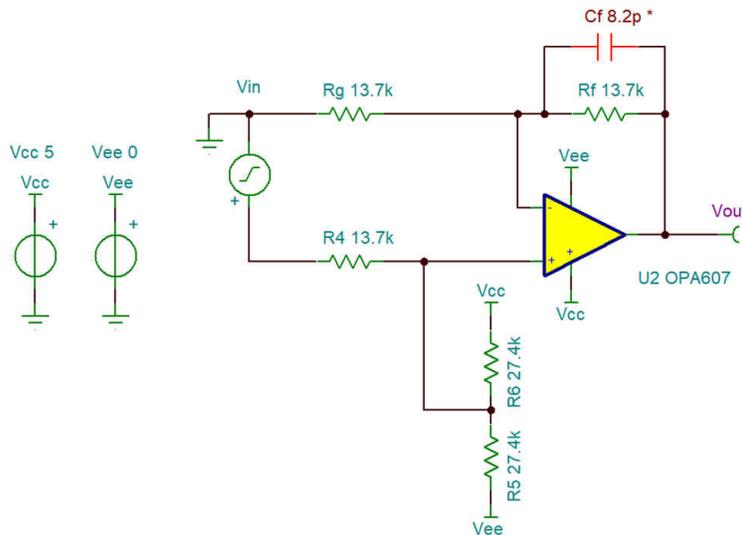
## Compensation Circuit 2: Feedback Capacitor ( $C_F$ )



Circuit 2 Schematic

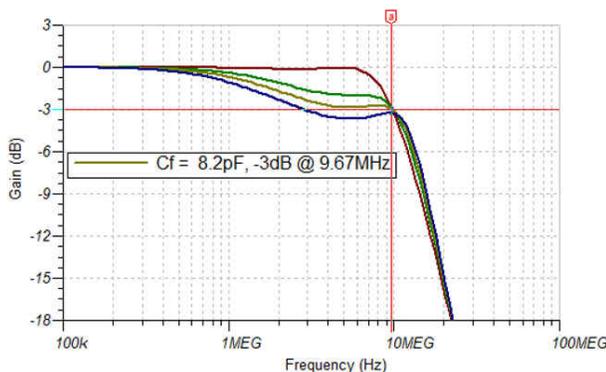

Frequency Response

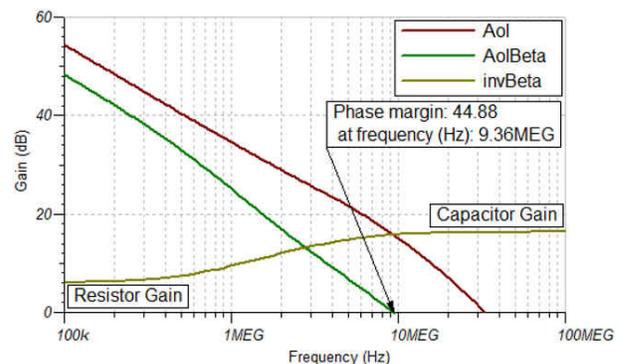

Noise-Gain (Amount of Feedback) Stability Analysis

## Design Notes

Add a feedback capacitor ( $C_F$ ) which creates a high-frequency gain  $\geq 6$  V/V in conjunction with the amplifier input capacitance, but use  $R_F / R_G$  to set a lower signal gain at low frequency and DC. Ensure that the high-frequency noise-gain both is  $\geq 6$  V/V and is achieved within the gain-bandwidth of the amplifier. That is, in the [noise-gain stability analysis](#) image, the maroon  $A_{OL}$  curve must intersect the olive  $1/\beta$  (invBeta) curve where both the  $A_{OL}$  curve is  $-20$  dB/decade and the  $1/\beta$  curve is flat versus frequency.

## Design Steps

The high-frequency gain is set by a capacitor divider, formed between  $C_F$  and the three parasitic input capacitances of the OPA607:  $C_{IN-} = 5.5$  pF;  $C_{IN+} = 5.5$  pF; and  $C_{INDIFF} = 11.5$  pF.  $\beta$  is calculated with the same factors discussed in [Circuit 1](#), but using these internal capacitors instead of external resistors.

$$\beta = \frac{\Delta V(C_{INDIFF})}{\Delta V(OUT)} = \frac{\Delta V(IN-)}{\Delta V(OUT)} \times \frac{\Delta V(C_{INDIFF})}{\Delta V(IN-)}$$

In this noise-gain stability analysis,  $C_F = 8.2$  pF raises the high-frequency capacitor gain to 6.57 V/V. A smaller feedback capacitor further decreases  $\beta$  and increases the high-frequency gain.

$$\frac{\Delta V(IN-)}{\Delta V(OUT)} = \frac{(1/C_{INDIFF} + 1/C_{IN+}) \parallel 1/C_{IN-}}{(1/C_{INDIFF} + 1/C_{IN+}) \parallel 1/C_{IN-} + 1/C_F} = \frac{(1/11.5 \text{ pF} + 1/5.5 \text{ pF}) \parallel 1/5.5 \text{ pF}}{(1/11.5 \text{ pF} + 1/11.5 \text{ pF}) \parallel 1/5.5 \text{ pF} + 1/8.2 \text{ pF}} = 0.47$$


$$\frac{\Delta V(C_{INDIFF})}{\Delta V(IN-)} = \frac{1/C_{INDIFF}}{1/C_{INDIFF} + 1/C_{IN+}} = \frac{1/11.5 \text{ pF}}{1/11.5 \text{ pF} + 1/5.5 \text{ pF}} = 0.32$$

$$\beta = \frac{\Delta V(IN-)}{\Delta V(OUT)} \times \frac{\Delta V(C_{INDIFF})}{\Delta V(IN-)} = 0.47 \times 0.32 = 0.152 = \frac{1}{6.57}$$


This stable  $\beta$  suggests that the amplifier now has a signal gain  $\geq 6$  V/V at high frequency. But careful selection of both  $C_F$  and  $R_F$  values can create both a stable amount of feedback and also a low-pass filter of the signal gain, to prevent the increasing  $1/\beta$  over frequency from creating issues like overshoot. It is easier to achieve both of these conditions when  $R_F$  is  $> 10$  k $\Omega$ .
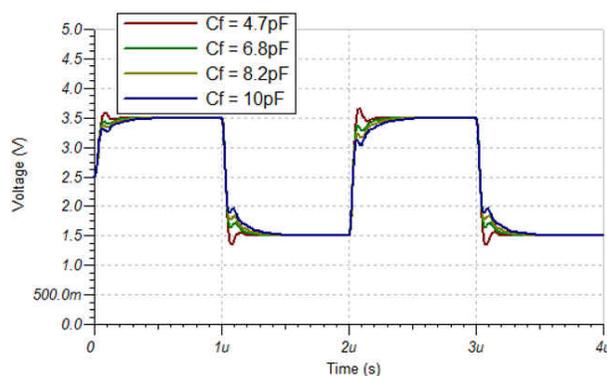
## Design Results

Measurement of this circuit shows that  $C_F = 8.2$  pF and  $R_F = 13.7$  k $\Omega$  were sufficient to both maintain a stable noise-gain = 6.57 V/V and filter overshoot.




**500 kHz, 2 Vpp Square-Wave Response**

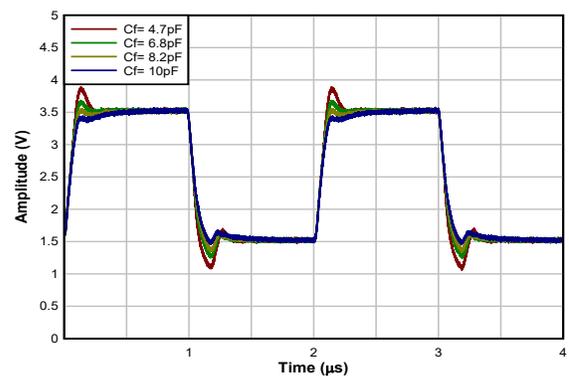


**Circuit 2 Measurement**

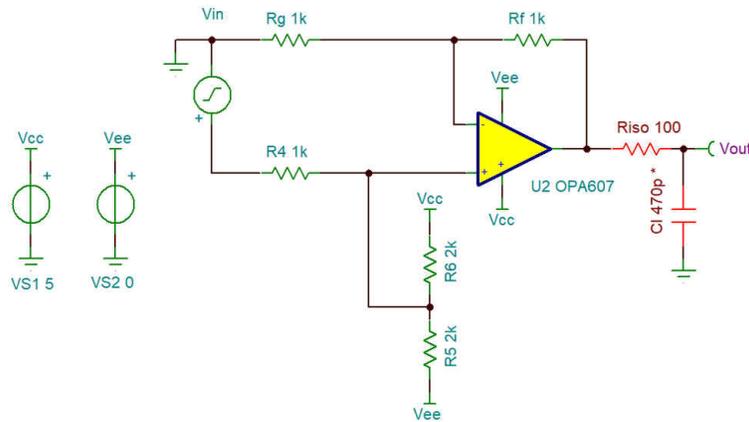
## Compensation Circuit 3: High-Frequency Load ( $R_{ISO}$ )



**Circuit 3 Schematic**

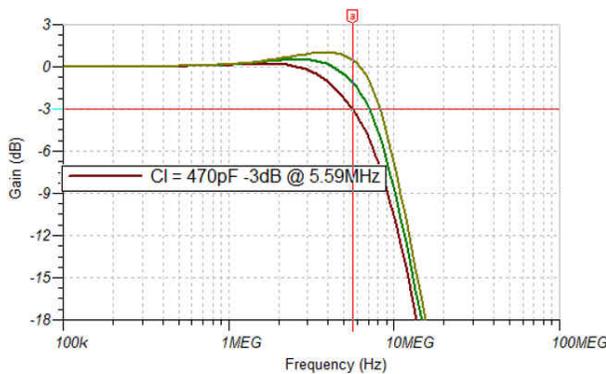


**Frequency Response**

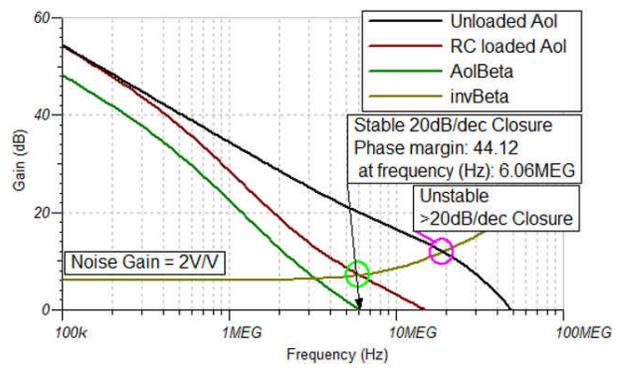

**Noise-Gain (Amount of Feedback) Stability Analysis**
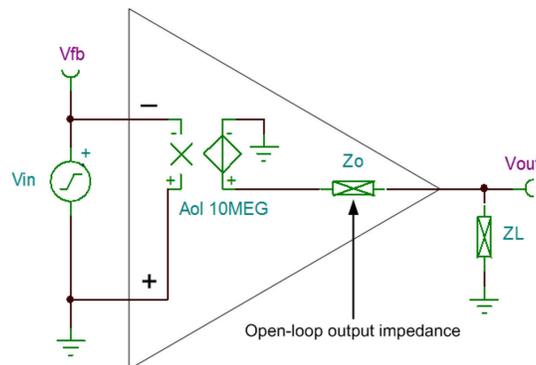
### Design Notes

Add a low-resistance load ( $R_{ISO}$ ) for high frequencies. The load forms a resistor divider with the amplifier open-loop output impedance (see [the following image](#)), and can attenuate the effective open-loop gain ( $A_{OL}$ ) of the amplifier to a compensated level. Since the OPA607 has 500  $\Omega$  of series output impedance, a 100- $\Omega$  load resistor attenuates the  $A_{OL}$  to 1/6 (-15.5 dB).



Alone, a small resistor load burns a lot of power. But for stability purposes, attenuating the  $A_{OL}$  is like increasing the noise-gain, and only a high-frequency load is required, such as an output filter. In the [noise-gain stability analysis](#) circuit, both the black unloaded  $A_{OL}$  and the maroon  $A_{OL}$  with an RC filter load are graphed. The olive 2 V/V (6 dB) noise-gain intersects with the maroon loaded  $A_{OL}$  at a more stable, 20-dB/decade rate of closure. This compensation technique is helpful for using the OPA607 as a drop-in replacement for unity-gain stable amplifiers where an output filter is present.

## Design Steps

The  $R_{ISO} + C_L$  filter bandwidth must be lower than the attenuated bandwidth of the loaded amplifier, because the frequency range above the filter bandwidth and below the loaded amplifier bandwidth is where the compensation is created. Otherwise, the load further decompensates the amplifier without creating a usable lower gain. In the stability analysis for this circuit, the  $-40$  dB/decade slope in the maroon loaded  $A_{OL}$  shows that higher gains will be less stable than the compensated low gain when a filter load attenuates the  $A_{OL}$ .


In this example circuit,  $GBWP = 50$  MHz and  $\beta = 1/2$ , but attenuation =  $1/6$ . Therefore, the attenuated amplifier bandwidth is  $50/12 = 4.2$  MHz. For  $R_{ISO} = 100 \Omega$ ,  $C_L$  should be  $> 380$  pF.

$$GBWP \times \beta \times \text{Attenuation} > \frac{1}{2\pi \times R_{ISO} \times C_L}$$


$$C_L > \frac{(2 \times 6)}{2\pi \times 100 \Omega \times 50 \text{ MHz}} = 380 \text{ pF}$$
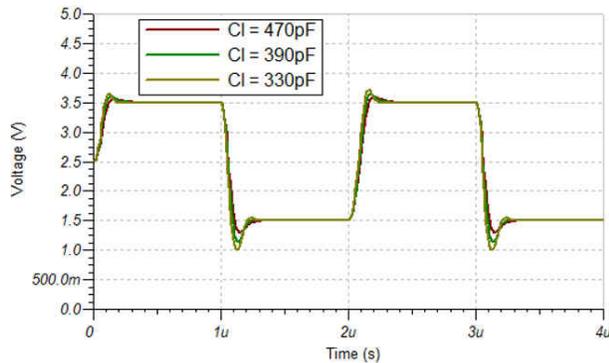
## Design Results

Measurement of this circuit shows that a  $R_{ISO} = 100 \Omega$ , 470-pF load was sufficient to make the OPA607 stable in a difference configuration with a gain of 1 V/V.



**500 kHz, 2 Vpp Square-Wave Response**

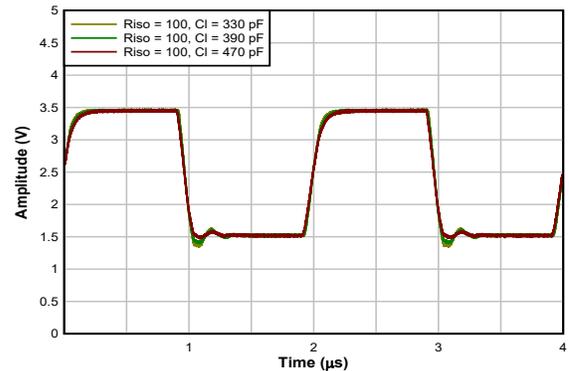

**Circuit 3 Measurement**

## Design Featured Device

OPA607	
Supply Range ( $V_{SS}$ )	2.2 V to 5.5 V
Gain Bandwidth Product, $G = 20$ V/V	50 MHz
Decompensated Gain ( $A_{V/V}$ )	$\geq 6$ V/V
Input Capacitance ( $C_{IN}$ )	Differential: 11.5 pF
	Common-mode: 5.5 pF
Input Range ( $V_{CMVR}$ )	(V-) to (V+) – 1.1 V
Output Range ( $V_{out}$ )	Rail to Rail
Overdrive Recovery Time ( $t_{OR}$ )	300 ns
Voltage Noise ( $e_N$ )	3.8 nV/ $\sqrt{\text{Hz}}$
Offset Voltage ( $V_{OS}$ )	$\pm 120$ $\mu$ V
Quiescent Current ( $I_q$ )	900 $\mu$ A
Input Bias Current ( $I_b$ )	$\pm 3$ pA
Slew Rate	24 V/ $\mu$ s
Open-loop Output Impedance ( $Z_o$ )	500 $\Omega$
<a href="#">OPA607</a>	

## Design Alternative Devices

Decompensated High-Speed Amplifiers		
Device Name	Gain Bandwidth	Decompensated Gain
<a href="#">LMV793</a> , <a href="#">LMV794</a> <a href="#">LMP7717</a> , <a href="#">LMP7718</a>	88 MHz	10 V/V
<a href="#">SM73302</a>	88 MHz	10 V/V
<a href="#">OPA838</a>	300 MHz	6 V/V
<a href="#">LMH6629</a>	900 MHz	10 V/V
<a href="#">LMH6626</a>	1.5 GHz	10 V/V
<a href="#">OPA818</a>	2.7 GHz	7 V/V
<a href="#">OPA858</a>	5.5 GHz	7 V/V

## Design References

- See the [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.
- Texas Instruments, [AN-1604 Decompensated Operational Amplifiers](#) application note
- For hardware evaluation, see [TIDA-060019](#)

## Additional Resources

- Texas Instruments, [OPAx607 50-MHz, Low-Power, Rail-to-Rail Output CMOS Operational Amplifier for Cost Sensitive Systems](#) data sheet

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated