

J.J. Guan

Systems Engineering and Marketing


Design Goals

Parameter	Value
Supply Voltage (V_{supply})	5 V
Input Voltage (V_{in})	0 V to 4.5 V
Output Current (I_{out})	0 mA to 90 mA
Output Voltage (V_{out})	3.5 V
Output Current Error at 90 mA	Circuit 1: < 0.106% Circuit 2: < 0.112%
Total Ionizing Dose (TID)	30-krad (Si)
Single Event Latch-up (SEL) Immunity	43 MeV*cm ² /mg

Design Description


This design generates programmable 90-mA current source to ground. This document shows simulations from two different current sourcing circuits. The simulation results highlight the positives and negatives of each circuit.

 [Circuit 1 Schematic](#) shows the first current-sourcing circuit (circuit 1) schematic. In this circuit, each OPA4H199-SEP op amp sources up to 30 mA to support a total of 90 mA current at the load.



Circuit 1 Schematic

 Circuit 2 Schematic shows the second current-sourcing circuit (circuit 2) schematic. In this circuit, the OPA4H199-SEP op amp biases the gate of the PMOS to source 90 mA to the load.



Circuit 2 Schematic

Design Note

In all simulations, both circuits assume an accurate voltage input for controlling the output current. Both circuits have similar accuracy, but circuit 2 needs calibration to eliminate error causing by the low dropout (LDO).

Circuit 1 vs Circuit 2

Parameter	Circuit 1	Circuit 2
Number of ICs	1	3
Power efficiency at 90 mA	69.7%	71%
Max error at 90 mA	0.106%	0.144%
Current sourcing range (mA)	0 to 90	0 to any (depends on PMOS and R1)
3-dB bandwidth (Hz)	447	11.9 kΩ

Applications

- Radio frequency (RF) front-end biasing
- Temperature sensing
- Battery charging

Design Steps

1. Op-amp selection

The OPA4H014 and OPA4H199-SEP devices are considered for use to generate the current source, and their characteristics are put together in the [Op-Amp Selection](#) table for comparison.

Op-Amp Selection

Device	# Ch	Vs MIN (V)	Vs MAX (V)	Vos MAX at 25°C (μV)	Drift TYP (μV/C)	MIN Vcm (V)	MAX Vcm (V)	I _Q typ (mA)	Vn (nV/√Hz)	IBias (TYP) (nA)
OPA4H199-SEP	4	2.7	40	895	0.30	V ⁻ - 0.2 V	V ⁺ + 3.2 V	0.56	10.8	0.01
OPA4H014-SEP	4	4.5	18	120	0.35	V ⁻ - 0.1 V	V ⁺ - 3.5 V	1.8	5.1	0.0005

The OPA4H014-SEP is more precise because this device has a smaller offset voltage (V_{os}) and drift. However, the upper limit of the common-mode voltage (V_{cm}) is 3.5 V below the positive supply voltage (V⁺), which is 5 V - 3.5 V = 1.5 V, in this case. The OPA4H199-SEP, conversely, allows rail-to-rail V_{cm}, and is selected for circuit 2.

In addition, to configure circuit 1, the op amp must source a large current. The OPA4H014-SEP can source only up to 36 mA when the output is shorted while the OPA4H199-SEP can source up to 75 mA. Hence, OPA4H014-SEP is selected for both circuits.

2. LDO selection

Note

Use of LDO in circuit 2 introduces inaccuracy to the system. To eliminate this inaccuracy, a current-sinking circuit instead of sourcing circuit can be configured.

If the 5-V power supply accuracy is not provided, create a reference voltage for circuit 2. Since the V_{supply} of the circuit is only 5 V, pick an LDO linear regulator with small dropout voltage (V_{DO}). The LDO selected is the TPS73801-SEP. This LDO has a very small dropout voltage (V_{DO}) of 0.24 V, allowing a maximum reference voltage (V_{ref}) up to 4.76 V with 3% accuracy.

3. Resistor selection for circuit 1 and circuit 2

In circuit 1, values of R3, R6, and R12 determine the output current. As an example, consider the left op-amp circuit. This circuit generates a current of V_{ref} / R6, which is 30 mA when V_{ref} is 4.5 V. Since all three op-amp circuits are equivalent, the total output current generated adds up to 90 mA.

In circuit 2, R1 and the voltage across R1 determines the output sourcing current, which is 90 mA when the output current is 0.4824 V. R2 and R5 in the circuit remap the 0-V to 4.5-V input voltage to around 4 V to 4.5 V, such that output current can swing from 0 mA to 90 mA.

4. PMOS selection

A MOSFET is used only in circuit 2. The op-amp output is rail to rail and the output ranges from 0 V to 5 V. Hence, the absolute value of the PMOS threshold voltage |V_{th}| must not be greater than 5 V for the op amp to bias the PMOS gate. The Zero Gate Voltage Drain Current (I_{DSS}) of the PMOS defines the leakage current when the gate voltage is equal to V_{bus}. I_{DSS} sets the minimum output current.

IRHNJ597230, a 100-krad PMOS is used in circuit 2. As shown in table 4, this IRHNJ597230 has a |V_{th}| that ranges from 2 - 4 V and a small |I_{DSS}| of 10 - 25 μA.


IRHNJ597230 Characteristics

IRHNJ597230	
D-S Breakdown (V)	-200
Vgs (V)	-2 to -4
Zero Gate Voltage Drain Current (µA)	-10 to -25
Input Capacitance (pF)	1344
Mounting Type	SMT
Size (mm)	10.28 × 7.64

Circuit 1 Simulation Results

- Error Analysis**

 [Circuit 1 Simulation Result](#) shows the circuit 1 simulation result. After calibration, the output error is smaller than 52 µA since the input voltage swings from 0 V to 4.5 V. This simulation does not include error caused by the temperature drift of the op-amp offset voltage and resistor tolerance.



Circuit 1 Simulation Result

The following equations are provided to predict a more accurate percent error.

Note

Assume all resistors have 0.1% tolerance. Op-amp offset voltage (V_{os}) is 125 µV and offset drift (V_{os_drift}) is 0.3 µV / °C found in the OPA4H199-SEP data sheet.

$$R3 \text{ Error } (e_{R3}) = 0.1\% \div 3 = 0.033\%$$

$$R6 \text{ Error } (e_{R6}) = R12 \text{ Error } (e_{R12}) = e_{R3} = 0.033\%$$

$$\text{buffer offset Error } (e_{V_{os1}}) = [V_{OS} + V_{OS_{drift}} \times (\text{temp} - 25)] \div V_{in} \times 100\%$$


$$= [125 \mu\text{V} + 0.3 \frac{\mu\text{V}}{^\circ\text{C}} \times (\text{temp} - 25)^\circ\text{C}] \div V_{in} \times 100\%$$

$$\begin{aligned}
 \text{Current Source offset Error } (e_{V_{OS2}}) &= [V_{OS} + V_{OS_{\text{drift}}} \times (\text{temp} - 25)] \div V_{in} \div 3 \times 100\% \\
 &= [125 \mu\text{V} + 0.3 \frac{\mu\text{V}}{^\circ\text{C}} \times (\text{temp} - 25)^\circ\text{C}] \div V_{in} \div 3 \times 100\%
 \end{aligned}$$

$$\text{Root Sum Square Error (RSS)} = \sqrt{e_{V_{OS1}}^2 + e_{V_{OS2}}^2 \times 3 + e_{R3}^2 + e_{R6}^2 + e_{R12}^2}$$

$$\text{Extreme Value Analysis (EVA)} = e_{V_{OS1}} + e_{V_{OS2}} \times 3 + e_{R3} + e_{R6} + e_{R12}$$

 Circuit 1 error analysis is done in MATLAB and shown in [Circuit 1 Error Analysis](#). The first plot shows both RSS and EVA with sourcing current sweeping from 2 mA to 90 mA at 25°C. The second plot shows RSS and EVA with 90-mA sourcing current and temperature sweeping from -55°C to 125°C.




Circuit 1 Error Analysis

As a conclusion from the two plots in the previous images, accuracy is proportional to the amount of current sourced. Temperature has a very minor effect on accuracy since the offset drift of the op amp is only 0.3 μV / °C. From the results in the images, when sourcing current above 20 mA, the percent error is expected to be smaller than 0.06%.

- **Power Consumption**

 
[Circuit 1 Power Efficiency](#) shows the circuit 1 power efficiency simulation with input voltage sweeps from 0 to 4.5 V. When the output current is 90 mA, the power consumption reaches the maximum of 465 mW with a power efficiency of 69.7%. When the sourcing current is shut down, the system power consumption is 11.5 mW.



Circuit 1 Power Efficiency

• **Stability Analysis**

 
Circuit 1 Stability Analysis shows the circuit 1 stability analysis simulation result. A small signal transient step response is applied at the op-amp input and percent overshoots are measured at Vo1 and Vo2. Vo1 has 3.89% overshoot, which is equivalent to a 66° phase margin. Vo2 does not have overshoot. Both Vo1 and Vo2 indicate the stability of the system.



Circuit 1 Stability Analysis

• **Bandwidth**

 Circuit 1 Bandwidth shows the gain of circuit 1, where Gain = load current / input voltage. The 1% full-power bandwidth and the 3-dB bandwidth are 214 Hz and 447 Hz.




Circuit 1 Bandwidth

Circuit 2 Simulation Results

Error Analysis

 [Circuit 2 Simulation Result](#) shows the circuit 2 simulation result. The output current error is smaller than 6.4 μA as input voltage swings from 0 V to 4.5 V. However, this simulation does not include error caused by temperature drift of the op-amp offset voltage and resistor tolerance.





Circuit 2 Simulation Result

To predict a more accurate percentage error, the worst-case analyses are simulated on TINA spice and shown in [Circuit 2 Worst-Case Analysis \(Minimum I_{OUT}\)](#) and [Circuit 2 Worst Case Analysis \(Maximum I_{OUT}\)](#).

Note

 
 
Assume all resistors have 0.1% tolerance. The maximum op-amp offset voltage (V_{os}) is 830 μV found in the OPA4H199-SEP data sheet. Calibration is done by applying offset to the output result to obtain a 0 error at 45-mA current output.



Circuit 2 Worst-Case Analysis (Minimum I_{OUT})

Circuit 2 Worst-Case Analysis (Minimum I_{OUT}) shows the lower end of the maximum current output error. Without calibration, the output current drops down to 86.7 mA at worst case when the output current is supposed to be 90 mA. After calibration, the output error swings from $-115 \mu\text{A}$ to $124 \mu\text{A}$. The percent error is 0.144% when sourcing 90 mA to the load, and increases as decreasing sourcing current.

  This Schematic simulate the worst case resulting in max output current (Iout)




Circuit 2 Worst-Case Analysis (Maximum I_{OUT})

Circuit 2 Worst-Case Analysis (Maximum I_{OUT}) shows the upper end of the maximum current output error. Without calibration, the output current raises up to 92.59 mA at the worst case when the output current is supposed to be 90 mA. After calibration, the output error swings from $-124 \mu\text{A}$ to $124 \mu\text{A}$. The percentage error is 0.134% when sourcing 90 mA to the load, and increases as the sourcing current decreases.

• **Power Consumption**

 
Circuit 2 Power Efficiency shows the circuit 2 power efficiency simulation with input voltage sweeps from 0 V to 4.5 V. When the output current is 90 mA, the power consumption reaches the maximum of 458 mW with a power efficiency of 71%. When the sourcing current is shut down, the system power consumption is 10.1 mW.



Circuit 2 Power Efficiency

• **Stability Analysis**


For stability purposes, a 6.8- μF capacitor is placed between the PMOS gate and source. [Circuit 2 Stability Analysis](#) shows the stability simulation result done in TINA spice. A small signal transient step response is applied at the op-amp input and percent overshoot is measured at V_o , which is the op-amp output pin as shown in the circuit 2 schematic. V_o has 7% overshoot, which is equivalent to a 62.1° phase margin, indicating the system is stable.

 

Circuit 2 Stability Analysis

• **Bandwidth**

 [Circuit 2 Bandwidth](#) is simulated with a 6.8- μF capacitor (C3). This simulation shows the gain of the circuit 2, where Gain = load current / input voltage. The 1% full power bandwidth and the 3-dB bandwidth are 2.26 kHz and 11.9 kHz.



Circuit 2 Bandwidth

Design References

1. IR HiRel, "[RADIATION HARDENED POWER MOSFET SURFACE MOUNT \(SMD-0.5\)](#)," IRHNJ597230 data sheet, Dec 2018.
2. Texas Instruments, [TPS73801-SEP 1-A Low-Noise Fast-Transient-Response Low-Dropout Regulator in Space Enhanced Plastic](#) data sheet

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated