

Do's and Don'ts for TXB and TXS Voltage Level-Shifters with Edge Rate Accelerators



Michael Ikwuyum, Ajith Narayansetty, Sahil Garg

ABSTRACT

Auto Directional level shifter families are designed with weaker outputs than devices from other level shifting families, to be easily overdriven by the hosts. This makes Auto Direction devices a requirement for bidirectional interfaces such as I²C, MDIO, Quad-SPI, and so on.

The TXS and TXB Auto Directional level shifter families as shown in [Voltage Translators and Level Shifters](#) are designed with edge rate accelerators (commonly known as one-shots). The one-shots are designed for a set duration of pulse width for optimal signal integrity, impacted by RC components. Therefore, intentional and careful considerations should be made when used with additional external components as majority of one-shot concerns are due to improper use of the devices, false triggering of the one-shots and poor layout design.

Table of Contents

1 Introduction	2
2 The One-shot's Designed Duration	3
2.1 Design Considerations.....	3
2.2 Recommended Parts.....	3
3 Design Considerations for Slow Rise and Fall Times	4
3.1 Design Considerations.....	4
3.2 Recommended Parts.....	4
4 Consider the Impact of External RC Components on Rise and Fall Times	5
4.1 Design Considerations.....	5
4.2 Recommended Parts.....	5
5 Consider the Lumped Capacitance	6
5.1 Design Considerations.....	6
5.2 Recommended Parts.....	6
6 Consider the Effects of Temperature on the Output Impedance	7
Design Considerations.....	7
7 Summary	8
8 References	9

List of Figures

Figure 2-1. Example of the one-shot timing out before reaching the designed duration.....	3
Figure 3-1. Example of Slow Rise and Fall Times, 2.4 μ S/V.....	4
Figure 4-1. Example of Rise and Fall Times Increasing with Lumped Capacitance.....	5
Figure 5-1. Example Voltage Translation showing Lumped Capacitance with a One-Shot Device.....	6
Figure 6-1. Example of Outputs at Varying Temperature.....	7

List of Tables

Table 1-1. Recommended Translator by Interface.....	2
Table 2-1. Recommended Parts.....	3
Table 3-1. Recommended Parts.....	4
Table 4-1. Recommended Parts.....	5
Table 5-1. Recommended Parts.....	6

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

Texas Instruments' portfolio of level shifter devices contains many different types of level translation functions that collectively is able to address almost any application requirement. TI's level translation portfolio includes Auto Directional, Direction Controlled, Fixed Direction, and Application Specific Level Translators in Industrial and Automotive ratings. For a list of recommended level translation devices for common interface types please see [Table 1-1](#). For more information on all of TI's level translation designs please visit TI's level translation landing page at www.ti.com/translation.

Table 1-1. Recommended Translator by Interface

Interface	Translation Level	
	Up to 3.6 V	Up to 5.5 V
FET Replacement	2N7001T	SN74LXC1T45 / TXU0101
1 Bit GPIO/Clock Signal	SN74AXC1T45	SN74LXC1T45 / TXU0101
2 Bit GPIO	SN74AXC2T245	SN74LXC2T45 / TXU0102
2-Pin JTAG/UART	SN74AXC2T45	SN74LXC2T45 / TXU0202
I2C/MDIO/SMBus	TXS0102 / LSF0102	TXS0102 / LSF0102
IC-USB	SN74AVC2T872 / TXS0202	NA
4 Bit GPIO	SN74AXC4T245	TXB0104 / TXU0104
UART	SN74AXC4T245	TXU0204
SPI	SN74AXC4T774	TXU0304
JTAG	SN74AXC4T774	TXU0304
I2S/PCM	SN74AXC4T774 / TXB0104	TXB0104 / TXU0204
Quad-SPI	TXB0106	TXB0106
SDIO/SD/MMC	TXS0206 / TWL1200	NA
8 Bit GPIO/RGMII	SN74AXC8T245	SN74LXC8T245

2 The One-shot's Designed Duration

 


Figure 2-1. Example of the one-shot timing out before reaching the designed duration.

2.1 Design Considerations

- [Figure 2-1](#) shows the one-shot expiring at about 200 pF.
- Do not expire or time-out the one-shot prior to reaching the designed duration.
- Consider short enough traces for round-trip delay reflections within the one-shot duration of 10-30 ns.
- Avoid excessive loading (similar to the datasheets) as the longer the trace length, the more the lumped capacitive loading
- Need additional assistance? Ask our engineers a question on the [TI E2E™ Logic Support Forum](#)

2.2 Recommended Parts

Applications with higher capacitive loading from longer trace lengths, connectors etc, typically do not require Auto Direction. Such applications (SPI for example) require devices with stronger output buffers. See [Table 2-1](#) for more suitable recommendations.

Table 2-1. Recommended Parts

Part Number	AEC-Q100	Voltage Translation Range	Features
TXU0304		1.1 V–5.5 V	Schmitt-trigger inputs Integrated pull-down resistors V_{CC} Isolation and V_{CC} Disconnect, Glitch-free power supply sequencing
TXU0304-Q1	✓		
SN74AXC4T774		0.65 V–3.6 V	Direction controlled Glitch-free power supply sequencing V_{CC} Isolation
SN74AXC4T774-Q1	✓		

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, and other features.

3 Design Considerations for Slow Rise and Fall Times

 


Figure 3-1. Example of Slow Rise and Fall Times, 2.4 $\mu\text{s/V}$

3.1 Design Considerations

- Figure 3-1 shows the one-shot false triggering due to a slow input rise time outside of the data sheet recommendation.
- Do not use slow input rise or fall transition rates.
- As shown, the one-shots can trigger or expire prior to the designed duration for adverse system-level effects.
- Consider using fast enough input edges per the data sheet's input transition rate.
- [Implications of Slow or Floating CMOS Inputs](#)
- Need additional assistance? Ask our engineers a question on the [TI E2E™ Logic Support Forum](#)

3.2 Recommended Parts

See [Table 3-1](#) for applications that may require the flexibility for slower inputs.

Table 3-1. Recommended Parts

Device Family	AEC-Q100	Voltage Translation Range	Features
TXU and LXC	✓	1.1 V–5.5 V	Schmitt-trigger inputs Integrated pull-down resistors
AUP	✓	0.6 V–3.6 V	Input hysteresis allows the input to support slew rates as slow as 200 ns/V, improving switching noise immunity
LSF	✓	0.65 V–5.5 V	No input transition rate requirement.

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, and other features.

4 Consider the Impact of External RC Components on Rise and Fall Times

 


Figure 4-1. Example of Rise and Fall Times Increasing with Lumped Capacitance

4.1 Design Considerations

- Figure 4-1 shows the relationship for rise / fall times being directly proportional to the lumped capacitance.
- Do not exceed the data sheet loading conditions as the rise or fall times will increase, impacting data throughput.
- Consider any tolerances of any additional RC components, similar to the data sheet recommendations.
- Need additional assistance? Ask our engineers a question on the [TI E2E™ Logic Support Forum](#).

4.2 Recommended Parts

The Auto Directional device family with the most flexibility for external resistors per RC components (for applications such as I²C), is the LSF family and then the TXS family. See [Table 4-1](#) for recommendations.

Table 4-1. Recommended Parts

Part Number	AEC-Q100 Qualified	Voltage Translation Range	Features
LSF0102		0.65 V – 5.5 V	Over-voltage tolerant I/O Low R _{ON} for low output voltage levels
LSF0102-Q1	✓		
TXS0102		1.65 V – 5.5 V	Edge-rate acceleration Supports Partial-Power-Down applications Integrated pull-up resistors
TXS0102-Q1	✓		

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, and other features.

5 Consider the Lumped Capacitance

 


Figure 5-1. Example Voltage Translation showing Lumped Capacitance with a One-Shot Device

5.1 Design Considerations

- Unless otherwise noted in the data sheets, ensure <70 pF lumped capacitance for optimal performance per the data sheet's recommended data rates.
- Additional parasitic capacitance is added from trace length and connectors.
- Additional loading impacts signal integrity at faster data rates.
- Need additional assistance? Ask our engineers a question on the [TI E2E™ Logic Support Forum](#)

5.2 Recommended Parts

The Fixed and Direction Control families are most suitable for applications for high data throughput. Consider [Table 5-1](#) for applications with connectors or excessive lumped capacitance such as GPIO, instead of TXB.

Table 5-1. Recommended Parts

Part Number	AEC-Q100	Data Rates	Voltage Translation Range	Features
SN74LXC8T245		Up To 420 Mbps	1.1 V–5.5 V	Schmitt-trigger inputs Dynamic pull-downs on I/O V _{CC} Isolation and V _{CC} Disconnect
SN74LXC8T245-Q1	✓			
TXU0104		Up To 200 Mbps	1.1 V–5.5 V	Schmitt-trigger inputs Integrated pull-down resistors V _{CC} Isolation and V _{CC} Disconnect
TXU0104-Q1	✓			
SN74AXC1T45		Up To 500 Mbps	0.65 V–3.6 V	Direction controlled Glitch-free power supply sequencing V _{CC} Isolation
SN74AXC1T45-Q1	✓			

For more devices, browse through the [online parametric tool](#) where you can choose between the three types of translators.

6 Consider the Effects of Temperature on the Output Impedance

 


Figure 6-1. Example of Outputs at Varying Temperature

Design Considerations

- Minimize reflections / ringing.
- Consider the impact of temperature on the output impedance, as mismatched impedance with PCB traces yield reflections.
- Reflections or ringing can be amplified by the one-shot as false edge triggers.
- Excessive ringing can cause false triggers observed as oscillating outputs.
- Ringing is also caused by capacitance and inductance of long cables or traces and can be amplified by unstable GND or VCC voltages.
- Use bypass capacitors or stable GND to minimize noise.
- Devices with Schmitt – Trigger are most recommended for noisy applications. See [Section 3.2](#) for recommendations.
- Need additional assistance? Ask our engineers a question on the [TI E2E™ Logic Support Forum](#)

7 Summary

- Consider short enough traces for round-trip delay reflections within the one-shot duration of 10-30 ns.
- Consider any tolerances of any additional RC components, similar to the data sheet recommendations.
- Consider utilizing fast enough input edges per the input transition rate while avoiding floating inputs as stated in the data sheets.
- Unless otherwise noted in the data sheets, make sure <70 pF lumped capacitance designed for performance per the data sheet's recommended data rates.
- Avoid timing-out the one-shot duration with additional parasitic capacitance as trace length and connectors yields additional capacitive loading.
- One-shot triggers when they detect rising or falling edges. Reflections and or ringing can cause false triggers. Ringing is also caused by capacitance and inductance of long cables and or traces and can also be amplified by unstable GND or V_{CC} voltages.
- Consider the impact on temperature per the output impedance, as mismatched impedance with PCB traces yield reflections that can be amplified by the one-shot as false edge triggers.

8 References

- Texas Instruments, [Designing With the SN74LVC1G123 Monostable Multivibrator](#), application note.
- Texas Instruments, [A Guide to Voltage Translation With TXS-Type Translators](#), application note.
- Texas Instruments, [A Guide to Voltage Translation With TXB-Type Translators](#), application note.
- Texas Instruments, [Effects of Pullup and Pulldown Resistors on TXS and TXB Devices](#), application note.
- Texas Instruments, [Implications of Slow or Floating CMOS Inputs](#), application note.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated