 



Catch a Digital Pulse



An error condition or other digital input might only occur for a very short time while the processor is busy with other tasks or asleep for power savings. In order to ensure that an error state is correctly identified, a dedicated latch circuit can be used to catch even very brief pulses while using very little power.



Single Positive Pulse Latch

 

Single Negative Pulse Latch

See more about similar use cases in the *Logic Minute* video [Design an Alarm / Tamper Circuit with an S-R Latch](#).

Design Considerations

- Ensure that the error signal is digital; analog signals should be converted using a comparator
- Reset latches on system startup; latch circuits do not have a default value
- [\[FAQ\] What is the default output of a latched device? \(Flip-Flop, latch, register\)](#)
- [\[FAQ\] How does a slow or floating input affect a CMOS device?](#)
- Ask a question on our [Engineer-to-Engineer forum](#)

Recommended Parts

Part Number	AEC-Q100	V _{CC} Range	Features
SN74AUP2G02		0.8 V – 3.6 V	Extremely low power – I _{CC} < 0.9 μA One latch per device (2 × 2-input gates)
SN74AUP2G00			
SN74HCS02-Q1	✓	2 V – 6 V	Schmitt-trigger input architecture Low power – I _{CC} < 2 μA Up to two latches per device (4 × 2-input gates)
SN74HCS02			
SN74HCS00-Q1	✓		
SN74HCS00			

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, and other features.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated